

---

# Ch 8. Working with Finite State Machines


---

# State Minimization / Reduction

## ■ Motivation
 
### □ Odd Parity Checker example

- Two alternative state diagrams
- Identical output behavior on all input strings
- FSMs are equivalent, but require different implementations
- S0, S2 are equivalent states
  - Both output a 0
  - Both transition to S1 on a 1 and self-loop on a 0



# State Minimization / Reduction (cont'd)

## ■ Goal

- Identify and combine equivalent states
  - Equivalent states:
    - same outputs (Mealy: for all input combinations)
    - for all input combinations, transition to same or equivalent states
- Design state diagram without concern for # of states, reduce later
- Implement FSM with fewest possible states
  - Reduce the number of gates and flip-flops needed for implementation

# State Minimization / Reduction (cont'd)

## ■ Example specification

- Name: four-bit sequence (0110 or 1010) detector
- Input:  $X = \{0, 1\}$
- Output:  $Z = \{0, 1\}$
- Behavior:


$$Z = \begin{cases} 1 & \text{if each 4-bit input sequence (no overlap) is 0110 or 1010} \\ 0 & \text{otherwise} \end{cases}$$

## ■ Sample behavior

- $X = 0010\ 0110\ 1100\ 1010\ 0011\ \dots$
- $Z = 0000\ 0001\ 0000\ 0001\ 0000\ \dots$
 
# State Minimization / Reduction (cont'd)

- Initial State Diagram (of a Mealy implementation)
  - There are 16 unique paths through the state diagram, one for each possible 4-bit pattern.
  - 15 states, and 30 transitions.



# State Minimization / Reduction (cont'd)

- Upper bound of #states and #transitions for n-length bit pattern
  - #states =  $\sum_{i=0}^{n-1} 2^i = 2^n - 1$
  - #transition = 2 x #states =  $2(2^n - 1)$
  - Example: n = 3: 7 states, 14 transitions  
n = 4: 15 states, 30 transitions

# State Minimization / Reduction (cont'd)

- Algorithm sketch for state reduction
  - 1. group together states that have the same outputs
    - These states are potentially equivalent.
  - 2. examine the transitions to see if they go to the same next state for every input combination
    - If they do, the states are equivalent.
    - combine them into a renamed new state.
    - change all transitions to the states into the newly combined states.
  - 3. repeat (1)~(2) until no additional states can be combined
  - polynomial time procedure

# Row-Matching method

## ■ Initial state transition table

| Past Input Seq. | Present State | Next State |          | Output |     |
|-----------------|---------------|------------|----------|--------|-----|
|                 |               | X=0        | X=1      | X=0    | X=1 |
| Reset           | $S_0$         | $S_1$      | $S_2$    | 0      | 0   |
| 0               | $S_1$         | $S_3$      | $S_4$    | 0      | 0   |
| 1               | $S_2$         | $S_5$      | $S_6$    | 0      | 0   |
| 00              | $S_3$         | $S_7$      | $S_8$    | 0      | 0   |
| 01              | $S_4$         | $S_9$      | $S_{10}$ | 0      | 0   |
| 10              | $S_5$         | $S_{11}$   | $S_{12}$ | 0      | 0   |
| 11              | $S_6$         | $S_{13}$   | $S_{14}$ | 0      | 0   |
| 000             | $S_7$         | $S_0$      | $S_0$    | 0      | 0   |
| 001             | $S_8$         | $S_0$      | $S_0$    | 0      | 0   |
| 010             | $S_9$         | $S_0$      | $S_0$    | 0      | 0   |
| 011             | $S_{10}$      | $S_0$      | $S_0$    | 1      | 0   |
| 100             | $S_{11}$      | $S_0$      | $S_0$    | 0      | 0   |
| 101             | $S_{12}$      | $S_0$      | $S_0$    | 1      | 0   |
| 110             | $S_{13}$      | $S_0$      | $S_0$    | 0      | 0   |
| 111             | $S_{14}$      | $S_0$      | $S_0$    | 0      | 0   |

**Row-Matching:**  
the same next-states  
and output values  
 $S_{10}$  and  $S_{12} \rightarrow S_{10}'$



# Row-Matching method (cont'd)

- Revised state transition table after S10 and S12 are combined

| Past Input Seq. | Present State   | Next State      |                 | Output |     |
|-----------------|-----------------|-----------------|-----------------|--------|-----|
|                 |                 | X=0             | X=1             | X=0    | X=1 |
| Reset           | S <sub>0</sub>  | S <sub>1</sub>  | S <sub>2</sub>  | 0      | 0   |
| 0               | S <sub>1</sub>  | S <sub>3</sub>  | S <sub>4</sub>  | 0      | 0   |
| 1               | S <sub>2</sub>  | S <sub>5</sub>  | S <sub>6</sub>  | 0      | 0   |
| 00              | S <sub>3</sub>  | S <sub>7</sub>  | S <sub>8</sub>  | 0      | 0   |
| 01              | S <sub>4</sub>  | S <sub>9</sub>  | S <sub>10</sub> | 0      | 0   |
| 10              | S <sub>5</sub>  | S <sub>11</sub> | S <sub>10</sub> | 0      | 0   |
| 11              | S <sub>6</sub>  | S <sub>13</sub> | S <sub>14</sub> | 0      | 0   |
| 000             | S <sub>7</sub>  | S <sub>0</sub>  | S <sub>0</sub>  | 0      | 0   |
| 001             | S <sub>8</sub>  | S <sub>0</sub>  | S <sub>0</sub>  | 0      | 0   |
| 010             | S <sub>9</sub>  | S <sub>0</sub>  | S <sub>0</sub>  | 0      | 0   |
| 011 or 101      | S <sub>10</sub> | S <sub>0</sub>  | S <sub>0</sub>  | 1      | 0   |
| 100             | S <sub>11</sub> | S <sub>0</sub>  | S <sub>0</sub>  | 0      | 0   |
| 110             | S <sub>13</sub> | S <sub>0</sub>  | S <sub>0</sub>  | 0      | 0   |
| 111             | S <sub>14</sub> | S <sub>0</sub>  | S <sub>0</sub>  | 0      | 0   |

# Row-Matching method (cont'd)

- Row-matching iteration

| Input Sequence | Present State | Next State |           | Output |     |
|----------------|---------------|------------|-----------|--------|-----|
|                |               | X=0        | X=1       | X=0    | X=1 |
| Reset          | $S_0$         | $S_1$      | $S_2$     | 0      | 0   |
| 0              | $S_1$         | $S_3$      | $S_4$     | 0      | 0   |
| 1              | $S_2$         | $S_5$      | $S_6$     | 0      | 0   |
| 00             | $S_3$         | $S_7$      | $S_8$     | 0      | 0   |
| 01             | $S_4$         | $S_9$      | $S'_{10}$ | 0      | 0   |
| 10             | $S_5$         | $S_{11}$   | $S'_{10}$ | 0      | 0   |
| 11             | $S_6$         | $S_{13}$   | $S_{14}$  | 0      | 0   |
| 000            | $S_7$         | $S_0$      | $S_0$     | 0      | 0   |
| 001            | $S_8$         | $S_0$      | $S_0$     | 0      | 0   |
| 010            | $S_9$         | $S_0$      | $S_0$     | 0      | 0   |
| 011 or 101     | $S'_{10}$     | $S_0$      | $S_0$     | 1      | 0   |
| 100            | $S_{11}$      | $S_0$      | $S_0$     | 0      | 0   |
| 110            | $S_{13}$      | $S_0$      | $S_0$     | 0      | 0   |
| 111            | $S_{14}$      | $S_0$      | $S_0$     | 0      | 0   |

# Row-Matching method (cont'd)

- Row-matching iteration (cont'd)


| Input Sequence    | Present State | Next State |           | Output |     |
|-------------------|---------------|------------|-----------|--------|-----|
|                   |               | X=0        | X=1       | X=0    | X=1 |
| Reset             | $S_0$         | $S_1$      | $S_2$     | 0      | 0   |
| 0                 | $S_1$         | $S_3$      | $S_4$     | 0      | 0   |
| 1                 | $S_2$         | $S_5$      | $S_6$     | 0      | 0   |
| 00                | $S_3$         | $S_7'$     | $S_7'$    | 0      | 0   |
| 01                | $S_4$         | $S_7'$     | $S_{10}'$ | 0      | 0   |
| 10                | $S_5$         | $S_7'$     | $S_{10}'$ | 0      | 0   |
| 11                | $S_6$         | $S_7'$     | $S_7'$    | 0      | 0   |
| not (01 1 or 101) | $S_7'$        | $S_0$      | $S_0$     | 0      | 0   |
| 011 or 101        | $S_{10}'$     | $S_0$      | $S_0$     | 1      | 0   |

# Row-Matching method (cont'd)

- Final reduced state transition table

| Input Sequence   | Present State | Next State |      | Output |     |
|------------------|---------------|------------|------|--------|-----|
|                  |               | X=0        | X=1  | X=0    | X=1 |
| Reset            | S0            | S1         | S2   | 0      | 0   |
| 0                | S1            | S3'        | S4'  | 0      | 0   |
| 1                | S2            | S4'        | S3'  | 0      | 0   |
| 00 or 11         | S3'           | S7'        | S7'  | 0      | 0   |
| 01 or 10         | S4'           | S7'        | S10' | 0      | 0   |
| not (011 or 101) | S7'           | S0         | S0   | 0      | 0   |
| 011 or 101       | S10'          | S0         | S0   | 1      | 0   |

- Corresponding State Diagram

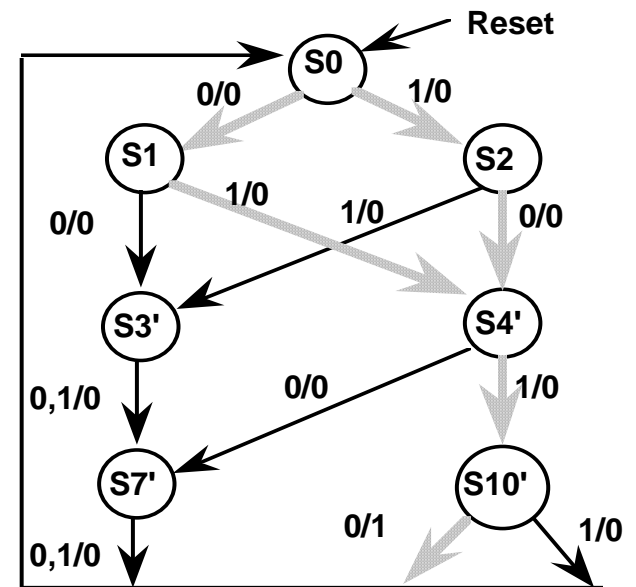


# Row-Matching method (cont'd)

- Row-matching methods
  - Straightforward to understand and easy to implement
  - Problem: does not yield the most reduced state table
    - Example: 3 State Odd Parity Checker

| Present State  | Next State     |                | Output |
|----------------|----------------|----------------|--------|
|                | X=0            | X=1            |        |
| S <sub>0</sub> | S <sub>0</sub> | S <sub>1</sub> | 0      |
| S <sub>1</sub> | S <sub>1</sub> | S <sub>2</sub> | 1      |
| S <sub>2</sub> | S <sub>2</sub> | S <sub>1</sub> | 0      |

 **No way to combine states S<sub>0</sub> and S<sub>2</sub> based on Next State Criterion!**



# Implication Chart method

## ■ Example specification

- Name: three-bit sequence (010 or 110) detector
- Input:  $X = \{0, 1\}$
- Output:  $Z = \{0, 1\}$
- Behavior:

$$Z = \begin{cases} 1 & \text{if each 3-bit input sequence (no overlap) is 010 or 110} \\ 0 & \text{otherwise} \end{cases}$$

## ■ Initial state transition table


| Past Input Seq. | Present State | Next State |       | Output |     |
|-----------------|---------------|------------|-------|--------|-----|
|                 |               | X=0        | X=1   | X=0    | X=1 |
| Reset           | $S_0$         | $S_1$      | $S_2$ | 0      | 0   |
| 0               | $S_1$         | $S_3$      | $S_4$ | 0      | 0   |
| 1               | $S_2$         | $S_5$      | $S_6$ | 0      | 0   |
| 00              | $S_3$         | $S_0$      | $S_0$ | 0      | 0   |
| 01              | $S_4$         | $S_0$      | $S_0$ | 1      | 0   |
| 10              | $S_5$         | $S_0$      | $S_0$ | 0      | 0   |
| 11              | $S_6$         | $S_0$      | $S_0$ | 1      | 0   |

# Implication Chart method (cont'd)

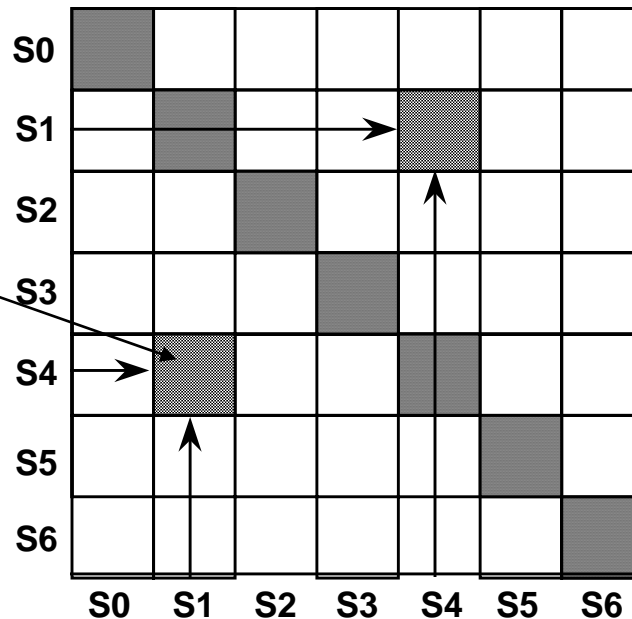
## ■ Implication Chart

- Enumerate all possible combinations of states taken two at a time

**Next States  
Under all  
Input  
Combinations**



 **Naive Data Structure:  
 $X_{ij}$  will be the same as  $X_{ji}$   
Also, can eliminate the diagonal**



**Implication Chart**

# Implication Chart method (cont'd)


- Filling in the Implication Chart
  - Entry  $X_{ij}$ : Row is  $S_i$ , Column is  $S_j$
  - $S_i$  is equivalent to  $S_j$  if outputs are the same and next states are equivalent
  - $X_{ij}$  contains the next states of  $S_i$ ,  $S_j$  which must be equivalent if  $S_i$  and  $S_j$  are equivalent
  - If  $S_i$ ,  $S_j$  have different output behavior, then  $X_{ij}$  is crossed out
- Example:
  - $S_0$  transitions to  $S_1$  on 0,  $S_2$  on 1;
  - $S_1$  transitions to  $S_3$  on 0,  $S_4$  on 1;
  - So square  $X_{\langle 0,1 \rangle}$  contains entries  $S_1$ - $S_3$  (transition on zero),  $S_2$ - $S_4$  (transition on one)






# Implication Chart method (cont'd)

## ■ Starting Implication Chart

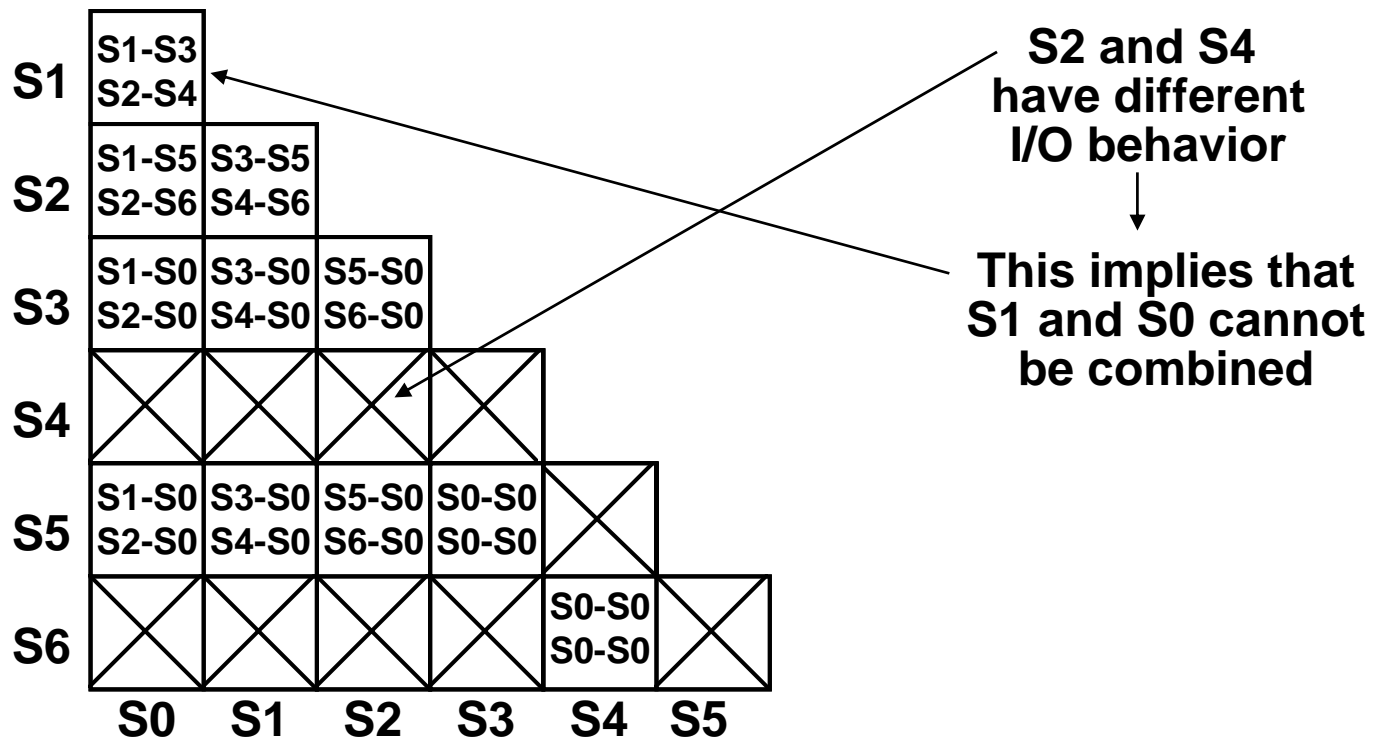
 
# Implication Chart method (cont'd)

- Results of First Marking Pass
- Second Pass Adds No New Information
  - S3 and S5 are equivalent
  - S4 and S6 are equivalent
  - This implies that S1 and S2 are too!




## ■ Reduced State Transition Table

| Input Sequence | Present State | Next State |       | Output |       |
|----------------|---------------|------------|-------|--------|-------|
|                |               | X = 0      | X = 1 | X = 0  | X = 1 |
| Reset          | $S_0$         | $S_1$      | $S_1$ | 0      | 0     |
| 0 or 1         | $S_1$         | $S_3$      | $S_4$ | 0      | 0     |
| 00 or 10       | $S_3$         | $S_0$      | $S_0$ | 0      | 0     |
| 01 or 11       | $S_4$         | $S_0$      | $S_0$ | 1      | 0     |

# Implication Chart method (cont'd)

## Multiple Input State Diagram Example

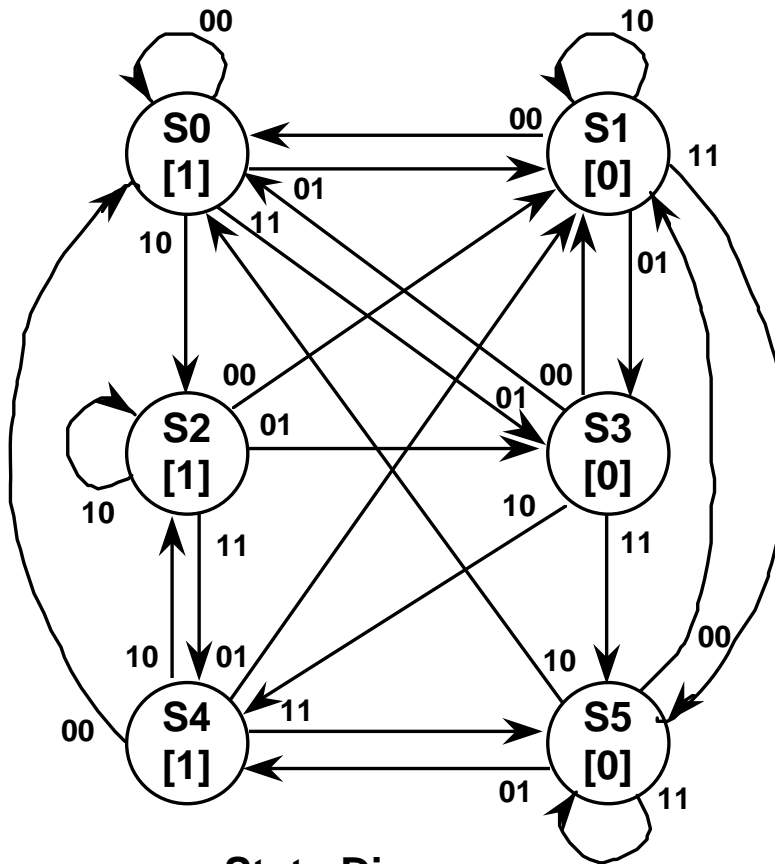


**State Diagram**

| Present State  | Next State     |                |                |                | Output |
|----------------|----------------|----------------|----------------|----------------|--------|
|                | 00             | 01             | 10             | 11             |        |
| S <sub>0</sub> | S <sub>0</sub> | S <sub>1</sub> | S <sub>2</sub> | S <sub>3</sub> | 1      |
| S <sub>1</sub> | S <sub>0</sub> | S <sub>3</sub> | S <sub>1</sub> | S <sub>5</sub> | 0      |
| S <sub>2</sub> | S <sub>1</sub> | S <sub>3</sub> | S <sub>2</sub> | S <sub>4</sub> | 1      |
| S <sub>3</sub> | S <sub>1</sub> | S <sub>0</sub> | S <sub>4</sub> | S <sub>5</sub> | 0      |
| S <sub>4</sub> | S <sub>0</sub> | S <sub>1</sub> | S <sub>2</sub> | S <sub>5</sub> | 1      |
| S <sub>5</sub> | S <sub>1</sub> | S <sub>4</sub> | S <sub>0</sub> | S <sub>5</sub> | 0      |

**Symbolic State Diagram**

# Implication Chart method (cont'd)

## Multiple Input Example

 

**Implication Chart**

| Present State | Next State |        |        |        | Output |
|---------------|------------|--------|--------|--------|--------|
|               | 00         | 01     | 10     | 11     |        |
| $S_0'$        | $S_0'$     | $S_1'$ | $S_2'$ | $S_3'$ | 1      |
| $S_1$         | $S_0'$     | $S_3'$ | $S_1'$ | $S_3'$ | 0      |
| $S_2$         | $S_1'$     | $S_3'$ | $S_2'$ | $S_0'$ | 1      |
| $S_3$         | $S_1'$     | $S_0'$ | $S_0'$ | $S_3'$ | 0      |

**Minimized State Table**


# Implication Chart method (cont'd)

- The detailed algorithm:
  1. Construct implication chart, one square for each combination of states taken two at a time.
  2. For each square labeled  $S_i, S_j$ ,
    - if outputs differ, then cross out the square.
    - otherwise, write down next state pairs for all input combinations.
  3. Advancing through the chart top-to-bottom and left-to-right,
    - if square  $S_i, S_j$  contains next state pair  $S_m-S_n$  and square  $S_m, S_n$  is already crossed out, then cross out square  $S_i, S_j$ .
  4. Continue executing Step 3 until no new squares are crossed out.
  5. For each remaining square  $S_i, S_j$ , we conclude that  $S_i$  and  $S_j$  are equivalent.

# Implication Chart method (cont'd)

- Does the method solve the problem with the odd parity checker?

| Present State  | Next State     |                | Output |
|----------------|----------------|----------------|--------|
|                | X=0            | X=1            |        |
| S <sub>0</sub> | S <sub>0</sub> | S <sub>1</sub> | 0      |
| S <sub>1</sub> | S <sub>1</sub> | S <sub>2</sub> | 1      |
| S <sub>2</sub> | S <sub>2</sub> | S <sub>1</sub> | 0      |

 

**S<sub>0</sub> is equivalent to S<sub>2</sub>  
since nothing contradicts this assertion!**

# Equivalent states in the presence of don't cares

- Equivalence of states is transitive when machine is fully specified
- But its not transitive when don't cares are present


- Example

|       |       |        |                                      |
|-------|-------|--------|--------------------------------------|
| e.g., | state | output |                                      |
|       | S0    | – 0    | S1 is compatible with both S0 and S2 |
|       | S1    | 1 –    | but S0 and S2 are incompatible       |
|       | S2    | – 1    |                                      |

- No polynomial time algorithm exists for determining best grouping of states into equivalent sets that will yield the smallest number of final states

# When state minimization doesn't help

 - Example: edge detector
  - outputs 1 when last two input changes from 0 to 1
- Implementation using minimized states



| X | Q <sub>1</sub> | Q <sub>0</sub> | Q <sub>1</sub> <sup>+</sup> | Q <sub>0</sub> <sup>+</sup> |
|---|----------------|----------------|-----------------------------|-----------------------------|
| 0 | 0              | 0              | 0                           | 0                           |
| 0 | 0              | 1              | 0                           | 0                           |
| 0 | 1              | 0              | 0                           | 0                           |
| 1 | 0              | 0              | 0                           | 1                           |
| 1 | 0              | 1              | 1                           | 0                           |
| 1 | 1              | 0              | 1                           | 0                           |
| - | 1              | 1              | -                           | -                           |



$$Q_1^+ = X (Q_1 + Q_0)$$

$$Q_0^+ = X Q_1' Q_0'$$


  
# When state minimization doesn't help (cont'd)

- Another implementation of edge detector
  - "Ad hoc" solution - not minimal but cheap and fast



# State assignment

- State assignment (encoding): choose bit vectors to assign to each “symbolic” state
  - with  $n$  state bits for  $m$  states ( $n \leq m \leq 2^n$ ),
    - there are  $2^n! / (2^n - m)!$  possible state assignments
    - huge number even for small values of  $n$  and  $m$ 
      - intractable for state machines of any practical size
      - heuristics are necessary for practical solutions
  - state encoding with fewer bits has fewer equations to implement
    - however, each may be more complex
  - state encoding with more bits (e.g., one-hot) has simpler equations
    - complexity directly related to complexity of state diagram


# State assignment (cont'd)

- Optimize some metric for the combinational logic
  - size (the amount of logic and number of FFs)
  - speed (depth of logic and fanout)
  - dependencies (decomposition)
- Possible strategies
  - sequential – just number states as they appear in the state table
  - random – pick random codes
  - one-hot – use as many state bits as there are states (bit=1 → state)
  - output-oriented – use outputs to help encode states
  - heuristic – rules of thumb that seem to work in most cases
- No guarantee of optimality – another intractable problem

# State assignment (cont'd)


- Example: traffic light controller
  - 4 states: 4 choices for first state, 3 for second, 2 for third, 1 for last  
-> 24 different encodings (4!)
  - Alternative state encodings of the traffic light controller

| HG | HY | FG | FY | HG | HY | FG | FY |
|----|----|----|----|----|----|----|----|
| 00 | 01 | 10 | 11 | 10 | 00 | 01 | 11 |
| 00 | 01 | 11 | 10 | 10 | 00 | 11 | 01 |
| 00 | 10 | 01 | 11 | 10 | 01 | 00 | 11 |
| 00 | 10 | 11 | 01 | 10 | 01 | 11 | 00 |
| 00 | 11 | 01 | 10 | 10 | 11 | 00 | 01 |
| 00 | 11 | 10 | 01 | 10 | 11 | 01 | 00 |
| 01 | 00 | 10 | 11 | 11 | 00 | 01 | 10 |
| 01 | 00 | 11 | 10 | 11 | 00 | 10 | 01 |
| 01 | 10 | 00 | 11 | 11 | 01 | 00 | 10 |
| 01 | 10 | 11 | 00 | 11 | 01 | 10 | 00 |
| 01 | 11 | 00 | 10 | 11 | 10 | 00 | 01 |
| 01 | 11 | 10 | 00 | 11 | 10 | 01 | 00 |

 

# State assignment (cont'd)

 - Example: traffic light controller (cont'd)
  - State diagram and Symbolic state transition table



| Inputs |    |    | Present State |       | Next State |       | Outputs |       |       |       |       |
|--------|----|----|---------------|-------|------------|-------|---------|-------|-------|-------|-------|
| C      | TL | TS | $Q_1$         | $Q_0$ | $P_1$      | $P_0$ | ST      | $H_1$ | $H_0$ | $F_1$ | $F_0$ |
| 0      | X  | X  | HG            |       | HG         |       | 0       | 00    |       | 10    |       |
| X      | 0  | X  | HG            |       | HG         |       | 0       | 00    |       | 10    |       |
| 1      | 1  | X  | HG            |       | HY         |       | 1       | 00    |       | 10    |       |
| X      | X  | 0  | HY            |       | HY         |       | 0       | 01    |       | 10    |       |
| X      | X  | 1  | HY            |       | FG         |       | 1       | 01    |       | 10    |       |
| 1      | 0  | X  | FG            |       | FG         |       | 0       | 10    |       | 00    |       |
| 0      | X  | X  | FG            |       | FY         |       | 1       | 10    |       | 00    |       |
| X      | 1  | X  | FG            |       | FY         |       | 1       | 10    |       | 00    |       |
| X      | X  | 0  | FY            |       | FY         |       | 0       | 10    |       | 01    |       |
| X      | X  | 1  | FY            |       | HG         |       | 1       | 10    |       | 01    |       |

# Sequential encoding

- Sequential encoding
  - Simply replace the symbolic state names with a regular encoding sequence
- Examples:
  - Sequential encoding: HG=00, HY=01, FG=10, FY=11
  - Encoding with Gray-code: HG=00, HY=01, FG=11, FY=10

| Inputs |    |    | Present State  |                | Next State     |                | Outputs |                |                |                |                |
|--------|----|----|----------------|----------------|----------------|----------------|---------|----------------|----------------|----------------|----------------|
| C      | TL | TS | Q <sub>1</sub> | Q <sub>0</sub> | P <sub>1</sub> | P <sub>0</sub> | ST      | H <sub>1</sub> | H <sub>0</sub> | F <sub>1</sub> | F <sub>0</sub> |
| 0      | X  | X  | 00             |                | 00             |                | 0       | 00             |                | 10             |                |
| X      | 0  | X  | 00             |                | 00             |                | 0       | 00             |                | 10             |                |
| 1      | 1  | X  | 00             |                | 01             |                | 1       | 00             |                | 10             |                |
| X      | X  | 0  | 01             |                | 01             |                | 0       | 01             |                | 10             |                |
| X      | X  | 1  | 01             |                | 11             |                | 1       | 01             |                | 10             |                |
| 1      | 0  | X  | 11             |                | 11             |                | 0       | 10             |                | 00             |                |
| 0      | X  | X  | 11             |                | 10             |                | 1       | 10             |                | 00             |                |
| X      | 1  | X  | 11             |                | 10             |                | 1       | 10             |                | 00             |                |
| X      | X  | 0  | 10             |                | 10             |                | 0       | 10             |                | 01             |                |
| X      | X  | 1  | 10             |                | 00             |                | 1       | 10             |                | 01             |                |

# Sequential encoding (cont'd)

- Example (cont'd)
  - Two level equation

$$P_1 = TS \cdot Q_1' \cdot Q_0 + C \cdot TL' \cdot Q_1 \cdot Q_0 + C' \cdot Q_1 \cdot Q_0 + TL \cdot Q_1 \cdot Q_0 + TS' \cdot Q_1 \cdot Q_0'$$

$$P_0 = C \cdot TL \cdot Q_1' \cdot Q_0' + TS' \cdot Q_1' \cdot Q_0 + TS \cdot Q_1' \cdot Q_0 + C \cdot TL' \cdot Q_1 \cdot Q_0$$

$$ST = C \cdot TL \cdot Q_1' \cdot Q_0' + TS \cdot Q_1' \cdot Q_0 + C' \cdot Q_1 \cdot Q_0 + TL \cdot Q_1 \cdot Q_0 + TS \cdot Q_1 \cdot Q_0'$$

$$H_1 = C \cdot TL' \cdot Q_1 \cdot Q_0 + C' \cdot Q_1 \cdot Q_0 + TL \cdot Q_1 \cdot Q_0 + TS' \cdot Q_1 \cdot Q_0' + TS \cdot Q_1 \cdot Q_0'$$

$$H_0 = TS' \cdot Q_1' \cdot Q_0 + TS \cdot Q_1' \cdot Q_0$$

$$F_1 = C' \cdot Q_1' \cdot Q_0' + TL' \cdot Q_1' \cdot Q_0' + C \cdot TL \cdot Q_1' \cdot Q_0' + TS' \cdot Q_1' \cdot Q_0 + TS \cdot Q_1' \cdot Q_0$$

$$F_0 = TS' \cdot Q_1 \cdot Q_0' + TS \cdot Q_1 \cdot Q_0'$$

# Sequential encoding (cont'd)

- Examples (cont'd):
  - Three-level implementation
    - More than two input gates: P1, P0, ST
    - Two input gates: the others

$$P_1 = TS \cdot HY + FG + TS' \cdot FY$$

$$P_0 = X \cdot HG + HY + Y \cdot FG$$

$$ST = X \cdot HG + TS \cdot HY + Y' \cdot FG + TS \cdot FY$$

$$H_1 = FG + FY$$

$$H_0 = HY$$

$$F_1 = HG + HY$$

$$F_0 = FY$$

---

$$HG = Q_1' \cdot Q_0'$$

$$HY = Q_1' \cdot Q_0$$

$$FG = Q_1 \cdot Q_0$$

$$FY = Q_1 \cdot Q_0'$$

$$X = C \cdot TL$$

$$Y = C \cdot TL'$$



# Random encoding

- Random encoding
  - replace the symbolic state names with a random encoding sequence
- Example: HG=00, HY=10, FG=01, FY=11
  - Two level implementation
    - No gates of more than three inputs

| Inputs |    |    | Present State  |                | Next State     |                | Outputs |                |                |                |                |
|--------|----|----|----------------|----------------|----------------|----------------|---------|----------------|----------------|----------------|----------------|
| C      | TL | TS | Q <sub>1</sub> | Q <sub>0</sub> | P <sub>1</sub> | P <sub>0</sub> | ST      | H <sub>1</sub> | H <sub>0</sub> | F <sub>1</sub> | F <sub>0</sub> |
| 0      | X  | X  | 00             |                | 00             |                | 0       | 00             |                | 10             |                |
| X      | 0  | X  | 00             |                | 00             |                | 0       | 00             |                | 10             |                |
| 1      | 1  | X  | 00             |                | 10             |                | 1       | 00             |                | 10             |                |
| X      | X  | 0  | 10             |                | 10             |                | 0       | 01             |                | 10             |                |
| X      | X  | 1  | 10             |                | 01             |                | 1       | 01             |                | 10             |                |
| 1      | 0  | X  | 01             |                | 01             |                | 0       | 10             |                | 00             |                |
| 0      | X  | X  | 01             |                | 11             |                | 1       | 10             |                | 00             |                |
| X      | 1  | X  | 01             |                | 11             |                | 1       | 10             |                | 00             |                |
| X      | X  | 0  | 11             |                | 11             |                | 0       | 10             |                | 01             |                |
| X      | X  | 1  | 11             |                | 00             |                | 1       | 10             |                | 01             |                |

$$P_1 = C \cdot TL \cdot Q_1' + TS' \cdot Q_1 + C' \cdot Q_1' \cdot Q_0$$

$$P_0 = TS \cdot Q_1 \cdot Q_0' + Q_1' \cdot Q_0 + TS' \cdot Q_1 \cdot Q_0$$

$$ST = C \cdot TL \cdot Q_1' + C' \cdot Q_1' \cdot Q_0 + TS \cdot Q_1$$

$$H_1 = Q_0$$

$$H_0 = Q_1 \cdot Q_0'$$

$$F_1 = Q_0'$$

$$F_0 = Q_1 \cdot Q_0$$

# One-Hot encoding

- One-Hot encoding
  - $n$  states is encoded using  $n$  flip-flops
  - Only 1 bit is asserted in each of the states.
    - ex) 0001, 0010, 0100, 1000
- Properties
  - Simple: easy to encode, easy to debug
  - Small logic functions
    - each state function requires only predecessor state bits as input
    - a lot of don't-care opportunities
  - Good for programmable devices
    - lots of flip-flops readily available
    - simple functions with small support (signals it's dependent upon)
  - Impractical for large machines
    - too many states require too many flip-flops
    - decompose FSMs into smaller pieces that can be one-hot encoded
- Many slight variations to one-hot
  - one-hot + all-0

# One-Hot encoding (cont'd)

- Example:
  - HG=0001, HY=0010, FG=0100, FY=1000

| Inputs |    |    | Present State  |                |                |                | Next State     |                |                |                | Outputs |                |                |                |                |
|--------|----|----|----------------|----------------|----------------|----------------|----------------|----------------|----------------|----------------|---------|----------------|----------------|----------------|----------------|
| C      | TL | TS | Q <sub>3</sub> | Q <sub>2</sub> | Q <sub>1</sub> | Q <sub>0</sub> | P <sub>3</sub> | P <sub>2</sub> | P <sub>1</sub> | P <sub>0</sub> | ST      | H <sub>1</sub> | H <sub>0</sub> | F <sub>1</sub> | F <sub>0</sub> |
| 0      | X  | X  |                | 0              | 0              | 0              | 1              |                |                |                | 0       | 0              | 0              | 1              | 0              |
| X      | 0  | X  |                | 0              | 0              | 0              | 1              |                |                |                | 0       | 0              | 0              | 1              | 0              |
| 1      | 1  | X  |                | 0              | 0              | 0              | 1              |                | 0              | 0              | 1       | 0              | 0              | 1              | 0              |
| X      | X  | 0  |                | 0              | 0              | 1              | 0              |                |                |                | 0       | 0              | 1              | 1              | 0              |
| X      | X  | 1  |                | 0              | 0              | 1              | 0              |                | 0              | 1              | 1       | 0              | 1              | 1              | 0              |
| 1      | 0  | X  |                | 0              | 1              | 0              | 0              |                |                |                | 0       | 1              | 0              | 0              | 0              |
| 0      | X  | X  |                | 0              | 1              | 0              | 0              |                |                |                | 1       | 1              | 0              | 0              | 0              |
| X      | 1  | X  |                | 0              | 1              | 0              | 0              |                |                |                | 1       | 1              | 0              | 0              | 0              |
| X      | X  | 0  |                | 1              | 0              | 0              | 0              |                |                |                | 0       | 1              | 0              | 0              | 1              |
| X      | X  | 1  |                | 1              | 0              | 0              | 0              |                |                |                | 1       | 1              | 0              | 0              | 1              |

# One-Hot encoding (cont'd)

## ■ Example (cont'd)

### □ Implementation:

$$P_3 = (C' + TL) \cdot Q_2 + (TS') \cdot Q_3$$

$$P_2 = (TS) \cdot Q_1 + (C \cdot TL') \cdot Q_2$$

$$P_1 = (C \cdot TL) \cdot Q_0 + (TS') \cdot Q_1$$

$$P_0 = (C' + TL') \cdot Q_0 + (TS) \cdot Q_3$$


$$ST = (C \cdot TL) \cdot Q_0 + (TS) \cdot Q_1 \\ + (C' + TL) \cdot Q_2 + (TS) \cdot Q_3$$

$$H_1 = Q_3 + Q_2$$

$$H_0 = Q_1$$

$$F_1 = Q_1 + Q_0$$

$$F_0 = Q_3$$

 

# Output-Oriented encoding

- Output-oriented encoding:
  - Reuse outputs as state bits - use outputs to help distinguish states
    - why create new functions for state bits when output can serve as well
    - Synchronous Mealy outputs, since they are implemented directly as the output of a flip-flop, can also be used this way
- Example: the traffic-light controller

| Inputs |    |    | Present State  |                | Next State     |                | Outputs |                |                |                |                |
|--------|----|----|----------------|----------------|----------------|----------------|---------|----------------|----------------|----------------|----------------|
| C      | TL | TS | Q <sub>1</sub> | Q <sub>0</sub> | P <sub>1</sub> | P <sub>0</sub> | ST      | H <sub>1</sub> | H <sub>0</sub> | F <sub>1</sub> | F <sub>0</sub> |
| 0      | X  | X  | HG             |                | HG             |                | 0       | 00             |                | 10             |                |
| X      | 0  | X  | HG             |                | HG             |                | 0       | 00             |                | 10             |                |
| 1      | 1  | X  | HG             |                | HY             |                | 1       | 00             |                | 10             |                |
| X      | X  | 0  | HY             |                | HY             |                | 0       | 01             |                | 10             |                |
| X      | X  | 1  | HY             |                | FG             |                | 1       | 01             |                | 10             |                |
| 1      | 0  | X  | FG             |                | FG             |                | 0       | 10             |                | 00             |                |
| 0      | X  | X  | FG             |                | FY             |                | 1       | 10             |                | 00             |                |
| X      | 1  | X  | FG             |                | FY             |                | 1       | 10             |                | 00             |                |
| X      | X  | 0  | FY             |                | FY             |                | 0       | 10             |                | 01             |                |
| X      | X  | 1  | FY             |                | HG             |                | 1       | 10             |                | 01             |                |

***Output signals  
are unique  
for the transitions  
to each state***

# Output-Oriented encoding (cont'd)

- Example (cont'd)

- Next state is represented by “present outputs” instead

*State equations*

$$HG = ST \cdot H_1 H_0' F_1' F_0 + ST' \cdot H_1' H_0' F_1 F_0'$$

$$HY = ST \cdot H_1' H_0' F_1 F_0' + ST' \cdot H_1' H_0 F_1' F_0'$$

$$FG = ST \cdot H_1' H_0 F_1 F_0' + ST' \cdot H_1 H_0' F_1' F_0'$$

$$FY = ST \cdot H_1 H_0' F_1' F_0' + ST' \cdot H_1 H_0 F_1' F_0'$$

*Output equations*

$$ST = (C \cdot TL \cdot HG) + (TS \cdot HY)$$

$$+ (C' \cdot FG) + (TL \cdot FG) + (TS \cdot FY)$$

$$H_1 = FG + FY, \quad H_0 = HY$$

$$F_1 = HG + HY, \quad F_0 = FY$$

| Inputs |    |    | Present State     |                |                |                |                | Outputs |                |                |                   |                | Next State |                |                |                |                |
|--------|----|----|-------------------|----------------|----------------|----------------|----------------|---------|----------------|----------------|-------------------|----------------|------------|----------------|----------------|----------------|----------------|
| C      | TL | TS | ST                | H <sub>1</sub> | H <sub>0</sub> | F <sub>1</sub> | F <sub>0</sub> | ST      | H <sub>1</sub> | H <sub>0</sub> | F <sub>1</sub>    | F <sub>0</sub> | ST         | H <sub>1</sub> | H <sub>0</sub> | F <sub>1</sub> | F <sub>0</sub> |
| 0      | X  | X  | HG: 00010 + 11001 |                |                |                |                | 0       | 00             | 10             | HG: 00010 + 11001 |                |            |                |                |                |                |
| X      | 0  | X  | HG: 00010 + 11001 |                |                |                |                | 0       | 00             | 10             | HG: 00010 + 11001 |                |            |                |                |                |                |
| 1      | 1  | X  | HG: 00010 + 11001 |                |                |                |                | 1       | 00             | 10             | HY: 10010 + 00110 |                |            |                |                |                |                |
| X      | X  | 0  | HY: 10010 + 00110 |                |                |                |                | 0       | 01             | 10             | HY: 10010 + 00110 |                |            |                |                |                |                |
| X      | X  | 1  | HY: 10010 + 00110 |                |                |                |                | 1       | 01             | 10             | FG: 10110 + 01000 |                |            |                |                |                |                |
| 1      | 0  | X  | FG: 10110 + 01000 |                |                |                |                | 0       | 10             | 00             | FG: 10110 + 01000 |                |            |                |                |                |                |
| 0      | X  | X  | FG: 10110 + 01000 |                |                |                |                | 1       | 10             | 00             | FY: 11000 + 01001 |                |            |                |                |                |                |
| X      | 1  | X  | FG: 10110 + 01000 |                |                |                |                | 1       | 10             | 00             | FY: 11000 + 01001 |                |            |                |                |                |                |
| X      | X  | 0  | FY: 11000 + 01001 |                |                |                |                | 0       | 10             | 01             | FY: 11000 + 01001 |                |            |                |                |                |                |
| X      | X  | 1  | FY: 11000 + 01001 |                |                |                |                | 1       | 10             | 01             | HG: 00010 + 11001 |                |            |                |                |                |                |


# Heuristic methods for state assignment

- Heuristic methods
  - To make the state encoding problem more tractable
  - Try to reduce the distance in Boolean n-space between related states
  - All current methods are variants of this
    - 1) determine which states “attract” each other (weighted pairs)
    - 2) generate constraints on states (which should be in same cube)
    - 3) place states on Boolean cube so as to maximize constraints satisfied (weighted sum)
  - Can't consider all possible embeddings of state clusters in Boolean cube
    - heuristics for ordering embedding
    - to prune search for best embedding
    - expand cube (more state bits) to satisfy more constraints

# Heuristic methods for state assignment (cont'd)

- State maps:
  - similar in concept to K-maps
  - If state X transitions to state Y, then assign "close" assignments to X and Y
  - provide a means of observing adjacencies in state assignments
- Example

| Present State | Next State |       |
|---------------|------------|-------|
|               | 0          | 1     |
| $S_0$         | $S_1$      | $S_2$ |
| $S_1$         | $S_3$      | $S_3$ |
| $S_2$         | $S_3$      | $S_3$ |
| $S_3$         | $S_4$      | $S_4$ |
| $S_4$         | $S_0$      | $S_0$ |

 





# Heuristic methods for state assignment (cont'd)

## ■ Example (cont'd)


### □ First state assignment and its state map

| State Name     | Assignment     |                |                |
|----------------|----------------|----------------|----------------|
|                | Q <sub>2</sub> | Q <sub>1</sub> | Q <sub>0</sub> |
| S <sub>0</sub> | 0              | 0              | 0              |
| S <sub>1</sub> | 1              | 0              | 1              |
| S <sub>2</sub> | 1              | 1              | 1              |
| S <sub>3</sub> | 0              | 1              | 0              |
| S <sub>4</sub> | 0              | 1              | 1              |

  

### □ Second state assignment and its state map

| State Name     | Assignment     |                |                |
|----------------|----------------|----------------|----------------|
|                | Q <sub>2</sub> | Q <sub>1</sub> | Q <sub>0</sub> |
| S <sub>0</sub> | 0              | 0              | 0              |
| S <sub>1</sub> | 0              | 0              | 1              |
| S <sub>2</sub> | 0              | 1              | 0              |
| S <sub>3</sub> | 0              | 1              | 1              |
| S <sub>4</sub> | 1              | 1              | 1              |

 

# Heuristic methods for state assignment (cont'd)

- Minimum Bit-Change Heuristic
  - Assigns states so that #(bit changes) for all transitions is minimized
- Example

| Transition | First assignment bit changes | Second assignment bit changes |
|------------|------------------------------|-------------------------------|
| S0 to S1   | 2                            | 1                             |
| S0 to S2   | 3                            | 1                             |
| S1 to S3   | 3                            | 1                             |
| S1 to S3   | 2                            | 1                             |
| S3 to S4   | 1                            | 1                             |
| S4 to S1   | 2                            | 2                             |
|            | +)<br>-----<br>13            | +)<br>-----<br>7              |

- cf. Traffic light controller: HG = 00, HY = 01, FG = 11, FY = 10
  - **yields minimum distance encoding but not best assignment!**


# Heuristic methods for state assignment (cont'd)

- Guidelines based on Next state and I/O
- Adjacent codes to states that share a common next state
  - group 1's in next state map

Highest  
Priority

| I | Q | Q <sup>+</sup> | O |
|---|---|----------------|---|
| i | a | c              | j |
| i | b | c              | k |

$$c = i * a + i * b$$

 


- Adjacent codes to states that share a common ancestor state
  - group 1's in next state map

| I | Q | Q <sup>+</sup> | O |
|---|---|----------------|---|
| i | a | b              | j |
| k | a | c              | l |

$$b = i * a$$

$$c = k * a$$

 

- Adjacent codes to states that have a common output behavior
  - group 1's in output map


Lowest  
Priority

| I | Q | Q <sup>+</sup> | O |
|---|---|----------------|---|
| i | a | b              | j |
| i | c | d              | j |

$$j = i * a + i * c$$


$$b = i * a$$

$$d = i * c$$

 

# Heuristic methods for state assignment (cont'd)

## ■ Example: 3-bit Sequence Detector

 

| Present State | Next State |     | Output |     |
|---------------|------------|-----|--------|-----|
|               | X=0        | X=1 | X=0    | X=1 |
| S0            | S1'        | S1' | 0      | 0   |
| S1'           | S3'        | S4' | 0      | 0   |
| S3'           | S0         | S0  | 0      | 0   |
| S4'           | S0         | S0  | 1      | 0   |

**Highest Priority: (S3', S4')**

**Medium Priority: (S3', S4')**


**Lowest Priority:**

**0/0: (S0, S1', S3')**

**1/0: (S0, S1', S3', S4')**


# Heuristic methods for state assignment (cont'd)

- Example (cont'd)

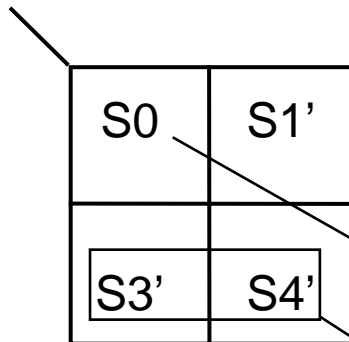

**Reset State = 00**

 
**Highest Priority Adjacency (S3', S4')**



**Not much difference in these two assignments**

# Heuristic methods for state assignment (cont'd)
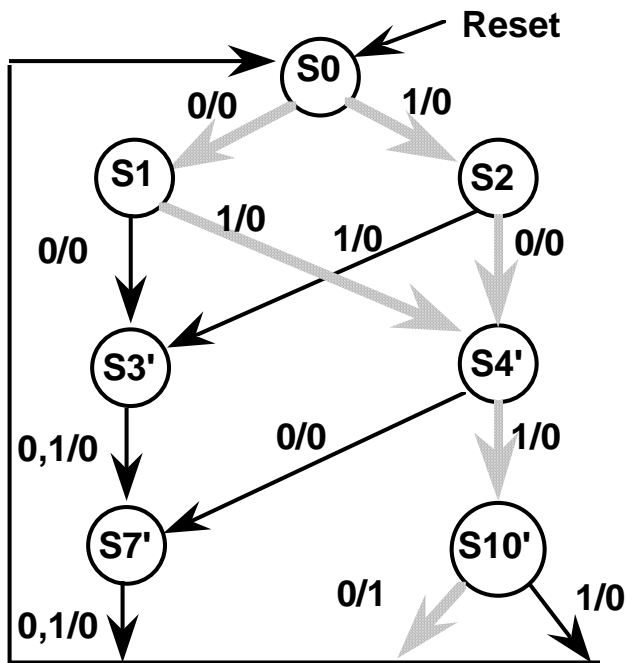
## ■ Another Example: 4 bit String Recognizer



| Present State | Next State |      | Output |     |
|---------------|------------|------|--------|-----|
|               | X=0        | X=1  | X=0    | X=1 |
| S0            | S1         | S2   | 0      | 0   |
| S1            | S3'        | S4'  | 0      | 0   |
| S2            | S4'        | S3'  | 0      | 0   |
| S3'           | S7'        | S7'  | 0      | 0   |
| S4'           | S7'        | S10' | 0      | 0   |
| S7'           | S0         | S0   | 0      | 0   |
| S10'          | S0         | S0   | 1      | 0   |

**Highest Priority: (S3', S4'), (S7', S10')**

**Medium Priority:  
(S1, S2), 2x(S3', S4'), (S7', S10')**

**Lowest Priority:**

**0/0: (S0, S1, S2, S3', S4', S7')**

**1/0: (S0, S1, S2, S3', S4', S7')**

# Heuristic methods for state assignment (cont'd)

State Map

|      |         |    |    |    |    |
|------|---------|----|----|----|----|
|      | Q1 \ Q0 | 00 | 01 | 11 | 10 |
| Q2 \ | 0       | S0 |    |    |    |
|      | 1       |    |    |    |    |

|      |         |    |    |    |    |
|------|---------|----|----|----|----|
|      | Q1 \ Q0 | 00 | 01 | 11 | 10 |
| Q2 \ | 0       | S0 |    |    |    |
|      | 1       |    |    |    |    |

**00 = Reset = S0**

**(S1, S2), (S3', S4'), (S7', S10')**  
placed adjacently

|      |         |    |    |     |    |
|------|---------|----|----|-----|----|
|      | Q1 \ Q0 | 00 | 01 | 11  | 10 |
| Q2 \ | 0       | S0 |    | S3' |    |
|      | 1       |    |    | S4' |    |

|      |         |     |    |    |      |
|------|---------|-----|----|----|------|
|      | Q1 \ Q0 | 00  | 01 | 11 | 10   |
| Q2 \ | 0       | S0  |    |    |      |
|      | 1       | S7' |    |    | S10' |

|      |         |    |    |     |      |
|------|---------|----|----|-----|------|
|      | Q1 \ Q0 | 00 | 01 | 11  | 10   |
| Q2 \ | 0       | S0 |    | S3' | S7'  |
|      | 1       |    |    | S4' | S10' |

|      |         |     |    |     |      |
|------|---------|-----|----|-----|------|
|      | Q1 \ Q0 | 00  | 01 | 11  | 10   |
| Q2 \ | 0       | S0  |    | S3' |      |
|      | 1       | S7' |    | S4' | S10' |

|      |         |    |    |     |      |
|------|---------|----|----|-----|------|
|      | Q1 \ Q0 | 00 | 01 | 11  | 10   |
| Q2 \ | 0       | S0 | S1 | S3' | S7'  |
|      | 1       |    | S2 | S4' | S10' |

|      |         |     |    |     |      |
|------|---------|-----|----|-----|------|
|      | Q1 \ Q0 | 00  | 01 | 11  | 10   |
| Q2 \ | 0       | S0  | S1 | S3' |      |
|      | 1       | S7' | S2 | S4' | S10' |




(a) First encoding

(b) Second encoding




# Heuristic methods for state assignment (cont'd)

## ■ Effect of Adjacencies on Next State Map

| Current State          | Next State |       |
|------------------------|------------|-------|
|                        | X = 0      | X = 1 |
| (S <sub>0</sub> ) 000  | 001        | 101   |
| (S <sub>1</sub> ) 001  | 011        | 111   |
| (S <sub>2</sub> ) 101  | 111        | 011   |
| (S <sub>3</sub> ) 011  | 010        | 010   |
| (S <sub>4</sub> ) 111  | 010        | 110   |
| (S <sub>7</sub> ) 010  | 000        | 000   |
| (S <sub>10</sub> ) 110 | 000        | 000   |

   

| Current State          | Next State |       |
|------------------------|------------|-------|
|                        | X = 0      | X = 1 |
| (S <sub>0</sub> ) 000  | 001        | 010   |
| (S <sub>1</sub> ) 001  | 011        | 100   |
| (S <sub>2</sub> ) 010  | 100        | 011   |
| (S <sub>3</sub> ) 011  | 101        | 101   |
| (S <sub>4</sub> ) 100  | 101        | 110   |
| (S <sub>7</sub> ) 101  | 000        | 000   |
| (S <sub>10</sub> ) 110 | 000        | 000   |

   

**First encoding exhibits a better clustering of 1's in the next state map**



# Summary

- State minimization / reduction
  - introduction to the row-matching and implication chart methods
    - Identify and eliminate redundant states
    - Reduce the number of flip-flops needed to implement a particular FSM
  - straightforward in fully-specified machines
  - computationally intractable, in general (with don't cares)
- State assignment (encoding)
  - Various approaches to state assignment