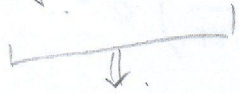


2017.09.04. Mechatronics.

Mechanical

electrical.

Flow rate. $[mm^3/min]$ Current $[A]$ Pressure $[Pa]$ Voltage $[V]$ 

Pipe line maker - Circuit

Nozzle.

Resistor $[\Omega]$ Accumulator.
(tank)Capacitor $[F]$

Laws of circuit


Kirchhoff's law.

1) Voltage.


Any loop (closed)

2) Current.


Any Junction.

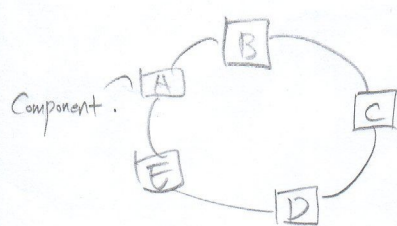

$$\sum V_i = 0.$$

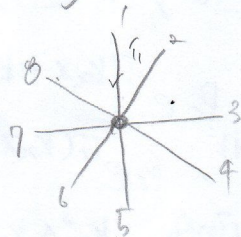

$$\sum I_i = 0$$

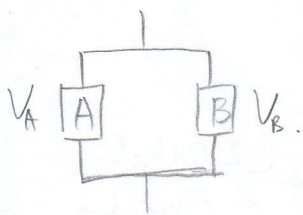

Parallel.

$$-V_A + V_B = 0$$

$$V_A = V_B = \text{const.}$$

Serial

$$-V_A - V_B + V = 0.$$


$$\therefore V = V_A + V_B \text{ (Voltage divide).}$$

$$I_A = I_B = I$$

Elements.

1. Resistor

: 60 ~ 70% all electrical elements

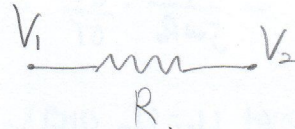: To restrict current.
= Control.

Drop voltage.

→ To Work/Functioning.


→ To dissipate Energy.

$$\text{Law: } i = \frac{V_1 - V_2}{R} \text{ (ohm's law)}$$

1) Parallel connection.

$$V_1 = V_2 = \text{const.}$$

$$I = I_1 + I_2.$$

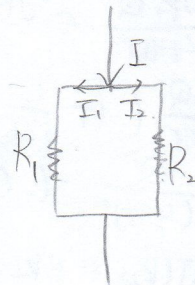

$$\frac{V}{R_{tot}} = \frac{V}{R_1} + \frac{V}{R_2}$$

$$R_{tot} = \frac{R_1 R_2}{R_1 + R_2}$$

$$\textcircled{1} R_1 = R_2 = R,$$


$$R_{tot} = \frac{R^2}{2R} = \frac{R}{2}.$$

$$\textcircled{2} R_1 \gg R_2$$

$$R_{tot} = \frac{R_1 R_2}{R_1 + R_2} = \frac{R_1 R_2}{R_1 (1 + \frac{R_2}{R_1})} \approx R_2$$

Smaller R_2 , dominates.

2) Serial Connection.

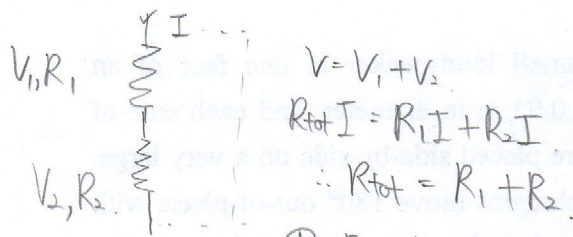

$$V = V_1 + V_2$$

$$R_{tot} I = R_1 I + R_2 I$$

$$\therefore R_{tot} = R_1 + R_2$$

① $R_1 = R_2 = R$

$$R_{tot} = 2R$$


② $R_1 \gg R_2$

$$R_{tot} = R_1 + R_2$$

$$= R_1 (1 + \frac{R_2}{R_1})$$

$$\approx R_1$$

* Voltage Divider.

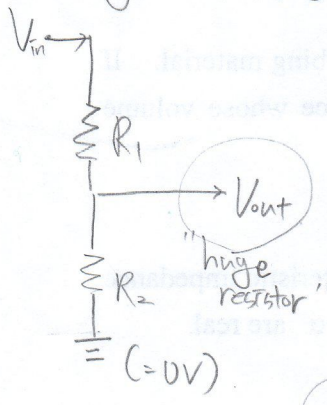

$$I = \frac{V_{in}}{R_1 + R_2}$$


$$V_{out} = I \cdot R_2$$

$$= V_{in} \frac{R_2}{R_1 + R_2}$$

$$\frac{V_{out}}{V_{in}} = \frac{R_2}{R_1 + R_2}$$


Can be adjusted by R_1, R_2 choosing.

Generalized Voltage Divider.

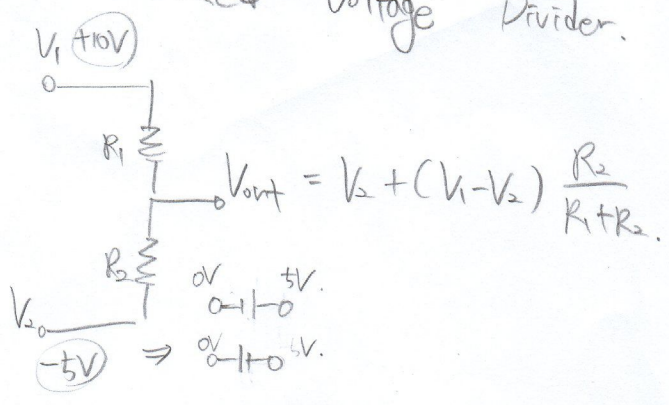

$$V_{out} = V_2 + (V_1 - V_2) \frac{R_2}{R_1 + R_2}$$

(ex)

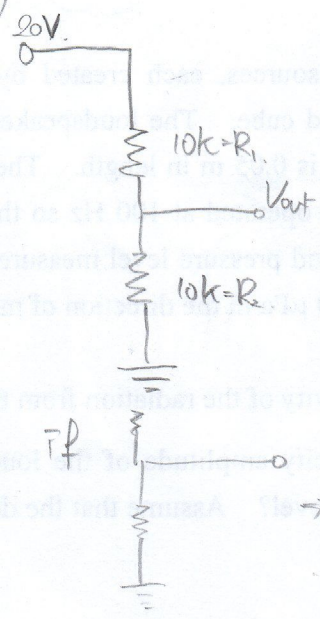


$$V_{out} = V_{in} \frac{R_2}{R_1 + R_2}$$

$$= \frac{1}{2} V_{in}$$

$$= 10V$$

① Conventional

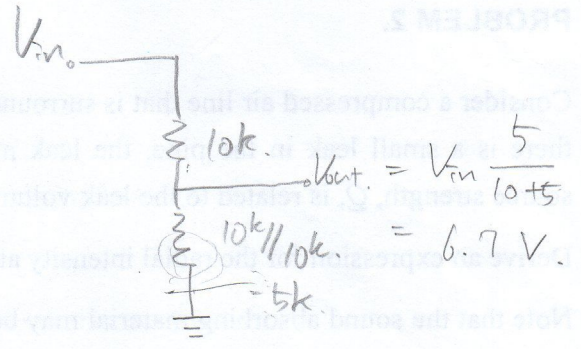


$$V_{out} = V_{in} \frac{5}{10 + 5}$$

$$= 6.7 V$$

② Thevenin's Metrices.

For Any Circuit, of R_i, V_i .

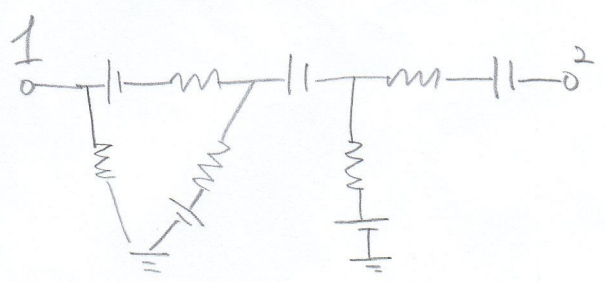

$$\equiv V_{th} - R_{th}$$



disconnected

V_{th} : Open Voltage when nothing is attached.

By Voltmeter measurement or Calculation.

$$R_{th} = \frac{V_{th}}{I_{sc}} \quad I_{sc} : \text{short circuited}$$

③

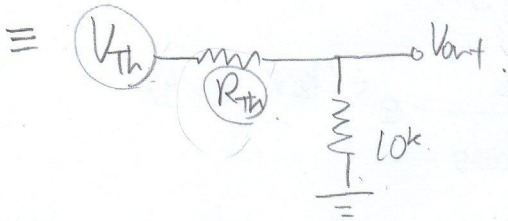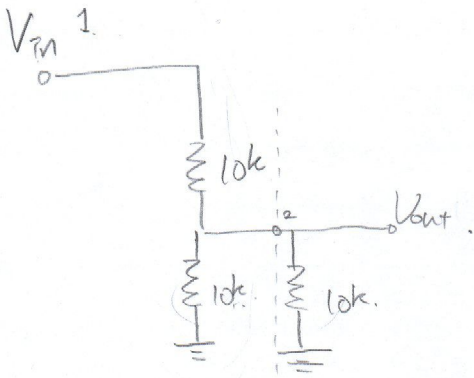

74 in

$V_{Th} = \text{Open Voltage.}$
 $= V_{in} \frac{R_2}{R_1 + R_2}$

$V_{out} = V_{Th} \cdot \frac{10k}{R_{Th} + 10k}$

$R_{Th} = \frac{V_{Th}}{I_{sc}}, I_{sc} = \frac{V_{in}}{R_1}$

$R_{Th} = V_{in} \frac{R_2}{R_1 + R_2} \cdot \frac{R_1}{V_{in}}$
 $= \frac{R_1 \cdot R_2}{R_1 + R_2} = R_1 \parallel R_2$

$\frac{10}{R_{Th} + 10} = \frac{10}{5 + 10} \neq \frac{1}{15}$
 $\frac{10}{20} = \frac{1}{2}$

HW1

$V_{in} = 10V$

