

## Capacitor (Cont).


1) Current source input.

$$V = \frac{1}{C} \int i dt.$$


$$= \frac{1}{C} \int I_0 dt.$$

$$= \frac{1}{C} I_0 t.$$


$i = I_0 = \text{const.}$

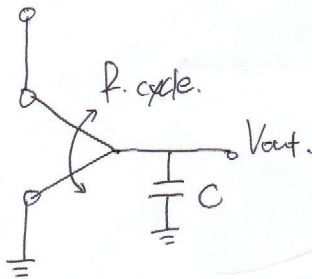

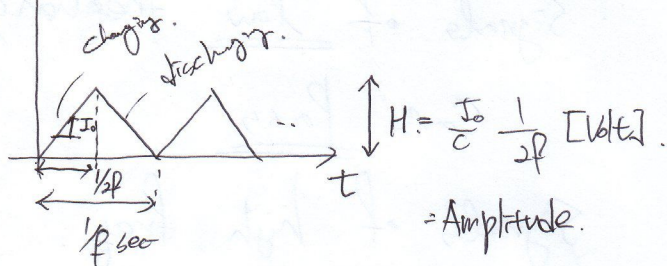"Ramp Signal generator"  $\Rightarrow$  oscilloscope.



2) Voltage source input.

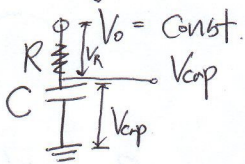

$$V_0 = V_R + V_{cap} \quad \leftarrow \text{Kirchhoff.}$$

$$V_0 = i \cdot R + \frac{1}{C} \int i dt$$

$$0 = R \cdot \frac{di}{dt} + \frac{1}{C} i$$

$$\therefore i(t) = I_0 e^{-t/\tau_c}$$



$$I_0 = \text{initial current (Capacitor still doesn't work)}$$

$$= i(0)$$

$$= \frac{V_0 - 0}{R} = \frac{V_0}{R}$$

$$V_{cap} = \frac{1}{C} \int_0^t i dt$$

$$= V_0 (1 - e^{-t/\tau_c})$$

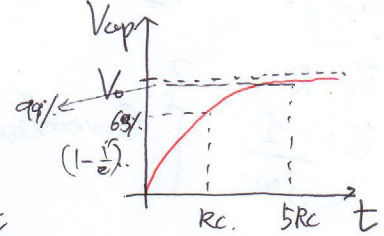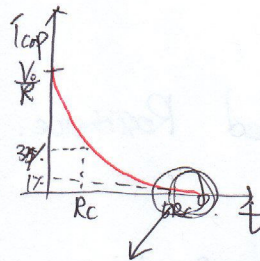

high Resistance ( $\infty$ )  
= "disconnected"

| R          | C             | R-C           |
|------------|---------------|---------------|
| k $\Omega$ | $\mu\text{F}$ | $10^{-3}$ sec |
| M $\Omega$ | $\mu\text{F}$ | 1 sec         |

if  $V_0 = \text{A.C. input?}$

$$V(t) = \sum V_i e^{j\omega_i t}, \quad i=0, 1, 2, \dots, \infty$$

$\Rightarrow$  general form of Voltage

1) Resistor

$$V(t) = \text{A.C.}, \quad i = \frac{V(t)}{R} = \frac{V}{R}$$

$\Rightarrow$  AC or DC?  $\frac{1 \text{ Hz} \times \dots}{\text{No matter}}$

$$\frac{V}{i} = \text{generalized Resistance} = R (\Omega)$$

2) Capacitor



$$V(t) = V_0 e^{j\omega t}, \quad \omega > 0$$

$$i = \frac{dV}{dt} [V_{cap}]$$

$$= j\omega V_0 e^{j\omega t} = j\omega \cdot V(t)$$

$$\frac{V}{i} = \text{Reactance} = \text{Generalized Resistance.}$$

$$= \frac{1}{j\omega C}$$

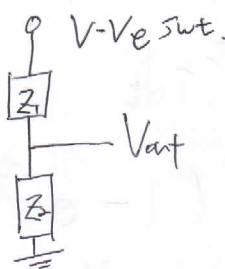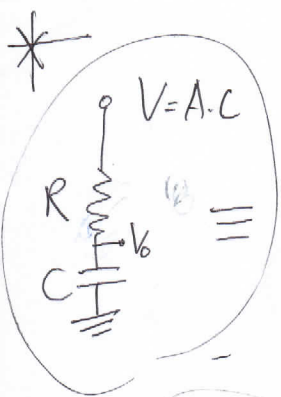

$$\left. \begin{aligned} Z_1 &= R \\ Z_2 &= \frac{1}{j\omega C} \end{aligned} \right\} \text{Generalized Resistance.}$$

$$\frac{V_{out}}{V_{in}} = \frac{Z_2}{Z_1 + Z_2} = \text{Generalized Voltage Divider.}$$

if  $\omega = 0$ ?

$$V(t) = V_0 e^{j\omega t} \rightarrow \text{D.C., } \frac{V}{I} \rightarrow \infty \rightarrow -90^\circ$$

if  $\omega = \infty$ ?  $\rightarrow \frac{V}{I} = 0$ .

$\rightarrow$  frequency dependent.  
 $\rightarrow$  Capacitor behavior.



$\therefore$  filtering, Blocking, Smoothing are possible.!!

$$\begin{aligned} \frac{V_{out}}{V_{in}} &= \text{Transfer fct.} \\ &= \frac{Z_2}{Z_1 + Z_2} = \frac{1/j\omega C}{R + 1/j\omega C} \end{aligned}$$

$$= \frac{1}{1 + j\omega RC}$$

$$\left| \frac{V_{out}}{V_{in}} \right| = \frac{1}{\sqrt{1 + (\omega RC)^2}}$$
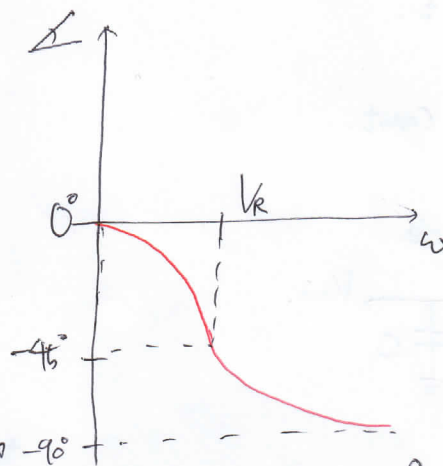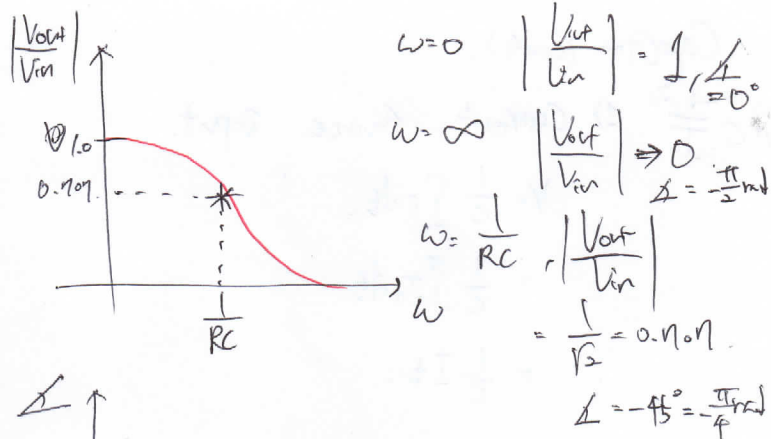
$$\angle \frac{V_{out}}{V_{in}} = \tan^{-1}(\omega RC).$$



\* Low Pass filter.

Signals of low frequency  
Can Pass

Signals of high freq.  
Cannot Pass.

At  $\omega = 1/RC$ ,

$$\left| \frac{V_{out}}{V_{in}} \right| = 0.707 = 70.7\%$$

(Engineer Compromise)

$$-20 \cdot \log_{10} \left| \frac{V_{out}}{V_{in}} \right| \stackrel{\text{def.}}{=} \text{dB}$$


$$-10 \cdot \log_{10} \left| \frac{P_{out}}{P_{in}} \right| \stackrel{\text{def.}}{=} \text{dB}$$

When  $\left| \frac{V_{out}}{V_{in}} \right| = 0.707 = \frac{1}{\sqrt{2}}$   
 $-20 \log_{10} \left| \frac{V_{out}}{V_{in}} \right| = 3 \text{ dB}$   
 $\therefore \frac{1}{RC}$  is called  $\omega_{3dB} = \frac{1}{RC}$



ea) Design a LPF
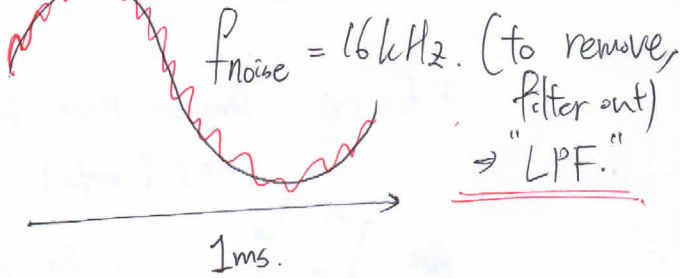
$$f_{\text{signal}} = 1 \text{ kHz (expect)}$$



$$\therefore R = 10 \text{ k}\Omega.$$

$$C = 1.5 \times 10^{-8} \text{ F} \quad \text{slightly distasteful.}$$

$$\approx \frac{2.0 \times 10^{-8} \text{ F}}{1.0 \times 10^{-4}} \quad \text{Commercially available (buy)}$$

3. Verification.


$$f_{\text{noise}} = 16 \text{ kHz} \Rightarrow \omega_{\text{noise}} = 2\pi f_{\text{noise}}$$

1. Freq identification.

$$f_{\text{signal}} = 1 \text{ kHz}, f_{\text{noise}} = 16 \text{ kHz}.$$

$$\left| \frac{V_{\text{out}}}{V_{\text{in}}} \right| = \frac{1}{\sqrt{1 + (\omega RC)^2}} \approx 0.06.$$

6%

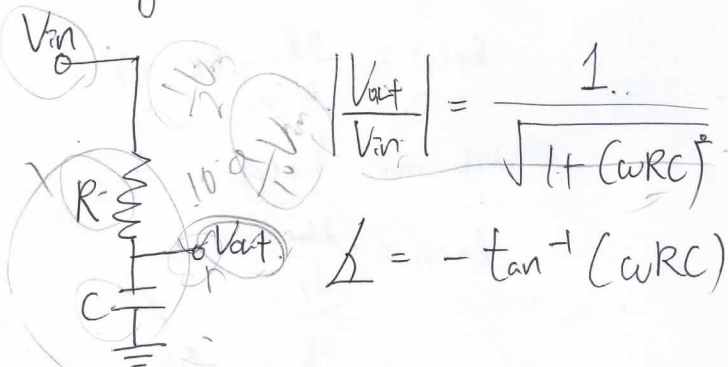

$$\Delta = -\tan^{-1}(\omega RC) = -89.1^\circ$$

$$f_{\text{signal}} = 1 \text{ kHz}.$$

$$\left| \frac{V_{\text{out}}}{V_{\text{in}}} \right| = \frac{1}{\sqrt{1 + (\omega RC)^2}} = 0.623.$$

(≠ 0.707) Why?

"because we choose  $2.0 \times 10^{-8} \text{ F}$  capacitor."

2.  $f_{\text{signal}} \equiv f_{\text{3dB}}$

$$1000 \text{ Hz} = 2\pi (1000) [\text{rad/sec}].$$

$$= \omega_{\text{signal}}.$$

$$\omega_{\text{3dB}} = 2\pi \cdot f_{\text{3dB}} = \omega_{\text{signal}}.$$

$$= \frac{1}{RC} \text{ by LPF.}$$

$$= 2\pi (1000) = 6280 \dots \text{①}$$

$$\Delta = -\tan^{-1}(\omega RC)$$

$$= -51.4^\circ (\neq -45^\circ)$$

4. Signal to Noise (S/N) Ratio.

Before LPF      After LPF.

$$S = 1.0$$

$$S = 0.623.$$

$$N = 1.0$$

$$N = 0.06.$$

$$S/N = 1$$

$$S/N = 10.3$$

$\therefore S/N$  ratio is 10.3 times improved.

