
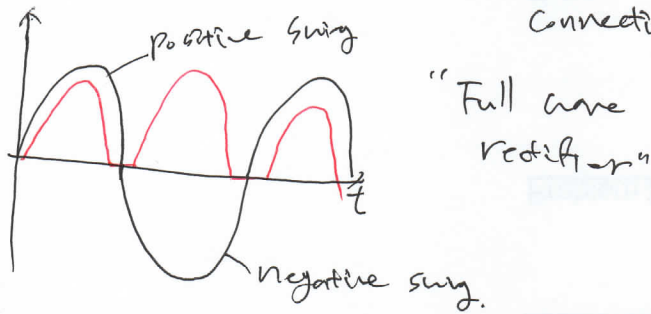
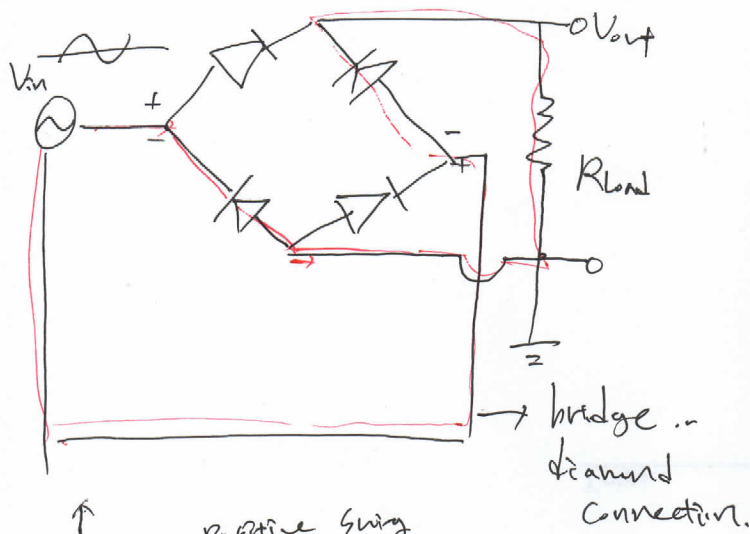


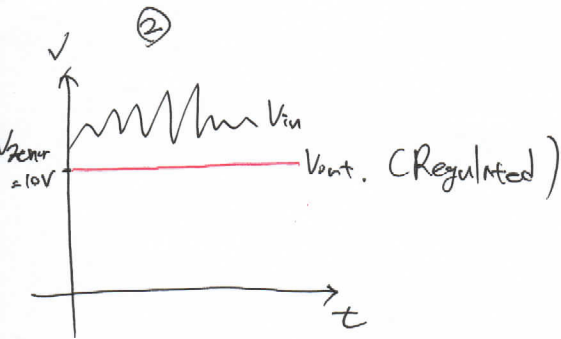

"Most important application
of Diode, Power Supply"


Power supply design

Spec) $V_{in} = 110V @ 60Hz$

$V_{out} = 20V \text{ (DC)}$

$\Delta V = V_{ripple} = 10\% \text{ of } V_{out}$
 $= 2V$

$I_{max} = 1A$

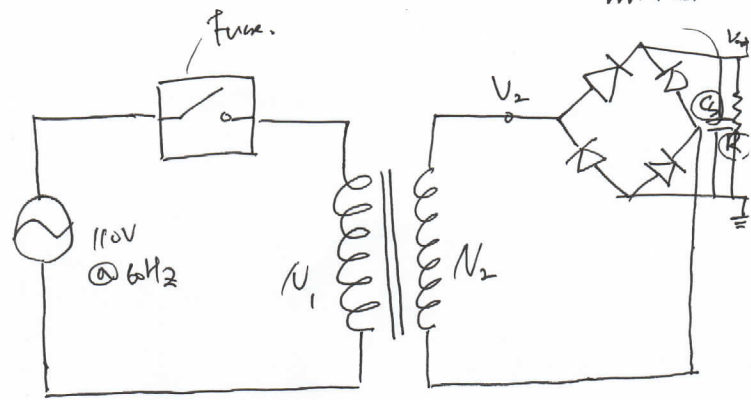

1. $N_1 : N_2$

$$N_1 : N_2 = V_1 |_{rms} : V_2 |_{rms}$$

$$= 110V : V_2 |_{rms}$$

$$V_2 |_{rms} = \sqrt{\frac{1}{T} \int_0^T V_{(t)}^2 dt}$$

$$= \frac{1}{\sqrt{2}} V_{-} |_{peak}$$

$$V_{-} |_{peak} = V_{out} + V_{ripple} + V_{prp}$$

$$= 20V + 2V + 2 \times 0.6V$$

$$= 23.2V$$

$$V_2 |_{rms} = \frac{1}{\sqrt{2}} V_{-} |_{peak} = 16.2V$$

$$N_1 : N_2 = 110 : 16.2 \approx 55 : 8$$

2. $V_2 |_{peak} = 23.2V$, $I_{max} = 1A$

$$\Rightarrow 1 \mu 9/4 m.dol.$$

3. C_s : Smoothing Capacitor

$$I = C_s \frac{dV}{dt} = C_s \frac{\Delta V}{\Delta t}$$

$$I = I_{max} = 1A, \Delta V = V_{ripple} = 2V$$

$$\Delta t = \frac{1}{120} \text{ sec. } C_s = \frac{I}{\Delta V / \Delta t}$$

$$= 4mF$$

③

4. Bleeding Resistor
→ "safety reason"

$$R_B C_S = \frac{\text{Time for bleeding}}{1} \\ = 4 \text{ sec. (given)}$$

$$R_B = 1k.$$

5. Fuse rating current.

$$I_1 V_1 = I_2 V_2$$

$$I_1 (110V) = (1A) (16V)$$

$$I_1 = 140 \text{ mA.}$$

$$\text{Fuse rating current} = S_2 \times S_1 \times I_1$$

S_2 : safety for S
= 4 times for

HWT. Design a V.G. (cheap small ripple benchtop) power supply

$$V_{in} = 240V \text{ @ } 50Hz.$$

$$V_{out} = 5V$$

$$I_{max} = 1A \rightarrow \text{design it!}$$

$$V_{ripple} = 10\%$$

Diode.



→ ok Normal flow
← x Reverse flow

Laws

$$1. \vec{Z} (Z \uparrow) = 0$$


$$\vec{Z} (Z \downarrow) = \infty$$

⇒ Direction control for current.

$$2. V_{out} = V_{in} - 0.6V \text{ When current flows.}$$

$$\Rightarrow \Delta V_{out} = \Delta V_{in}$$
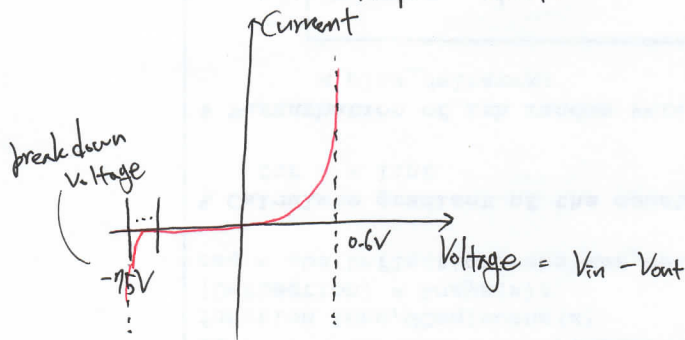
$$0.6V = \text{Diode Prop.} = \text{Const.}$$



I-V relationship for diode.

Application.



- current diode Valve.
(Safety Circuit)
forward flow allowed.
reverse flow prohibited.

2. Clamper.



To pick up the range of Voltage
 $V_{in} \neq V_{out} \leq V_c$

3. Rectifier AC to DC.

4. Voltage source. ($\neq$ Power supply)

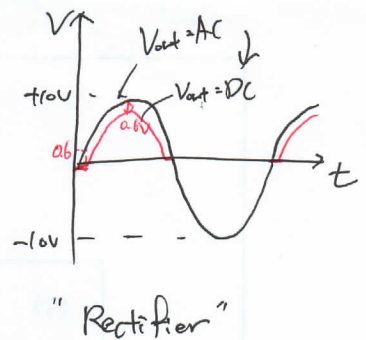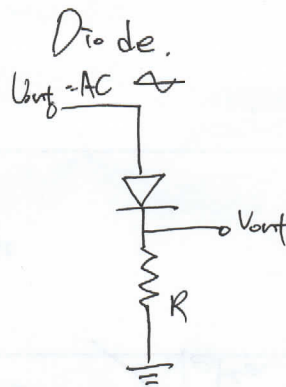



"Halfwave rectifier"

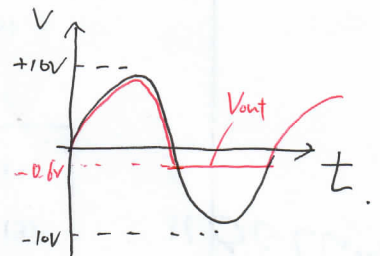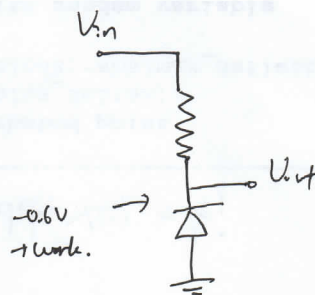

$$\frac{V_{out}}{V_{in}} = \frac{Z_1}{Z_1 + Z_2} = \frac{\infty}{R + \infty} = 1.$$


$$-10V \leq V_{in} \leq +10V$$

$$-0.6V \leq V_{out}$$

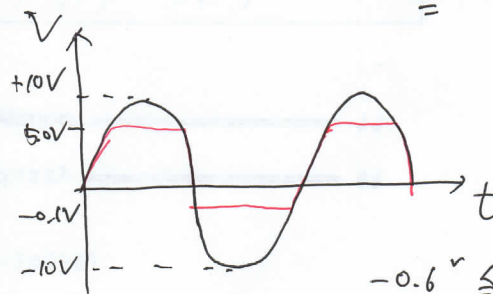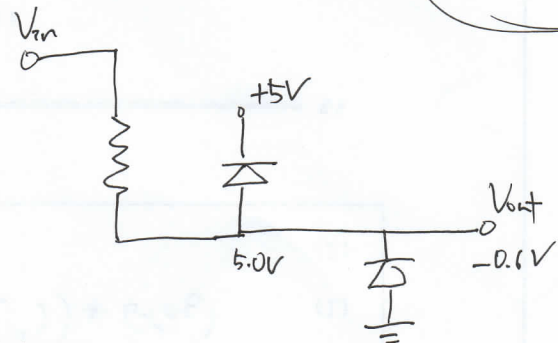

$$-0.6V \leq V_{out} \leq 5.0V$$

"clamper"

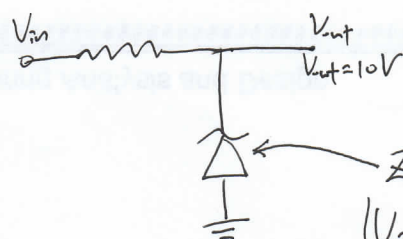

Zener diode.
 $|V_{Z_{max}}| < 75V.$

Breakdown voltage

$$|V_{Z_{max}}| = 10V, 12V,$$