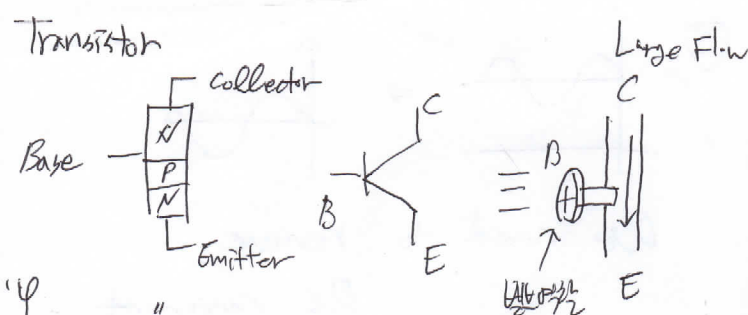


1



"4 Laws"


- $V_C > V_E$ ($V_C - V_E \geq 0.2V$)
for current flow
- $V_B - V_E = \text{Const} = 0.6V$
when current flows.
- $I_C \approx \beta \cdot I_B$, $I_E \approx I_C + I_B$
 $\approx (\beta + 1) I_B$
 $\approx \beta I_B$ (1% error)

Application

1) Current Source.

To generate constant current

* Power supply.

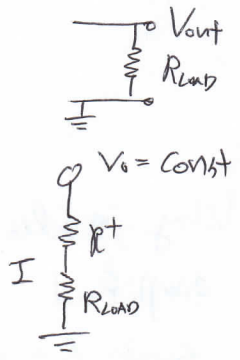


$$I_{LOAD} = \frac{V_0}{R_{LOAD}} \neq \text{const} = f(R_{LOAD})$$

$$I_{LOAD} = \frac{V_0}{R + R_{LOAD}}$$

$$= \frac{V_0}{R \left(1 + \frac{R_{LOAD}}{R}\right)}$$
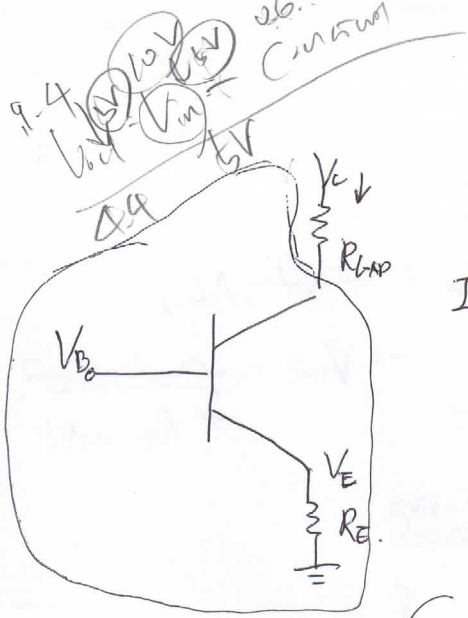
$$\approx \frac{V_0}{R} \text{ (if } R \gg R_{LOAD})$$




$$I_{LOAD} = I_C \approx I_E = \frac{V_E}{R_E}$$

$$= \frac{V_B - 0.6V}{R_E}$$

$\neq f(R_{LOAD})$

= Const = Current supply

2) Emitter follower

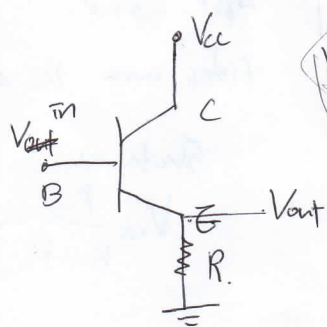

$$V_{out} = V_E = V_B - 0.6V$$

$$= V_{in} - 0.6V$$

$$\therefore \Delta V_{out} = \Delta V_{in}$$

" Gain = $\frac{\Delta V_{out}}{\Delta V_{in}} = 1$

$$I_E \approx I_C = \beta \cdot I_B$$

$$\therefore I_{out} = \beta \cdot I_{in}$$

(11/1) (WEP)

β times current ~~Mag~~ Amplification

small current \rightarrow Large current.


3) To drive RLOAD

Z_{in} = Input Impedance

to Emitter follower

$$Z_{in} = Z_B = \frac{\Delta V_B}{\Delta I_B} = \frac{\Delta V_E}{\frac{1}{\beta} \Delta I_E} = \beta \left(\frac{\Delta V_E}{\Delta I_E} \right)$$

$$= \beta R' = \beta R$$

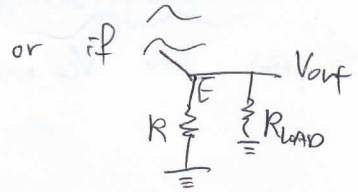



\rightarrow "Very High Z_{in} is ideal" $\approx R (R_{LOAD} \gg R)$
 \rightarrow for driver current (10X Rule)

What happen?


When $V_{in} = \text{AC}$,

$\rightarrow V_{out} = \text{AC?}$
 \rightarrow No out!!

We need Biassing.

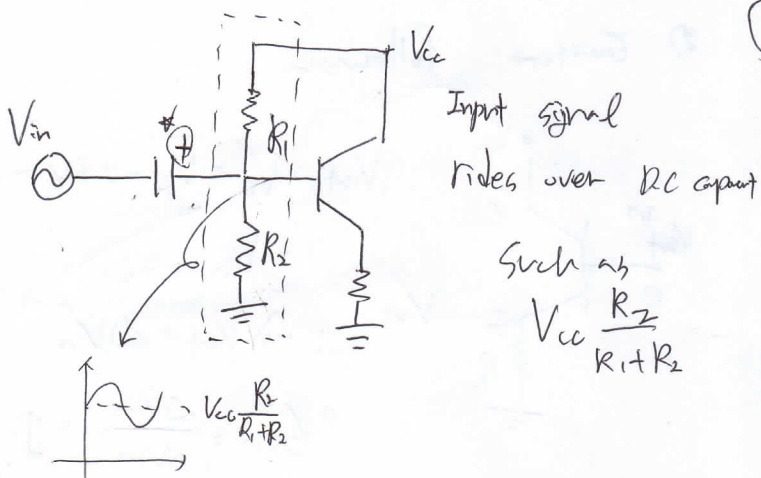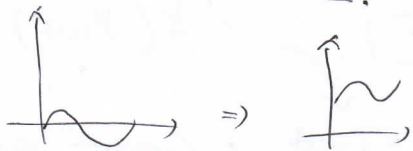

Blocking Capacitor

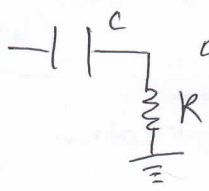


Smoothing capacitor
 \rightarrow parallel connection

\Rightarrow a kind of HPF.

Passing $\omega \gg \omega_{dB} = \frac{1}{RC}$

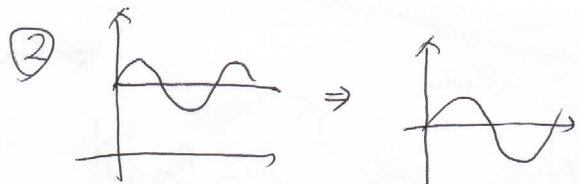Biassing: To pull TR's Quiescent Voltage $\overset{=0}{}$ to mid point both V_{cc} and GND.




We need to remove D.C component.

\rightarrow put blocking capacitor (C_2)


Passing $\omega \gg \omega_{dB} = \frac{1}{RC}$

3) Emitter follower with split supply

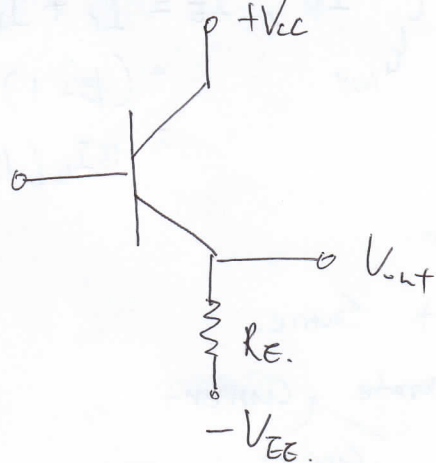

$+V_{cc}, -V_{cc} \rightarrow$ split supply.

3)

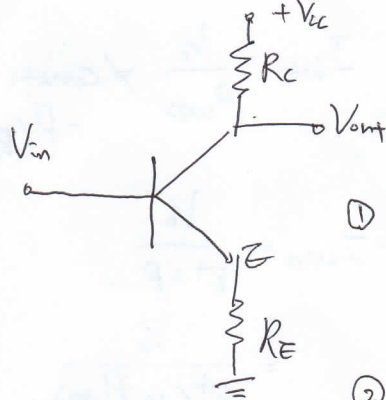

1) Voltage is also amplified

such $G = -\frac{R_C}{R_E}$

2) $I_{out} = \beta I_{in}$

3) $V_{out} = V_{cc} - I_C R_C$
 $I_E = \frac{V_E}{R_E} = \frac{V_{in} - 0.6V}{R_E}$

$\therefore V_{out} = V_{cc} - \frac{R_C}{R_E} (V_{in} - 0.6) = -\frac{R_C}{R_E} \Delta V_{in}$