

VLSI-based Implementation of Digital Signal Processing Systems

Wonyong Sung

School of Electrical Engineering
Seoul National University

Contents

1. Architectures for DSP Systems
2. High-speed Parallel Architecture
3. Time-multiplexed (bit-parallel) Architecture
4. Bit-serial Architecture
5. Distributed Arithmetic-based Architecture
6. CAD and Implementation Architecture

1. Architectures for DSP Systems

❖ Requirements for DSP system implementation

- Correct operation (algorithm level)
- Speed (throughput)
- Low chip area and power consumption (cost)
- Fast and low-cost design, design flexibility (design upgrade, portability)

❖ Custom VLSI (HW based) vs Programmable DSP (SW based)

- HW based for higher throughput
- Large initial investment for VLSI
- Low power and low chip cost for large volume VLSI

Custom VLSI vs Programmable DSP

- ❖ **Large initial investment, but small cost for each chip – good for large volume**
 - Needs to be ~ 1M units or over in most cases
 - FPGA based designs are alternatives for small quantities
- ❖ **High-throughput architecture, highly optimized for each application**
 - Inflexible in most cases
- ❖ **Low-power consumption when compared to program based architecture**
- ❖ **CPU + peripheral + application specific HW -> SOC (System On Chip), platform based design**

Issues in VLSI based system design

- ❖ **BW matching between the difference of the signal sampling clock frequency and the system clock frequency**
 - Reduce the number of hardware elements when the signal sampling frequency is small.
 - Full array architecture: high hardware cost, high throughput
 - Time multiplexed architecture
 - Bit serial architecture: low hardware cost, low throughput

Characteristics of DSP algorithms

❖ Arithmetic intensive

- ex) FIR filter order of 60, 10 MHz
multiplication, addition 600 Mop/sec.

❖ In most cases, $f_{\text{system}} \gg f_{\text{sampling}}$

- f_{system} (system clock frequency): mostly 10MHz ~ 1GHz
- f_{sampling} (sampling clock frequency):
 - Speech and Audio: 8KHz ~ 100KHz
 - Video: 10MHz ~ 100MHz

Algorithm v.s. System

❖ Algorithm

- Operating at a rate of sampling clock freq.
- Sample delay: z^{-1} ($= 1/f_{\text{signal}}$)
- Arithmetic: multiplication, addition operations
- Corresponds to the clock freq to ADC or DAC

❖ System (Hardware)

- Clock for digital systems
- Arithmetic: multipliers or adders
- Delay: D-FF ($= 1/f_{\text{system}}$)

$f_{\text{signal}} = f_{\text{system}}$: full array architecture

$f_{\text{signal}} > f_{\text{system}}$: hyper parallel architecture

$f_{\text{signal}} < f_{\text{system}}$: time-multiplexed architecture

Bandwidth matching

❖ Compensates for the difference of system and signal frequencies to better utilize the resources.

- For example, 10 tap FIR filtering and 4th order IIR filtering (2*5 multiply operations) with 10MHz sampling clock frequency:
 - Needed multiplications: $10 \times 10\text{M} + 2 \times 5 \times 10\text{M} = 200\text{M/sec}$
- Assuming that system clock frequency is 100MHz, only two multipliers are needed.
- 20 multiply operations with 10MHz
–BW matching-> 2 multipliers with 100MHz

Note: Another important factor determining the architecture: algorithm complexity. When the algorithm is too complex, it would be very difficult to implement using a custom VLSI architecture.

Methods of BW matching

❖ **$f_{\text{signal}} \geq f_{\text{system}}$**

- Algorithm transformation to increase the f_{system} (pipelining)
- Parallel (or block) processing to obtain multiple output samples per each system clock.

❖ **$f_{\text{signal}} < f_{\text{system}}$**

- Use one HW unit for multiple operations (time-multiplexed architecture)
- Use simple but slow arithmetic units (bit serial architecture)


Implementation architectures

- ❖ **Fully serial:** Use only one processor, program based implementation (ultimate time-multiplexed implementation)
- ❖ **Time multiplexed:** Utilize one hardware unit (multiplier, adder) several times during one sampling period. Hardware delay \ll sampling period
- ❖ **Bit serial architecture:** Utilize one slow hardware unit (bit serial arithmetic components) only one or a few times during one sampling point.
- ❖ **Full array:** $f_{\text{signal}} = f_{\text{system}}$, use one arithmetic elements for each arithmetic operation
- ❖ **Hyper-parallel:** $f_{\text{signal}} \geq f_{\text{system}}$
Needs to transform the algorithm, use multiple or pipelined elements for each operation

Time-multiplexed operation

- ❖ **Bit-parallel arithmetic elements, operation time-muxed**
 - processes one word of signal at one clock, but sequentially conducts different operations
 - needs parallel multipliers, adders, and memory
 - needs fairly complex control and address generation
- ❖ **Bit-serial simple arithmetic elements, operation dedicated**
 - processes one bit of signal at one clock using a dedicated one-bit arithmetic or memory elements
 - almost hardwired (simple) control
 - efficient implementation, limit in throughput

Applications and architectures

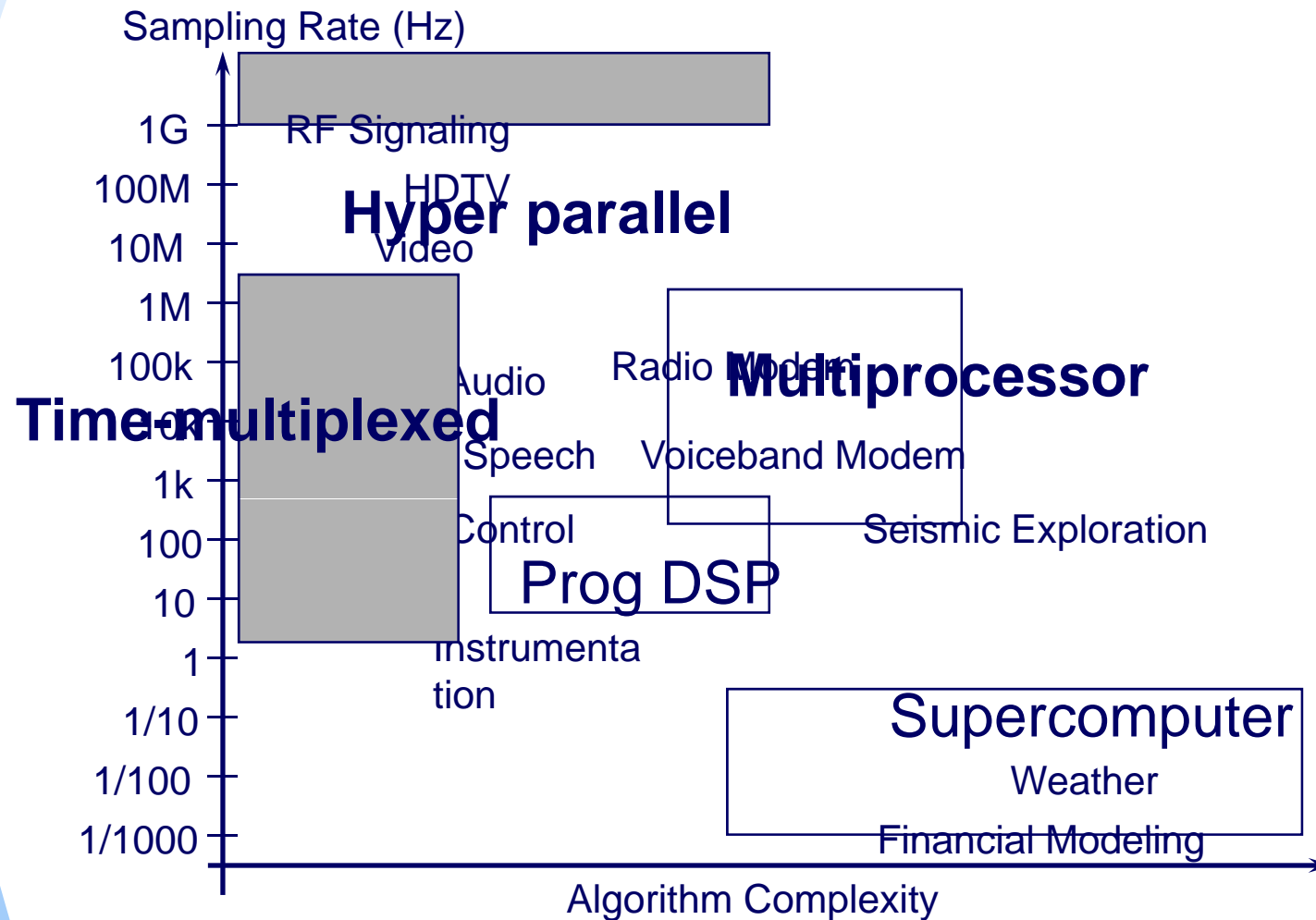

Algorithm complexity v.s. architectures

❖ For simple but repeating blocks

- Digital filter, FFT
- hardwired control
- efficient hardware and VLSI implementation

❖ For complex algorithms

- Speech, audio, data modem
- program controlled is advantageous
- programmable DSP based implementation

2. High-speed Parallel Architecture

❖ Full array implementation architecture

- Sampling rate = system clock rate
- Mostly high-bandwidth RF
- Signal flow graph – (**retiming**) -> Hardware schematic
 - Addition or multiplication operations -> adder, multiplier
 - z^{-1} -> D-FF
- Speed limitation: circuit delay from the output of D-FF (or input port) to input of the D-FF (the output). -> retiming equalizes the delays and minimizes the maximum of them
- No scheduling for HW resource minimization needed

Speed limitation?

❖ Is it right?


- For a given signal flow graph, the throughput can be increased without any limit as long as enough HW resources are available.
- If there is no loop (circle) inside, it is yes.
- If not,...


- In terms of resource hazard, this may be right.
- But, what is another kind of hazard?

Full array architecture and speed limitation

❖ 1st order IIR digital filter

 
- Path 1: T_{add} (10 ns)
- Path 2,3: $T_{\text{add}} + T_{\text{mul}}$ (30 ns) = 40 ns <- critical path delay, this determines the maximum clock freq.



 


Implementation 1:
critical path delay: 40ns

$$H[z] = 1/(1-az^{-1})$$

 

Implementation 2:
critical path delay: 40ns


$$H[z] = 1/(1-az^{-1})$$

 

Implementation 3:
critical path delay: 40ns

$$H[z] = z^{-1}/(1-az^{-1})$$

 Different transfer function but the same frequency response. Zero at the center does not affect the f.r.



Implementation 2:
Critical path delay: 20ns

$$H[z] = 1/(1-az^{-2}) \leftarrow \text{different filter!}$$

Max operating frequency of a signal flow graph and equivalence transform

- ❖ The number of delay in a loop (N), the total circuit delay (T_a) \Rightarrow Theoretical min iteration period (after retiming) (Iteration Period Bound): T_a/N
- ❖ For multiple loops, the largest delay determines the maximum clock frequency \leftarrow critical loop
- ❖ Retiming : move the location of delays to reduce the critical path delay (doing equivalence transform)


Longest path matrix algorithm

- ❖ Find out the total circuit delays from an output of a storage (D) to the input of another one. And find out the max (circuit delay/#of_delays).
- ❖ Start with constructing $L^{(1)}$ matrix
 - $I^m(i,j)$ is the longest computation time of all paths from delay d_i to delay d_j that path through $m-1$ delays.
 - From $L^{(1)}$ matrix, compute $L^{(2)}$ $L^{(3)}$ $L^{(4)}$
 - $L^{(m+1)}_{i,j} = \max (-1, I^{(1)}_{i,k} + I^{(m)}_{k,j})$
 - $T = \max (\text{for all } i, m) \{I^m(i,i)/m\}$, (diagonal elements)

Equivalence transform

- ❖ Move the location of delays while not changing the transfer function and the finite wordlength effects of digital filters. -> this changes the critical path delay in many cases
- ❖ For a certain directed graph, make a closed loop so that it just cut the branches (not any node), and add d_0 delays to branches that are going out and subtract d_0 delays to branches that are going in. In this case, the total number of delays for any loop is not changing, and, as a result, the transfer function is not altered.
- ❖ If the above closed loop pass through a loop in a signal flow graph, the number of delays added equals to the one that are subtracted. -> The total number of delays for a loop is unchanged. -> The transfer function is preserved.
- ❖ For a feedforward path, the closed loop inserts delays, but the number to each path to the output is the same, as a result, the output just comes later as much as the number of delays added.

2nd order IIR filter

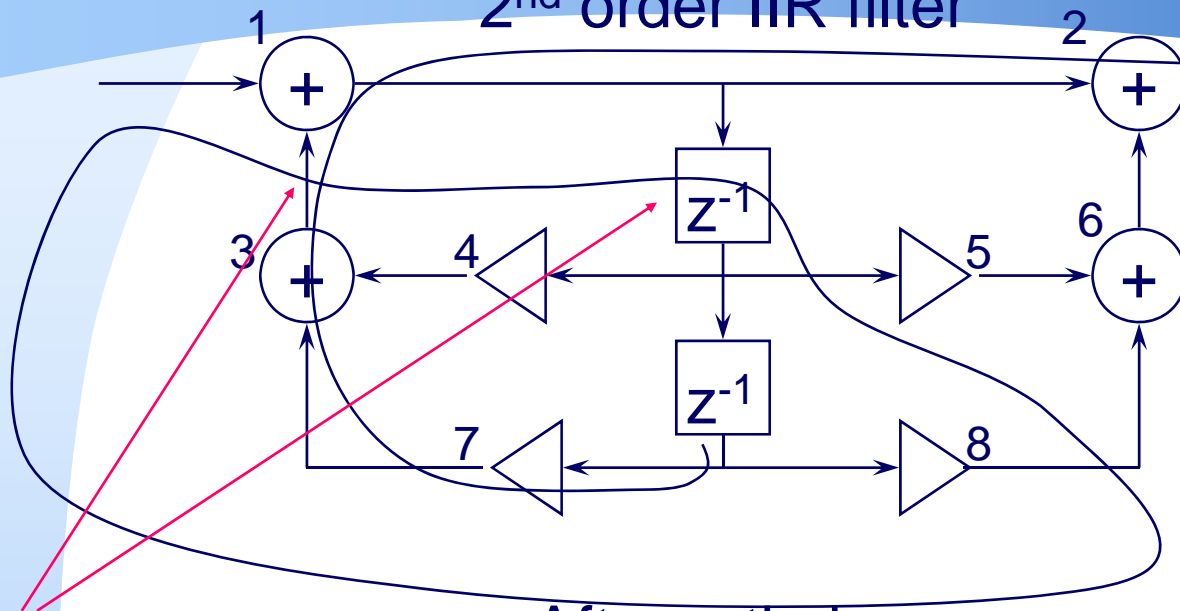


Canonical form:
Minimum # of
storages

Critical path
delay : $T_{mul} + 3T_{add}$

After retiming

Delay added or subtracted
to a loop




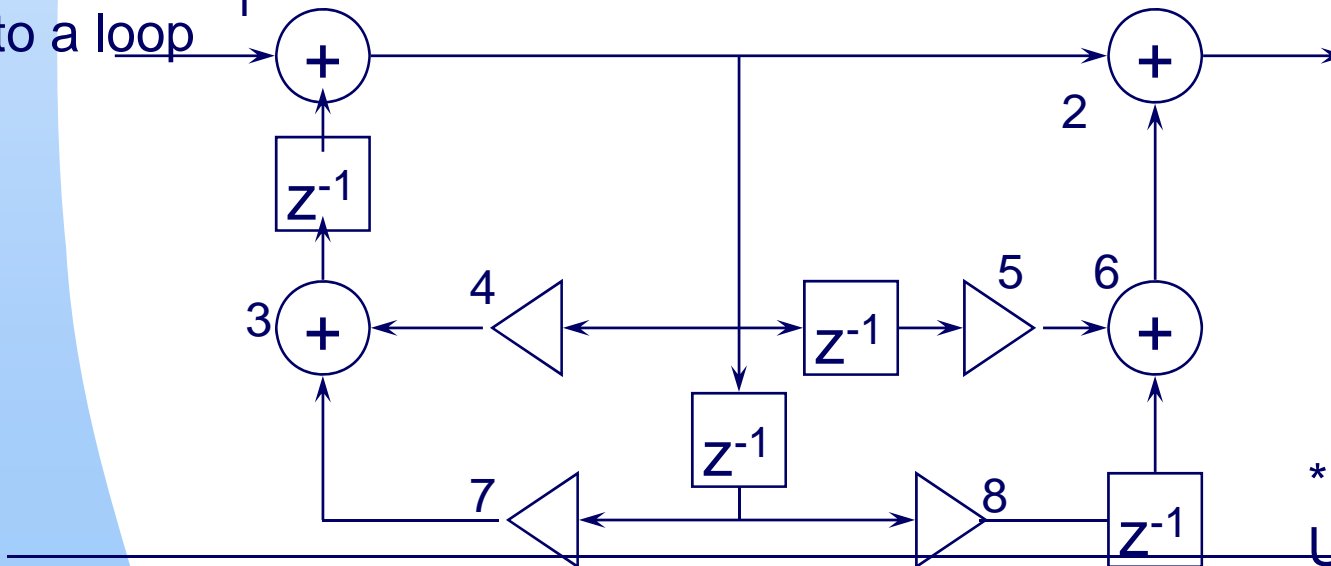


Critical path
delay : $T_{mul} + 2T_{add}$

*More registers are
Used! Not canonical


Pipelining

    - ❖ Increasing the speed by inserting delays inside
- ❖ Throughput : the rate of applying periodic input
- ❖ Latency : the delay from the input to the corresponding output




Effects of pipelining

 - Throughput is more important than the latency in real-time signal processing.
- The throughput is increased by pipelining but not the latency
- For feedback based system, the pipelining may change the transfer functions.
- Usually, pipelining in the feed-forward path is OK.
(add delays and retiming)




- Full array implementation example of an N-tap FIR filter
 
$$\text{Max delay} = T_{\text{mul}} + N T_{\text{add}}$$



 
$$\text{Max delay} = T_{\text{mul}} + T_{\text{add}}$$



Hyper parallel implementation(1)



- ❖ Is it possible to increase the speed (sampling clock freq.) beyond the iteration period bound?
 - Yes. By applying the look-ahead transformation.
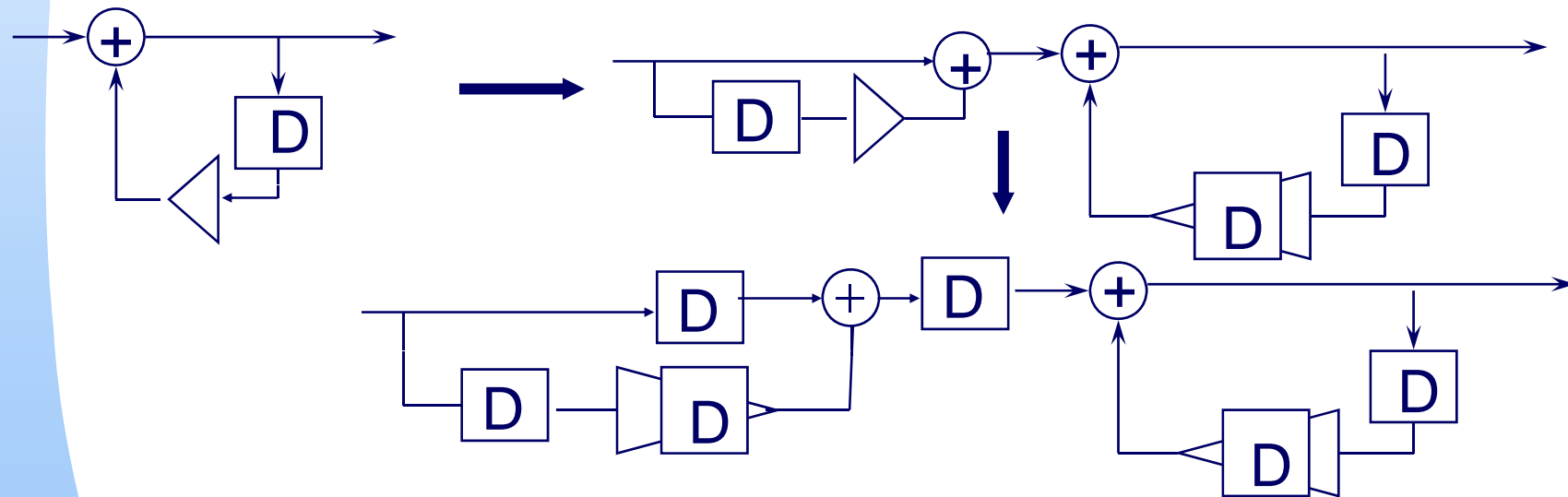
$$H(z) = 1 / (1 - az^{-1}) = (1 + az^{-1}) / (1 - a^2z^{-2})$$



The total number of multiplication is increased.
Quantization effects are different.

Hyperparallel implementation(2)

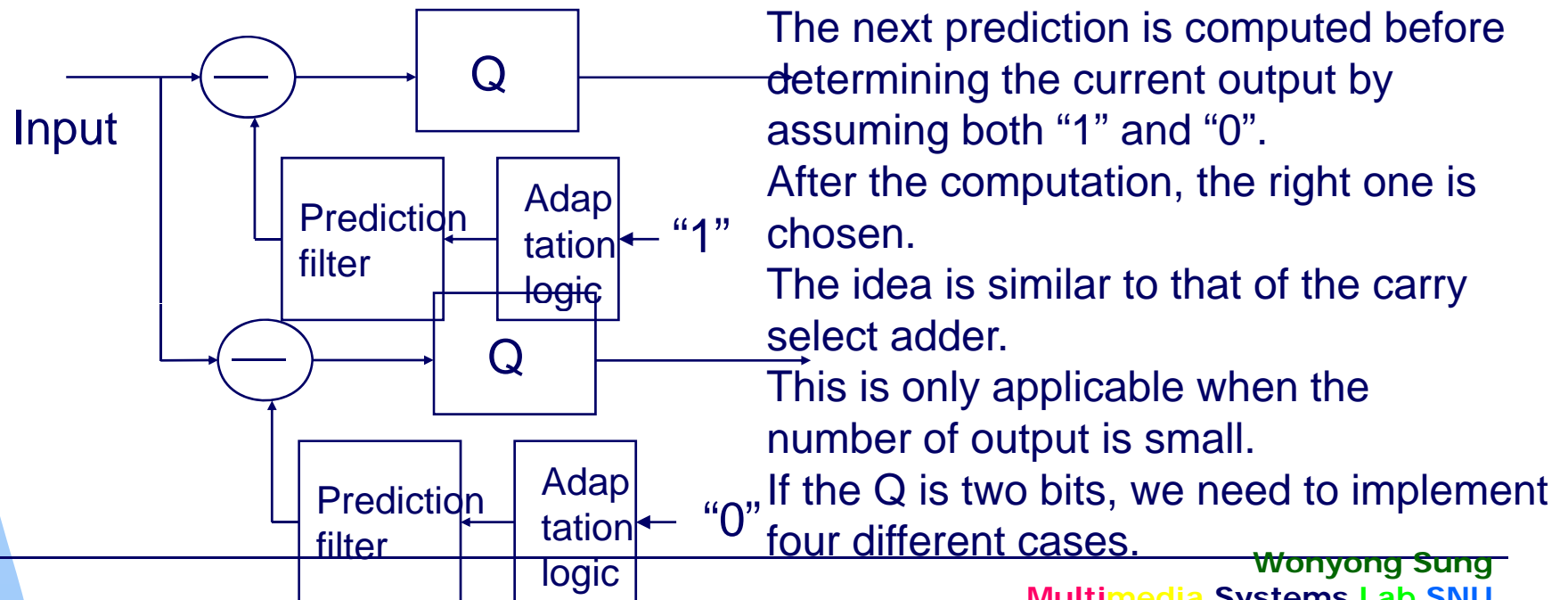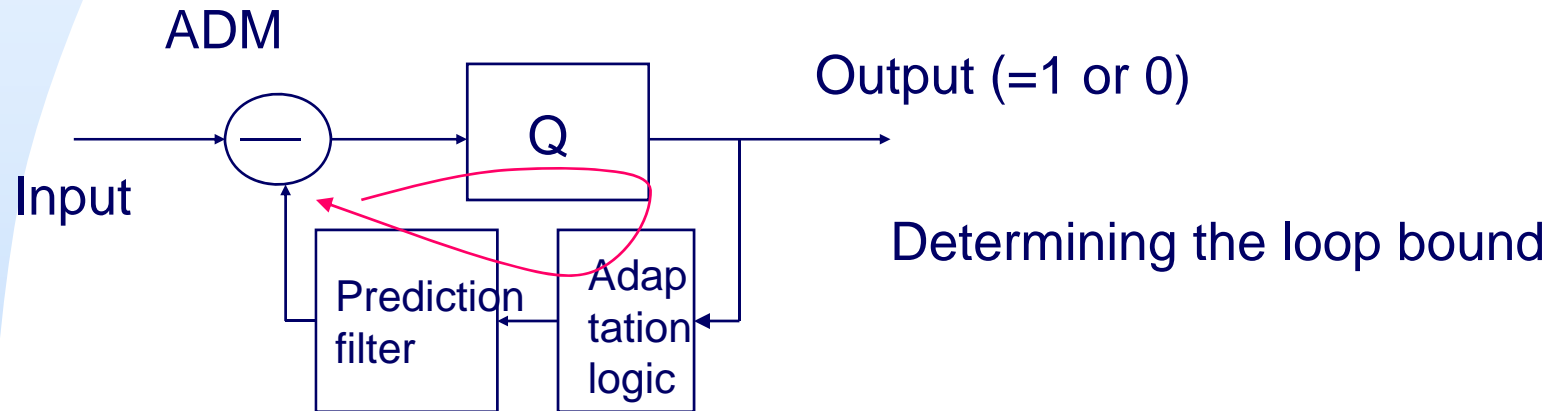

CSD (Canonic Signed Digit) coefficients based FIR filter

- ❖ Reduces the complexity of constant multiplications
 - One multiplication is converted to a few (one to three, usually) addition/subtractions.
- ❖ Represent the coefficients with +1/-1/0 and try to increase the number of zero's.
 - 00111111 \Rightarrow 0100000(-1) : effective coefficients word-length is 2
- ❖ May increase the passband and stop band ripples when the number of '1' is limited.
- ❖ Only applicable to full-array (not for time-multiplexed) implementations.

3. Time-multiplexed Architecture (Folded Architecture)

- ❖ **System frequency > Sampling frequency**
 - Use a smaller number of arithmetic elements than that of the arithmetic operations
 - Ex: 10MHz sampling frequency, 30 tap FIR filter
 - With the system clock of 50MHz, the minimum number of HW would be 6.
 - With the system clock of 100MHz, the minimum HW would be 3.
 - More HW resources are needed in many cases.
 - Dependency relation which forces some units underutilized
 - Unequal job allocation
 - Internal signal delay (interconnection delays)

Design methods for time-muxed architecture

❖ Scheduling based method

- Start from a data flow graph, consider the HW resource and time-bound.

❖ Utilizing the iterative structure

- 12th order IIR filter using 2nd order section
- Use 6-times time-multiplexing of one 2nd order section

❖ Program based method

- Flexible but needs program memory storage

Scheduling algorithm

- ❖ **Unconstrained minimum-latency scheduling**
 - ASAP (As Soon As Possible)
 - ALAP (As Late As Possible)
- ❖ **Resource-constrained minimum-latency (or Latency-constrained minimum-resource) scheduling**
 - List scheduling
 - Force-directed scheduling
- ❖ **Example (Euler's method for solving differential equation)**

$$y'' + 3xy' + 3y = 0$$

initial value: $x(0), y(0), y'(0)$

$$y(a) = ?$$

stepsize = dx

$$x_{i+1} = x_i + dx$$


$$u = y'$$

$$u' + 3xu + 3y = 0$$

$$u_{i+1} = u_i + u'_i dx = u_i - 3x_i u_i dx - 3y_i dx$$

$$y_{i+1} = y_i + y'_i dx = y_i + u_i dx$$

 ❖ Data flow graph for a differential equation




$$xl = x + dx;$$

$$ul = u - (3 * x * u * dx) - (3 * y * dx);$$

$$yl = y + (u * dx);$$


$$c = xl < a;$$

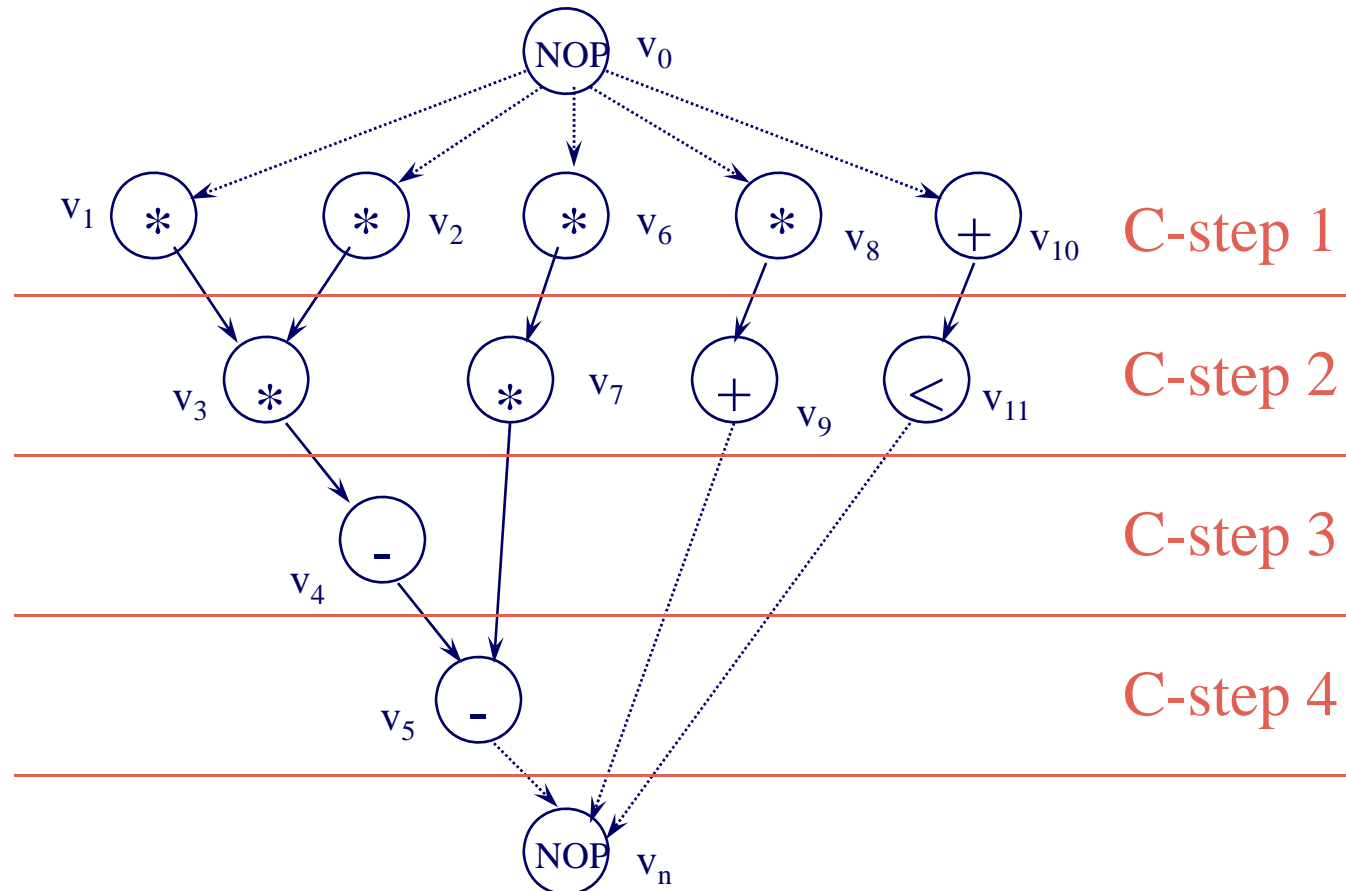❖ **ASAP (As Soon As Possible) scheduling – unconstrained minimum latency**




4 steps, 5 units needed (C-step1 needs 5 units)

❖ ALAP (As Late As Possible) scheduling

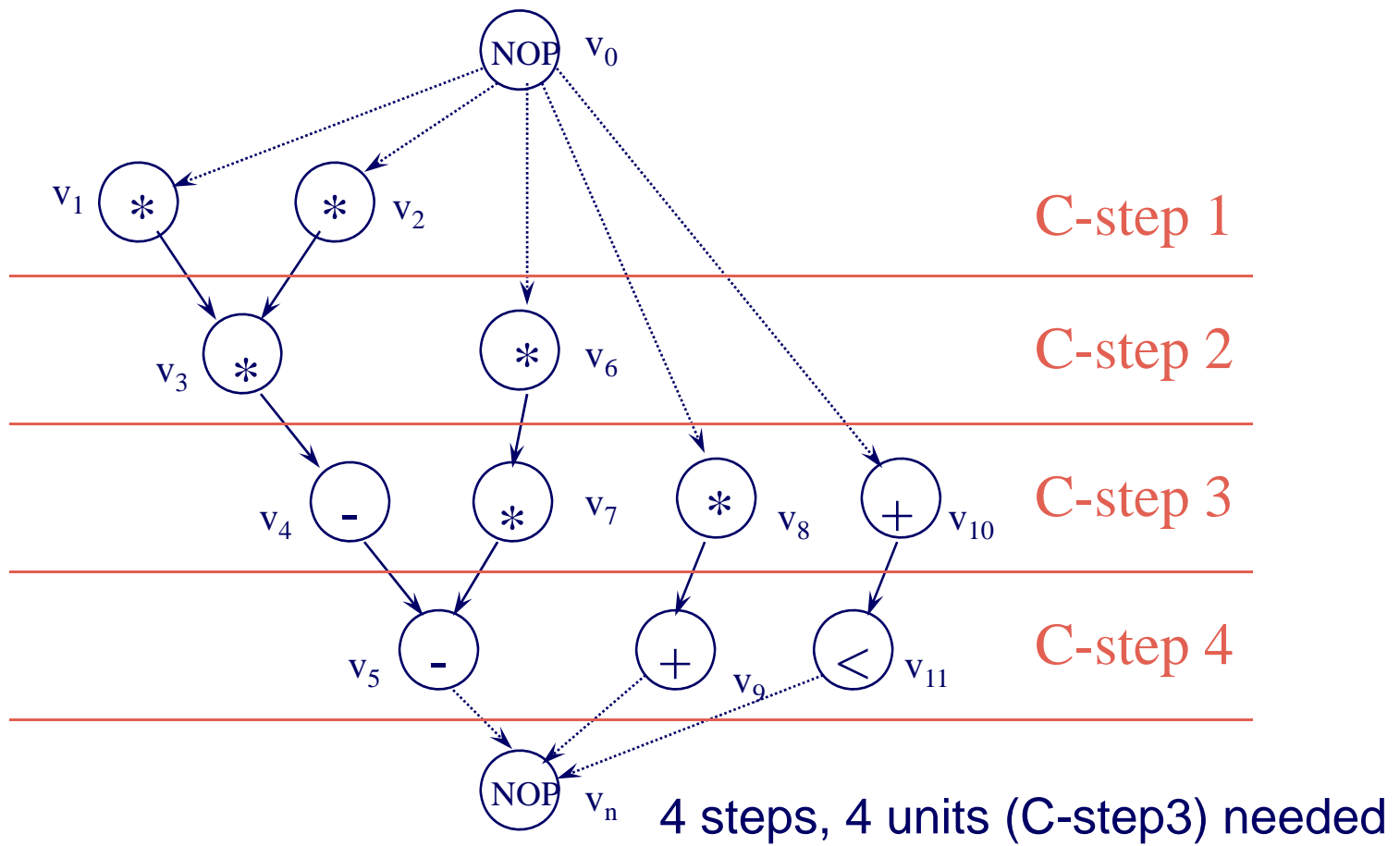

Mobility

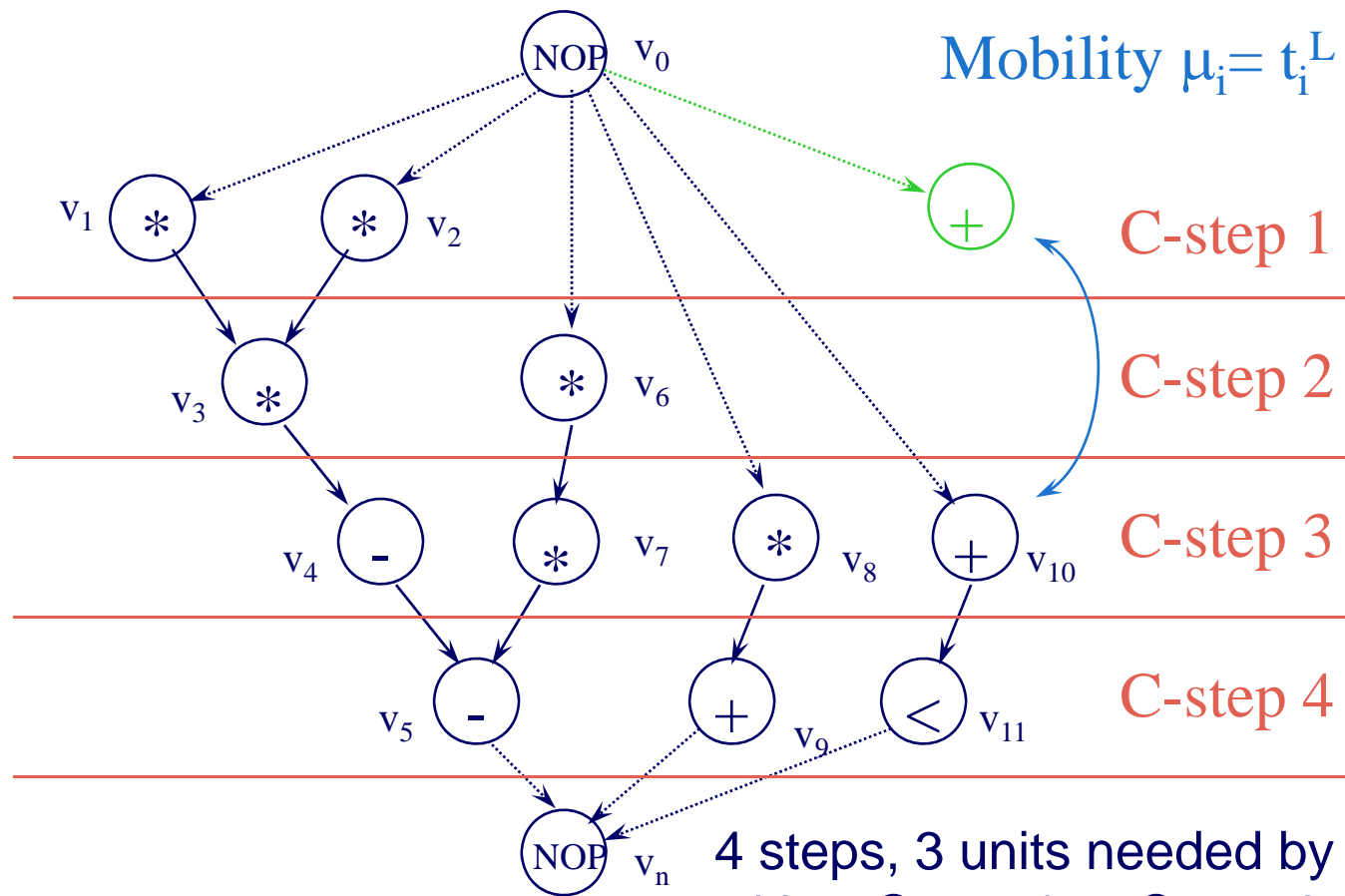- ❖ The difference of timing step between the ASAP and ALAP for an operation.
- ❖ It is allowed to move the corresponding operations within the mobility region. -> this allows a better resource utilization by moving an operation from a busy step to a free step.



4 steps, 3 units needed by moving v10 to C-step1 or C-step2.

❖ List scheduling (resource-constrained minimum-latency)

■ example 1

$a_1 = 2$ mult

$a_2 = 2$ ALU



$\{v_1, v_2\}$ $\{v_{10}\}$

$\{v_3, v_6\}$ $\{v_{11}\}$

$\{v_7, v_8\}$ $\{v_4\}$

$\{v_5, v_9\}$

  Schedule the operations that are urgent (which are in the critical path, or longest way to go to the completion) first.



❖ List scheduling (latency-constrained minimum-resource)

■ example

$$a = [1, 1]^T$$

$$\{v_1, v_2\} \dashrightarrow a = [2, 1]^T$$

$$\{v_3, v_6\}$$

$$\{v_7, v_8\}$$


zero slack

$$\{v_{10}\}$$

$$\{v_{11}\}$$

$$\{v_4\}$$
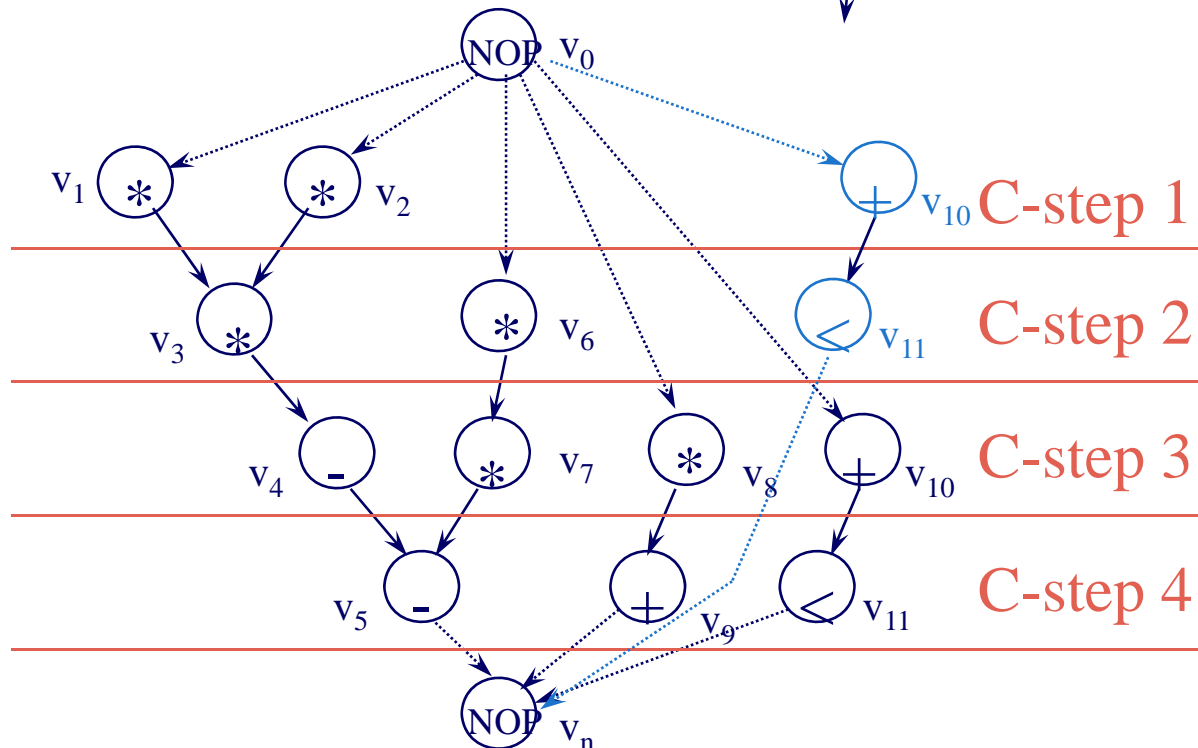
$$\{v_5, v_9\} \dashrightarrow a = [2, 2]^T$$



Resource sharing and binding

❖ Scheduling before binding

- resource dominated circuits: operation scheduling

❖ Binding before scheduling

- general circuit: mux and wire delay/area may not be ignored

❖ General circuit

- scheduling affects binding
 - > affects the use of mux, wire, and register
 - > affects delay and area (non-linear function of binding B)
 - > affects scheduling
- use piecewise linear functions and solve scheduling and binding simultaneously with an ILP solver
- iterate scheduling and binding
- simulated annealing
- genetic algorithm

Scheduling and retiming

- ❖ Retiming changes the signal flow graph (starting and ending points)
- ❖ Ex: 2nd order IIR filter : 4 mult, 4 add/output
 - Time multiplexing ratio (system clock freq. / sampling freq.) = 4



CYCLE	MULTIPLIER	ADDER
1	4, 7	
2	5, 8	3
3		1, 6
4		2

IIR filter scheduling before retiming
(2 mult, 2 adder needed)



CYCLE	MULTIPLIER	ADDER
1	5	1
2	4	6
3	7	2
4	8	3

IIR filter scheduling after retiming
(1 mult, 1 adder needed)

2nd order IIR filter

 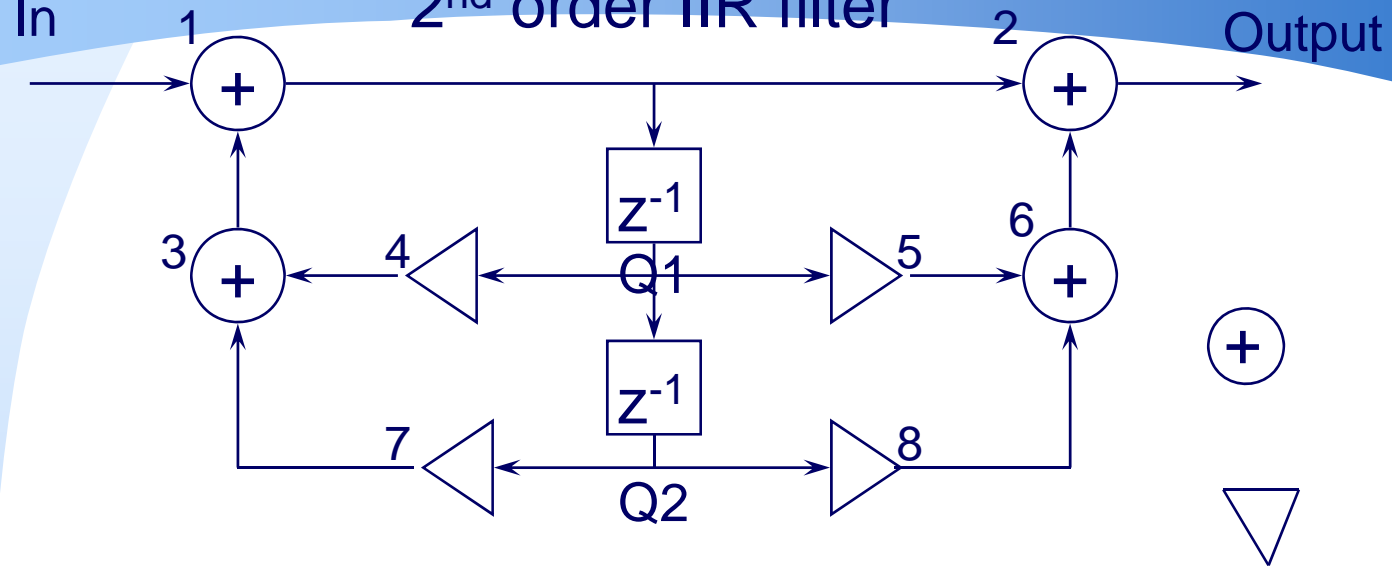

After retiming

 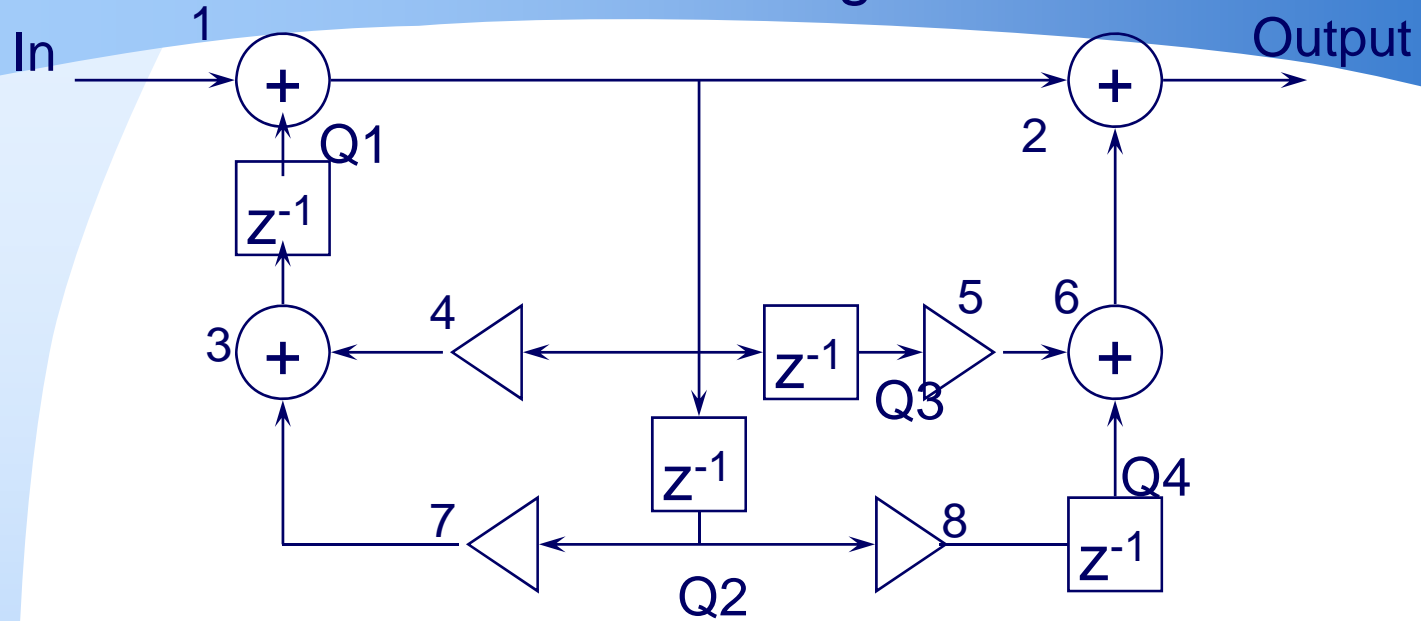

Memory design


❖ Why needed?

- To store the state variables shown in the flow graph (retimed version needs 4, while the original needs only 2)
- To store the early finished results for synchronization. In the original flow graph, if it is scheduled in 4 clock cycles, "In" signal needs to wait 2 cycles to be added.

❖ Memory architecture

- Addressable memory based: flexible but need more area. Maybe a bottleneck for high throughput (in this case, multi-ported, or multiple memory blocks are needed).
- Distributed register based: inflexible, but good for high-throughput

How many registers? 4

 


Binding 1

Binding



In

How many registers? 4

 


Whole circuit

(n) Time index, one of 0, 1, 2, 3

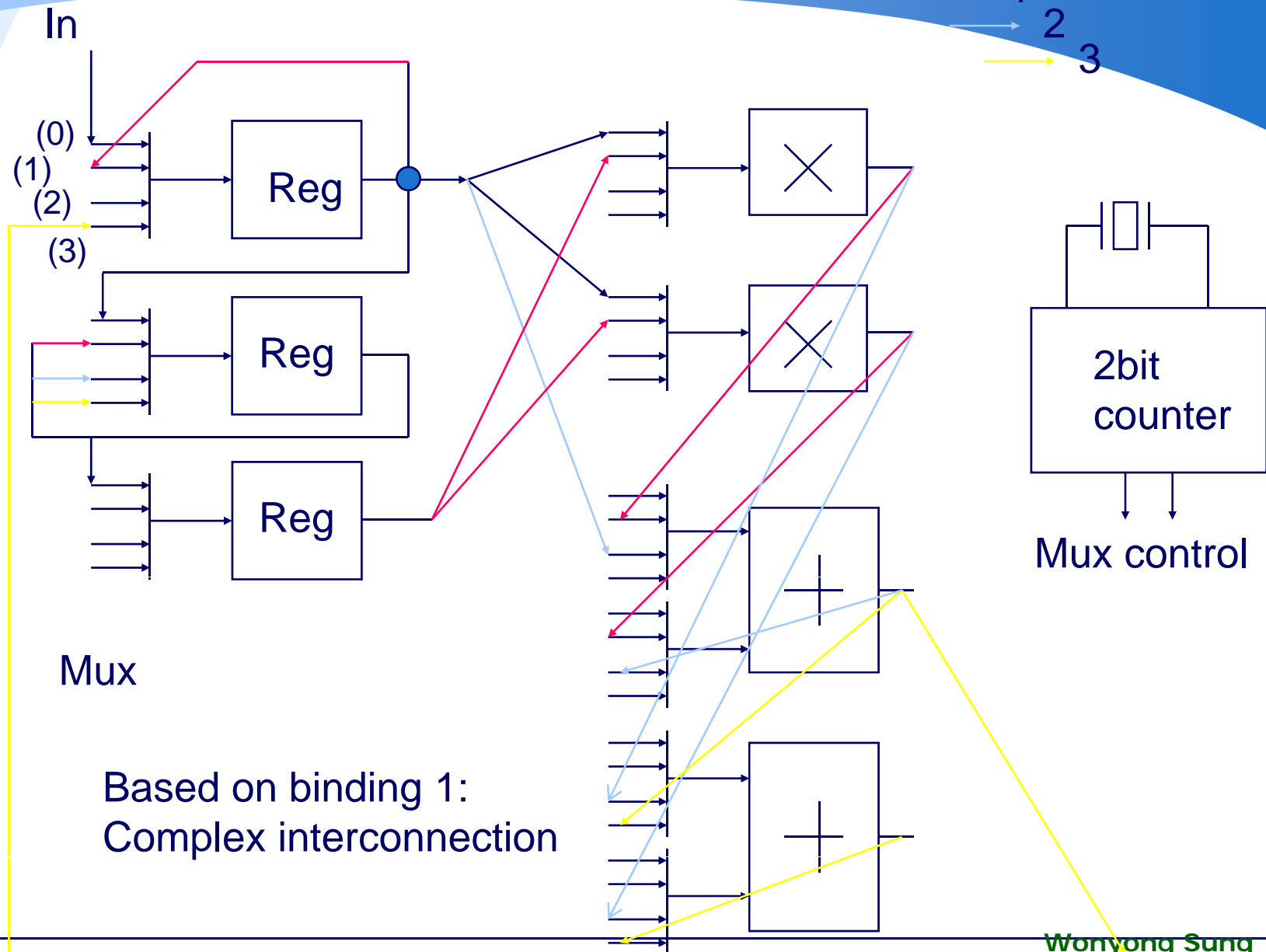 

Mux

 
Based on binding 1:
Complex interconnection



Whole circuit

(n) Time index, one of 0, 1, 2, 3

→ 0
→ 1
→ 2
→ 3

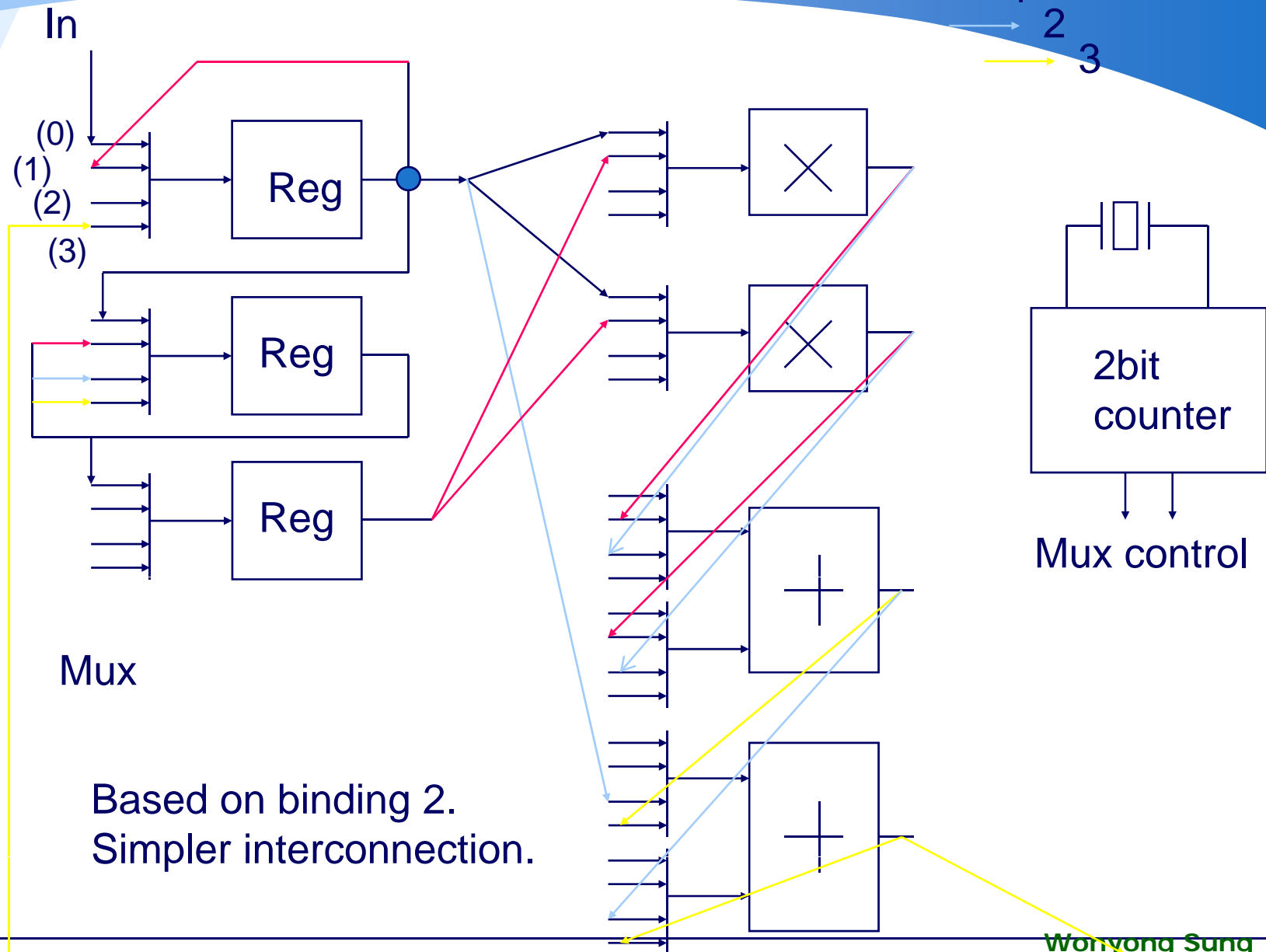

Interleaving and iterative structure based design

❖ Interleaving


- Processing multiple input channel alternatively. So, it is a kind of time-multiplexing supporting the same function for both channels.
- z^{-1} corresponds to two (or interleaving factor) clock delays, which leads to shorter loop bound for a recursive loop.
- Can increase the efficiency of the hardware, but do not increase the throughput for a certain channel.

❖ Application: stereo processing with mono hardware. Multi-stage system implementation

Interleaving

❖ Time multiplexing through interleaving

 
- Insert two (or three, ...) registers for one z^{-1} , and retiming for critical path minimization. And, apply two (or three, ...) channels of input. In this case, one register delay corresponds to $z^{-1/2}$ and the original transfer function is not changed.



If $D = z^{-1}$

$$H(z) = 1/(1-az^{-1})$$


original

 

If $D = z^{-1}$

$$H(z) = 1/(1-az^{-2})$$


High throughput
But different filter

 

If $D = z^{-1/2}$


$$H(z) = 1/(1-az^{-1})$$

Interleaving for multi-channel

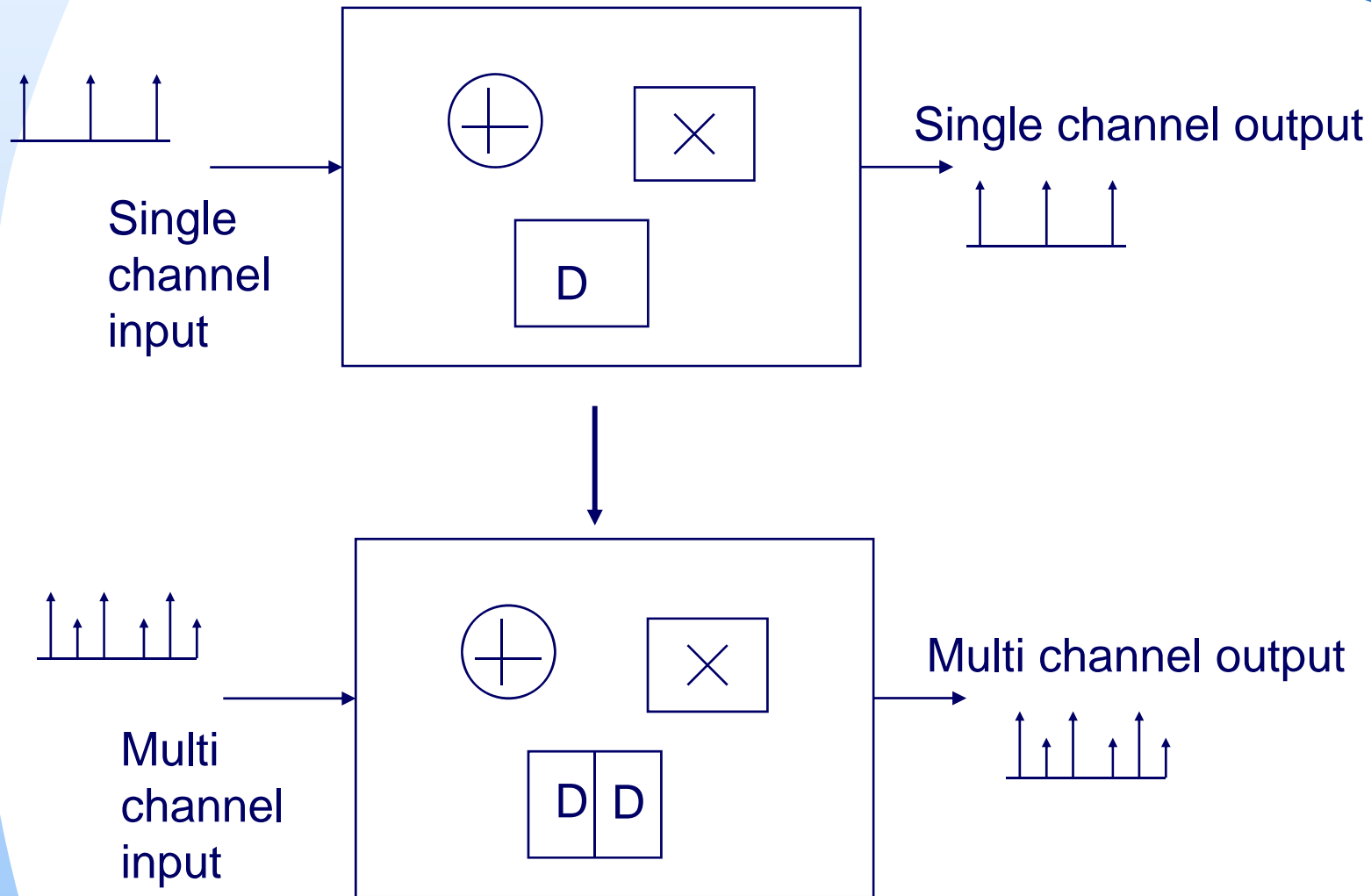


Interleaving for cascade or parallel systems

Equiv. transf.

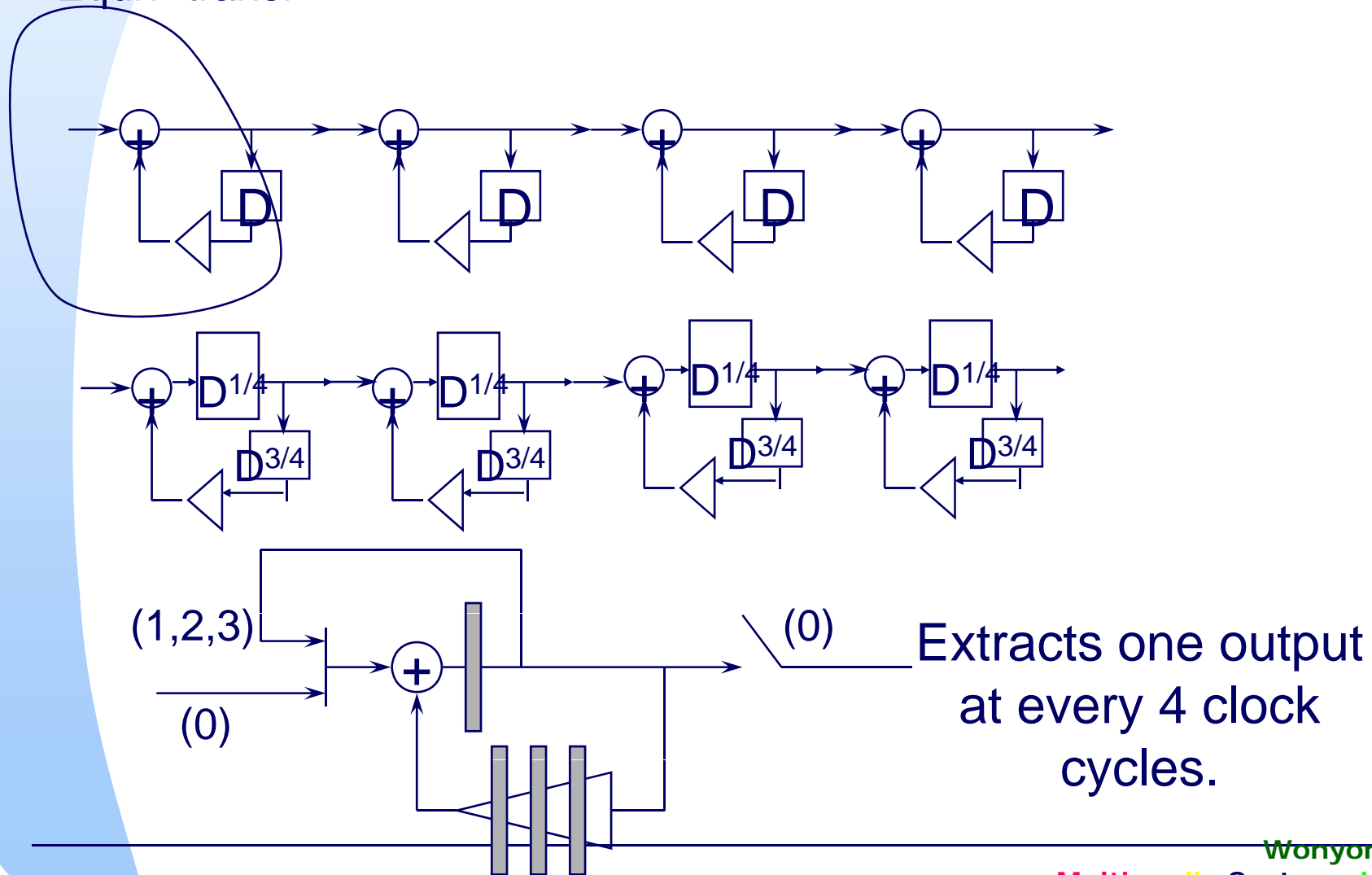


Iterative structure based design of time-multiplexed architecture (generalized interleaving)

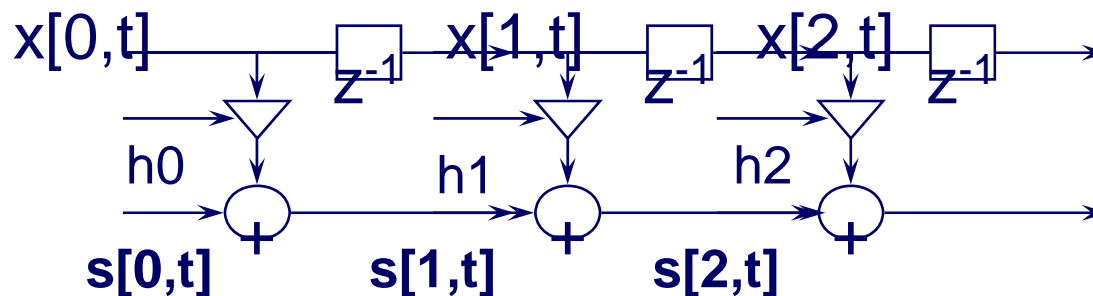Digital filter: consists of iterative operations (stage, tap, or so on)




 $x[n,t]$
 n : stage index,
 t : time index





 
Forward computation: $x[0,t] \rightarrow x[1,t] \rightarrow x[2,t]$





buffer: needed for HW operation

If the time-mux ratio is M ,
 z^{-1} corresponds to M clock delays.

FIR filter with time-mux ratio M

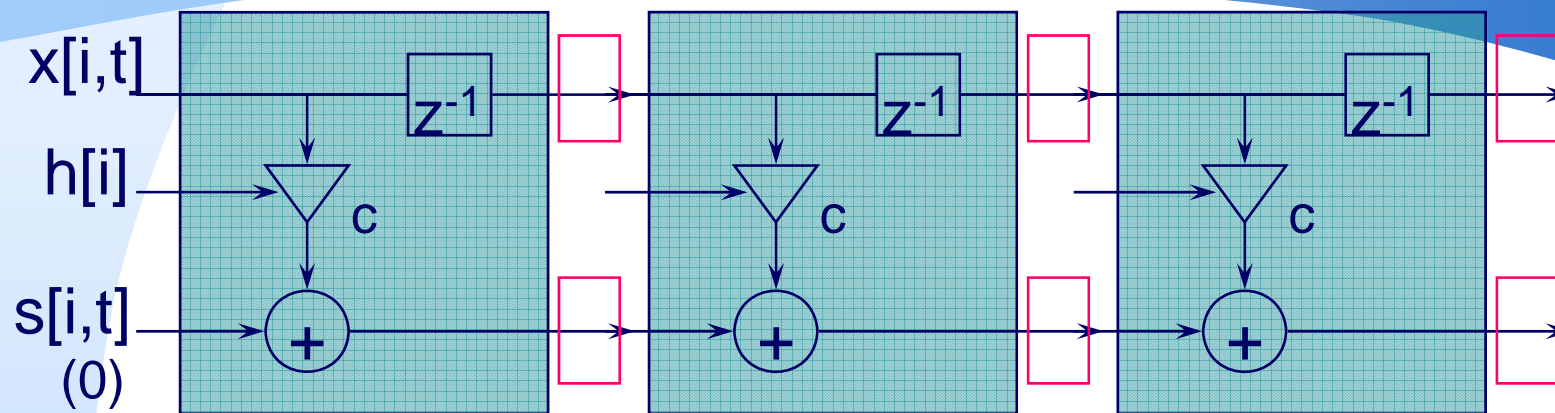

Iteration process

 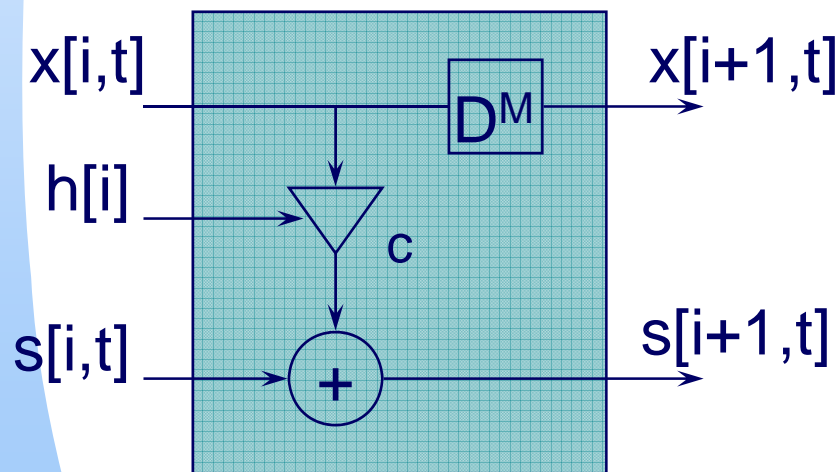

$h[M-1]$ $h[0]$


Wonyong Sung
Multimedia Systems Lab SNU



Program based method

- ❖ Generate control signal using program ROM
- ❖ Consists of datapath, program ROM, data memory, and controller.
- ❖ Can optimize the data-path structure (the performance is better than the general purpose DSP's).
- ❖ CAD software => Cathedral II (microcoded multiprocessor architecture), Lisatek (application specific instruction set and data-path design)

Mircro-program based implementation

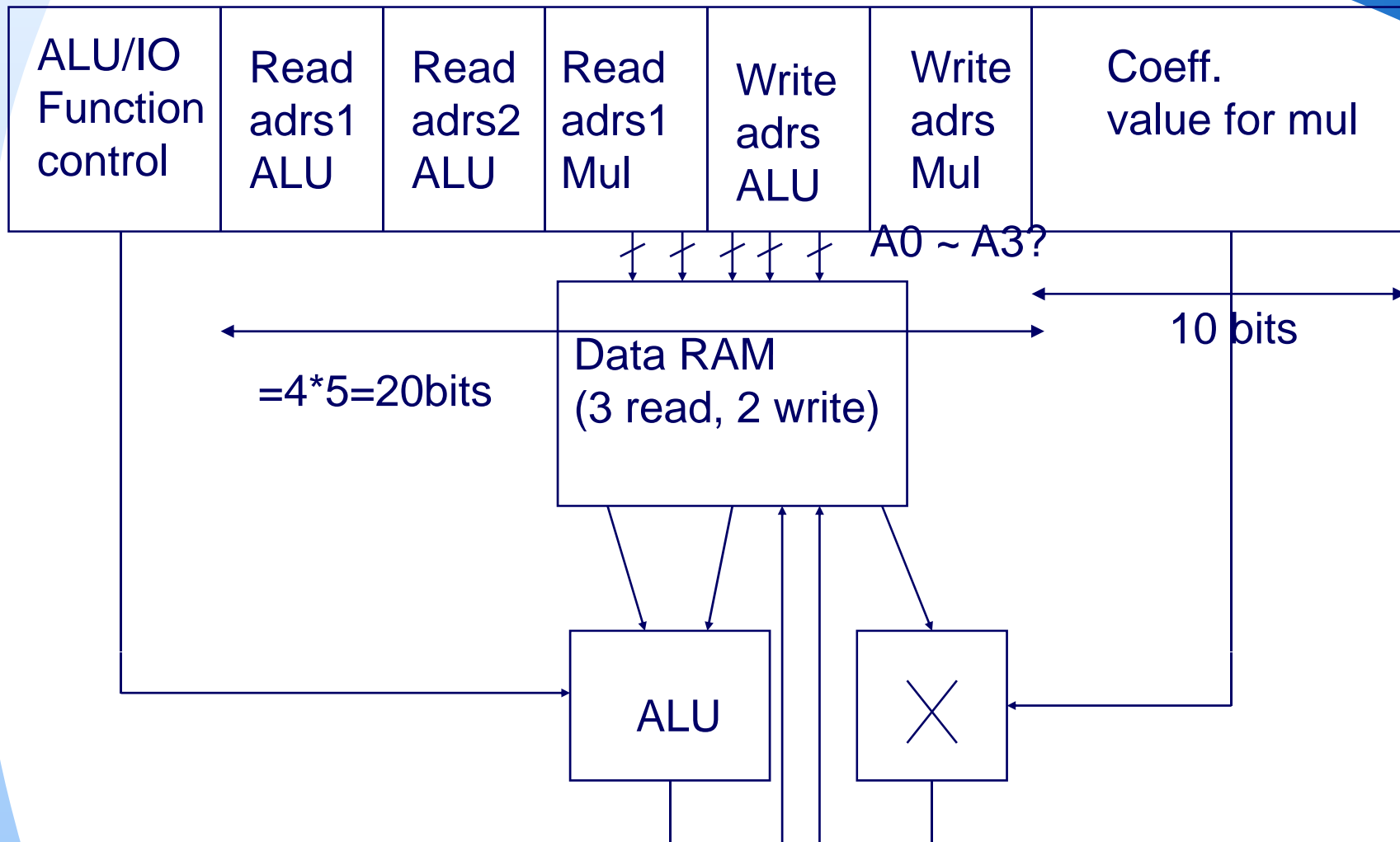Microprogram ROM: total 4 words, but very wide.



  

Determining
the total number
of registers

Overall design procedure for program based architecture


- ❖ Data-path structure design by scheduling and binding
- ❖ Memory system design
- ❖ Interconnection of the components or develop microprogram
- ❖ Control signal generation

Cathedral (Mistral) II

A silicon compiler for complex decision making applications in the KHz - 1Mhz range

- micorcoded architecture
- multiple parameterizable execution units
- behavioral specification in Silage


Microcoded processor architecture

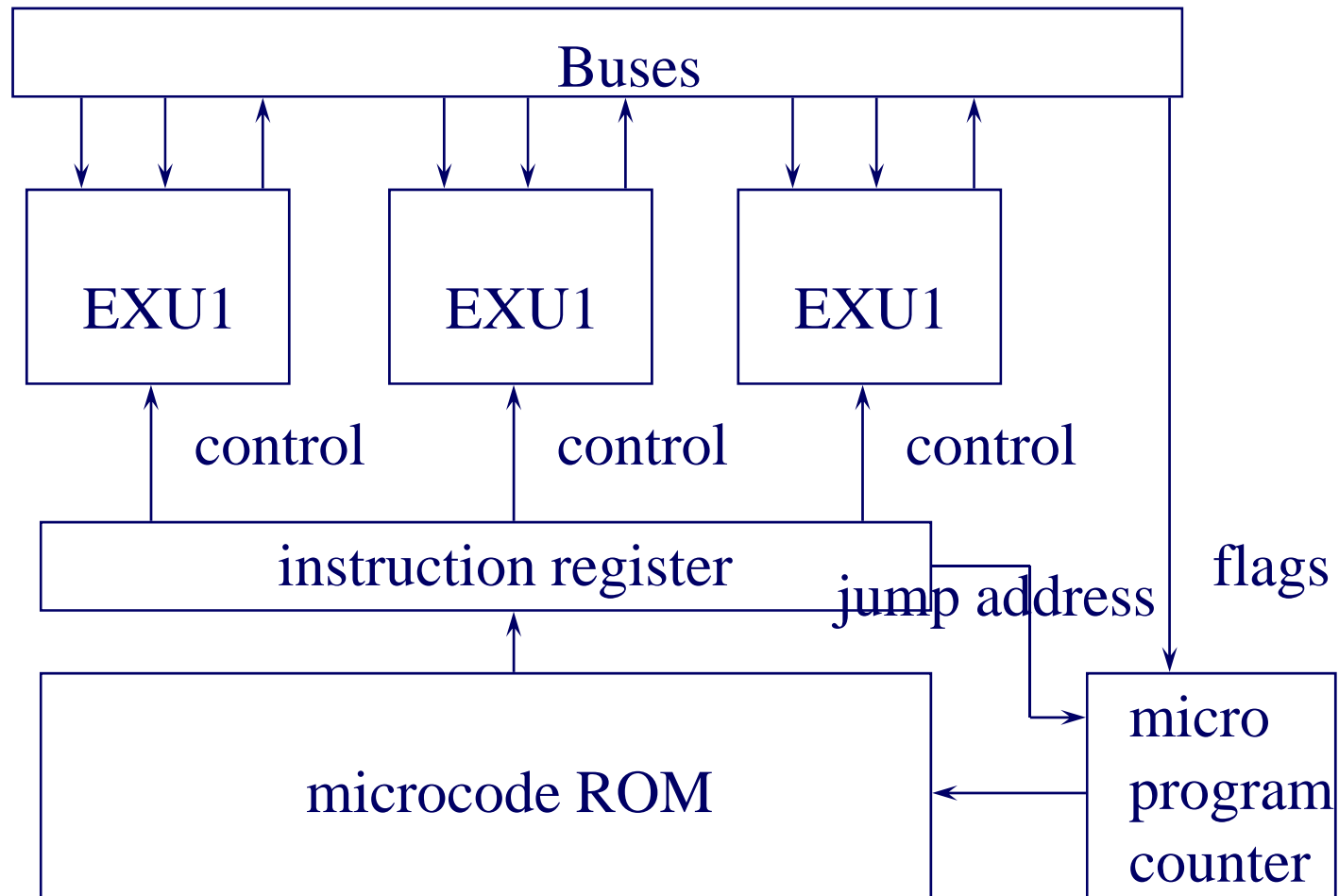

EXU overview

- ❖ **Arithmetic EXU:**
- ❖ **ALU: 2's comp ALU operations**
 - ACU: unsigned arithmetic modulo comp.
 - MULT
- ❖ **Memory EXU**
 - ROM and RAM
- ❖ **I/O EXU**
 - In, Out, Tri, IO(bidirectional)
- ❖ **Controller EXU**

EXU architecture

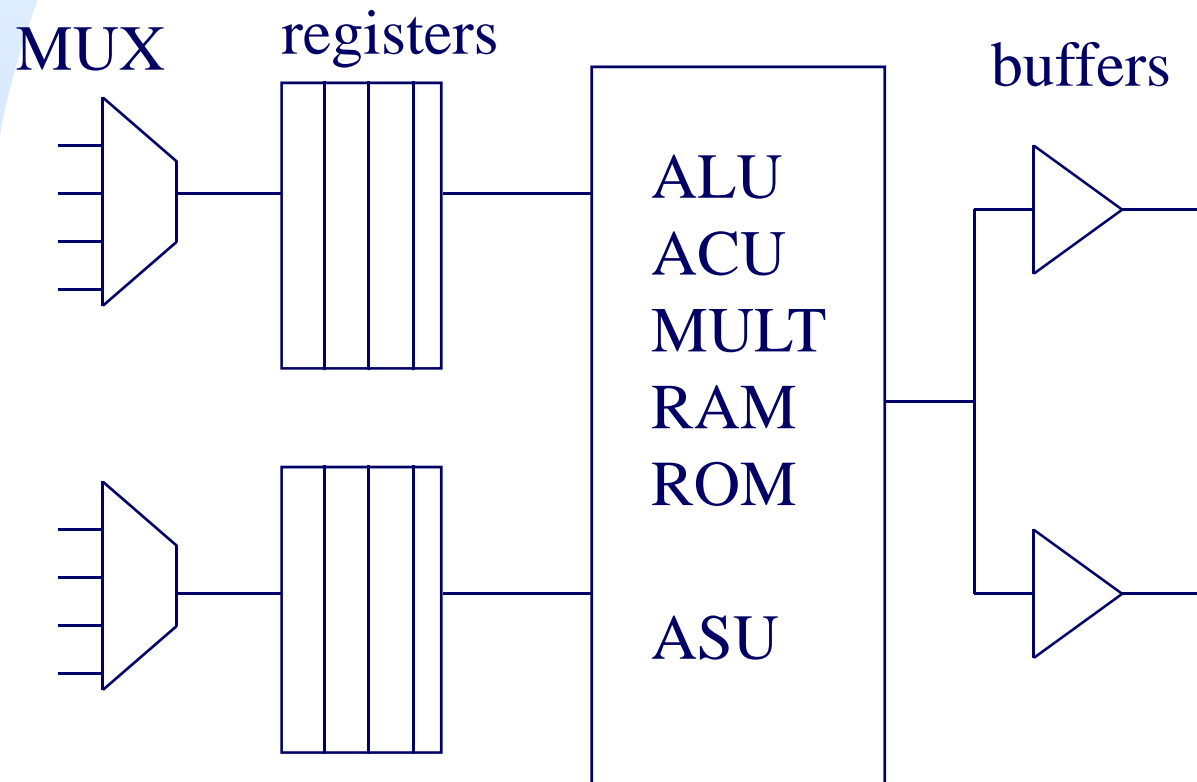


Multi processor architecture


IN1

IN2

BUS1

BUS2

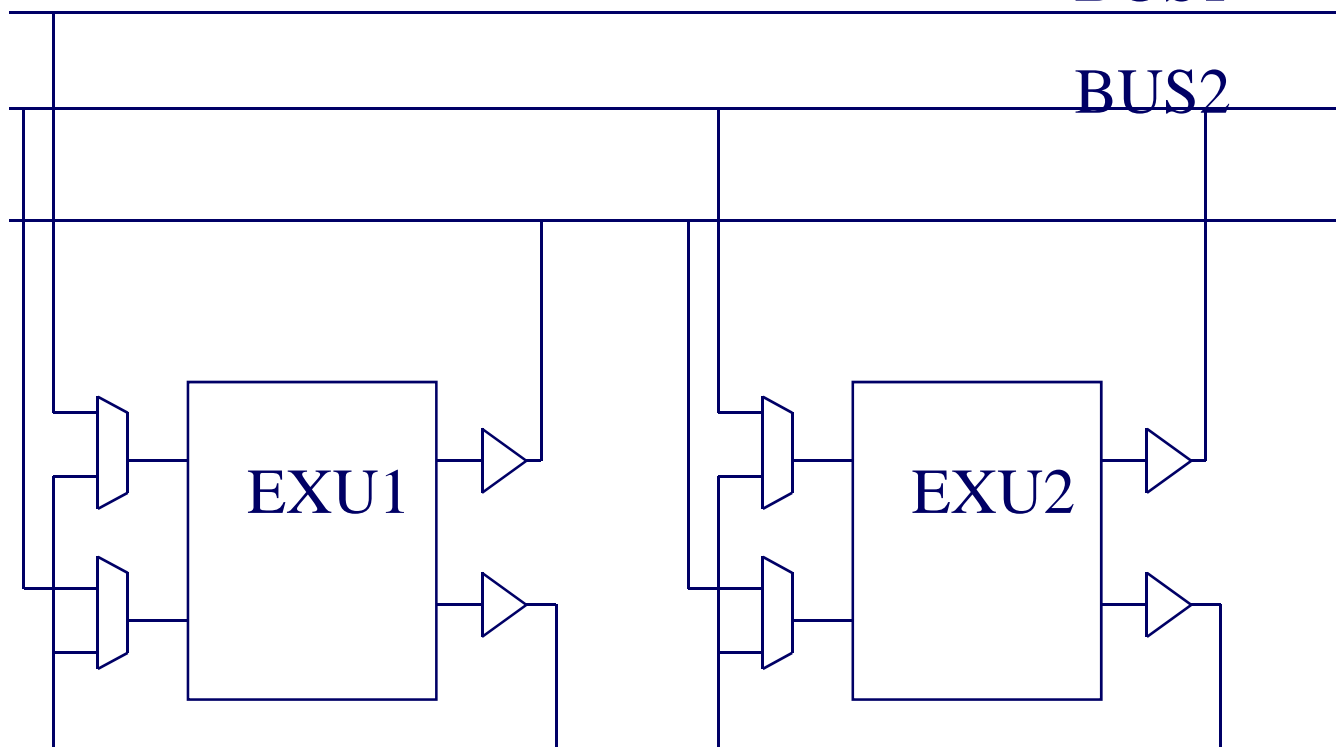

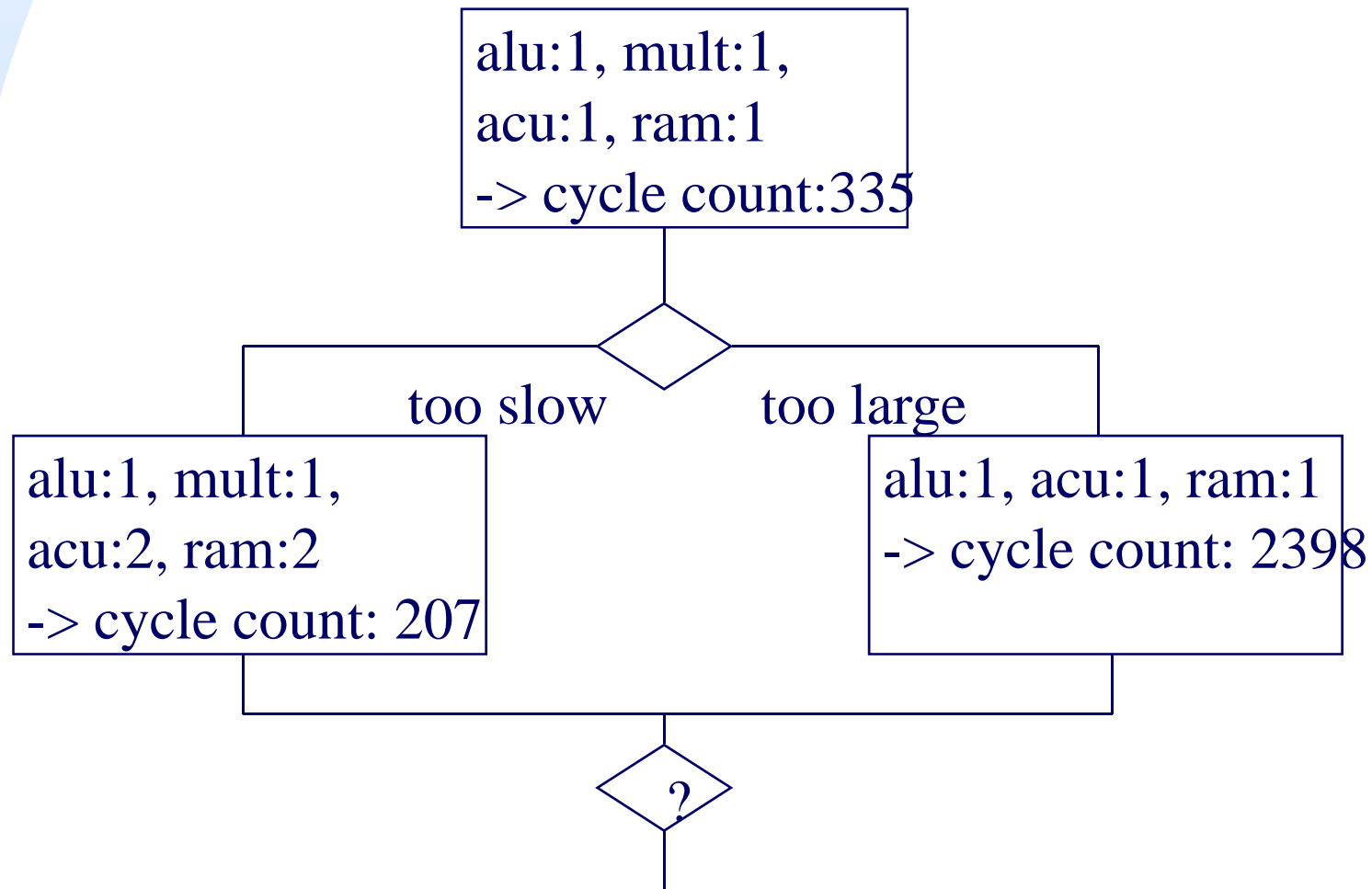

Architecture comparison

❖ **general purpose DSP**

- have a fixed data-path (usually multiply and accumulate)
- program width 16 - 32 bits
- flexible programming including C language
- only code generation required

❖ **hardwired DSP (Mistral-I, Mistral-III)**

- have a very flexible data-path
- not good for decision making (if ..)
- mostly data-path generation

Architecture comparison - cont.

❖ **Microcoded processor architecture**

- flexible and multiple data-path structure
- program width: 32 - 256 bits
- programmable, but code space requirement is less efficient
- need both data-path and code generations
- good for algorithms requiring specific data-path architectures with decision making

e.g. speech pitch extractor, speech coder

4. Bit Serial Architecture

❖ Bit-serial, operation dedicated

- Use bit-serial multipliers (complexity of a parallel adder), bit-serial adders, and shift-registers
- processes one bit of signal at one clock using a dedicated one-bit arithmetic or memory elements -> slowing down the effective f_{system}
- almost hardwired (simple) control
- efficient implementation (good for digital filters), limit in throughput
- Limitation: hard to be applied to control intensive algorithms.

Timing of bit-serial operation

❖ **LSB (least significant bit) first**

- supply the LSB of a signal first,
- carry propagation is allowed
- can employ ordinary number system
- needs large delay(latency) for multiplication,
limit for high throughput application

Timing of bit-serial operation - cont.


- ❖ **MSB(most significant bit) first**
 - supply the MSB of a signal first,
 - carry propagation is not allowed
 - redundant number system is used
 - Carry is propagated to only one stage
 - needs small latency, can be used for high throughput system
 - Complex and larger cell area

Bit serial components – for 'w' clock/sample

Delay



Adder

 


one clock latency occurred!

Bit serial components - cont.

scaler

- 1 bit delay: $\times 2$
- 1 bit advance with sign extension: $\times 0.5$
(implemented with relative delay)

multiplier

 

w bit of signal

c bit of coefficients


$w+c-1$ bit $\rightarrow w$ bit

should delete the first $c-1$ bits \rightarrow total c bit latency



Retiming and delay management

- ❖ Maximum throughput of a digital filter is determined by the number of delay blocks(z^{-1}) and the total latency of the arithmetic blocks
- ❖ When the latency is large, the data wordlength for bit-serial implementation should be increased even if it is not needed for signal representation

Example - 1st order filter

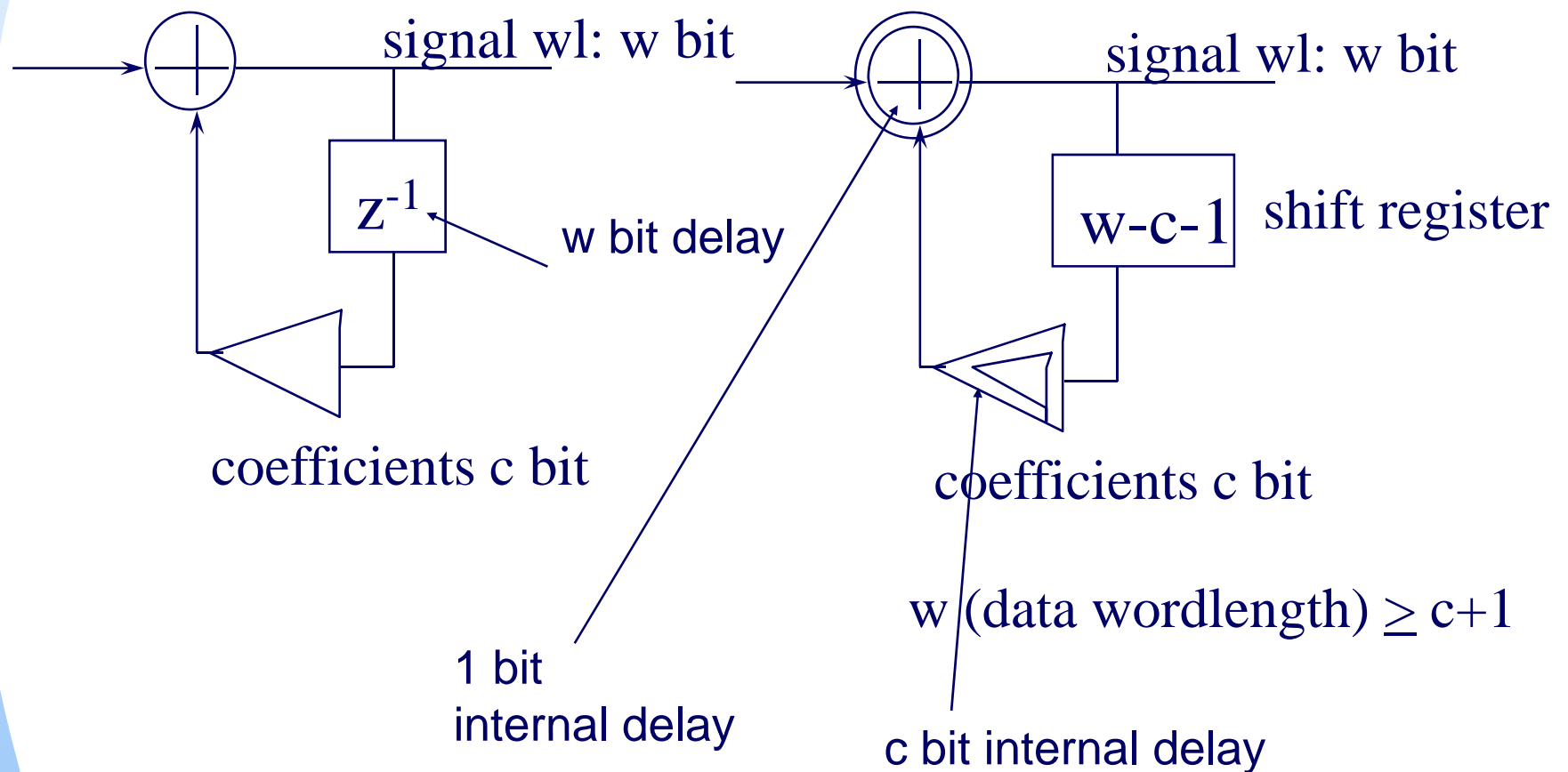



Assume $w=24, c=12$ 2nd order bit-serial

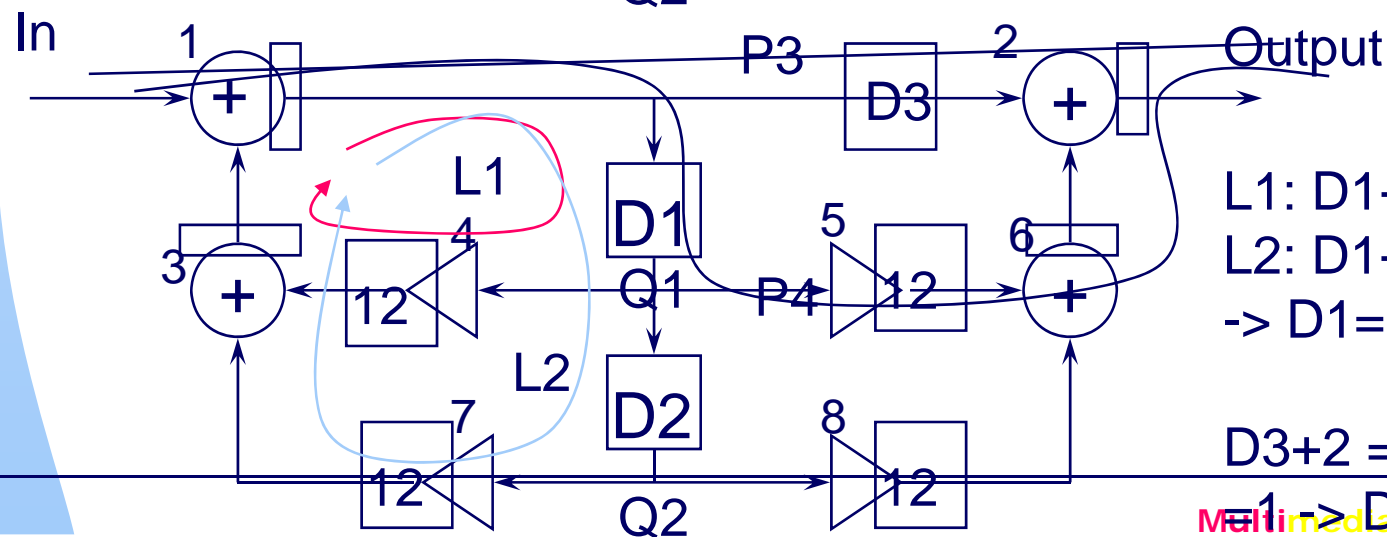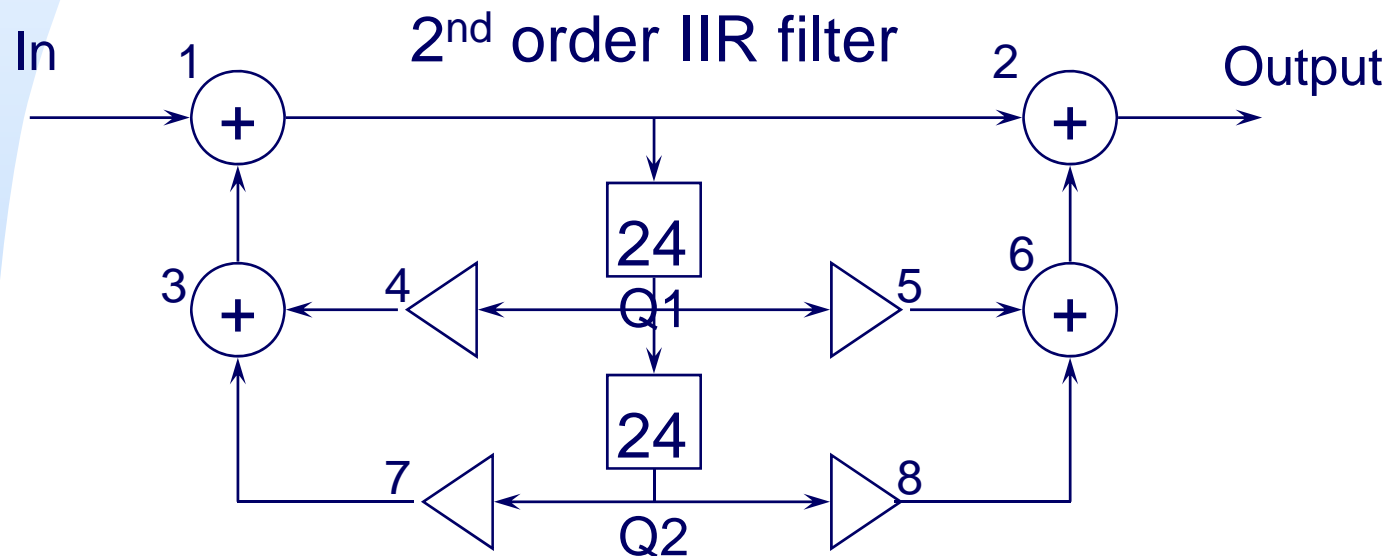

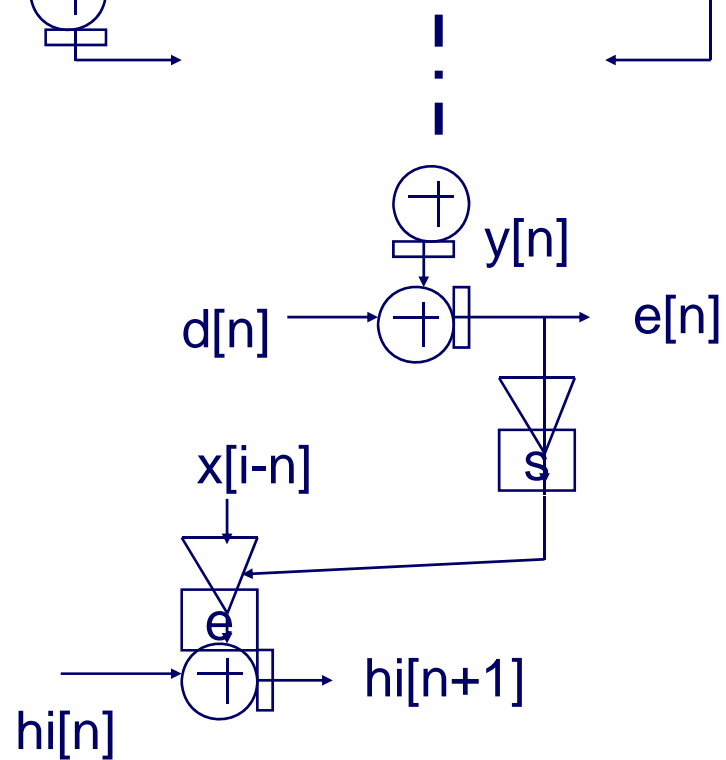 Example - adaptive LMS digital filter

- ❖ data wl: w , coefficients wl: c ,
number of taps: N ($\log_2 N = M$),
step size wl: s , error wl: e
- ❖ total delay in one sampling time =
 $c + M + s + e$
-> $w \geq c + M + s + e$

So, we may need to increase w (just for timing, not for better precision)



MSB first serial processing

❖ Redundant number system

- A Radix B RNS is allowed to possess digits from the set $\{-(B-1), \dots, -1, 0, 1, \dots, (B-1)\}$
- Let $X = x_{n-1}x_{n-2} \dots x_0$ be a n-digit radix beta number, then
- $X = x_{n-1}B^{n-1} + x_{n-2}B^{n-2} + \dots + x_0B^0$
- So, the number of values a digit is allowed to possess by the number system is $(2B-1)$

❖ Low latency even for multiplication, thus good for feedback based systems.

- Not popular because the complexity of each arithmetic element is high.

❖ **B=4**

+3, +2, +1, 0, -1, -2, -3

❖ **Representation of 9, multiple (redundant) forms**

$2, 1 = 2 \times 4 + 1$ <- basic representation

$3, -3 = 3 \times 4 - 3$

❖ **The carry propagation is limited to just one stage, so we can do arithmetic from the MSB**

$$1, 2, 1 + 1, 1, 2 \rightarrow (0, 2) \times 4^2 + (1, -1) \times 4 + (1, -1) = 0, 3, 0, -1$$

0, 2

1, -1

1, -1

<- 0, 3 is represented as 1, -1 to have a room for carry pro.

0, 3, 0, -1

❖ **Why not keep propagating**

- Because the number system has a room that prevents overflow even when there is a carry propagated from the low digit.

Time-multiplexing and multi-rate

- ❖ processes two or more different signals with the same operations using one hardware
- ❖ $f_{\text{sample_max}} = f_{\text{clock_max}} / WL / MF$,
where MF is the multiplexing factor
- ❖ **Example: stereo circuit**

Bit-serial summary

❖ advantages

- small chip area per throughput
- Low complex control and interconnection
- <- high system clock rate, small arithmetic elements, hardwired control

❖ disadvantages

- limited throughput (but faster than program controlled architectures)
- High power consumption at shift registers
- limited control capability
- > not good for integrating general control functions

5. Distributed Arithmetic Architecture

- ❖ A special kind of bit-serial architecture
- ❖ ROM + accumulator based, instead of multiply + adder.
- ❖ Many of digital filtering algorithms are Sum of Product (multiply and accumulation) based - convolution, transformation, dot-product
- ❖ Distributed arithmetic computes the inner product in a bit-serial manner, using ROM and Accumulator based HW
 - Bit-serial operation reduces the needed ROM size.
 - Still, it is needed to decompose the algorithm for high order digital filters
 - Not flexible, so not adequate for adaptive filters

Implementation of the sum of product

$$\diamond Y = A_0 * X_0 + A_1 * X_1 + A_2 * X_2 + A_3 * X_3$$

$$\diamond X_i = x_{i7} x_{i6} x_{i5} \dots x_{i0}$$


($x_{i7} x_{i6} \dots$ is 1 or 0, assume 8 bit)


$$= (-1)^{x_{i7}} * 2^7 + x_{i6} * 2^6 + x_{i5} * 2^5 + \dots + x_{i0} * 1$$

$$\begin{aligned} \diamond Y = & (-1)^{x_{07}} * 2^7 * (A_0 * x_{07} + A_1 * x_{17} + \dots + A_3 * x_{37}) \\ & + 2^6 * (A_0 * x_{06} + A_1 * x_{16} + \dots + A_3 * x_{36}) \\ & \dots \\ & + (A_0 * x_{00} + A_1 * x_{10} + \dots + A_3 * x_{30}) \end{aligned}$$

Why bit-serial?

 
A direct bit-parallel implementation with ROM



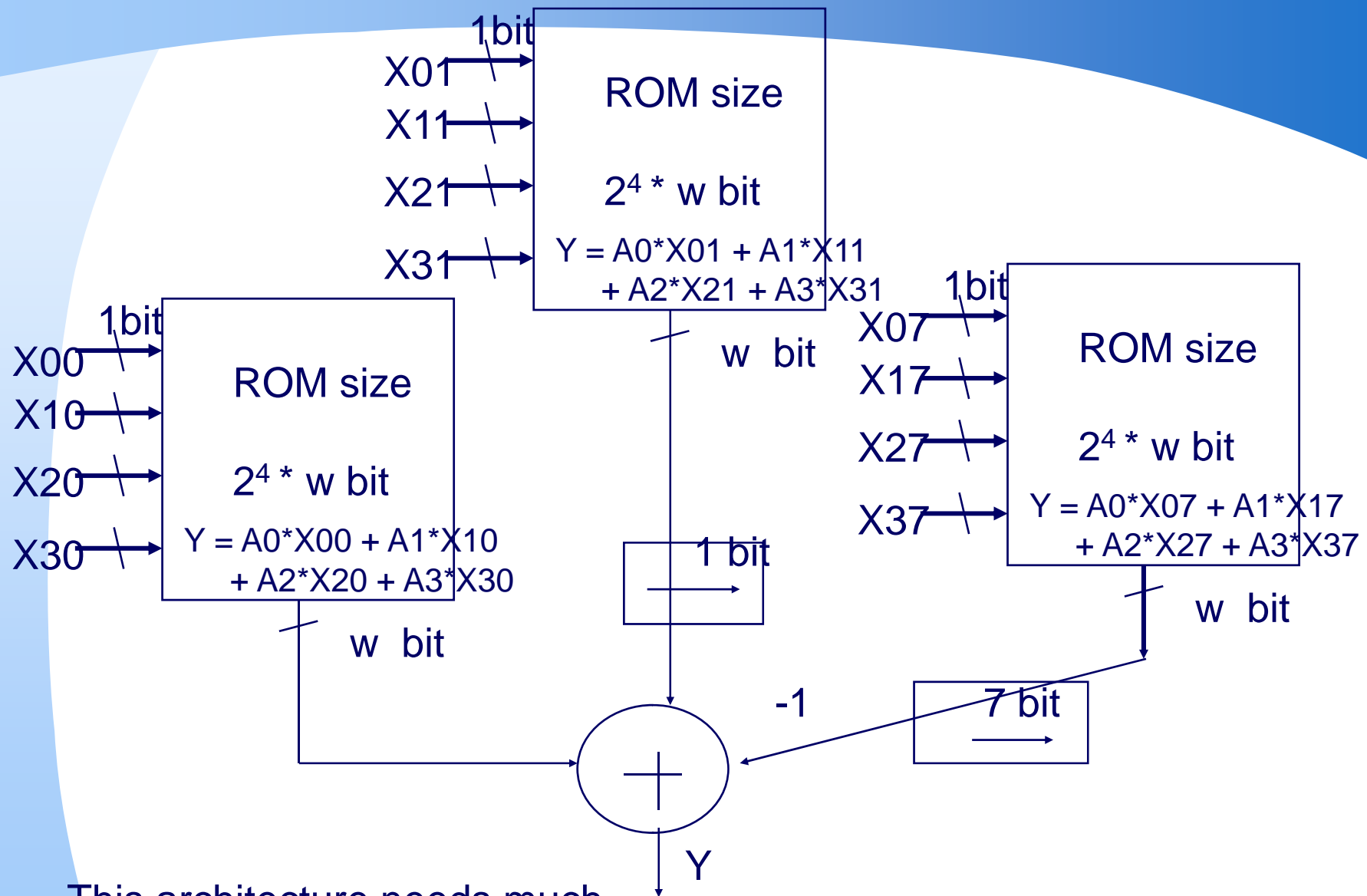

This architecture needs much smaller ROM (8 * 16word ROM) size although it requires an 8 input adder

Distributed arithmetic

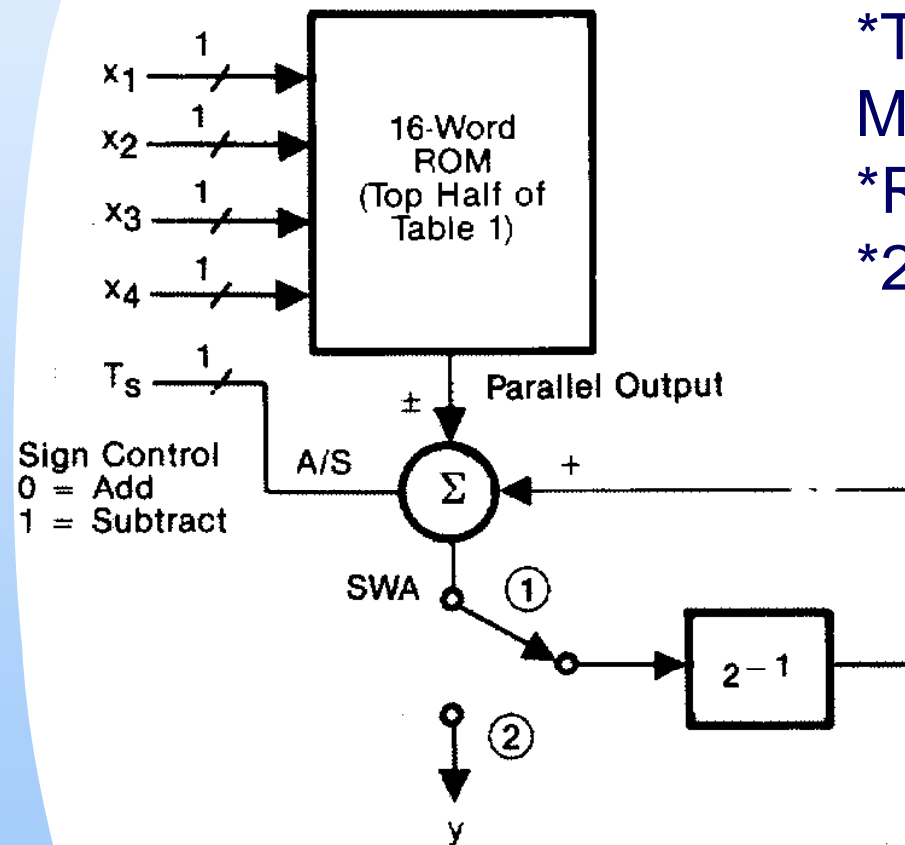

* T_s controls add/sub: sub for MSB

*ROM size $\rightarrow 16 \times$ word length

* 2^{-1} is arithmetic right shift

Figure 1b. Adder/Subtractor and Memory

Distributed arithmetic (ROM Table)

Add					
ress	b3	b2	b1	b0	contents
0	0	0	0	0	0
1	0	0	0	1	A_0 (=0.25)
2	0	0	1	0	A_1 (= -0.1)
3	0	0	1	1	$A_1 + A_0$ (=0.25-0.1)
	...				
15	1	1	1	1	$A_3 + A_2 + A_1 + A_0$

Distributed arithmetic (Minimum ROM)

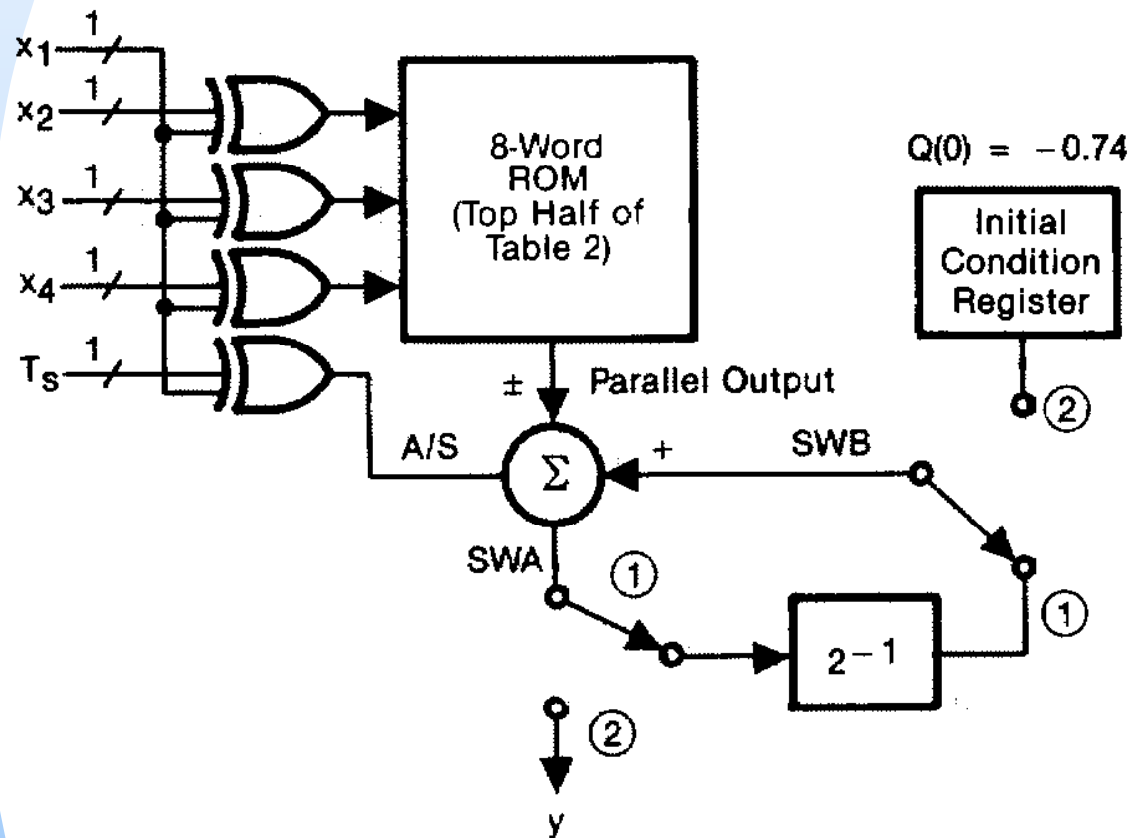


Figure 1c. Adder/Subtractor and Reduced Memory

Speeding-up the distributed arithmetic based circuits

Apply 2-bit at a time for speed-up.
Needs two ROM-> 2 times speed

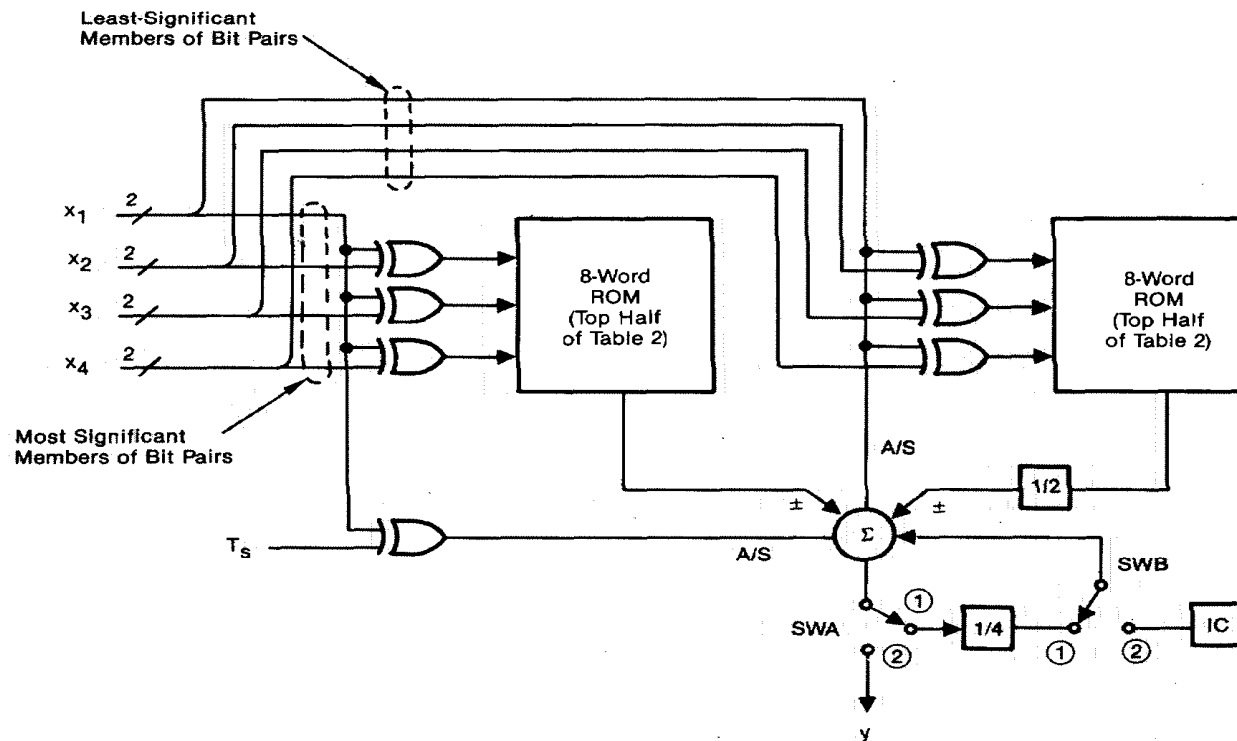


Figure 2. 2-Memory, 2 BAAT version of Figure 1C.

Application of distributed arithmetic

- ❖ FIR filter
- ❖ DCT, IDCT -- matrix vector product
-- no need of complex inter-connections found in efficient structure
- ❖ Distributed arithmetic is not good when the filter coefficients need to be changed. This (all bit serial arithmetic based one) is also not adequate for floating-point arithmetic.


6. SoC based Architecture

- ❖ HW based architecture is efficient in terms of throughput for a given silicon area and power consumption, but not flexible enough
- ❖ Today's multimedia and communication standards are very complex and need SW much.
- ❖ Today's consumers want something special for them – needs differentiation
- ❖ -> Mix of CPU for programmability and HW blocks for high throughput

Example

- ❖ TI developed C6x architecture for massive communication (not mobile) markets
- ❖ And, acquired the Amati Communications that developed ADSL technology
- ❖ But, TI's solution (C6x based ADSL) couldn't win the market. TI's solution was too expensive. The winning solution was based on CPU (such as ARM7) + HW modem blocks (FFT and ..).

Multimedia I/O Architecture

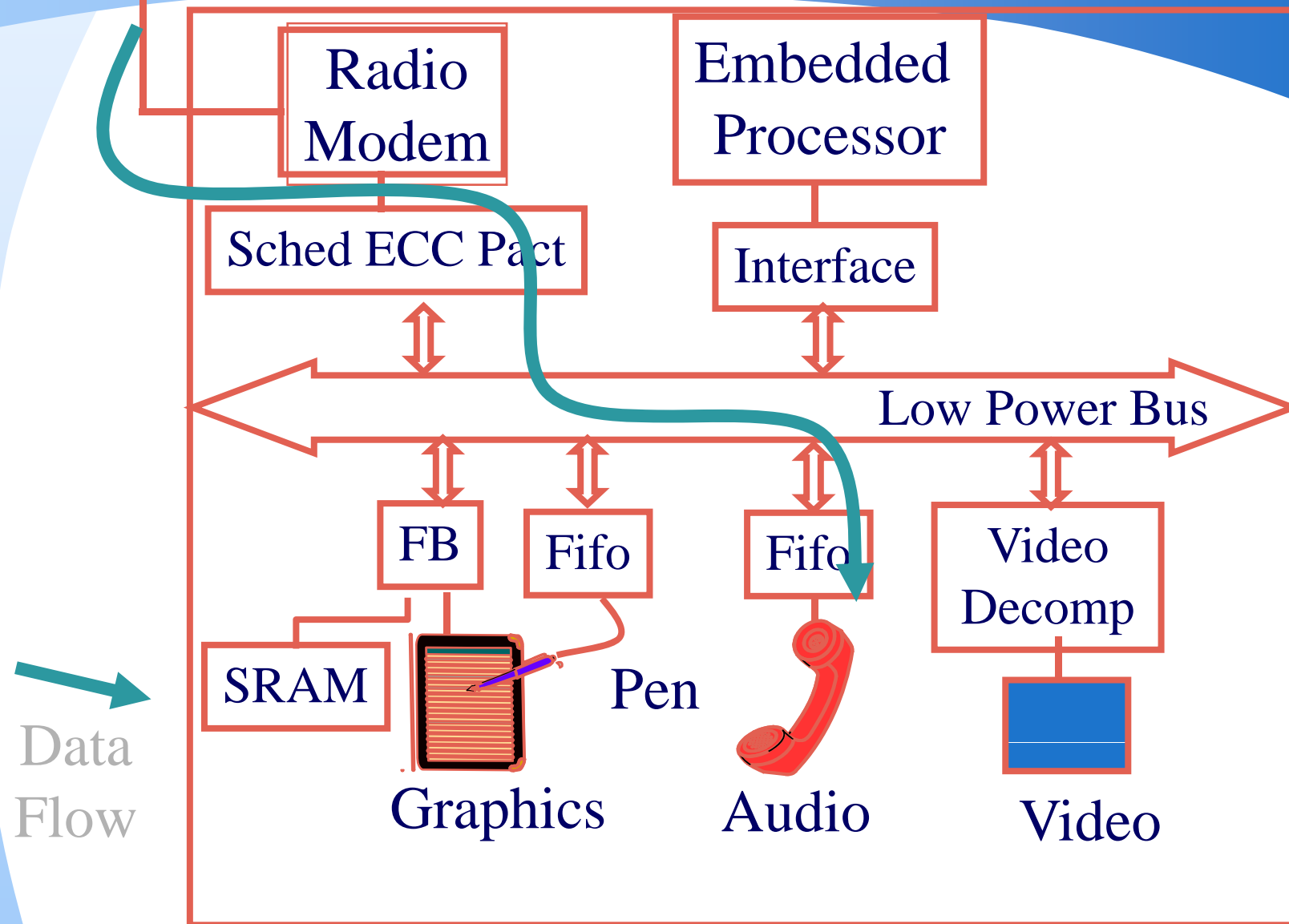

Concluding Remarks

- ❖ **Implementation of digital filtering algorithms requires adequate architectural choice because the system clock frequency is much different from the signal sampling clock frequency.**
 - Fully parallel
 - Bit parallel, time multiplexed
 - Distributed register based
 - Program ROM based
 - Bit serial
- ❖ **The flexibility of the architecture needs to be considered too. -> SoC architecture**