


Text: Electrical Engineering Principles and Applications
- A. Hambley, Pearson Education

Ch. 1 Introduction

- Electric charge : q (C)
electron $e = -1.602 \times 10^{-19}$ (C)
- Current : Flow of electric charges


$$i(t) = \frac{dq}{dt} \quad (\text{A})$$
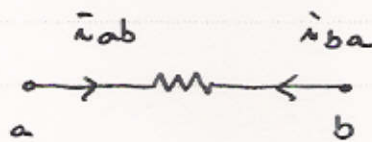
$$q(t) = \int_{t_0}^t i(\tau) d\tau + q(t_0) \quad (\text{C})$$




- Electric potential : Voltage
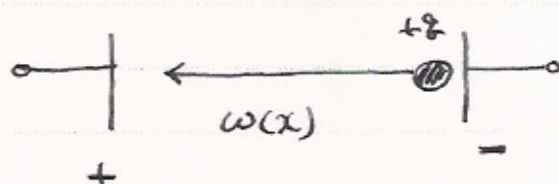
$$V(x) = \frac{dw}{dq} \quad (\text{V})$$



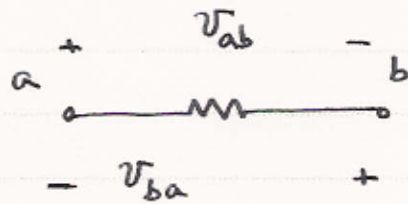Energy ^{required} needed to move unit charge for x .




$$v_{ab} = -v_{ba}$$

v_{ab} : electric potential difference between a and b.

• Energy and power

$$p(t) = \frac{dW}{dt} = \frac{dW}{dq} \cdot \frac{dq}{dt} = v \cdot i \quad (\text{W})$$
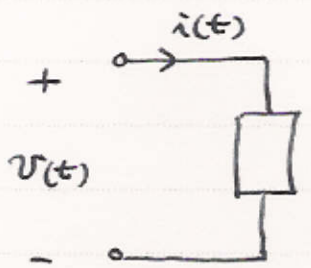
$$p(t) = v(t) \cdot i(t) \quad (\text{W}) : \text{instantaneous power}$$



if $p(t) = v(t) \cdot i(t) > 0 \Rightarrow$ power consumed.
Passive element

if $p(t) = v(t) \cdot i(t) < 0 \Rightarrow$ power generated.
Active element.

$$W(t) = \int_{t_1}^{t_2} p(z) \cdot dz$$

Example 1.3)

§1.4 Kirchhoff's Current Law (KCL)

- Net current entering a node is zero.


$$\sum_{\text{node}} \dot{i}_k(t) = 0$$




$$\sum_{\text{in}} \dot{i}_k(t) = \sum_{\text{out}} \dot{i}_d(t)$$

§1.5 Kirchhoff's Voltage Law (KVL)

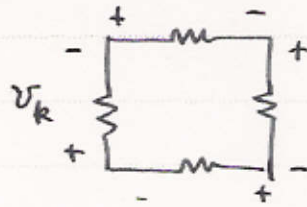- For any closed path, the sum of voltage drops equals zero.



$$\sum_{\text{loop}} v_k(t) = 0$$

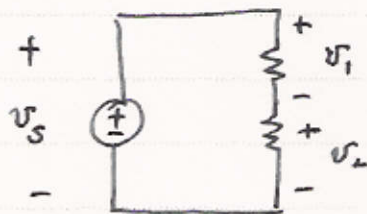


$$\sum_{\text{up}} v_k(t) = \sum_{\text{down}} v_d(t)$$

- Parallel circuits } See Figures
- Series circuits }

§ 1.6 Circuit Elements

- Independent voltage source

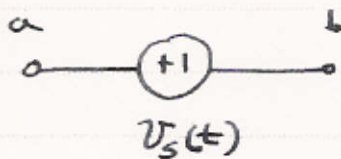


- Dependent voltage source



αU_x — voltage controlled voltage source

$\beta \hat{i}_x$ — current controlled voltage source

- Independent current source

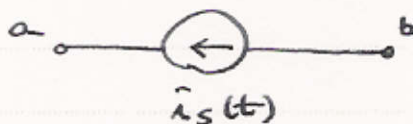

- Dependent current source



$\alpha \alpha U_x$ — Voltage controlled current source


$\beta \hat{i}_x$ — Current controlled current source

• Ohm's Law

$$i(t) = \frac{v(t)}{R} \rightarrow \begin{aligned} v(t) &= R \cdot i(t) \\ R &= \frac{v(t)}{i(t)} \end{aligned}$$

$R (\Omega)$ - resistance

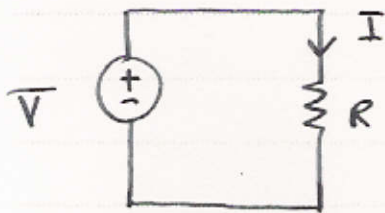$G (S, \text{mho}) = \frac{1}{R}$: conductance



$$I = \frac{V}{R}$$

$$P = VI = \frac{V^2}{R} = I^2 R$$


$$R = \frac{\sigma L}{A} (\Omega)$$

$\left\{ \begin{array}{l} L : \text{length} \\ \sigma : \text{conductivity} \\ A : \text{cross section area} \end{array} \right.$


< Example 1.7 > Explain

CH.2 Resistive Circuits

§ 2.1 Series and Parallel Circuit

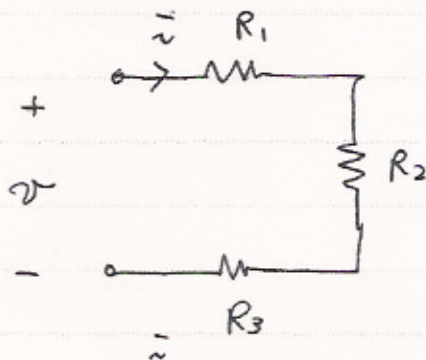
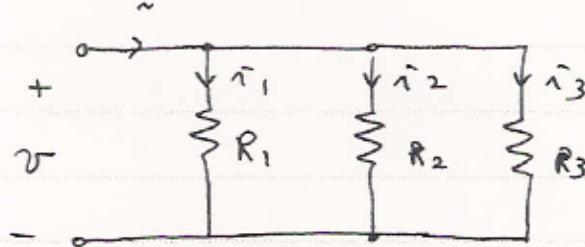
$$\begin{aligned} V &= i R_1 + i R_2 + i R_3 \\ &= i (R_1 + R_2 + R_3) \\ &= i R_{eq} \end{aligned}$$




$$\begin{aligned} i &= i_1 + i_2 + i_3 \\ &= \frac{V}{R_1} + \frac{V}{R_2} + \frac{V}{R_3} \\ &= V \cdot \left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right) \end{aligned}$$


$$\frac{V}{i} = R_{eq} = \frac{1}{\left(\frac{1}{R_1} + \frac{1}{R_2} + \frac{1}{R_3} \right)}$$

< Example 2.2 > Explain

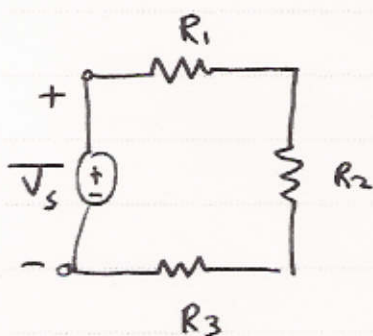§ 2.3 Voltage divider and current divider



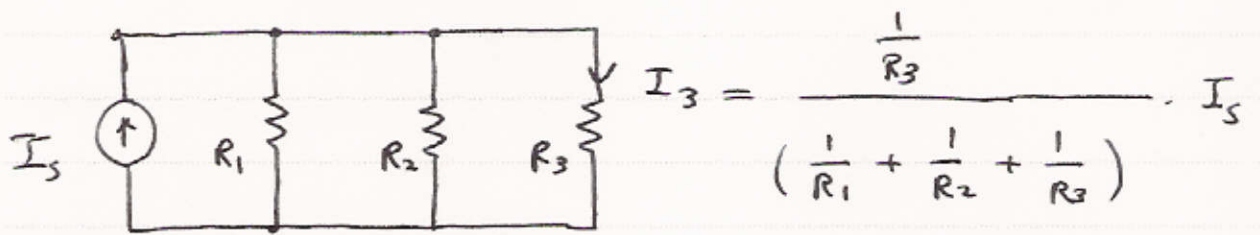
$$V_2 = \frac{R_2}{R_1 + R_2 + R_3} V_s$$



§ 2.4 Node Voltage Analysis

1. Select a reference node ($V = 0$)
2. Assign node voltages as variables.
3. Apply KCL at each node. to get circuit equations
4. Solve for node voltages

Fig. 2.16

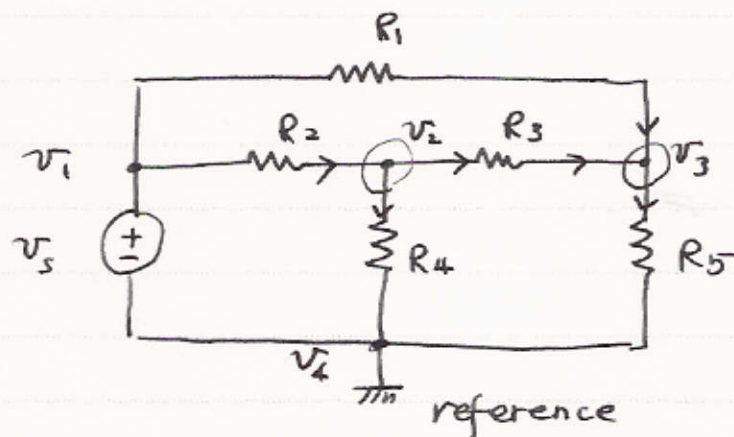

$$v_1 = v_s \quad : \text{ known (given)}$$

$$v_4 = 0 \quad : \text{ selected as 0 (reference)}$$

$$\frac{(v_1 - v_2)}{R_2} = \frac{v_2}{R_4} + \frac{(v_2 - v_3)}{R_3} \quad \text{--- ①}$$

$$\frac{(v_1 - v_3)}{R_1} + \frac{(v_2 - v_3)}{R_3} = \frac{v_3}{R_5} \quad \text{--- ②}$$

$$\begin{bmatrix} a_{11} & a_{12} \\ a_{21} & a_{22} \end{bmatrix} \begin{bmatrix} v_1 \\ v_2 \end{bmatrix} = \begin{bmatrix} b_1 \\ b_2 \end{bmatrix}$$

$$A \cdot v = b$$

$$\text{Solve for } v = A^{-1} \cdot b$$

- Note) 1) Reference node : $v_{ref} = 0$
 2) Voltage source \rightarrow voltage will be known
 3) Apply KCL for unknown node voltages.
 4) # of unknown voltages = # of equations

Fig. 2.18 : Explain


Fig. 2.19 : Explain

Fig. 2.20 : Explain

Fig. 2-23 : Explain

- Super node : Treat voltage source as a node
 Apply KCL at the supernode (area)

Fig. 2.24

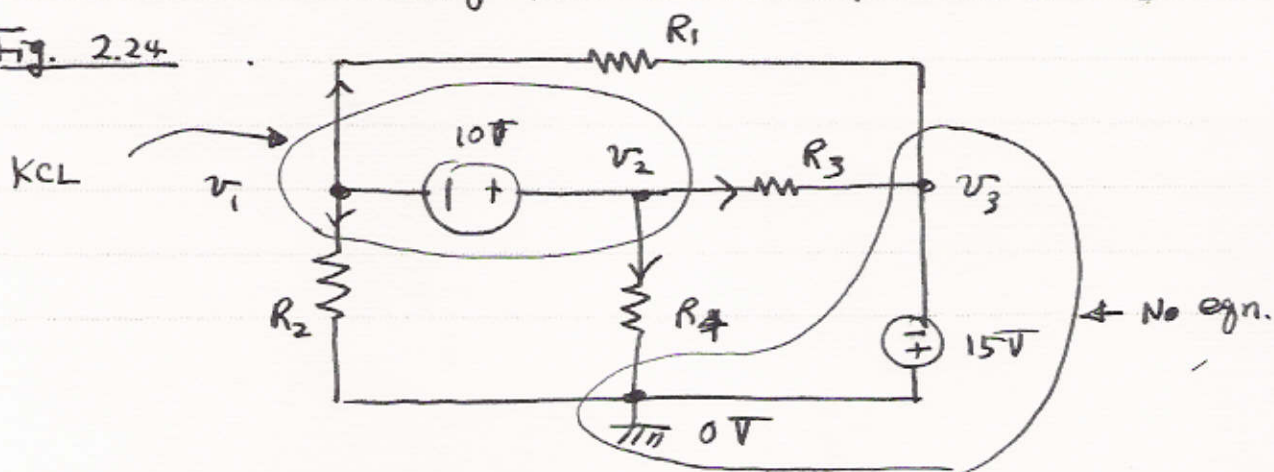

$$v_3 = -15 \text{ V} \quad : \text{ Known}$$

$$v_2 = v_1 + 10 \quad : \text{ Constraint}$$

KCL at Supernode:


$$\frac{v_1}{R_2} + \frac{v_1 - (-15)}{R_1} + \frac{v_1 + 10}{R_4} = 0$$

Solve for v_1 .

Note) (# of equations) = (# of nodes) - 1 - (# of VS)

- Circuit with dependent source

Fig. 2.27

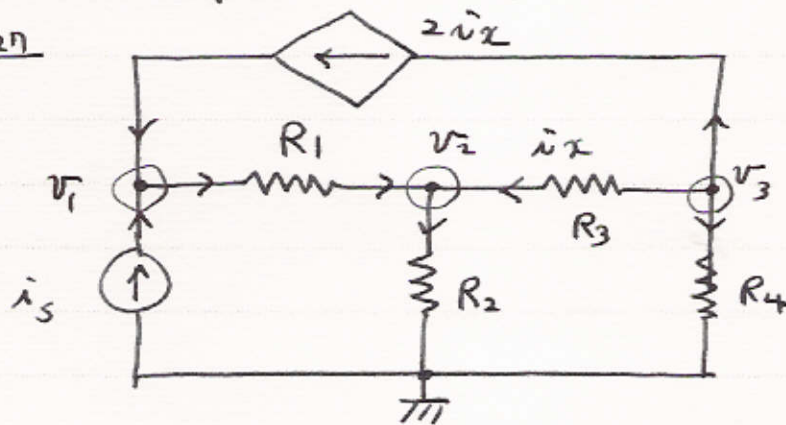

$$\cancel{i_s} + i_s + 2i_x = \frac{v_1 - v_2}{R_1} \quad \text{--- (1)}$$

$$\frac{v_1 - v_2}{R_1} + \frac{v_3 - v_2}{R_3} = \frac{v_2}{R_2} \quad \text{--- (2)}$$


$$2i_x + \frac{v_3 - v_2}{R_3} + \frac{v_3}{R_4} = 0 \quad \text{--- (3)}$$

$$\text{where, } i_x = \frac{v_3 - v_2}{R_3} \quad \text{--- (4)}$$

§ 2.5 Mesh Current Analysis

- Mesh : Elementary loop.
- 1. Select meshes (loops)
- 2. Assign mesh currents as variables
- 3. Apply KVL for each mesh to get circuit eqns.
- 4. Solve for the mesh current.
- (# of equations) = (# of meshes) - (# of CS).

• Fig. 2.32

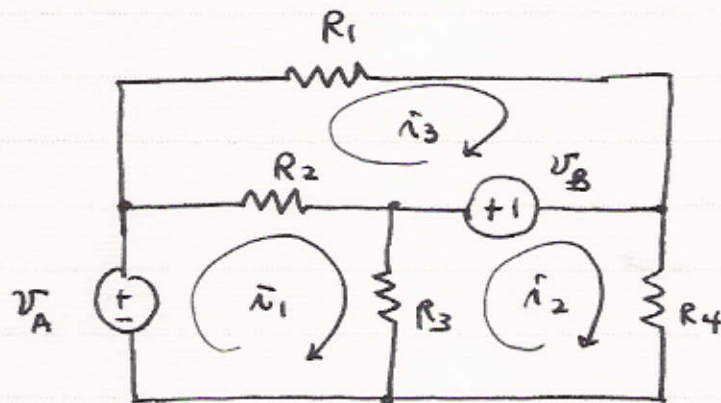

$$V_A = R_2 (i_1 - i_3) + R_3 (i_1 - i_2)$$

$$0 = R_3 (i_2 - i_1) + V_B + R_4 \cdot i_2$$

$$0 = R_1 \cdot i_3 + V_B + R_2 (i_3 - i_1)$$

→ Solve for $\{i_1, i_2, i_3\}$


(f) - Compare to Node Analysis

- Note) Loop current and Branch current

Fig. 2.32 b) Explain.

• Super Mesh : Mesh by eliminating current source

Fig 2.36

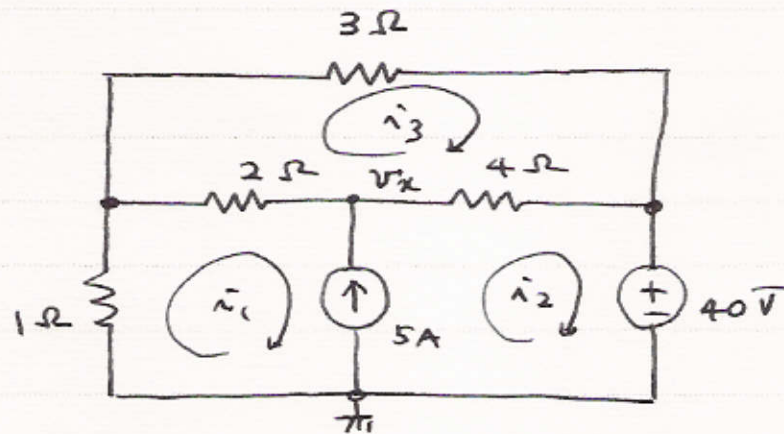

$$1. i_1 + 2(i_1 - i_3) + v_x = 0 \quad \text{--- (1)}$$


$$-v_x + 4(i_2 - i_3) + 40 = 0 \quad \text{--- (2)}$$

$$3 \cdot i_3 + 4(i_3 - i_2) + 2(i_3 - i_1) = 0 \quad \text{--- (3)}$$

$$i_2 - i_1 = 5 \quad \text{--- (4)}$$

Note) Dummy variable v_x is introduced.

After ~~By~~ Eliminating current source,

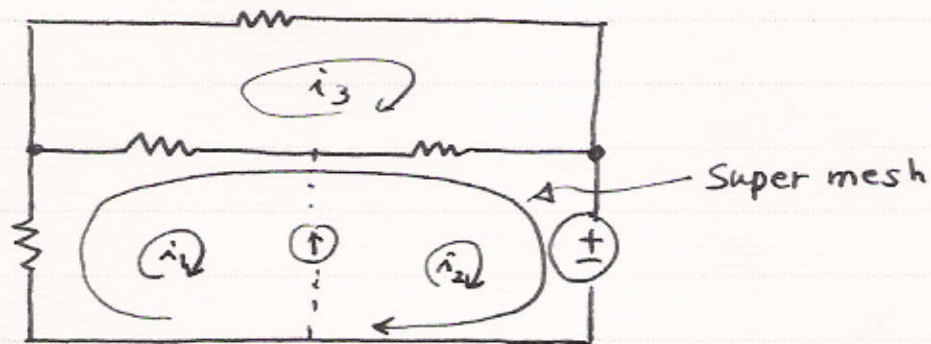


apply KVL along the super mesh.

$$\text{Super Mesh : } 1 \cdot i_1 + 2(i_1 - i_3) + 4(i_2 - i_3) + 40 = 0 \quad \text{--- (1)}$$

$$3 \cdot i_3 + 4(i_3 - i_2) + 2(i_3 - i_1) = 0 \quad \text{--- (2)}$$

$$\bullet \quad i_2 - i_1 = 5 \quad \text{: constraint}$$

• (Example 2.13)

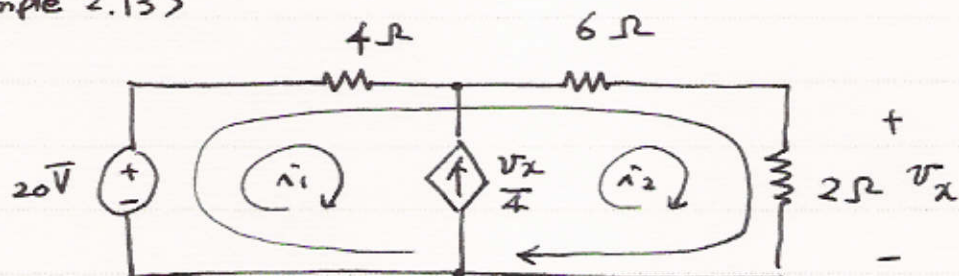


$$20 = 4 \cdot i_1 + 6 \cdot i_2 + 2 \cdot i_2 \quad \text{--- (1)}$$

$$i_2 - i_1 = \frac{1}{4} \cdot v_x = \frac{1}{4} \cdot (2 \cdot i_2) \quad \text{--- (2)}$$


§2-6 Thevenin and Norton Equivalent Circuits

• Source Transformation

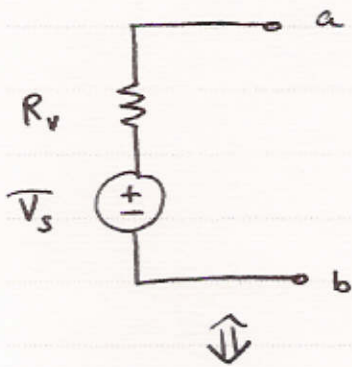

$$V_{oc} = V_s \quad \text{— open circuit voltage}$$
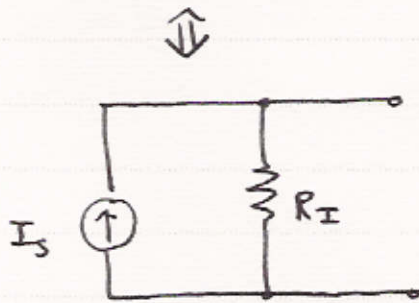
$$I_{sc} = \frac{V_s}{R_s} \quad \text{— short circuit current}$$




$$V_{oc} = R_I \cdot I_s$$

$$I_{sc} = I_s$$




If $I_s = \frac{V_{oc}}{R_v}$ and $R_v = R_I$,

then two circuits are equivalent.


Note)

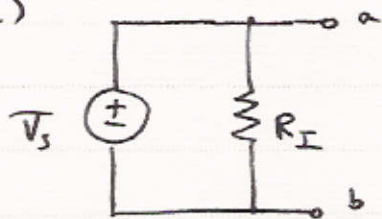

~~R_I in parallel~~
 \Leftrightarrow

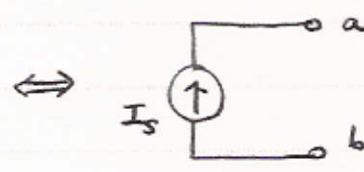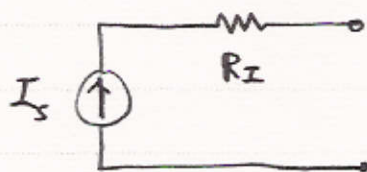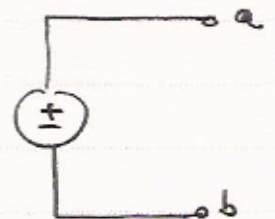

• Thevenin Equivalent Circuit

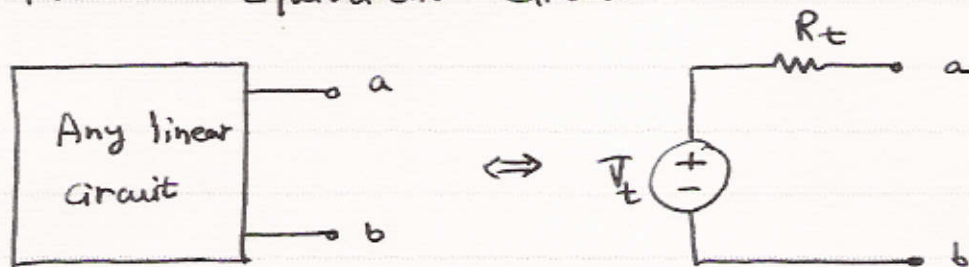


$$V_t = V_{oc} \quad : \text{Thevenin source voltage}$$

$$R_t \quad : \text{internal resistance}$$

$$I_{sc} = \frac{V_t}{R_t} \quad : \text{short circuit current}$$

$$\rightarrow R_t = \frac{V_{oc}}{I_{sc}} = \frac{V_t}{I_{sc}}$$


Example 2.14 >

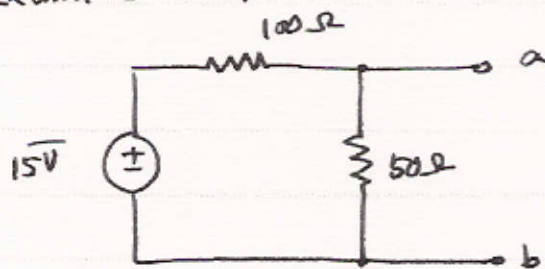

$$V_{oc} = 5V \quad , \quad I_{sc} = 0.15A$$

$$R_t = \frac{5}{0.15} = 33.3 \Omega$$

<Example 2.15>

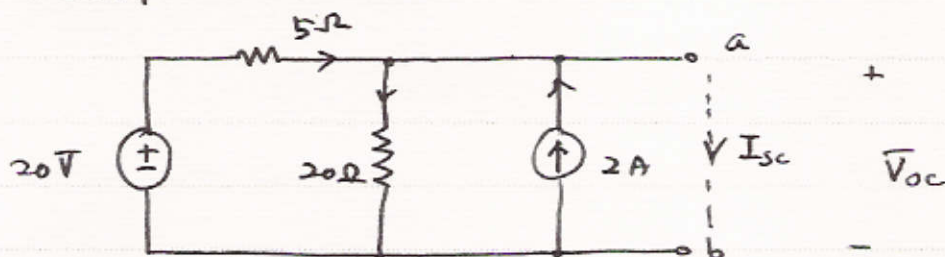


$$\frac{20 - V_{oc}}{5} + 2 = \frac{V_{oc}}{20} \rightarrow V_{oc} = 24 \text{ V}$$

$$I_{sc} = \frac{20}{5} + 2 - \frac{0}{20} \rightarrow I_{sc} = 6 \text{ A}$$

$$R_t = \frac{24}{6} = 4 \Omega$$


Note) Source elimination

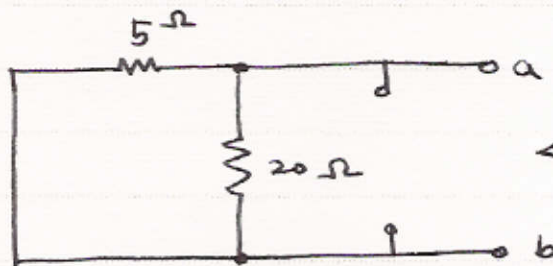- [Short independent VS → Super node
- [Open independent CS → Super mesh



$$\leftarrow R_t = 5 \parallel 20 = 4 \Omega$$

<Example 2.16 >

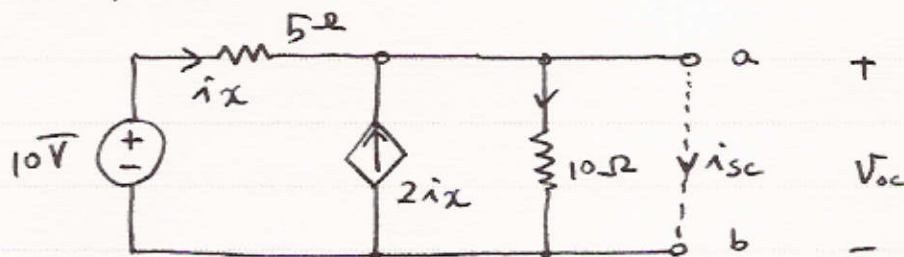


$$\frac{10 - V_{oc}}{5} + 2 \times \frac{10 - V_{oc}}{5} = \frac{V_{oc}}{10} \rightarrow V_{oc} = 8.57 \text{ (V)}$$

$$\frac{10 - 0}{5} + 2 \times \frac{10}{5} = i_{sc} \rightarrow i_{sc} = 6 \text{ (A)}$$

$$R_t = \frac{V_{oc}}{i_{sc}} = 1.43 \text{ (}\Omega\text{)}$$

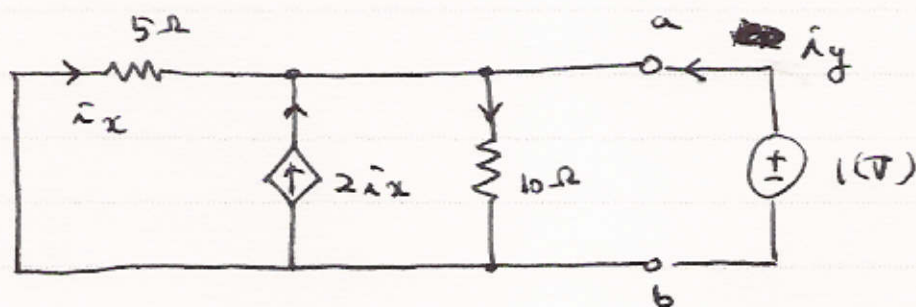By eliminating the voltage source, we get




And assume a dummy VS is applied on a-b.

$$i_y = \frac{1}{10} - 3 \cdot i_x = \frac{1}{10} - 3 \times \left(\frac{-1}{5}\right) = \frac{7}{10} \text{ (A)}$$


$$\rightarrow R_t = \frac{1 \text{ (V)}}{i_y \text{ (A)}} = \frac{10}{7} \text{ (}\Omega\text{)}$$

We get the Thevenin's circuit as

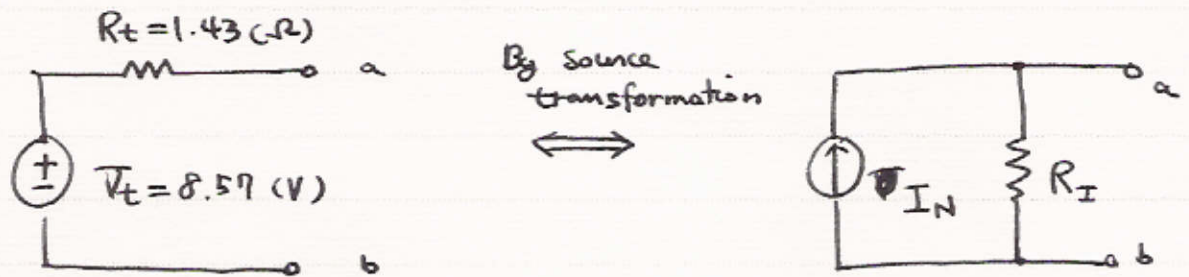

where $I_N = \frac{V_T}{R_T}$ and $R_N = R_T$.

• Norton's Equivalent Circuit

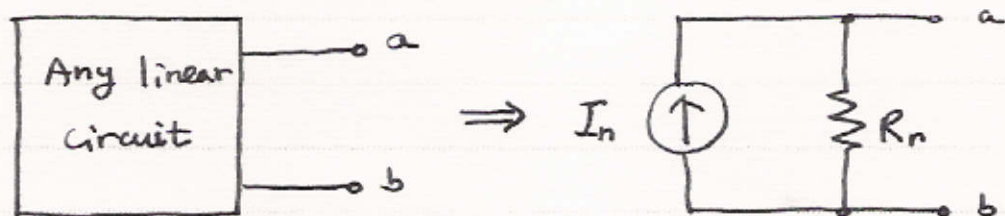


$$I_{sc} = I_n$$

$$V_{oc} = R_n \cdot I_n$$

$$R_n = \frac{V_{oc}}{I_{sc}}$$

< Example 2.17 >

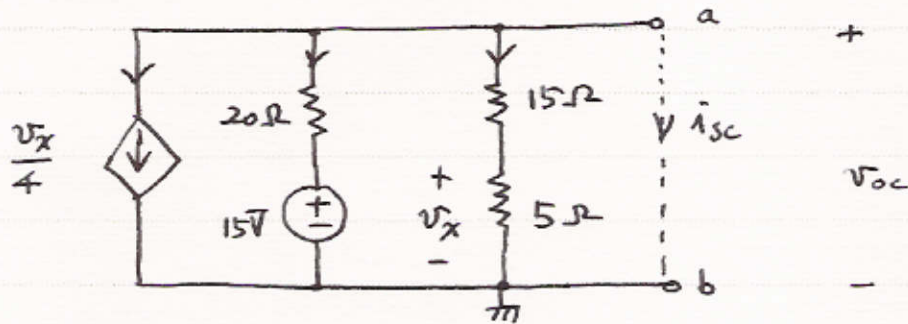

OPEN: $\frac{v_x}{4} + \frac{v_{oc} - 15}{20} + \frac{v_{oc}}{20} = 0$ — ①

where $v_x = \frac{1}{4} v_{oc}$ — ②


$\rightarrow v_{oc} = 4.62 \text{ (V)}$

SHORT: $\frac{v_x}{4} + \frac{0 - 15}{20} + \frac{0}{20} + i_{sc} = 0$ — ①

where $v_x = 0$ — ②

$\rightarrow i_{sc} = 0.75 \text{ (A)}$

By source elimination:

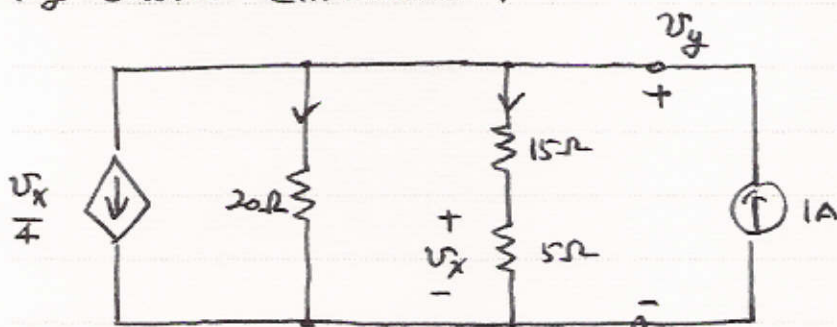


$$\frac{v_x}{4} + \frac{v_y}{20} + \frac{v_y}{20} = 1 \quad \text{--- ①}$$


$$\text{where } v_x = \frac{1}{4} v_y \quad \text{--- ②}$$

$$\rightarrow v_y = 6.15 \text{ (V)}$$

By source transformation:

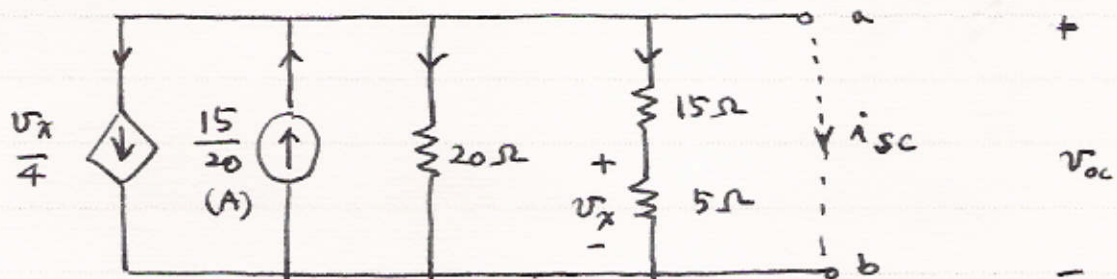

- Maximum Power Transfer

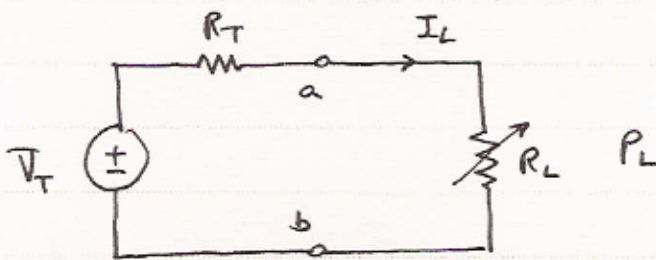



$$P_L = \left(\frac{V_T}{R_T + R_L} \right)^2 \cdot R_L$$

$$\frac{dP_L}{dR_L} = 0 \quad \rightarrow \quad \underline{R_T = R_L}$$

$$P_{L \max} = \frac{V_T^2}{4R_T}$$


§2.1 Superposition Principle

<Example 2.20>

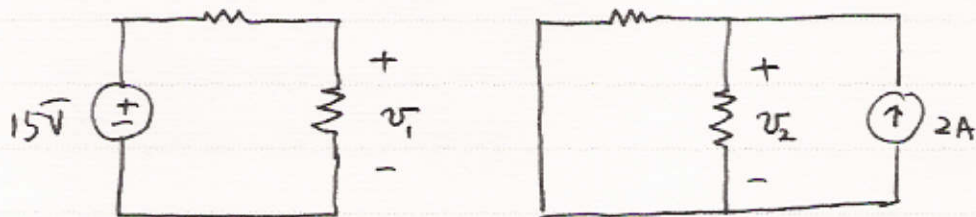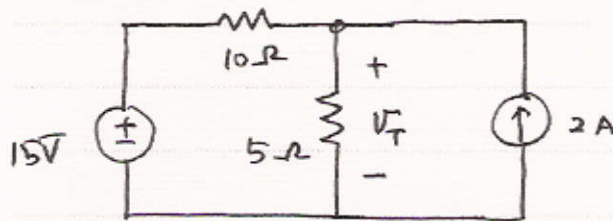


→ $v_T = v_1 + v_2$ by superposition (linearity)

- With dependent source:

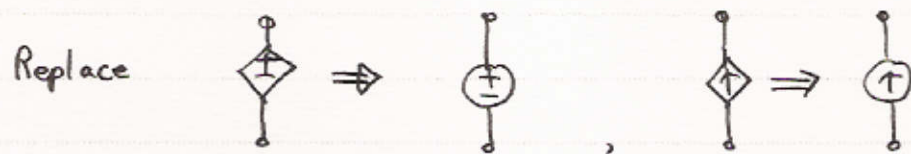

then apply the superposition principle

<Fig. 262> Explain

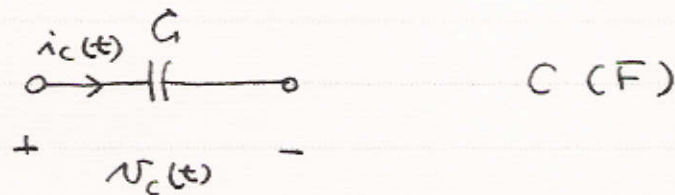CH.3 Inductance and Capacitance§ 3-1 Capacitor

$$q(t) = C \cdot v_c(t) \quad : \text{charge}$$



$$i_c(t) = \frac{dq(t)}{dt} = C \cdot \frac{dv_c(t)}{dt}$$


$$v_c(t) = v_c(0) + \frac{1}{C} \int_0^t i_c(\tau) \cdot d\tau$$

$$p_c(t) = v_c(t) \cdot i_c(t) = C \cdot v_c(t) \cdot \frac{dv_c(t)}{dt} \quad (\text{W})$$

$$w_c(t) = \int_{t_0}^t p(\tau) \cdot d\tau = \int_0^{v_c(t)} C \cdot v_c \cdot dv_c \quad : \text{Stored energy}$$
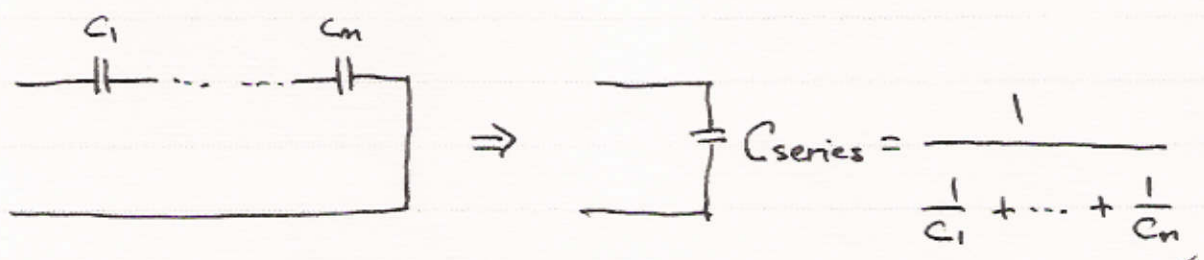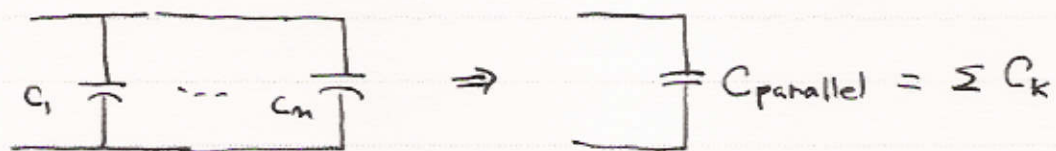
$$= \frac{1}{2} C \cdot v_c^2(t) = \frac{1}{2} v_c(t) \cdot q(t) = \frac{1}{2} \frac{q^2(t)}{C} \quad (\text{J})$$



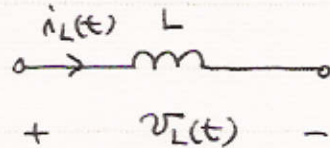§ 3-4 Inductor

$$\lambda(t) = L \cdot i_L(t) \quad : \text{ Flux linkage}$$


$$v_L(t) = \frac{d\lambda(t)}{dt} = L \cdot \frac{di_L(t)}{dt}$$

$$i_L(t) = i_L(0) + \frac{1}{L} \int_0^t v_L(\tau) \cdot d\tau$$


$$P_L(t) = v_L(t) \cdot i_L(t) = L \cdot i_L(t) \cdot \frac{di_L}{dt}$$

$$w_L(t) = \int_0^t P_L(\tau) \cdot d\tau = \int_0^{i_L(t)} L \cdot i_L \cdot di_L \quad : \text{ stored energy}$$

$$= \frac{1}{2} L \cdot i_L^2(t) = \frac{1}{2} i_L(t) \cdot \lambda(t) = \frac{1}{2} \frac{\lambda^2(t)}{L} \quad (\text{J})$$

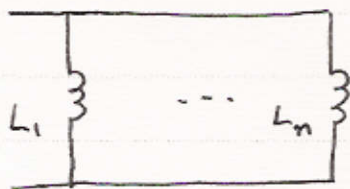

 \Rightarrow


$$L_{\text{parallel}} = \frac{1}{\frac{1}{L_1} + \dots + \frac{1}{L_n}}$$

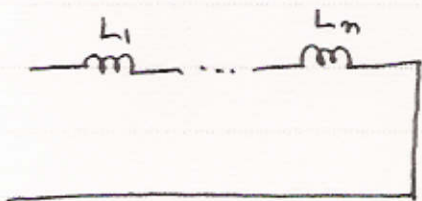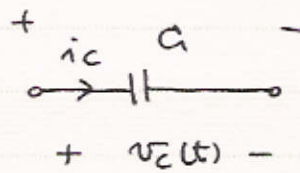
 \Rightarrow


$$L_{\text{series}} = L_1 + \dots + L_n$$

Date : 22-1



$$i_c(t) = C \frac{dv_c}{dt}$$


$v_c(t)$: continuous

$$v_c(0^-) = v_c(0^+)$$

Open for DC



Take $v_c(t)$ as
variable

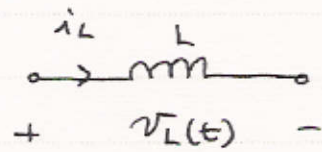

$$v_L(t) = L \cdot \frac{di_L}{dt}$$

$i_L(t)$: continuous

$$i_L(0^-) = i_L(0^+)$$


Short for DC



Take $i_L(t)$ as
variable

CH.4 Transients

§4.1 R-C Circuits

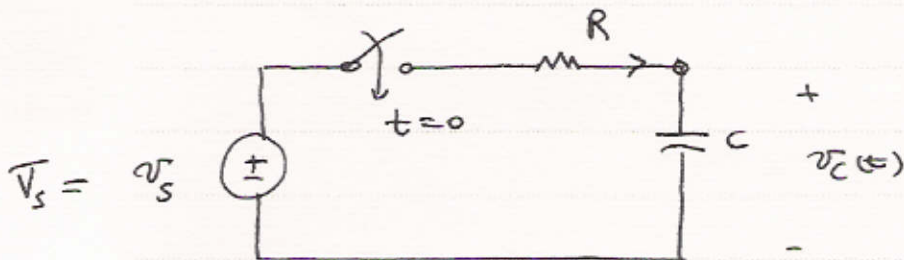

$$t=0^- : v_c(\bar{\omega}) = 0 = v_c(0^+)$$

$$t \geq 0^+ :$$

$$v_s(t) = R \cdot i(t) + v_c(t)$$

$$i(t) = C \frac{dv_c}{dt} \quad \uparrow$$

$$v_s(t) = RC \cdot \frac{dv_c}{dt} + v_c(t)$$

$$\frac{dv_c}{dt} + \frac{1}{RC} \cdot v_c(t) = \frac{\bar{V}_c}{RC}$$

$$s + \frac{1}{RC} = 0 \quad \rightarrow \quad s = -\frac{1}{RC}$$

$$v_c(t) = A \cdot e^{-\frac{t}{RC}} + B$$

$t \rightarrow \infty$: steady state


$$v_c(\infty) = B = \bar{V}_s$$

$t = 0$: initial condition

$$v_c(0) = A + \bar{V}_s = 0, \quad A = -\bar{V}_s$$

$$\therefore v_c(t) = \bar{V}_s \left[1 - e^{-\frac{1}{RC}t} \right], \quad \text{for } t \geq 0$$

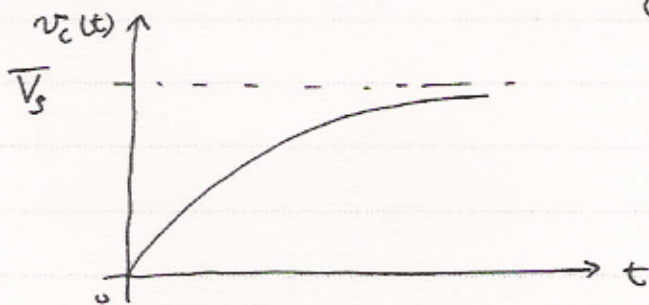Where, $\tau = RC$: time constant
(Speed of change)




cf) Using KCL,

$$\frac{V_s - v_c(t)}{R} = C \frac{dv_c}{dt}$$

$$V_s(t) = RC \frac{dv_c}{dt} + v_c(t)$$

§4-3 R-L Circuits

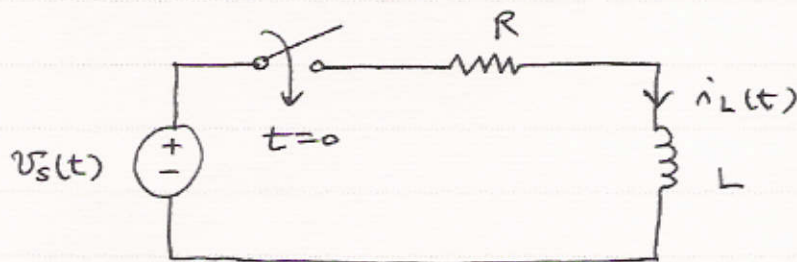

$$t=0^- : i_L(0^-) = 0 = i_L(0^+)$$

$$t \geq 0^+ : v_s(t) = R \cdot i_L(t) + L \cdot \frac{di_L}{dt}$$

$$\frac{di_L}{dt} + \frac{R}{L} \cdot i_L(t) = \frac{1}{L} \bar{V}_s$$

$$s + \frac{R}{L} = 0 \rightarrow s = -\frac{R}{L}$$


$$i_L(t) = A \cdot e^{-\frac{R}{L}t} + B$$

$$t \rightarrow \infty : i_L(\infty) = B = \frac{\bar{V}_s}{R}$$

$$t=0^+ : i_L(0) = A + \frac{\bar{V}_s}{R} = 0$$

$$\therefore i_L(t) = \frac{\bar{V}_s}{R} \left[1 - e^{-\frac{t}{L/R}} \right], \quad (t \geq 0)$$

where $\tau = \frac{L}{R}$: time constant

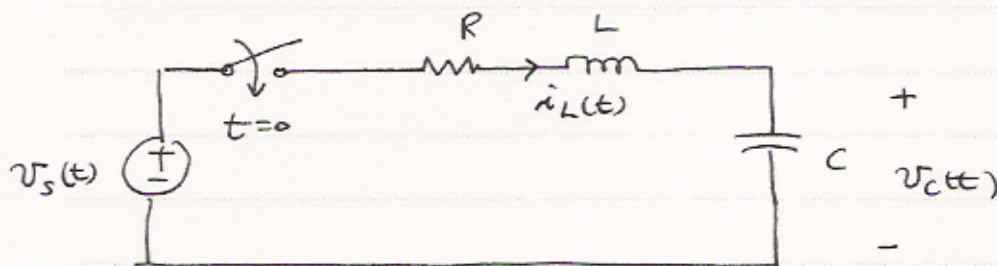§4-5 Second Order Circuits

$$t=0^-: i_L(0^-) = 0 \text{ (A)}, \quad v_C(0^-) = V_{C0} \text{ (V)}$$

$$t \geq 0^+: v_s(t) = R \cdot i_L(t) + L \cdot \frac{di_L}{dt} + v_C(t) \quad \text{--- (1)}$$

$$i_L(t) = C \cdot \frac{dv_C}{dt} \quad \text{--- (2)}$$

② \rightarrow ①:

$$v_s(t) = RC \cdot \frac{dv_C}{dt} + LC \cdot \frac{d^2 v_C}{dt^2} + v_C(t)$$

$$\frac{d^2 v_C}{dt^2} + \frac{R}{L} \cdot \frac{dv_C}{dt} + \frac{1}{LC} \cdot v_C(t) = \frac{1}{LC} \cdot v_s(t) \quad \text{--- (3)}$$

$$\text{②: } v_C'(0^-) = \frac{1}{C} i_L(0^-) = 0$$

$$s^2 + \frac{R}{L} s + \frac{1}{LC} = 0 \quad \text{--- (4)}$$

$$s = s_1, s_2$$

$$v_C(t) = A \cdot e^{s_1 t} + B \cdot e^{s_2 t} + C \quad \text{--- (5)}$$

• Solutions of 2nd order equation

$$\frac{d^2x(t)}{dt^2} + 2\alpha \frac{dx(t)}{dt} + \omega_0^2 \cdot x(t) = f(t)$$

$$x(t) = x_p(t) + x_c(t)$$

- Forced response:

$$\frac{d^2x_p}{dt^2} + 2\alpha \cdot \frac{dx_p}{dt} + \omega_0^2 \cdot x_p(t) = f(t)$$

- Complementary Solution:

$$s^2 + 2\alpha s + \omega_0^2 = 0$$

Let $\zeta = \frac{\alpha}{\omega_0}$: damping ratio

$$s_1, s_2 = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}$$

1) $\zeta > 1$: $x_c(t) = K_1 \cdot e^{s_1 t} + K_2 \cdot e^{s_2 t}$ (over damped)

2) $\zeta = 1$: $x_c(t) = K_1 \cdot e^{s_1 t} + K_2 \cdot t \cdot e^{s_1 t}$ (critically damped)

3) $\zeta < 1$: $x_c(t) = K_1 \cdot e^{-\alpha t} \cdot \cos(\omega_n t) + K_2 \cdot e^{-\alpha t} \cdot \sin(\omega_n t)$


where $s_1, s_2 = -\alpha \pm j\omega_n$ (under damped)

$$= -\alpha \pm j\sqrt{\omega_0^2 - \alpha^2}$$

Date : 28

- Unit step function:
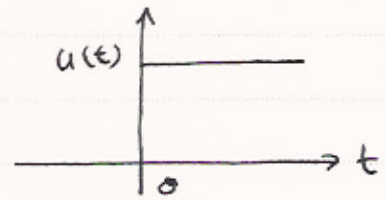
$$u(t) = \begin{cases} 1 & , (t \geq 0) \\ 0 & , (t < 0) \end{cases}$$




- Impulse function (delta function)

$$\frac{du(t)}{dt} = \delta(t)$$


$$\int_{-\infty}^{\infty} \delta(t) \cdot dt = 1$$
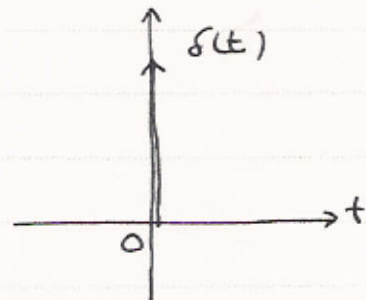
$$\int_{-\infty}^{\infty} f(t) \cdot \delta(t - t_0) \cdot dt = f(t_0)$$





- Rectangular function

$$\nabla [u(t) - u(t-1)]$$

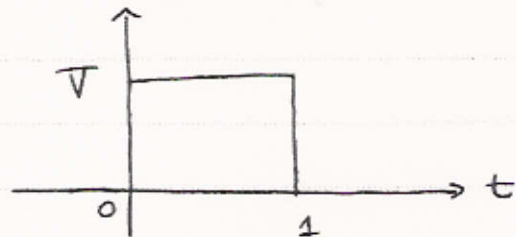


Example)

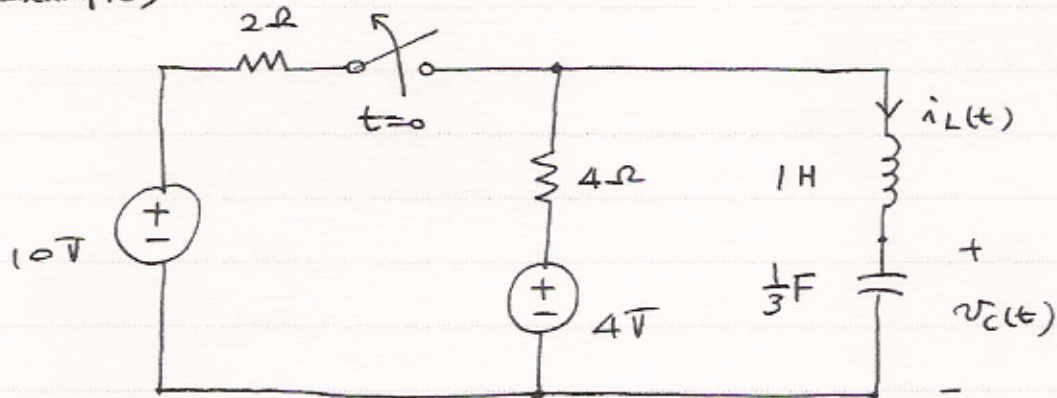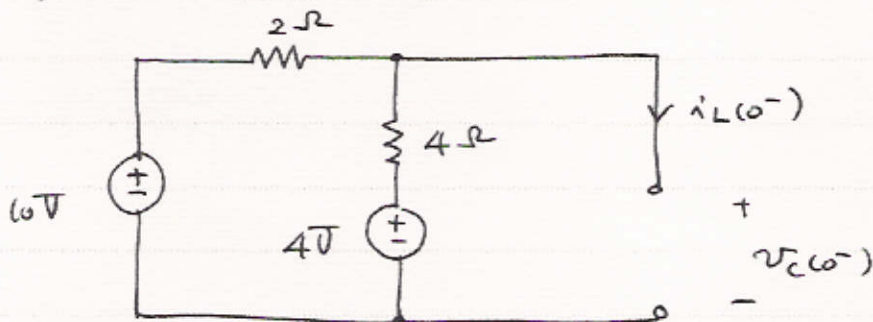a) $t=0^-$: Initial condition

$$i_L(0^-) = 0 \text{ (A)} = i_L(0^+)$$

$$v_C(0^-) = 8 \text{ (V)} = v_C(0^+)$$

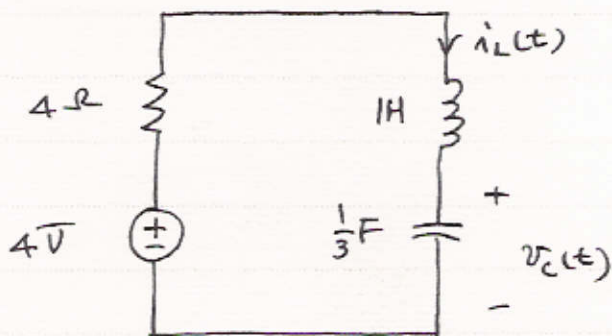b) $t \geq 0^+$:

$$\begin{cases} 4 = 4 \cdot i_L(t) + 1 \cdot \frac{di_L}{dt} + v_C(t) & \text{--- ①} \\ i_L(t) = \frac{1}{3} \frac{dv_C}{dt} & \text{--- ②} \end{cases}$$

② \rightarrow ①:

$$4 = \frac{4}{3} \frac{dv_C}{dt} + \frac{1}{3} \cdot \frac{d^2v_C}{dt^2} + v_C(t)$$

$$\frac{d^2v_C}{dt^2} + 4 \cdot \frac{dv_C}{dt} + 3 \cdot v_C(t) = 12 \quad \text{--- ③}$$

$$s^2 + 4s + 3 = (s+3)(s+1) = 0 \quad \text{--- ④}$$

$$\rightarrow v_C(t) = [A \cdot e^{-3t} + B \cdot e^{-t}] + C$$

$$0 + 4 \cdot 0 + 3 \cdot C = 12 \quad \rightarrow \quad C = 4$$


$$v_C(t) = A \cdot e^{-3t} + B \cdot e^{-t} + 4$$

$$\text{②: } v_C'(0^-) = 3 \cdot i_L(0^-) = 0$$

$$v_C(0^+) = A + B + 4 = 8$$

$$v_C'(0^+) = -3A - B = 0$$
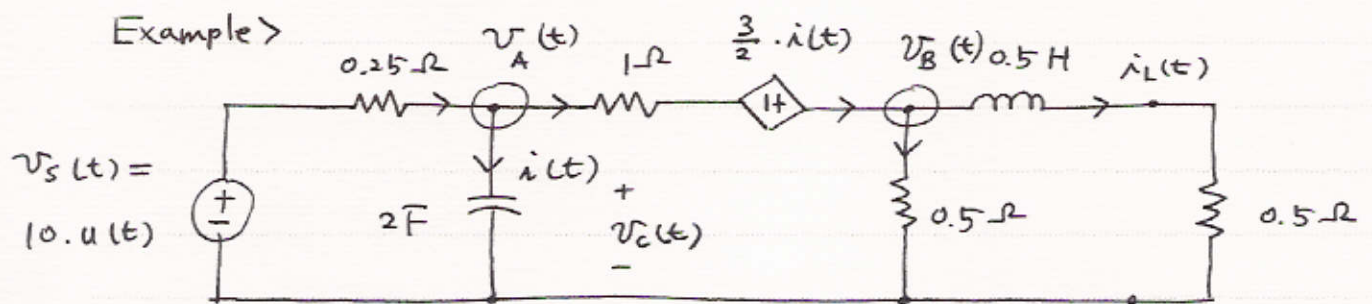
$$\therefore v_C(t) = -2 \cdot e^{-3t} + 6 \cdot e^{-t} + 4, \quad (t \geq 0)$$



a) $t=0^-$; No active source

$$v_c(0^-) = 0 \text{ (V)} = v_c(0^+)$$

$$i_L(0^-) = 0 \text{ (A)} = i_L(0^+)$$

b) $t \geq 0^+$: Nodal Analysis

$$\begin{cases} v_a(t) = v_c(t) \\ v_B(t) = 0.5 \frac{di_L}{dt} + 0.5 i_L(t) \end{cases} \text{ and } i(t) = 2 \cdot \frac{dv_c}{dt}$$

$$A: \frac{10 - v_c}{0.25} = 2 \cdot \frac{dv_c}{dt} + \frac{v_c - \left[\left\{ 0.5 \frac{di_L}{dt} + 0.5 i_L(t) \right\} - \frac{3}{2} \cdot 2 \frac{dv_c}{dt} \right]}{1}$$

$$B: \frac{v_c - \left[\left\{ 0.5 \frac{di_L}{dt} + 0.5 \cdot i_L(t) \right\} - \frac{3}{2} \cdot 2 \frac{dv_c}{dt} \right]}{1}$$

$$= \frac{0.5 \cdot \frac{di_L}{dt} + 0.5 \cdot i_L(t)}{0.5} + i_L(t)$$

Arrange ① and ② as the state equation:

$$\begin{bmatrix} \frac{dv_c(t)}{dt} \\ \frac{di_L(t)}{dt} \end{bmatrix} = \begin{bmatrix} a_{11} & a_{12} \\ a_{21} & a_{22} \end{bmatrix} \begin{bmatrix} v_c(t) \\ i_L(t) \end{bmatrix} + \begin{bmatrix} u_1(t) \\ u_2(t) \end{bmatrix}$$

Initial conditions are obtained as

$$v_c'(0^+) = a_{11} \cdot v_c(0^+) + a_{12} \cdot i_L(0^+) + u_1(0^+)$$

$$i_L'(0^+) = a_{21} \cdot v_c(0^+) + a_{22} \cdot i_L(0^+) + u_2(0^+)$$

In general, the second order ODE is expressed as

$$\begin{cases} p \cdot x_1 = a_{11} \cdot x_1 + a_{12} \cdot x_2 + u_1(t) \\ p \cdot x_2 = a_{21} \cdot x_1 + a_{22} \cdot x_2 + u_2(t) \end{cases}$$

where $p = \frac{d}{dt}$ operator.

To get a single variable differential equation,

$$\begin{cases} (p - a_{11}) \cdot x_1 - a_{12} \cdot x_2 = u_1 \\ -a_{21} \cdot x_1 + (p - a_{22}) \cdot x_2 = u_2 \end{cases}$$

And eliminate x_2 and get

$$\begin{aligned} (p^2 - a_{11} \cdot p - a_{22} \cdot p + a_{11} \cdot a_{22}) \cdot x_1 - a_{12} \cdot a_{21} \cdot x_1 \\ = (p - a_{22}) \cdot u_1 + a_{12} \cdot u_2 \end{aligned}$$

$$\begin{aligned} \left. \begin{aligned} \frac{d^2 x_1}{dt^2} - (a_{11} + a_{22}) \cdot \frac{dx_1}{dt} + (a_{11} \cdot a_{22} - a_{12} \cdot a_{21}) \cdot x_1(t) \\ = \frac{du_1}{dt} - a_{22} \cdot u_1 + a_{12} \cdot u_2 \end{aligned} \right\} \text{--- (a)} \end{aligned}$$

Similarly,

$$\begin{aligned} \left. \begin{aligned} \frac{d^2 x_2}{dt^2} - (a_{11} + a_{22}) \cdot \frac{dx_2}{dt} + (a_{11} \cdot a_{22} - a_{12} \cdot a_{21}) \cdot x_2(t) \\ = \frac{du_2}{dt} - a_{11} \cdot u_1 + a_{21} \cdot u_2 \end{aligned} \right\} \text{--- (b)} \end{aligned}$$

CH. 10 Diodes

§ Semiconductors

• Silicon : covalent bond

• Carriers { electrons (-)
 holes (+)



• p-type { majority carriers - holes
 minority carriers - electrons

• n-type { majority carriers - electrons
 minority carriers - holes


• { Donor - Phosphorus : donates electrons : n-type
 { Acceptor - Boron : accepts electrons : p-type

Diodes


p-n junction

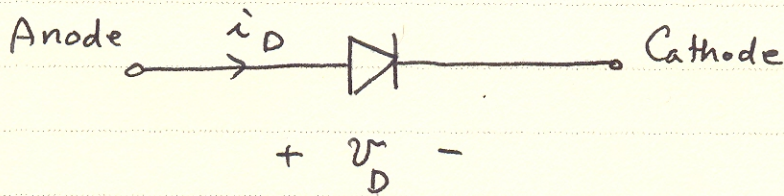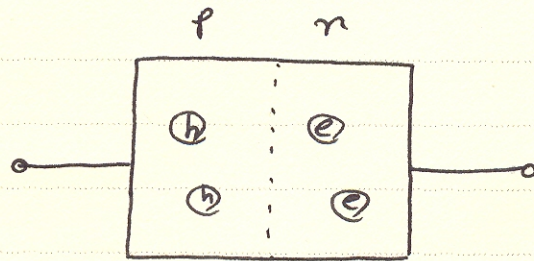


Unbiased p-n junction

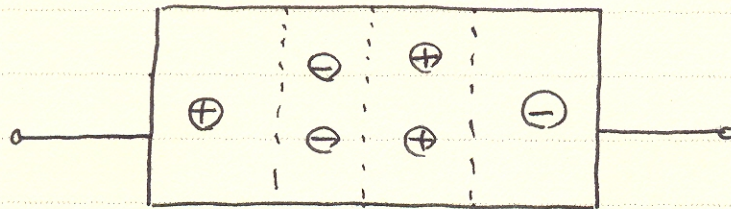

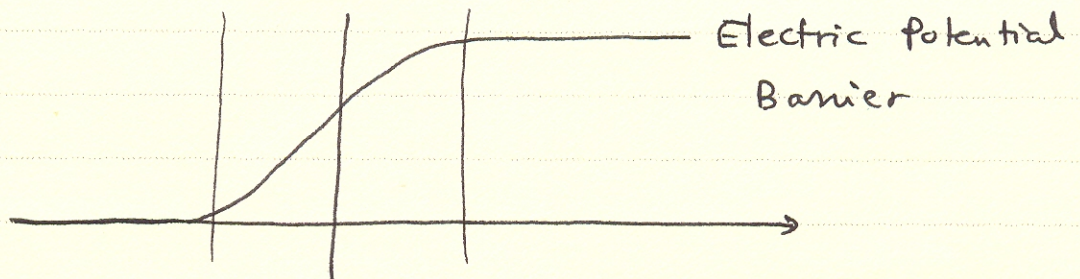\longrightarrow holes } by diffusion
 \longleftarrow electrons }
 depletion region




o Reverse biased p-n junction

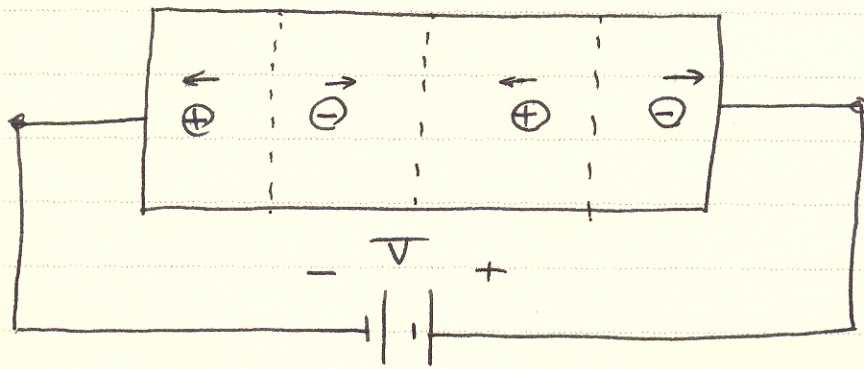


{ depletion region increases
potential barrier increase by V - no more current

o Forward biased p-n junction

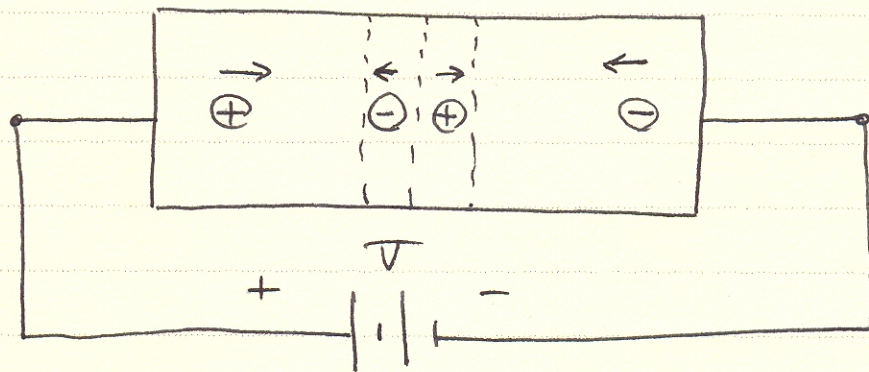

{ depletion region ~~decreases~~ neutralized
potential barrier decreases \rightarrow current flows

• Shockley Equation

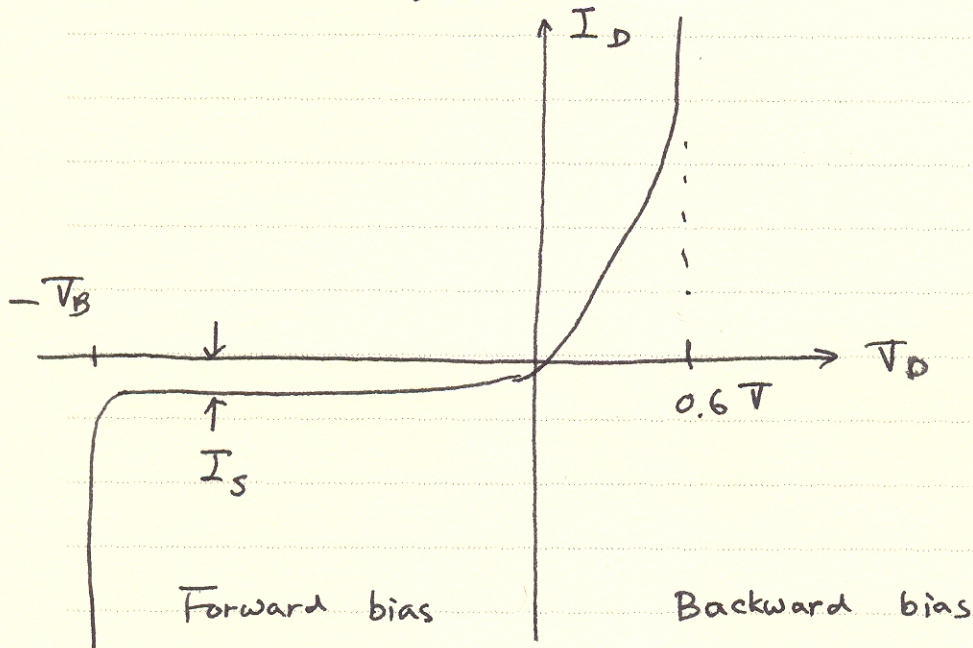

$$i_D = I_S \cdot \left[\exp\left(\frac{V_D}{nV_T}\right) - 1 \right] \quad \text{Remember!}$$

I_S : saturation current ($\sim 10^{-7}A$)

n : emission coefficient (~ 1 for Si)

$$V_T = \frac{kT}{q} = \frac{T}{11600} \quad \text{: Thermal voltage}$$

$$k = 1.38 \times 10^{-23} \quad \text{: Boltzmann constant}$$



$$q = 1.60 \times 10^{-19} \quad \text{: electron charge}$$

V_B : Breakdown voltage


• At room temperature : $T = 293^\circ\text{K}$

$$i_D \approx \begin{cases} I_S \cdot e^{40V_D} & , (V_D > 0.1\text{V}) \\ -I_S & , (V_D < -0.1\text{V}) \end{cases}$$

• By approximation,

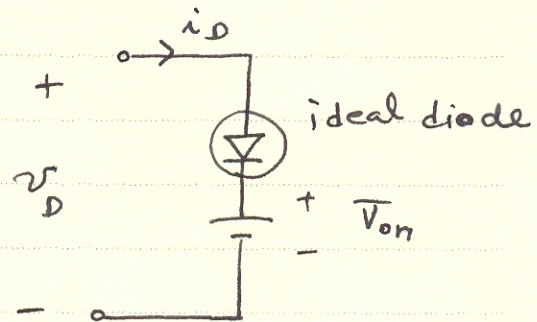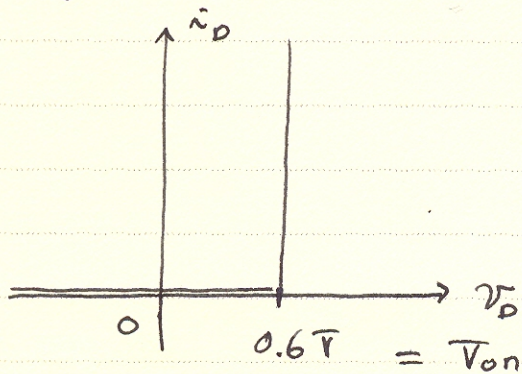

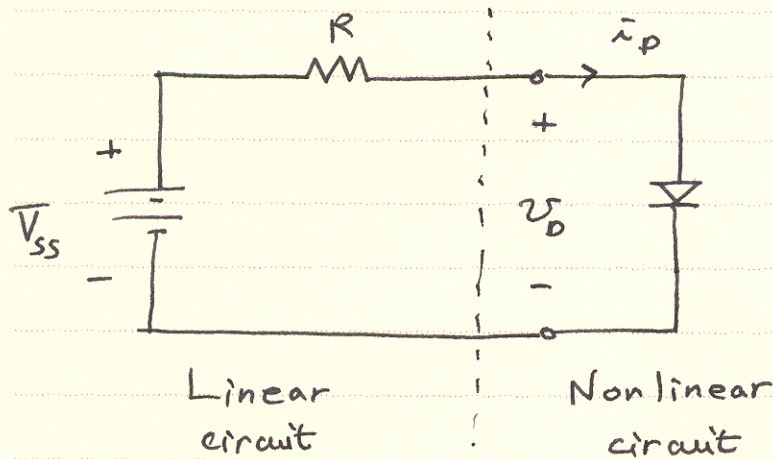
§ 10-2. Load Line Analysis : Graphical Analysis



Linear : $v_D = V_{SS} - R \cdot i_D$


$$i_D = \frac{V_{SS}}{R} - \frac{v_D}{R}$$

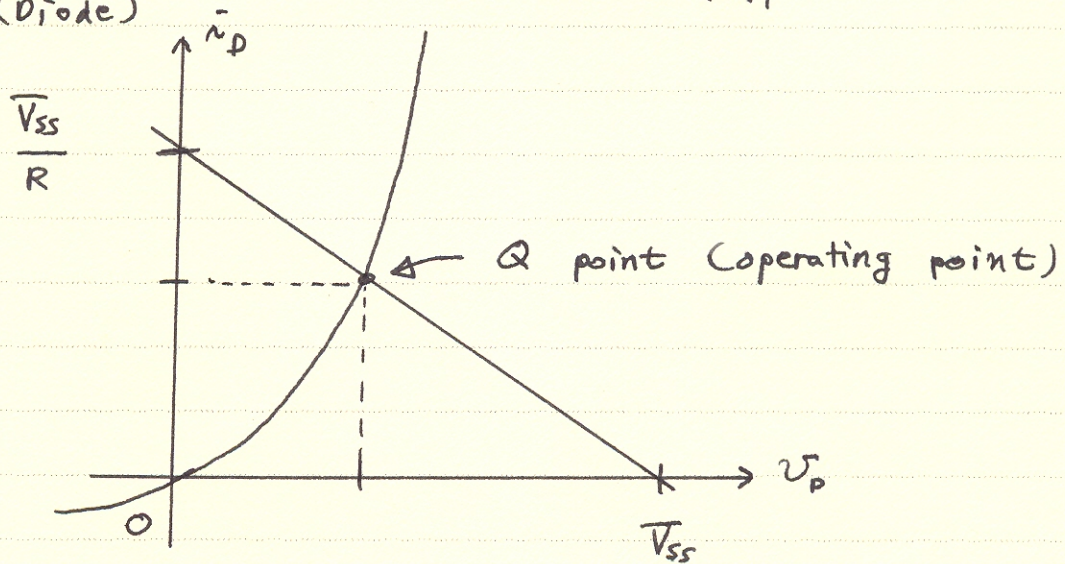Nonlinear : $i_D = I_S \cdot \left[\exp\left(\frac{v_D}{nV_T}\right) - 1 \right]$
(Diode)




§10-6. Rectifier Circuits


o Half wave rectifier

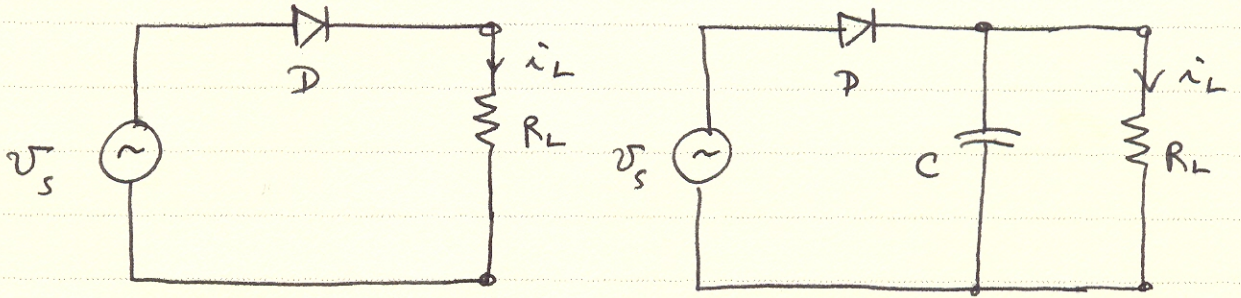

o Full wave rectifier

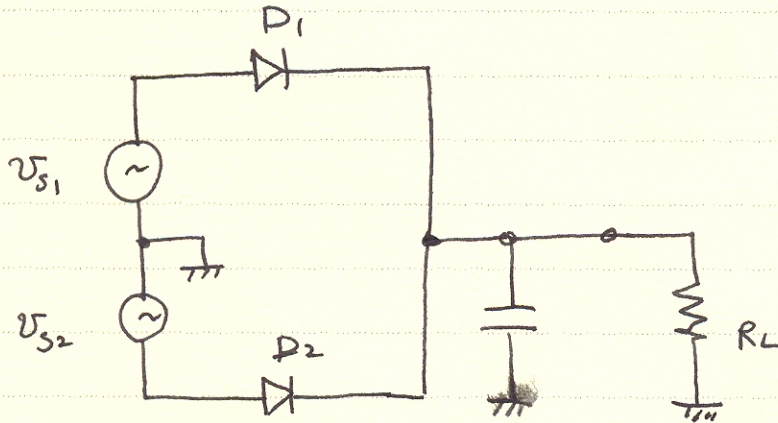


o Diode Bridge

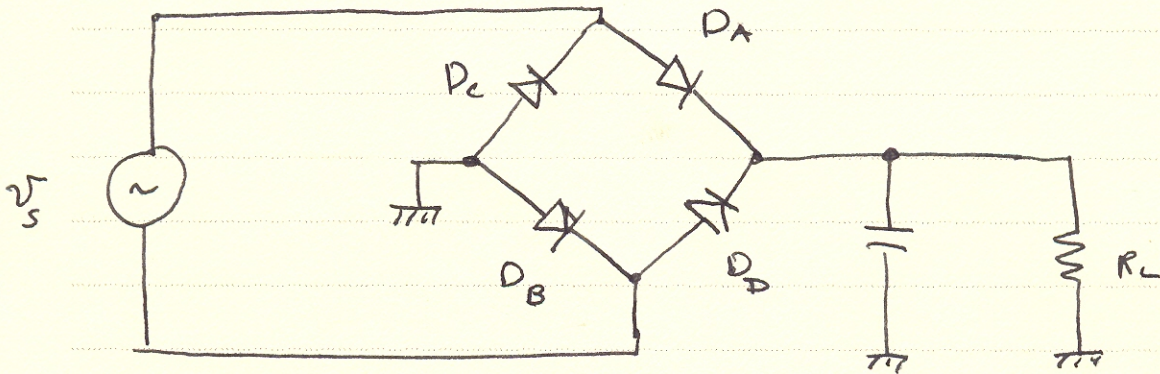

§7-3. Bipolar Junction Transistor (BJT)

- Current and voltage relationship.

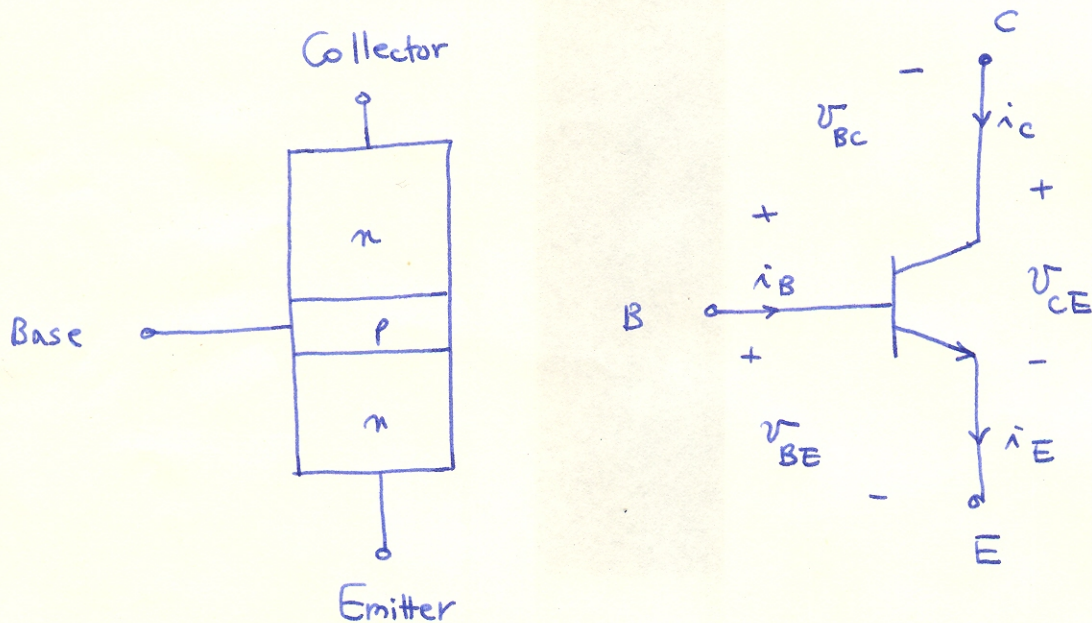

- Bias {
 - base - collector : reverse bias
 - base - emitter : forward bias

- Emitter current

$$i_E = I_{SE} \cdot \left[\exp\left(\frac{V_{BE}}{V_T}\right) - 1 \right] \quad \leftarrow \text{forward biased diode}$$

$$i_E = i_B + i_C$$

- Define α

$$\alpha = \frac{\hat{i}_c}{\hat{i}_E} \quad (= 0.9 \sim 0.999)$$

- Collector current

$$\begin{aligned} \hat{i}_c &= \alpha \cdot \hat{i}_E = \alpha \cdot I_{SE} \cdot \left[\exp\left(\frac{V_{BE}}{V_T}\right) - 1 \right] \\ &\approx I_S \cdot \exp\left(\frac{V_{BE}}{V_T}\right) \end{aligned}$$

where $I_S = \alpha \cdot I_{SE}$

- Base current


$$\hat{i}_B = (1 - \alpha) \cdot \hat{i}_E = (1 - \alpha) \cdot I_{SE} \cdot \left[\exp\left(\frac{V_{BE}}{V_T}\right) - 1 \right]$$

- Define β

$$\beta = \frac{\hat{i}_c}{\hat{i}_B} = \frac{\alpha}{1 - \alpha} \quad (= 10 \sim 1000)$$

$$\rightarrow \hat{i}_c = \beta \cdot \hat{i}_B$$

° Principle of BJT

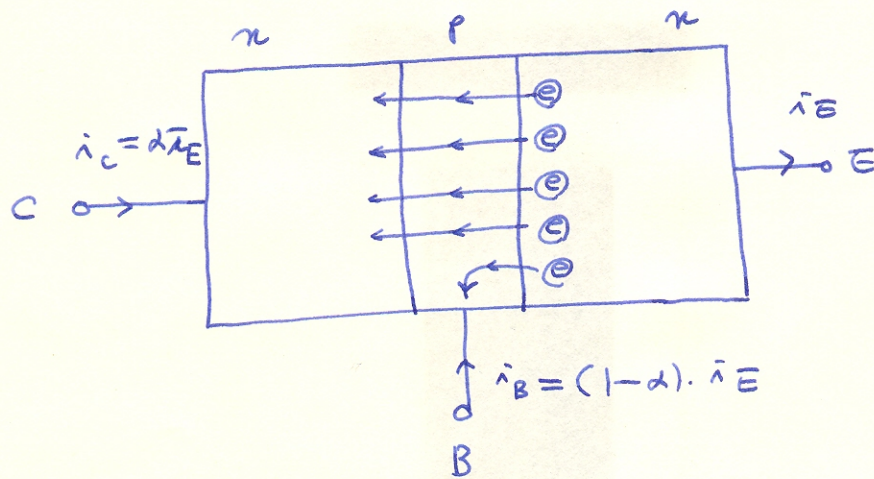

V_{BE} - forward bias

- electrons are injected into base
- base is thin
- most of the electrons (α) are diffused into collector
- only $(1 - \alpha)$ electrons reach base.


ratio α is constant.

$$\rightarrow i_c = \frac{\alpha}{1 - \alpha} \cdot \bar{i}_B = \beta \cdot \bar{i}_B$$



⇒ Collector current \bar{i}_c can be controlled by small \bar{i}_B .

^
Large

Common Emitter Characteristics

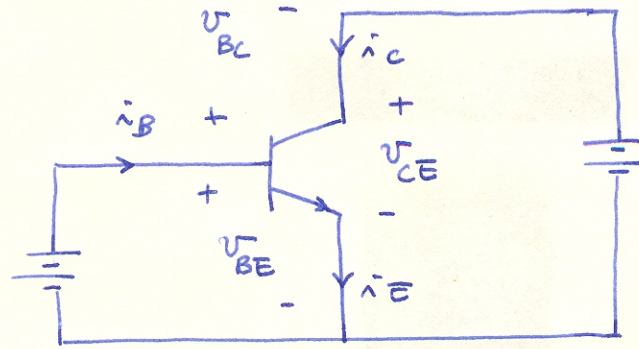

$v-i$ characteristics

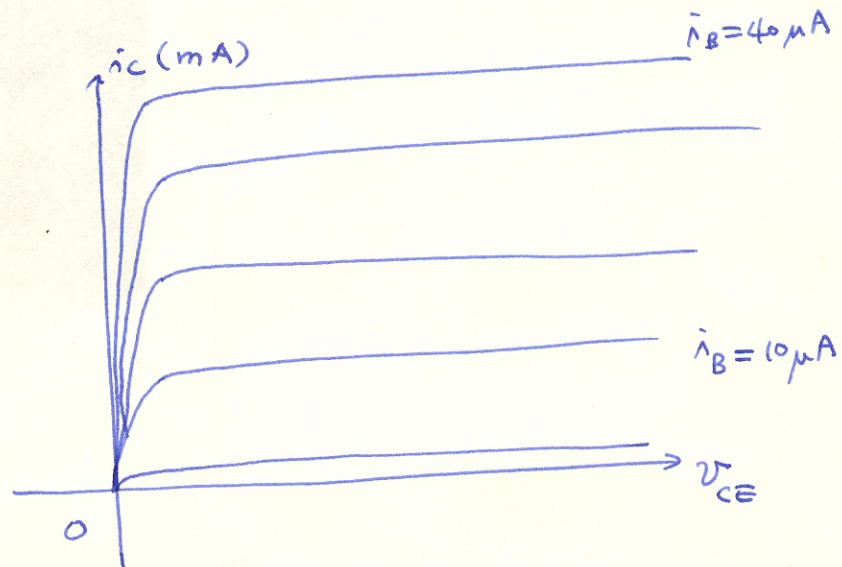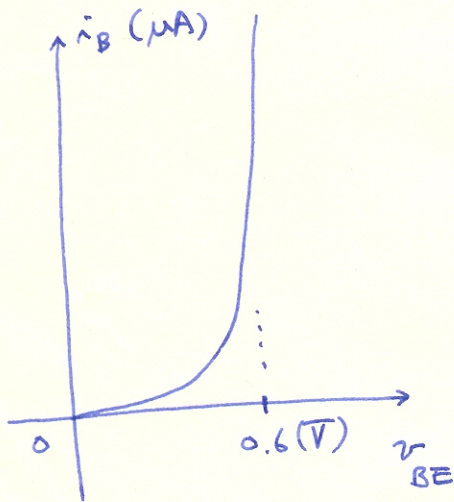


i_C is constant regardless v_{CE} .

$$i_C = \beta \cdot i_B$$


§ Load Line Analysis

• Common Emitter Amplifier.

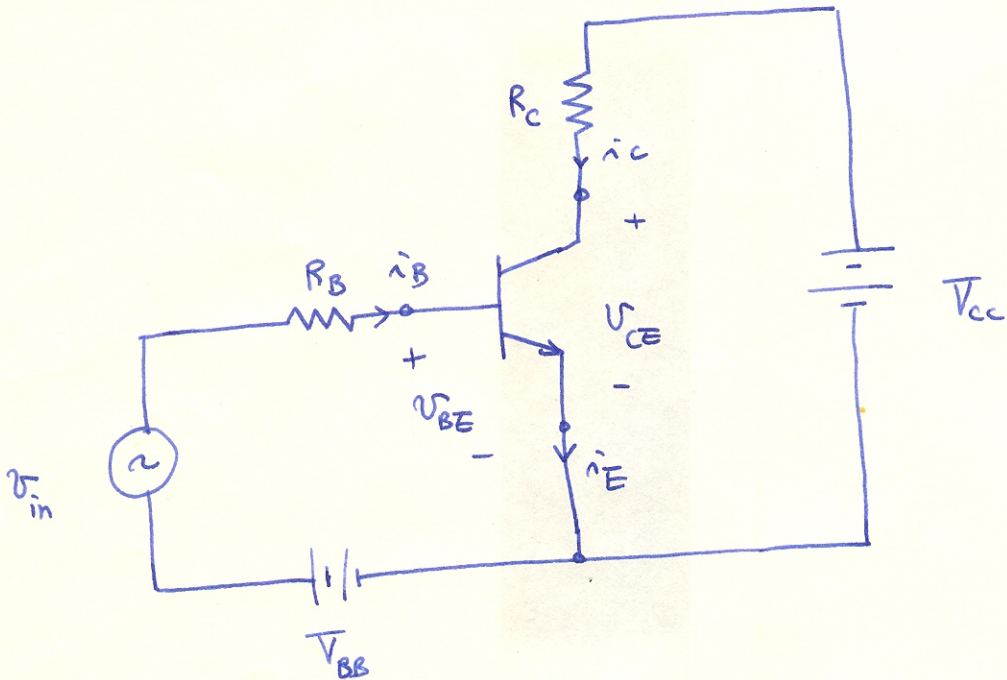


$$V_{BB} + V_{in} = R_B \cdot i_B + V_{BE} \quad : \text{input circuit}$$
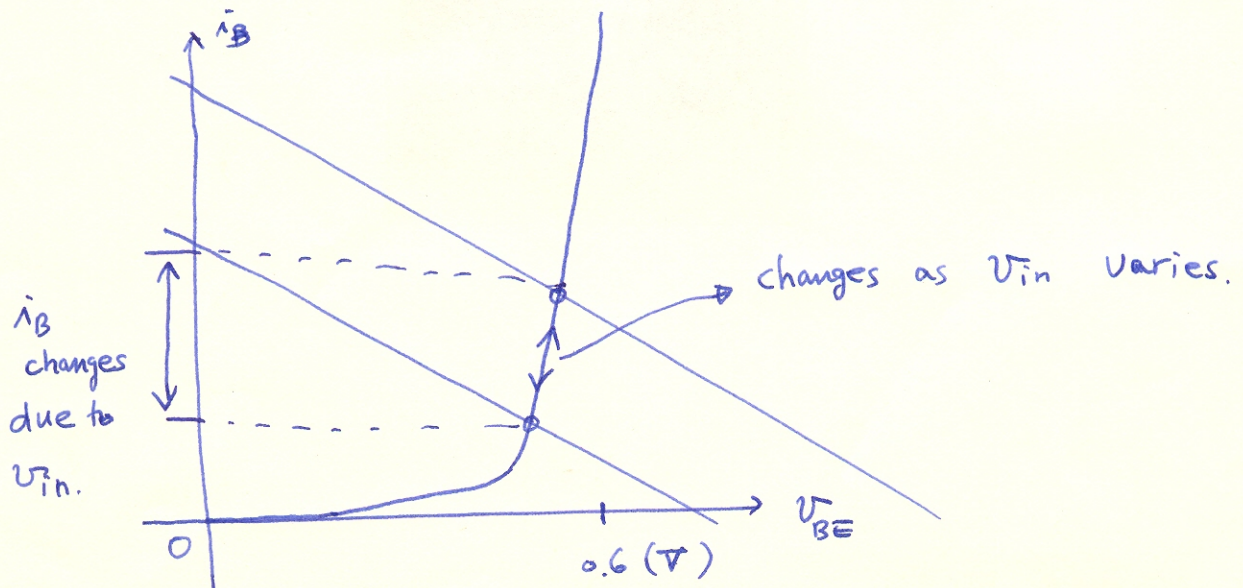
$$V_{CC} = R_C \cdot i_C + V_{CE} \quad : \text{output circuit}$$




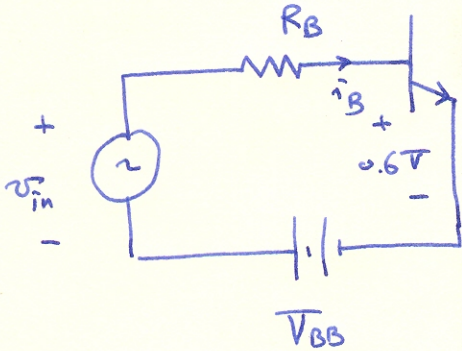- Input circuit analysis : i_B vs. V_{BE}



$$\hat{i}_B \approx \frac{V_{in} + V_{BB} - 0.6}{R_B}$$

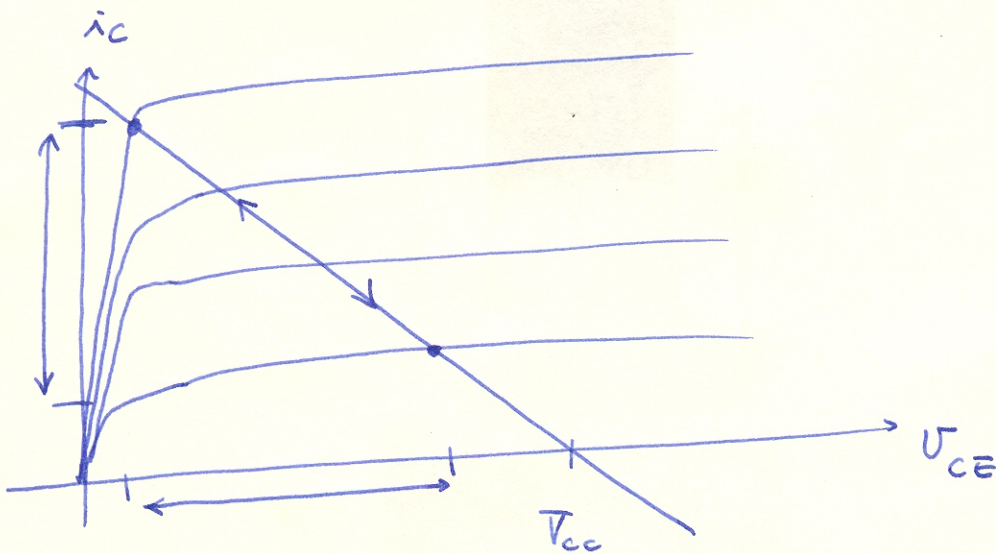- output circuit analysis : i_c vs. V_{CE}




V_{in} changes i_B .

i_B changes i_c and V_{CE} .

$V_{in} \longrightarrow V_{CE}$.

§ BJT Operating regions

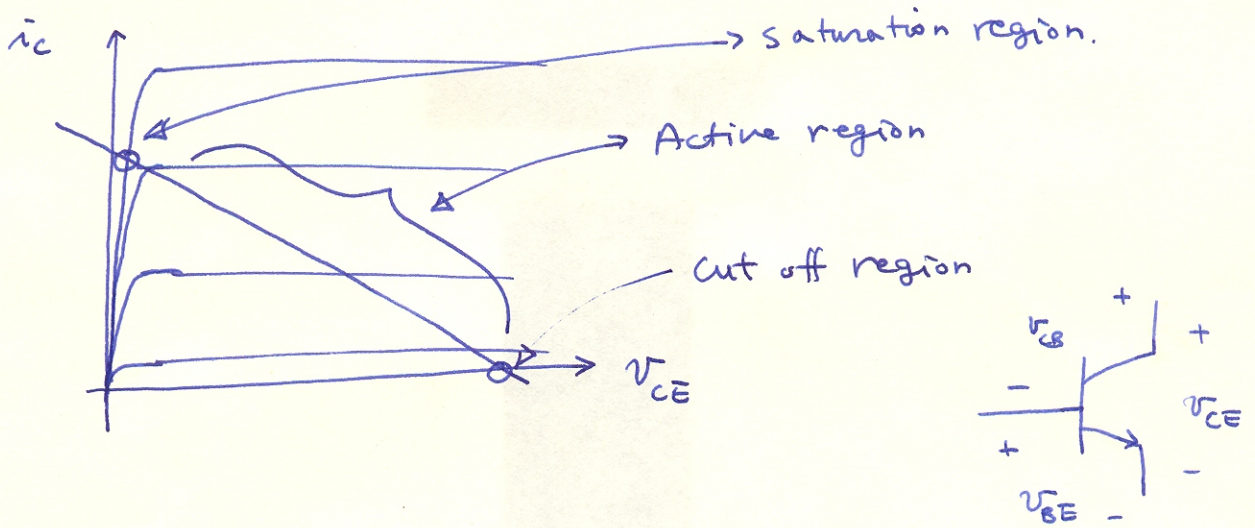

• Active region.

$$i_c = \beta \cdot i_B$$

- B-E : forward bias , $V_{BE} = 0.6\text{V}$
- C-B : reverse bias

• Cut off region


$$i_c = 0$$

- B-E : reverse bias $\rightarrow i_B = 0$
- C-B : reverse bias

• Saturated region


$$i_c < \beta \cdot i_B$$

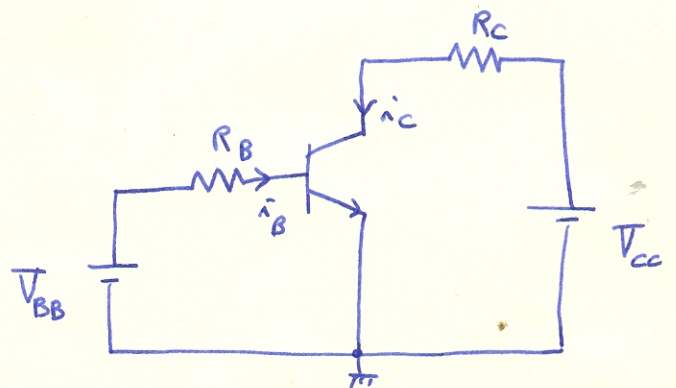- B-E : forward bias
- $V_{CE} \approx 0.2\text{V}$
- C-B : forward bias





As i_B increases, $R_C \cdot i_c \rightarrow V_{CC}$.

Ex).

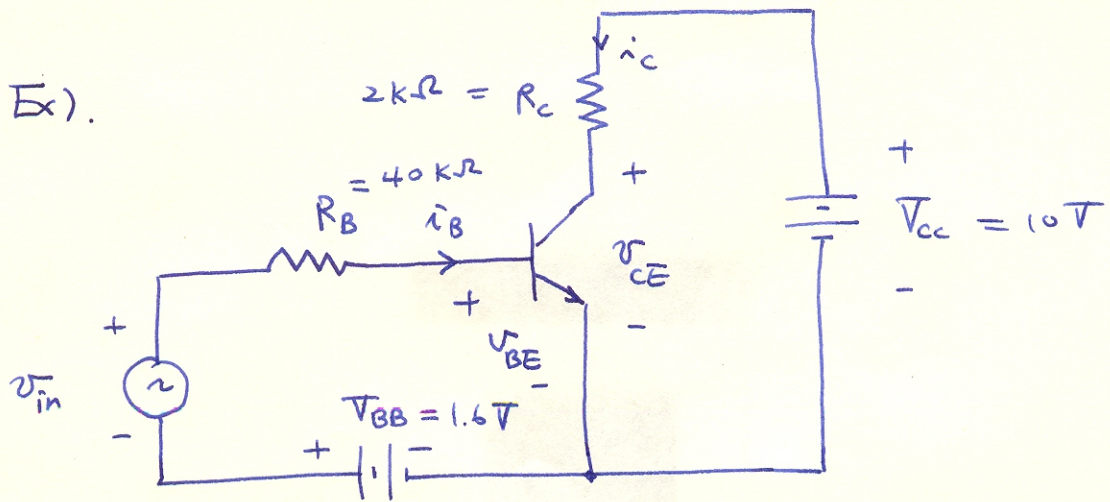

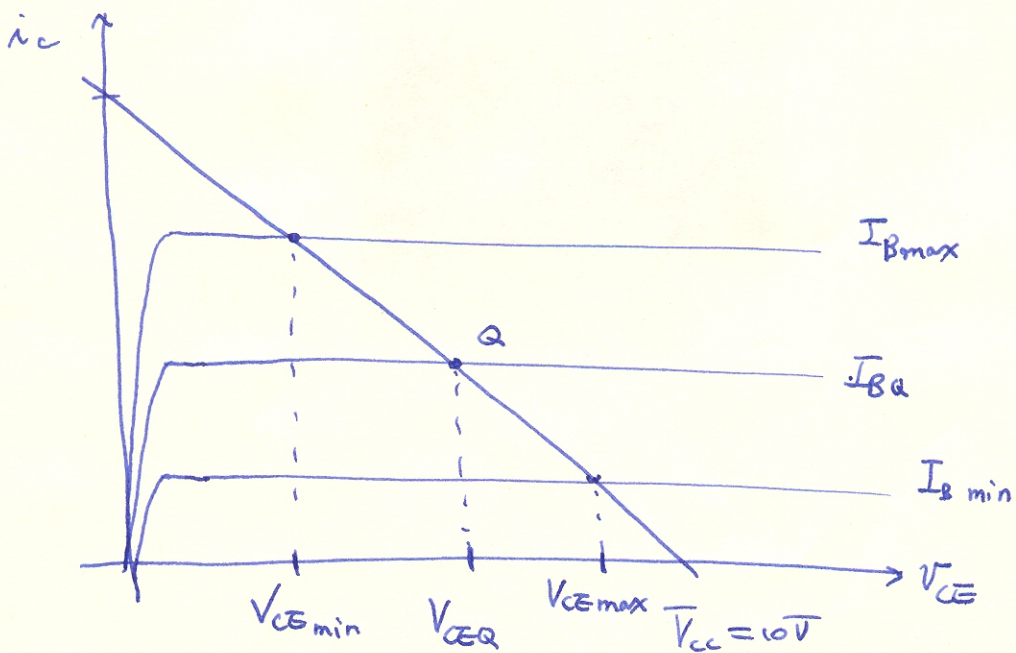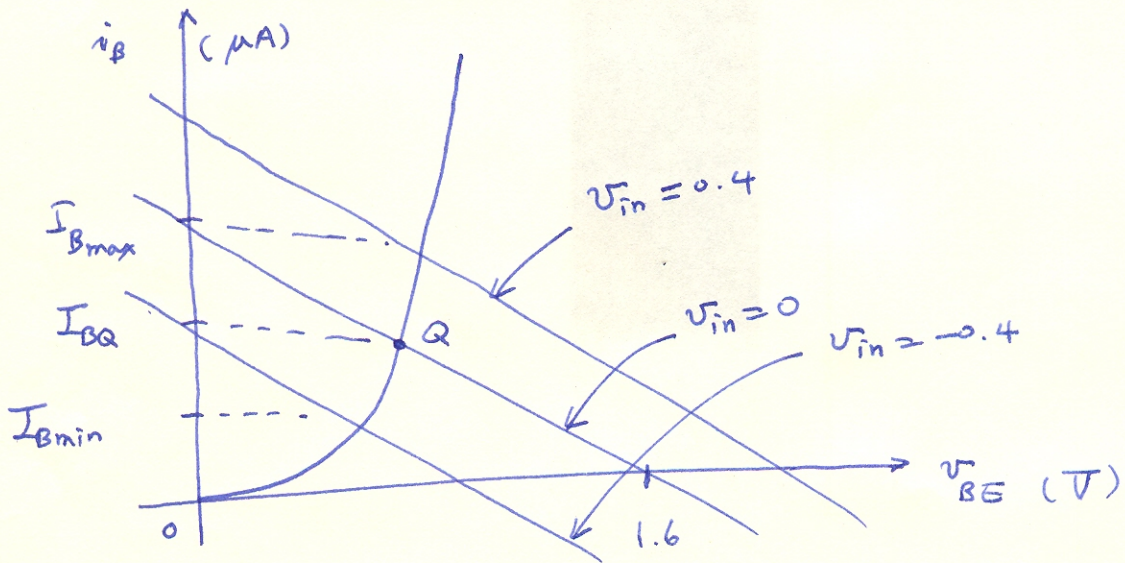
$$v_{in}(t) = 0.4 \cdot \sin(2000\pi t)$$



§ Large Signal DC model. (Bias Analysis)


- Active region model.
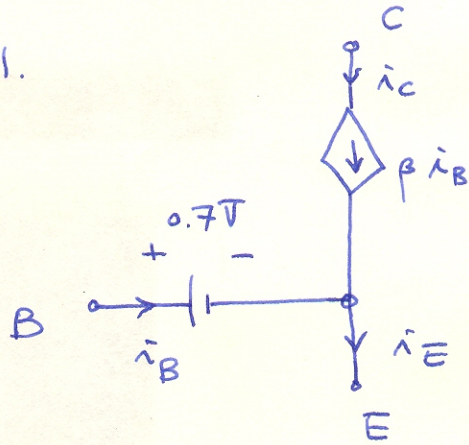
$$\begin{cases} \hat{i}_c = \beta \cdot \hat{i}_B \\ V_{BE} = 0.7 \text{ V} \\ V_{CE} \approx 0.2 \text{ V} \end{cases}$$




- Saturation region model.
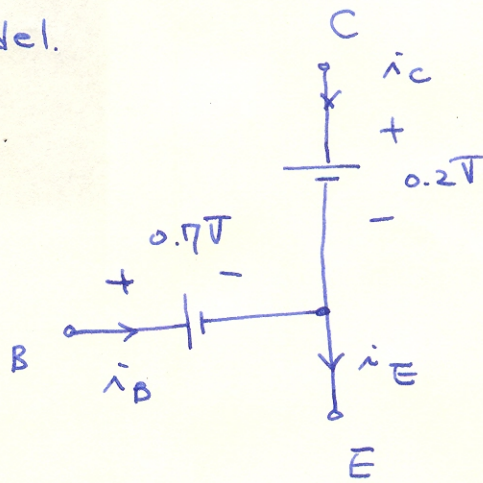
$$\begin{cases} V_{BE} = 0.7 \text{ V} \\ V_{CE} \approx 0.2 \text{ V} \\ 0 < \hat{i}_c < \beta \hat{i}_B \end{cases}$$



- Cutoff region model
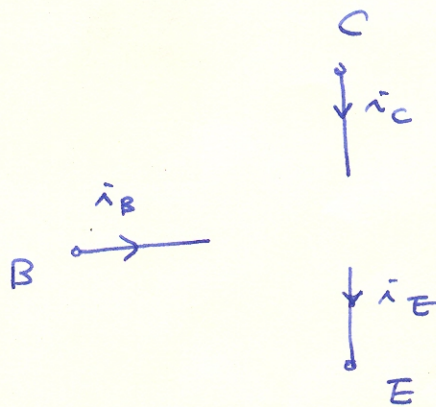
$$\begin{cases} V_{BE} < 0.5 \text{ V} \\ V_{BC} < 0.5 \text{ V} \\ \hat{i}_B \approx 0 \\ \hat{i}_c \approx 0 \end{cases}$$



Ex.) $\beta = 100$

a) $I_B = 50 \mu A$, $I_C = 3 mA$

$i_c = 3 mA < \beta \cdot i_B \rightarrow$ saturation region.


b) $i_B = 50 \mu A$, $V_{CE} = 5 V > 0.2 V \rightarrow$ active

c) $V_{BE} = -2 V$, $V_{CE} = -1 V \rightarrow$ cut off.

§ Large signal DC Analysis

- Bias Analysis (Q point operation mode

Ex)

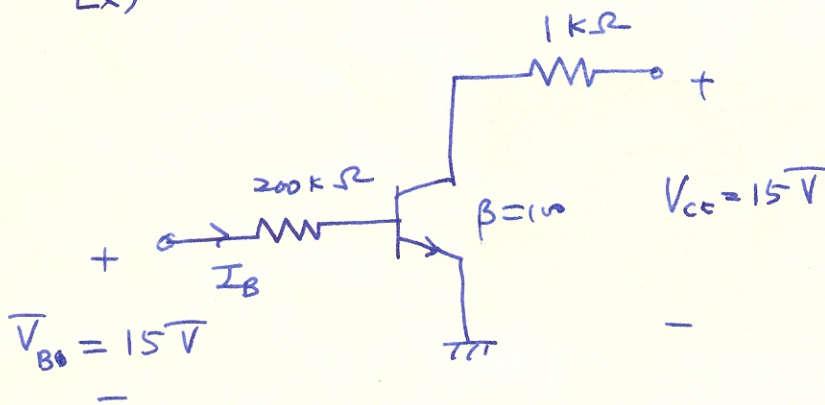

$$I_C = \beta I_B = 7.15 mA$$

$$V_{CE} = 15 - 1000 \times 0.00715 = 7.85 > 0.2 V$$

\rightarrow Active region.

Assume active region.

$$I_B = \frac{15 - 0.7}{200,000} = 71.5 \mu A$$

Ex) $\beta = 300$

Assume active region.

$$I_B = 71.5 \mu\text{A}$$

$$I_C = 21.45 \text{ mA}$$


$$V_{CE} = V_{CC} - R_C \cdot I_C = -6.45 < 0.2\text{V} \rightarrow \text{saturation!}$$

Assume saturation region.


$$V_{CE} = 0.2 \text{ V}$$

$$I_C = \frac{V_{CC} - 0.2}{R_C} = 14.8 \text{ mA} < \beta I_B \rightarrow \text{saturation region.}$$

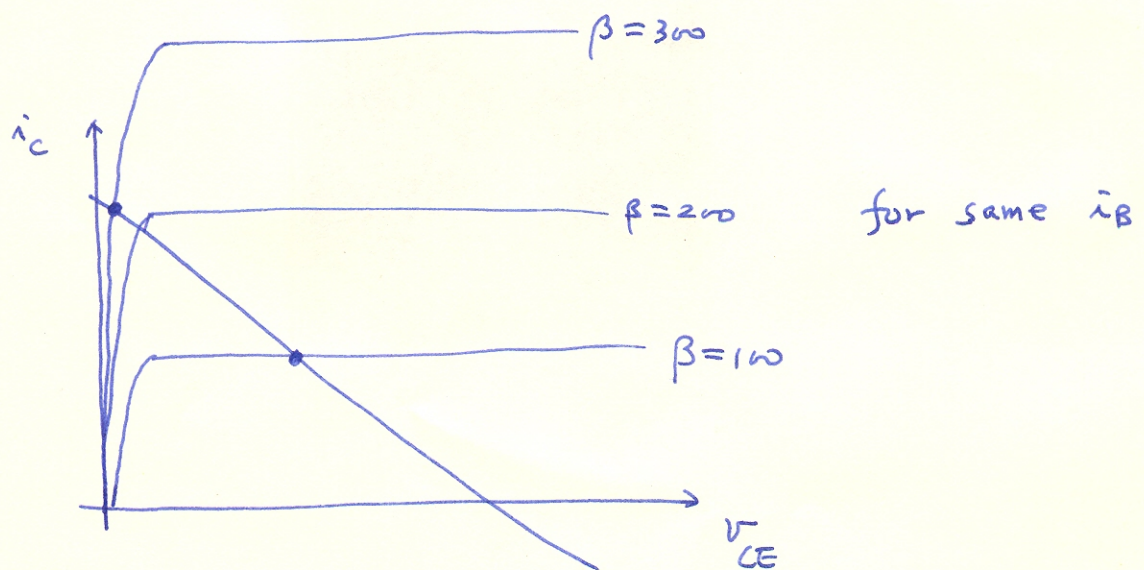\Rightarrow Operating point Q is sensitive to β .



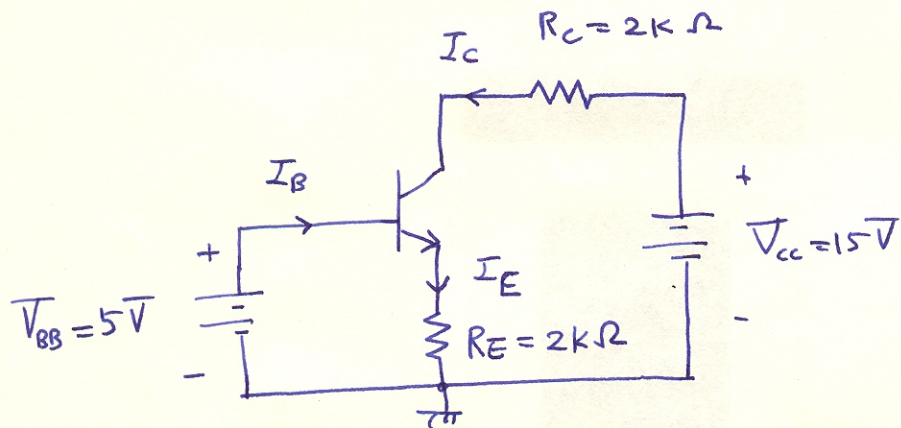Ex) $V_{CC} = 15V$, $V_{BB} = 5V$, $R_C = 2k\Omega$, $R_E = 2k\Omega$



a) $\beta = 100$:

Assume active,
$$I_E = \frac{V_{BB} - 0.7}{2000} = 2.15 \text{ mA}$$

$$I_E = (\beta + 1) \cdot I_B \rightarrow I_B = \frac{I_E}{(\beta + 1)} = 21.3 \mu\text{A}$$

$$I_C = I_E - I_B = 2.13 \text{ mA}$$

$$V_{CE} = V_{CC} - R_C \cdot I_C - R_E \cdot I_E = 6.44 \text{ V} > 0.2 \text{ V}$$

b) $\beta = 300$:


$$I_B = 7.14 \mu\text{A}$$

$$I_C = 2.14 \text{ mA}$$


$$V_{CE} = 6.42 \text{ V} > 0.2$$

$\rightarrow Q$ is not sensitive to β .

Four Resistor Bias Circuit

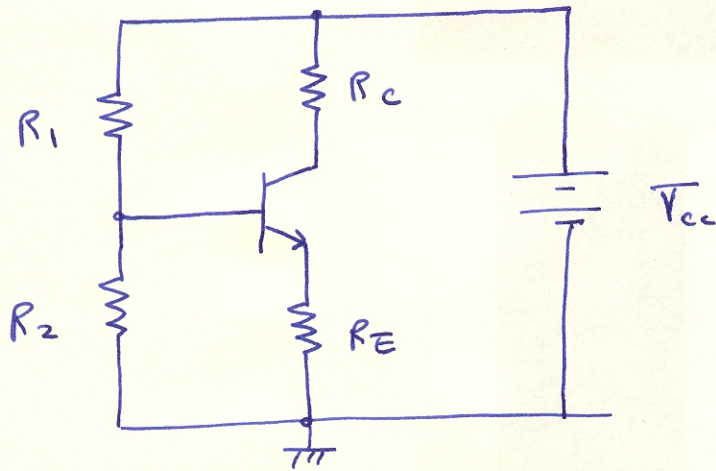

Note) R_1 and R_2 are voltage divider

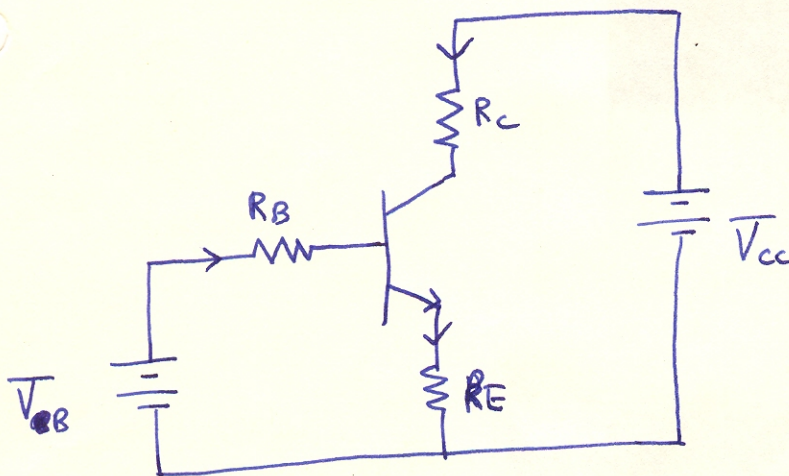

$$V_B = \frac{R_2}{R_1 + R_2} \cdot V_{CC}$$

$$R_B = R_1 \parallel R_2$$

$$V_B = R_B \cdot I_B + V_{BE} + R_E \cdot I_E$$

$$I_E = (1 + \beta) \cdot I_B$$


$$\rightarrow I_B = \frac{V_B - V_{BE}}{R_B + (1 + \beta) \cdot R_E}$$

$$V_{cc} = R_c \cdot I_c + V_{ce} + R_E \cdot I_E$$

$$I_c = \beta I_B = \frac{\beta (V_B - V_{BE})}{R_B + (\beta + 1) \cdot R_E} \approx \frac{(V_B - V_{BE})}{R_E}$$

→ Q point is not sensitive to β .

Ex)

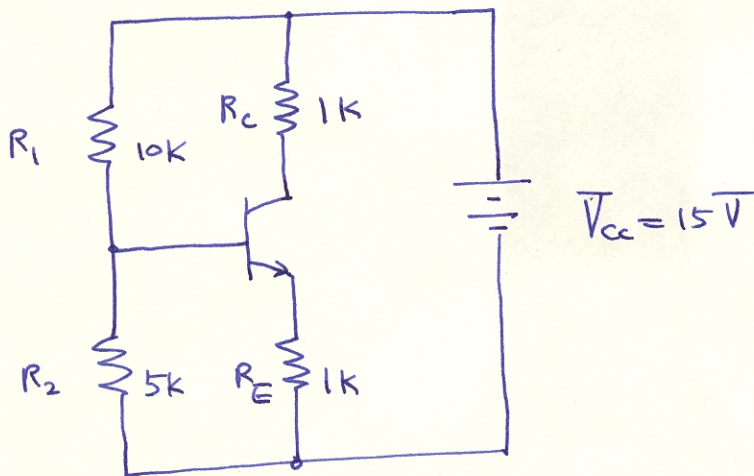

a) $\beta = 100$

$$R_B = 10\text{k} \parallel 5\text{k} = 3.33\text{ k}\Omega$$

$$V_B = \frac{5}{10+5} \times 15 = 5\text{V}$$

$$I_B = \frac{V_B - V_{BE}}{R_B + (\beta + 1) \cdot R_E} = 41.2\ \mu\text{A}$$

$$I_c = \beta \cdot I_B = 4.12\ \text{mA}$$

$$V_{ce} = 6.72\ \text{V}$$

$$b) \quad \beta = 300$$

$$I_B = 14.1 \mu A$$

$$I_C = \beta \cdot I_B = 4.24 \text{ mA}$$



$$V_{CE} = 6.51 \text{ V}$$

§ Small Signal Equivalent Circuit

Consider DC biased signal i_B current

$$i_B = I_{BQ} + i_b$$

\uparrow \uparrow
 DC bias AC signal

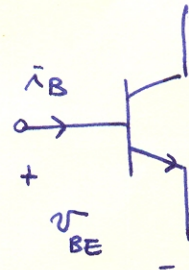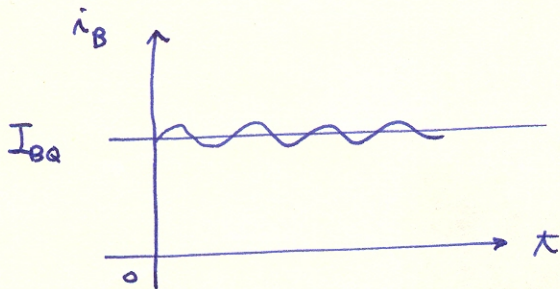

$$i_B = (1 - \alpha) \cdot I_{ES} \cdot \left[\exp\left(\frac{v_{BE}}{V_T}\right) - 1 \right]$$

$$I_{BQ} + i_b = (1 - \alpha) \cdot I_{ES} \cdot \exp\left(\frac{V_{BEQ} + v_{be}}{V_T}\right)$$

$$= I_{BQ} \cdot \exp\left(\frac{v_{be}}{V_T}\right) \approx I_{BQ} \cdot \left(1 + \frac{v_{be}}{V_T}\right)$$

$$\rightarrow \bar{i}_b = \left(\frac{I_{BQ}}{V_T} \right) \cdot v_{be} = \frac{v_{be}}{r_{\pi}}$$

$$r_{\pi} = \frac{V_T}{I_{BQ}} = \frac{\beta V_T}{I_{CQ}}$$


where $V_T \approx 0.026 \text{ V}$

$$\bar{i}_c = \beta \bar{i}_b$$

$$I_{CQ} + \bar{i}_c = \beta I_{BQ} + \beta \bar{i}_b$$

$$\rightarrow \bar{i}_c = \beta \bar{i}_b$$

o Small Signal Equivalent Circuit.

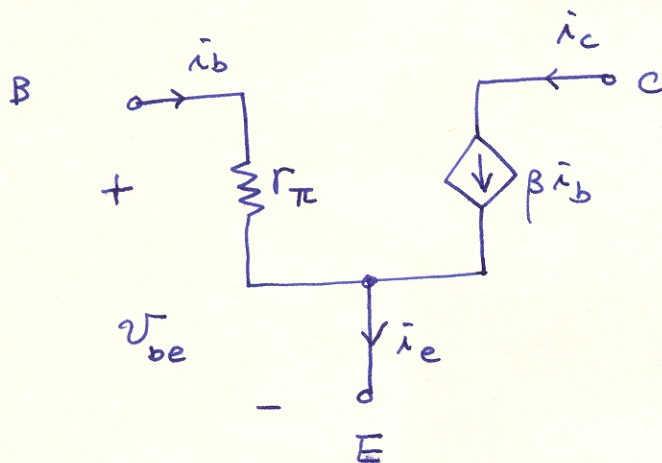


Note) Two stage Analysis for BJT

1. DC bias analysis \rightarrow Q point

2. Small signal analysis \rightarrow Ac signal analysis

Common Emitter Amplifier.

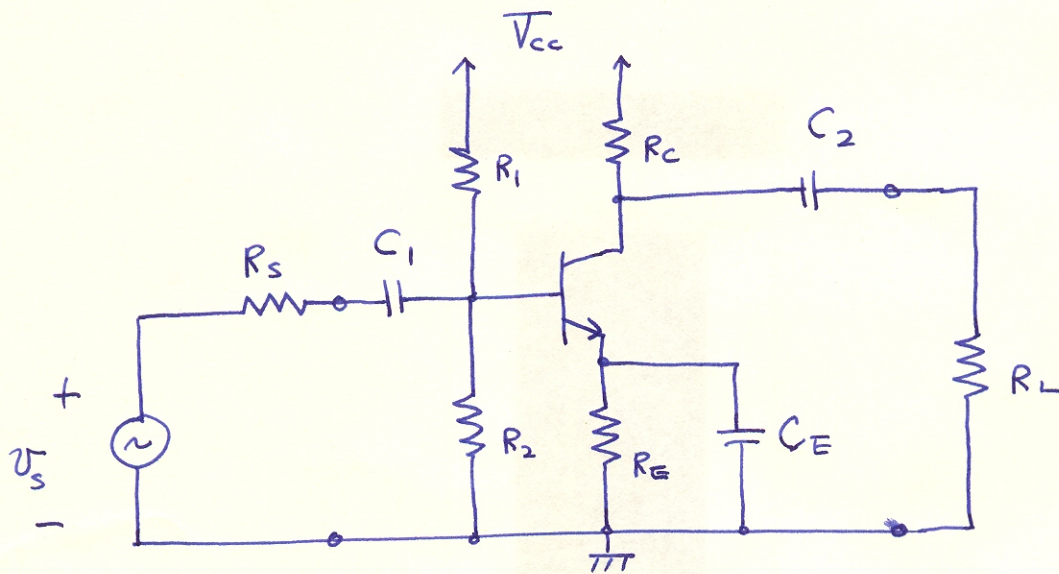


• DC Analysis :

$\left(\begin{array}{l} C_1, C_2, C_E \text{ are open for DC.} \\ \text{Find } I_{BQ} \text{ and } I_{CQ} \rightarrow r_{\pi}. \end{array} \right.$

• AC Analysis :

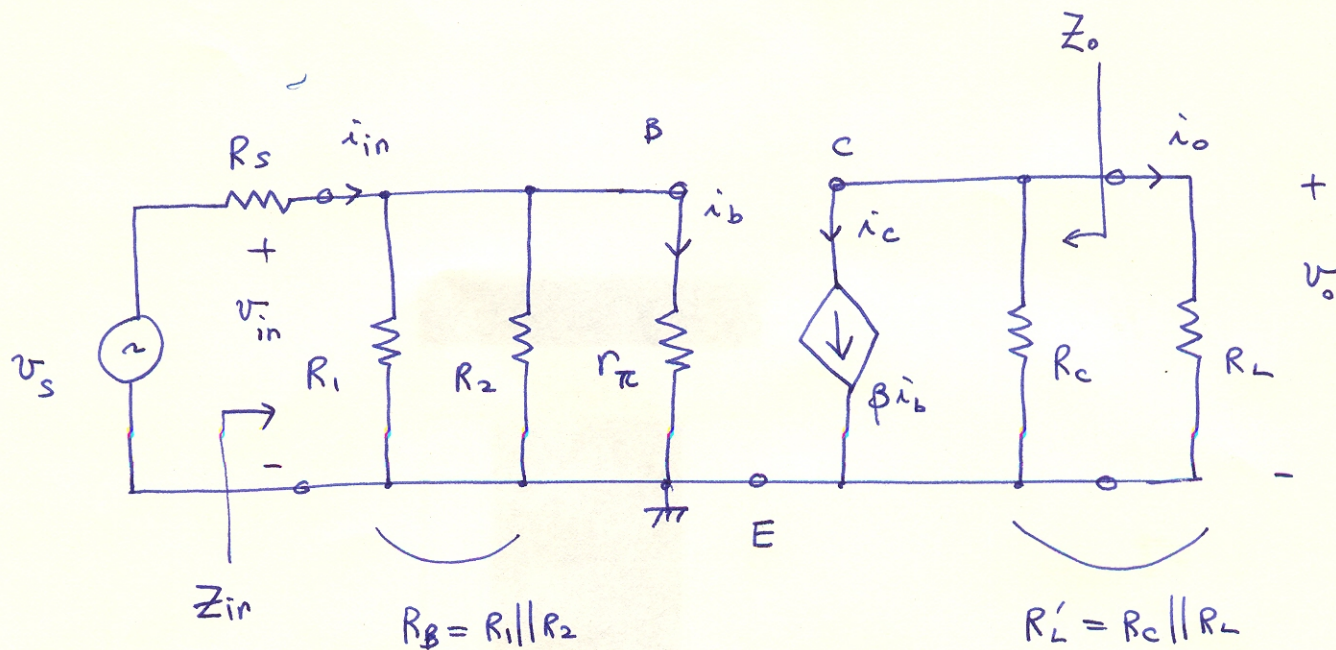$\left(\begin{array}{l} C_1, C_2, C_E \text{ are short for AC.} \\ V_{CC} \rightarrow 0V \text{ for AC.} \\ \text{Small signal BJT Equivalent circuit.} \end{array} \right.$



- Voltage gain.

$$A_v = \frac{v_o}{v_{in}}$$

$$v_{in} = v_{be} = r_{\pi} \cdot i_b$$

$$v_o = -i_c \cdot R'_L = -\beta \cdot R'_L \cdot i_b$$

$$A_v = \frac{-R'_L \cdot \beta}{r_{\pi}}$$

- Open circuit voltage gain: $R_L \rightarrow \infty$, $R'_L \rightarrow R_c$

$$A_{v_o} = \frac{v_o}{v_{in}} \Big|_{R_L \rightarrow \infty} = -\frac{R_c \cdot \beta}{r_{\pi}}$$

- Input impedance

$$Z_{in} = \frac{v_{in}}{i_{in}} = R_B \parallel r_{\pi}$$

- Current gain.

$$A_i = \frac{i_o}{i_{in}} = \left(\frac{v_o}{R_L} \right) / \left(v_{in} / Z_{in} \right) = A_v \cdot \frac{Z_{in}}{R_L}$$

$$Z_{in} = R_1 \parallel R_2 \parallel r_{\pi} = R_B \parallel r_{\pi}$$

- Power gain

$$G = A_v \cdot A_i$$

- Output impedance

$$Z_o = \frac{v_o}{-i_o} \Big|_{v_{in}=0} = R_c$$

$$\text{Ex }) \quad v_s(t) = 0.001 \cdot \sin(\omega t)$$

$$R_s = 500 \Omega, \quad R_1 = 10 \text{ k}\Omega, \quad R_2 = 5 \text{ k}\Omega,$$

$$R_C = 1 \text{ k}\Omega, \quad R_E = 1 \text{ k}\Omega, \quad R_{L'} = 2 \text{ k}\Omega$$

$$V_{BE} = 0.7 \text{ V}, \quad \beta = 100$$

By DC Analysis,

$$I_{CQ} = 4.12 \text{ mA}, \quad V_{CE} = 6.72 \text{ V}$$

$$r_{\pi} = \frac{\beta V_T}{I_{CQ}} = 631 \Omega$$

For AC Analysis,

$$R_B = R_1 \parallel R_2 = 3.33 \text{ k}\Omega$$

$$R_{L'} = R_L \parallel R_C = 667 \Omega$$

$$A_v = \frac{v_o}{v_{in}} = - \frac{R_{L'} \beta}{r_{\pi}} = -106$$

$$A_{v_o} = \frac{v_o}{v_{in}} = - \frac{R_C \beta}{r_{\pi}} = -158$$

$$Z_{in} = \frac{v_{in}}{i_{in}} = R_B \parallel r_{\pi} = 531 \Omega$$

$$A_i = \frac{i_o}{i_{in}} = A_v \cdot \frac{Z_{in}}{R_L} = -28.1$$

$$G = A_v \cdot A_i = 2980$$


$$Z_o = R_C = 1 \text{ k}\Omega$$

$$V_{in} = V_s \cdot \frac{Z_{in}}{Z_{in} + R_s} = 0.515 \cdot V_s$$


$$V_o = A_v \cdot V_{in} = -106 \times 0.515 \cdot V_s$$

$$= -54.6 \cdot \sin(\omega t) \text{ (mV)}$$

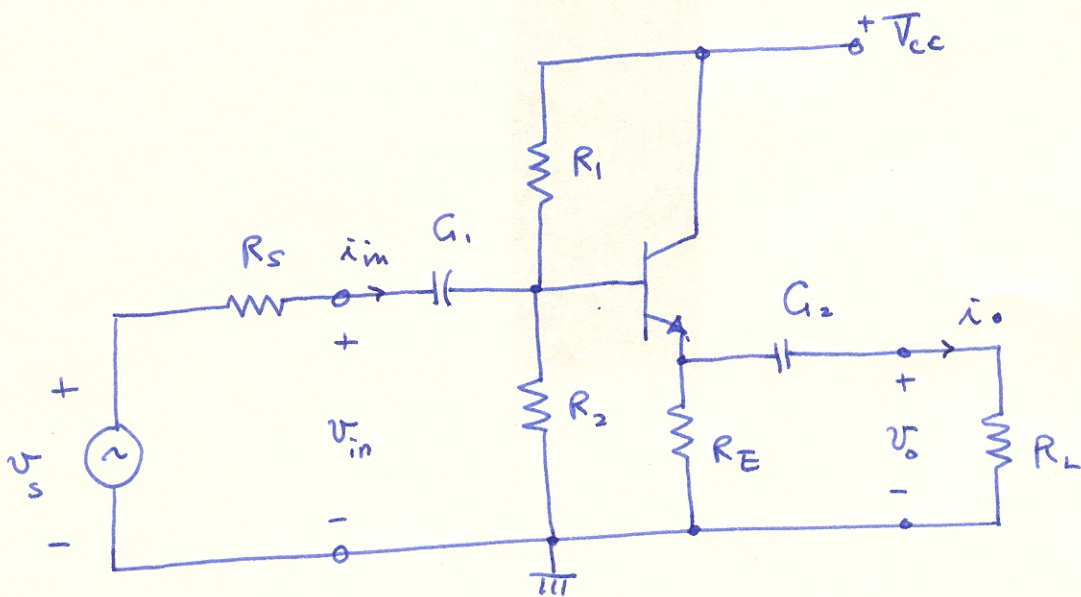
§ Emitter Follower (Common Collector Amplifier)



• AC Small Signal Equivalent Circuit

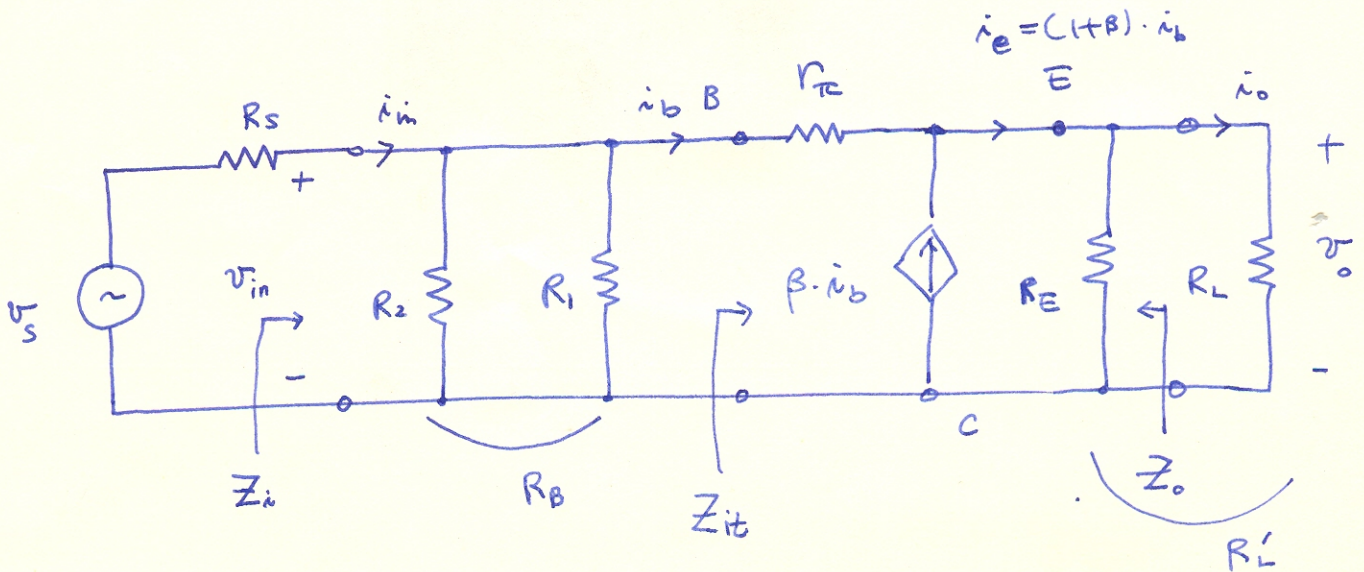

• DC Bias Analysis

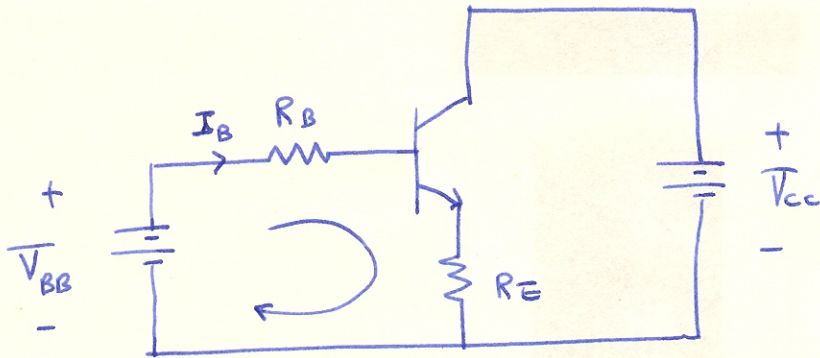

$$\overline{V_{BB}} = R_B \cdot I_B + v_{BE} + R_E (1 + \beta) \cdot I_B$$

• AC Analysis

$$R_B = R_1 \parallel R_2$$

$$R_L' = R_E \parallel R_L$$

$$v_o = R_L' \cdot (1 + \beta) \cdot i_b$$

$$v_{in} = r_{\pi} \cdot i_b + v_o = [r_{\pi} + (1 + \beta) \cdot R_L'] \cdot i_b$$

$$A_v = \frac{(1 + \beta) \cdot R_L'}{r_{\pi} + (1 + \beta) \cdot R_L'} \approx 1$$

$$\rightarrow v_o \approx v_{in} \quad : \text{ Buffer}$$

Input Impedance

$$Z_i = R_B \parallel Z_{it}$$

$$Z_{it} = \frac{v_{in}}{i_b} = r_{\pi} + (1+\beta) \cdot R_L' \longrightarrow \text{High}$$

Current Gain


$$A_i = \frac{i_o}{i_{in}} = \frac{v_o / R_L}{v_{in} / Z_{in}} = \left(\frac{v_o}{v_{in}} \right) \cdot \left(\frac{Z_{in}}{R_L} \right) = A_v \left(\frac{Z_{in}}{R_L} \right)$$

Power Gain

$$G = A_v \cdot A_i$$

Output Impedance

$$Z_o = \frac{v_o}{-i_o} \Big|_{v_s=0}$$

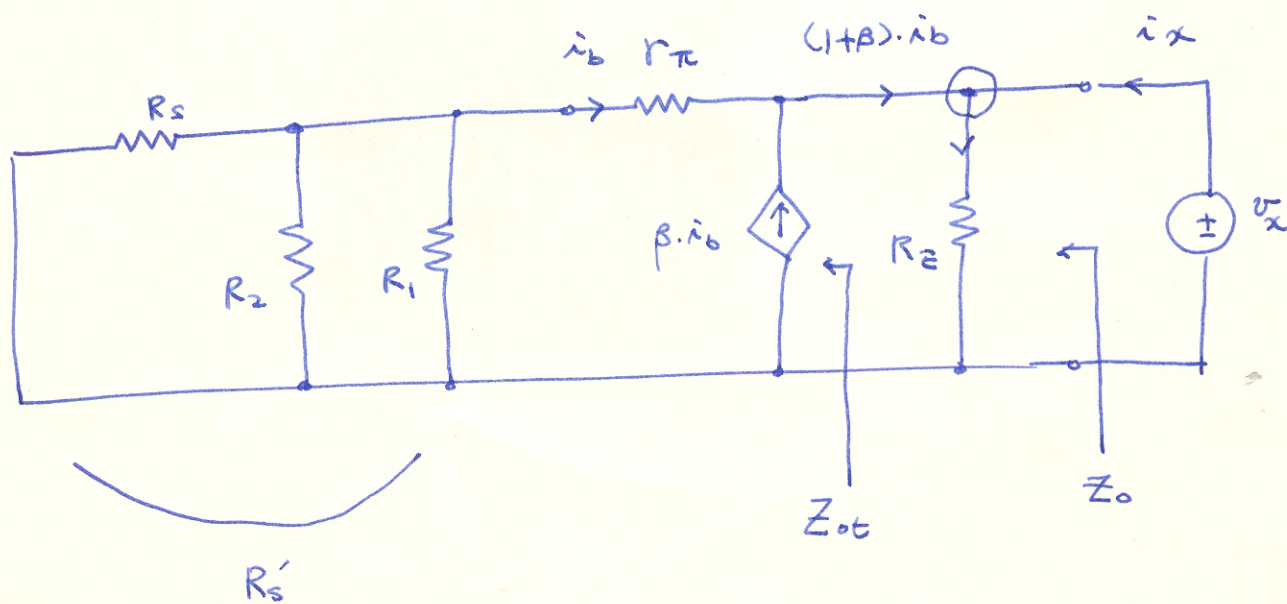

$$Z_o = \frac{v_x}{i_x}$$

$$\left(\begin{array}{l} (1+\beta) \cdot i_b + i_x = \frac{v_x}{R_E} \\ R_s' \cdot i_b + r_\pi \cdot i_b + v_x = 0 \end{array} \right.$$

$$Z_o = \frac{v_x}{i_x} = \frac{1}{\left[\frac{(1+\beta)}{(R_s' + r_\pi)} \right] + \left[\frac{1}{R_E} \right]} = Z_{ot} \parallel R_E \rightarrow \text{small.}$$

Ex) $R_s = 10 \text{ k}\Omega$, $R_1 = 100 \text{ k}\Omega$, $R_2 = 100 \text{ k}\Omega$
 $R_E = 2 \text{ k}\Omega$, $R_L = 1 \text{ k}\Omega$, $\beta = 200$, $V_{BEQ} = 0.7 \text{ V}$

• DC Bias Analysis

$$V_B = R_B \cdot I_{BQ} + V_{BEQ} + R_E \cdot (1+\beta) \cdot I_{BQ}$$

$$I_{BQ} = 20.6 \mu\text{A}, \quad I_{CQ} = \beta I_{BQ} = 4.12 \text{ mA},$$

$$V_{CEQ} = V_{CC} - I_{EQ} \cdot R_E = 11.7 \text{ V}$$

$$r_\pi = \frac{\beta V_T}{I_{CQ}} = 1260 \Omega$$

• AC Small Signal Analysis

$$R_B = R_1 \parallel R_2 = 50 \text{ k}\Omega$$

$$R_L' = R_L \parallel R_E = 667 \Omega$$

$$A_v = \frac{(1+\beta) \cdot R_L'}{r_\pi + (1+\beta) R_L'} = 0.991 \rightarrow \text{near } 1$$

$$Z_{it} = r_\pi + (1+\beta) \cdot R_L' = 135 \text{ k}\Omega$$

$$Z_i = \frac{1}{\frac{1}{R_B} + \frac{1}{Z_{it}}} = R_B \parallel Z_{it} = 36.5 \text{ k}\Omega$$

$$R_s' = R_s \parallel R_1 \parallel R_2 = 8.33 \text{ k}\Omega$$

$$Z_o = \frac{1}{(1+\beta)/(R_s' + r_\pi) + 1/R_E} = 46.6 \Omega$$

$$A_i = A_v \cdot \frac{Z_s}{R_L} = 36.2$$

$$G = A_v \cdot A_i = 35.8$$