


Chapter 13 Output Stages and Power Amplifiers

- **13.1 General Considerations**
- **13.2 Emitter Follower as Power Amplifier**
- **13.3 Push-Pull Stage**
- **13.4 Improved Push-Pull Stage**
- **13.5 Large-Signal Considerations**
- **13.6 Short Circuit Protection**
- **13.7 Heat Dissipation**
- **13.8 Efficiency**
- **13.9 Power Amplifier Classes**

Why Power Amplifiers?

- **Drive a load with high power.**
- **Cellular phones need 1W of power at the antenna.**
- **Audio systems deliver tens to hundreds of watts of power.**
- **Ordinary Voltage/Current amplifiers are not suitable for such applications**

Chapter Outline

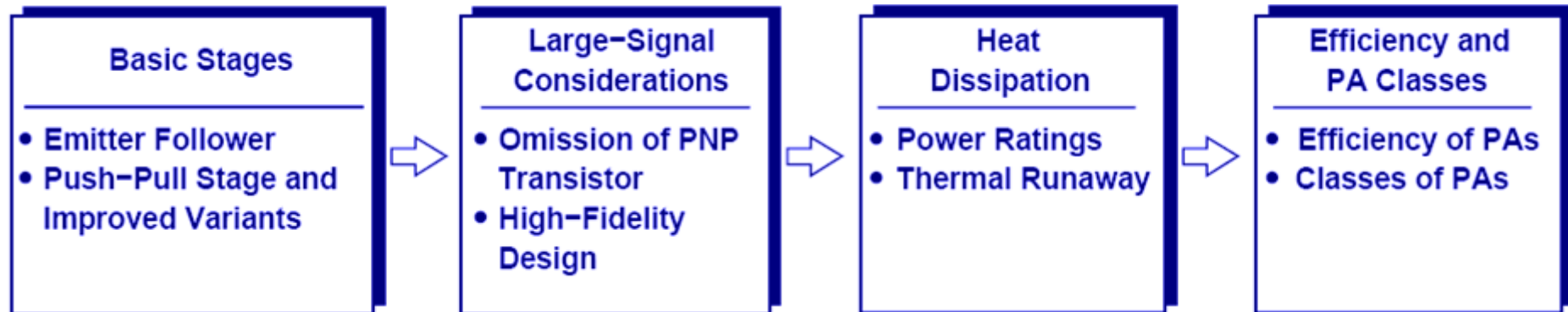


Power Amplifier Characteristics

- **Experiences low load resistance.**
- **Delivers large current levels.**
- **Requires large voltage swings.**
- **Draws a large amount of power from supply.**
- **Dissipates a large amount of power, therefore gets “hot”.**


Power Amplifier Performance Metrics

- **Distortion - Linearity**
- **Power Efficiency**
- **Voltage Rating – Transistor Breakdown voltage**

Emitter Follower Large-Signal Behavior I

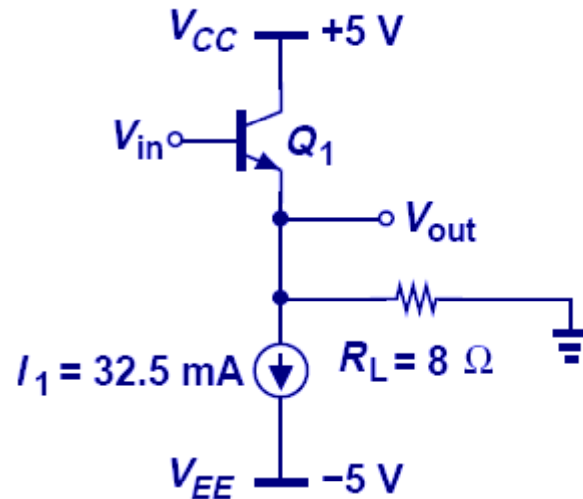

(a)

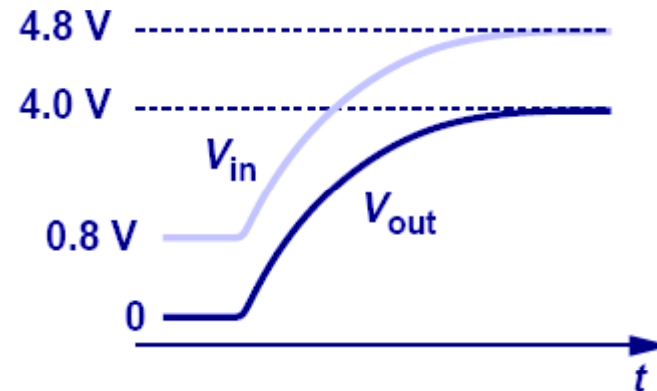

(b)

$$A_v = R_L / (R_L + 1/g_m)$$


For $R_L = 8 \Omega$,

$1/g_m = 0.8 \Omega$, thus, $I_C = 32.5 \text{ mA}$


➤ As V_{in} increases V_{out} also follows and Q_1 provides more current.

➤ For $V_{in} = 4.8 \text{ V}$, $V_{out} = 4.0 \text{ V}$, $I_L = 500 \text{ mA}$, $I_{E1} = 532.5 \text{ mA}$

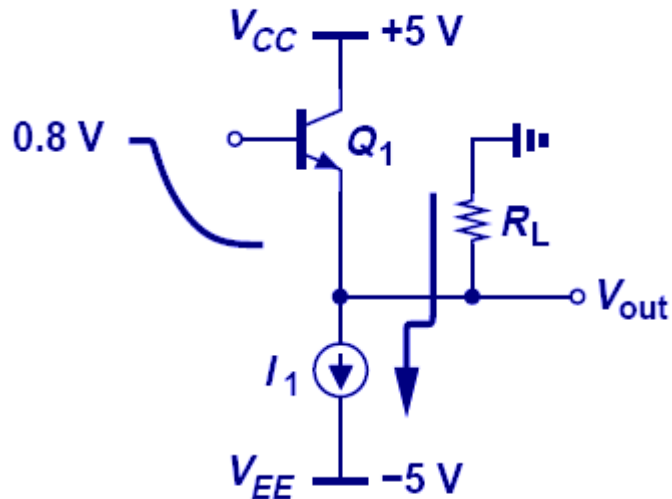Emitter Follower Large-Signal Behavior II



(c)

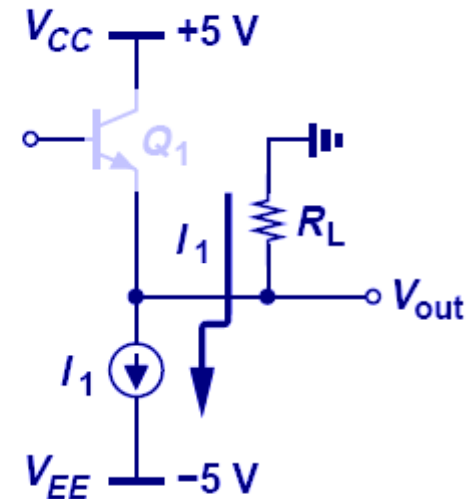


(d)

- However, as V_{in} decreases, V_{out} also decreases, shutting off Q_1 and resulting in a constant V_{out} .
- For $V_{in}=0.8\text{V}$, $V_{out}=0\text{V}$, $I_L=0\text{mA}$, $I_{E1}=32.5\text{mA}$
- For $V_{in}=0.7\text{V}$, $V_{out}=-0.1\text{V}$, $I_L=12.5\text{mA}$, $I_{E1}=20\text{mA}$
- When all current (32.5mA) flows to the load, $V_{out}=-0.26\text{V}$

Example 13.1: Emitter Follower

➤ $V_{in} = 0.5V$, $V_{out} = ?$

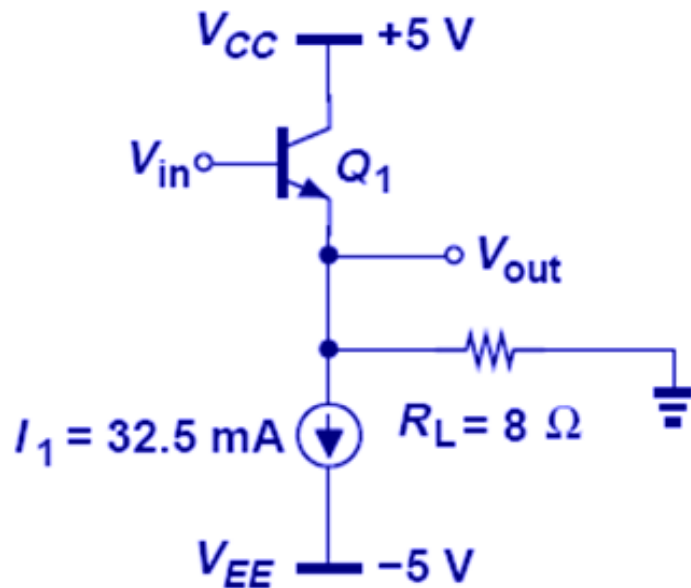

$$V_{in} - V_{BE1} = V_{out}, \quad \frac{V_{out}}{R_L} + I_1 = I_{C1}$$

$$V_{BE1} = V_T \ln(I_{C1} / I_S)$$


$$V_{in} - V_T \ln \left[\left(\frac{V_{out}}{R_L} + I_1 \right) \frac{1}{I_S} \right] = V_{out}$$

For $V_{in} = 0.5V$

$\Rightarrow V_{out} \approx -211 \text{ mV}$ by a few iterations

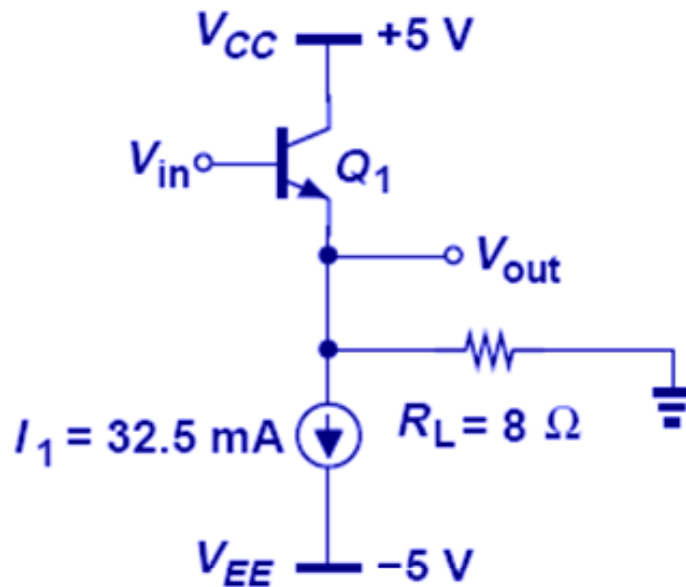Example 13.1: Emitter Follower



➤ For what V_{in} , Q_1 carries only 1% of I_1 ?



$$V_{in} = V_T \ln \frac{I_{C1}}{I_S} + (I_{C1} - I_1) R_L$$


$$\begin{aligned} \text{For } I_{C1} &\approx 0.01 \cdot I_1 \\ \Rightarrow V_{in} &\approx 390 \text{ mV} \end{aligned}$$

Linearity of an Emitter Follower

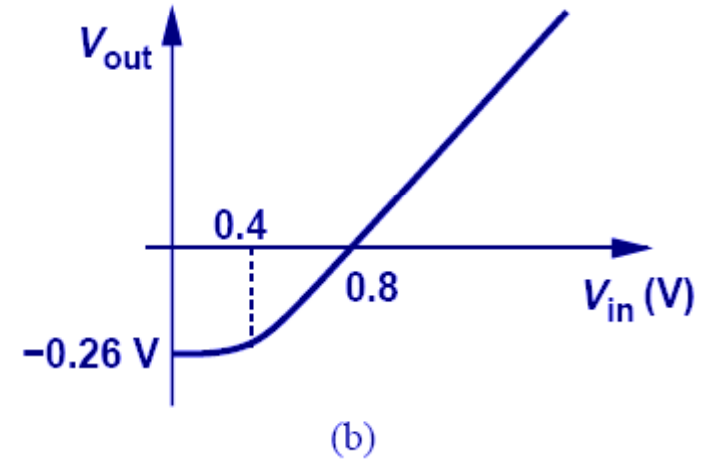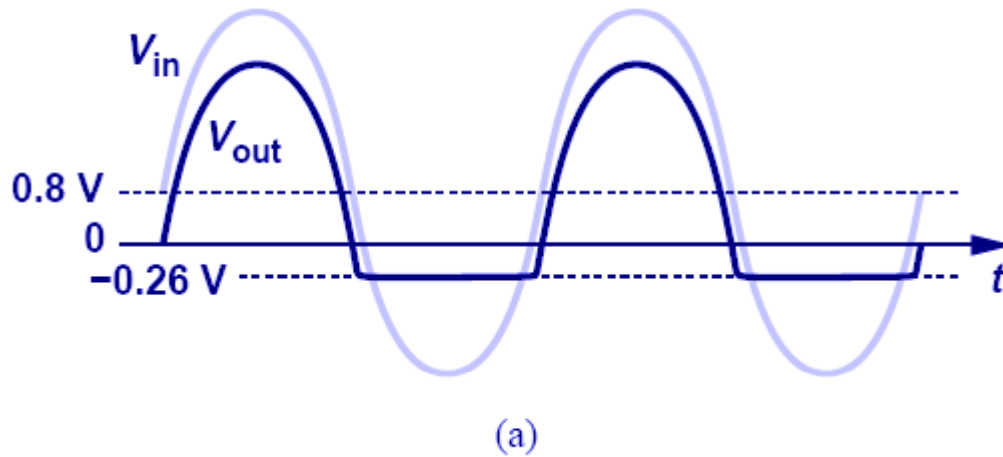


➤ As V_{in} decreases the output waveform will be clipped, introducing nonlinearity in I/O characteristics.

Push-Pull Stage

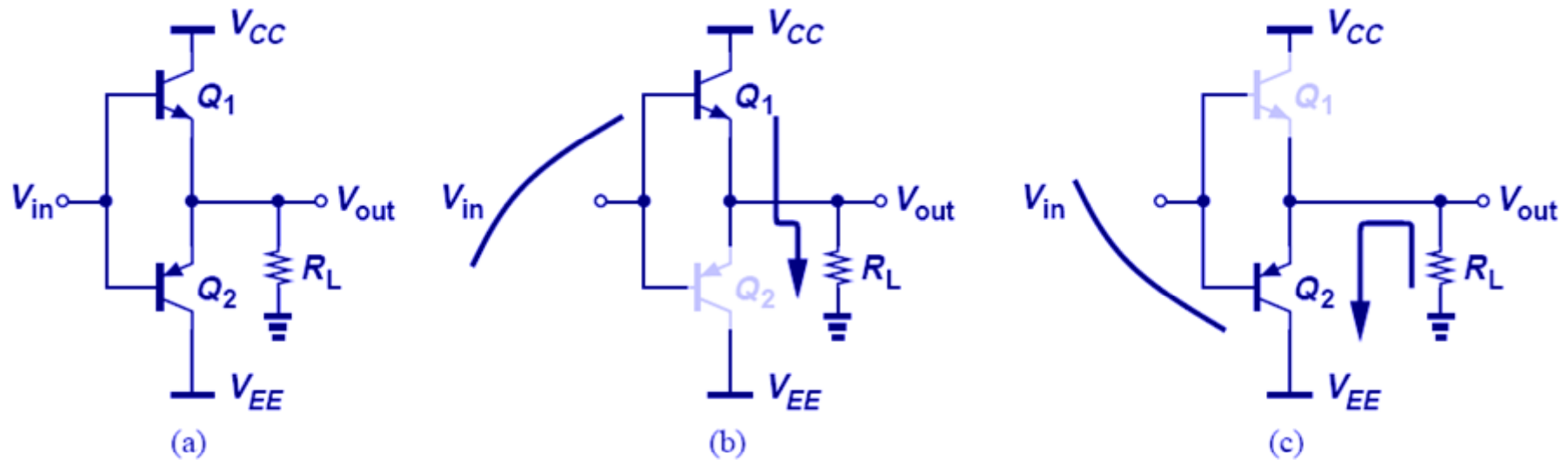

- As V_{in} increases, Q_1 is on and pushes current into R_L .
- As V_{in} decreases, Q_2 is on and pulls current out of R_L .

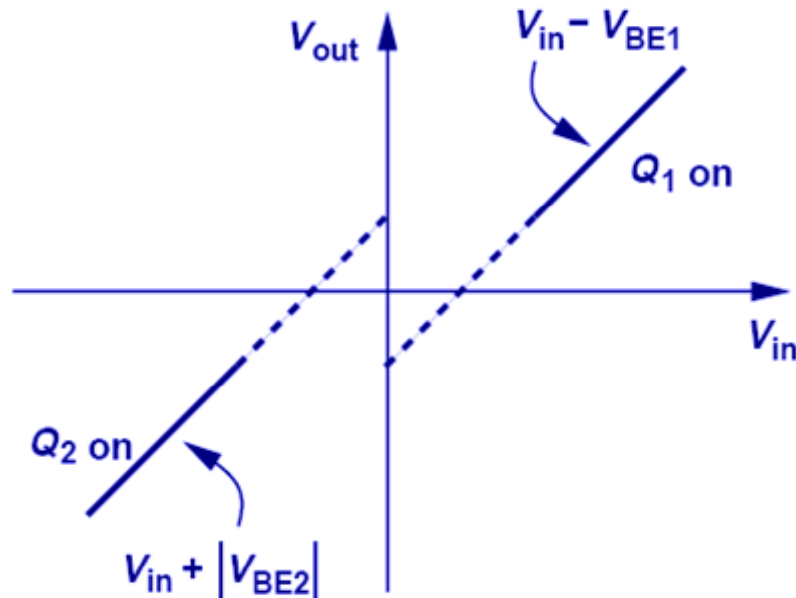Example 13.2: I/O Characteristics for Large V_{in}




$$V_{out} = V_{in} - V_{BE1} \quad \text{for large } +V_{in}$$

$$V_{out} = V_{in} + |V_{BE2}| \quad \text{for large } -V_{in}$$


- For positive V_{in} , Q_1 shifts the output down and for negative V_{in} , Q_2 shifts the output up.

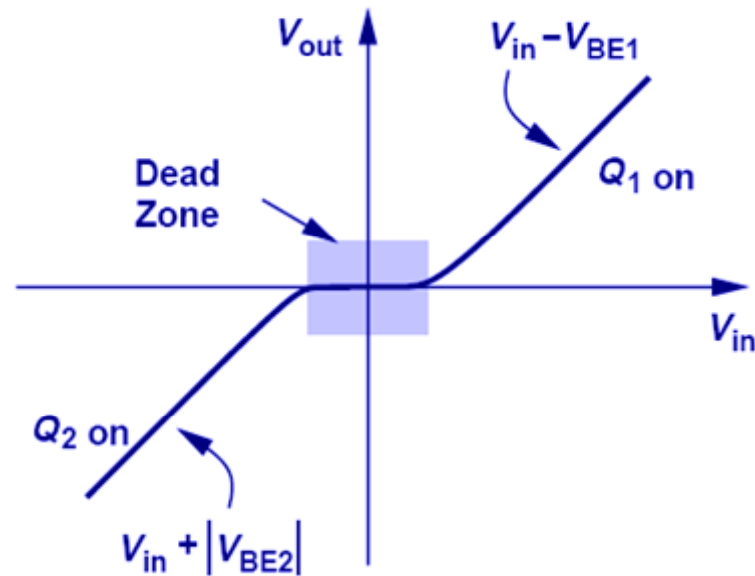Overall I/O Characteristics of Push-Pull Stage




- However, for small V_{in} , there is a “dead zone” (both Q_1 and Q_2 are off) in the I/O characteristic, resulting in gross nonlinearity.

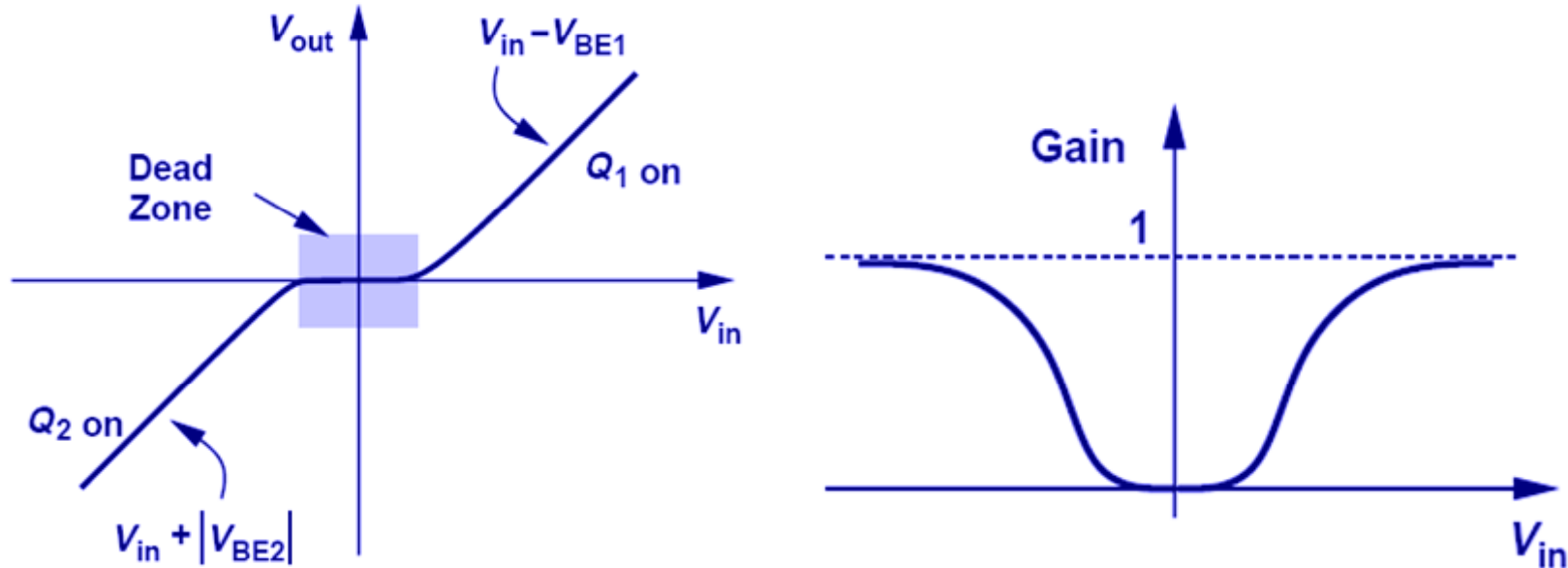Example 13.3: Small-Signal Gain of Push-Pull Stage




- The push-pull stage exhibits a gain that tends to unity when either Q_1 or Q_2 is on.
- When V_{in} is very small, the gain drops to zero.

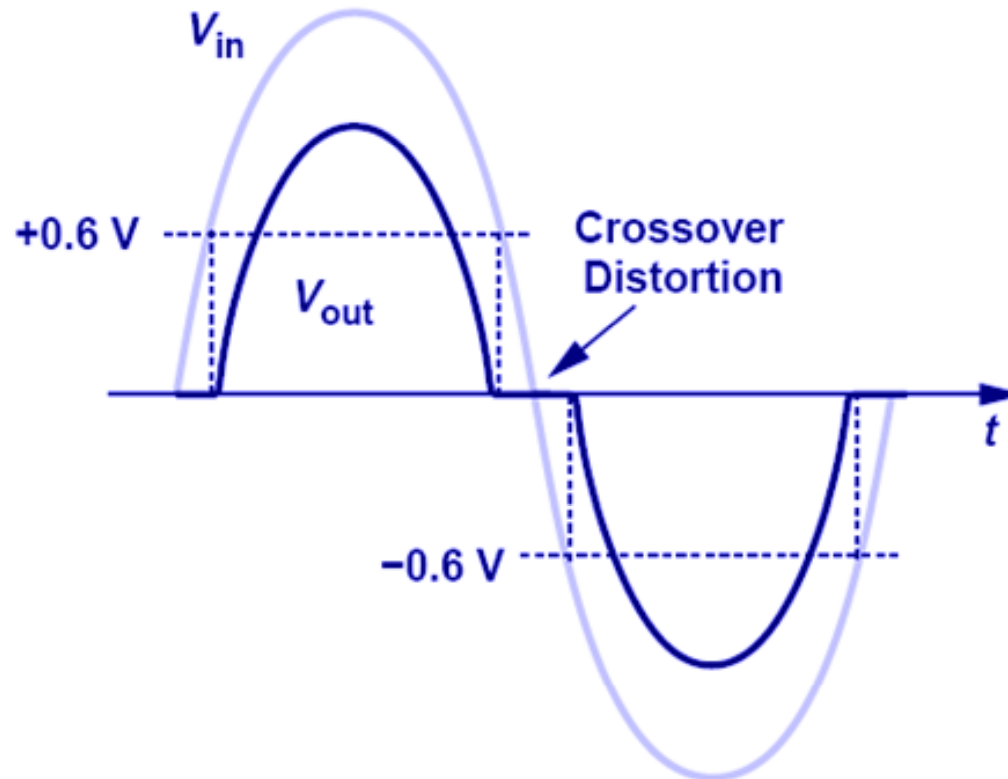Example 13.4: Sinusoidal Response of Push-Pull Stage




- For large V_{in} , the output follows the input with a fixed DC offset, however as V_{in} becomes small the output drops to zero and causes "Crossover Distortion."


Improved Push-Pull Stage

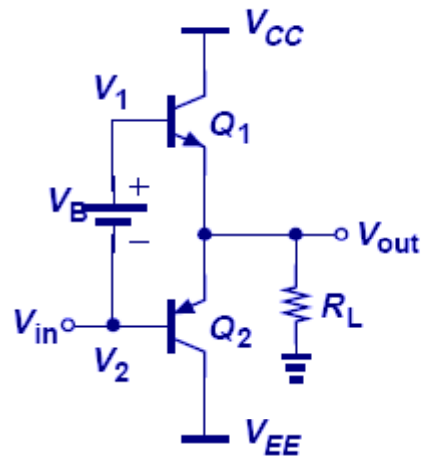

(a)

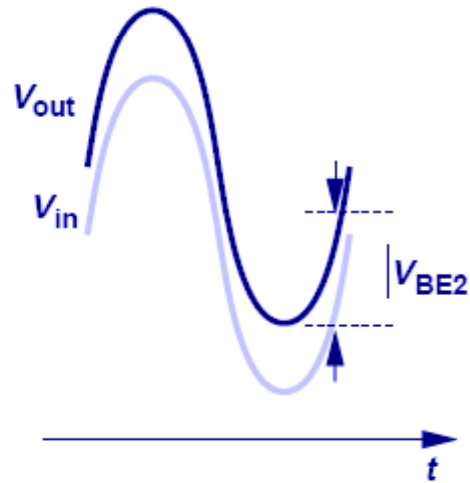

(b)

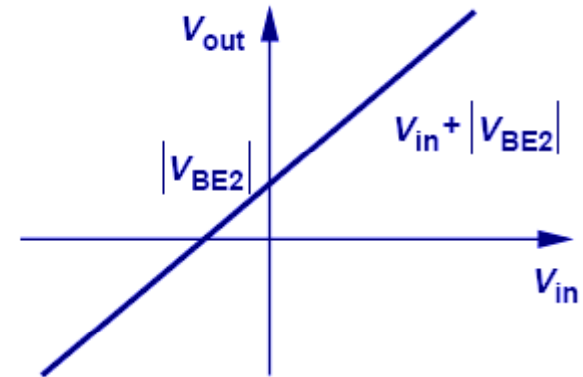


(c)


$$V_B = V_{BE1} + |V_{BE2}|$$

- With a battery of V_B inserted between the bases of Q_1 and Q_2 , the dead zone is eliminated.

Implementation of V_B

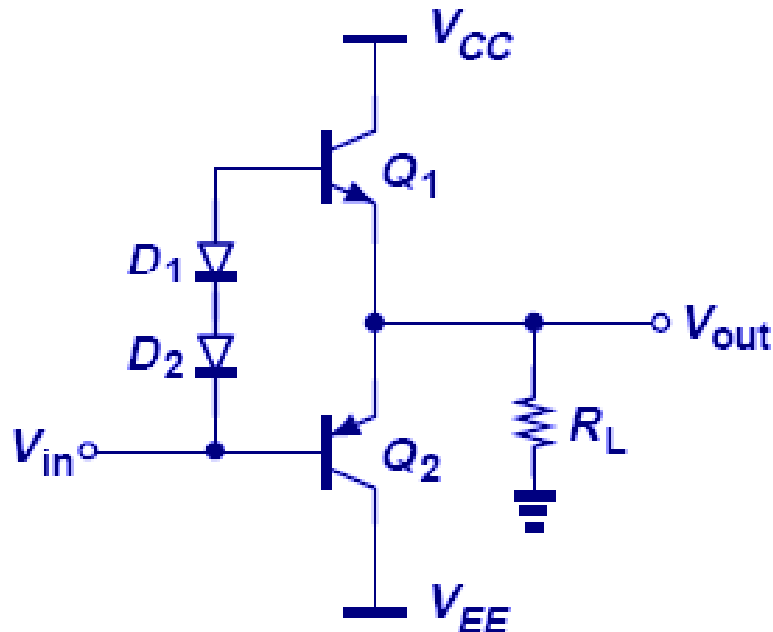


(a)

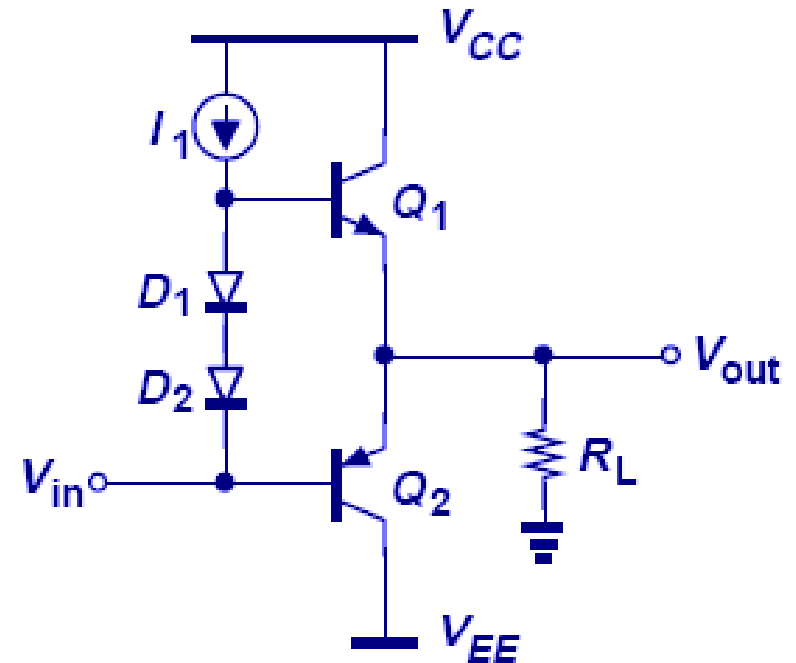

(b)

- Since $V_B = V_{BE1} + |V_{BE2}|$, a natural choice would be two diodes in series.
- I_1 in figure (b) is used to bias the diodes and Q_1 .

Example 13.6: Current Flow I

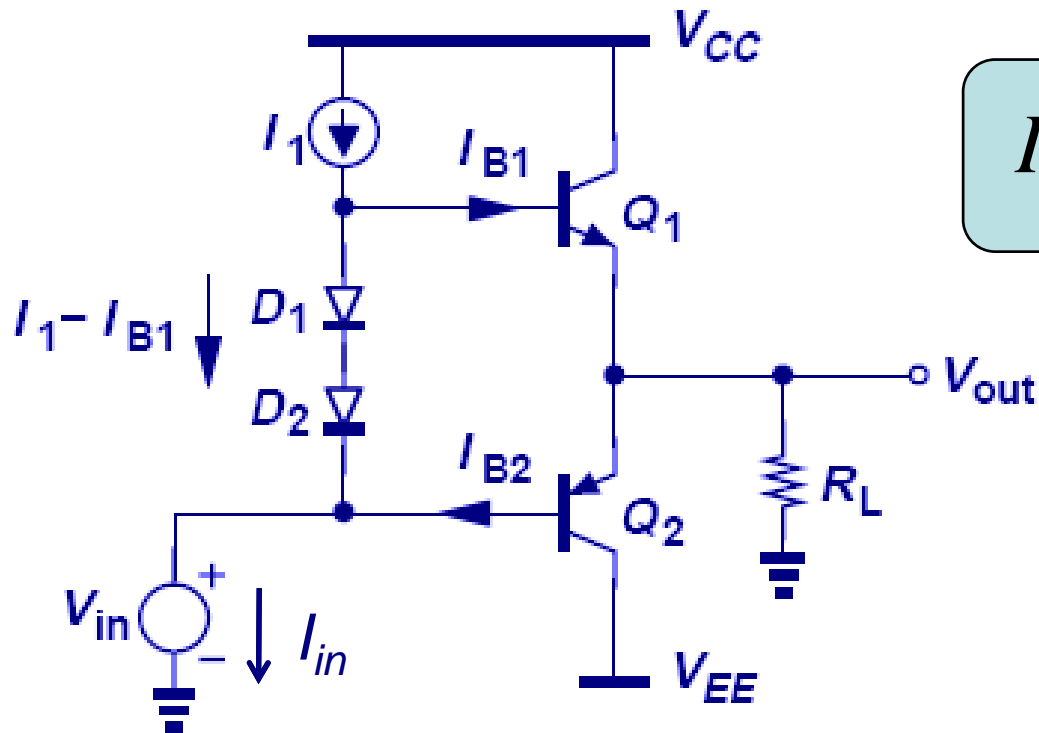


$$I_{in} = I_1 - I_{B1} + |I_{B2}|$$

Usually $I_{B1} \neq |I_{B2}|$ unless $V_{out} = 0$

I_{in} flows even when $V_{out} = 0$.


Example 13.8: Current Flow II

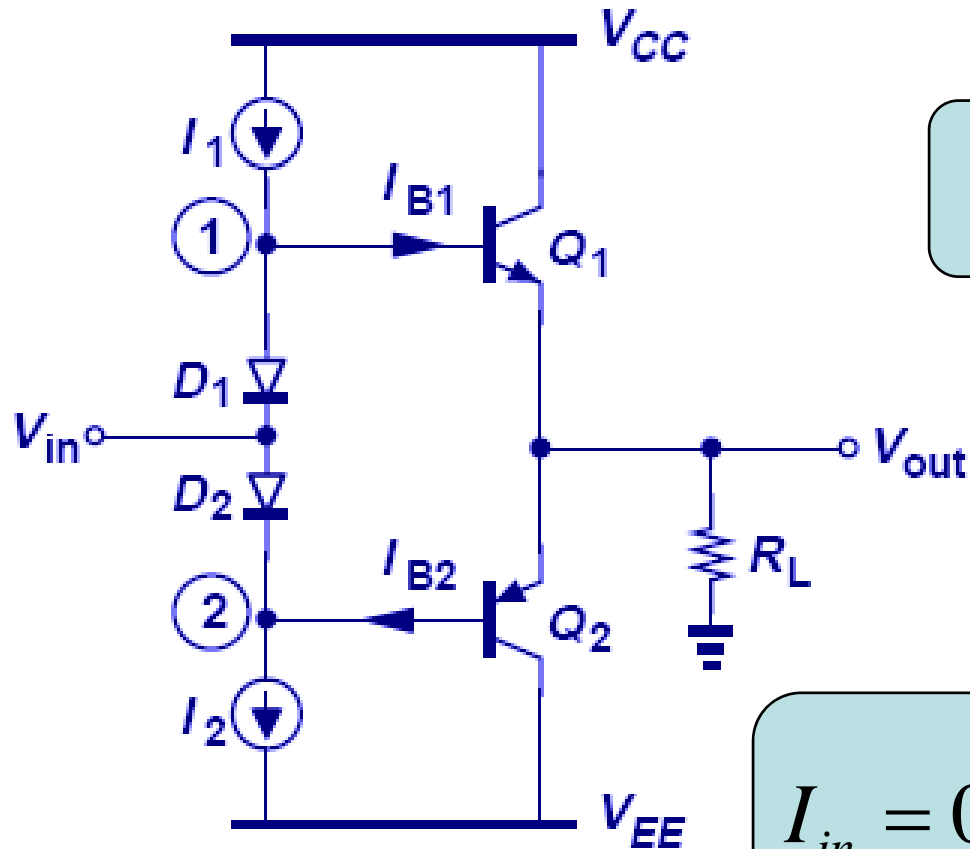

$$V_{D1} \approx V_{BE} \rightarrow V_{out} \approx V_{in}$$


$$I_{in} = 0 \text{ when } V_{out} = 0 \text{ if } I_1 = I_2$$

Addition of CE Stage

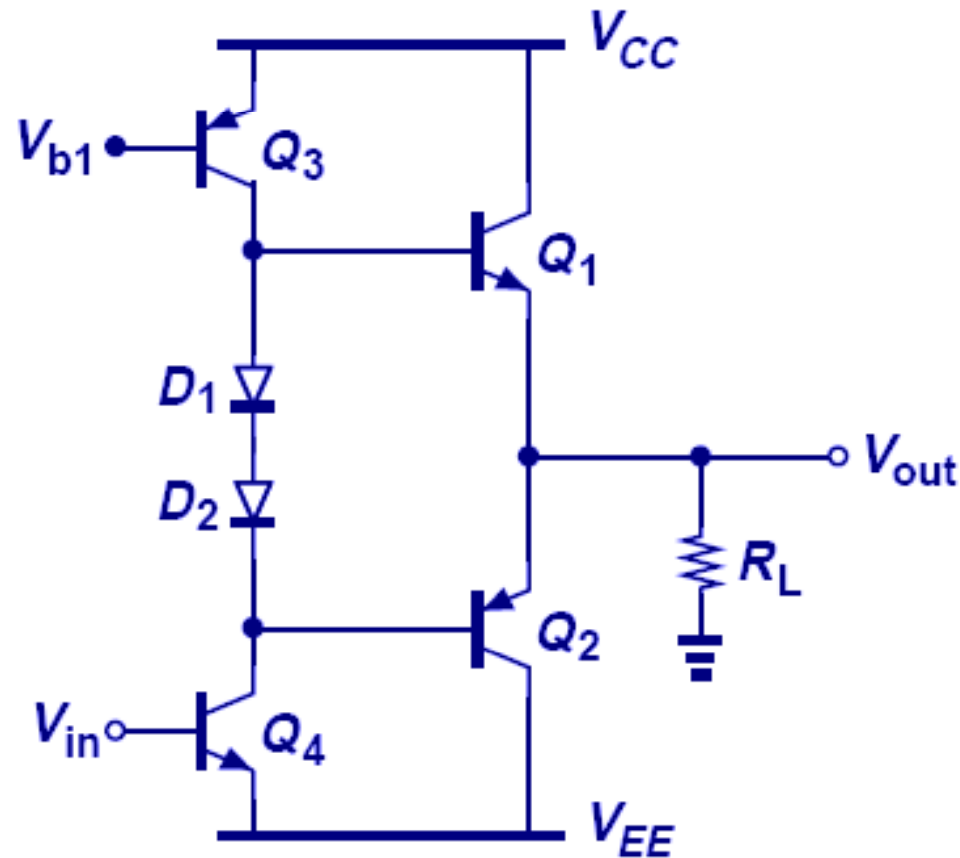

- A CE stage (predriver) is added to provide voltage gain from the input to the bases of Q_1 and Q_2 .


Bias Point Analysis

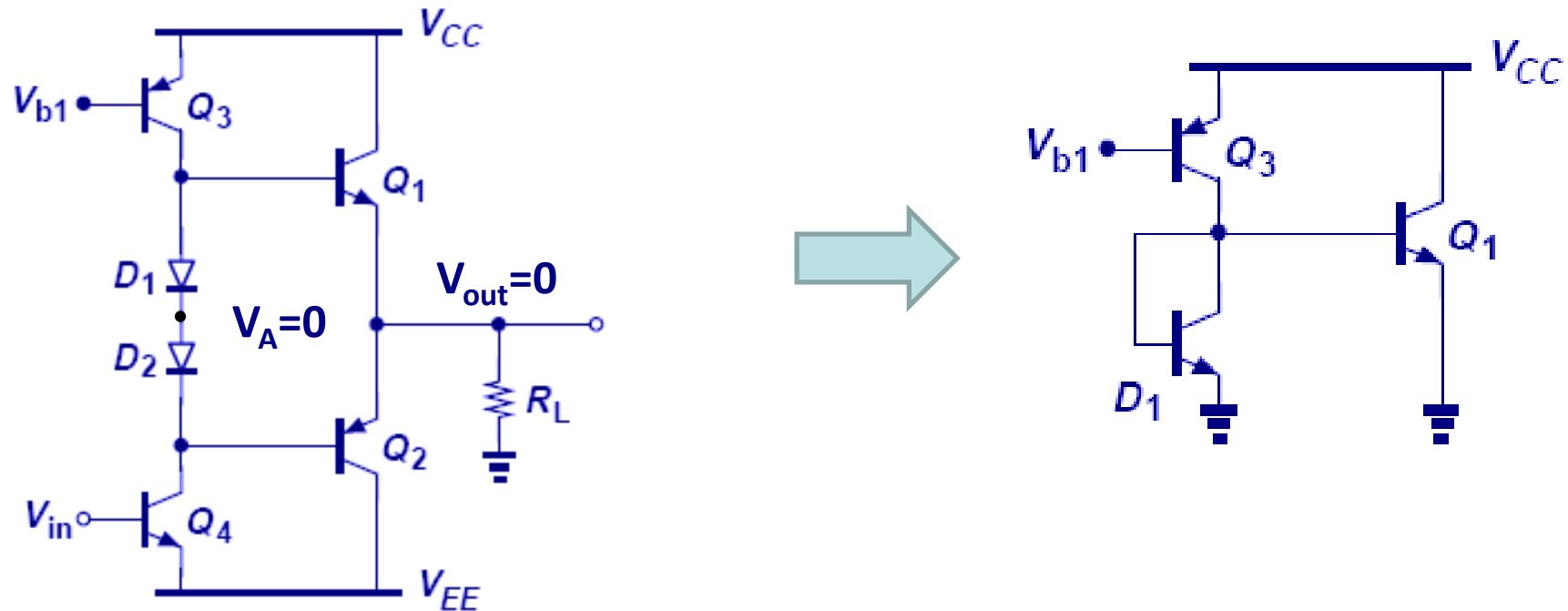

➤ For bias point analysis for $V_{out}=0$, the circuit can be simplified to the one on the right, which resembles a current mirror.

$$I_{C1} = \frac{I_{S,Q1}}{I_{S,D1}} \cdot |I_{C3}|$$


Small-Signal Analysis

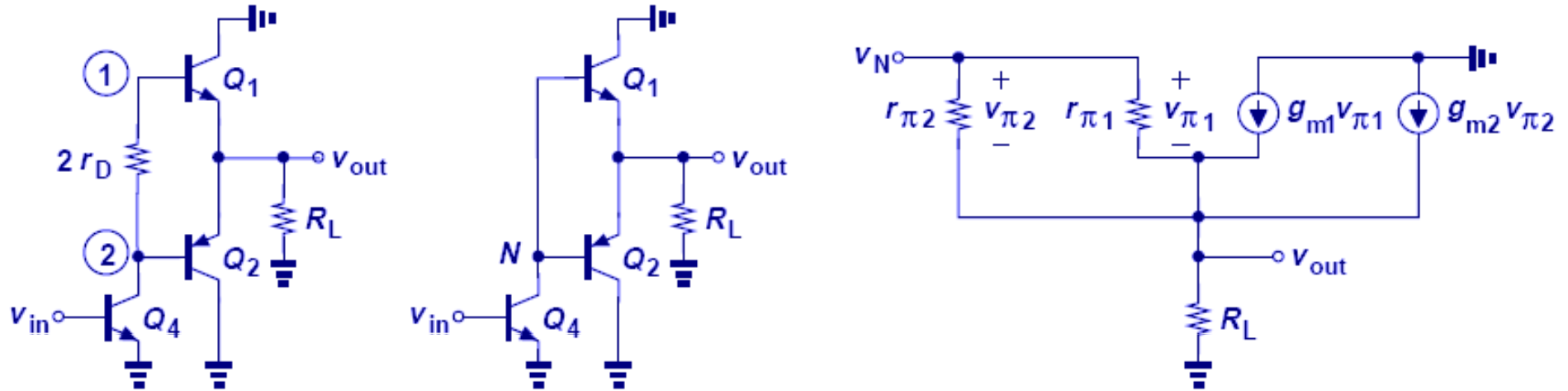

➤ Assuming $2r_D$ is small and $(g_{m1} + g_{m2})R_L$ is much greater than 1,

$$A_v = -g_{m4} (r_{\pi 1} \parallel r_{\pi 2}) (g_{m1} + g_{m2}) R_L$$

Example 13.9: Output Resistance Analysis

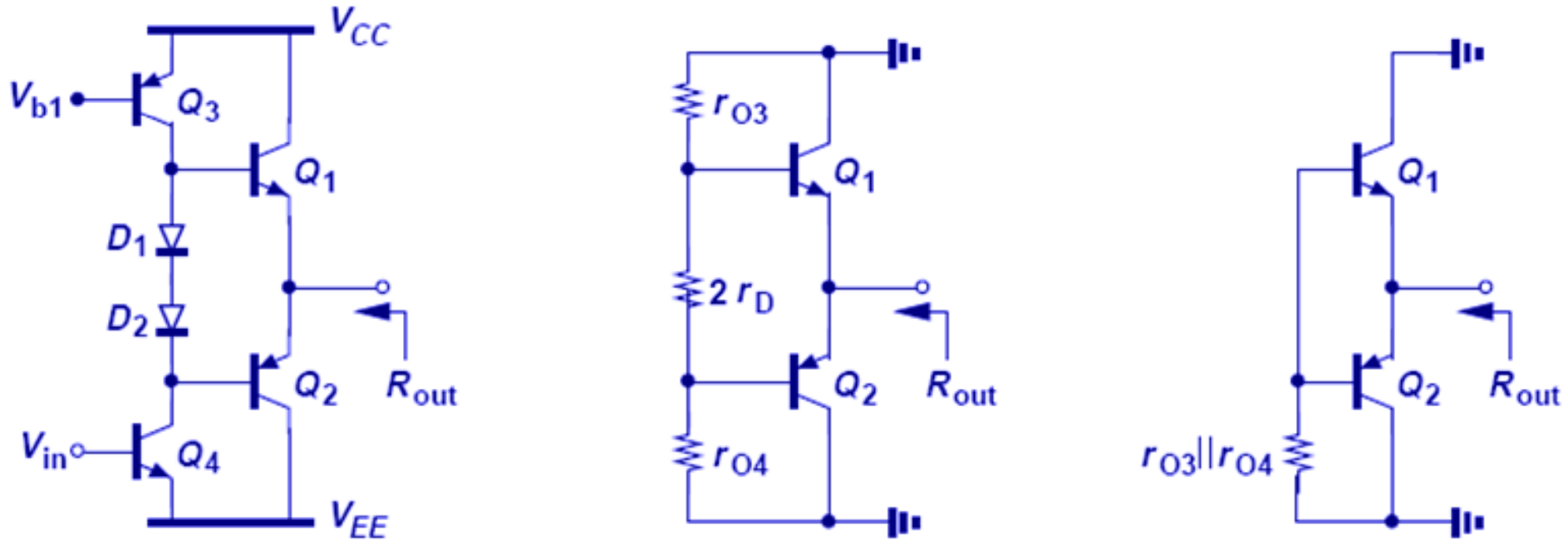


$$R_{out} \approx \frac{1}{g_{m1} + g_{m2}} + \frac{r_{O3} \parallel r_{O4}}{(g_{m1} + g_{m2})(r_{\pi 1} \parallel r_{\pi 2})}$$

- If β is low, the second term of the output resistance will rise, which will be problematic when driving a small resistance.

Example 13.10: Biasing

➤ Compute the required bias current.

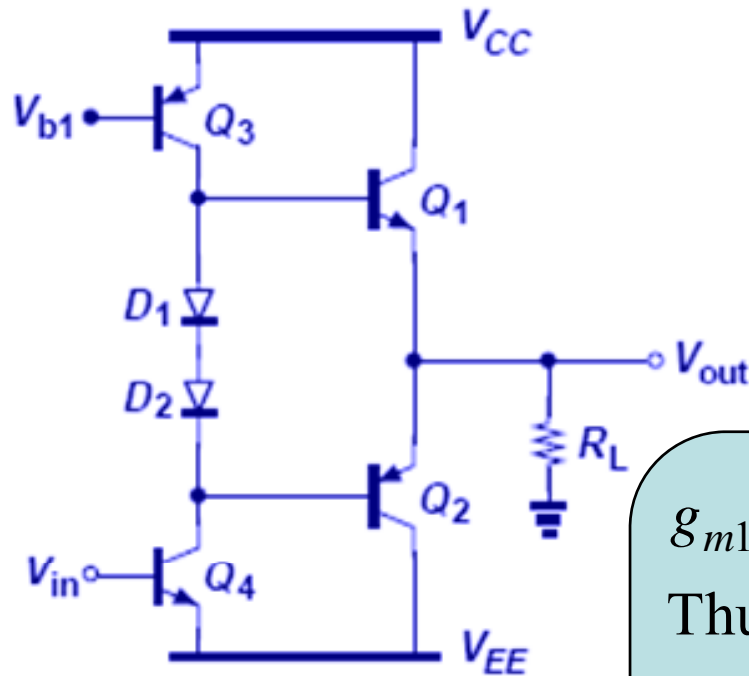

Predriver (CE stage): $A_V = 5$

Output Stage: $A_V = 0.8$ for $R_L = 8 \Omega$

$\beta_{nnp} = 2\beta_{pnp} = 100$, $I_{C1} \approx I_{C2}$

$$g_{m1} + g_{m2} = (2 \Omega)^{-1} \Rightarrow g_{m1} \approx g_{m2} \approx (4 \Omega)^{-1}$$


Thus, $I_{C1} \approx I_{C2} \approx 6.5 \text{ mA}$

$$r_{\pi 1} \parallel r_{\pi 2} = 400 \Omega \parallel 200 \Omega = 133 \Omega$$

$$g_{m4} \cdot (r_{\pi 1} \parallel r_{\pi 2}) \cdot [1 + (g_{m1} + g_{m2}) \cdot R_L] = 4$$


$$\Rightarrow g_{m4} = (133 \Omega)^{-1} \Rightarrow I_{C3} \approx I_{C4} \approx 195 \mu\text{A}$$

Problem of Base Current

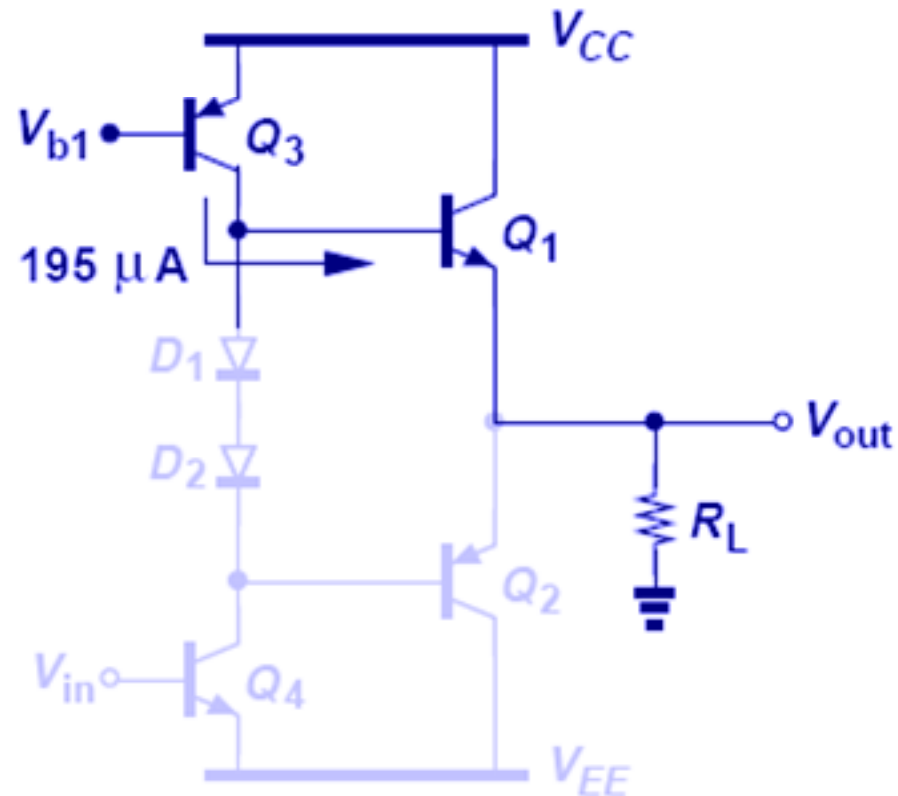

- **195 μA of base current in Q_1 can only support 19.5 mA of collector current, insufficient for high current operation (500 mA for 4 V on 8 Ω).**



Modification of the PNP Emitter Follower

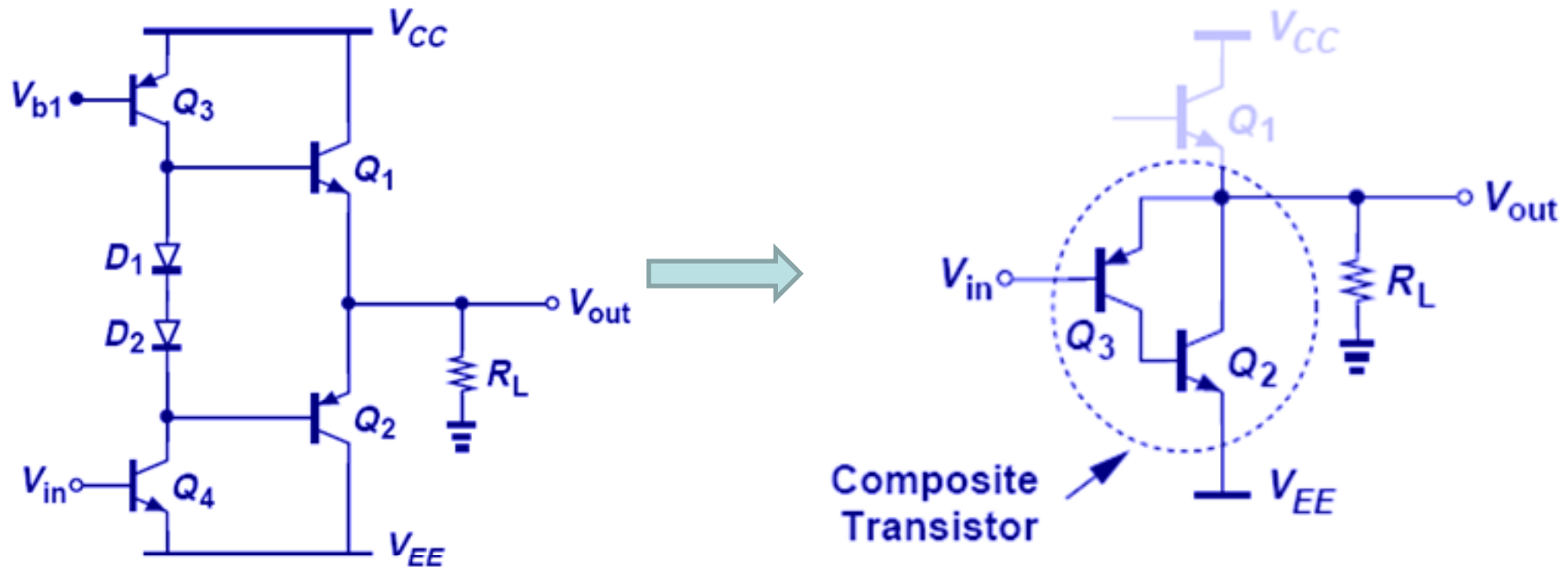

$$R_{out} \approx \frac{1}{(\beta_2 + 1)g_{m3}}$$

- Instead of having a single PNP as the emitter-follower, it is now combined with an NPN (Q_2), providing a lower output resistance.

Example 13.11: Input Resistance

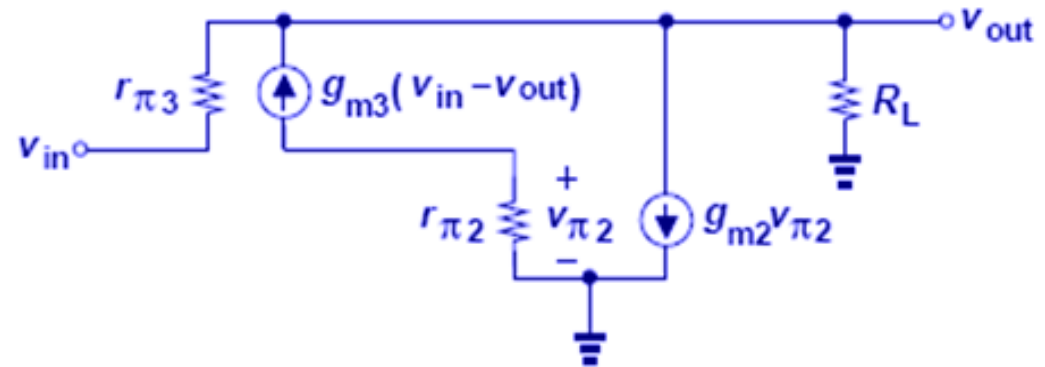
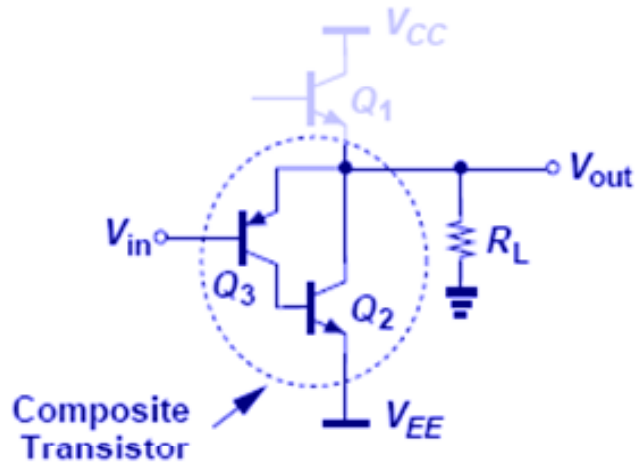


$$\frac{v_{out}}{v_{in}} = \frac{R_L}{R_L + \frac{1}{(\beta_2 + 1)g_{m3} + \frac{1}{r_{\pi 3}}}}$$

Comparing with the standard EF,

$$r_{out} = \frac{1}{(\beta_2 + 1)g_{m3} + \frac{1}{r_{\pi 3}}} \approx \frac{1}{(\beta_2 + 1)g_{m3}}$$


Example 13.11: Input Resistance

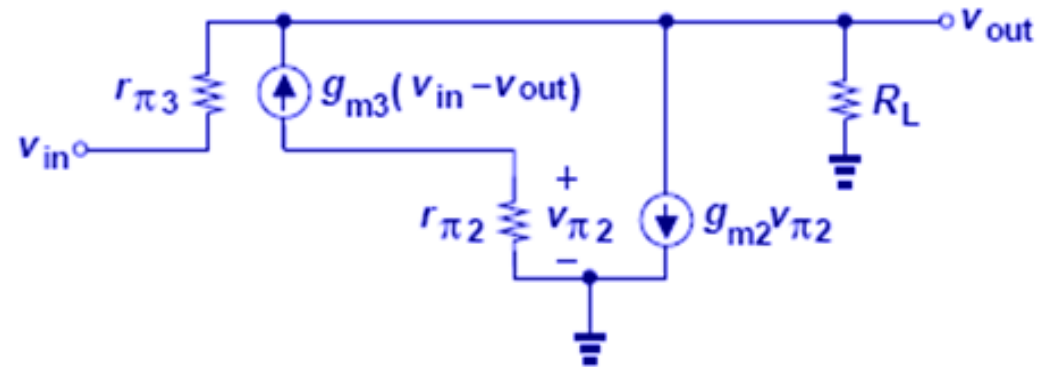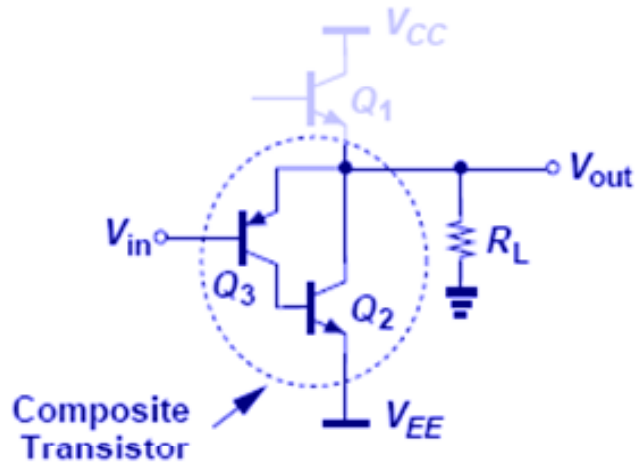

$$i_{in} = \frac{1}{r_{\pi 3}} \left(v_{in} - v_{in} \frac{R_L}{R_L + \frac{1}{(\beta_2 + 1) g_{m3}}} \right)$$


$$r_{in} = \beta_3 (\beta_2 + 1) R_L + r_{\pi 3}$$

Additional Bias Current

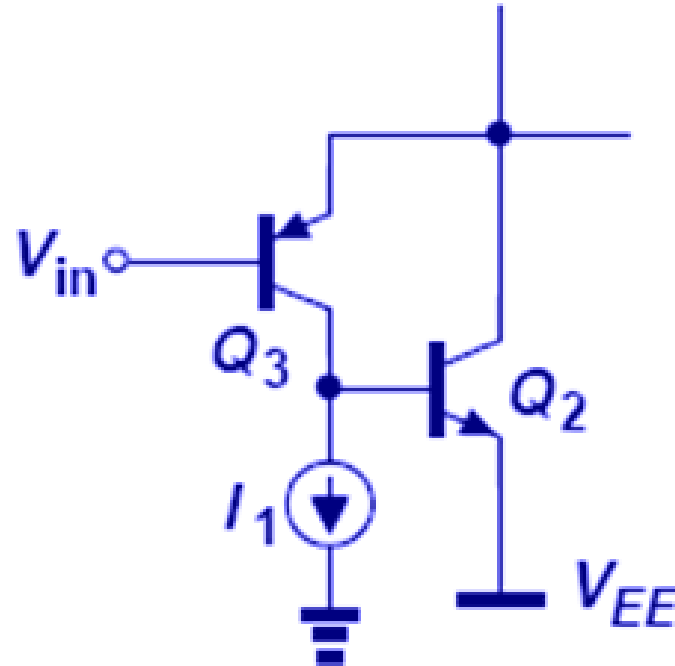

- I_1 is added to the base of Q_2 to provide an additional bias current to Q_3 so the capacitance at the base of Q_2 can be charged/discharged quickly. Additional pole at the base of Q_2 .


Example 13.12: Minimum V_{in}

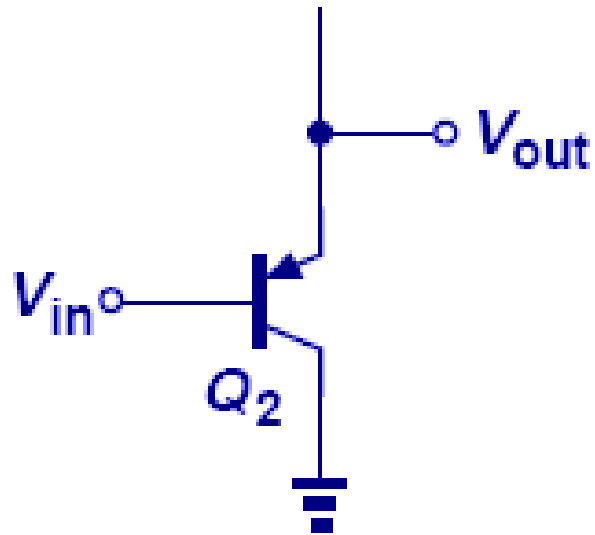

(a)

$$\text{Min } V_{in} \approx 0$$

$$V_{out} \approx |V_{EB2}|$$

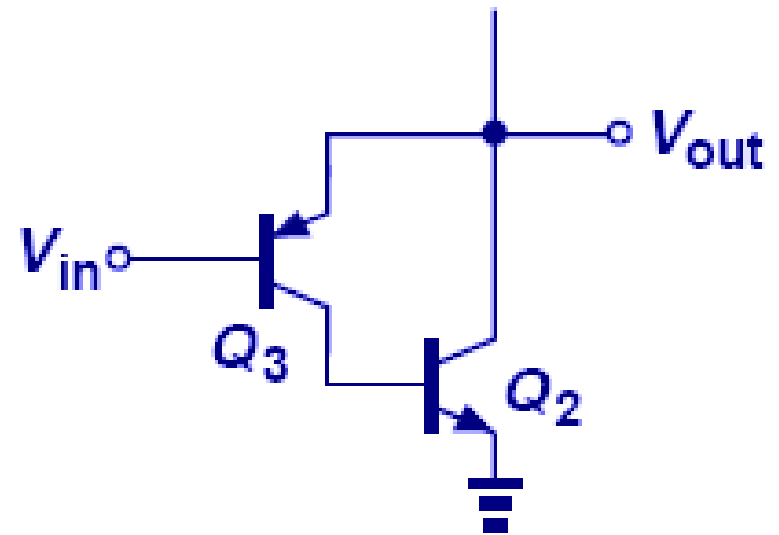


(b)

$$\text{Min } V_{in} \approx V_{BE2}$$


$$V_{out} \approx |V_{EB3}| + V_{BE2}$$

HiFi Design

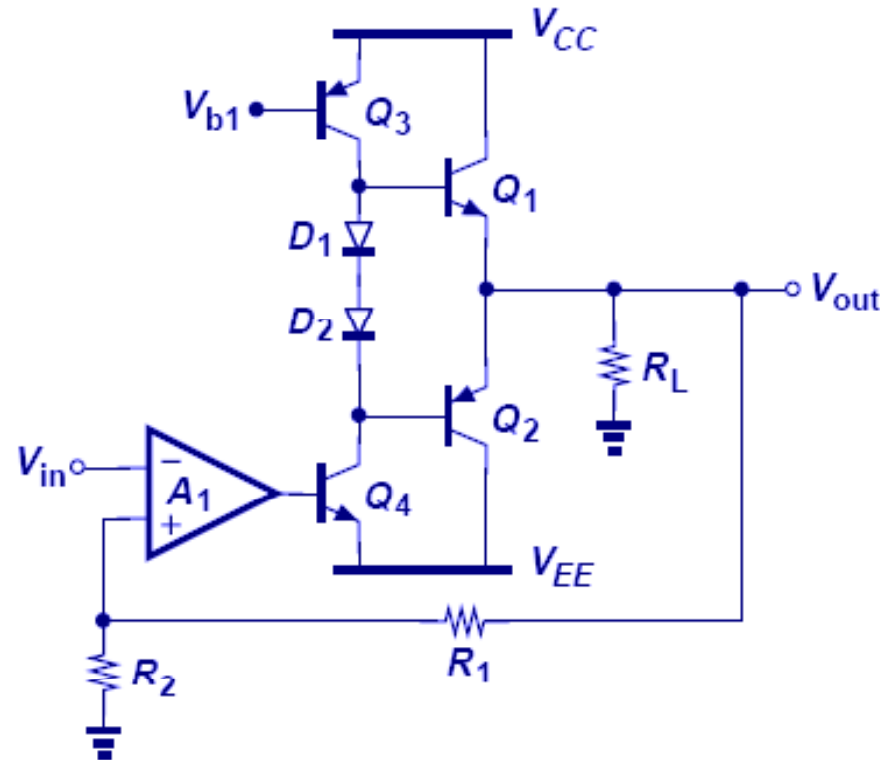


- As V_{out} becomes more positive, g_m rises and A_v comes closer to unity, resulting in nonlinearity.
- Using negative feedback, linearity is improved, providing higher fidelity.

Short-Circuit Protection

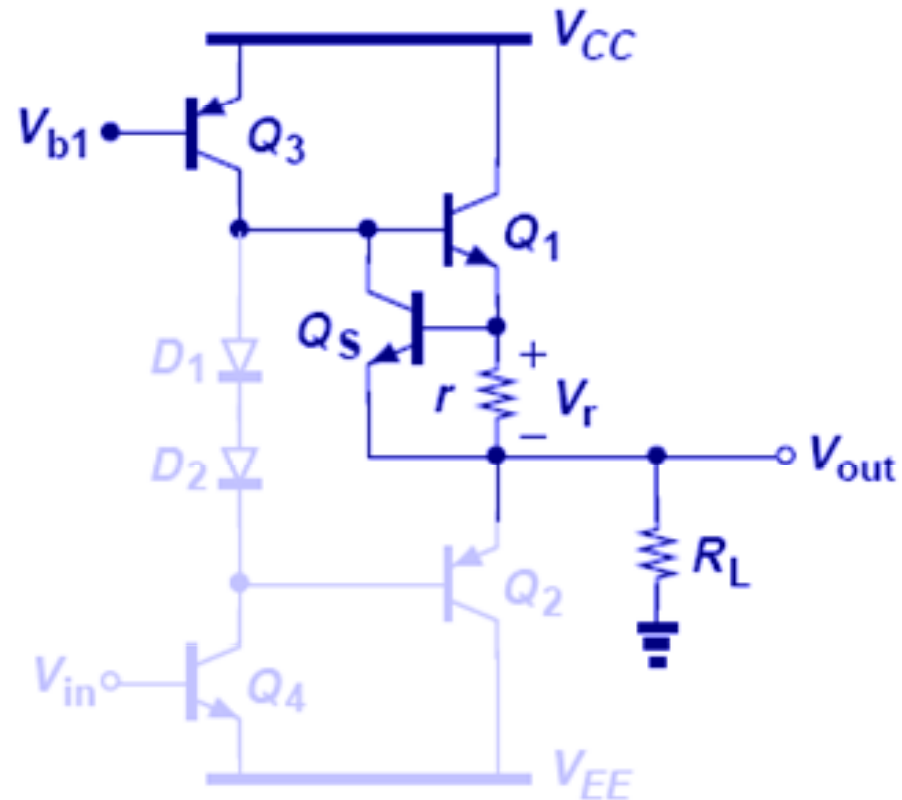

- Q_s and r are used to “steal” some base current away from Q_1 when the output is accidentally shorted to ground, preventing short-circuit damage.

Emitter Follower Power Rating

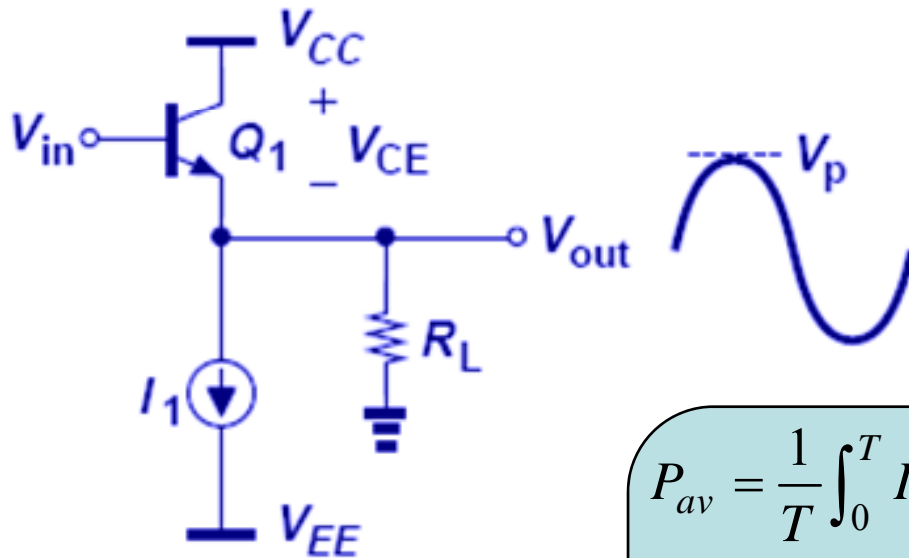


$$\begin{aligned}
 P_{av} &= \frac{1}{T} \int_0^T I_C \cdot V_{CE} dt \\
 &= \frac{1}{T} \int_0^T \left(I_1 + \frac{V_P \sin \omega t}{R_L} \right) \cdot (V_{CC} - V_P \sin \omega t) dt \\
 &= I_1 \cdot V_{CC} - \frac{V_P^2}{R_L} = I_1 \left(V_{CC} - \frac{V_P}{2} \right) \text{ if } I_1 = \frac{V_P}{R_L}
 \end{aligned}$$

- **Maximum power dissipated across Q_1 occurs in the *absence* of a signal.**

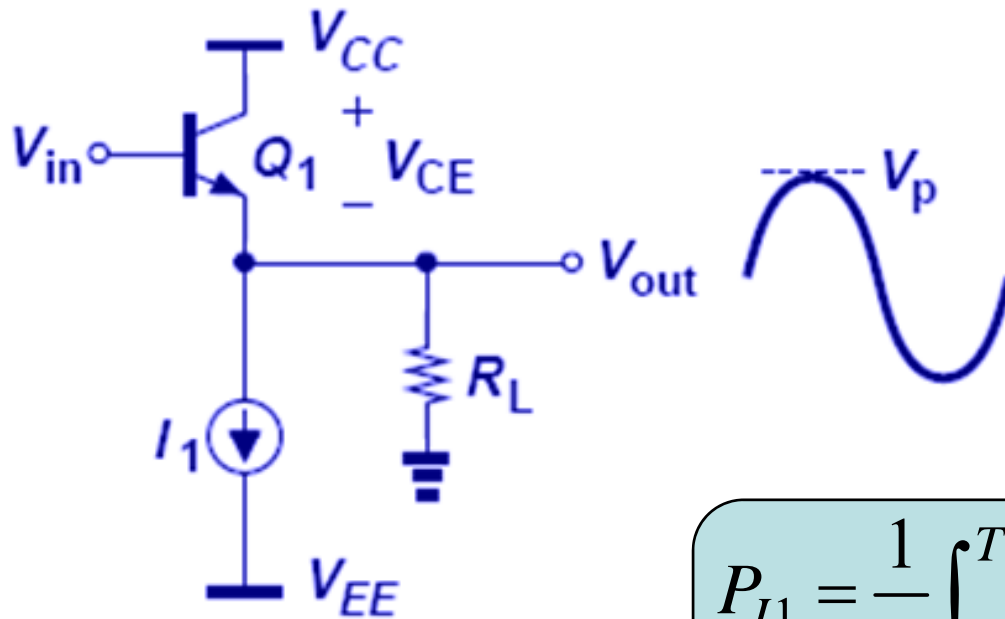
Example 13.13: Power Dissipation

➤ Avg Power Dissipated in the Current Source I_1



$$P_{I1} = \frac{1}{T} \int_0^T I_1 (V_p \sin \omega t - V_{EE}) dt$$
$$= -I_1 \cdot V_{EE}$$


Push-Pull Stage Power Rating

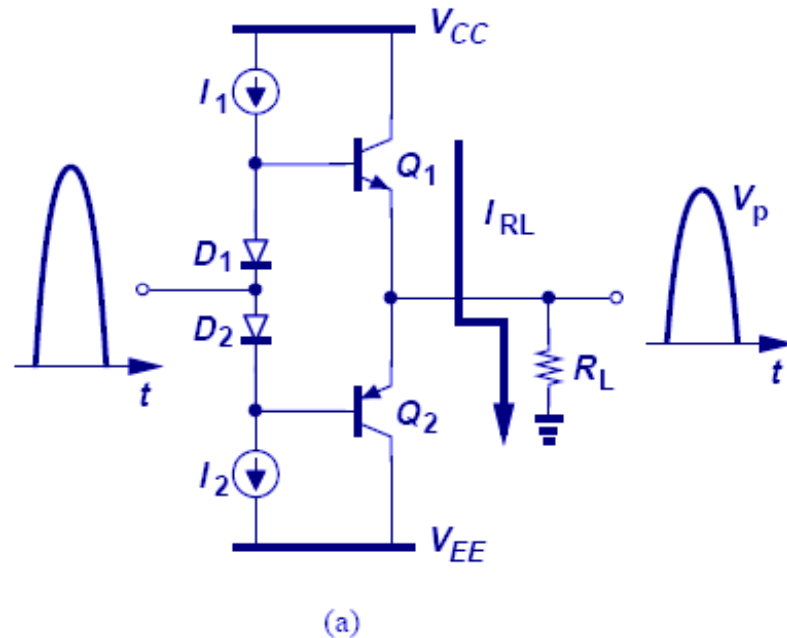

$$\begin{aligned}
 P_{av,NPN} &= \frac{1}{T} \int_0^{T/2} I_C \cdot V_{CE} dt \\
 &= \frac{1}{T} \int_0^{T/2} (V_{CC} - V_P \sin \omega t) \cdot \frac{V_P \sin \omega t}{R_L} dt \\
 &= \frac{V_{CC} \cdot V_P}{\pi R_L} - \frac{V_P^2}{4R_L} = \frac{V_P}{R_L} \left(\frac{V_{CC}}{\pi} - \frac{V_P}{4} \right)
 \end{aligned}$$

➤ **No power for half of the period.**

Push-Pull Stage Power Rating

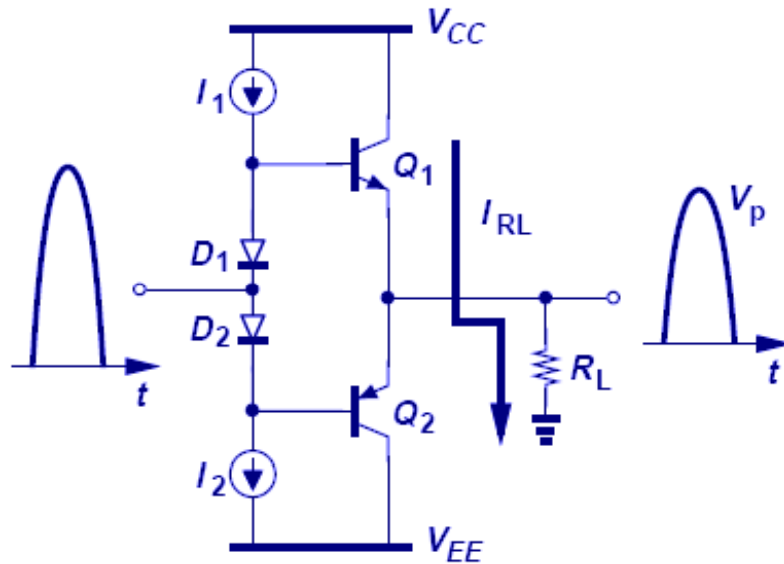

(a)


$$\begin{aligned}
 P_{av,NPN} &= \frac{1}{T} \int_0^{T/2} I_C \cdot V_{CE} dt \\
 &= \frac{1}{T} \int_0^{T/2} (V_{CC} - V_P \sin \omega t) \cdot \frac{V_P \sin \omega t}{R_L} dt \\
 &= \frac{V_{CC} \cdot V_P}{\pi R_L} - \frac{V_P^2}{4R_L} = \frac{V_P}{R_L} \left(\frac{V_{CC}}{\pi} - \frac{V_P}{4} \right)
 \end{aligned}$$

- No power for half of the period.
- Maximum power occurs between $V_p=0$ and $4V_{cc}/\pi$.

$$P_{av,max} = \frac{V_{CC}^2 \cdot V_P}{\pi^2 R_L} \text{ when } V_P = 2 \cdot \frac{V_{CC}}{\pi}$$

Push-Pull Stage Power Rating


$$\begin{aligned}
 P_{av,PNP} &= \frac{1}{T} \int_{T/2}^T |I_C| \cdot |V_{CE}| dt \\
 &= \frac{1}{T} \int_{T/2}^T (V_P \sin \omega t - V_{EE}) \cdot \left(-\frac{V_P \sin \omega t}{R_L} \right) dt \\
 &= \frac{-V_{EE} \cdot V_P}{\pi R_L} - \frac{V_P^2}{4R_L} = \frac{V_P}{R_L} \left(\frac{-V_{EE}}{\pi} - \frac{V_P}{4} \right)
 \end{aligned}$$

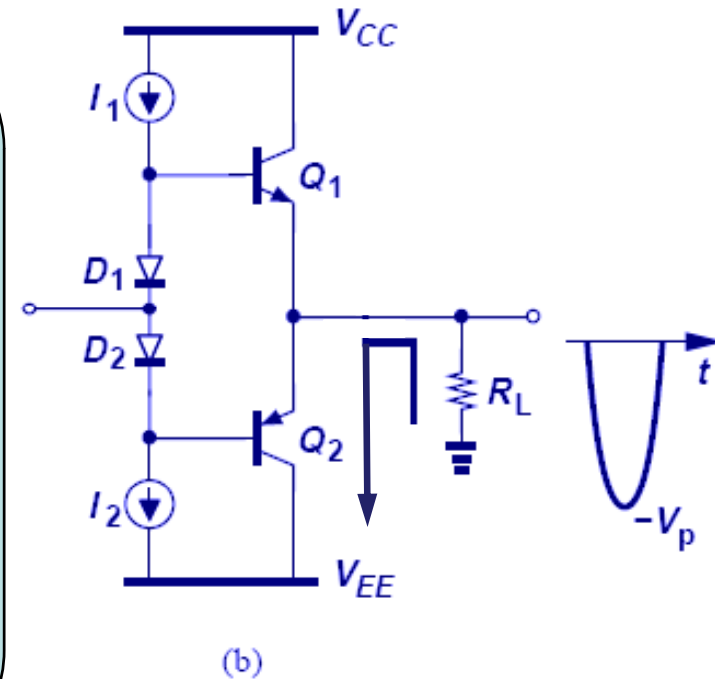

➤ Maximum power occurs between $V_p=0$ and $4V_{CC}/\pi$.


$$P_{av,max} = \frac{V_{CC}^2 \cdot V_P}{\pi^2 R_L} \text{ when } V_P = 2 \cdot \frac{V_{CC}}{\pi}$$

Heat Sink

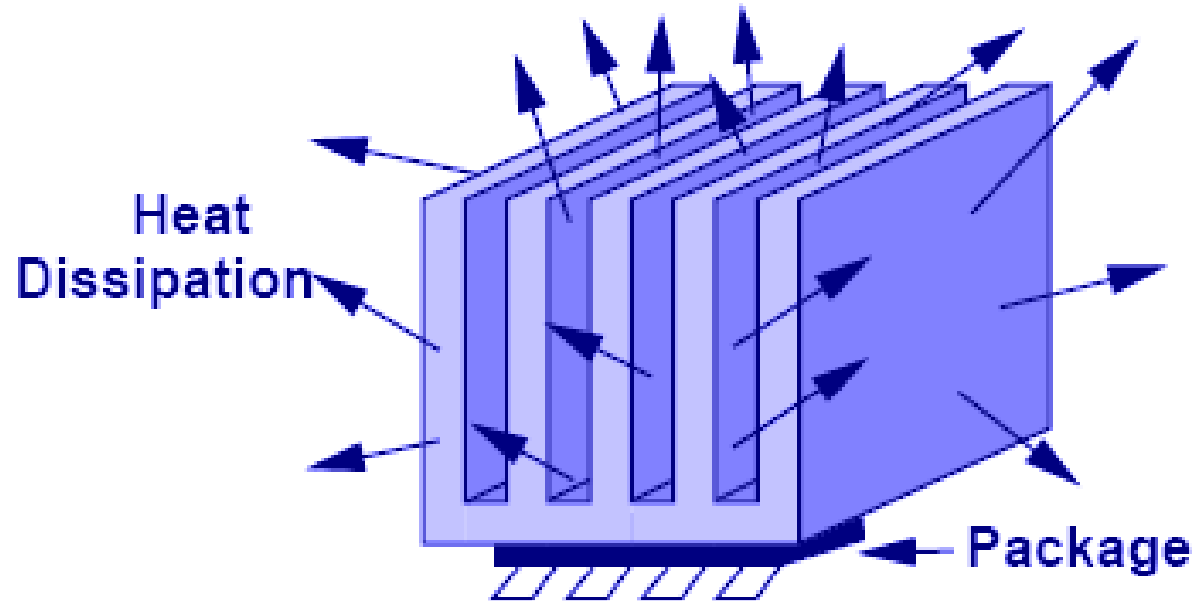

- **Heat sink, provides large surface area to dissipate heat from the chip.**

Thermal Runaway Mitigation

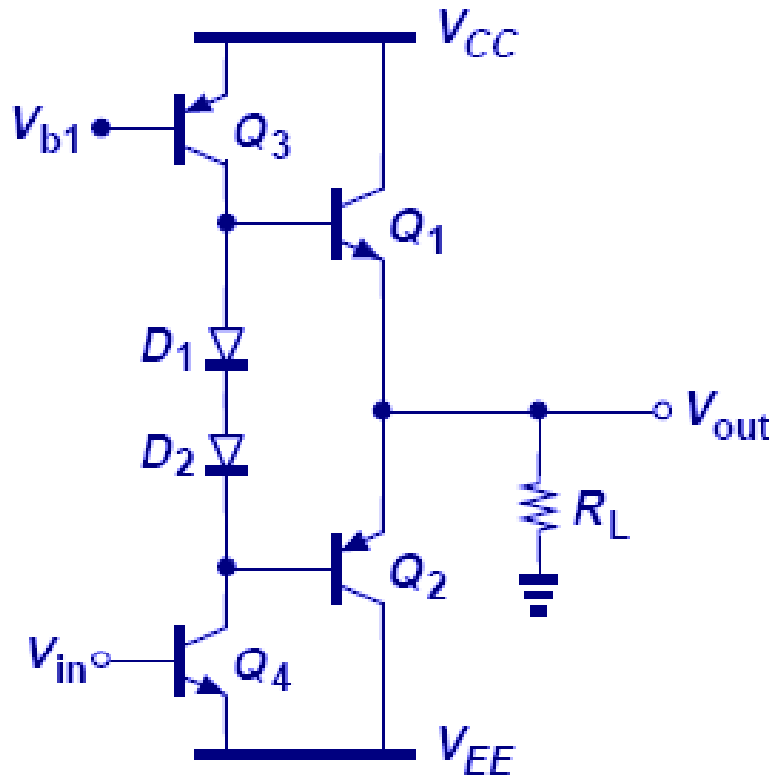

$$V_{D1} + V_{D2} = V_T \ln \frac{I_{D1}}{I_{S,D1}} + V_T \ln \frac{I_{D2}}{I_{S,D2}}$$

$$= V_T \ln \frac{I_{D1} I_{D2}}{I_{S,D1} I_{S,D2}}$$

$$V_{BE1} + V_{BE2} = V_T \ln \frac{I_{C1}}{I_{S,Q1}} + V_T \ln \frac{I_{C2}}{I_{S,Q2}}$$

$$= V_T \ln \frac{I_{C1} I_{C2}}{I_{S,Q1} I_{S,Q2}}$$

With the same V_T ,

$$\frac{I_{D1} I_{D2}}{I_{S,D1} I_{S,D2}} = \frac{I_{C1} I_{C2}}{I_{S,Q1} I_{S,Q2}}$$

- Using diode biasing prevents thermal runaway since the currents in Q_1 and Q_2 will track those of D_1 and D_2 as long as their I_s 's track with temperature.

Efficiency

- **Efficiency is defined as the average power delivered to the load divided by the power drawn from the supply**

$$\eta = \frac{\text{Power Delivered to Load}}{\text{Power Drawn From Supply Voltage}} = \frac{P_{out}}{P_{out} + P_{ckt}}$$


Emitter Follower

$$\begin{aligned}\eta_{EF} &= \frac{V_P^2 / 2R_L}{V_P^2 / 2R_L + I_1 (V_{CC} - V_P / 2) - I_1 \cdot V_{EE}} \\ &= \frac{V_P}{4V_{CC}} \text{ if } I_1 = \frac{V_P}{R_L} \text{ and } -V_{EE} = V_{CC}\end{aligned}$$

- **Maximum efficiency for EF is 25%.**

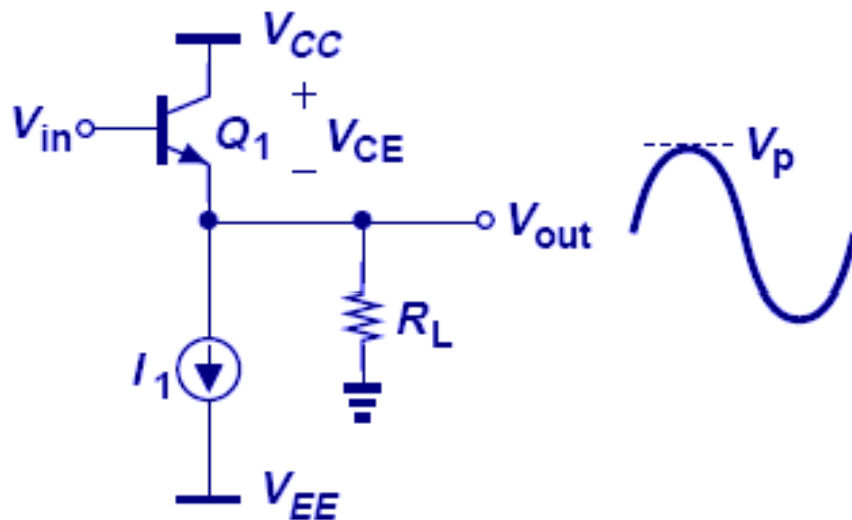Example 13.15: Efficiency of EF

➤ EF designed for full swing operates with half swing.



$$\text{With } I_1 = \frac{V_P}{R_L} = \frac{V_{CC}}{R_L} \text{ and } -V_{EE} = V_{CC}$$

$$\eta_{EF} = \frac{V_P^2 / 2R_L}{V_P^2 / 2R_L + I_1(V_{CC} - V_P/2) - I_1 \cdot V_{EE}}$$

$$= \frac{V_P^2 / 2R_L}{V_P^2 / 2R_L + \frac{V_{CC}}{R_L}(V_{CC} - V_P/2) + \frac{V_{CC}}{R_L} \cdot V_{CC}}$$

Thus,

$$\eta_{EF} \Big|_{V_P=V_{CC}/2} = \frac{1}{15}$$

Efficiency

Push-Pull Stage

$$\eta_{PP} = \frac{\frac{V_P^2}{2R_L}}{\frac{V_P^2}{2R_L} + \frac{2V_P}{R_L} \left(\frac{V_{CC}}{\pi} - \frac{V_P}{4} \right)}$$
$$= \frac{\pi V_P}{4 V_{CC}}$$

➤ **Maximum efficiency for PP is 78.5%.**


Example 13.16: Efficiency incl. Predriver

$$I_1 = (V_P / R_L) / \beta$$


$$\eta = \frac{\frac{V_P^2}{2R_L}}{\frac{2V_P V_{CC}}{\pi R_L} + (V_{CC} - V_{EE}) \frac{V_P}{\beta R_L}}$$

$$= \frac{1}{4} \frac{V_P}{V_{CC} / \pi + V_{CC} / \beta}$$
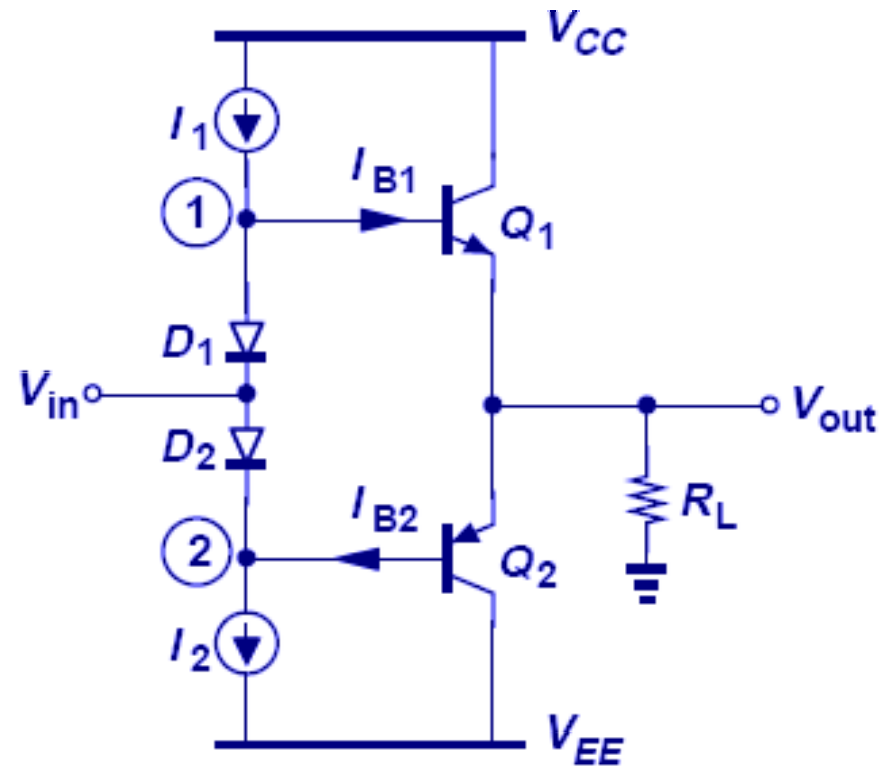
$$= \frac{1}{4} \frac{1}{\frac{1}{\pi} + \frac{1}{\beta}} \frac{V_P}{V_{CC}}$$




Power Amplifier Classes

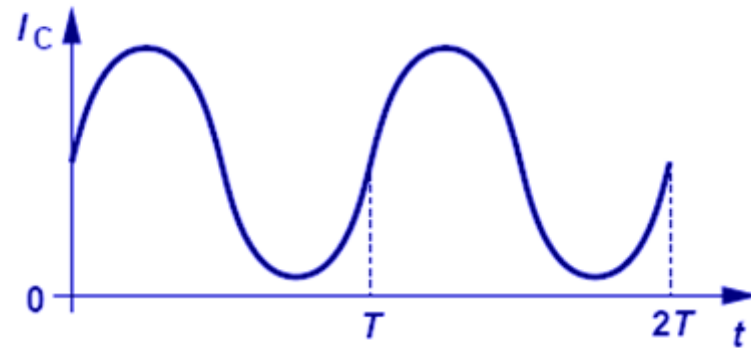


(a)

Class A: High linearity, low efficiency

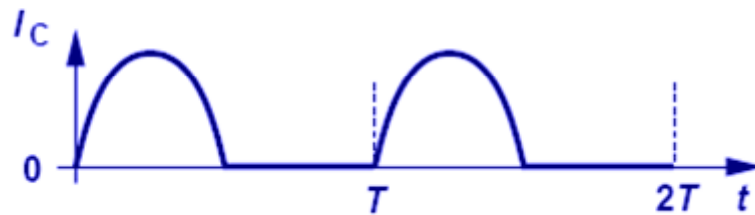

(b)

Class B: High efficiency, low linearity

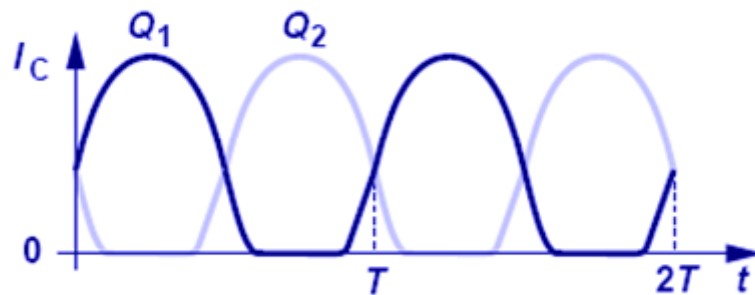

(c)

Class AB: Compromise between Class A and B