

Chapter 9

Operational Amplifiers

Important Parameters

Gain

Small-Signal Bandwidth

Large-Signal Bandwidth



Output Swing

Linearity



Noise and Offset

Supply Rejection



One-Stage Op Amps

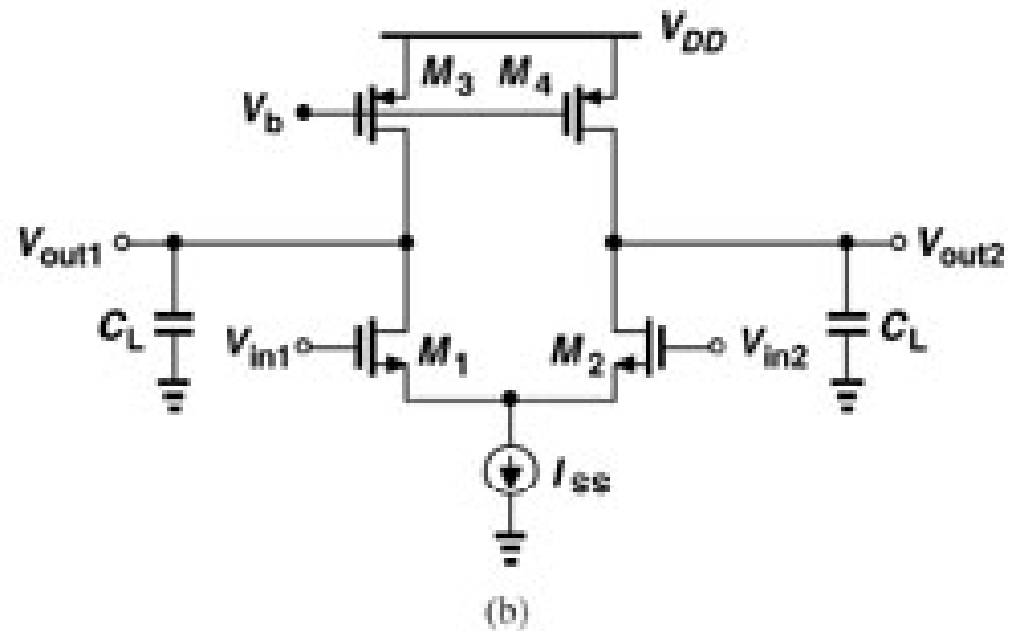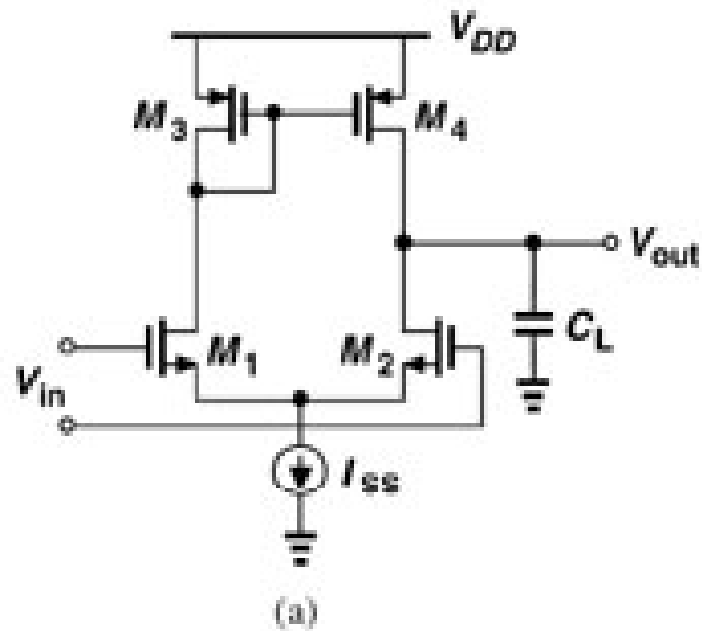

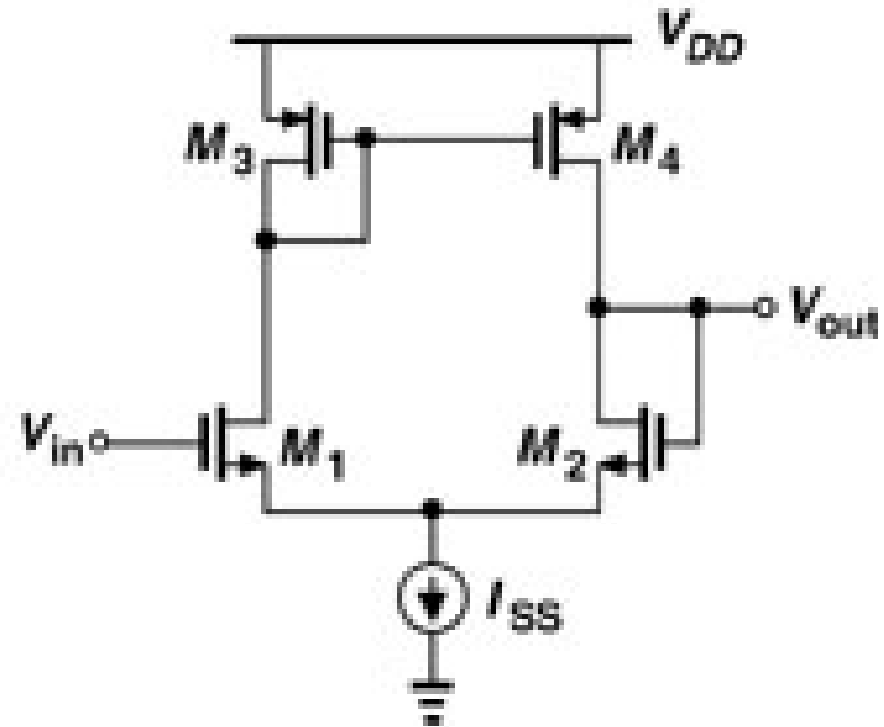
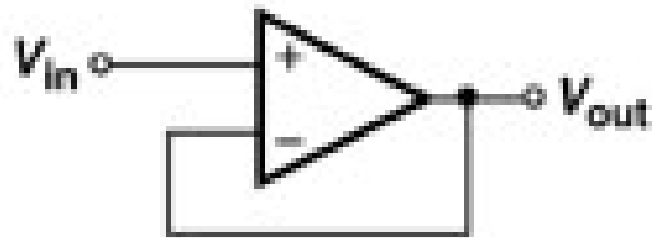
One-Stage Op Amp in Unity Gain Configuration




Cascode Op Amps

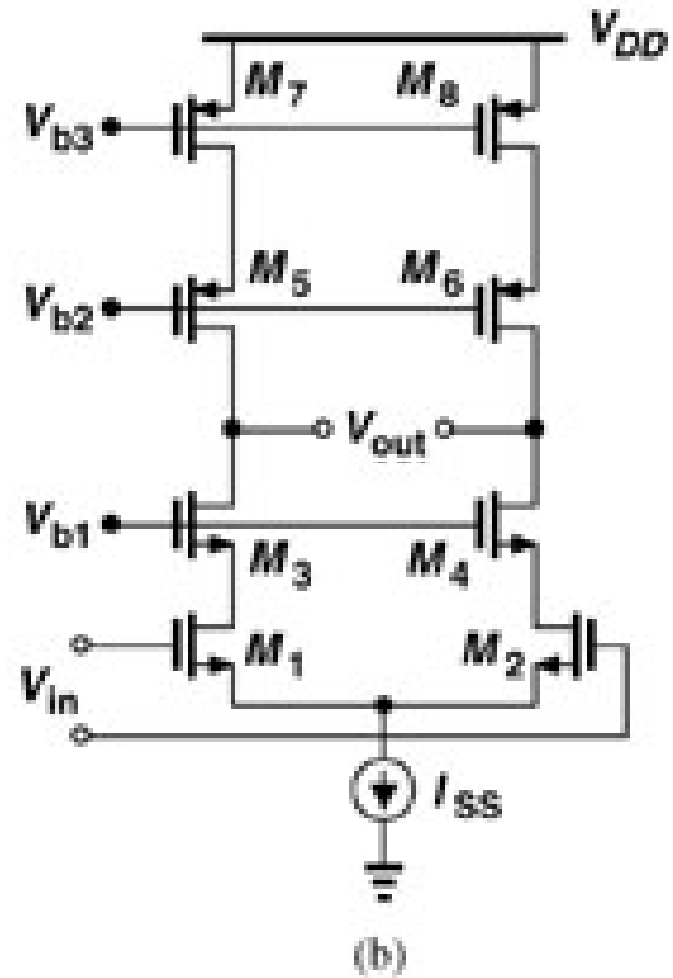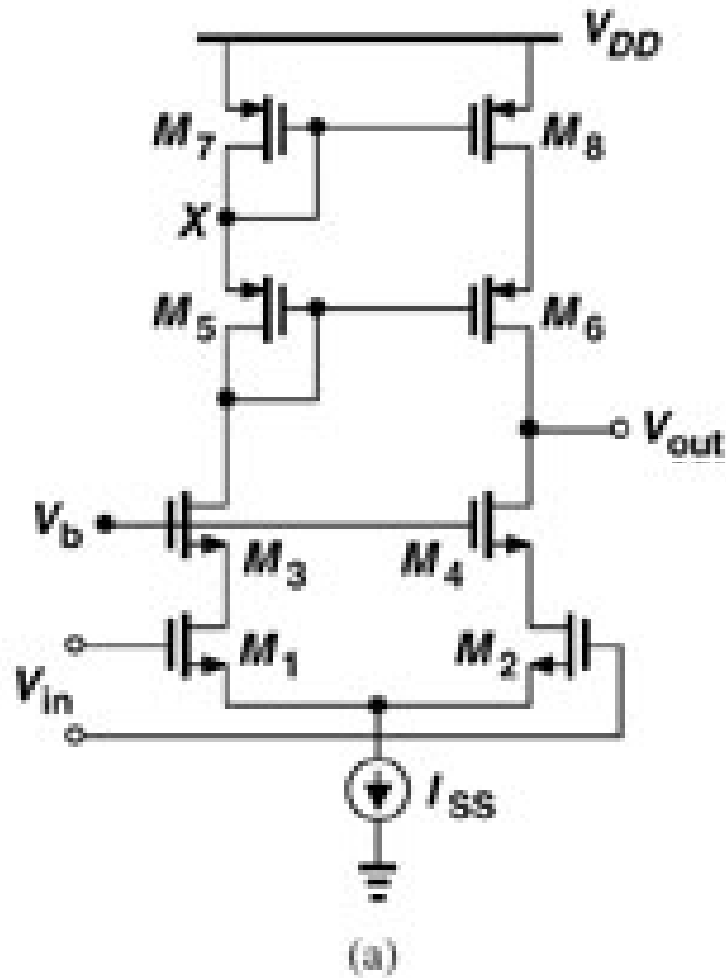


Unity Gain One Stage Cascode

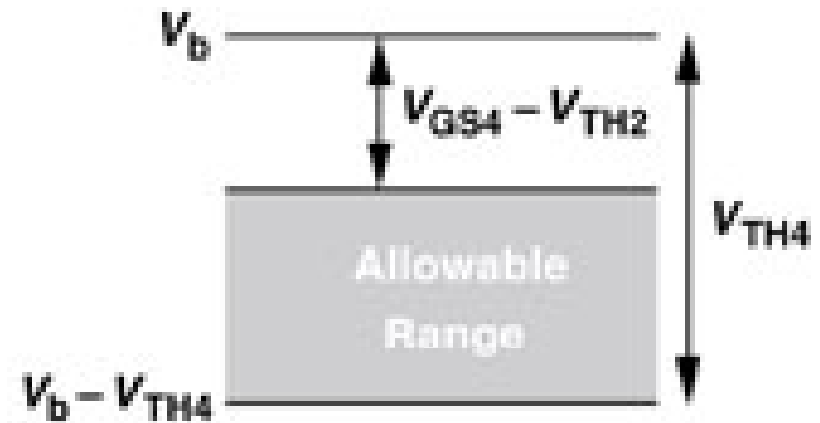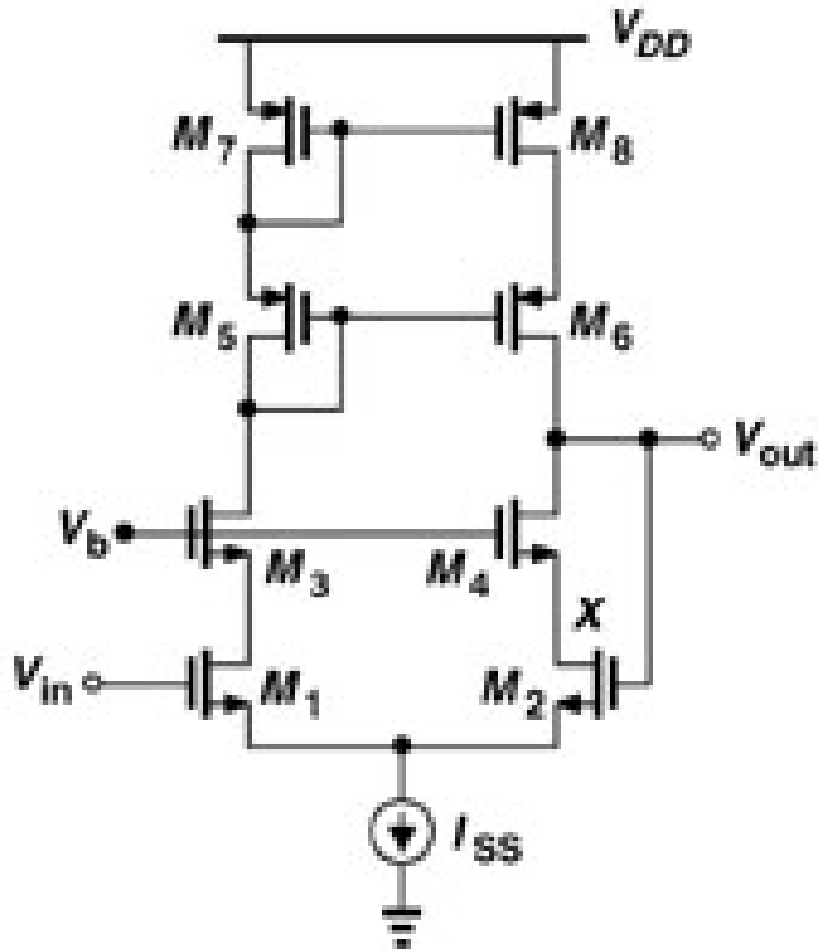



Folded Cascode Op Amps

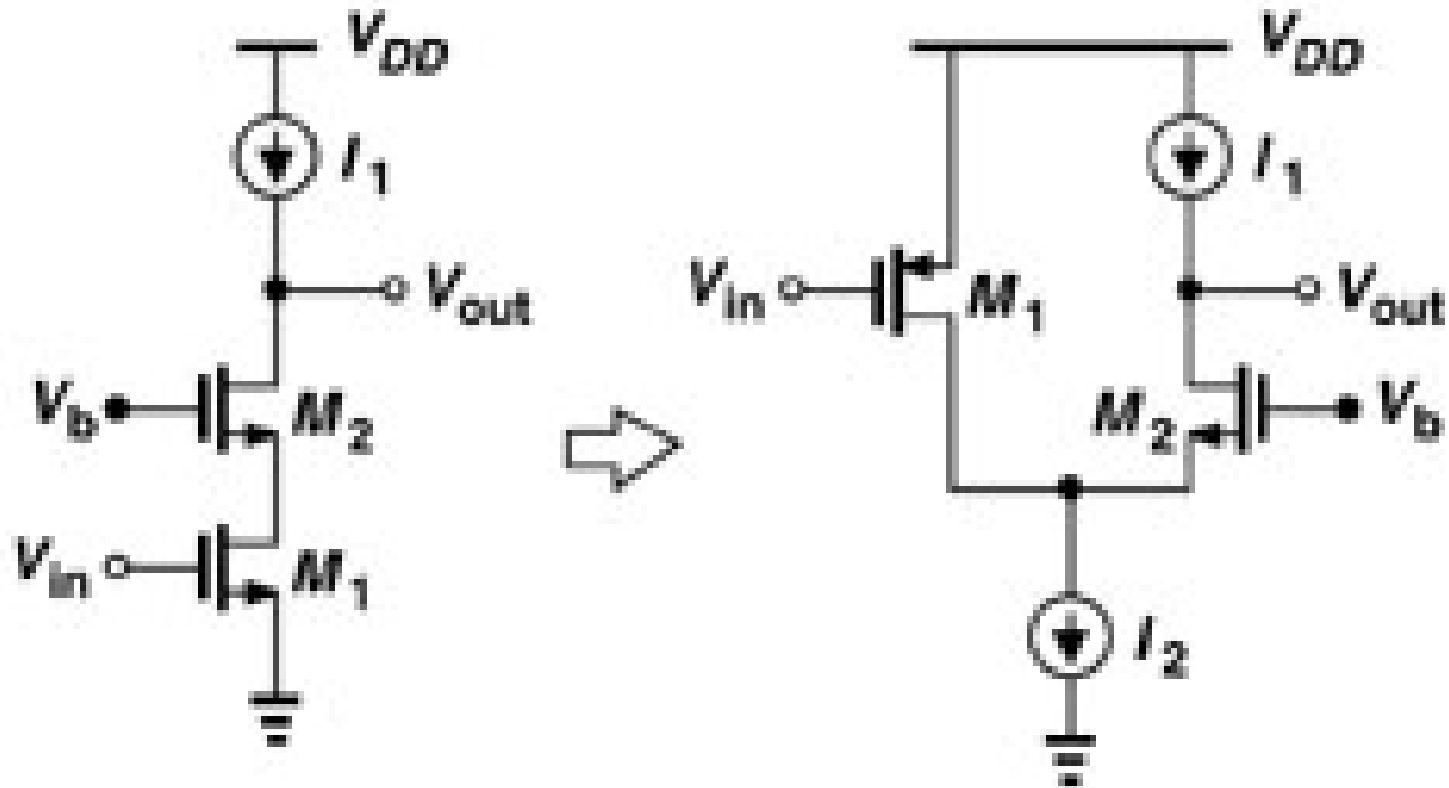


Folded Cascode Stages (cont.)

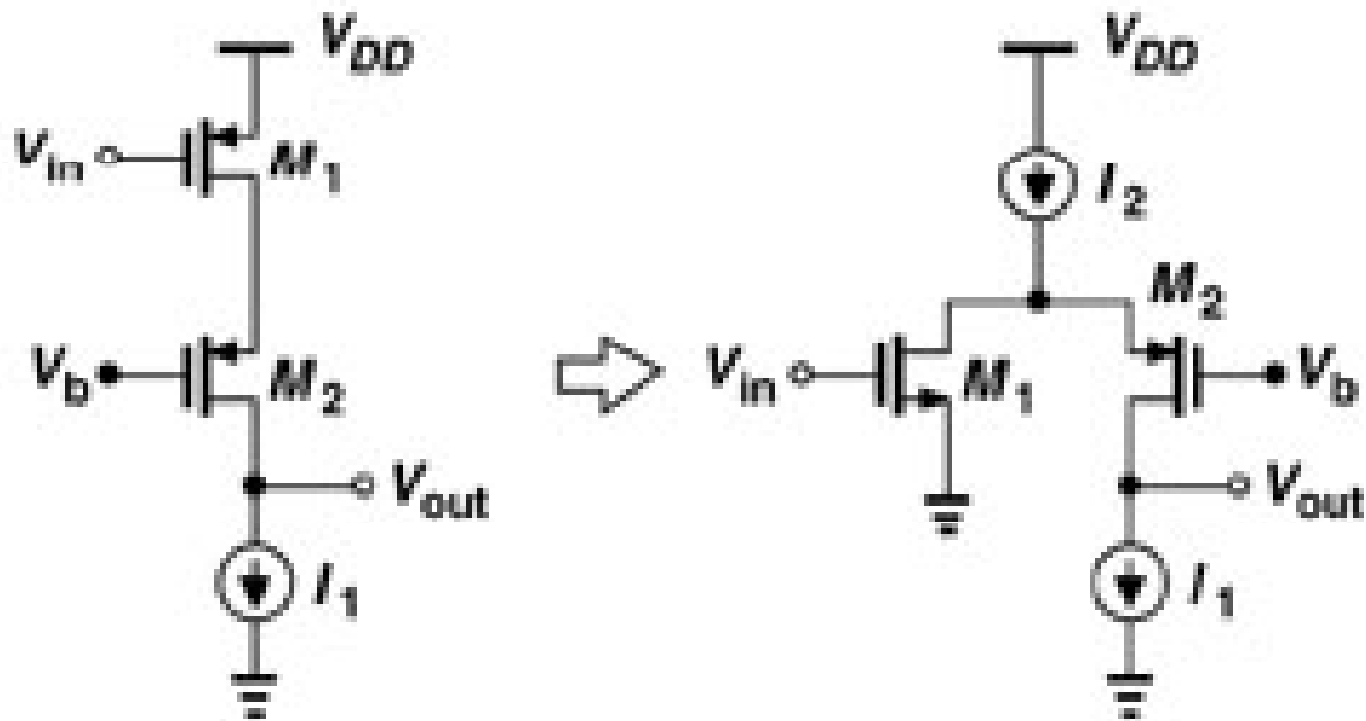

Folded Cascode (cont.)

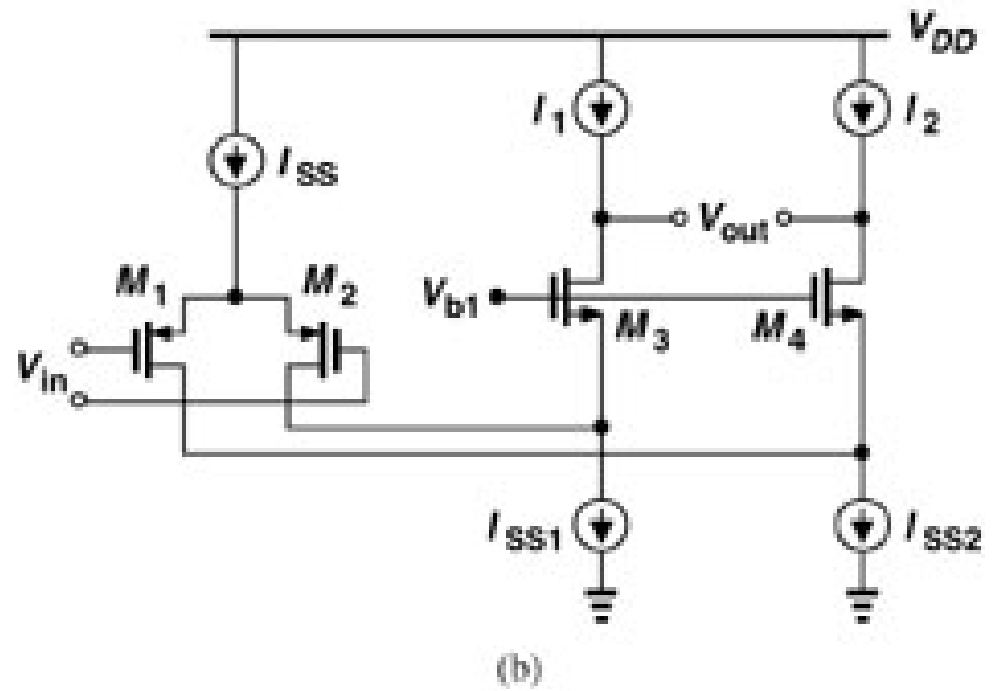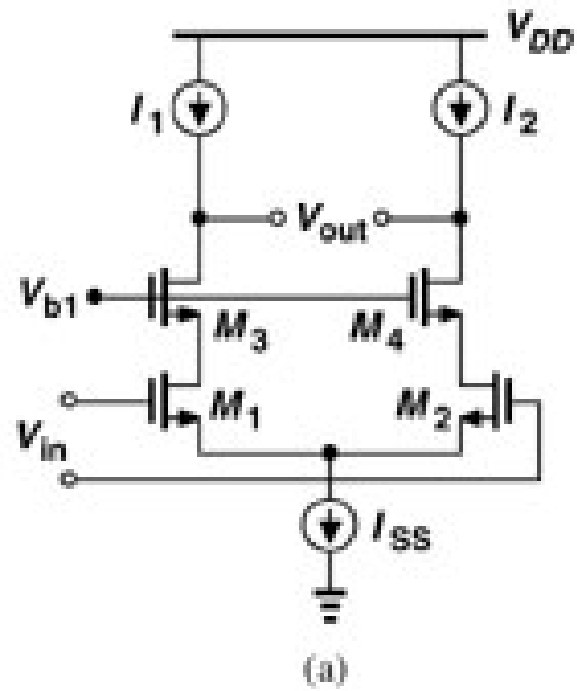


Folded Cascode (cont.)

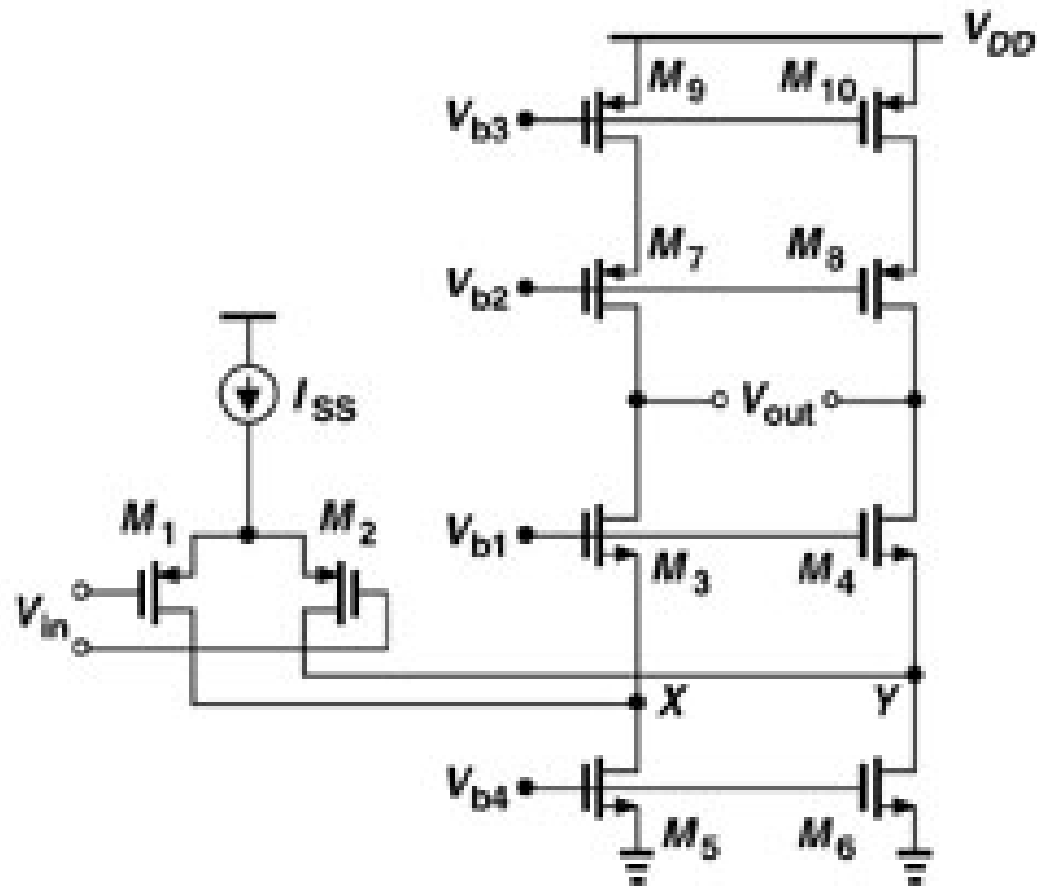


$$|A_v| \approx g_{m1} \{ [(g_{m3} + g_{mb3})r_{o3}(r_{o1} \parallel r_{o5})] \parallel [(g_{m7} + g_{mb7})r_{o7}r_{o9}] \}$$

Telescopic vs. Folded Cascode Pole


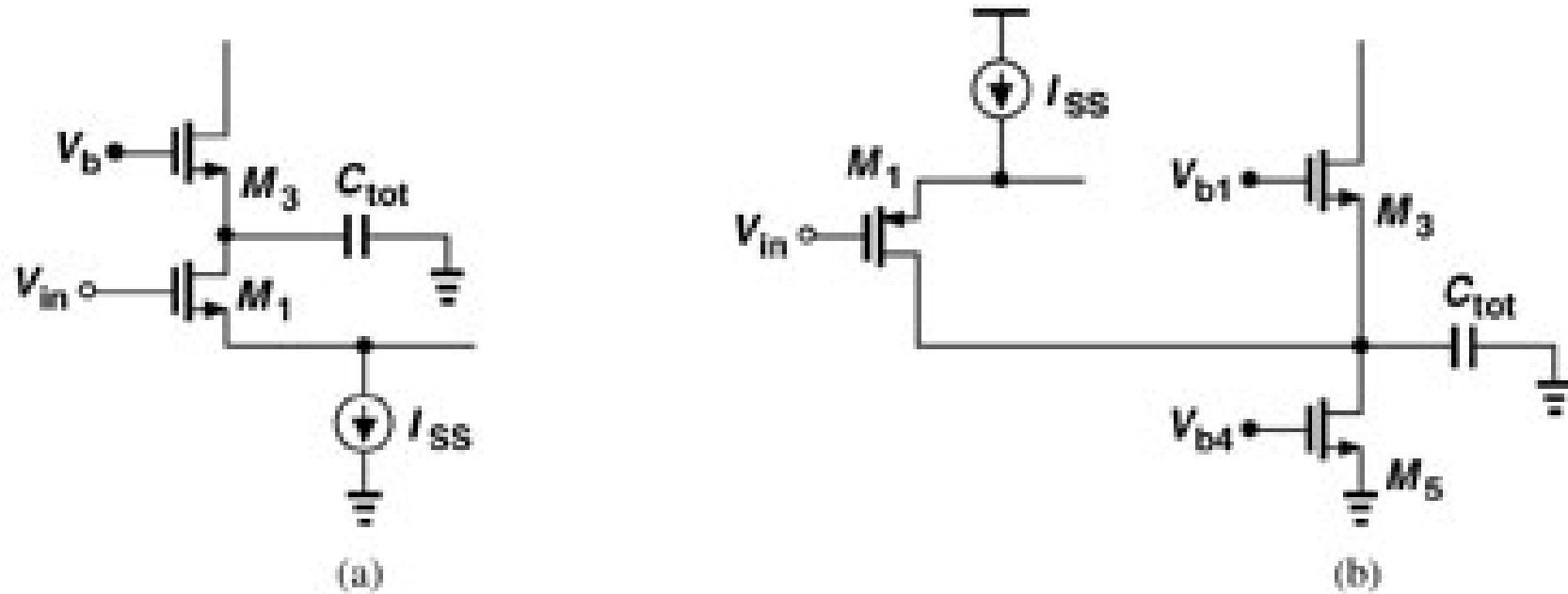


Example Folded-Cascode Op Amp

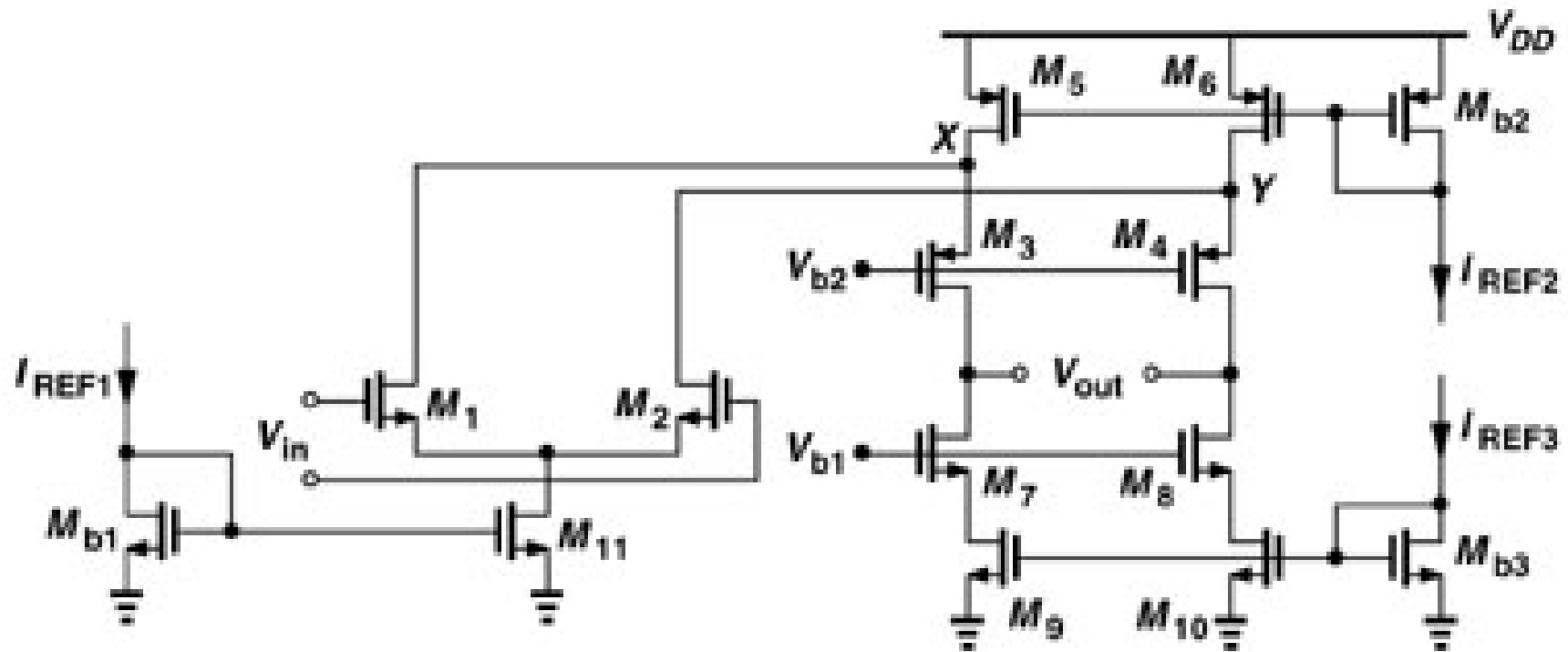


See Example 9.6

Single-Ended Output Cascode Op Amps

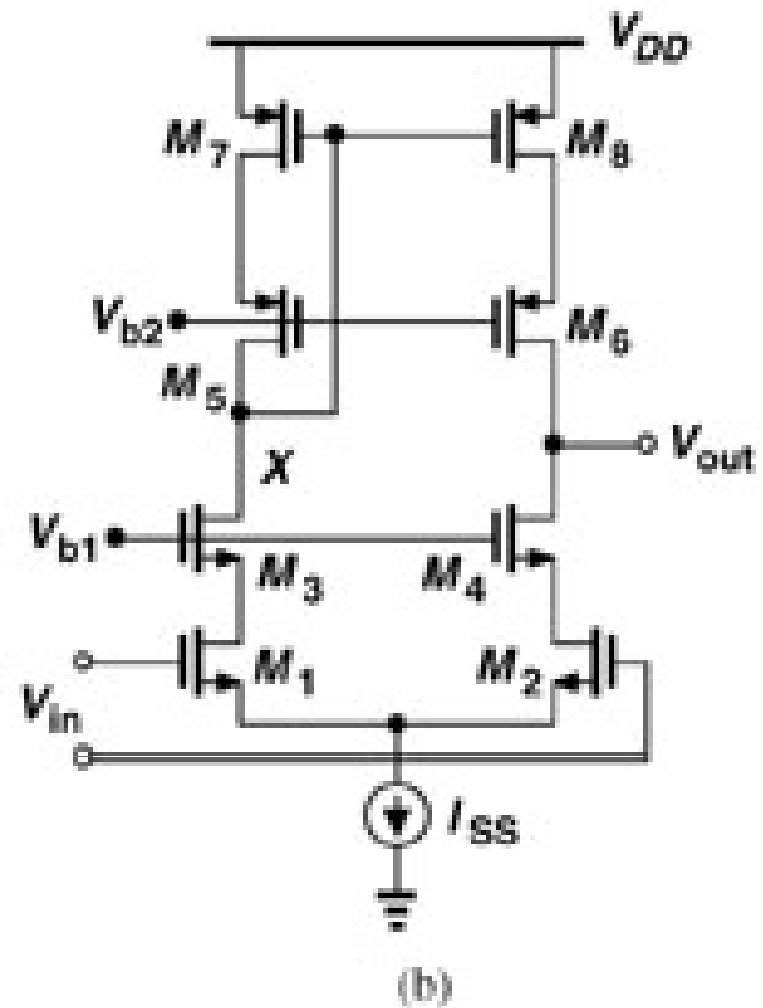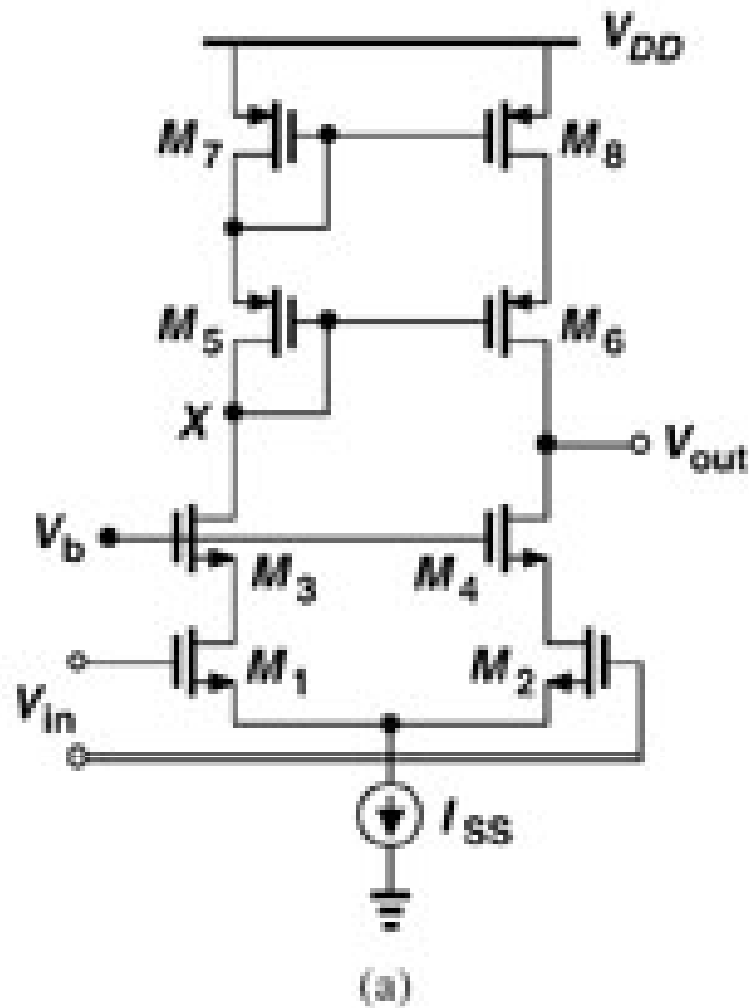


Triple Cascode

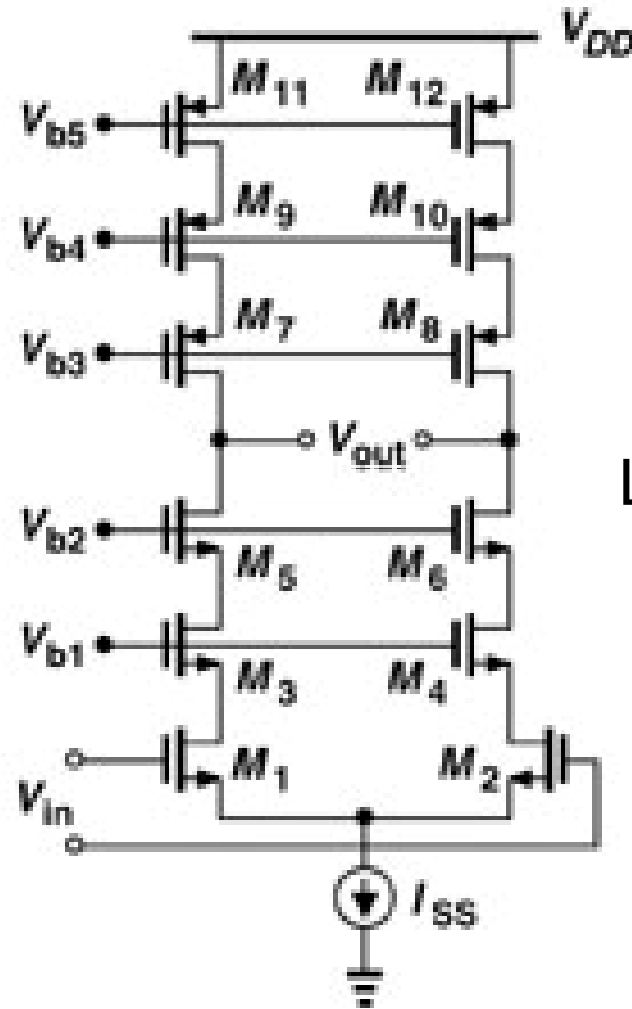


A_v app. $(g_m r_o)^{3/2}$
Limited Output Swing
Complex biasing

Two-Stage Op Amps

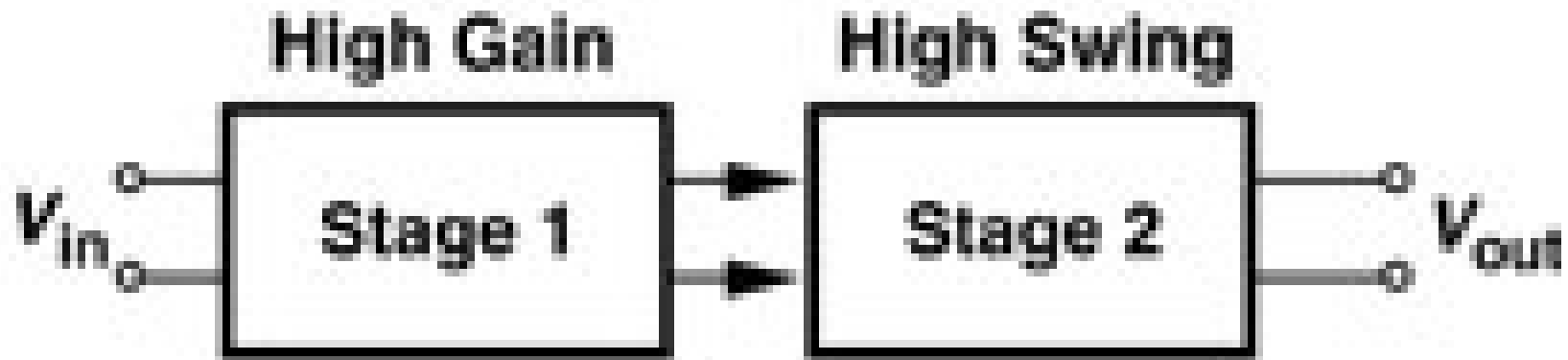


Design Approach for Two-Stage Op Amps


Single-Ended Output Two-Stage Op Amp

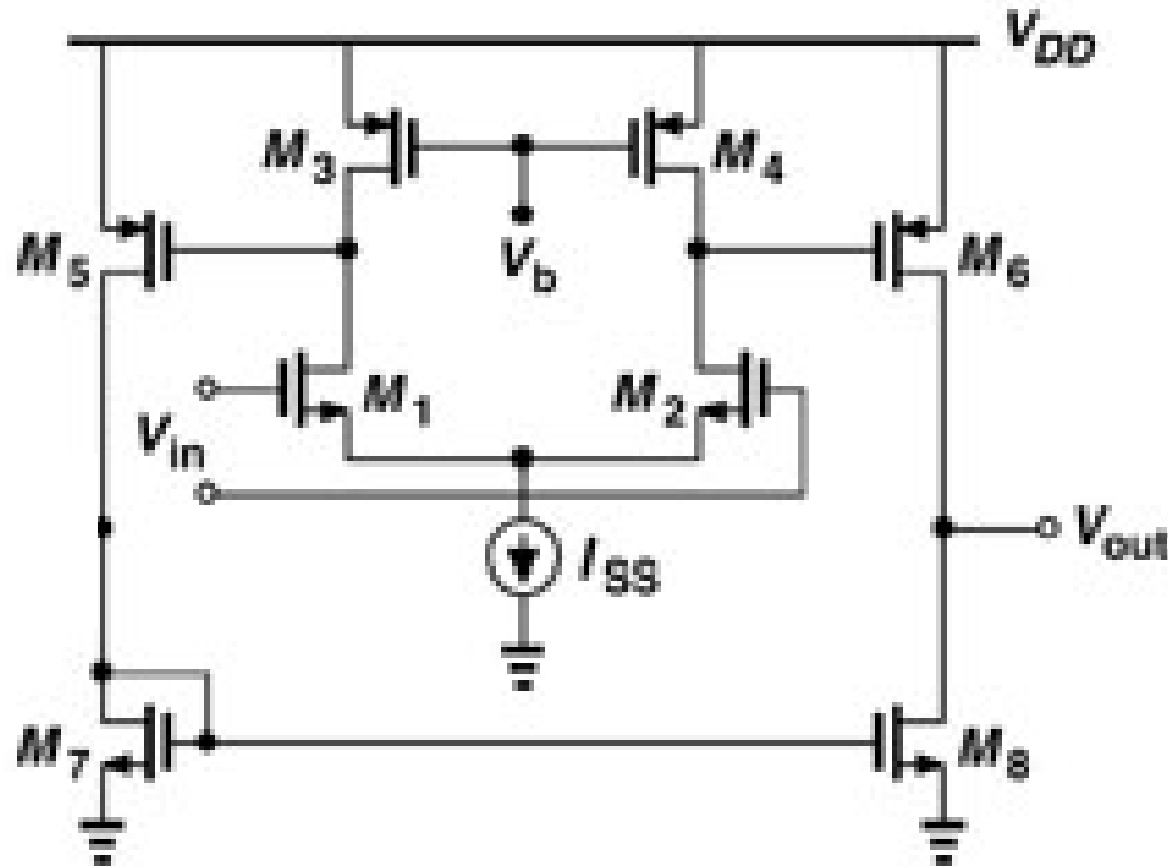

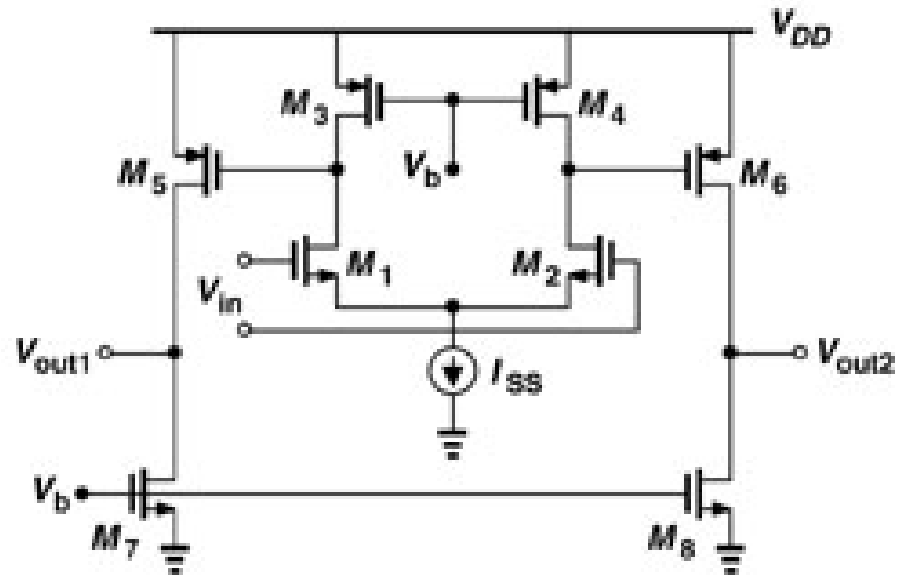
Simple Implementation of a Two-Stage Op-Amp




Two-Stage Op-Amp employing Cascading

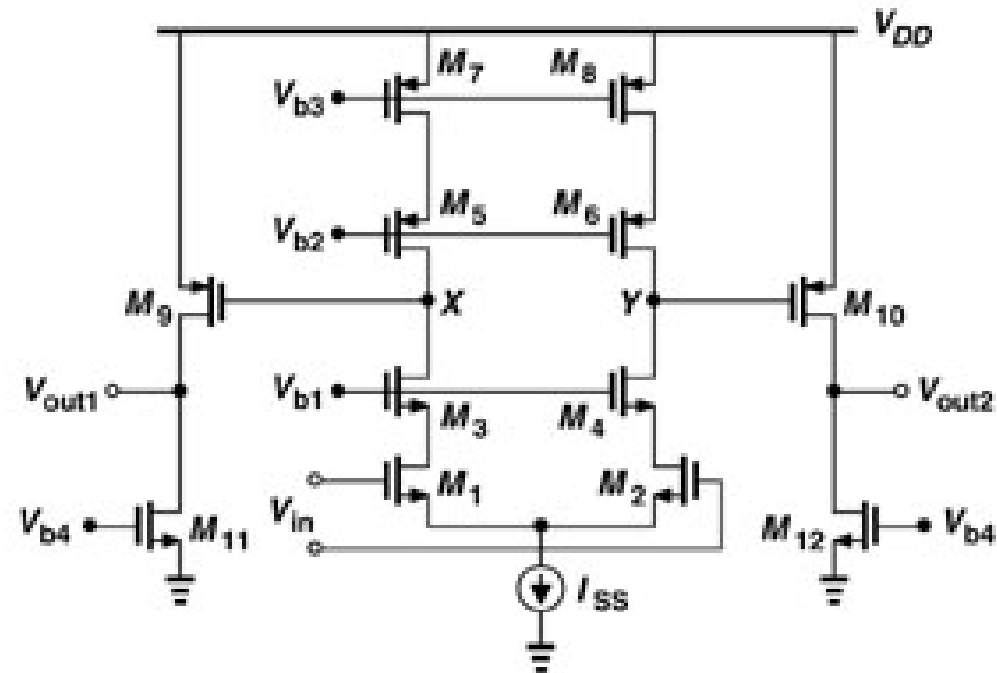

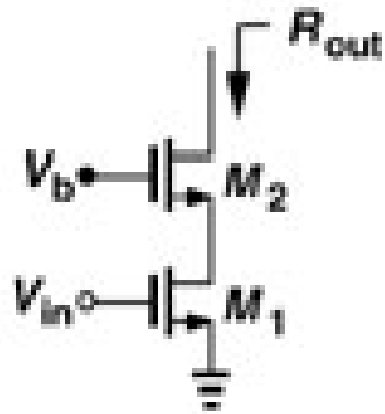
Output Impedance Enhancement With Feedback



(a)

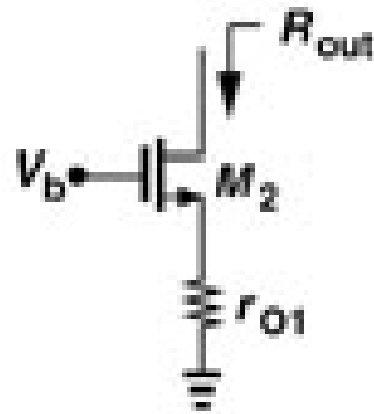


(b)

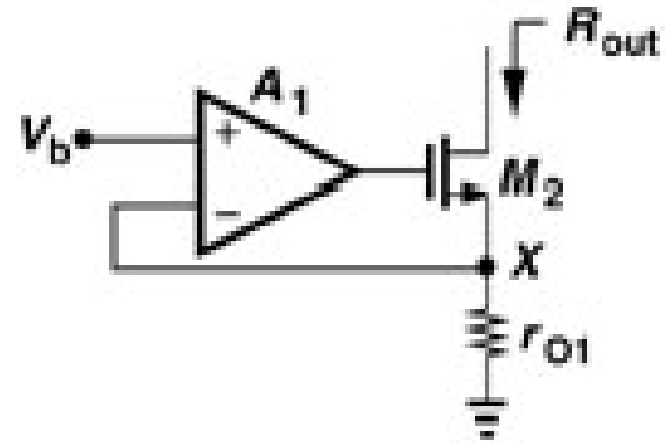


(c)

$$R_{out} = A_1 g_{m2} r_{o2} r_{o1}$$


Gain Boosting in Cascode Stage

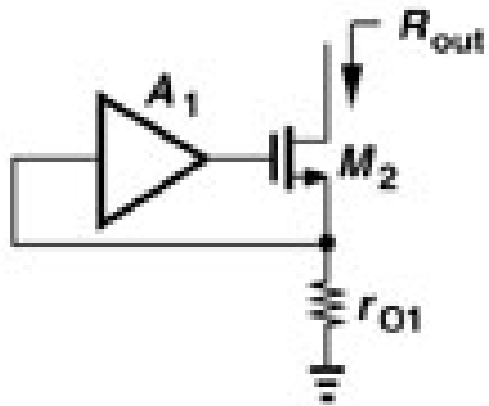

(a)

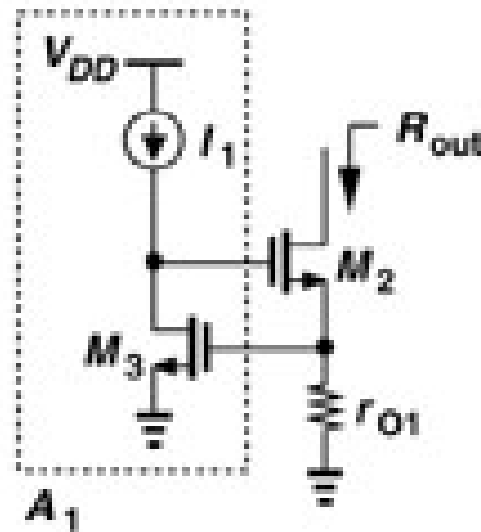


(b)

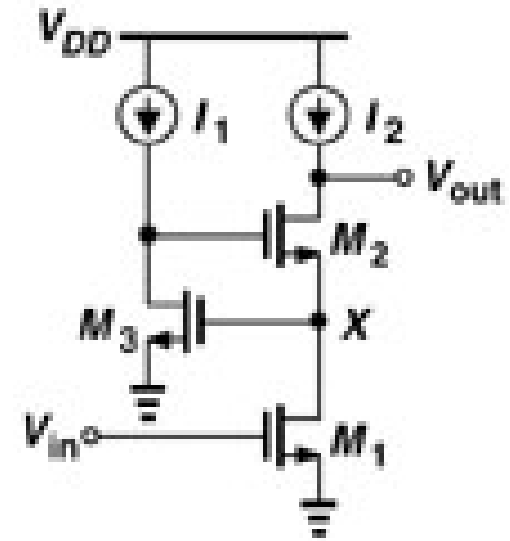


(c)

Differential Gain Boosting

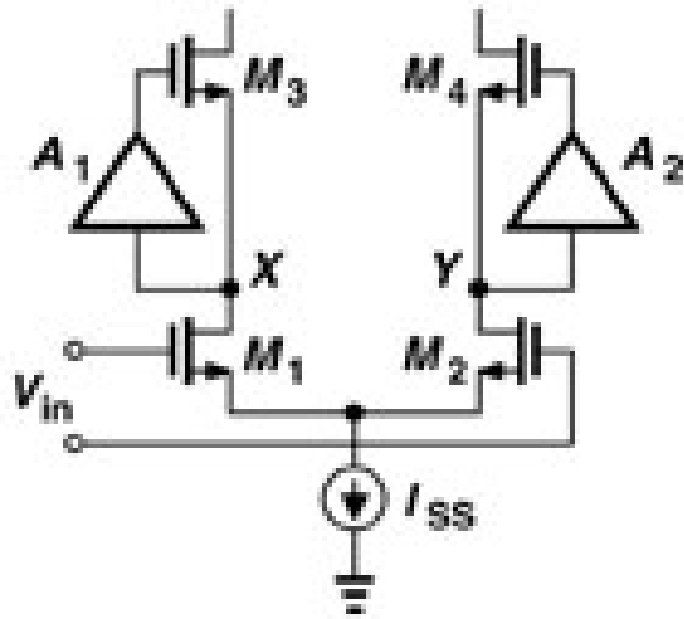


(a)

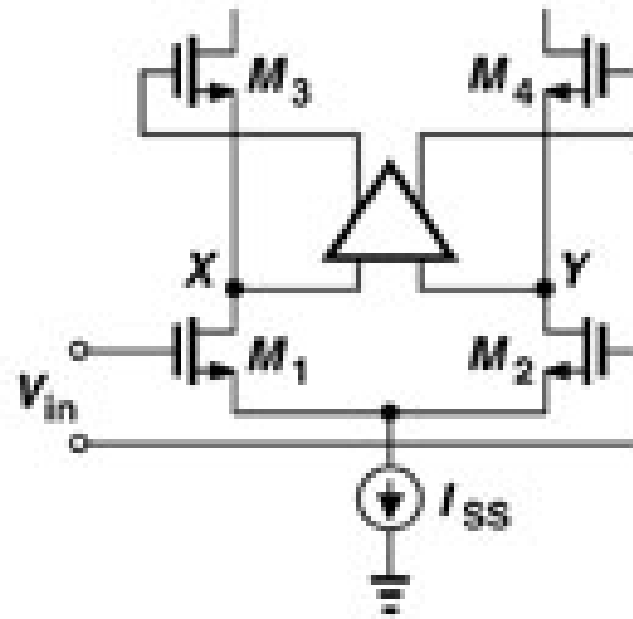


(b)

Differential Gain Boosting (cont.)

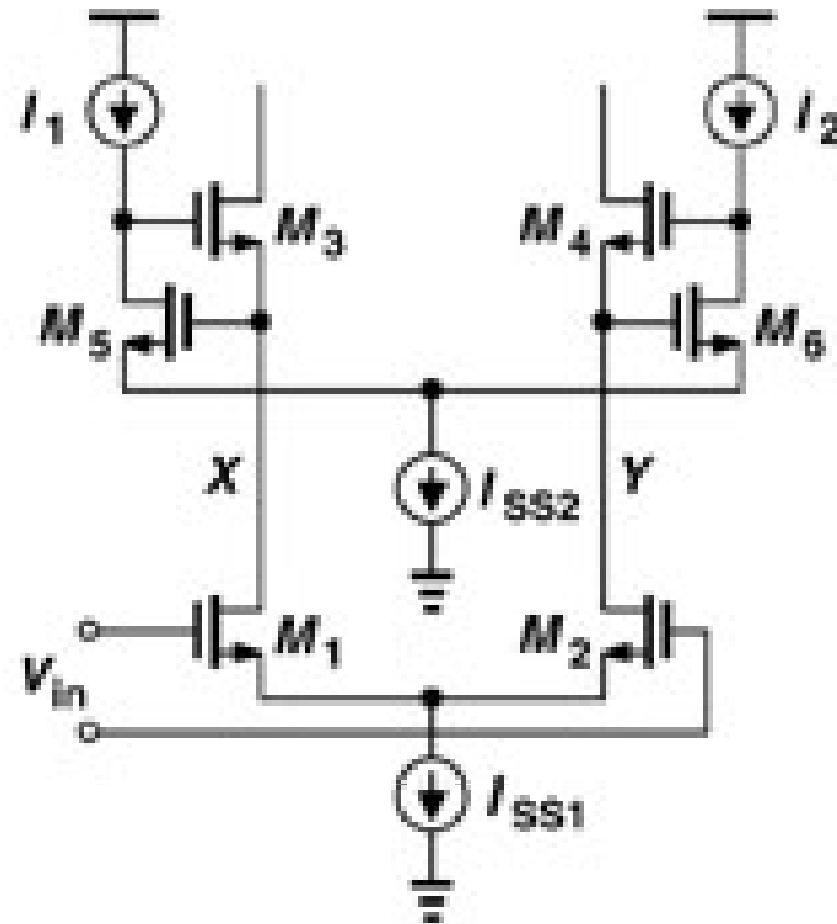





Differential Gain Boosting (cont.)

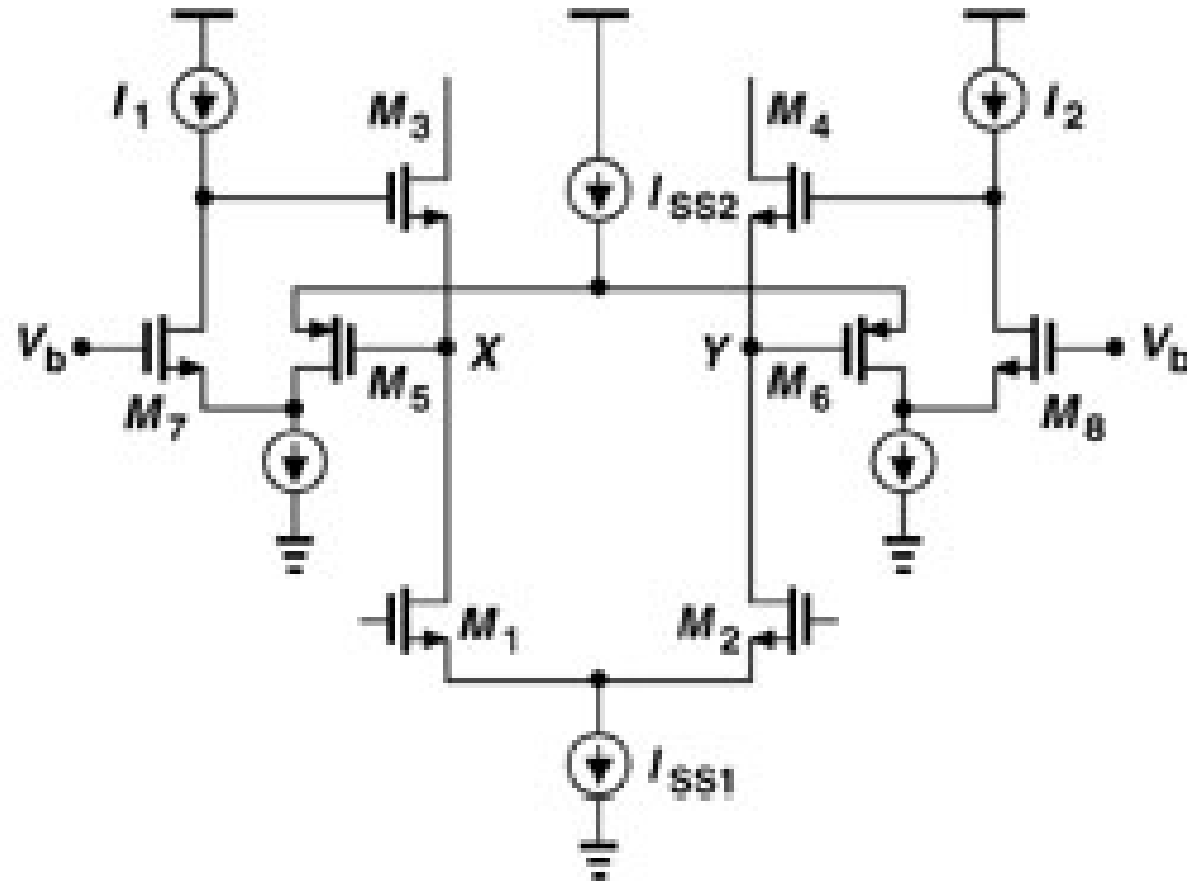


Comparison

	Gain	Output Swing	Speed	Power Dissipation	Noise
Telescopic	Medium	Medium	Highest	Low	Low
Folded-Cascode	Medium	Medium	High	Medium	Medium
Two-Stage	High	Highest	Low	Medium	Low
Gain-Boosted	High	Medium	Medium	High	Medium


Common-Mode Feedback

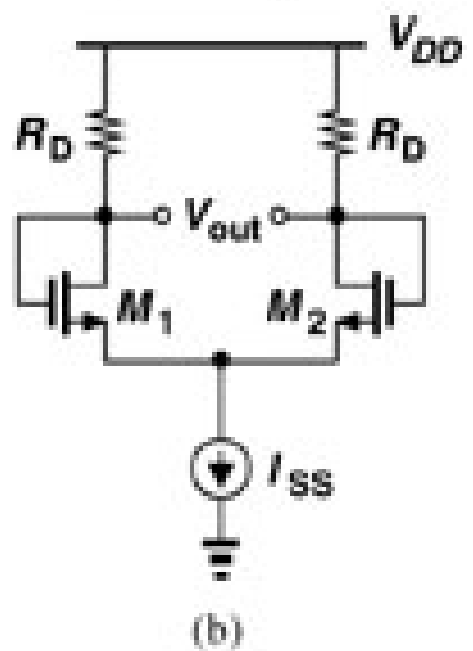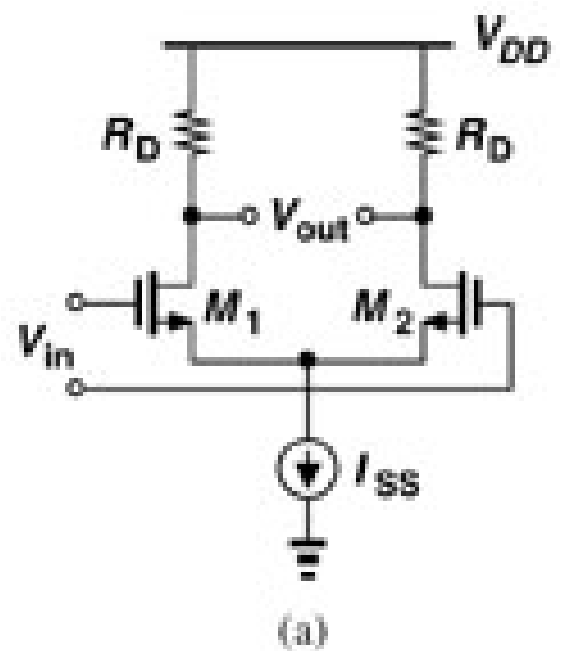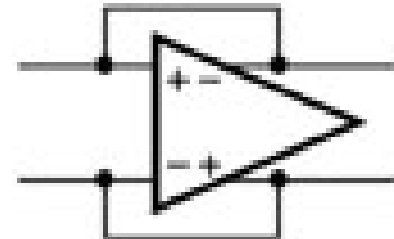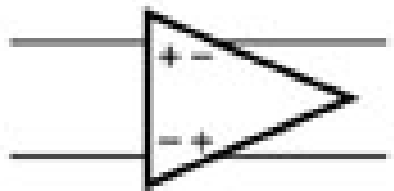

Common-Mode Feedback (cont.)

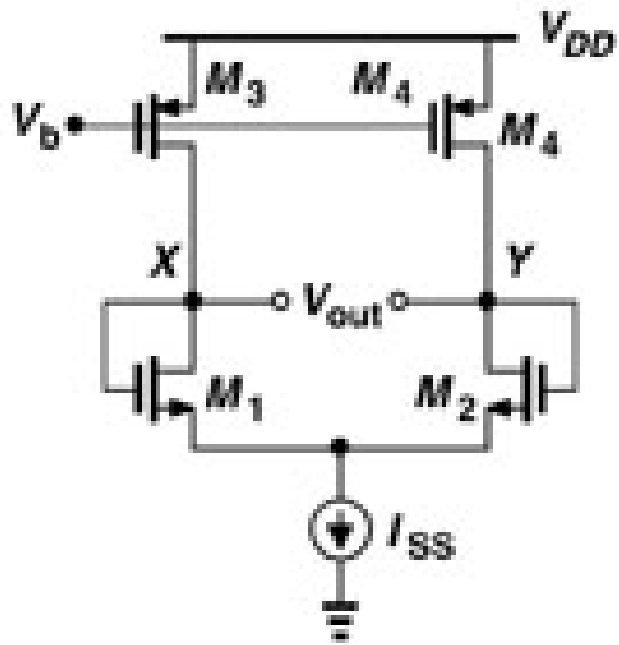


(a)

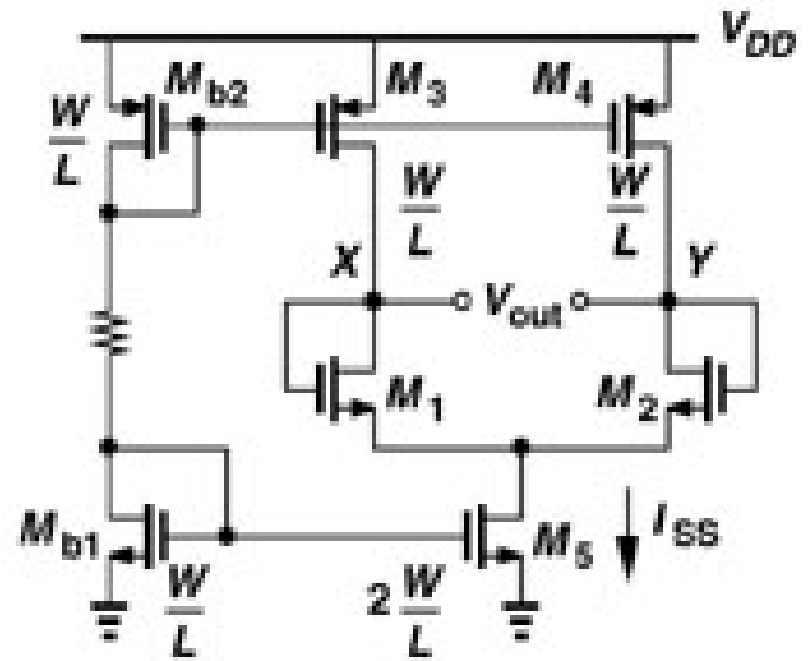


(b)


High Gain Amp Model

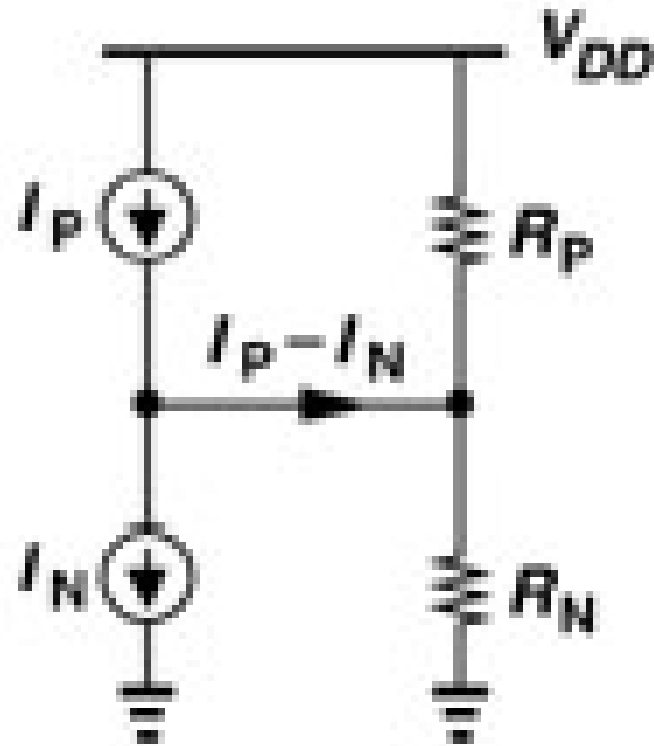


Common-Mode Feedback (cont.)

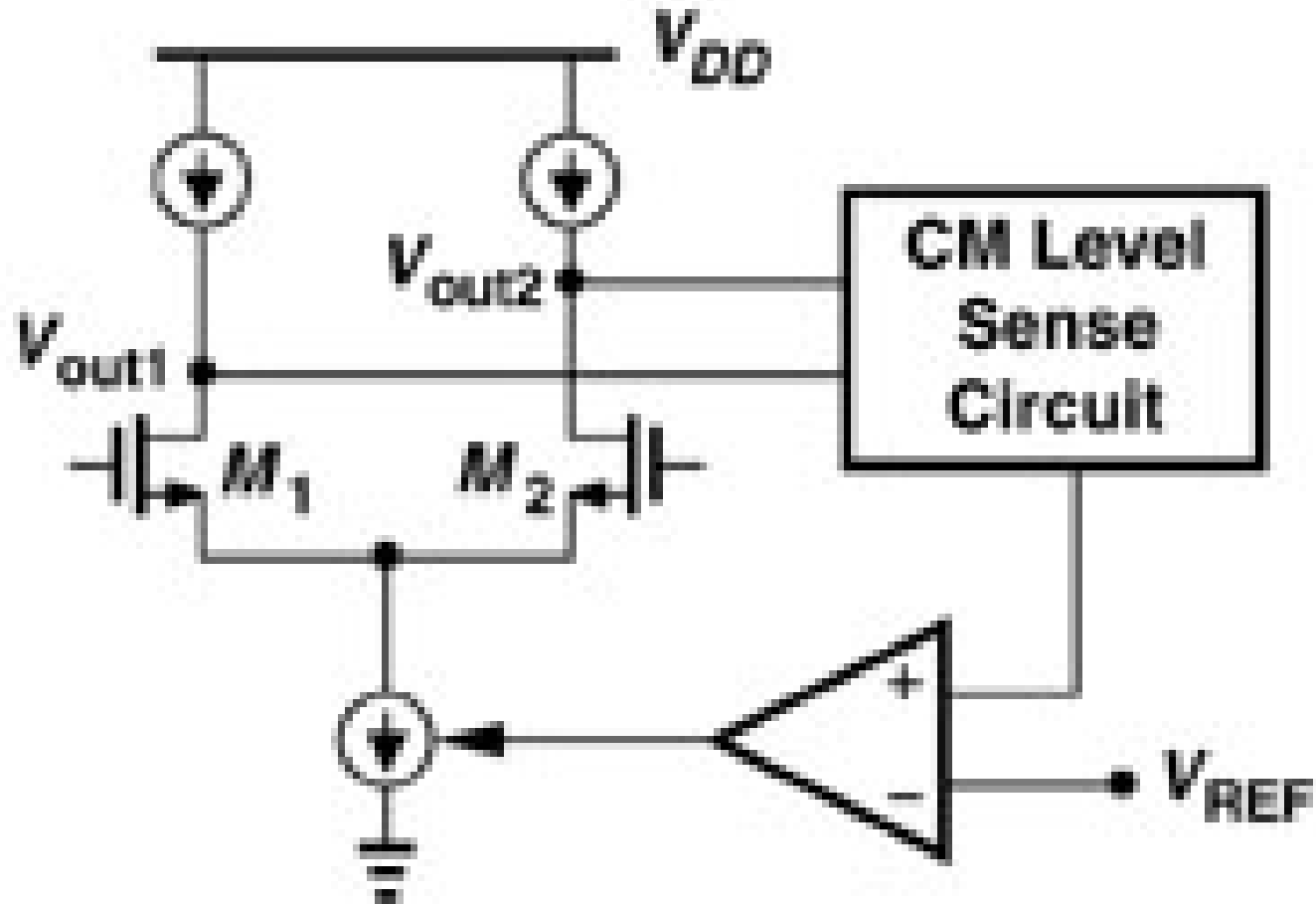


Resistive Sensing

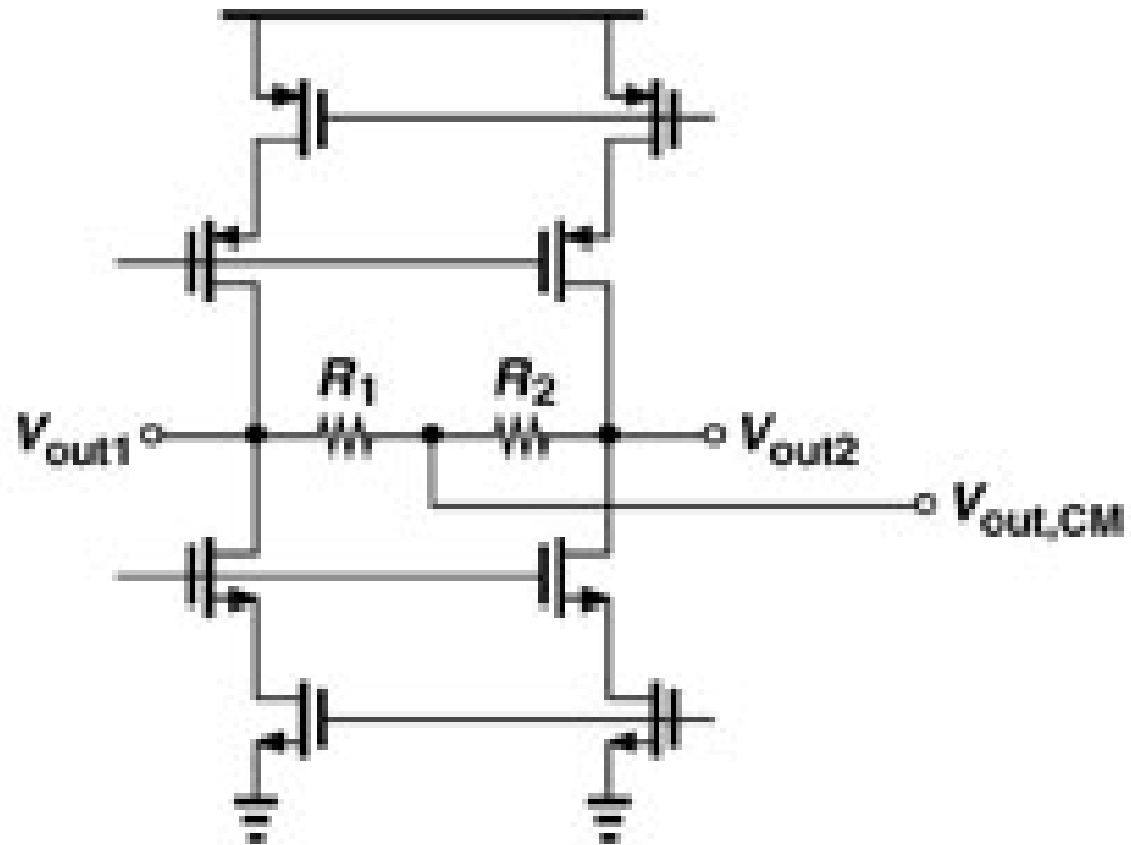


Source-Follower Buffering

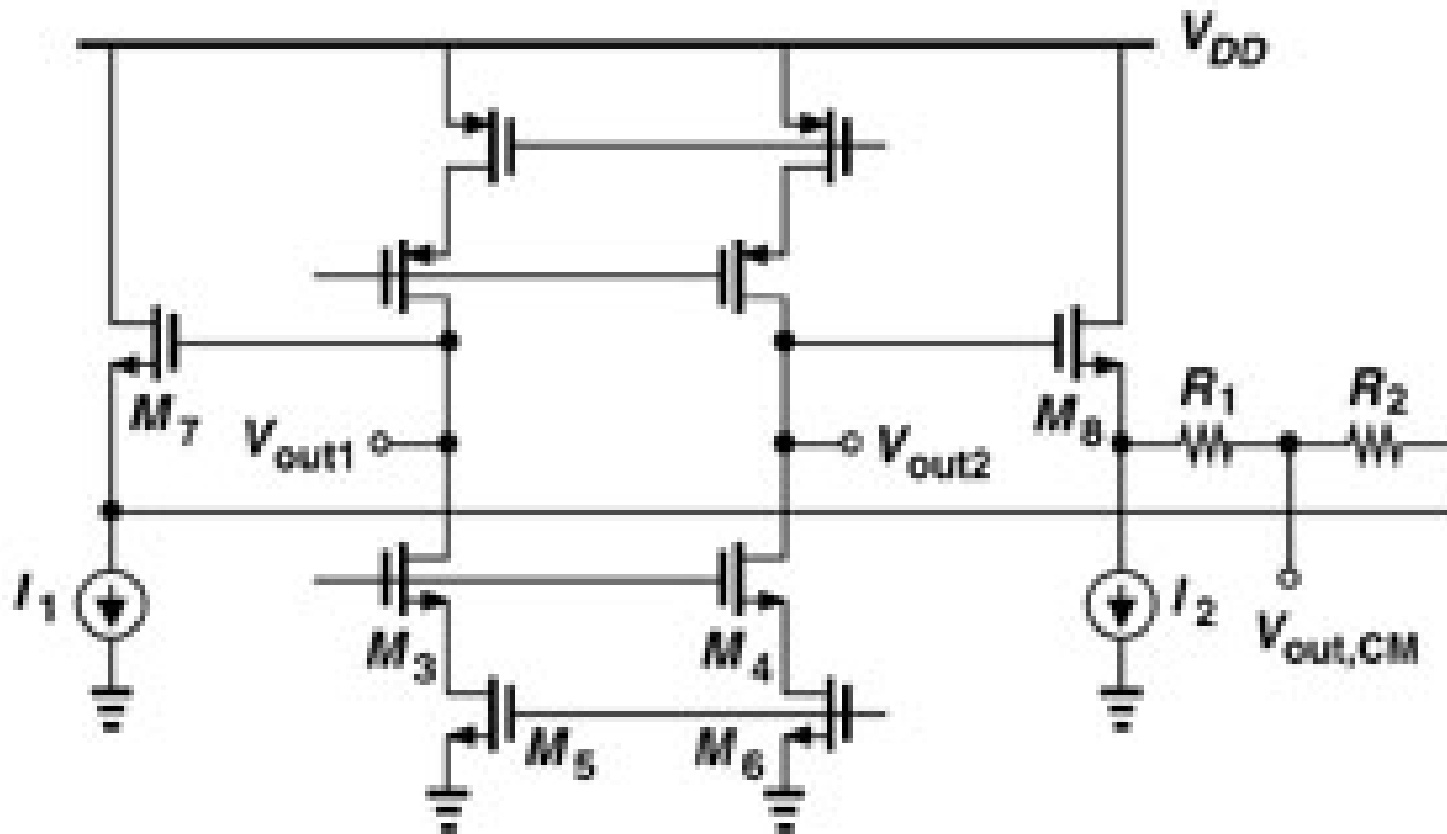


Deep Triode FET CM Sensing

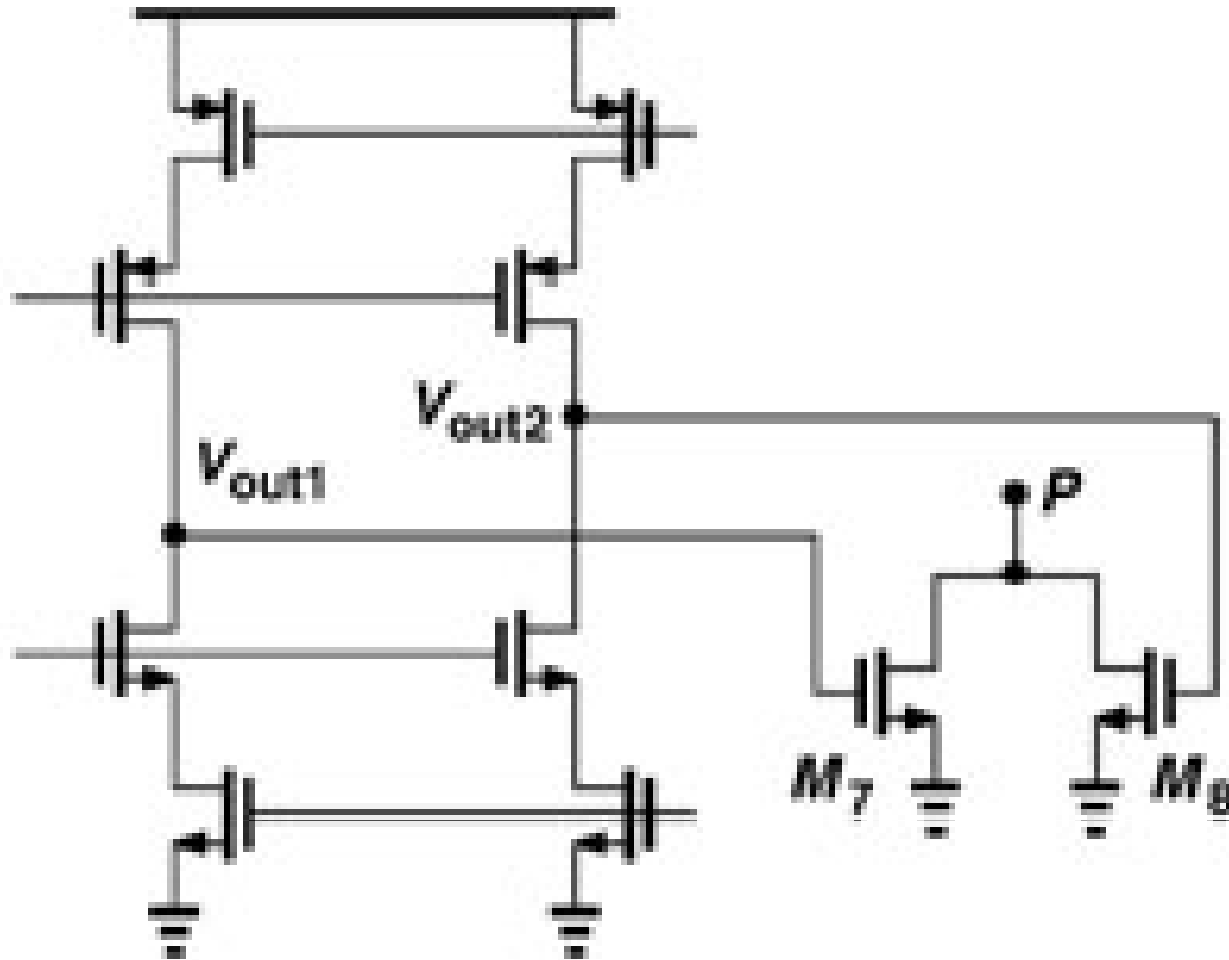


CMFB Example

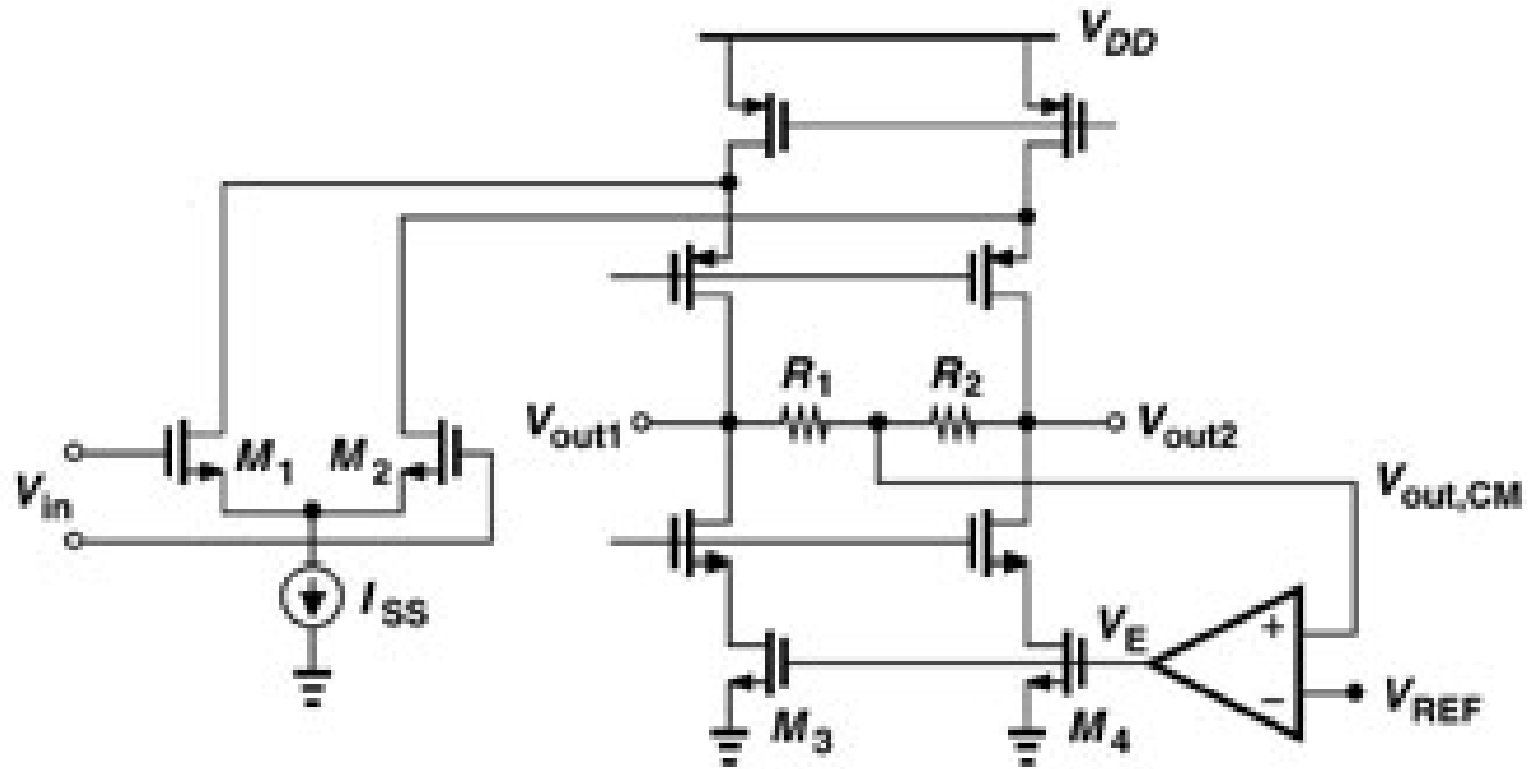


Alternative CMFB for Folded Cascode

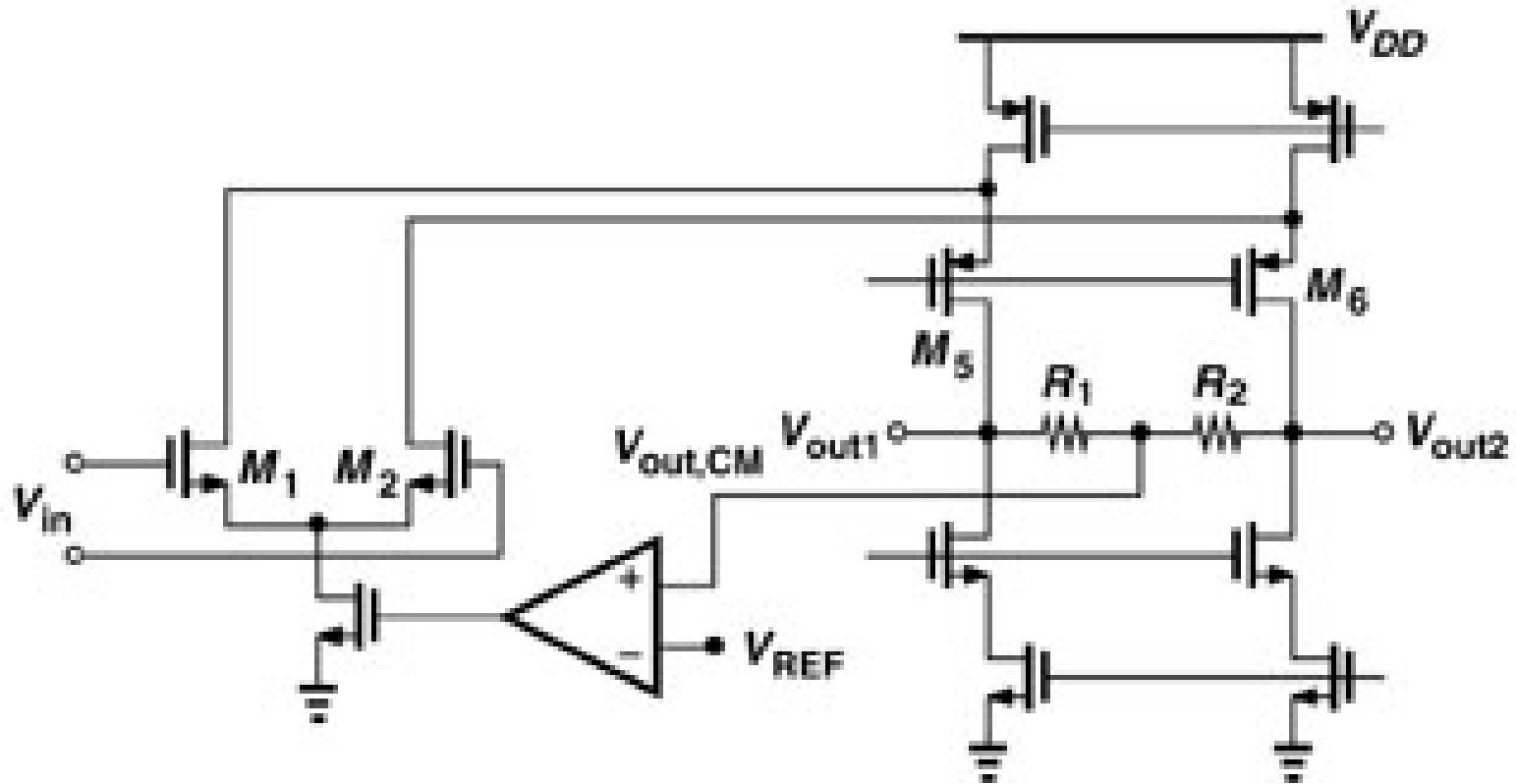


Simplified CMFB with Triode Devices

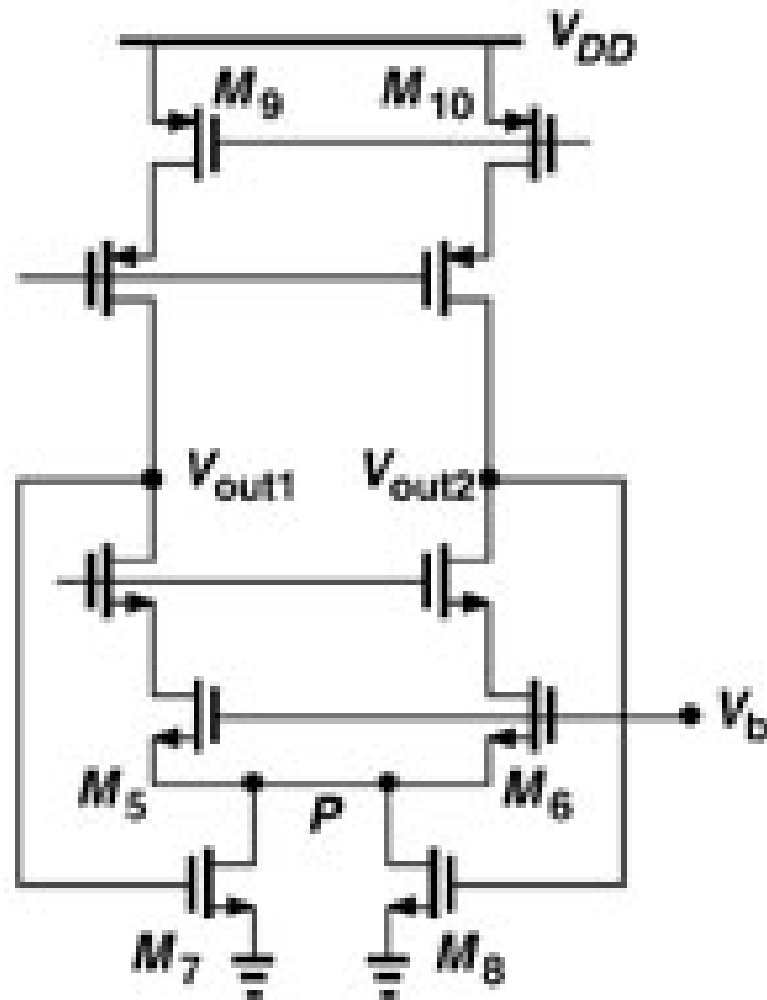


CMFB Triode Example with Reference

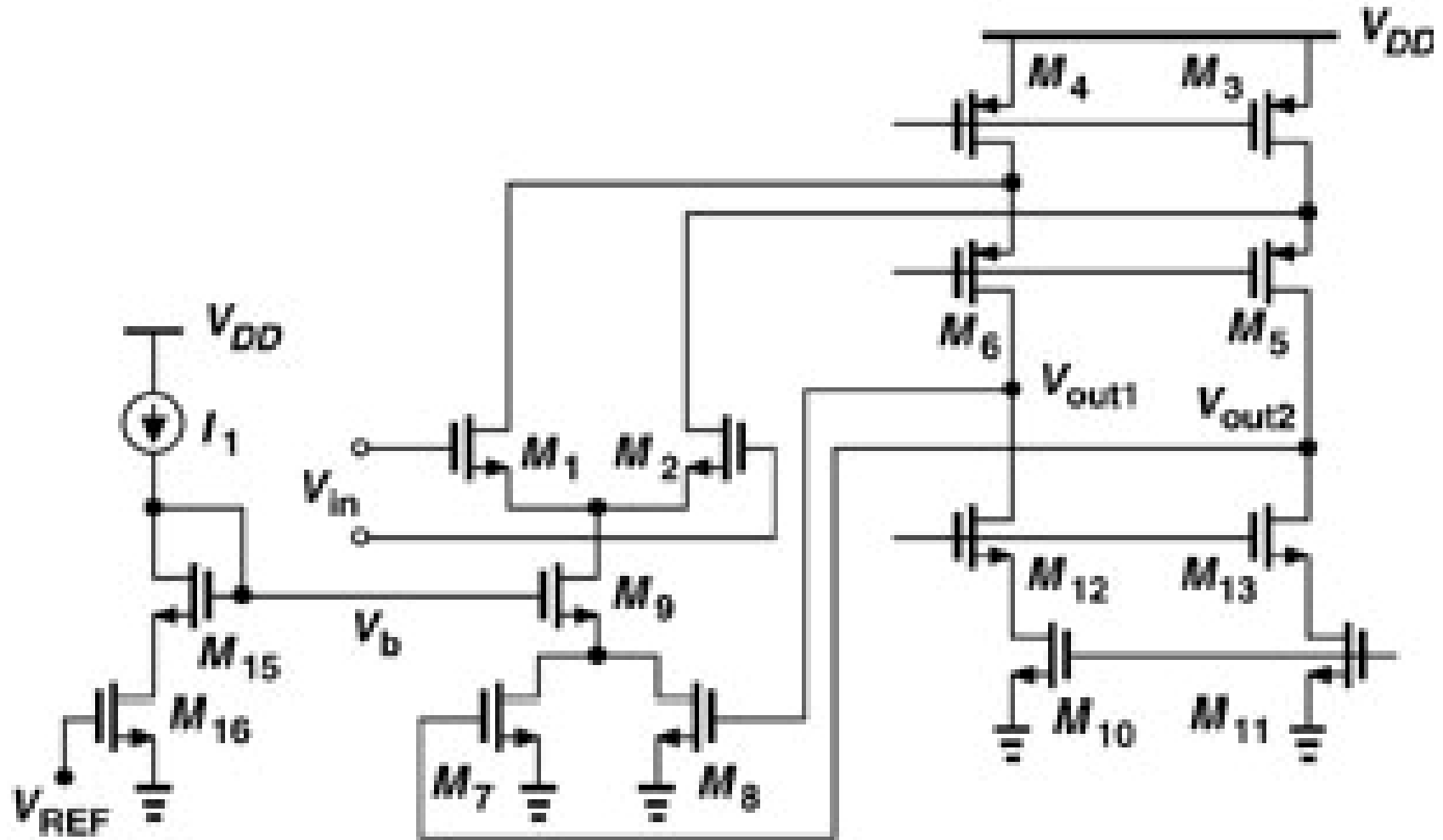

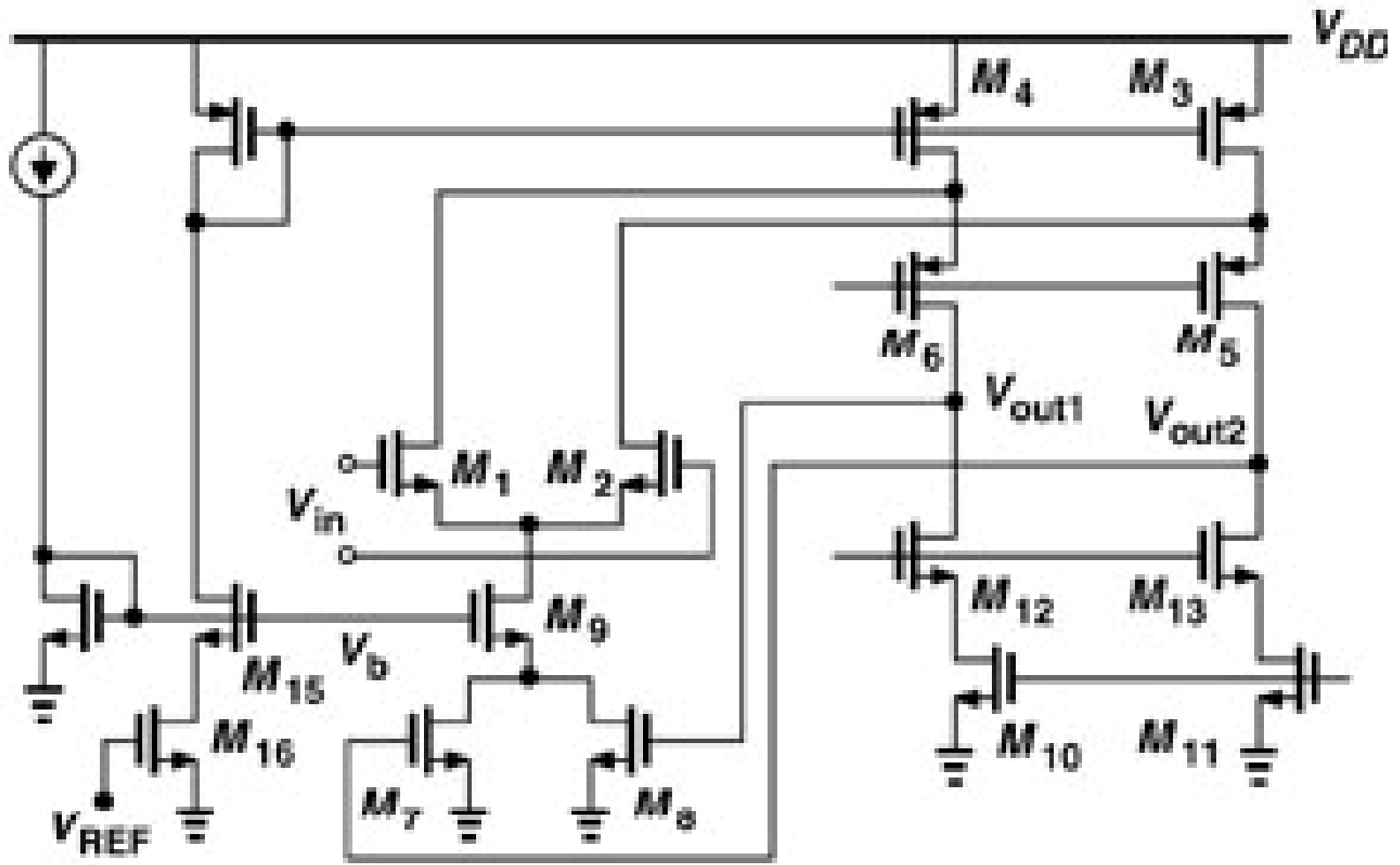
CMFB Triode Example with Reference (cont.)



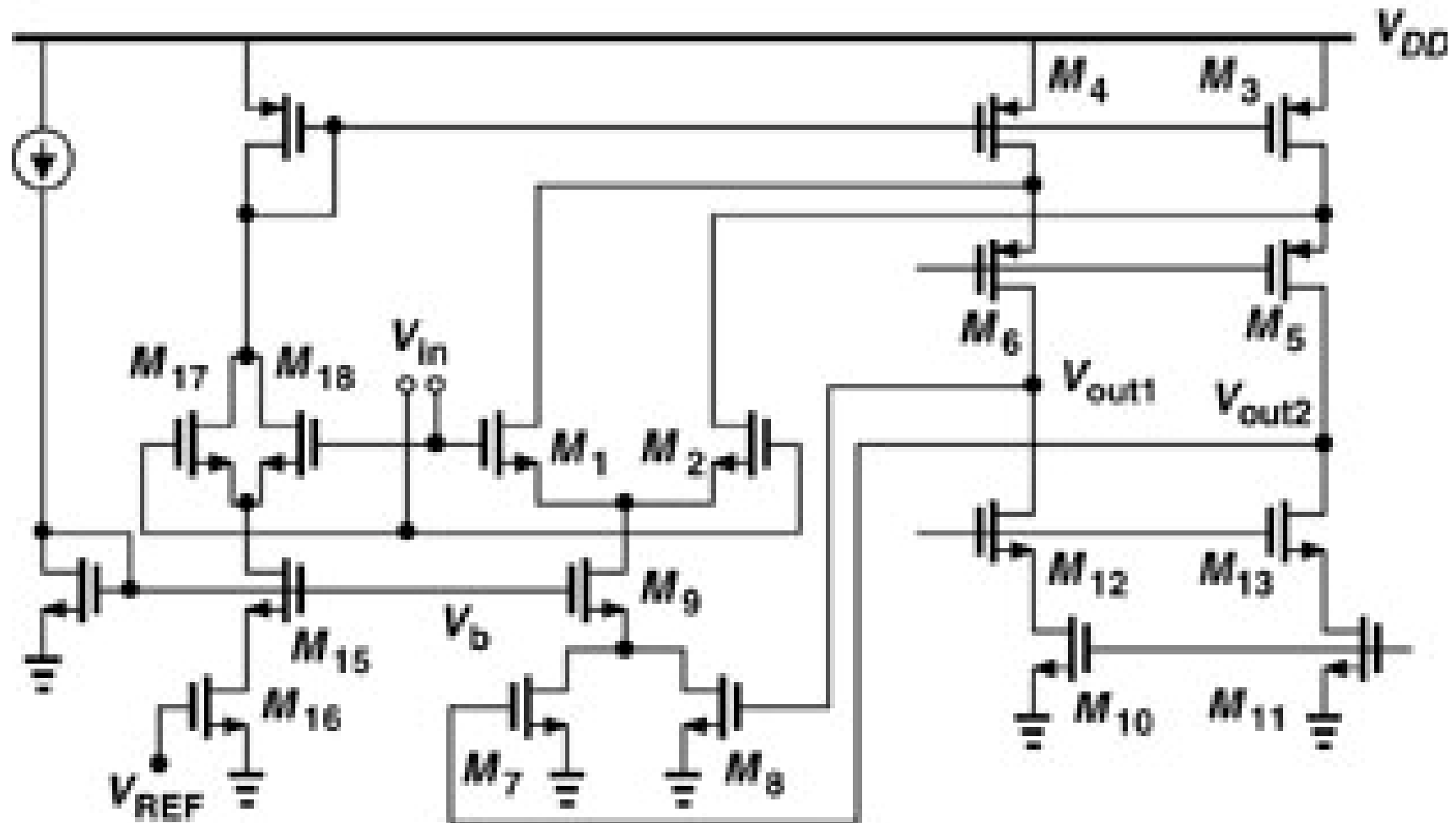CMFB Triode Example with Reference (cont.)





Input Range Limitations

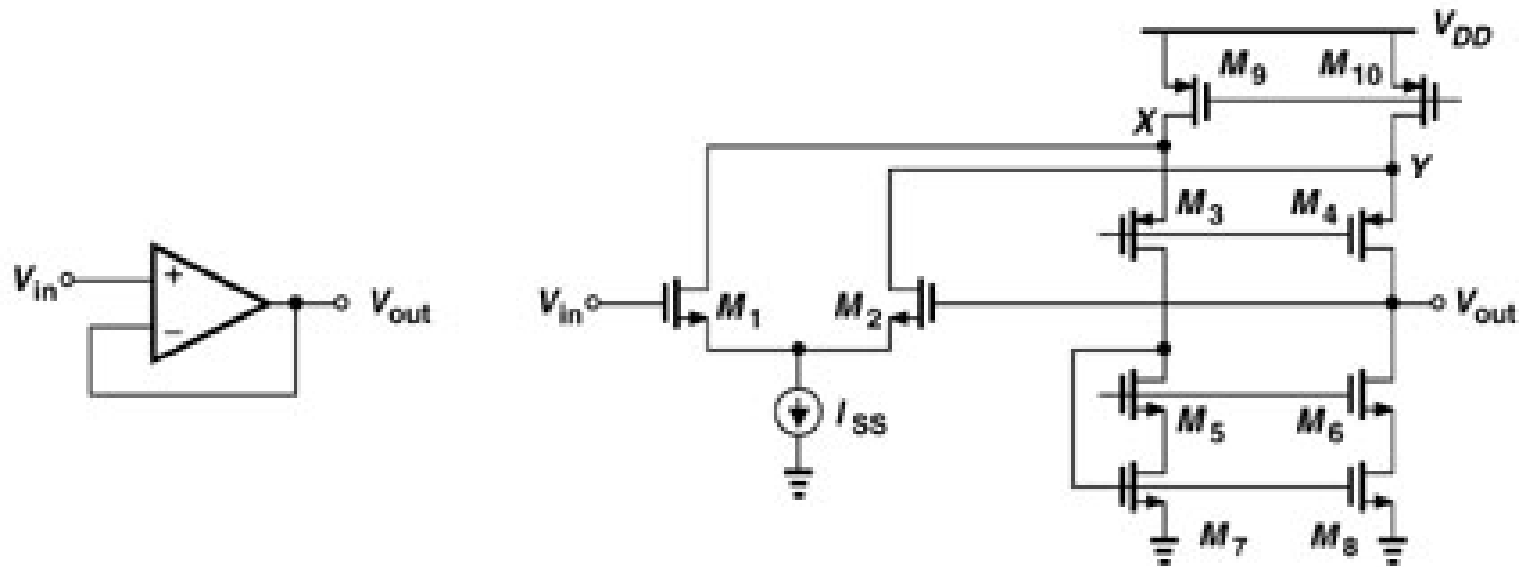



Unity-Gain Buffer

Extension of Input CM Range

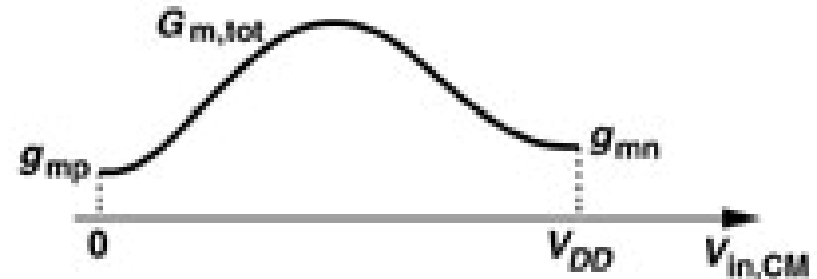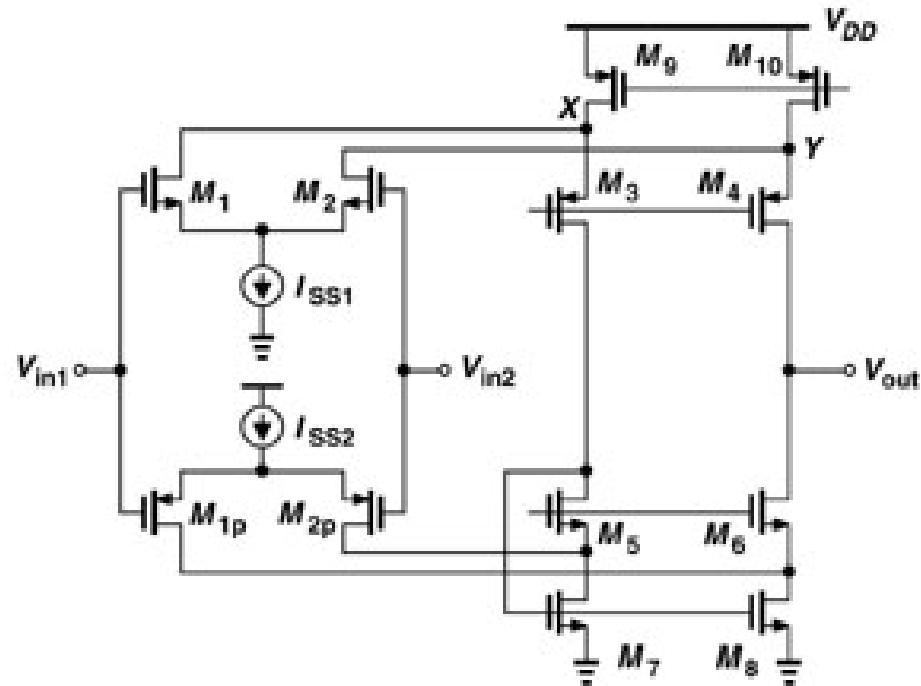



Variation of equivalent transconductance with the input CM level

Slew Rate

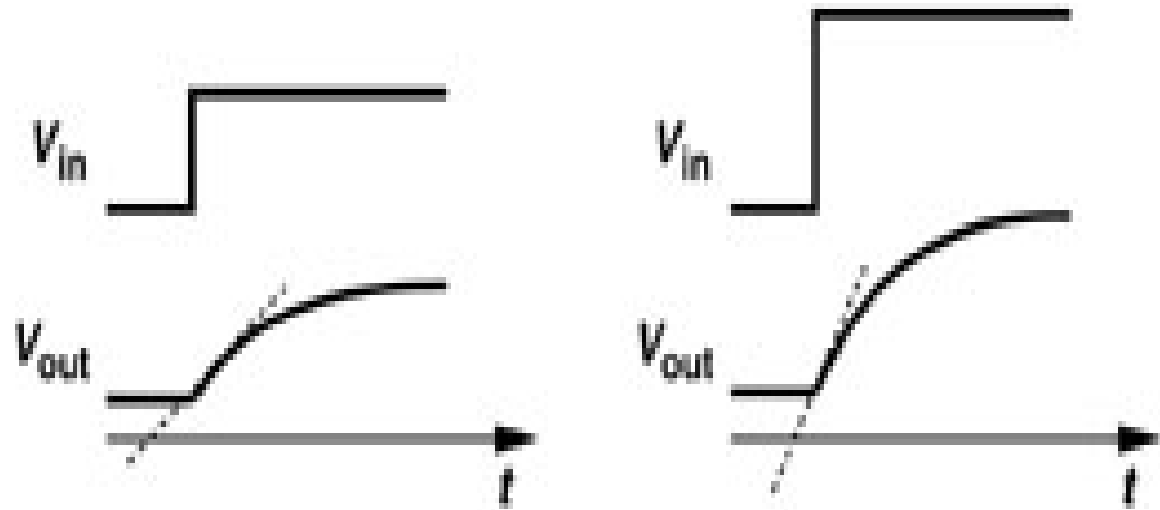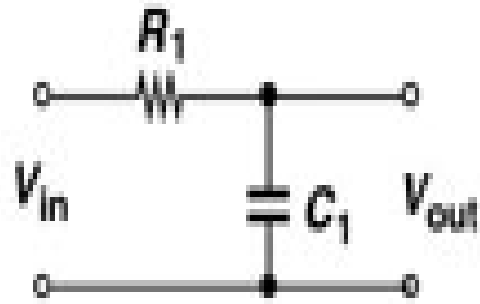


Linear RC Step Response


Slewing in Op Amp

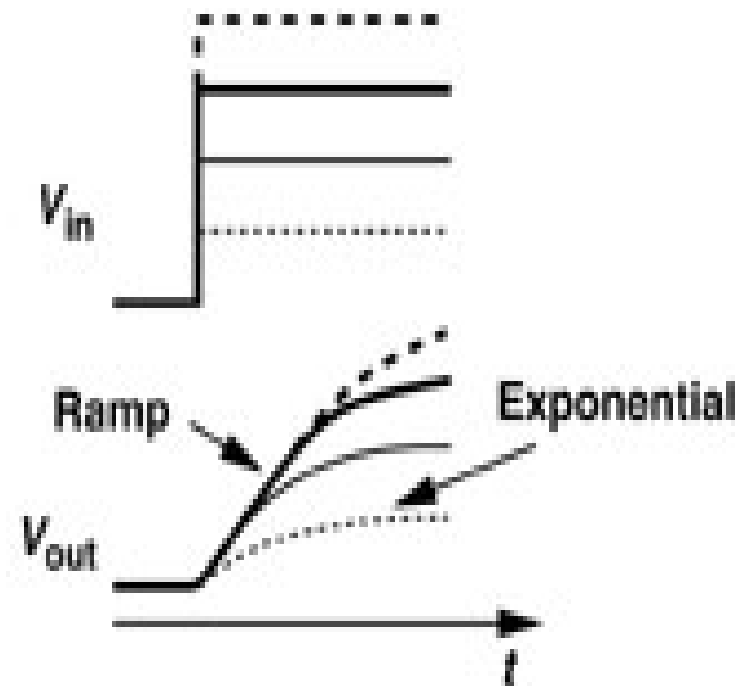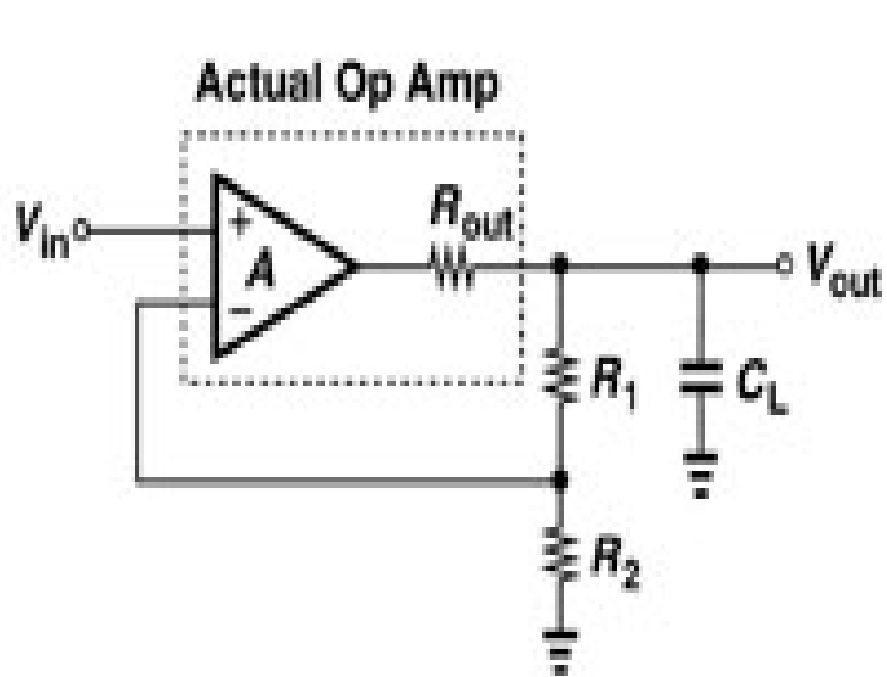

Small-Signal Operation of Op Amp

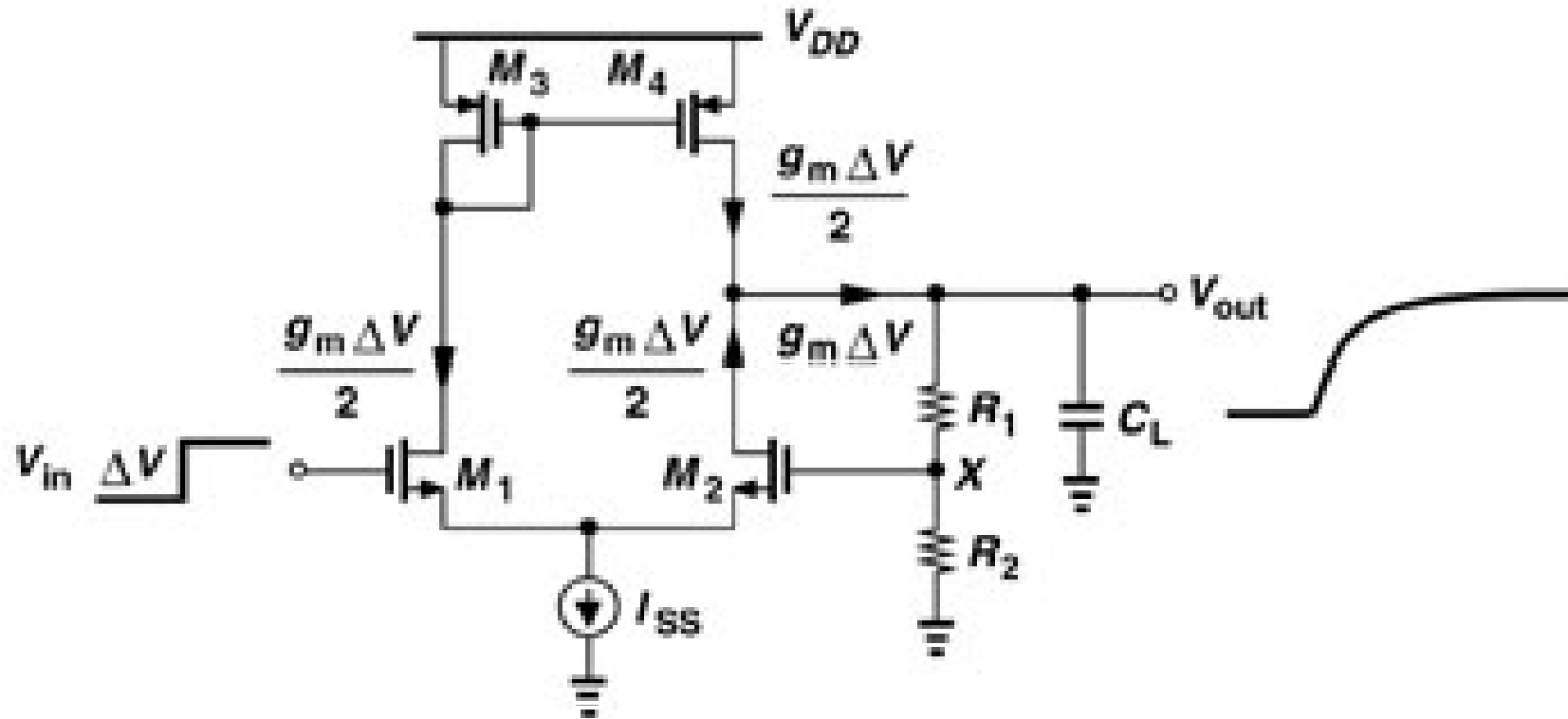


Op Amp Slewing

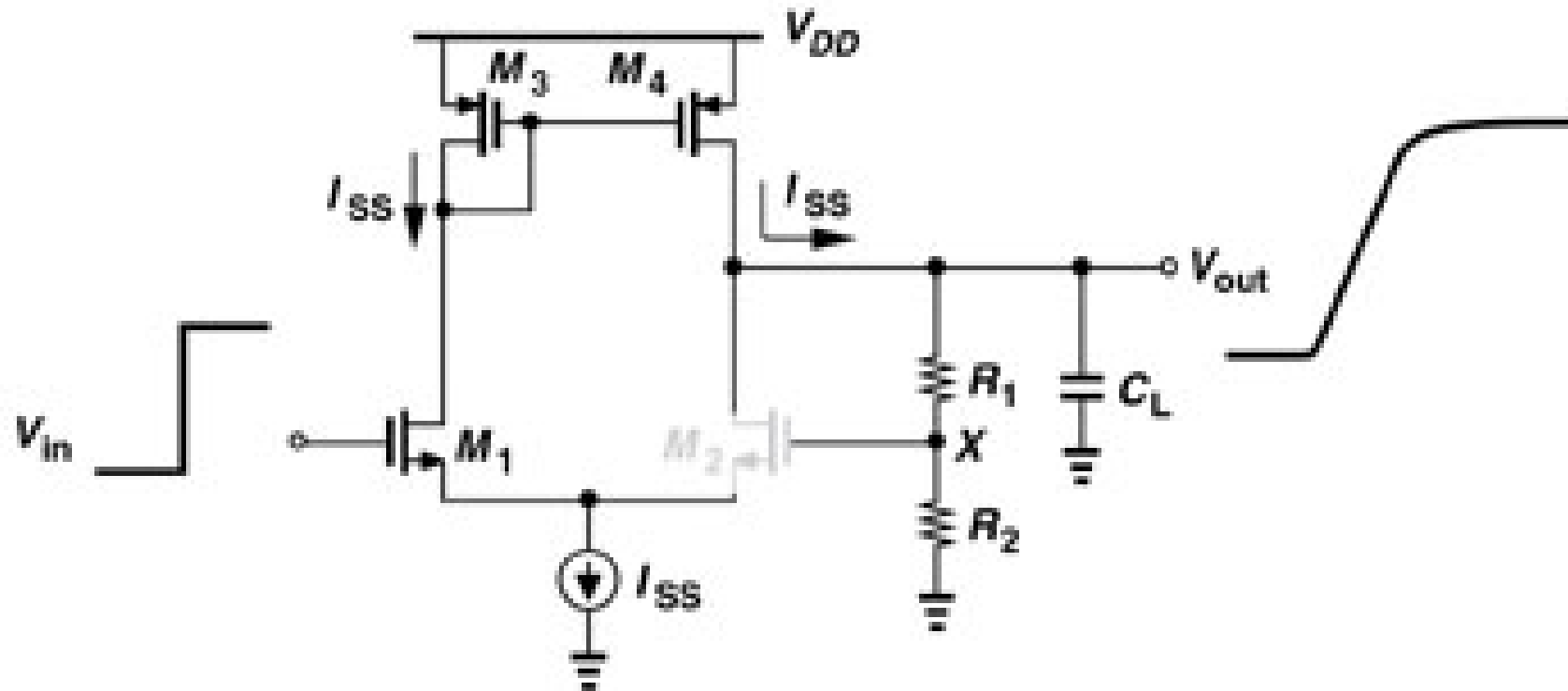


$$\text{Slew rate} = V/S = I/C$$


Op Amp Slewing (cont.)

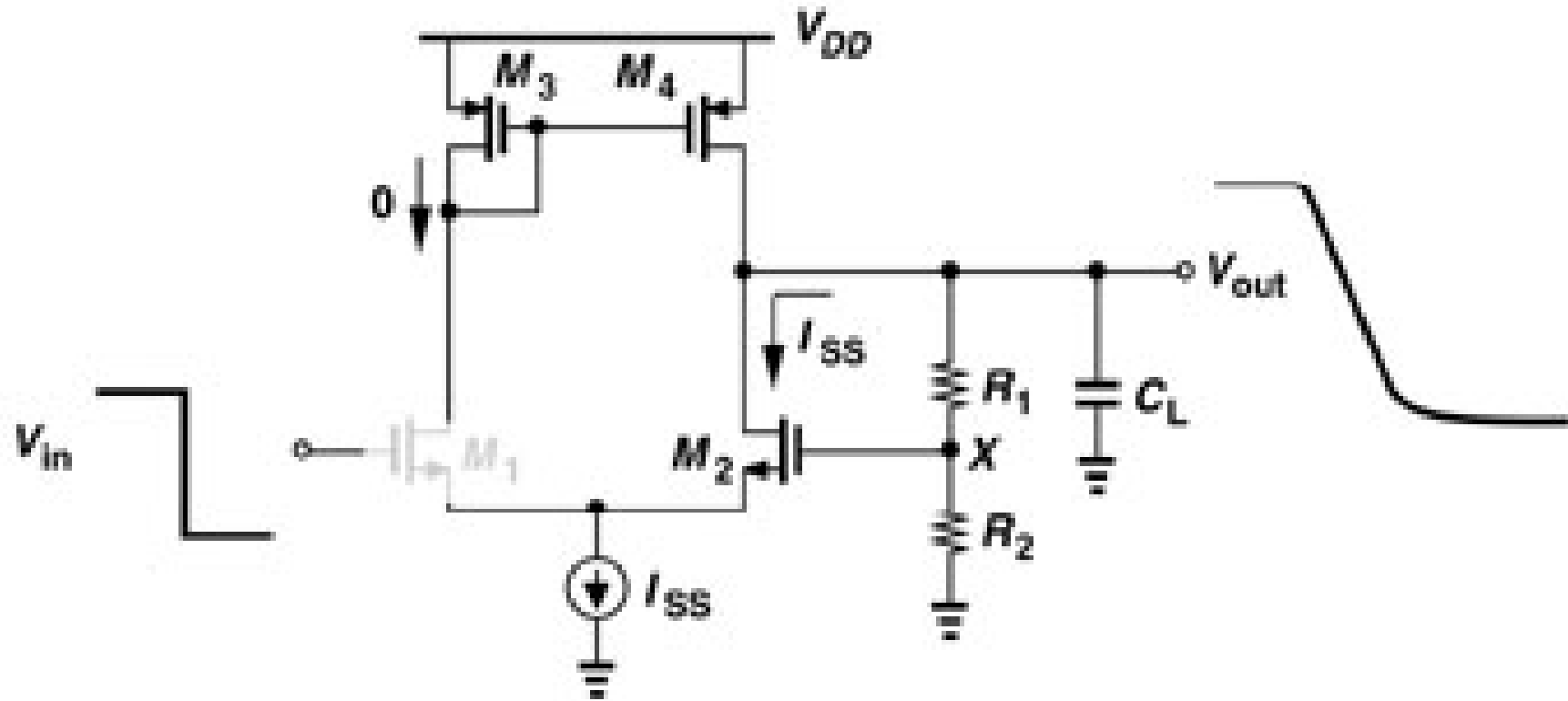

Slewing in Telescopic Op Amp

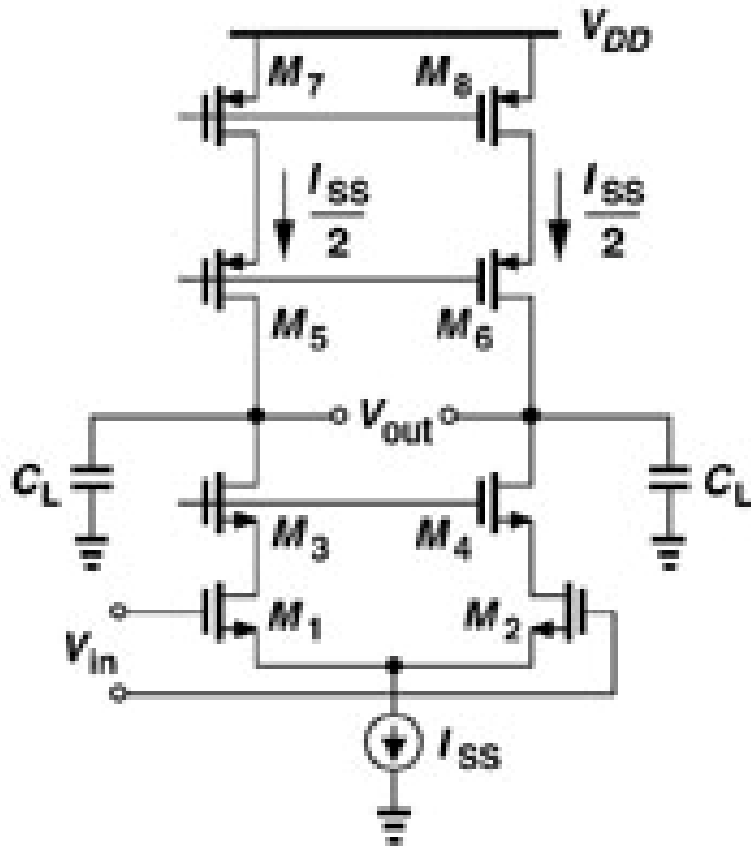


(a)

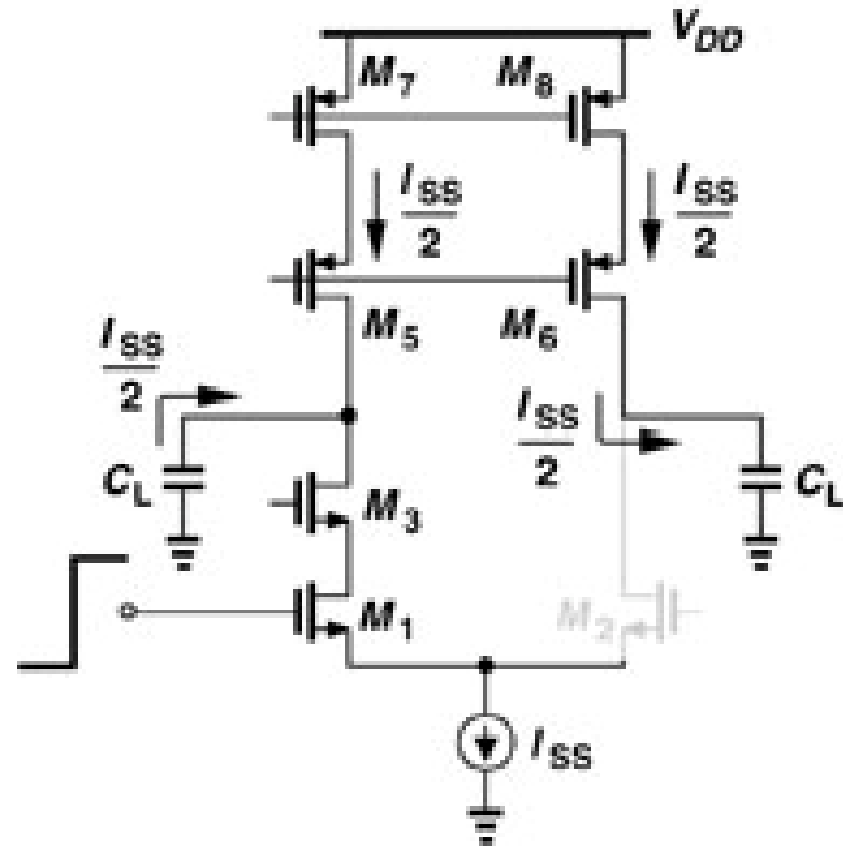


(b)


Folded-Cascode Slewing

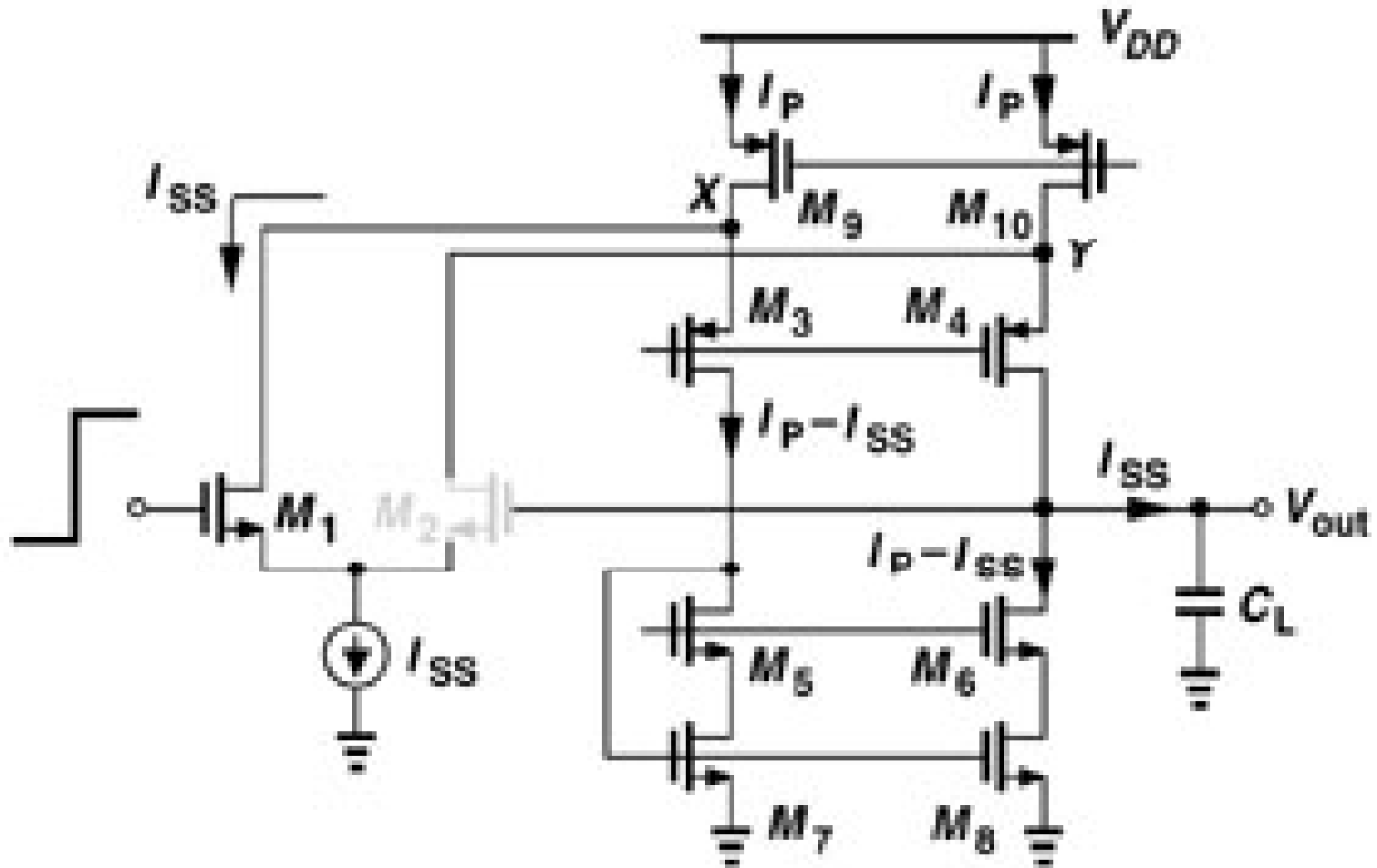


Folded-Cascode (cont.)

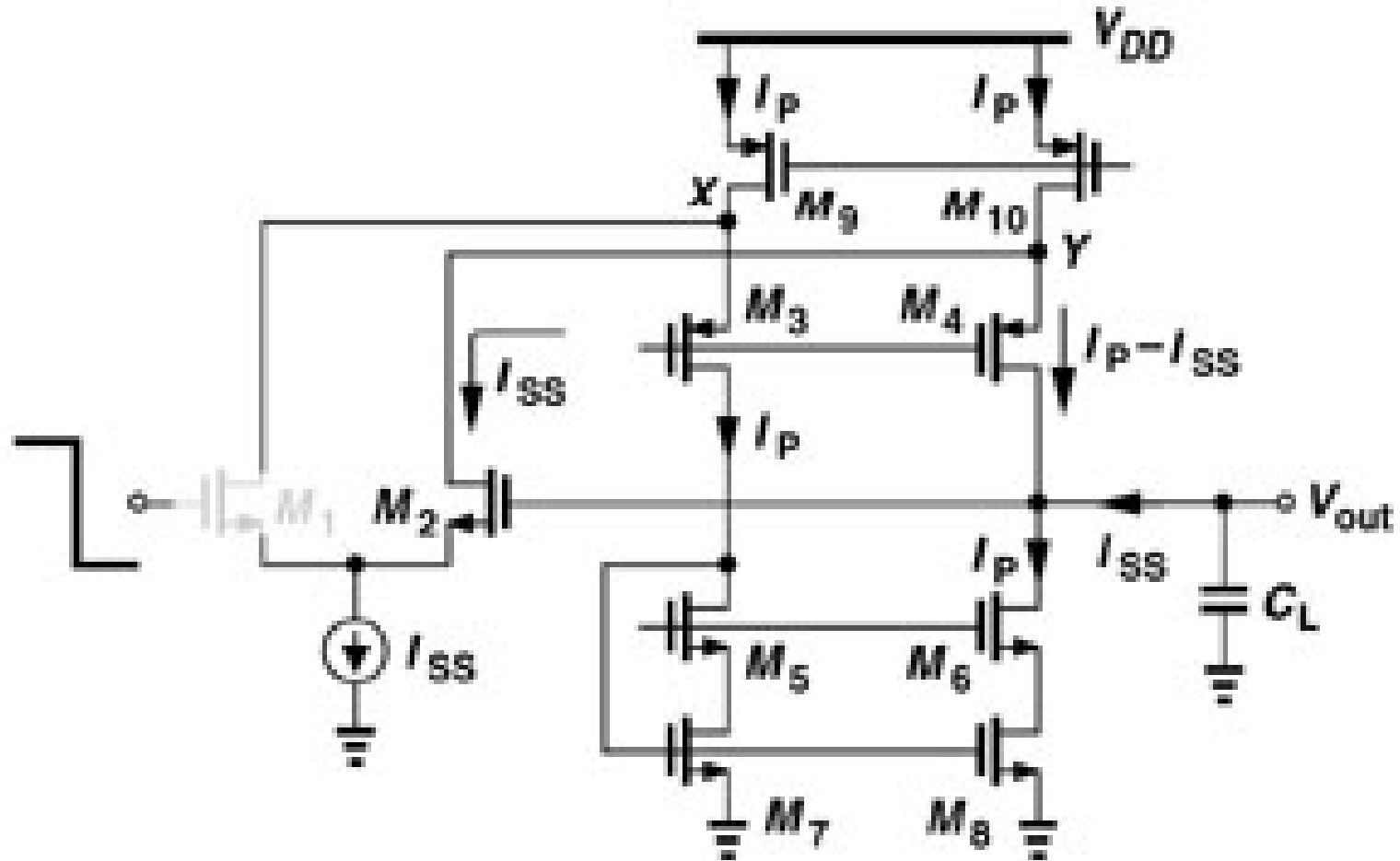


Slewing Recovery

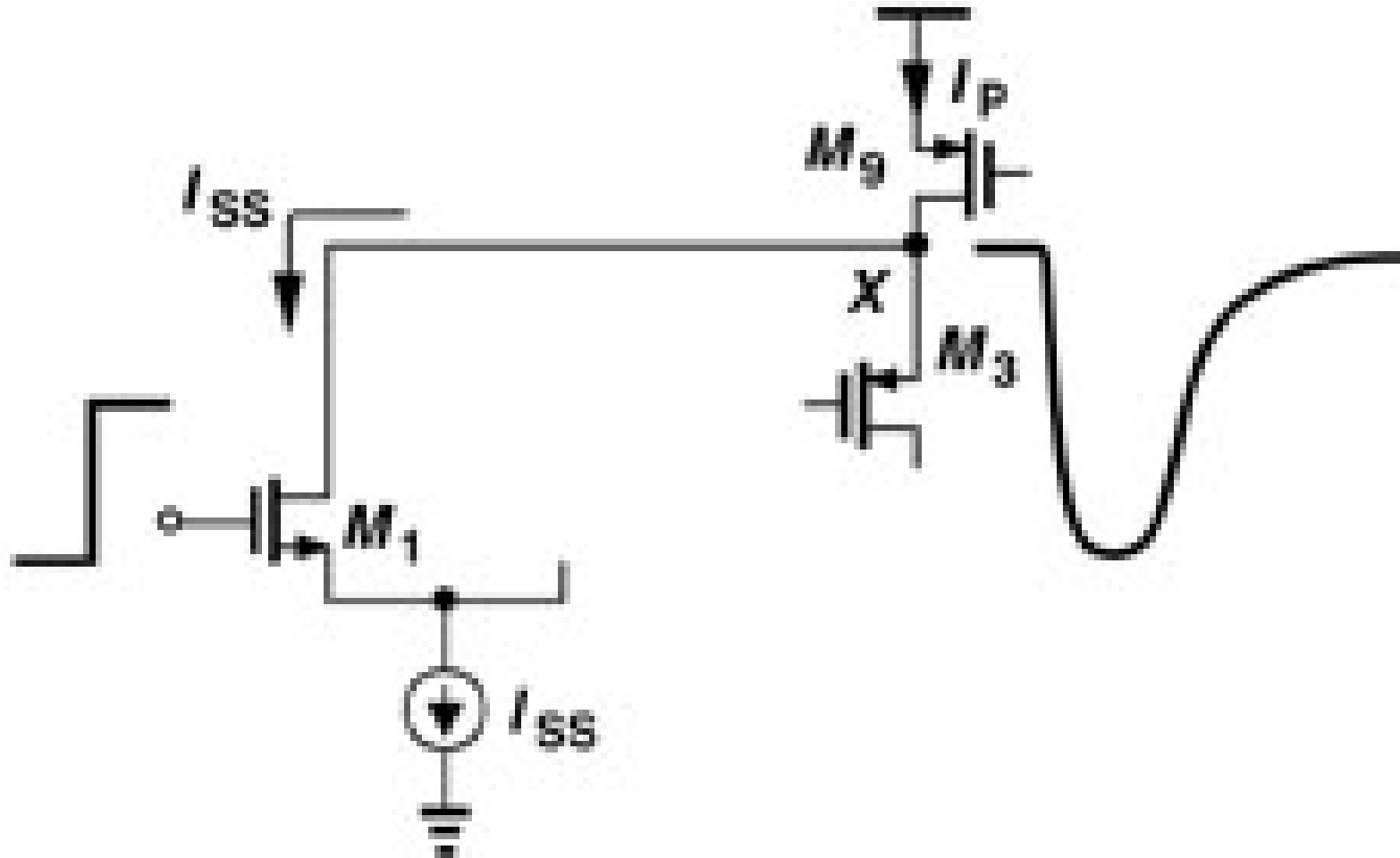

Slewing Recovery (cont.)

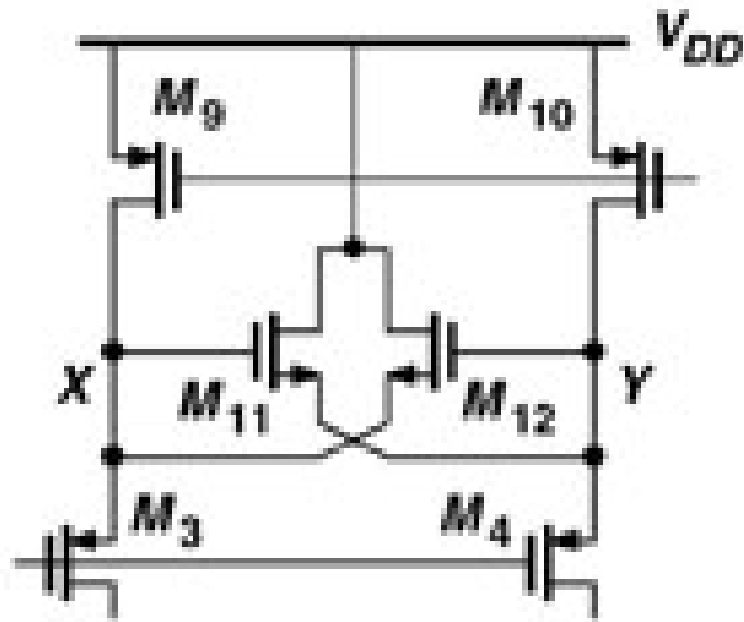

(a)

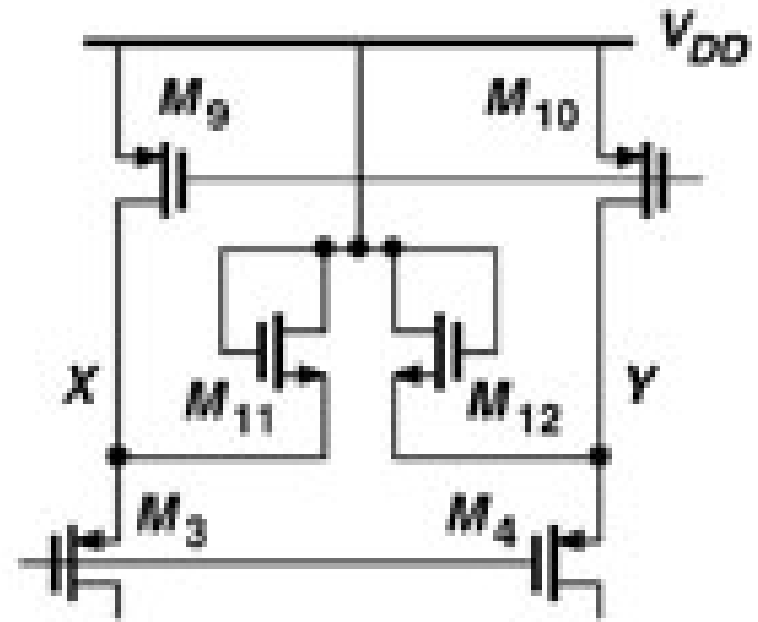

(b)

Power Supply Rejection

