

Chapter 8: Combinational Logic Modules

Prof. Soo-Ik Chae

Objectives

After completing this chapter, you will be able to:

- ❖ Understand the features of **decoders**
- ❖ Understand the features of **encoders**
- ❖ Understand the features of **priority encoders**
- ❖ Understand the features of **multiplexers**
- ❖ Understand the features of **demultiplexers**
- ❖ Describe how to design **comparators** and **magnitude comparators**
- ❖ Describe how to design **a parameterized module**

Basic Combinational Logic Modules

- ❖ Commonly used combinational logic modules:
 - Decoder
 - Encoder
 - Multiplexer
 - Demultiplexer
 - Comparator
 - Adder (CLA)
 - Subtractor (subtractor)
 - Multiplier
 - PLA
 - Parity Generator

-

Options for Modeling Combinational Logic

- ❖ Options for modeling combinational logic:
 - Verilog HDL primitives
 - Continuous assignment
 - Behavioral statement
 - Function
 - Task without delay or event control
 - Combinational UDP
 - Interconnected combinational logic modules

Three Descriptions of Combination Logic

Logic Description

Verilog Description

Circuit Schematic

Structural Model

Truth Table


User-Defined Primitives

Switching Equations


Continuous Assignments

Decoder Block Diagrams

 - ❖ An $n \times m$ decoder has n input lines and m output lines. Each output line Y_i corresponds to the i th minterm of input (line) variables.
 - Total decoding: when $m = 2^n$.
 - **Partial** decoding: when $m < 2^n$.




A 2-to-4 Decoder Example

 

E	x_1	x_0	Y_3	Y_2	Y_1	Y_0
1	ϕ	ϕ	1	1	1	1
0	0	0	1	1	1	0
0	0	1	1	1	0	1
0	1	0	1	0	1	1
0	1	1	0	1	1	1

(b) Function table


ϕ : don't care

 

 (c) Logic circuit

A 2-to-4 Decoder Example

```
// a 2-to-4 decoder with active low output
module decoder_2to4_low(x,enable,y);
input [1:0] x;
input enable;
output reg [3:0] y;
// the body of the 2-to-4 decoder
always @ (x or enable)
  if (!enable) y = 4'b1111; else
    case (x)
      2'b00 : y = 4'b1110;
      2'b01 : y = 4'b1101;
      2'b10 : y = 4'b1011;
      2'b11 : y = 4'b0111;
      default : y = 4'b1111;
    endcase
endmodule
```




A 2-to-4 Decoder with Enable Control

// a 2-to-4 decoder with active-high output

```
module decoder_2to4_high(x,enable,y);
input [1:0] x;
input enable;
output reg [3:0] y;
```


// the body of the 2-to-4 decoder
 
```
always @(x or enable)
if (!enable) y = 4'b0000; else
  case (x)
    2'b00 : y = 4'b0001;
    2'b01 : y = 4'b0010;
    2'b10 : y = 4'b0100;
    2'b11 : y = 4'b1000;
    default : y = 4'b0000;
  endcase
endmodule
```




A Parameterized Decoder Module
 
```
// an m-to-n decoder with active-high output
module decoder_m2n_high(x,enable,y);
parameter m = 3; // define the number of input lines
parameter n = 8; // define the number of output lines
input [m-1:0] x;
input enable;
output reg [n-1:0] y;
// The body of the m-to-n decoder
always @(x or enable)
  if (!enable) y = {n{1'b0}};
  else          y = {{n-1{1'b0}},1'b1} << x;
endmodule
```




Encoder Block Diagrams

 - ❖ An encoder has $m = 2^n$ (or fewer) input lines and n output lines. The output lines generate the binary code corresponding to the input value.



(a) Noninverted output

 


(b) Inverted output

A 4-to-2 Encoder Example

I_3	I_2	I_1	I_0	Y_1	Y_0
0	0	0	1	0	0
0	0	1	0	0	1
0	1	0	0	1	0
1	0	0	0	1	1

(a) Function table

 


(b) Logic circuit

Q: What is the problem of this encoder?

There are many undefined input cases!


A 4-to-2 Encoder Example

```
// a 4-to-2 encoder using if ... else structure
module encoder_4to2_ifelse(in, y);
input [3:0] in;
output reg [1:0] y;
// the body of the 4-to-2 encoder
always @(in) begin
    if (in == 4'b0001) y = 0; else
    if (in == 4'b0010) y = 1; else
    if (in == 4'b0100) y = 2; else
    if (in == 4'b1000) y = 3; else
        y = 2'bx;
end
endmodule
```

 


Another 4-to-2 Encoder Example
 
```
// a 4-to-2 encoder using case structure
module encoder_4to2_case(in, y);
input [3:0] in;
output reg [1:0] y;
// the body of the 4-to-2 encoder
always @(in)
  case (in)
    4'b0001 : y = 0;
    4'b0010 : y = 1;
    4'b0100 : y = 2;
    4'b1000 : y = 3;
    default : y = 2'bx;
  endcase
endmodule
```



A 4-to-2 Priority Encoder

 


(a) Block diagram

Input				Output	
I_3	I_2	I_1	I_0	A_1	A_0
0	0	0	1	0	0
0	0	1	ϕ	0	1
0	1	ϕ	ϕ	1	0
1	ϕ	ϕ	ϕ	1	1

(b) Function table


A 4-to-2 Priority Encoder Example

```
// a 4-to-2 priority encoder using if ... else structure
module priority_encoder_4to2_ifelse (in, valid_in, y);
input [3:0] in;
output reg [1:0] y;
output valid_in;
// the body of the 4-to-2 priority encoder
assign valid_in = |in;
always @(in) begin
    if (in[3]) y = 3; else
        // MSB: higher priority
        if (in[2]) y = 2; else
            if (in[1]) y = 1; else
                if (in[0]) y = 0; else
                    y = 2'bx;
end
endmodule
```

 

Another 4-to-2 Priority Encoder Example


```
// a 4-to-2 priority encoder using case structure
module priority_encoder_4to2_case(in, valid_in, y);
input [3:0] in;
output reg [1:0] y;
output valid_in;
// the body of the 4-to-2 priority encoder
assign valid_in = |in;
always @(in) casex (in)
  4'b1xxx: y = 3;
  4'b01xx: y = 2;
  4'b001x: y = 1;
  4'b0001: y = 0;
  default:   y = 2'bx;
endcase
endmodule
```

 

A Parameterized Priority Encoder Example

```
// an m-to-n priority encoder
module priencoder_m2n(x, valid_in, y);
parameter m = 8; // define the number of inputs
parameter n = 3; // define the number of outputs
input [m-1:0] x;
output valid_in; // indicates the data input x is valid.
output reg [n-1:0] y;
integer i;
// the body of the m-to-n priority encoder
assign valid_in = |x;
always @(*) begin: check_for_1
    for (i = m - 1 ; i > 0 ; i = i - 1)
        if (x[i] == 1) begin y = i; disable check_for_1; end
        else y = 0; // Why need else ...?
end
endmodule
```

 
Q: Explain the philosophy behind this program. Why is it so simple?



A Better Parameterized Priority Encoder Example


```
// an m-to-n priority encoder
```

```
module priencoder_m2n_while(x, valid_in, y);
parameter m = 4; // define the number of inputs
parameter n = 2; // define the number of outputs
input [m-1:0] x;
output valid_in; // indicates the data input x is valid.
output reg [n-1:0] y;
integer i;
// the body of the m-to-n priority encoder
assign valid_in = |x;
always @(*) begin
    i = m - 1 ;
    while(x[i] == 0 && i >= 0 ) i = i - 1;
    y = i;
end
endmodule
```

 


Multiplexer Block Diagrams

 - An m -to-1 ($m = 2^n$) multiplexer has m input lines, 1 output line, and n selection lines. The input line I_i selected by the binary combination of n source selection lines is directed to the output line, Y .




(a) Without enable control

 

(b) With enable control


A 4-to-1 Multiplexer Example

Gate-based 4-to-1 multiplexers

 


S_1	S_0	Y
0	0	I_0
0	1	I_1
1	0	I_2
1	1	I_3

(b) Function table

 

An n -bit 4-to-1 Multiplexer Example
 
```
// an N-bit 4-to-1 multiplexer using conditional operator.
module mux_nbit_4to1(select, in3, in2, in1, in0, y);
parameter N = 4; // define the width of 4-to-1 multiplexer
input [1:0] select;
input [N-1:0] in3, in2, in1, in0;
output [N-1:0] y;
// the body of the N-bit 4-to-1 multiplexer
assign y = select[1] ?
    (select[0] ? in3 : in2) :
    (select[0] ? in1 : in0);
endmodule
```



The Second n -bit 4-to-1 Multiplexer Example

```
// an N-bit 4-to-1 multiplexer with enable control.
module mux_nbit_4to1_en (select, enable, in3, in2, in1, in0, y);
parameter N = 4; // define the width of 4-to-1 multiplexer
input [1:0] select;
input enable;
input [N-1:0] in3, in2, in1, in0;
output reg [N-1:0] y;
// the body of the N-bit 4-to-1 multiplexer
always @ (select or enable or in0 or in1 or in2 or in3)
  if (!enable) y = {N{1'b0}};
  else y = select[1] ?
    (select[0] ? in3 : in2) :
    (select[0] ? in1 : in0);
endmodule
```

The Third n -bit 4-to-1 Multiplexer Example

// an N-bit 4-to-1 multiplexer using case structure.

module mux_nbit_4to1_case(select, in3, in2, in1, in0, y);

parameter N = 8; // define the width of 4-to-1 multiplexer

input [1:0] select;

input [N-1:0] in3, in2, in1, in0;

output reg [N-1:0] y;

// the body of the N-bit 4-to-1 multiplexer

always @(*)

case (select)

2'b11: y = in3 ;


2'b10: y = in2 ;

2'b01: y = in1 ;

2'b00: y = in0 ;


endcase

endmodule

 


A Parameterized Multiplexer Example

```
// an example of parameterized M-to-1 multiplexer.
module mux_m_to_1(select, in, y);
parameter M = 4; // define the size of M-to-1 multiplexer
parameter K = 2; // define the number of selection lines
input [K-1:0] select;
input [M-1:0] in;
output reg y;
// the body of the M-to-1 multiplexer
integer i;
always @(*)
    for (i = 0; i < M; i = i + 1)
        if (select == i) y = in[i];
endmodule
```

 


DeMultiplexer Block Diagrams

 - ❖ A 1-to- m ($m = 2^n$) demultiplexer has 1 input line, m output lines, and n destination selection lines. The input line D is directed to the output line Y_i selected by the binary combination of n destination selection lines.




(a) Without enable control

 

(b) With enable control

A 1-to-4 DeMultiplexer Example


Gate-based 1-to-4 demultiplexers

 

(a) Logic symbol

E	S_1	S_0	Y_3	Y_2	Y_1	Y_0
1	ϕ	ϕ	0	0	0	0
0	0	0	0	0	0	D
0	0	1	0	0	D	0
0	1	0	0	D	0	0
0	1	1	D	0	0	0

(b) Function table

 


(c) Logic circuit

An n -bit 1-to-4 DeMultiplexer Example

```
// an N-bit 1-to-4 demultiplexer using if ... else structure
module demux_1to4_ifelse (select, in, y3, y2, y1, y0);
parameter N = 4; // define the width of the demultiplexer
input [1:0] select;
input [N-1:0] in;
output reg [N-1:0] y3, y2, y1, y0;

 // the body of the N-bit 1-to-4 demultiplexer
always @ (select or in) begin
    if (select == 3) y3 = in; else y3 = {N{1'b0}};
    if (select == 2) y2 = in; else y2 = {N{1'b0}};
    if (select == 1) y1 = in; else y1 = {N{1'b0}};
    if (select == 0) y0 = in; else y0 = {N{1'b0}};
end
endmodule
```




The Second n -bit 1-to-4 DeMultiplexer Example

```
// an N-bit 1-to-4 demultiplexer with enable control
module demux_1to4_ifelse_en(select, enable, in, y3, y2, y1, y0);
parameter N = 4;      // Define the width of the demultiplexer
input    [1:0] select;
input    enable;
input    [N-1:0] in;
output reg [N-1:0] y3, y2, y1, y0;
// the body of the N-bit 1-to-4 demultiplexer
always @ (select or in or enable) begin
  if (enable)begin
    if (select == 3) y3 = in; else y3 = {N{1'b0}};
    if (select == 2) y2 = in; else y2 = {N{1'b0}};
    if (select == 1) y1 = in; else y1 = {N{1'b0}};
    if (select == 0) y0 = in; else y0 = {N{1'b0}};
  end else begin
    y3 = {N{1'b0}}; y2 = {N{1'b0}}; y1 = {N{1'b0}}; y0 = {N{1'b0}};
  end
end
endmodule
```

A Parameterized DeMultiplexer Example


```
// an example of 1-to-M demultiplexer module
```
 
```
module demux_1_to_m(select, in, y);
parameter M = 4; // define the size of 1-to-m demultiplexer
parameter K= 2; // define the number of selection lines
input [K-1:0] select;
input in;
output reg [M-1:0] y;
integer i;
// the body of the 1-to-M demultiplexer
always @(*)
  for (i = 0; i < M; i = i + 1) begin
    if (select == i) y[i] = in; else y[i] = 1'b0; end
endmodule
```



Comparators

 
- ❖ A magnitude comparator is a device that determines the relative magnitude of two numbers being applied to it.
- ❖ Two types of magnitude comparator circuits:
 - Comparator
 - Cascadable comparator



A 4-bit cascadable comparator block diagram

Comparators

 - ❖ Cascading two 4-bit comparators to form an 8-bit comparator.




- ❖ What will happen if you set the input value (010) at the rightmost end to other values?

A Simple Comparator Example

```
// an N-bit comparator module example
module comparator_simple(a, b, cgt, clt, ceq);
parameter N = 4; // define the size of comparator

// I/O port declarations
input [N-1:0] a, b;
output cgt, clt, ceq;

 // the body of the N-bit comparator
assign cgt = (a > b);
assign clt = (a < b);
assign ceq = (a == b);
endmodule
```



A Cascadable Comparator Example

```
module comparator_cascadable (Iagt, Iaeqb, Ialt, a, b, Oagt, Oaeqb, Oalt);
```

parameter N = 4; // define the size of comparator

// I/O port declarations

```
input Iagt, Iaeqb, Ialt;
```

```
input [N-1:0] a, b;
```

```
output Oagt, Oaeqb, Oalt;
```

// dataflow modeling using relation operators

```
assign Oaeqb = (a == b) && (Iaeqb == 1); // equality
```

```
assign Oagt = (a > b) || ((a == b)&& (Iagt == 1)); // greater than
```

```
assign Oalt = (a < b) || ((a == b)&& (Ialt == 1)); // less than
```

```
endmodule
```

