
 


Sequential Circuit Analysis and Timing


Various Types of FFs

 

Input D	Next state
0	0
1	1




J	K	Next state
0	0	Q
0	1	0
1	0	1
1	1	Q'

 


Input EN	Next state
0 at rising edge T	Q
1 at rising edge T	Q'

Analysis of Clocked Synchronous State Machines

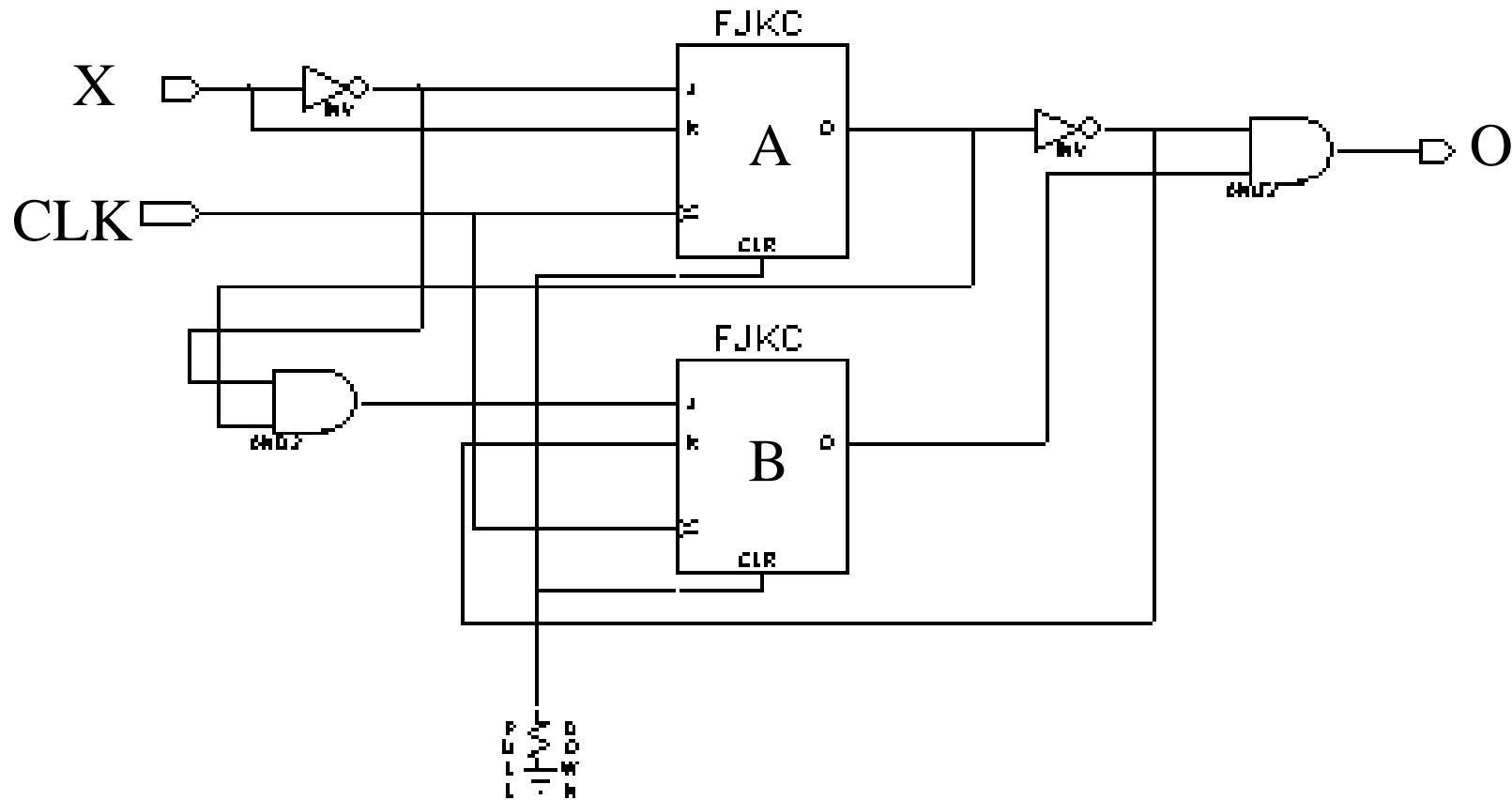- Begin with circuit
- End with state diagram – word description
- 3 step approach



Synchronized Operation With CLK

 

Step 1: Excitation and Output Equations

- Derive Excitation and Output Equations from the schematic

$$J_A = \overline{X}, K_A = X,$$

$$J_B = Q_A \overline{X}, K_B = \overline{Q_A},$$

$$O = \overline{Q_A} Q_B$$

Step 2: State/Output Table

C.S. Input Output				C.S. Input				Excitation				C.S. Input N.S			
QB	QA	X	O	QB	QA	X	JB	KB	JA	KA	QB	QA	X	QB	QA
0	0	0	0	0	0	0	0	1	1	0	0	0	0	0	1
0	0	1	0	0	0	1	0	1	0	1	0	0	1	0	0
0	1	0	0	0	1	0	1	0	1	0	0	1	0	1	1
0	1	1	0	0	1	1	0	0	0	1	0	1	1	0	0
1	0	0	1	1	0	0	0	1	1	0	1	0	0	0	1
1	0	1	1	1	0	1	0	1	0	1	1	0	1	0	0
1	1	0	0	1	1	0	1	0	1	0	1	1	0	1	1
1	1	1	0	1	1	1	0	0	0	1	1	1	1	1	0

Output Table

Excitation Table


Transition Table

Step 2: State/Output Table

		P.S.			Input				Output				Excitation				N.S.	
		QB	QA	X	O	JB	KB	JA	KA	JB	KB	JA	KA	QB	QA			
a	{	0	0	0	0	0	1	1	0	0	1	1	0	0	1			
		0	0	1	0	0	0	1	0	1	0	1	0	0	0			
b	{	0	1	0	0	0	1	0	1	0	1	0	0	1	1			
		0	1	1	0	0	0	0	0	1	0	0	1	0	0			
c	{	1	0	0	1	0	1	1	0	1	0	1	0	0	1			
		1	0	1	1	0	1	0	1	0	1	0	1	0	0			
d	{	1	1	0	0	1	0	1	0	1	0	1	0	1	1			
		1	1	1	0	0	0	0	0	1	0	0	1	1	0			

Step 2: State/Output Table (Cont.)


C.S.	X	O	N.S.
a	0	0	b
a	1	0	a
b	0	0	d
b	1	0	a
c	0	1	b
c	1	1	a
d	0	0	d
d	1	0	c

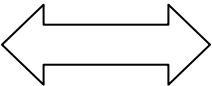


State	X	
	0	1
a	b,0	a,0
b	d,0	a,0
c	b,1	a,1
d	d,0	c,0

Step 3: State Diagram

 - Can you tell what this machine is doing?




Example

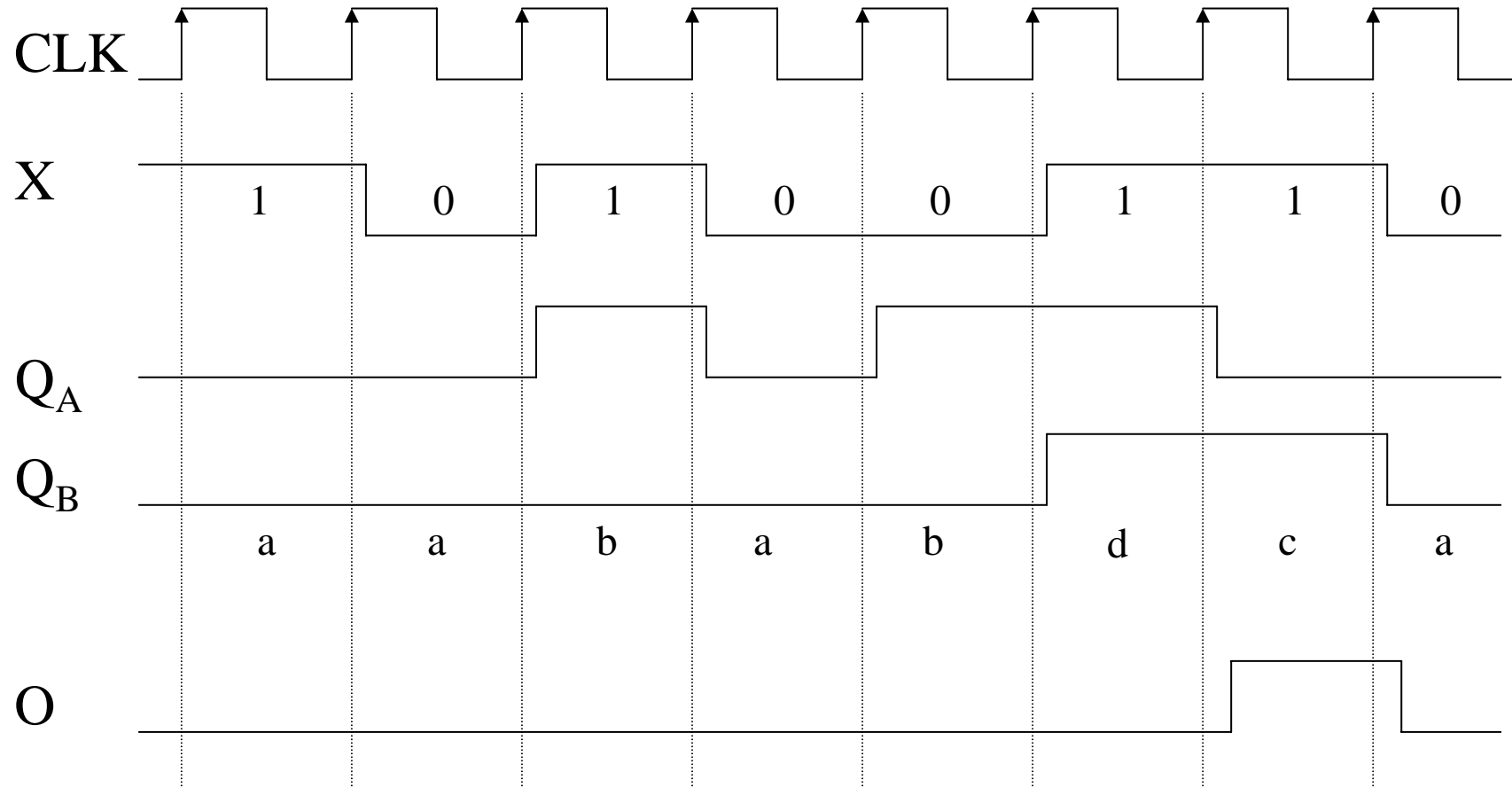


Timing

 
- If this circuit is to work with a larger system, what are the timing requirements? – Timing specification




Metastability

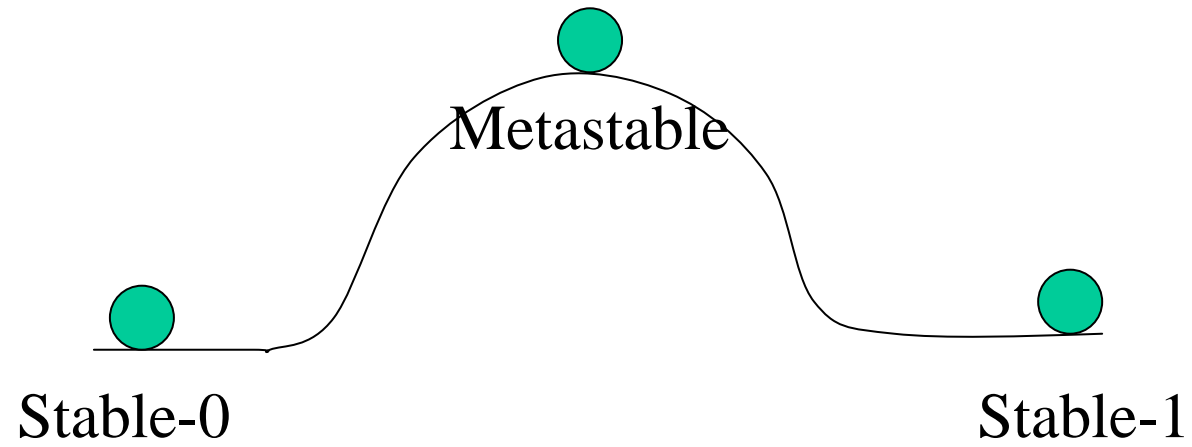



Metastability of a sequential logic

 

S	R	Q	QN
0	0	last Q	last QN
0	1	0	1
1	0	1	0
1	1	0	0

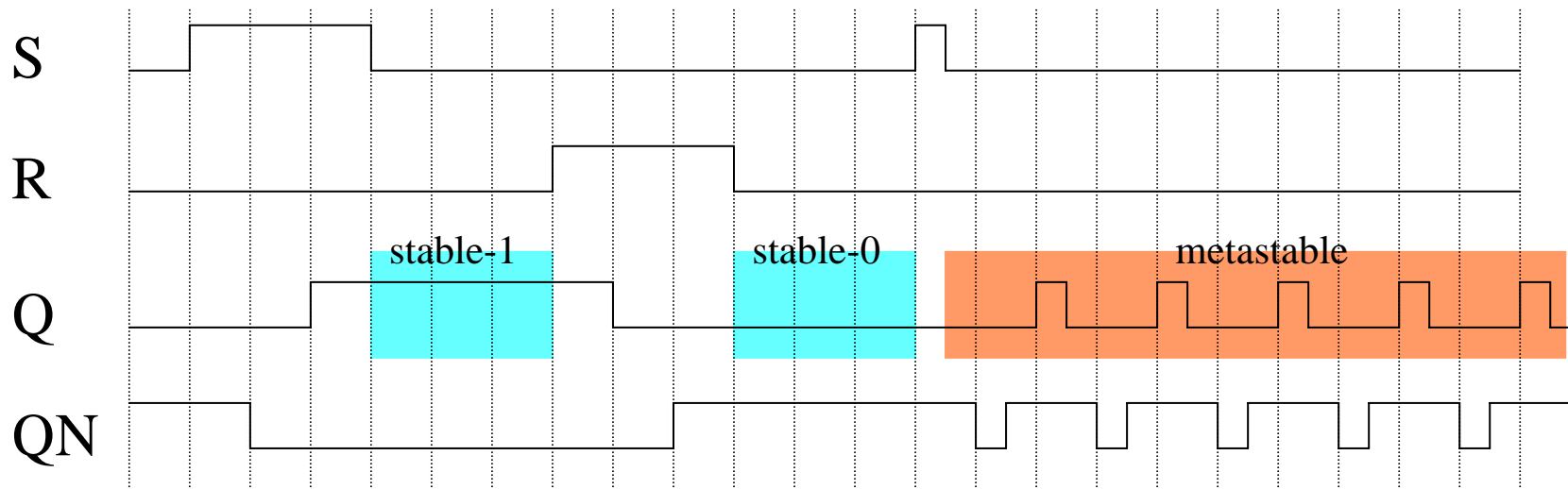


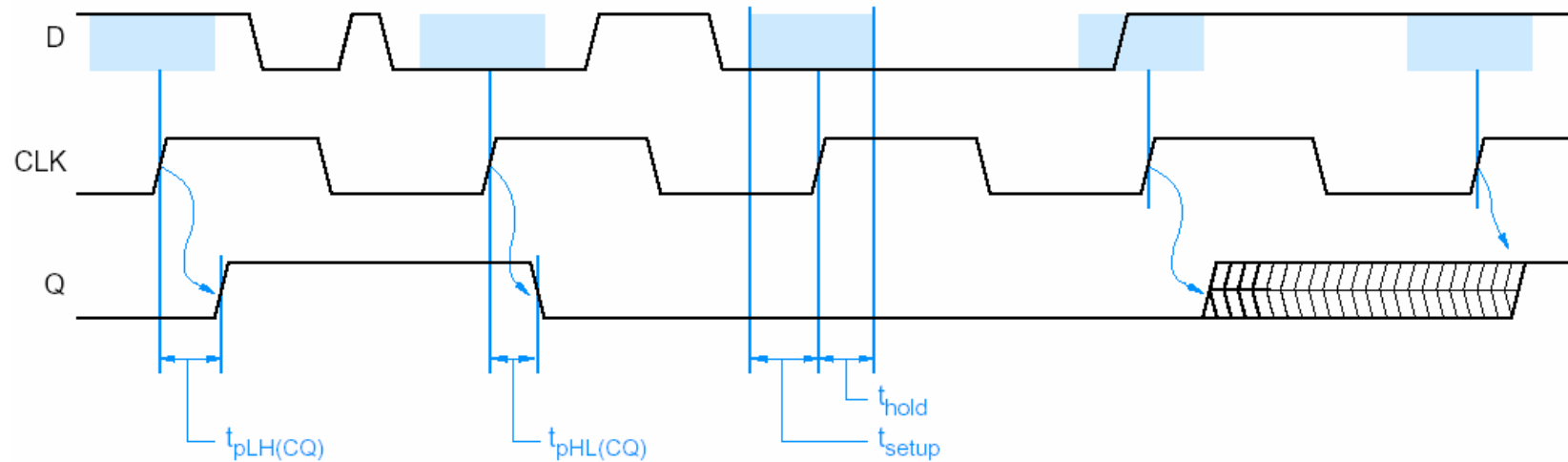 Setup & Hold Times of Sequential Components (e.g. D-ff)




Maximum CLK frequency

- How fast can the circuit work?

 

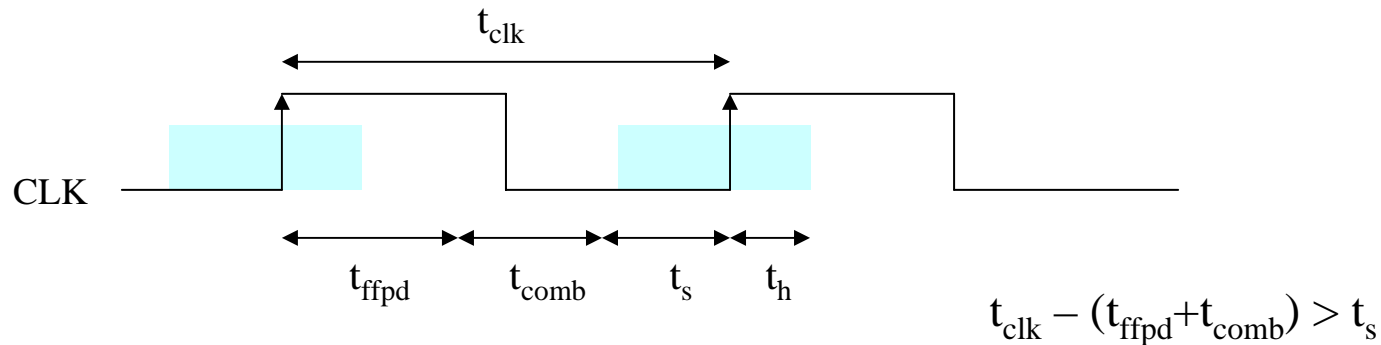- Assume inputs are ready at the right time



Maximum CLK frequency


- Timing specs for 74LS parts

	Propagation delay	Setup time	Hold time	Max freq.
74LS04 (Inverter)	$t_{pLH} = 15 \text{ ns}$ $t_{pHL} = 15 \text{ ns}$	N/A		
74LS08 (AND)	$t_{pLH} = 15 \text{ ns}$ $t_{pHL} = 20 \text{ ns}$	N/A		
74LS109 (JK f/f)	$t_{pLH} = 25 \text{ ns}$ $t_{pHL} = 40 \text{ ns}$	$t_s = 35\text{ns}$ for H data in $t_s = 25\text{ns}$ for L data in	$t_h = 5\text{ns}$	25 Mhz


- Find the worst case delay path
 - Sum up worst case component delay, independent of transition direction H->L, L->H
 - 109 t_p ->08 t_p ->109 t_{setup} : $40 + 20 + 35 = 95 \text{ ns}$
 - 109 t_p ->04 t_p ->109 t_{setup} : $40 + 15 + 35 = 90 \text{ ns}$
- $\text{Max } f_{\text{clk}} = 1/95\text{ns} = 10.5 \text{ Mhz}$

Setup and Hold time specifications on X

- t_s for X

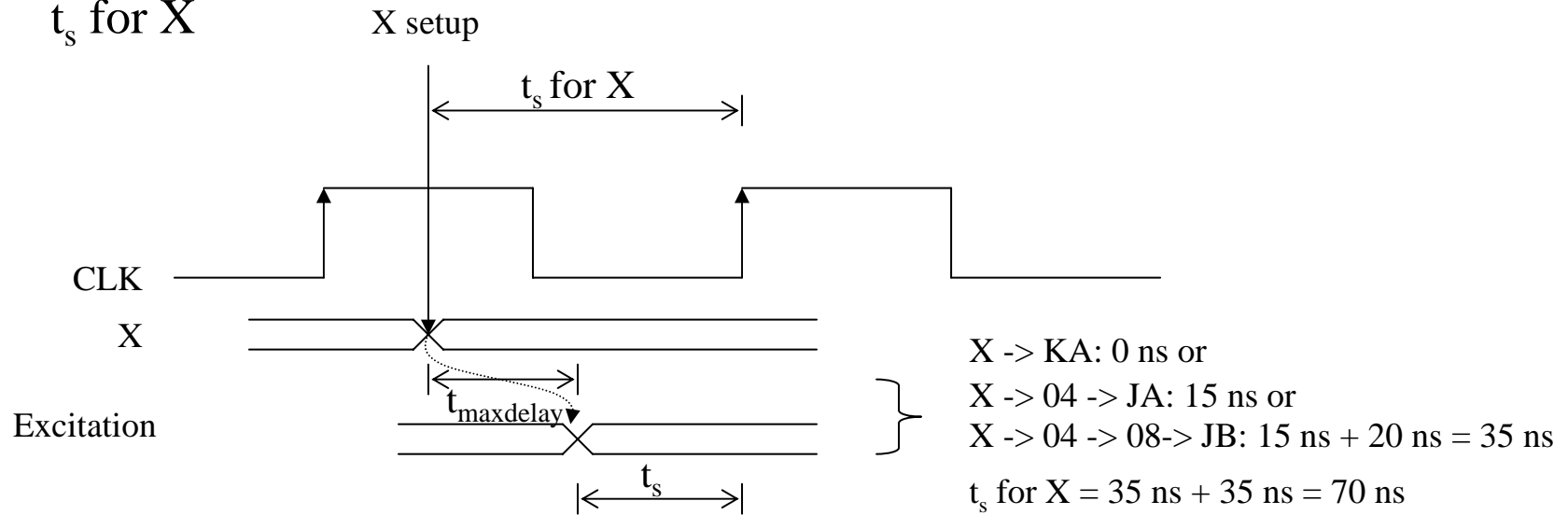

- t_h for X

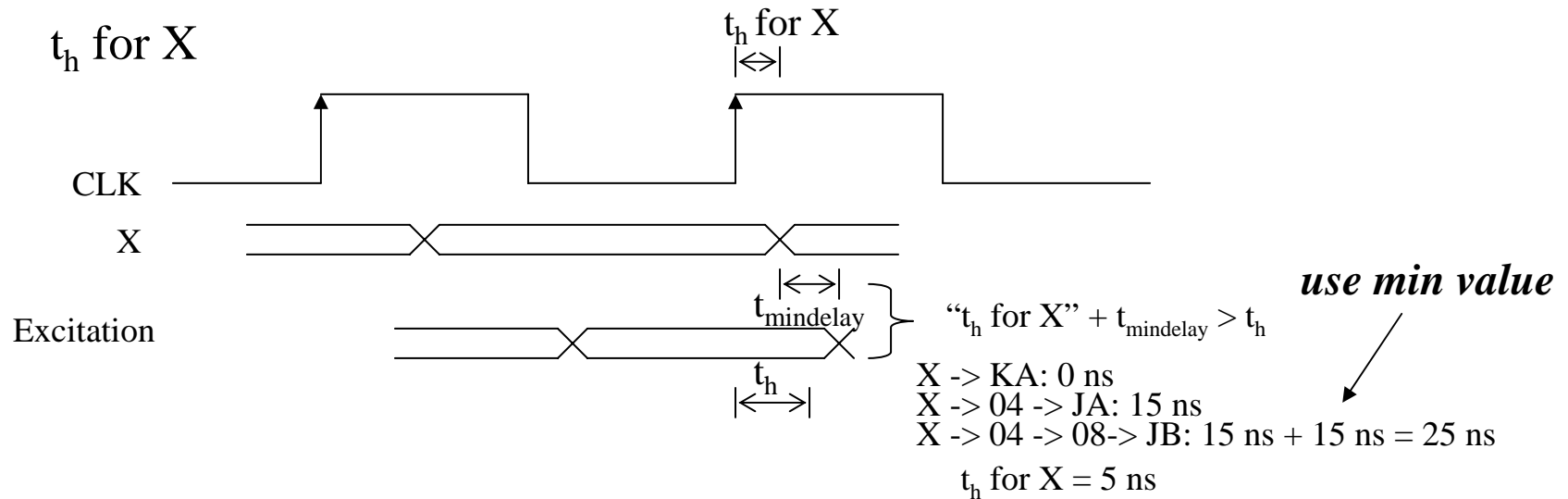

Propagation delay

- X -> O: N/A (Applicable only for Mealy type output)
- CLK -> O:
 - $tp_{LH} = \max (tp_{LH} '109 + tp_{LH} '08, tp_{HL} '109 + tp_{LH} '04 + tp_{LH} '08)$
 $= \max (25 \text{ ns} + 15 \text{ ns}, 40 \text{ ns} + 15 \text{ ns} + 15 \text{ ns}) = 70 \text{ ns}$
 - $tp_{HL} = \max (tp_{HL} '109 + tp_{HL} '08, tp_{LH} '109 + tp_{HL} '04 + tp_{HL} '08)$
 $= \max (40 \text{ ns} + 20 \text{ ns}, 25 \text{ ns} + 15 \text{ ns} + 20 \text{ ns}) = 60 \text{ ns}$


Final timing spec for our circuit

	Propagation delay	Setup time	Hold time	Max freq.
Our circuit	$t_{pLH} = 70 \text{ ns}$ $t_{pHL} = 60 \text{ ns}$	$t_s = 70 \text{ ns}$	$t_h = 5 \text{ ns}$	10.5 Mhz


- This spec will be used for analyzing timing of a larger system containing our circuit as a component.

Quiz

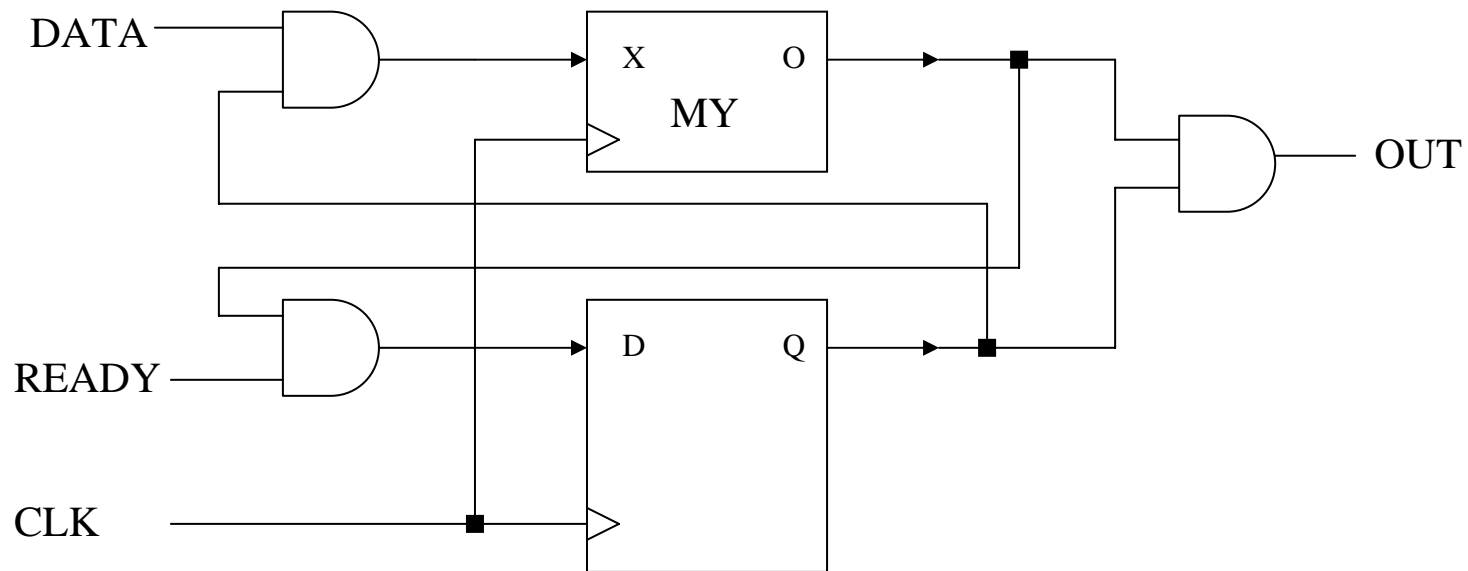
- What is the maximum clock frequency of the following circuit?







Can you tell what this guy is doing?

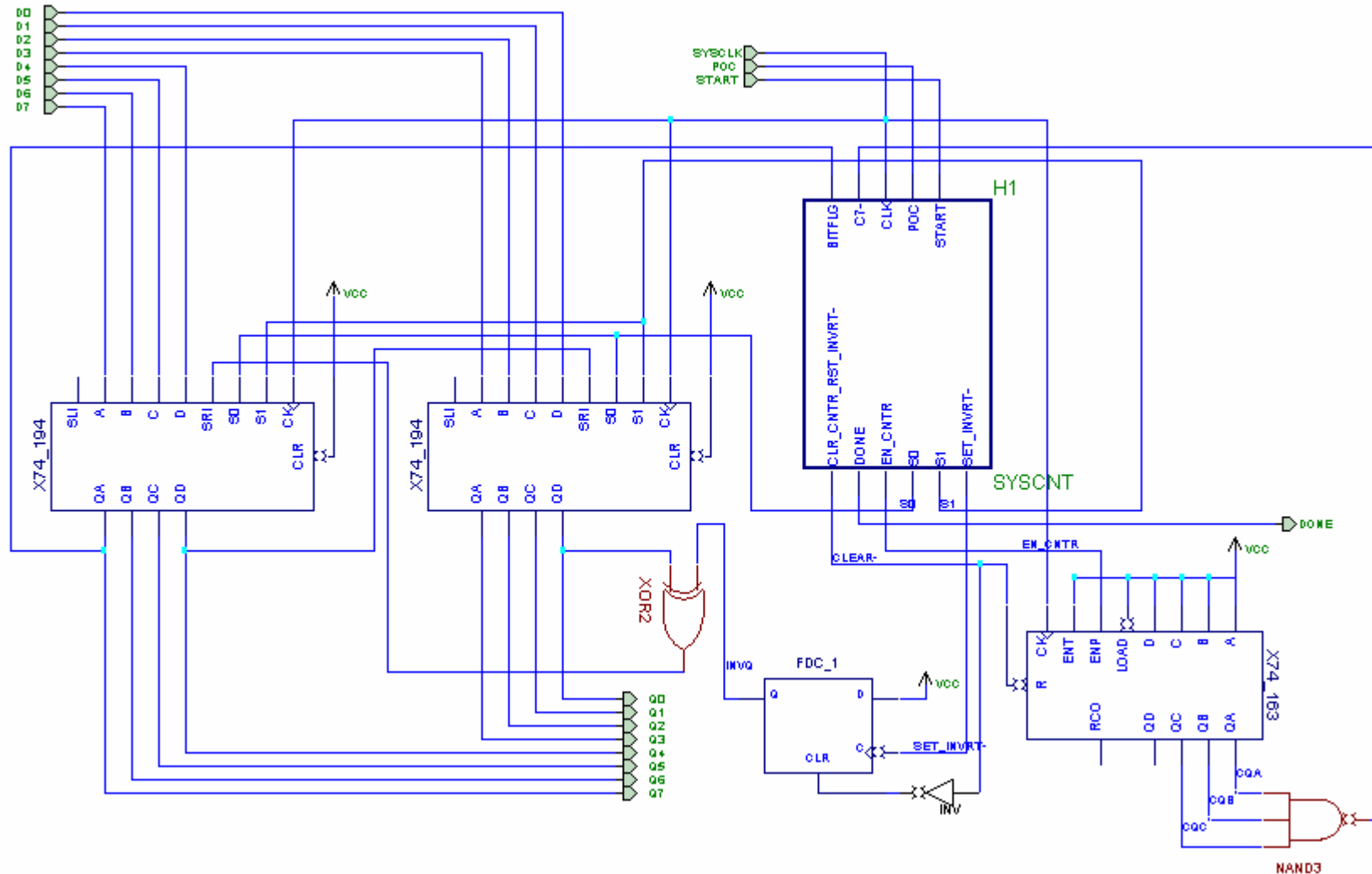

SYSCNT

 


Bubble-to-bubble approach

    


Copyright © 2000 by Prentice Hall, Inc.
Digital Design Principles and Practices, 3/e

Proper use of bubbles and naming

 
- Name of a signal: Help understanding the circuit like meaningful variable names in C programs (READY, GO, ENABLE, REQUEST, etc)
- Active High or Active Low (to take advantage of gate implementation, e.g., NOR is faster than OR)
- Use the bubble to represent Active Low signal and its name has “_L” or “-” (e.g., READY_L or READY-)




(a)

 

(b)

 

(c)


 


(d)



Copyright © 2000 by Prentice Hall, Inc.
Digital Design Principles and Practices, 3/e

Examples

Active low inputs
(Async.)

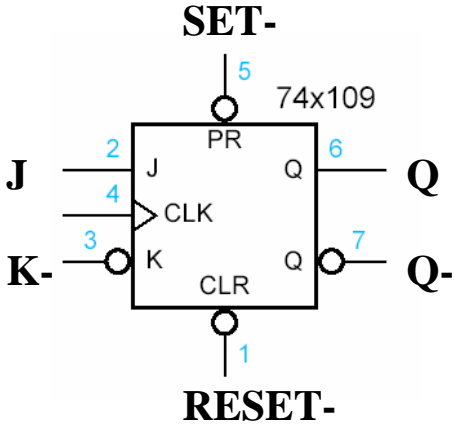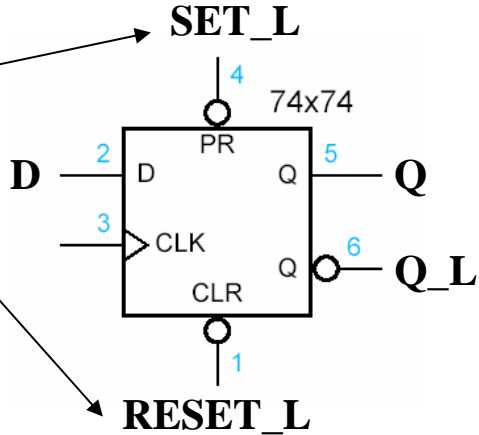

Active low inputs (Sync.)

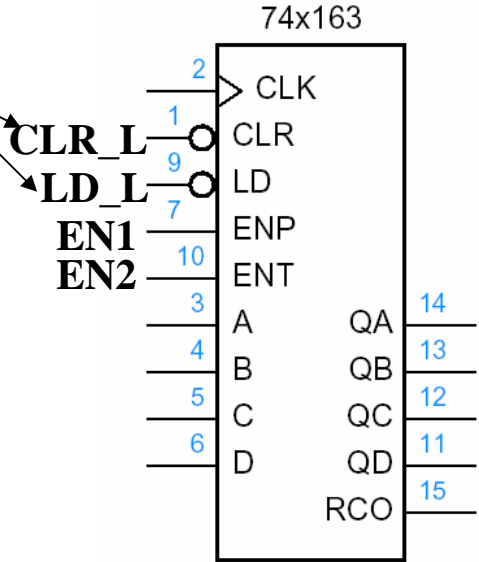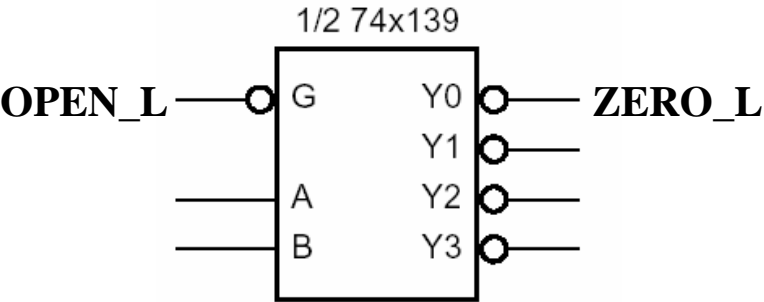

MSI Chips

(used in our 2's complement machine)

Read: 8.4, 8.5, 6.4

(3rd Edition 8.4, 8.5, 5.4)

74LS163

- 4-bit, synchronous, parallel load, binary counter

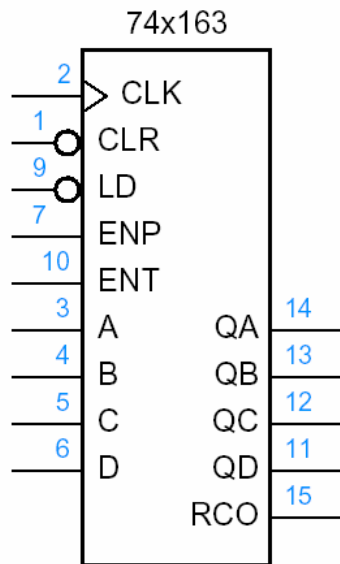


Table 8-11 State table for a 74x163 4-bit binary counter.

Inputs				Current State				Next State			
CLR_L	LD_L	ENT	ENP	QD	QC	QB	QA	QD*	QC*	QB*	QA*
0	x	x	x	x	x	x	x	0	0	0	0
1	0	x	x	x	x	x	x	D	C	B	A
1	1	0	x	x	x	x	x	QD	QC	QB	QA
1	1	x	0	x	x	x	x	QD	QC	QB	QA
1	1	1	1	0	0	0	0	0	0	0	1
1	1	1	1	0	0	0	1	0	0	1	0
1	1	1	1	0	0	1	0	0	0	1	1
1	1	1	1	0	0	1	1	0	1	0	0
1	1	1	1	0	1	0	0	0	1	0	1
1	1	1	1	0	1	1	0	0	1	1	1
1	1	1	1	0	1	1	1	1	0	0	0
1	1	1	1	1	0	0	0	1	0	0	1
1	1	1	1	1	0	0	1	1	0	1	0
1	1	1	1	1	0	1	0	1	0	1	1
1	1	1	1	1	0	1	1	1	1	0	0
1	1	1	1	1	1	1	0	0	1	1	0
1	1	1	1	1	1	1	0	1	1	1	1
1	1	1	1	1	1	1	1	0	0	0	0


RCO

0

1


8 bit counter using 74LS163 ?

- Cascading using RCO

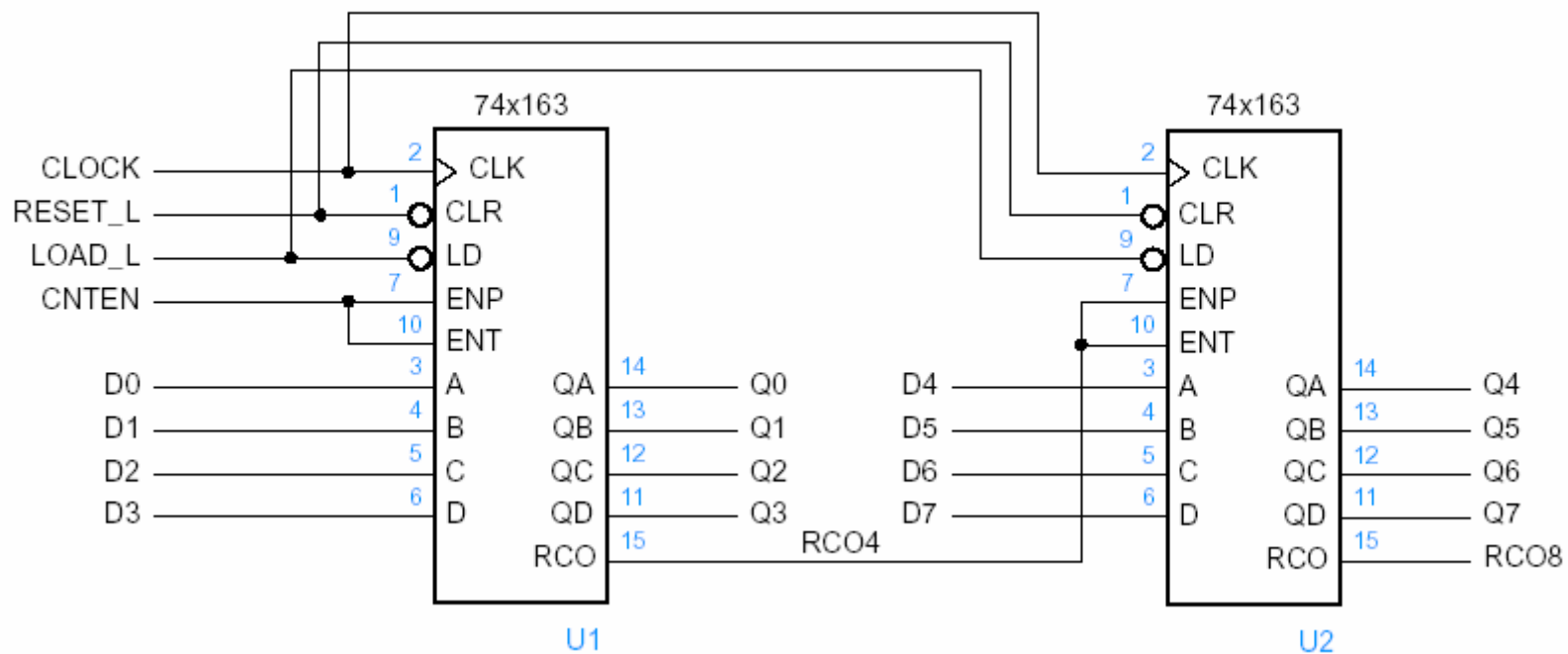

74LS194

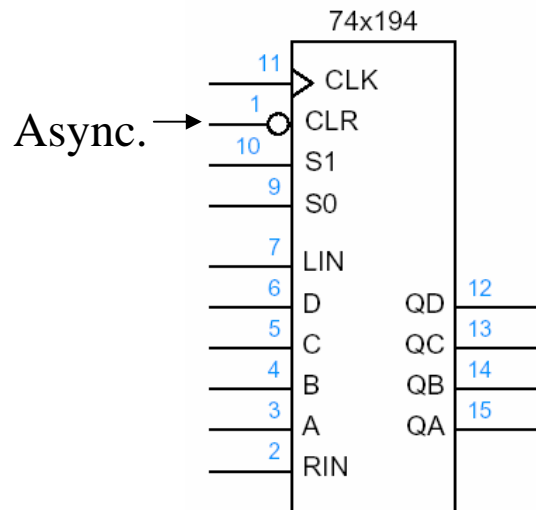
- 4-bit, parallel in, parallel out, bi-directional shift register



Function	Inputs		Next state			
	S1	S0	QA*	QB*	QC*	QD*
Hold	0	0	QA	QB	QC	QD
Shift right	0	1	RIN	QA	QB	QC
Shift left	1	0	QB	QC	QD	LIN
Load	1	1	A	B	C	D

74LS139

- Dual 2-to-4 Decoder

 

<i>Inputs</i>			<i>Outputs</i>			
G_L	B	A	Y3_L	Y2_L	Y1_L	Y0_L
1	x	x	1	1	1	1
0	0	0	1	1	1	0
0	0	1	1	1	0	1
0	1	0	1	0	1	1
0	1	1	0	1	1	1

74LS138

- 3 Enables, 3-to-8 Decoder


 


Table 5-7 Truth table for a 74x138 3-to-8 decoder.

Inputs						Outputs							
G1	G2A_L	G2B_L	C	B	A	Y7_L	Y6_L	Y5_L	Y4_L	Y3_L	Y2_L	Y1_L	Y0_L
0	x	x	x	x	x	1	1	1	1	1	1	1	1
x	1	x	x	x	x	1	1	1	1	1	1	1	1
x	x	1	x	x	x	1	1	1	1	1	1	1	1
1	0	0	0	0	0	1	1	1	1	1	1	1	0
1	0	0	0	0	1	1	1	1	1	1	1	0	1
1	0	0	0	1	0	1	1	1	1	0	1	1	1
1	0	0	1	0	0	1	1	1	0	1	1	1	1
1	0	0	1	0	1	1	1	0	1	1	1	1	1
1	0	0	1	1	0	1	0	1	1	1	1	1	1
1	0	0	1	1	1	0	1	1	1	1	1	1	1


Applications of Decoder

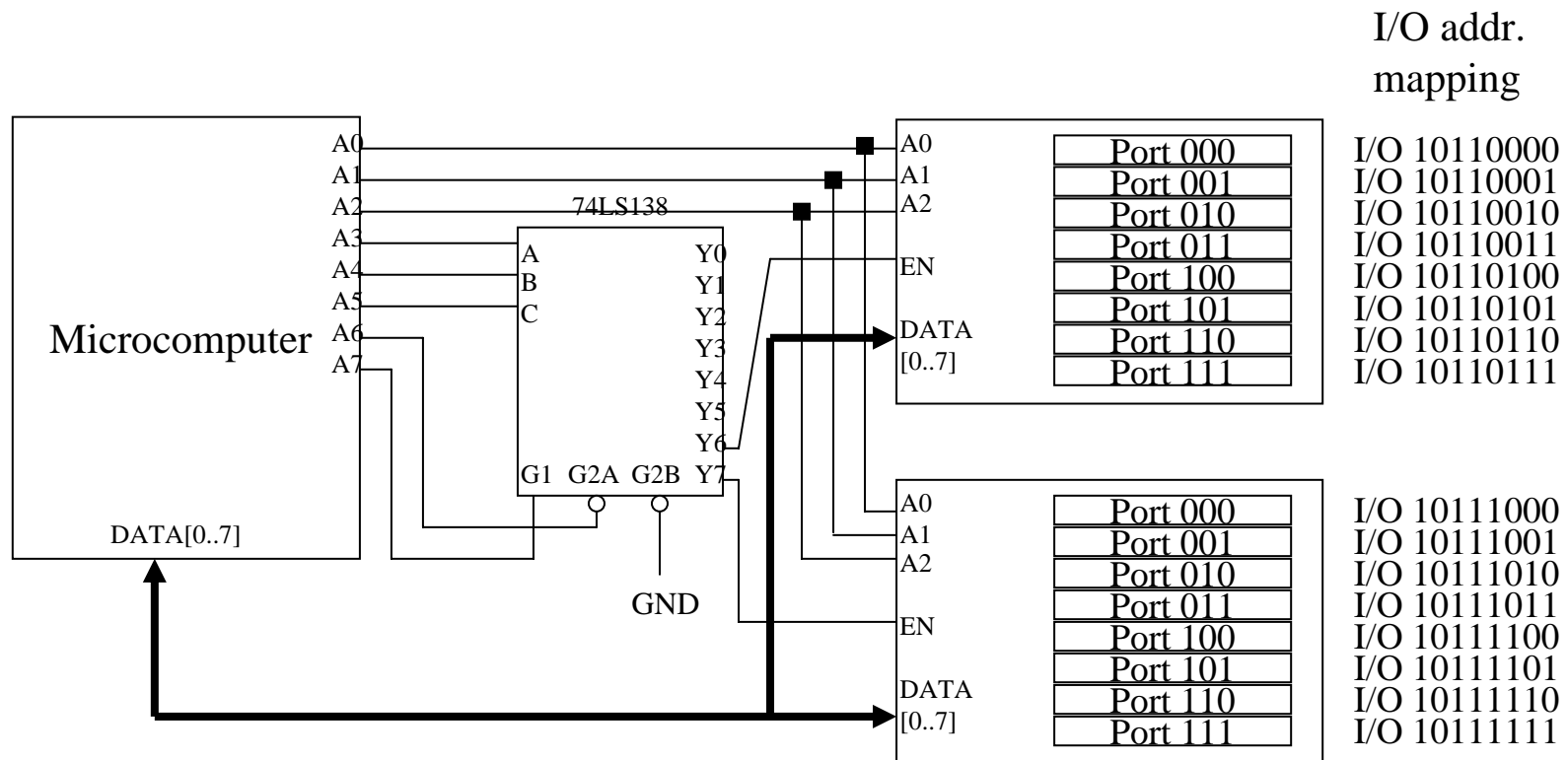- Address decoder
 - In microcomputers, an I/O address is 8 bits so that there are 256 unique device addresses.
 - How to make 16 I/O ports of two I/O chips (8 ports of each) to the following I/O mapped addresses?




Applications of Decoder

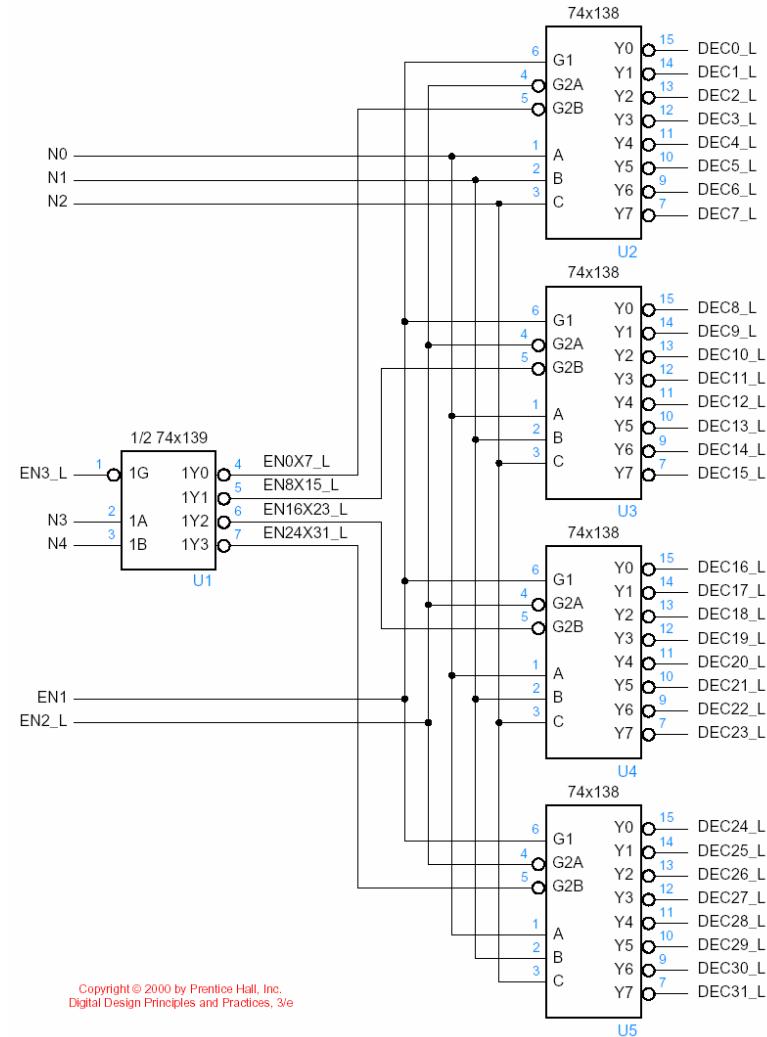- Cascading
 - Cascade small decoders for longer bits decoding
 - How to make 5-to-32 decoder (with 3 enables EN1, EN2-, EN3-) using 74LS138 and 74LS139?




Applications of Decoder


- Use as a Demultiplexer

 

 
- Use in combinational logic design
 - Use a 74LS138 to implement $F = D\bar{E}\bar{F}(AB + \bar{A}\bar{B}\bar{C})$



		BA			
		00	01	11	10
C	0	1	0	1	0
	1	0	0	1	0

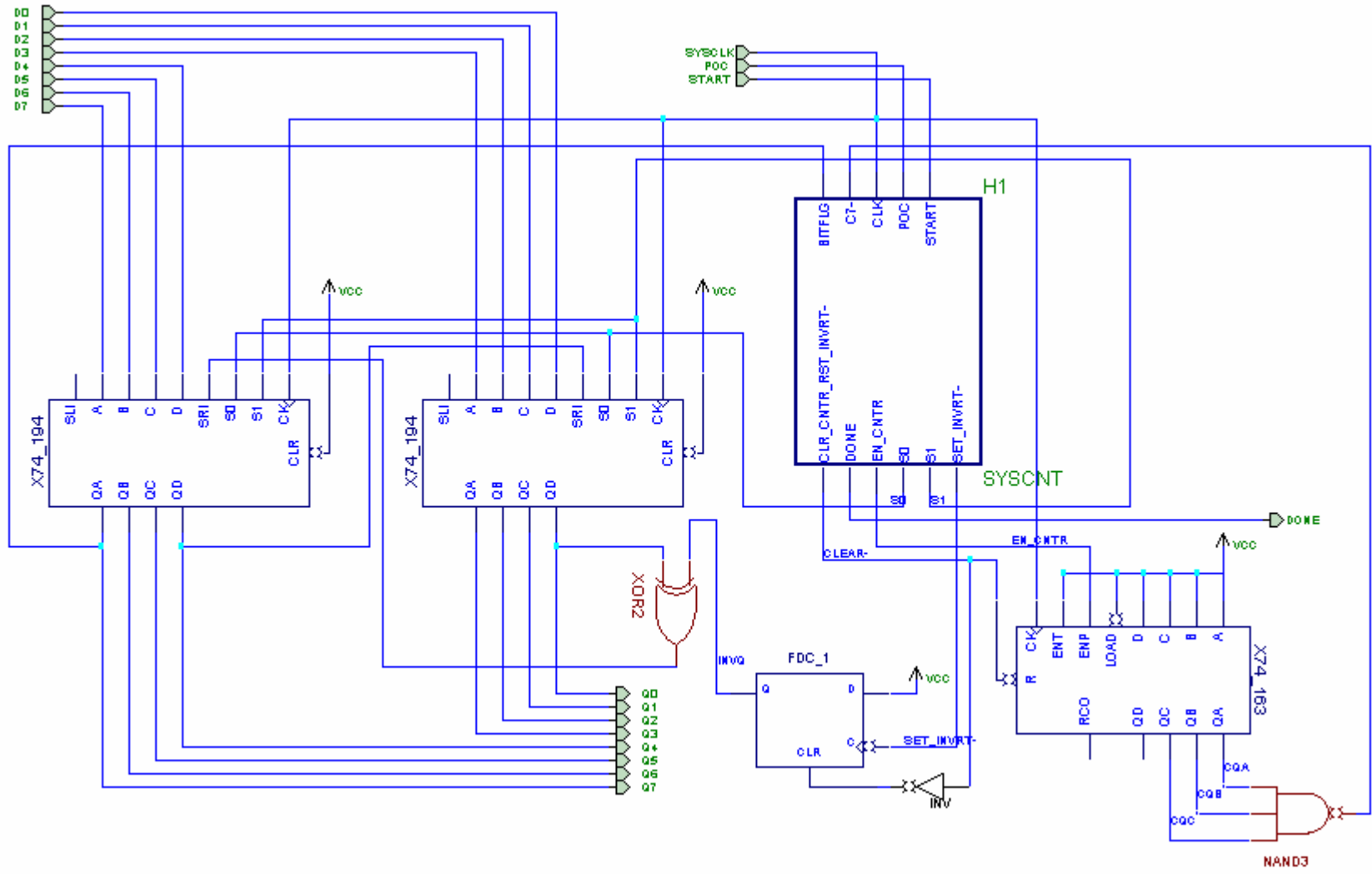

SYSCNT

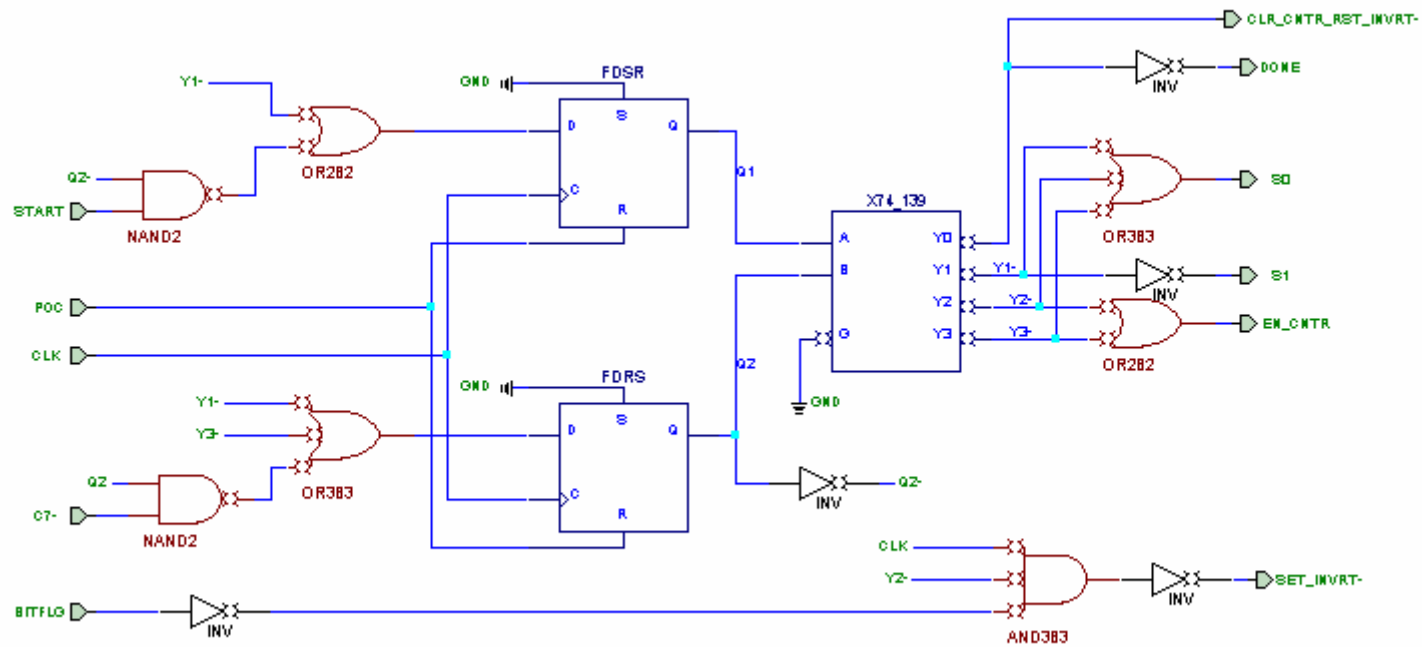

Hints

- Sequential Two's complement machine
 - Analyze a machine that takes the 2's complement of an 8-bit number
 - 8 bits in, START → 8 bits out, DONE
 - More realistic example that uses MSI chips
 - For PLDs, FPGAs design, we usually use functional blocks (LBB – Logic Building Block) equivalent to the counters, shift registers, decoders, etc

General Architecture and Operation

- Example: $01001010 \rightarrow 10110110$ (2's complement of $A = 2^n - A$)
 - $01001010 \rightarrow 11111111 + 1 - 01001010 = 10110101 + 1 = 10110110$
 - Write down bits from right until a 1 is encountered. Complements all bits there after
- General Operation Flow
 - Load 8 bits into 2×74194 (4 bit shift right/left register)
 - Do a circular shift on the data, inverting bits as necessary
 - Finally, the 2's complement data will appear at the output after 8 shift operations

	Parallel Data Out $Q_7 Q_6 Q_5 Q_4 Q_3 Q_2 Q_1 Q_0$	Invert InvertQ
	- - - - -	0
	0 1 0 0 1 0 1 $\overline{0}$	0
1	$\overline{0}$ 0 1 0 0 1 0 1	0
2	1 $\overline{0}$ 0 1 0 0 1 0	1
3	1 1 $\overline{0}$ 0 1 0 0 1	1
4	0 1 1 $\overline{0}$ 0 1 0 0	1
5	1 0 1 1 $\overline{0}$ 0 1 0	1
6	1 1 0 1 1 $\overline{0}$ 0 1	1
7	0 1 1 0 1 1 $\overline{0}$ 0	1
8	1 0 1 1 0 1 1 $\overline{0}$	1

General Architecture and Operation


- 74LS194 (4 bit shift register) is used for loading & shifting 8 bit data
- We use D f/f (with asynchronous clear) to remember from when inverting is necessary
- We use 74LS163 (a synchronous 4-bit counter) to count 8 shifts
- System controller control the overall operation
 - The system controller determines when data should be loaded, shifted or held by controlling S1 and S0
 - The system controller also looks at BITFLG so as to know when to set the INVERT D f/f
 - The system controller also clears 74LS163 at the beginning, increments it each time a bit is shifted, and detects when 8 bits have been shifted.
 - Finally, the system controller asserts DONE signal


Much larger system analysis

- Analysis of the structure
 - More than a few f/fs in circuit – not practical to treat as a single state machine
 - Try directly applying the 3-step approach
 - How many f/fs?
 - Shift reg – 8, Counter – 4, INVERT –1, System Controller –2
 - 15 f/fs $\Rightarrow 2^{15}$ states
- Then, 3 step analysis only on system controller

Synchronous System Structure

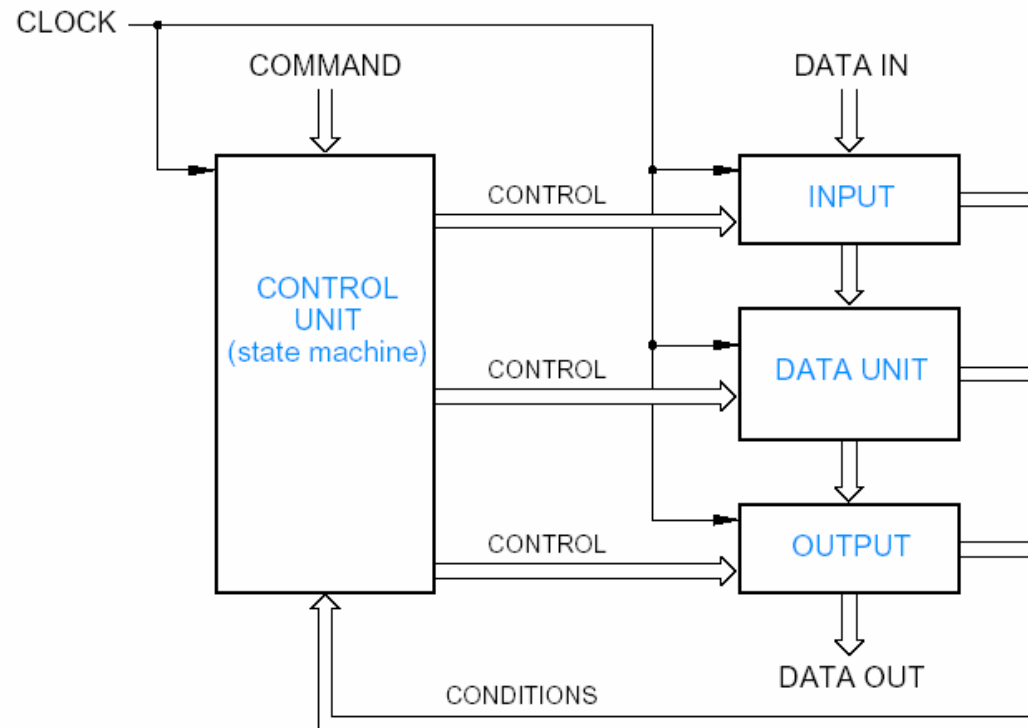- Generally 2 Parts: Data Unit & Control Unit
 - Data unit: process data (store, route, combine)
 - Control unit: starting and stopping actions, test conditions, decide what to do next
 - Only control unit – designed as state machine



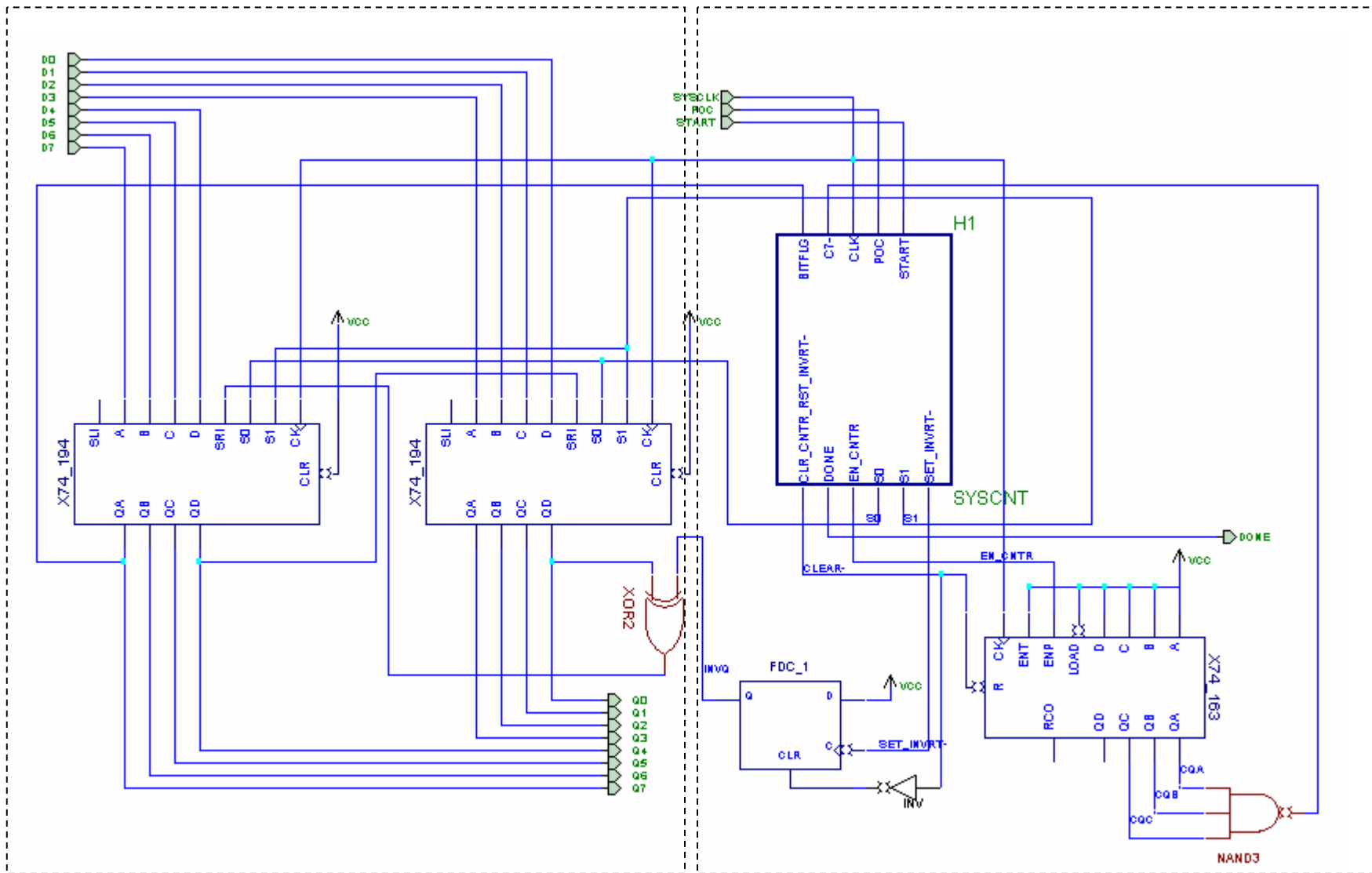



Data unit

Control unit (State Machine)

Decomposing State Machines

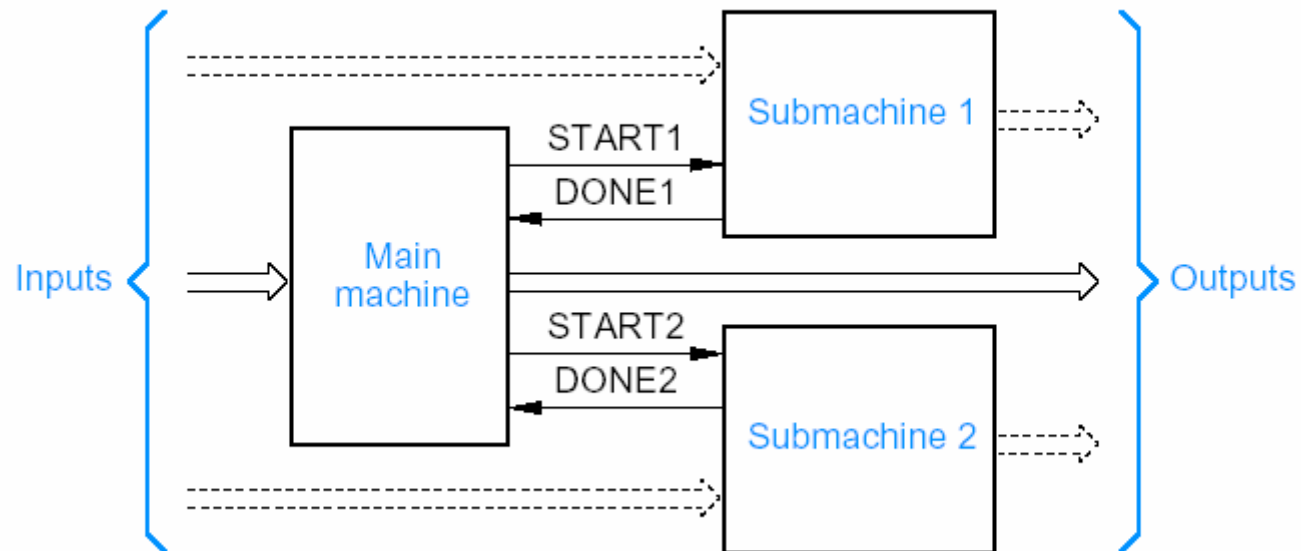- The control unit may be further partitioned
 - Main machine – system controller
 - Sub machines – counter, INVERT D f/f




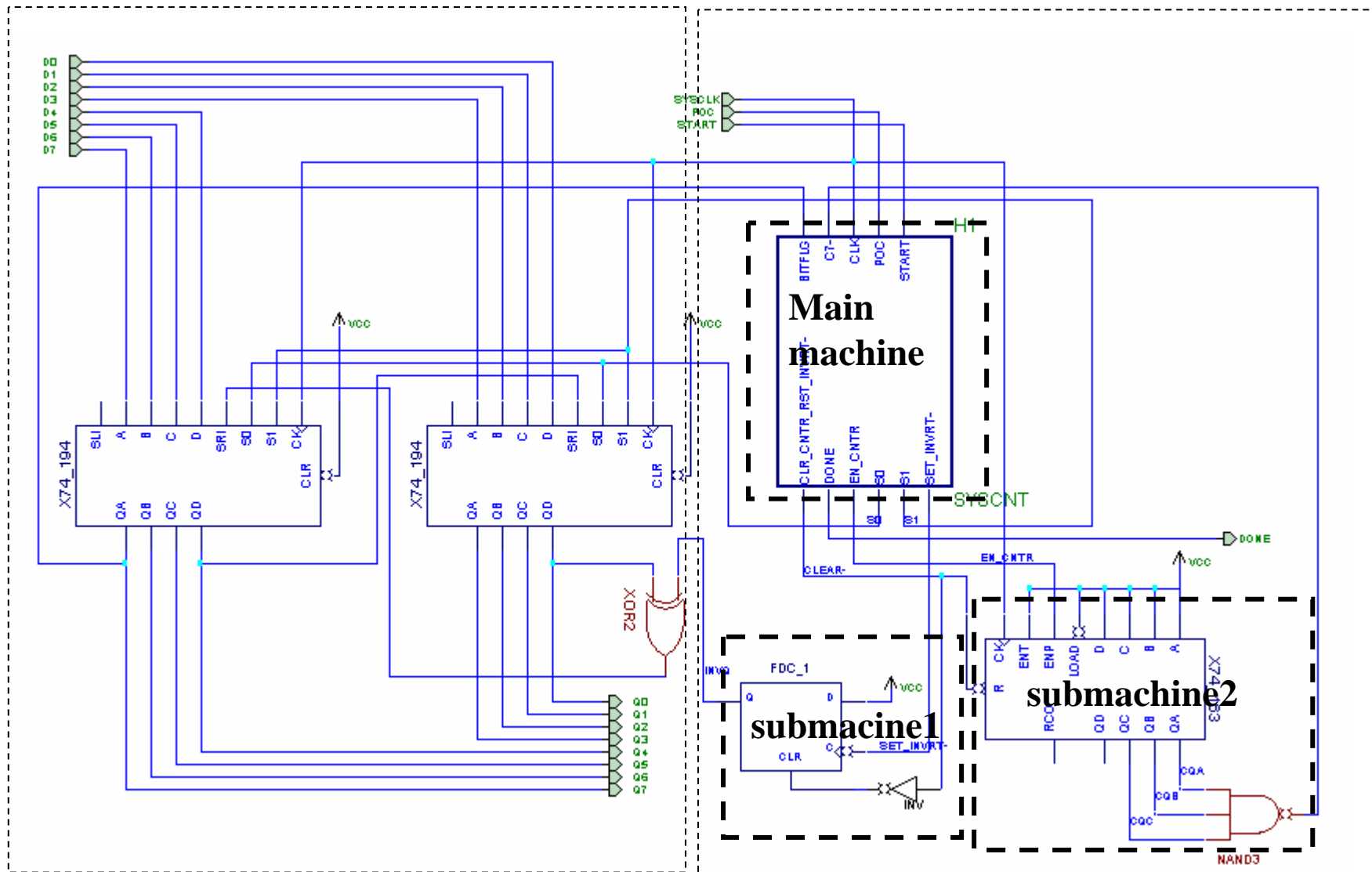

Data unit


Control unit (State Machine)

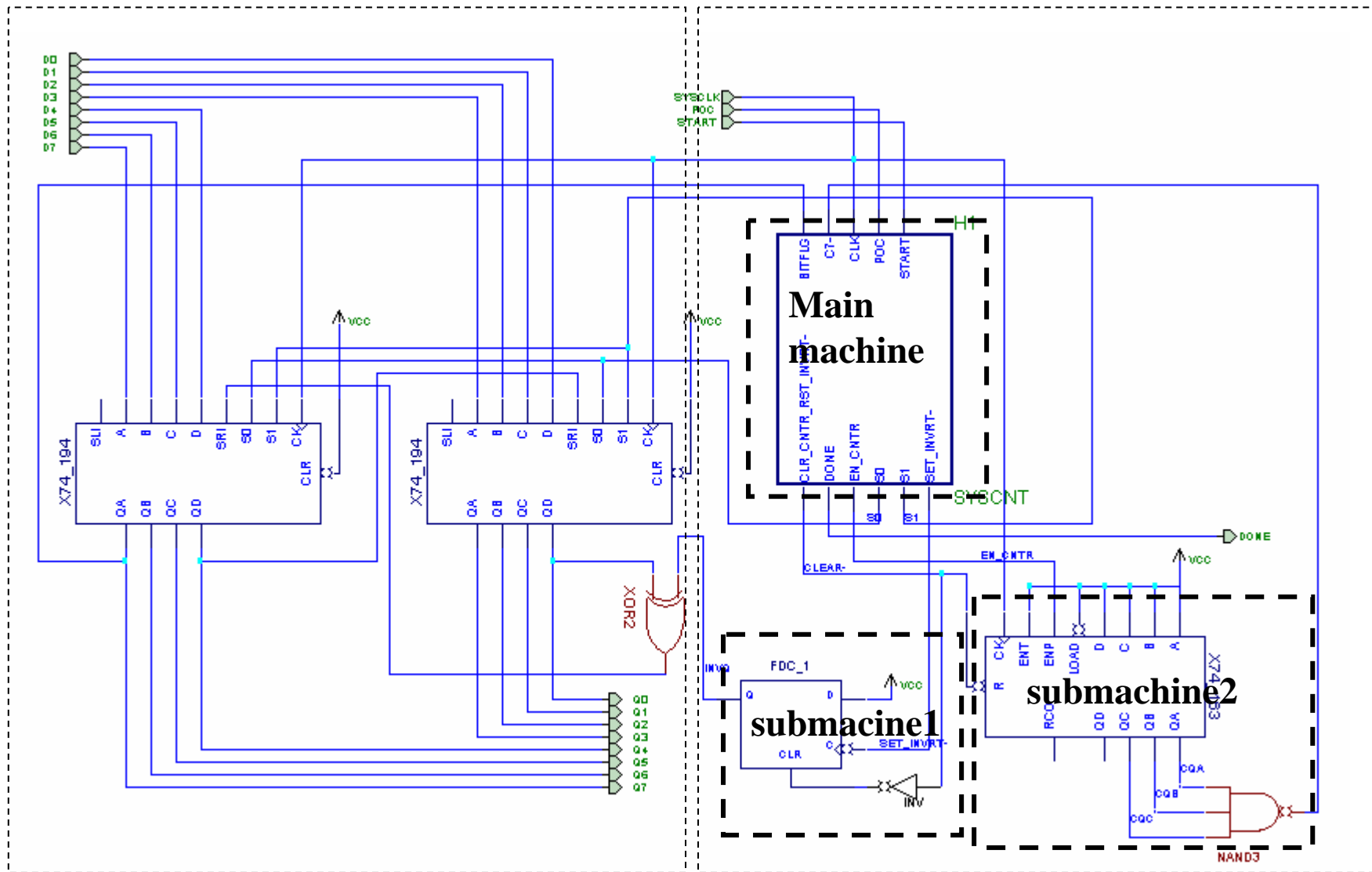Do a 3 step analysis only on
system controller



Data unit

Control unit (State Machine)

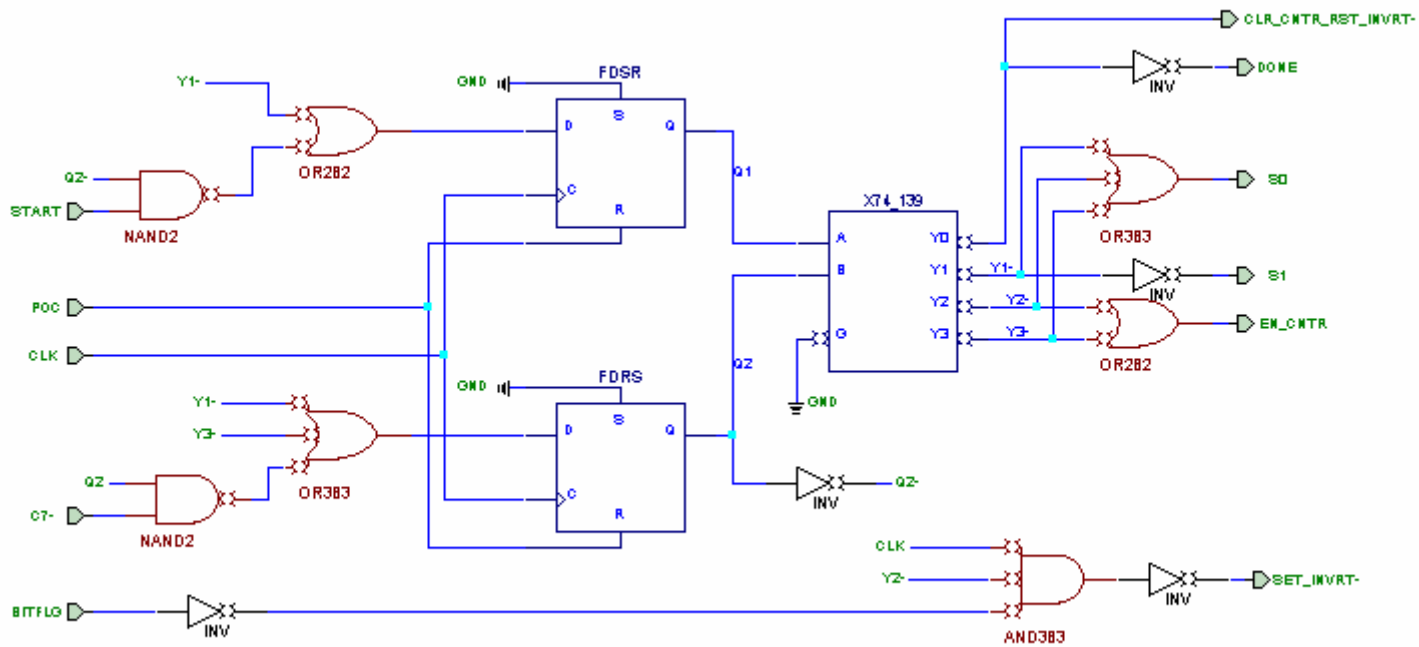

Step 1: Excitation and Output Eqs.

- Inputs?
 - External inputs (4): CLK, START, BITFLAG, C7 (ignore POC for simplification)
 - P.S. (2): Q1, Q2
- Outputs?
 - External outputs (7): CLR_CNTR, RST_INVRT, S0, S1, ENCNTR, SET_INVRT, DONE
 - N.S. (2): = Excitations D1, D2

$$D_2 = Y_1 + Y_3 + Q_2 \bar{C}_7 = Q_1 + Q_2 \bar{C}_7$$

$$D_1 = Y_1 + \bar{Q}_2 START = \bar{Q}_2 Q_1 + \bar{Q}_2 START$$

$$ENCNTR = Y_3 + Y_2 = Q_2$$

$$S_1 = Y_1 = \bar{Q}_2 Q_1$$

$$S_0 = Y_3 + Y_2 + Y_1 = Q_2 + Q_1$$

$$DONE = Y_0 = \bar{Q}_2 \bar{Q}_1$$

$$CLR_CNTR = \bar{Q}_2 \bar{Q}_1$$

$$RST_INVRT = \bar{Q}_2 \bar{Q}_1$$

$$SET_INVRT = \overline{CLK \cdot Y \cdot BITFLAG} = \overline{CLK \cdot Q_2 \bar{Q}_1 \cdot BITFLAG}$$

Why falling edge of CLK?


Can we remove CLK from SI equation? → No

1. avoid glitch on SI when transit to Y2

2. hold time on RIN (not likely the problem)

Step 2: State/Output Table

- How many rows and columns?

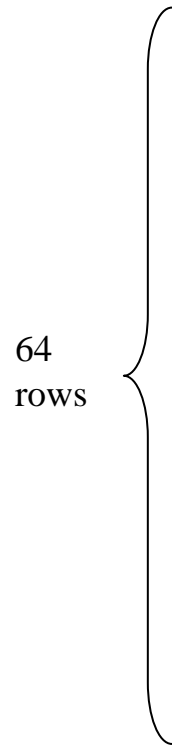P.S.		Inputs					Outputs							N.S.	
Q2	Q1	CLK	START	BFLAG	C7	EC	CC	S1	S0	RI	SI	DONE	Q2(=D2)	Q1(=D1)	
															


Step 2: State/Output Table

- Variable entered table

	P.S.		Outputs							N.S.	
	Q2	Q1	EC	CC	S1	S0	RI	SI	DONE	Q2	Q1
Y0	0	0	0	1	0	0	1	0	1	0	ST
Y1	0	1	0	0	1	1	0	0	0	1	1
Y3	1	1	1	0	0	1	0	0	0	1	0
Y2	1	0	1	0	0	1	0	↑	0	$\overline{C_7}$	0

$\overline{CLK} \cdot BITFLG$

Step 3: State Diagram

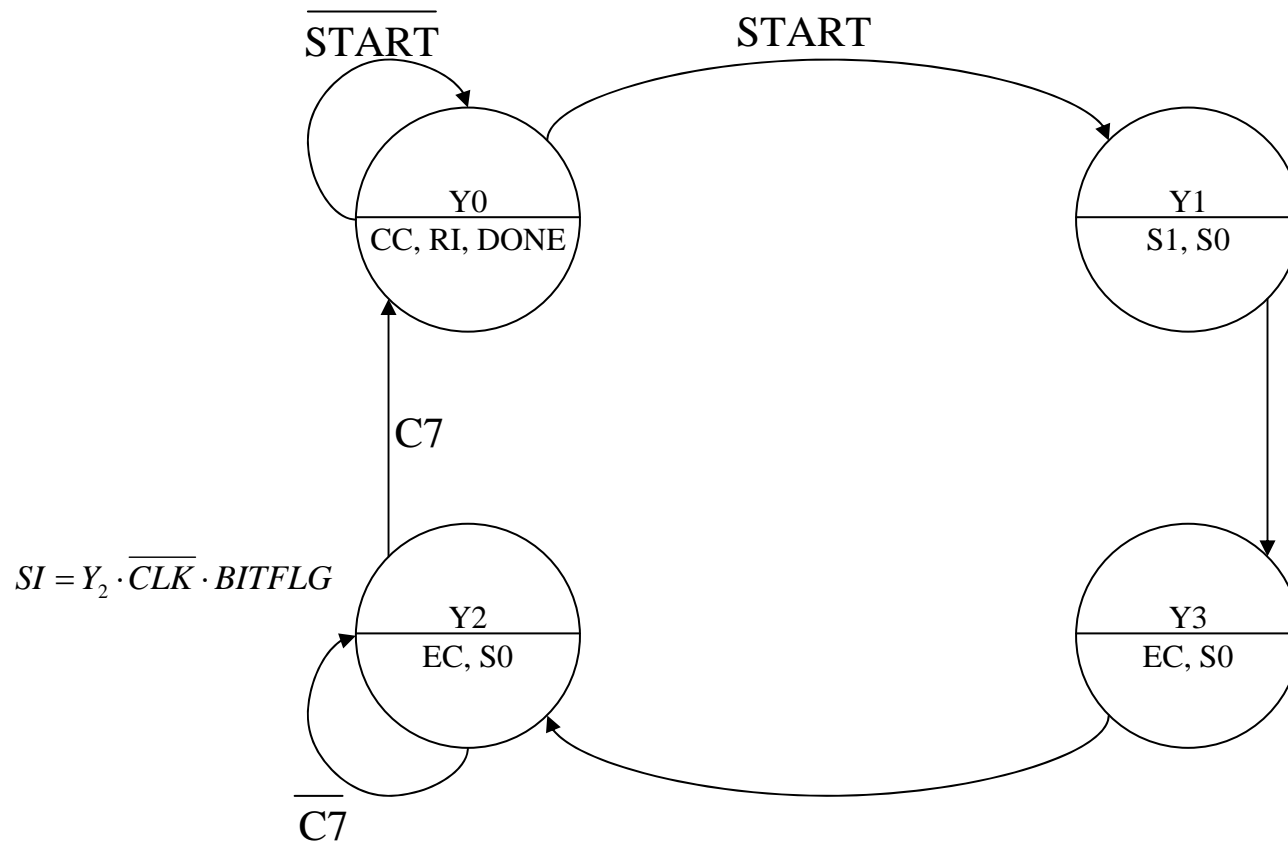


Quiz: Why we need Y3? Can we merge it with Y2?

Example

	<u>Shift register</u>	<u>State</u>	<u>Counter</u>	<u>Invert</u>	
START →	XXXXXX	Y0	-	-	
	XXXXXX	Y1	0	0	
	11001010	Y3	0	0	
	01100101	Y2	1	0	
	10110010	Y2	2	0 → 1	
	11011001	Y2	3	1	
	01101100	Y2	4	1	
	10110110	Y2	5	1	
	11011011	Y2	6	1	
	01101101	Y2	7	1	
	00110110	Y0	8	1	→
	00110110	Y0	0	0	DONE

Sample Timing Diagram

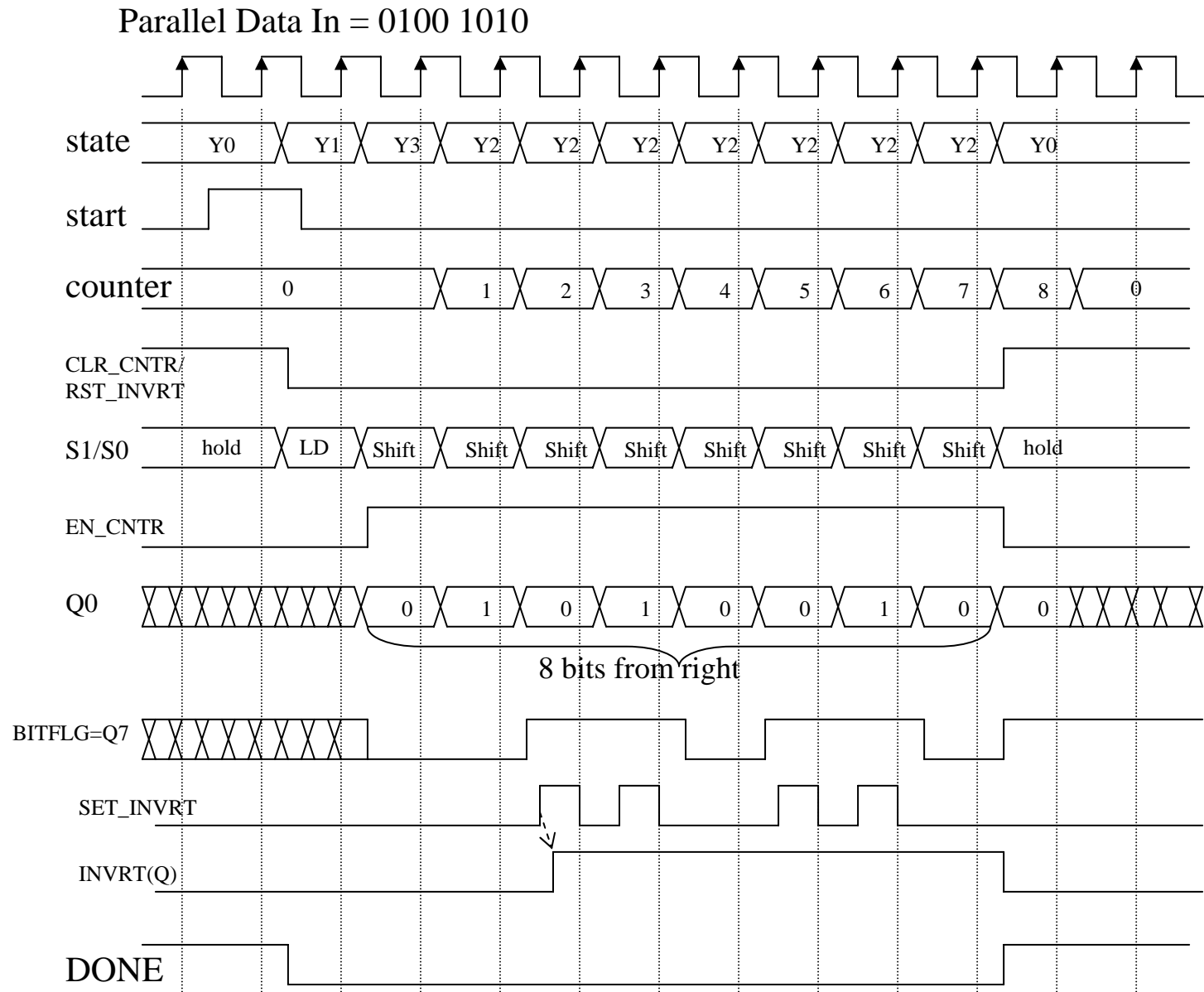

Timing Analysis

- Timing specs. for the parts we have used

Chip	tpLH(ns)	tpHL(ns)
LS00, LS04, LS10, LS27	15	15
LS86	30	22
LS139 A,B -> Y	29	38
LS139 G -> Y	24	32

LS74	tpLH	tpHL	ts	th
CLR, CLK, PR->Q	25	40		
D			20	5
fmax = 25 Mhz				

LS163	tpLH	tpHL	ts	th
CLK->Q	24	27		
CLK->RCO	35	35	20	5
ENT->RCO	14	14		
CLR->Q		28		
A,B,C,D,ENP,ENT, LD			20	0
fmax = 25 Mhz				

LS194	tpLH	tpHL	ts	th
CLR->Q		35		
CLK->Q	26	30		
S1, S0			30	
L,R,A,B,C,D			20	
All				0
fmax = 25 Mhz				

Maximum CLK frequency

- We must satisfy setup time for all f/f inputs (we will consider only D2, S0, RIN as examples)

D2 setup	Path1: $\underline{\text{CLK}} \rightarrow \underline{\text{Q2}}(\underline{\text{LS74}}) + \underline{\text{B}} \rightarrow \underline{\text{Y3}}(\underline{\text{LS139}}) + \underline{\text{Y3}} \rightarrow \underline{\text{D2}}(\underline{\text{LS10}}) + \underline{\text{D2_setup}}$ = 40+38+15+20=113ns
	Path2: $\underline{\text{CLK}} \rightarrow \underline{\text{Q2}}(\underline{\text{LS74}}) + \underline{\text{LS00}} + \underline{\text{LS10}} + \underline{\text{D2_setup}}$ = 40+15+15+20=90ns
	Path3: $\underline{\text{CLK}} \rightarrow \underline{\text{CNTR_Q}}(\underline{\text{LS163}}) + \underline{\text{CNTR_Q}} \rightarrow \underline{\text{C7}}(\underline{\text{LS10}}) + \underline{\text{LS00}} + \underline{\text{LS10}} + \underline{\text{D2_setup}}$ = 27+15+15+15+20=92ns
S0 setup	Path1: $\underline{\text{CLK}} \rightarrow \underline{\text{Q2,Q1}}(\underline{\text{LS74}}) + \underline{\text{A,B}} \rightarrow \underline{\text{Y}}(\underline{\text{LS139}}) + \underline{\text{Y}} \rightarrow \underline{\text{S0}}(\underline{\text{LS10}}) + \underline{\text{S0_setup}}$ = 40+38+15+30=123ns
RIN (=SRI: Shift Right Input of Left 'x194' setup	Path1: $\underline{\text{CLK}} \rightarrow \underline{\text{Q0}}(\underline{\text{LS194}}) + \underline{\text{LS86}} + \underline{\text{RIN_setup}}$ = 30+30+20=80ns
	Path2: $\underline{\text{CLK}}(\text{falling edge}) \rightarrow \underline{\text{SI}}(\underline{\text{LS27,LS04}}) + \underline{\text{SI}} \rightarrow \underline{\text{INVQ}}(\underline{\text{LS74}}) + \underline{\text{LS86}} + \underline{\text{RIN_setup}}$ = 15+15+25(40?)+30+20=105(120?)ns $\rightarrow \frac{1}{2} \text{ tclk} > 105(120?)\text{ns} \rightarrow 210(240?)\text{ns}$


$$\text{Max clk frequency} = 1/210\text{ns} = 4.8\text{Mhz}$$

If we use the pure maximum value approach,


$$\text{Max clk frequency} = 1/240\text{ns} = 4.2\text{Mhz}$$

Setup and Hold time specifications on START

- t_s for START

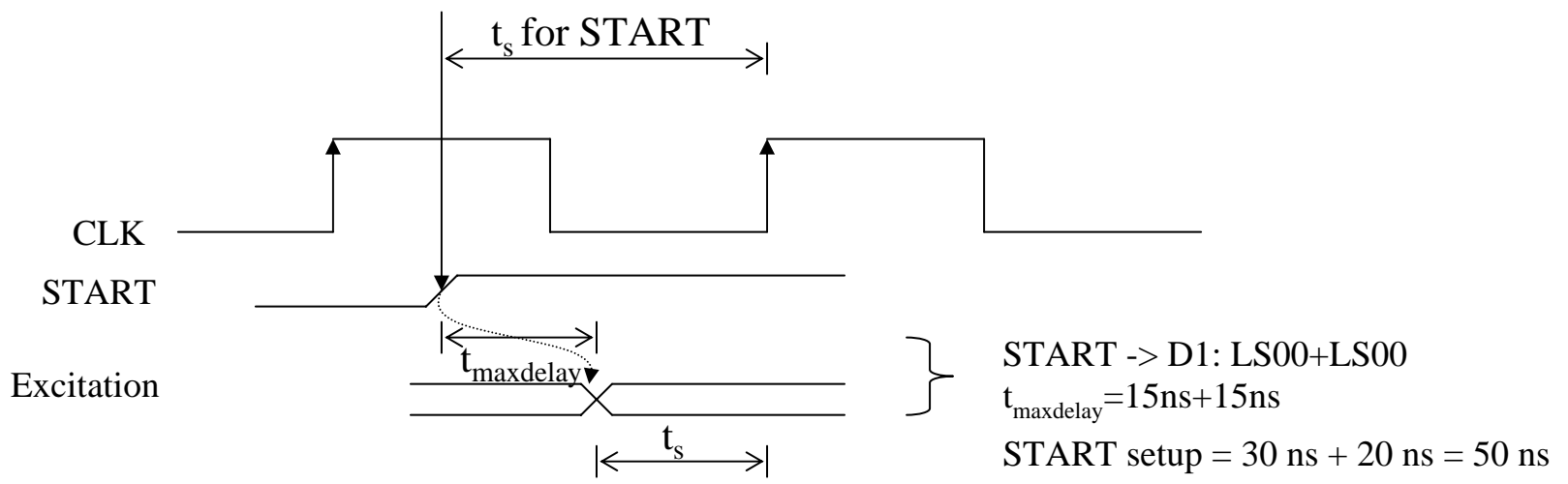


- t_h for START

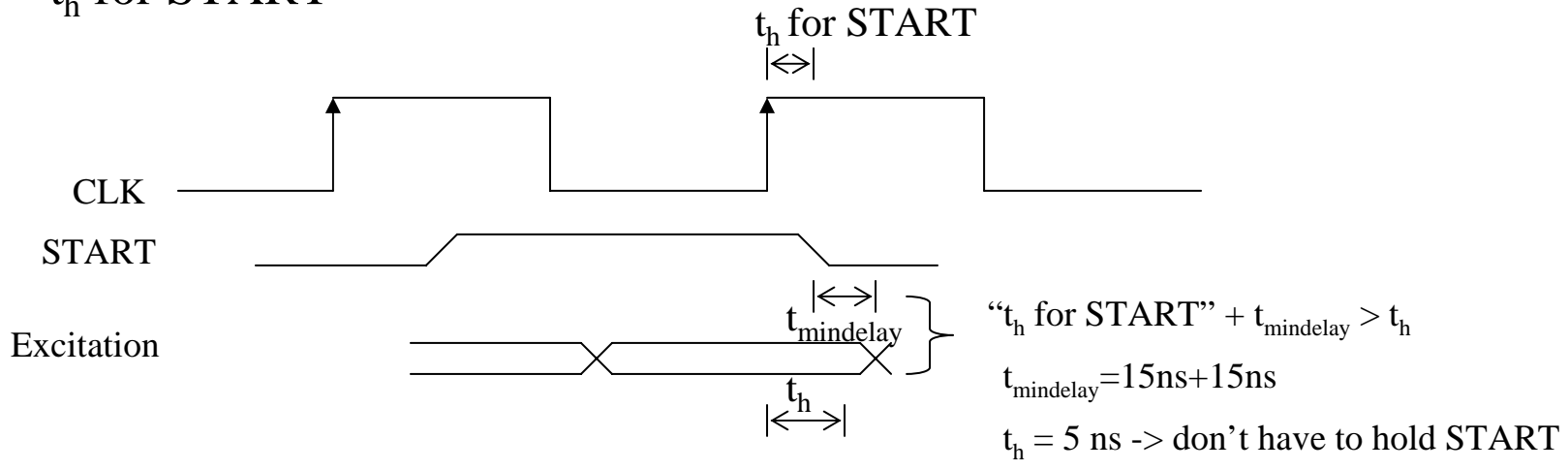

 Problem Statement

- Design 74x166 – 8 bit parallel-in, serial-out shift register with enable



CLR – Asynchronous

EN – when asserted -> according to LD

otherwise -> hold

LD – when asserted -> LD

otherwise -> Shift

Step 1: State/Output Table

- A state table (or diagram) isn't very helpful since LD can take you from any state to any other -> messy!

– Inputs:	A-H	8	}	2^{20} rows!
	SER	1		
	CLR	1		
	EN	1		
	LD	1		
State variables:	Qs	8		

Alternatives

- CLR asynchronous – not needed
- EN – take care in special way
 - initially assume always asserted
- Think 2 bits rather than 8 bits and then generalize
- Variables: SER, A, B, LD, Q_A , Q_B → still $2^6=64$ rows! → “Variable Entered Table”

Variable-Entered Table

Q_A	Q_B	LD	Q_A	Q_B
0	0	0	SER	0
0	0	1	A	B
0	1	0	SER	0
0	1	1	A	B
1	0	0	SER	1
1	0	1	A	B
1	1	0	SER	1
1	1	1	A	B

Steps 2-6

- Step 2: state minimization – not relevant
- Step 3: state assignment – not relevant
- Step 4: Transit/output table – we already have
- Step 5: Choose f/f – D f/f
- Step 6: Excitation table – same as transit table

Steps 7-8: Excitation/Output Eqs. (Variable Entered Map)

D_A

$Q_A Q_B$	LD	
	0	1
00	SER	A
01	SER	A
11	SER	A
10	SER	A


$$D_A = \overline{LD} \cdot SER + LD \cdot A$$

D_B


$Q_A Q_B$	LD	
	0	1
00	0	B
01	0	B
11	1	B
10	1	B

$$D_B = \overline{LD} \cdot Q_A + LD \cdot B$$


Steps 9: Logic Diagram

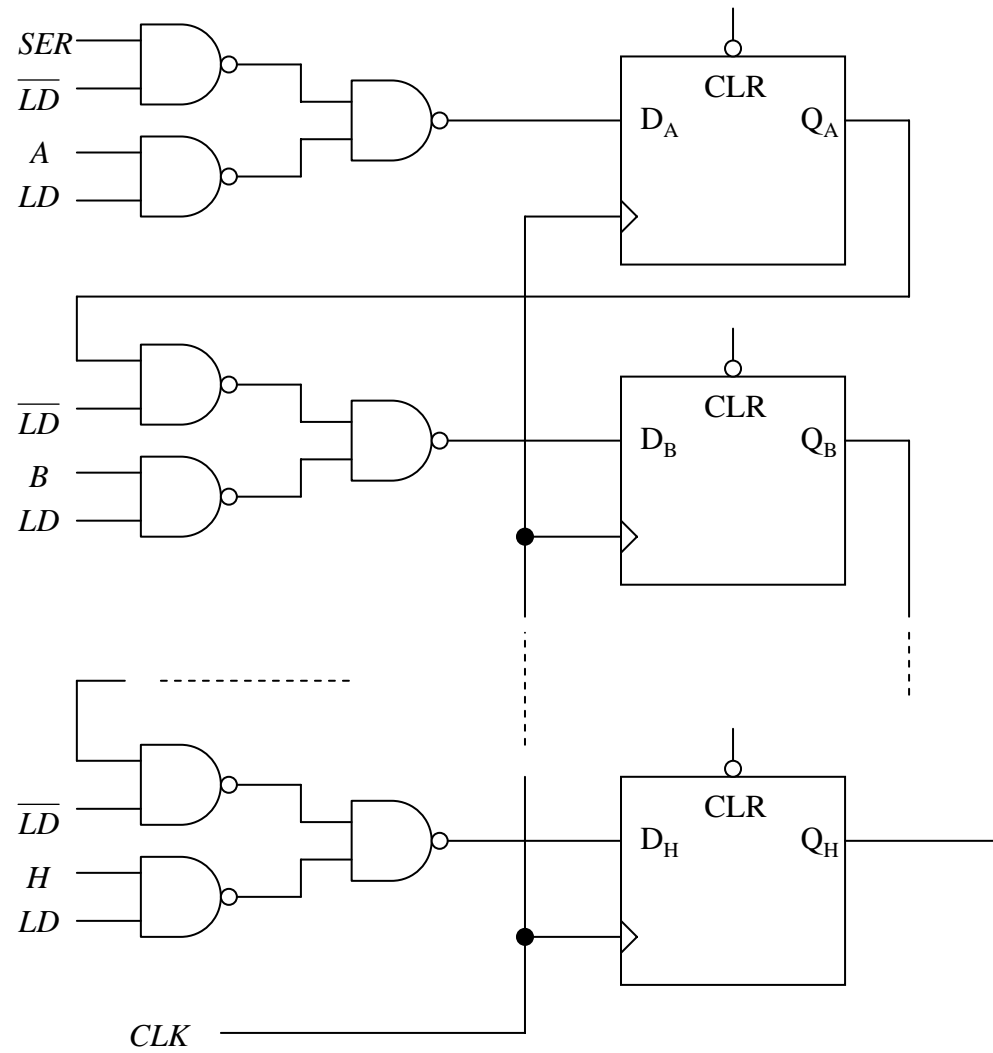


Steps 9: Logic Diagram

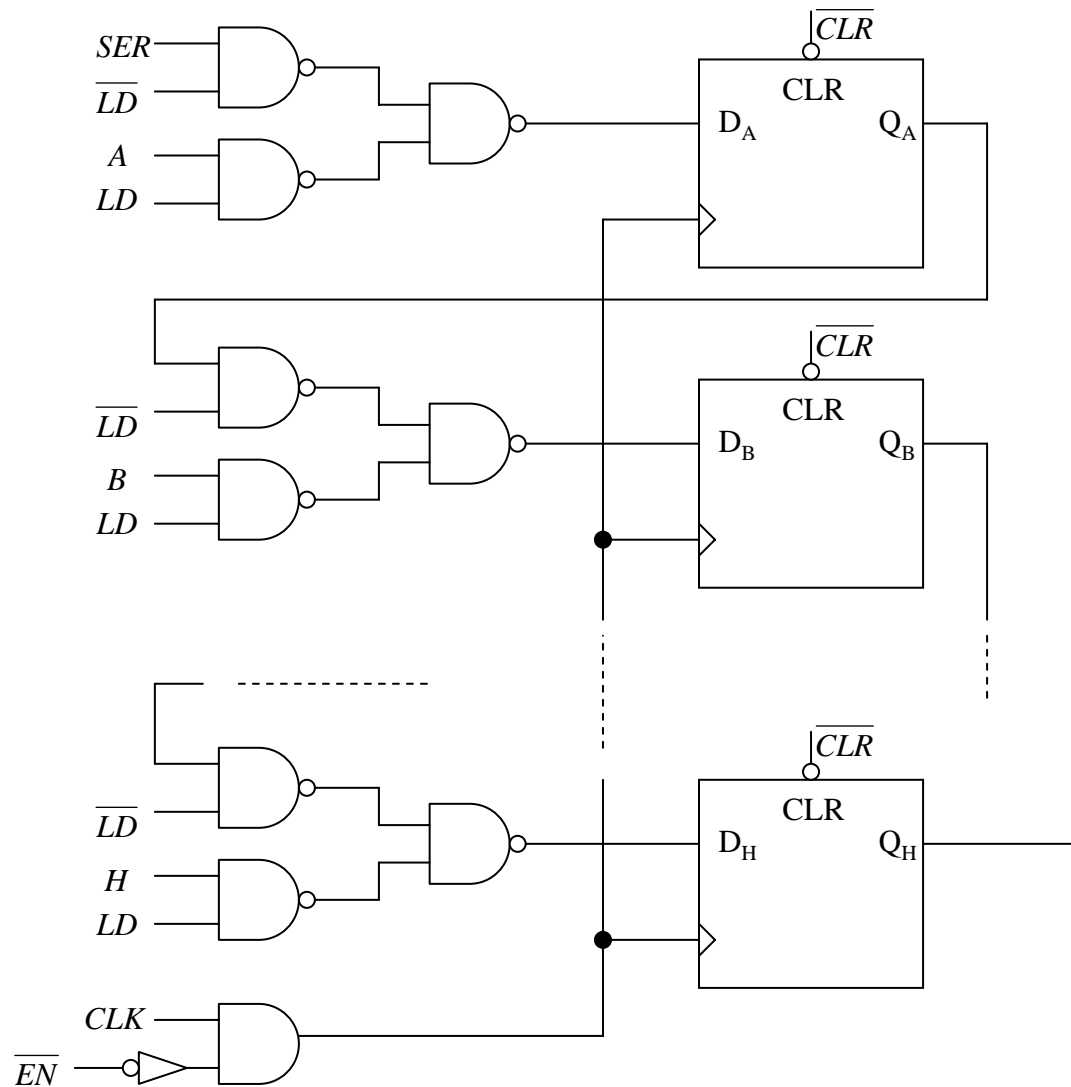

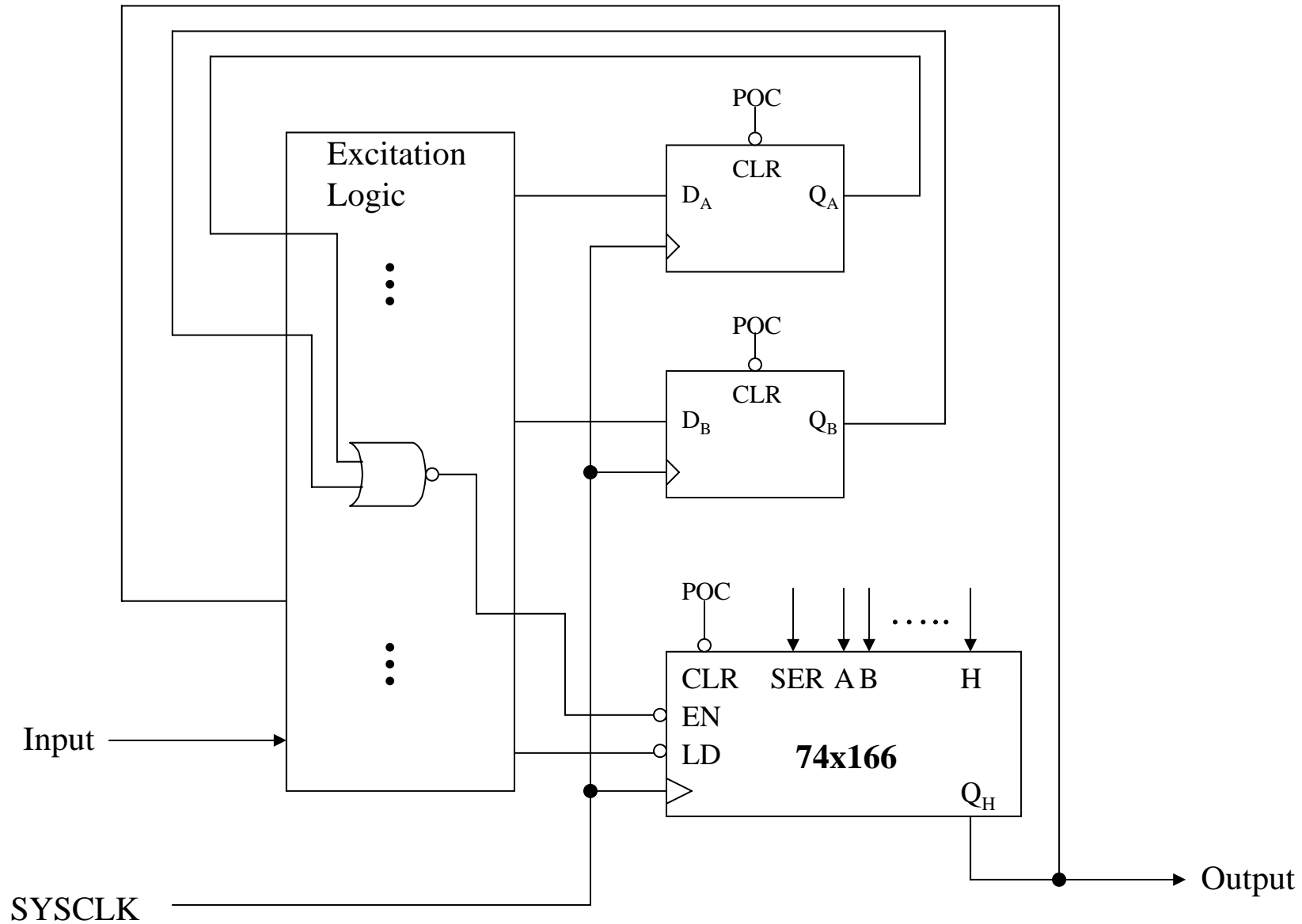
Remind (General Sequential Circuit Structure)



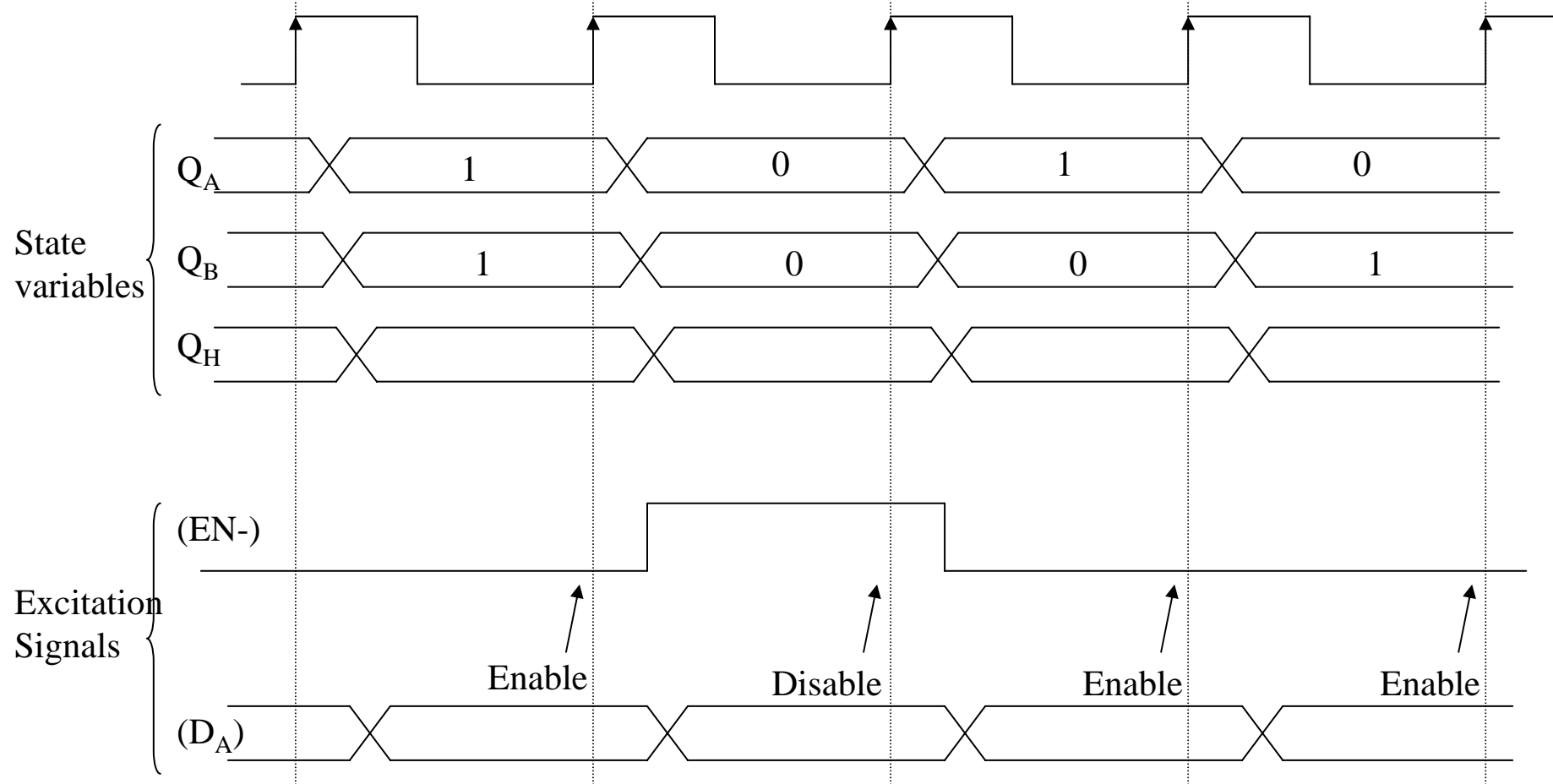Remind (General Sequential Circuit Timing)




Gating the CLK

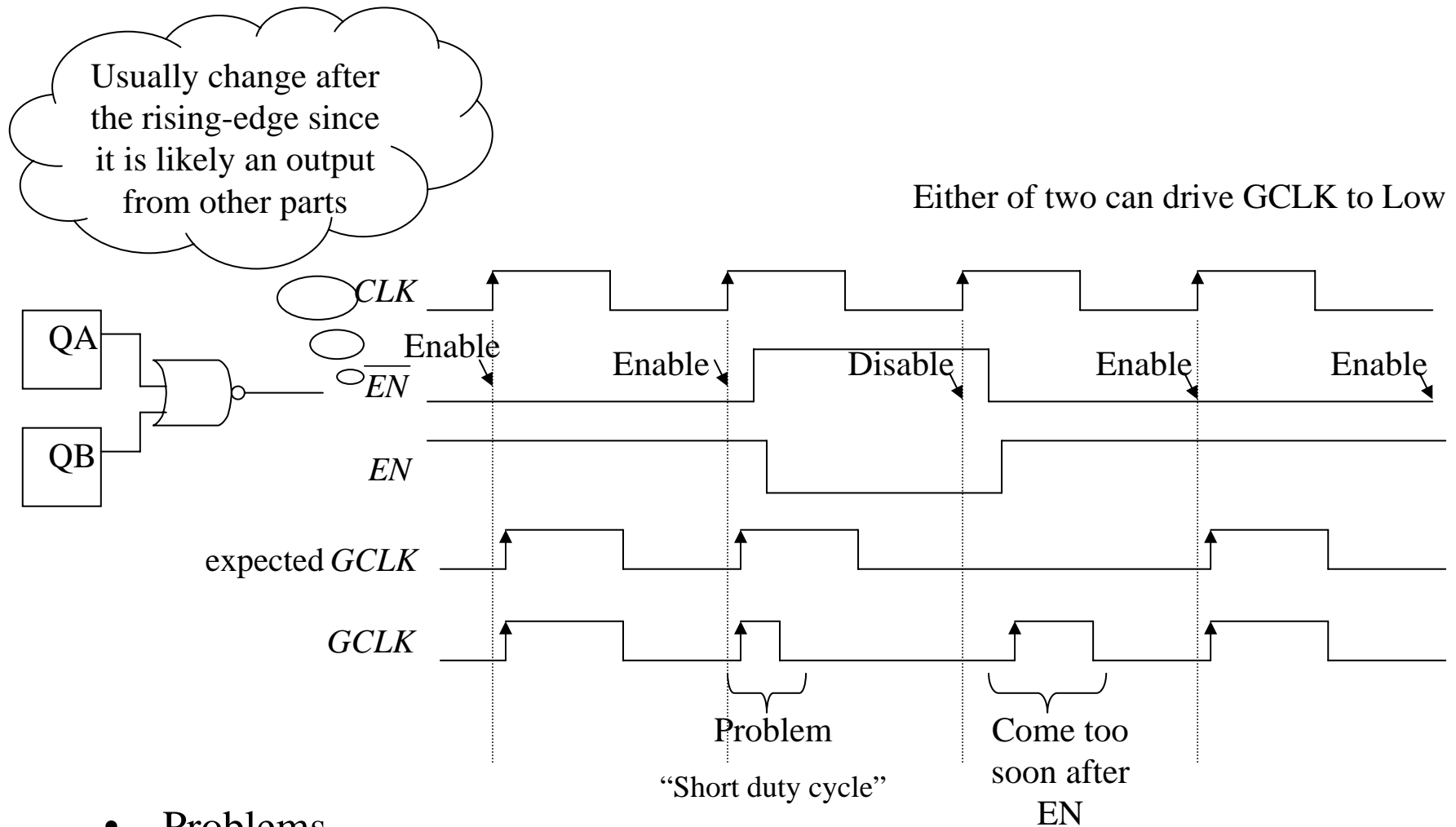

Different approach to holding

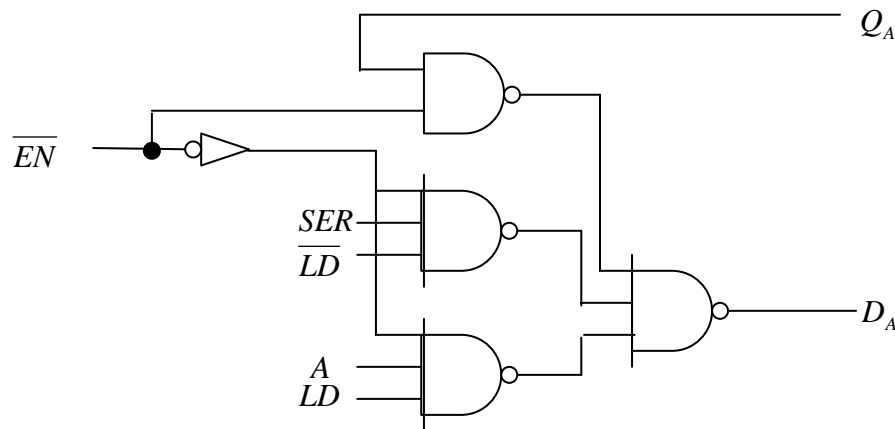- Delay in CLK line is not good design practice
 - Puts in CLK skew
 - All f/f CLKs don't triggered at same time → eliminates the good points to use synchronous design (we can ignore a lot of difficult timing issues)
- Desired: “Synchronous function-enable input”
 - EN should sampled along with data at CLK edge





Clock Skew

- Clock skew: difference between arrival times of CLK at different devices
- Caused by
 - Gating in the CLK line
 - Delay along long lines (1ns/ft – speed of light) – CAD serial routing

Clock Skew

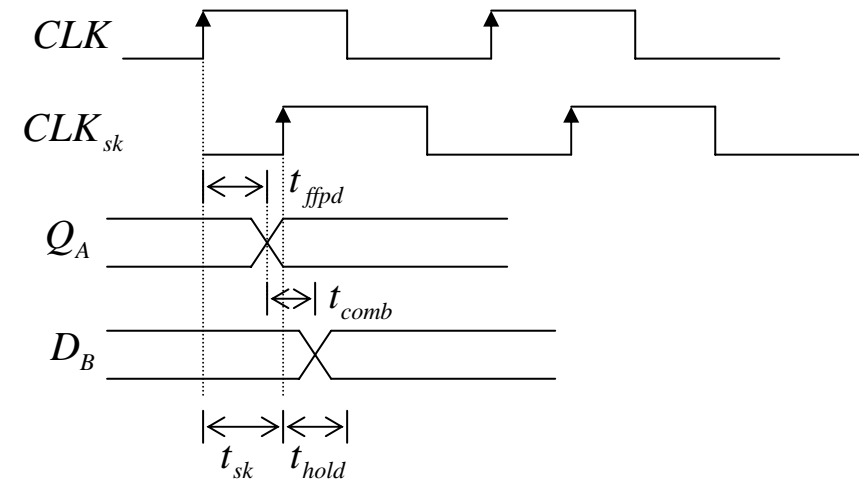 - Problem

- If t_{sk} too long – CLK edge get to B f/f after D_B changes => Wrong operations
- In general – hold time on D_B can be violated



$$t_{ffpd}(\text{min}) + t_{comb}(\text{min}) > t_{sk} + t_h$$

t_{sk} max?: use timing specs

$$x74 (25\text{ns}) + x00 (9\text{ns}) + x10 (9\text{ns}) - x74\text{hold} (5\text{ns}) = 38\text{ns}$$