


Chapter 13 Output Stages and Power Amplifiers

- **13.1 General Considerations**
- **13.2 Emitter Follower as Power Amplifier**
- **13.3 Push-Pull Stage**
- **13.4 Improved Push-Pull Stage**
- **13.5 Large-Signal Considerations**
- **13.6 Short Circuit Protection**
- **13.7 Heat Dissipation**
- **13.8 Efficiency**
- **13.9 Power Amplifier Classes**

Why Power Amplifiers?

- **Drive a load with high power.**
- **Cellular phones need 1W of power at the antenna.**
- **Audio systems deliver tens to hundreds of watts of power.**
- **Ordinary Voltage/Current amplifiers are not suitable for such applications**

Chapter Outline

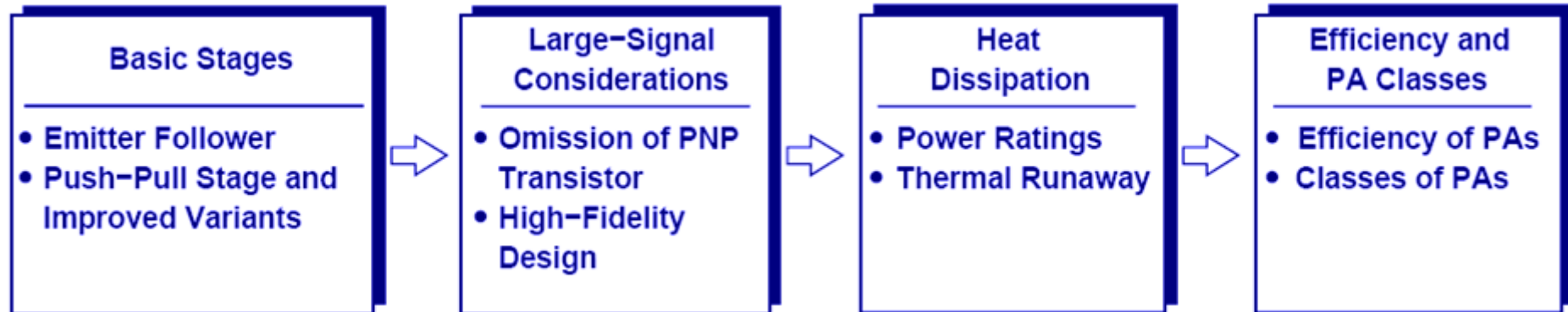

Power Amplifier Characteristics

- **Experiences low load resistance.**
- **Delivers large current levels.**
- **Requires large voltage swings.**
- **Draws a large amount of power from supply.**
- **Dissipates a large amount of power, therefore gets “hot”.**



Power Amplifier Performance Metrics

➤ **Distortion - Nonlinearity**

➤ **Power Efficiency** $\eta = \frac{\text{Power Delivered to Load}}{\text{Power Drawn from Supply}}$

➤ **Voltage Rating – Transistor Breakdown voltage**

Emitter Follower Large-Signal Behavior I

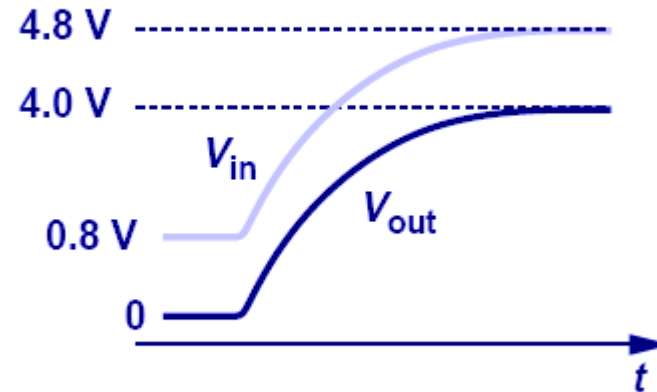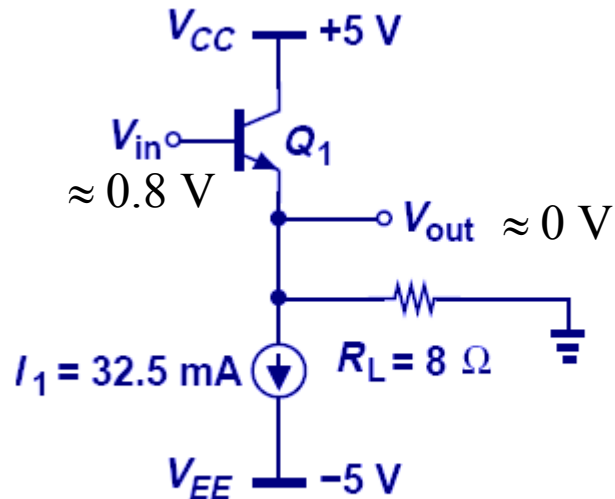

(a)

$$A_v = R_L / (R_L + 1/g_m)$$

For $R_L = 8 \Omega$,

$$\therefore g_m = \frac{I_C}{V_T}$$


$1/g_m = 0.8 \Omega$, thus, $I_C = 32.5 \text{ mA}$

(b)


➤ As V_{in} increases V_{out} also follows and Q_1 provides more current.

➤ If V_{in} rises from 0.8 V to 4.8V, $V_{out} = 4.0\text{V}$, $I_L = 500\text{mA}$

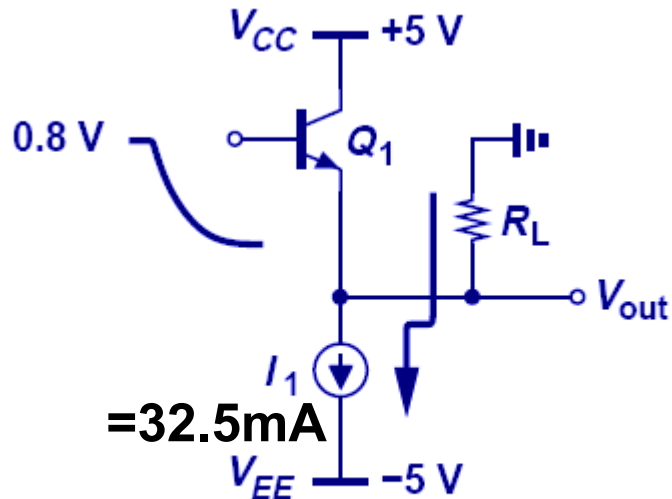Emitter Follower Large-Signal Behavior II



(c)

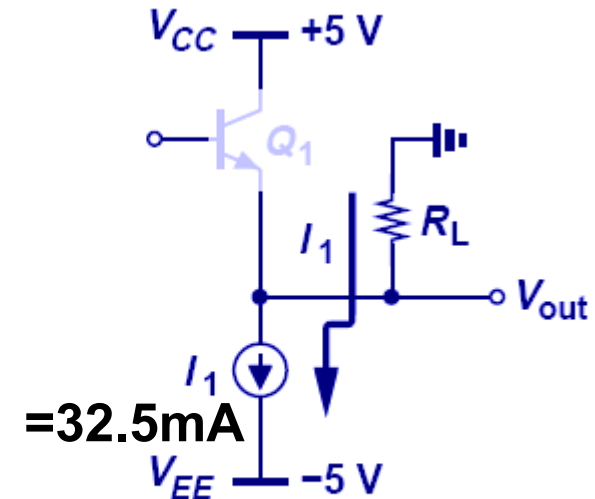

(d)

➤ However, as V_{in} decreases, V_{out} also decreases, shutting off Q_1 and resulting in a constant V_{out} .


➤ For $V_{in} = 0.8\text{ V}$, $V_{out} = 0\text{ V}$, $I_L = 0\text{ mA}$, $I_{E1} = 32.5\text{ mA}$

➤ For $V_{in} \approx 0.7\text{ V}$, $V_{out} \approx -0.1\text{ V}$, $I_L = 12.5\text{ mA}$, $I_{C1} \approx I_{E1} = 20\text{ mA}$

➤ When all current (32.5 mA) flows to the load, $V_{out} = -0.26\text{ V}$

Example 13.1: Emitter Follower

➤ $V_{in} = 0.5V$, $V_{out} = ?$

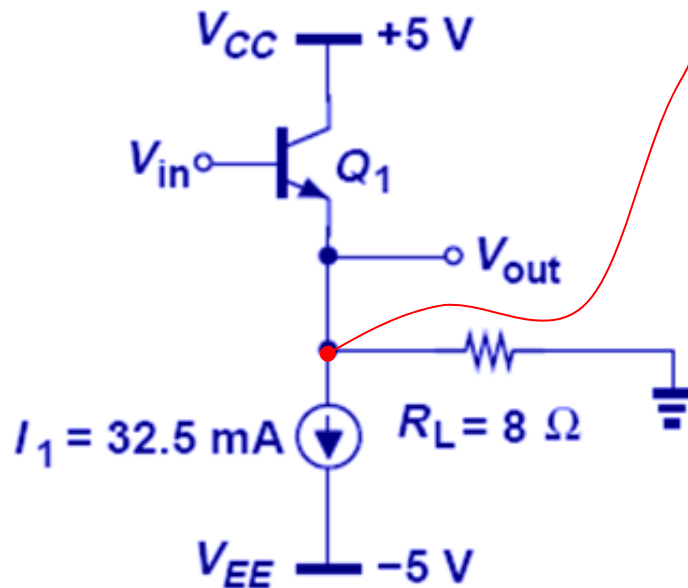

By KCL

By KVL

$$V_{in} - V_{BE1} = V_{out}, \quad \frac{V_{out}}{R_L} + I_1 = I_{C1}$$

$$V_{BE1} = V_T \ln(I_{C1} / I_S)$$


$$V_{in} - V_T \ln \left[\left(\frac{V_{out}}{R_L} + I_1 \right) \frac{1}{I_S} \right] = V_{out}$$

For $V_{in} = 0.5 V$

$\Rightarrow V_{out} \approx -211 \text{ mV}$ by a few iterations

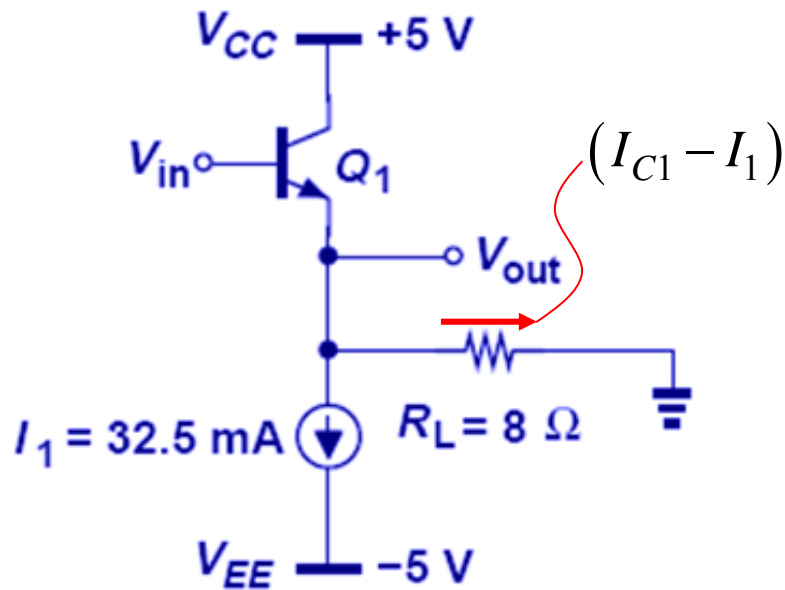Example 13.1: Emitter Follower



➤ For what V_{in} , Q_1 carries only 1% of I_1 ?



$$V_{in} = V_T \ln \frac{I_{C1}}{I_S} + (I_{C1} - I_1) R_L$$


$$\begin{aligned} \text{For } I_{C1} &\approx 0.01 \cdot I_1 \\ \Rightarrow V_{in} &\approx 390 \text{ mV} \end{aligned}$$

Linearity of an Emitter Follower

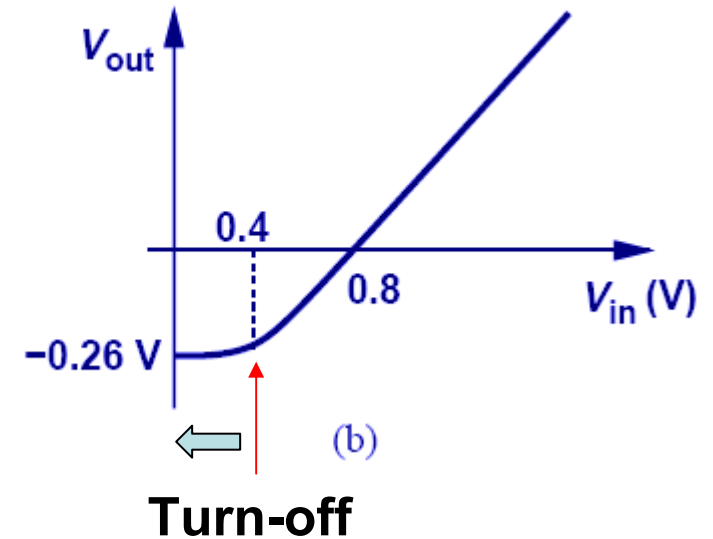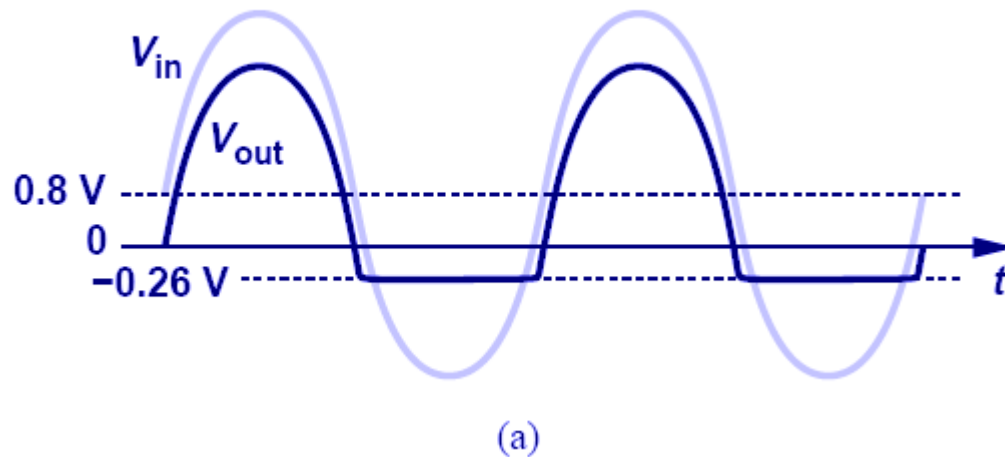


- As V_{in} decreases the output waveform will be clipped, introducing nonlinearity in I/O characteristics.

Push-Pull Stage

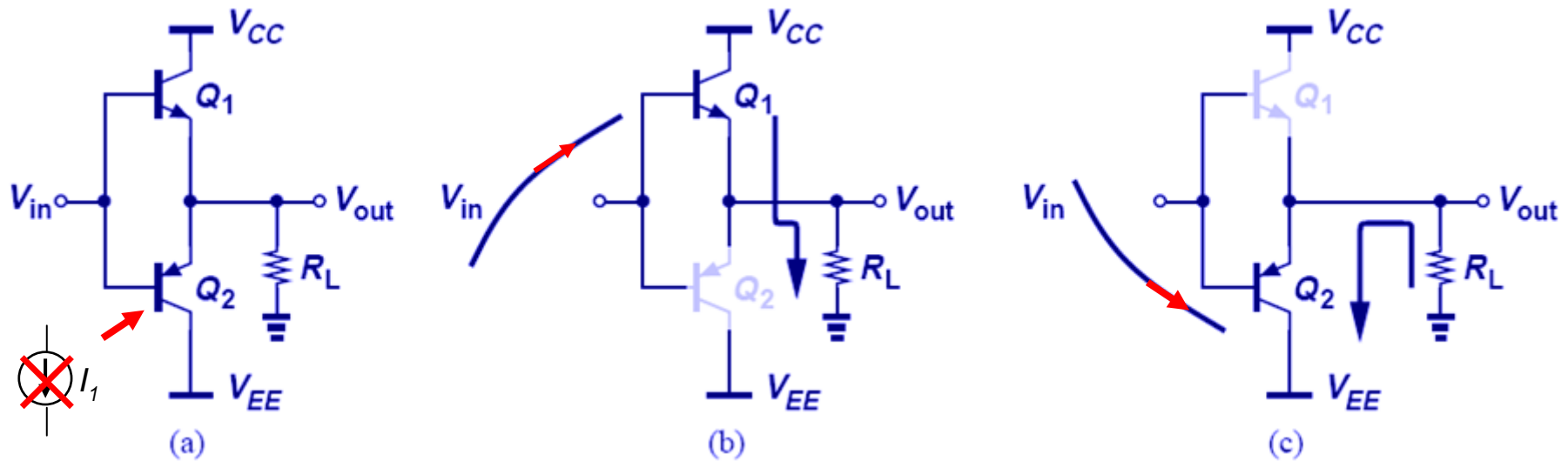

- As V_{in} increases, Q_1 is on and pushes current into R_L .
- As V_{in} decreases, Q_2 is on and pulls current out of R_L .

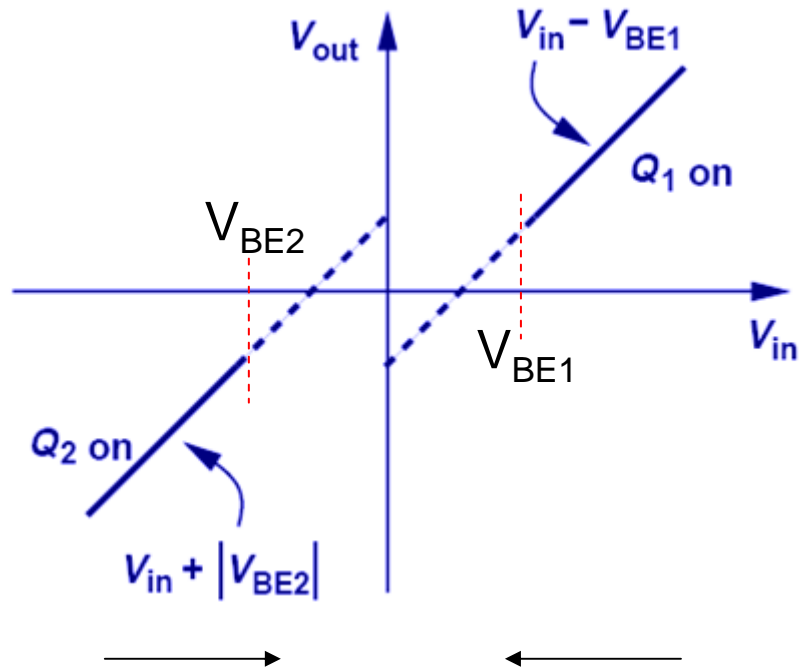Example 13.2: I/O Characteristics for Large V_{in}




$$V_{out} = V_{in} - V_{BE1} \quad \text{for large } +V_{in}$$

$$V_{out} = V_{in} + |V_{BE2}| \quad \text{for large } -V_{in}$$

- For positive V_{in} , Q_1 shifts the output down and for negative V_{in} , Q_2 shifts the output up.

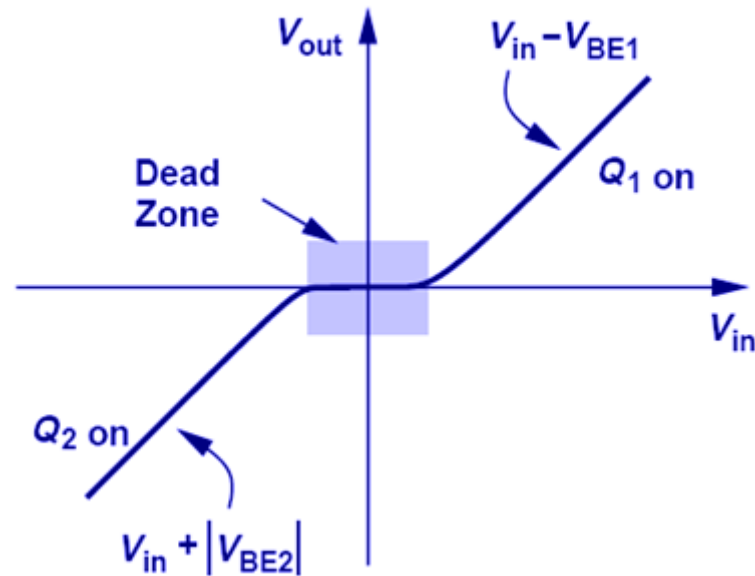
Overall I/O Characteristics of Push-Pull Stage



At least $V_{BE} \approx 600 \sim 700$ mV before BJT turns on


- However, for small V_{in} , there is a “dead zone” (both Q_1 and Q_2 are off) in the I/O characteristic, resulting in gross nonlinearity.

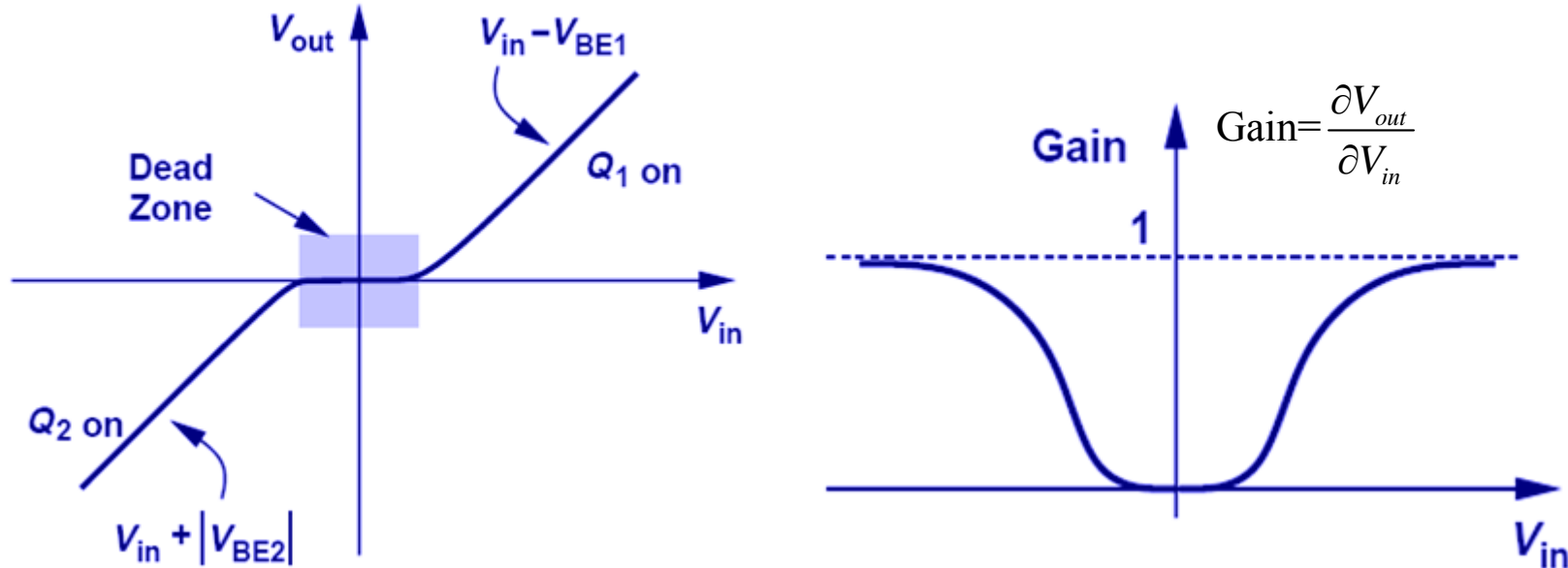Example 13.3: Small-Signal Gain of Push-Pull Stage



- The push-pull stage exhibits a gain that tends to unity when either Q_1 or Q_2 is on.
- When V_{in} is very small, the gain drops to zero.

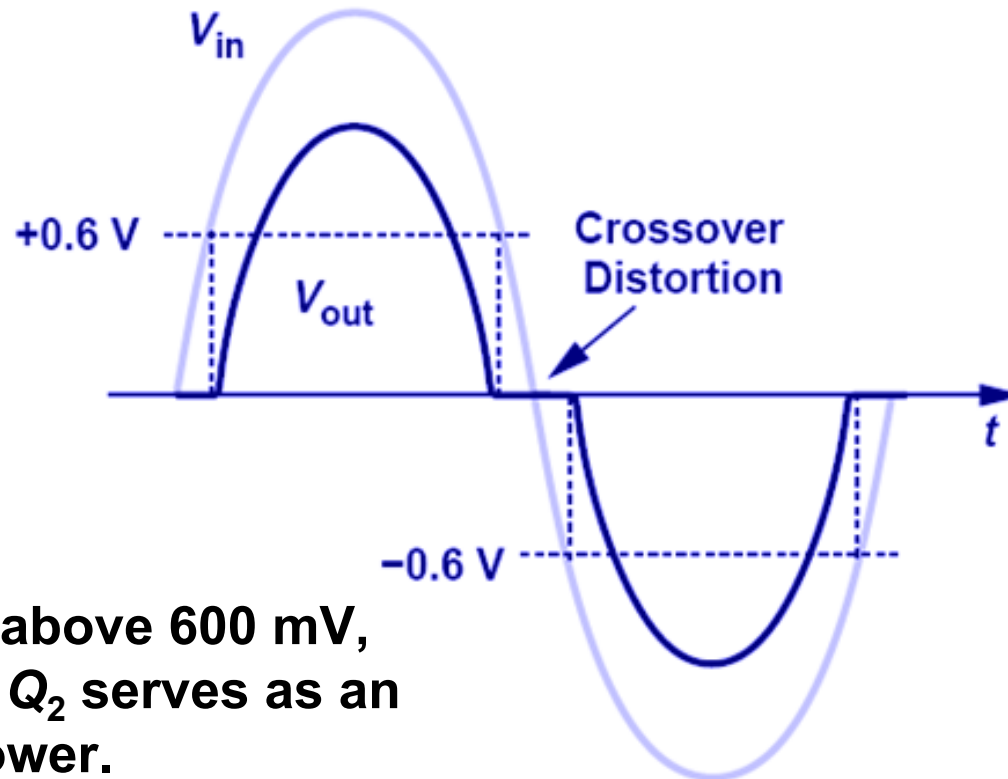Example 13.4: Sinusoidal Response of Push-Pull Stage





For V_{in} well above 600 mV, either Q_1 or Q_2 serves as an emitter follower.

Within the dead zone, $V_{out} \approx 0\text{ V}$

- For large V_{in} , the output follows the input with a fixed DC offset, however as V_{in} becomes small the output drops to zero and causes "Crossover Distortion."

Improved Push-Pull Stage

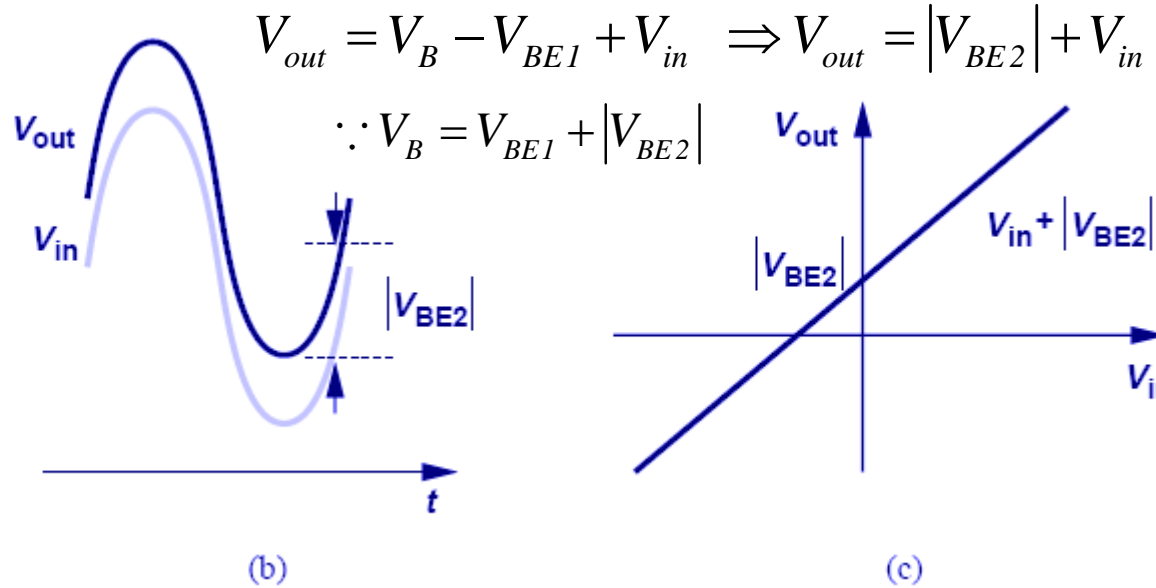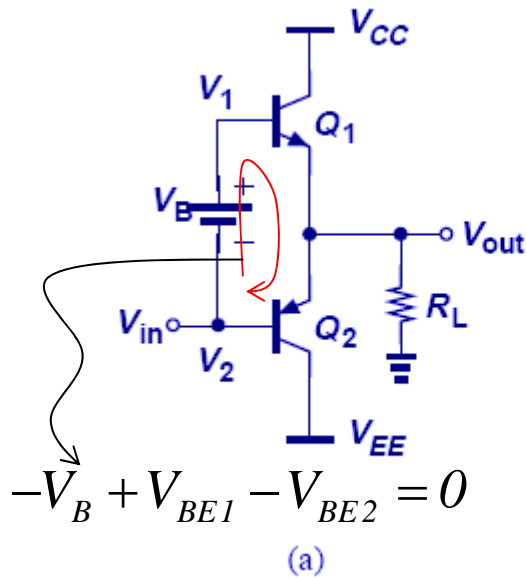

If Q_1 is to remain on,
then $V_1 = V_{out} + V_{BE1}$


If Q_2 is to remain on,
then $V_2 = V_{out} - |V_{BE2}|$

$$\begin{aligned} V_B &= V_1 - V_2 \\ &= V_{BE1} + |V_{BE2}| \end{aligned}$$

$$V_B = V_{BE1} + |V_{BE2}|$$


➤ With a battery of V_B inserted between the bases of Q_1 and Q_2 , the dead zone is eliminated.

Implementation of V_B

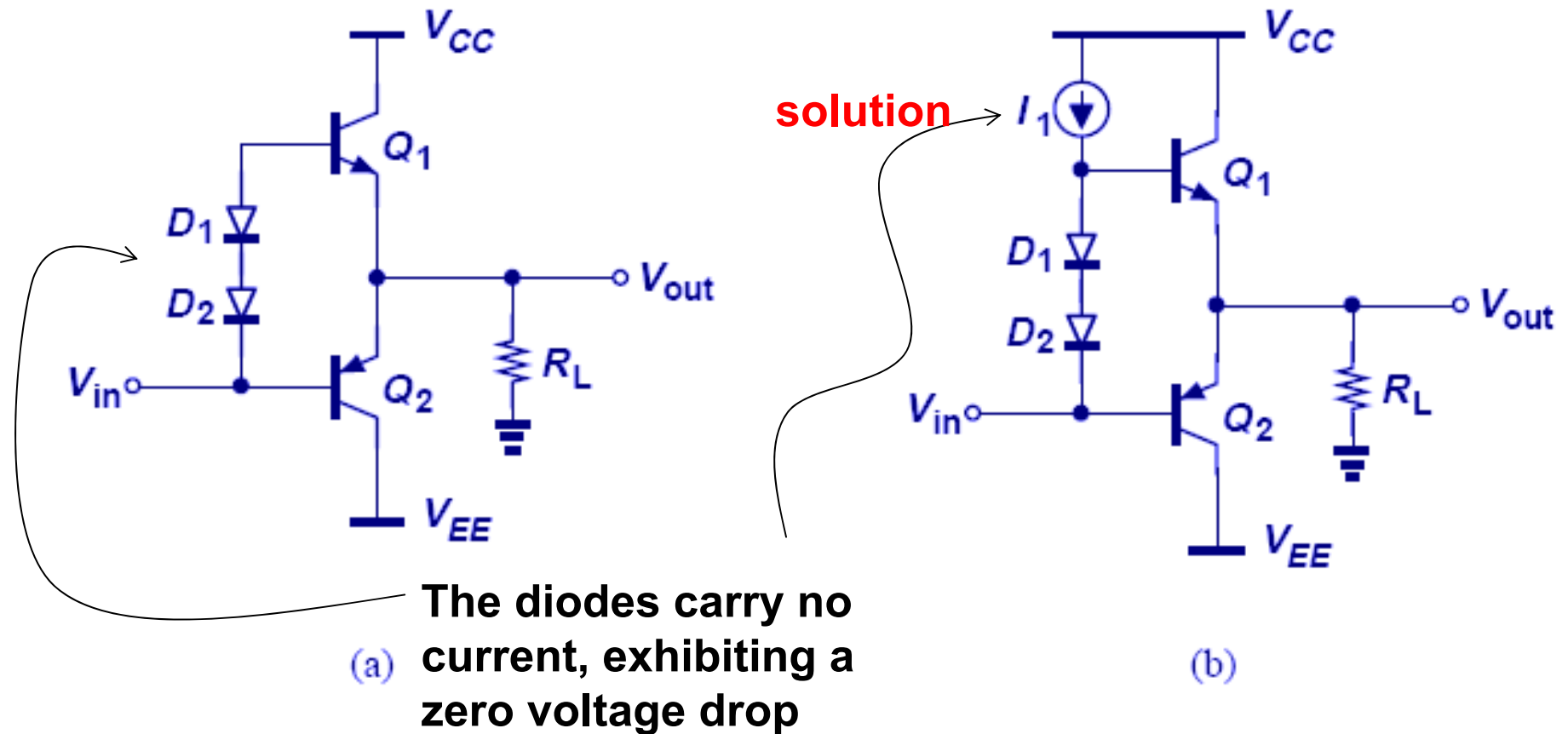

- Since $V_B = V_{BE1} + |V_{BE2}|$, a natural choice would be two diodes in series.
- I_1 in figure (b) is used to bias the diodes and Q_1 .

Example 13.6: Current Flow I

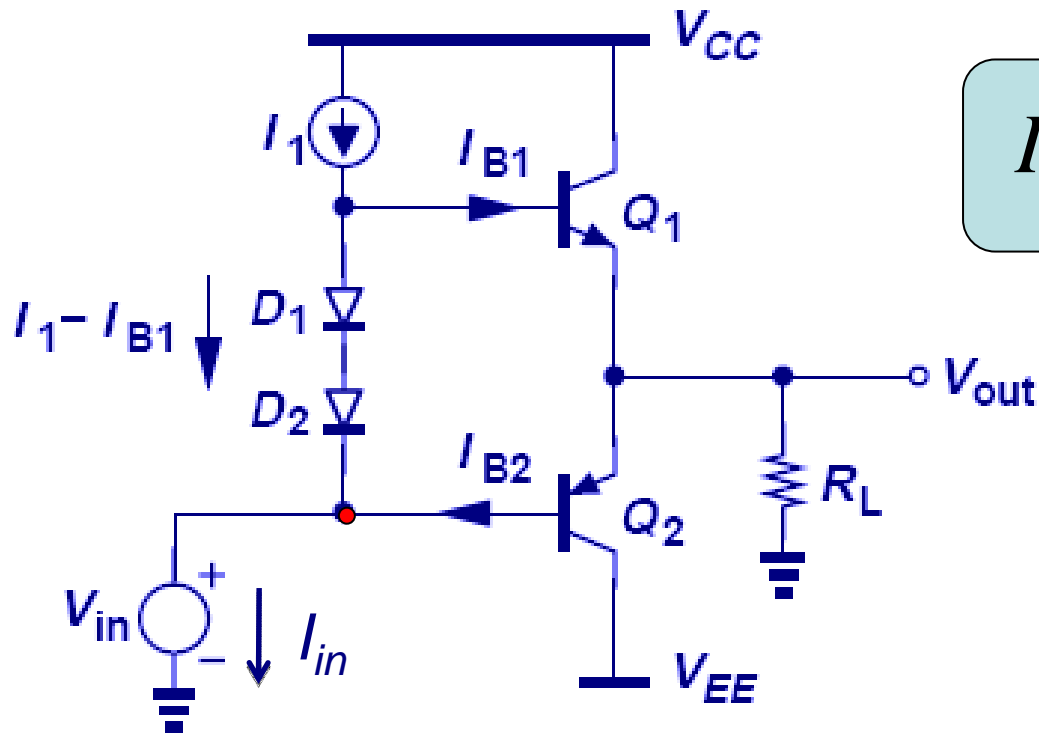

$$I_{in} = I_1 - I_{B1} + |I_{B2}|$$

When $V_{out} = 0$ V, I_L through R_L is 0. Then


$$I_{C1} = |I_{C2}|$$

$$\text{if } \beta_1 = \beta_2, I_{B1} = |I_{B2}|$$

Usually $I_{B1} \neq |I_{B2}|$ unless $V_{out} = 0$

I_{in} flows even when $V_{out} = 0$.

Example 13.8: Current Flow II

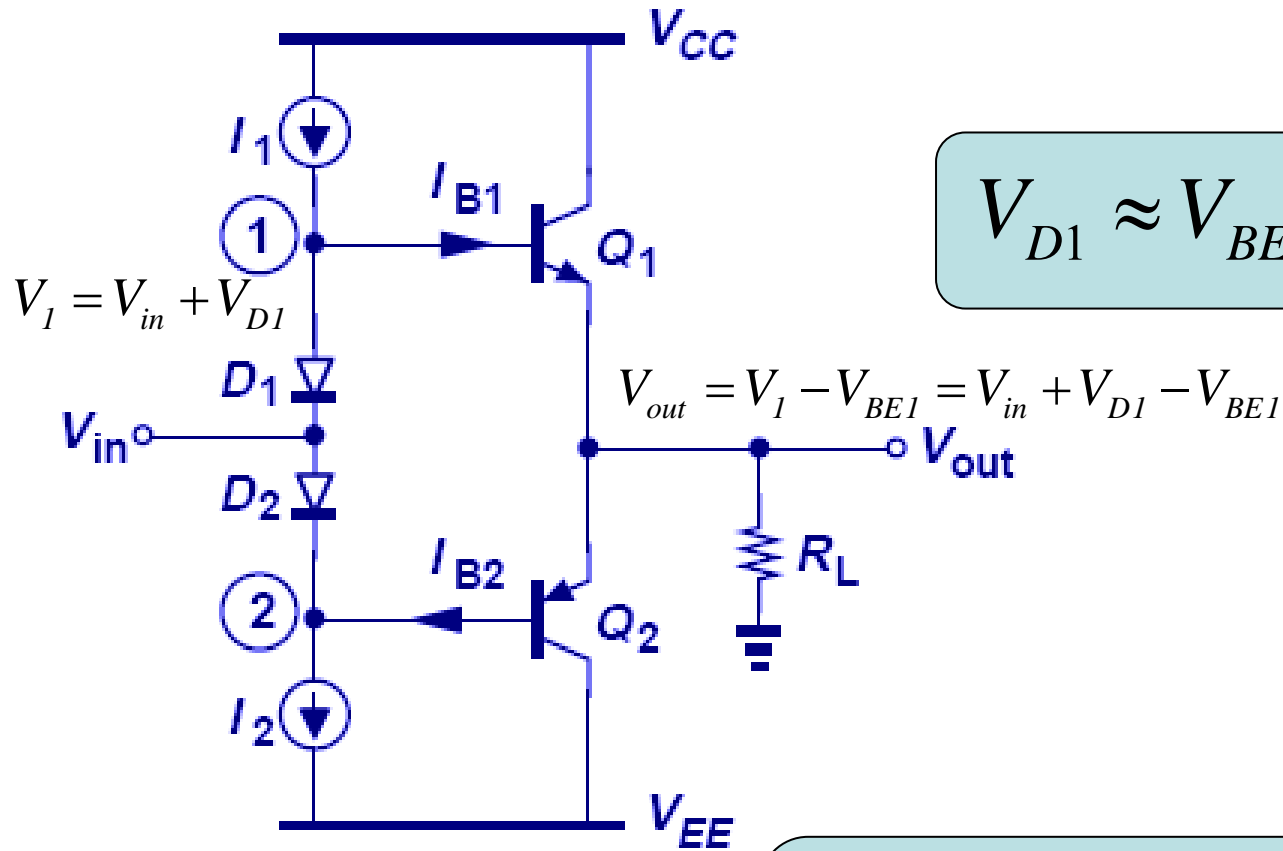


$$V_{D1} \approx V_{BE} \rightarrow V_{out} \approx V_{in}$$

$$I_{in} = 0 \text{ when } V_{out} = 0 \text{ if } I_1 = I_2$$

$$I_{B1} \approx I_{B2}$$


Addition of CE Stage

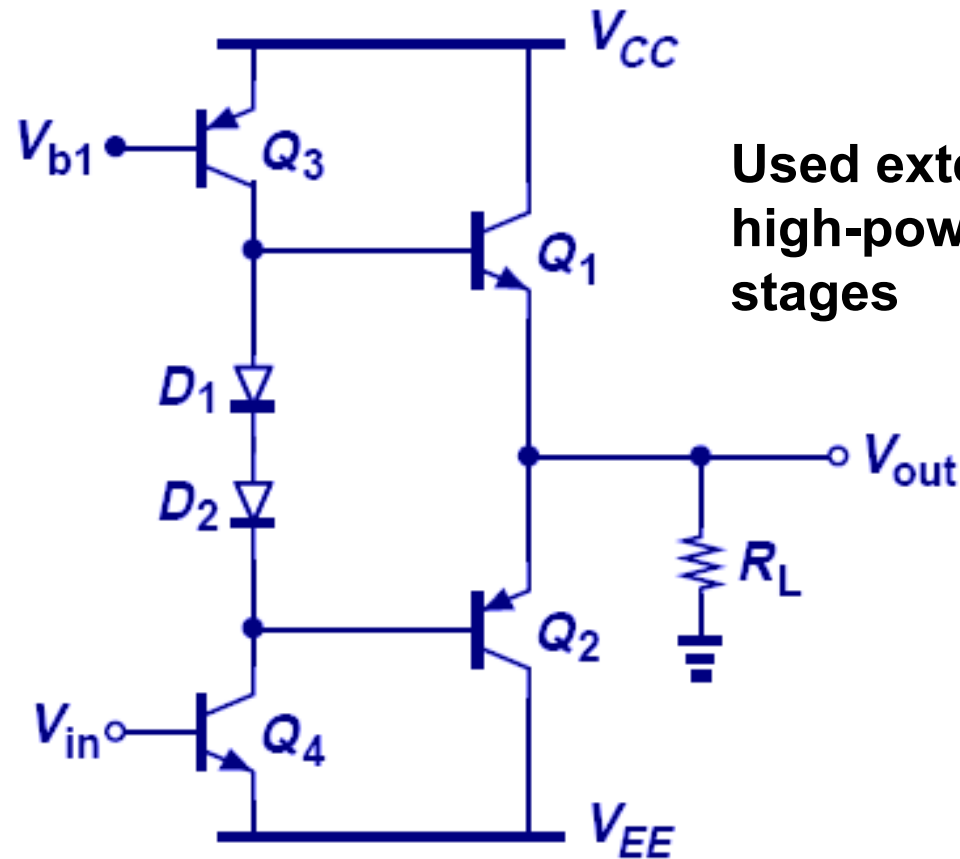

Used extensively in high-power output stages

- A CE stage (predriver) is added to provide voltage gain from the input to the bases of Q_1 and Q_2 .

Bias Point Analysis

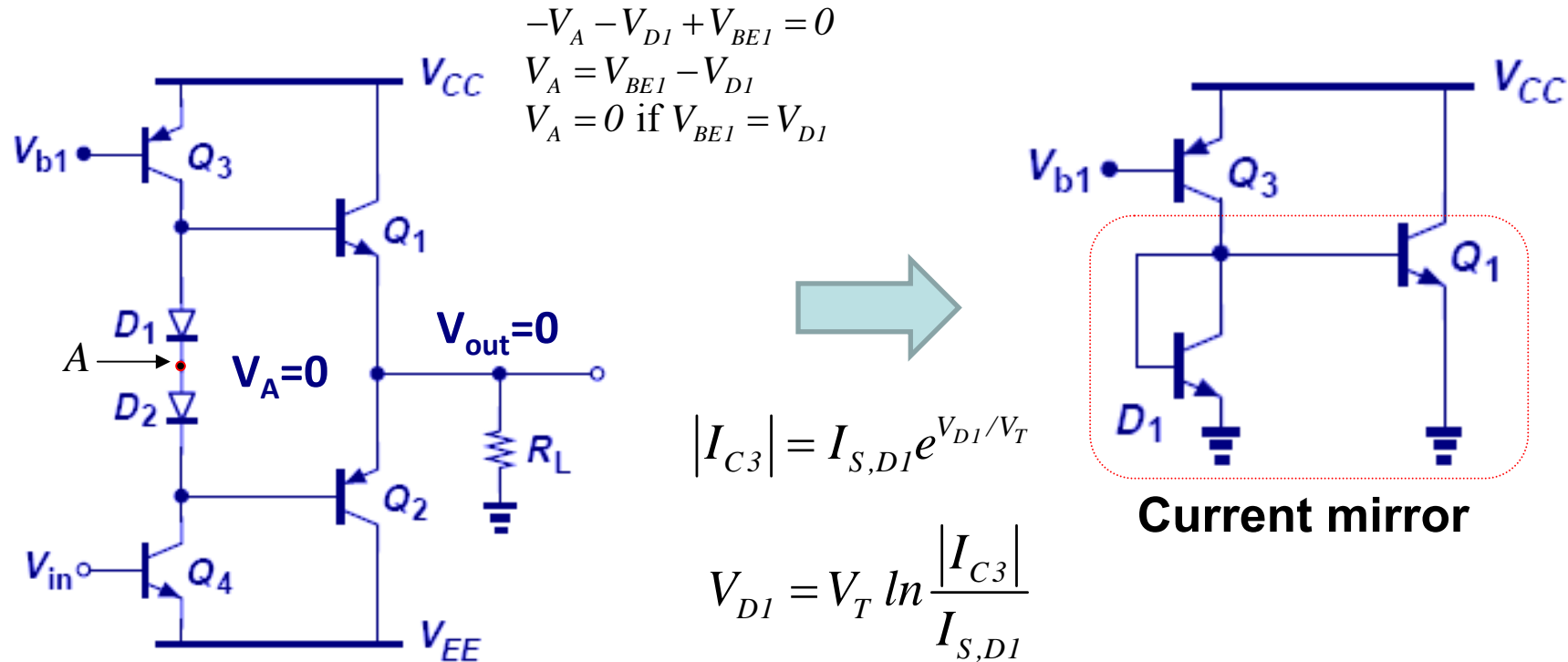

➤ For bias point analysis for $V_{out}=0$, the circuit can be simplified to the one on the right, which resembles a current mirror.


$$I_{C1} = \frac{I_{S,Q1}}{I_{S,D1}} \cdot |I_{C3}|$$

Emitter size difference between Q_1 and D_1


Summary

- Need to understand large signal behavior of emitter follower.
- As V_{in} decreases the output waveform will be clipped, introducing nonlinearity in I/O characteristics.
- Push-Pull stage could be a possible solution to solve the nonlinearity in emitter follower, but there is still nonlinearity due to dead zone near small V_{in} .
- With a battery of V_B inserted between the bases of Q_1 and Q_2 , the dead zone is eliminated.
- Two diodes in series are used to implement the battery of V_B .
- A CE stage (pre-driver) is added to provide voltage gain from the input to the bases of Q_1 and Q_2 .

Small-Signal Analysis

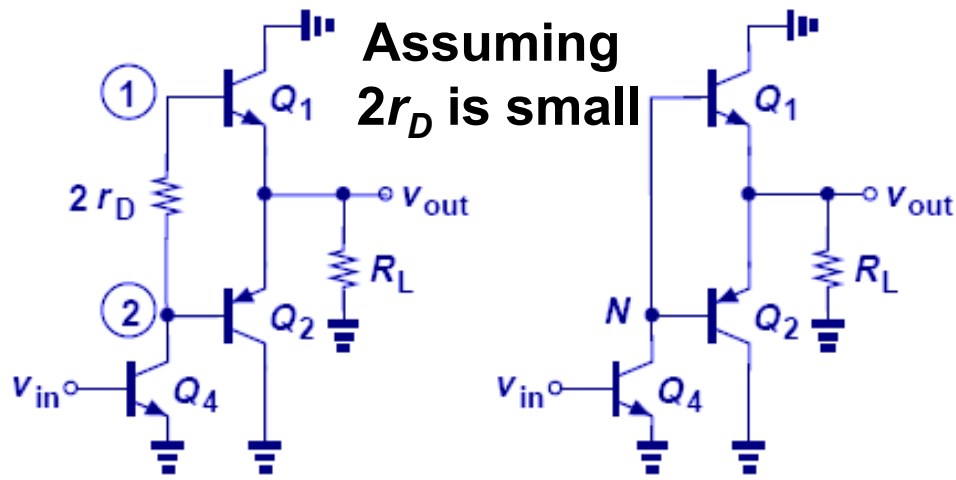

Assuming $2r_D$ is small

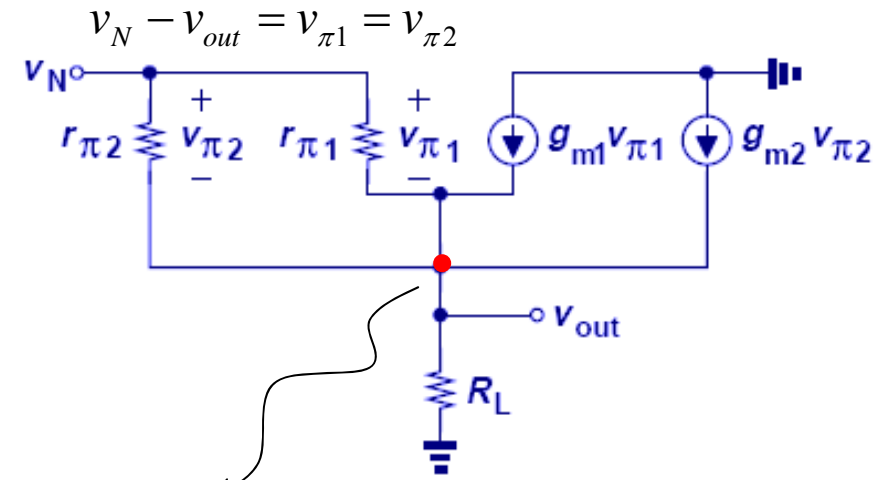

$$A_V = \frac{v_{out}}{v_{in}} = \frac{v_N}{v_{in}} \frac{v_{out}}{v_N}$$


$$\frac{v_{out}}{R_L} = \frac{v_N - v_{out}}{r_{\pi 1} \parallel r_{\pi 2}} + (g_{m1} + g_{m2})(v_N - v_{out})$$

if $1 + (g_{m1} + g_{m2})(r_{\pi 1} \parallel r_{\pi 2}) \gg 1$

$$\frac{v_{out}}{v_N} = \frac{R_L}{R_L + \frac{1}{g_{m1} + g_{m2}}}$$

Emitter follower having a transconductance of $g_{m1} + g_{m2}$

Small-Signal Analysis

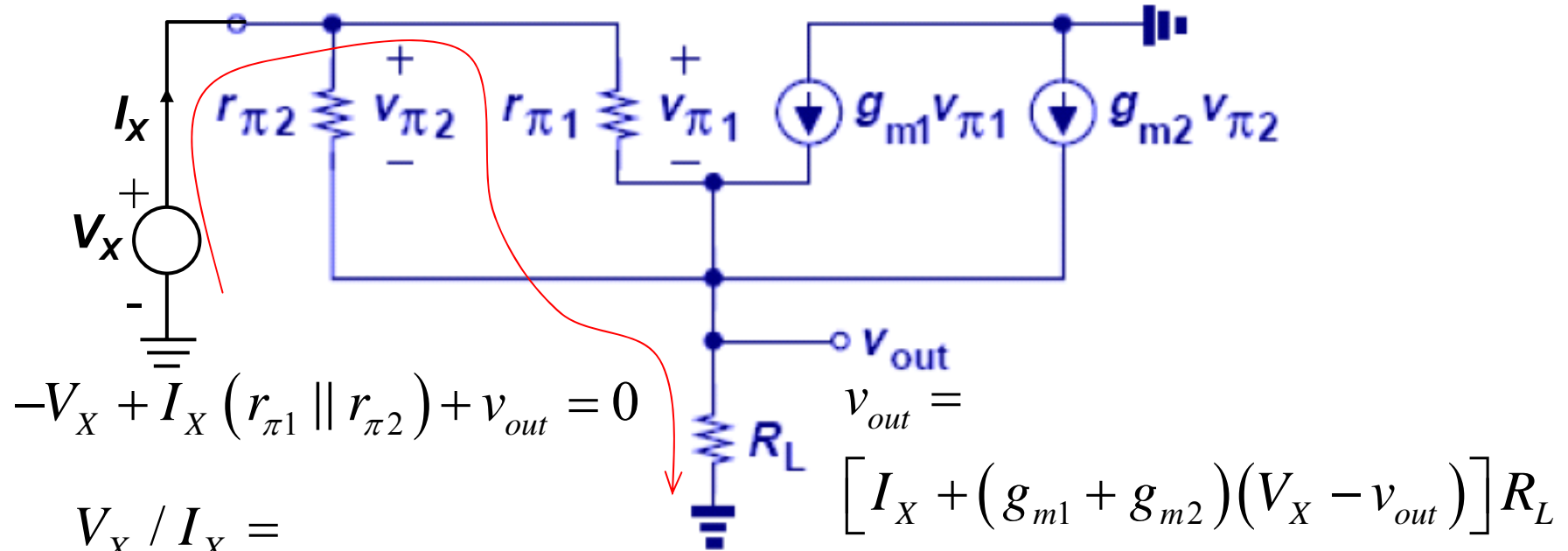



$$V_X / I_X =$$

$$R_N = (g_{m1} + g_{m2})(r_{\pi 1} \parallel r_{\pi 2}) R_L + r_{\pi 1} \parallel r_{\pi 2}$$


$$\frac{v_{out}}{v_{in}} = -g_{m4} \left[(g_{m1} + g_{m2})(r_{\pi 1} \parallel r_{\pi 2}) R_L + r_{\pi 1} \parallel r_{\pi 2} \right] \frac{R_L}{R_L + \frac{1}{g_{m1} + g_{m2}}}$$

$$A_v = -g_{m4} (r_{\pi 1} \parallel r_{\pi 2}) (g_{m1} + g_{m2}) R_L \quad \text{if } R_L (g_{m1} + g_{m2}) \gg 1$$

Example 13.9: Output Resistance Analysis

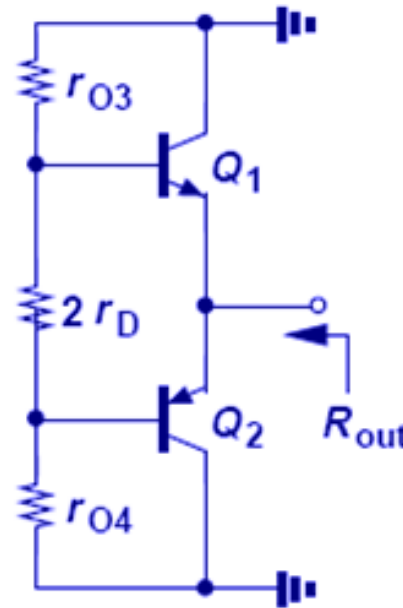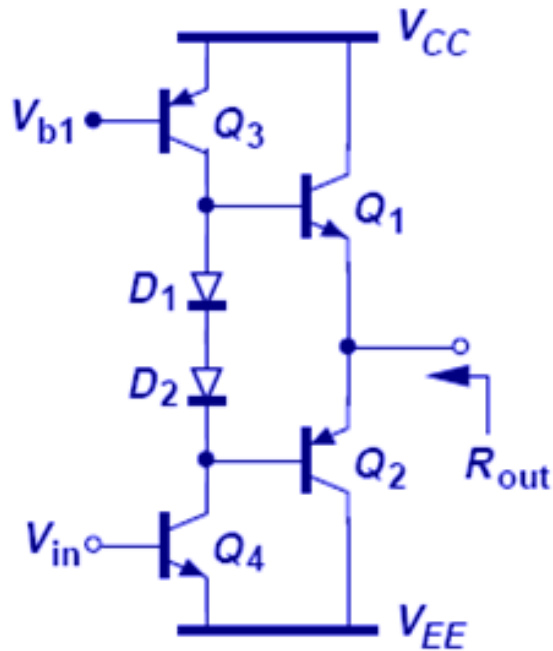


Assuming
 $2r_D$ is small

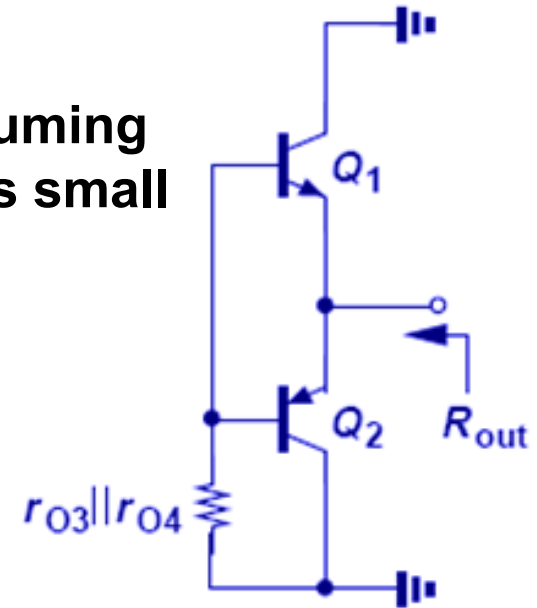

$$R_{out} \approx \frac{1}{g_{m1} + g_{m2}} + \frac{r_{O3} \parallel r_{O4}}{(g_{m1} + g_{m2})(r_{\pi 1} \parallel r_{\pi 2})}$$

- If β is low, the second term of the output resistance will rise, which will be problematic when driving a small resistance.

Example 13.9: Output Resistance Analysis

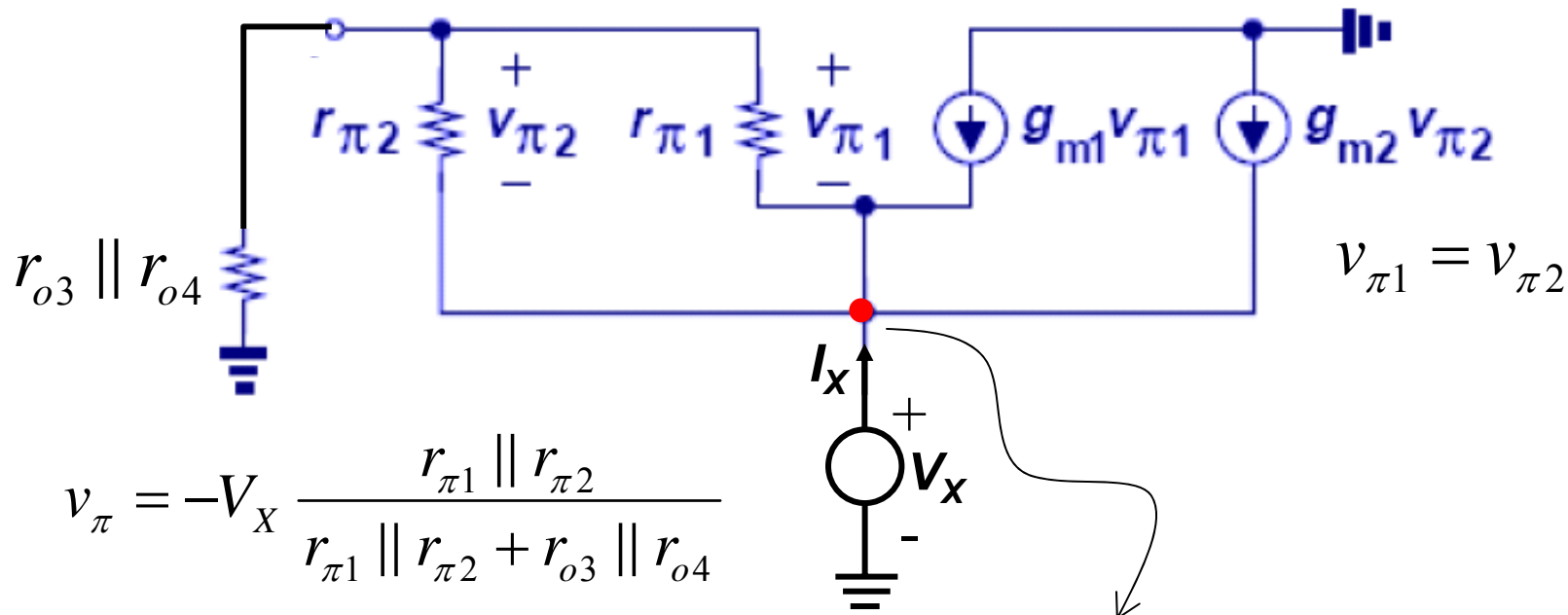

$$v_{\pi} = -V_X \frac{r_{\pi 1} \parallel r_{\pi 2}}{r_{\pi 1} \parallel r_{\pi 2} + r_{o3} \parallel r_{o4}}$$


$$I_X = \frac{V_X}{r_{\pi 1} \parallel r_{\pi 2} + r_{o3} \parallel r_{o4}} + (g_{m1} + g_{m2}) V_X \frac{r_{\pi 1} \parallel r_{\pi 2}}{r_{\pi 1} \parallel r_{\pi 2} + r_{o3} \parallel r_{o4}}$$

$$\frac{V_X}{I_X} = \frac{r_{\pi 1} \parallel r_{\pi 2} + r_{o3} \parallel r_{o4}}{1 + (g_{m1} + g_{m2})(r_{\pi 1} \parallel r_{\pi 2})}$$

$$\text{if } (g_{m1} + g_{m2})(r_{\pi 1} \parallel r_{\pi 2}) \gg 1 \quad R_{out} \approx \frac{1}{g_{m1} + g_{m2}} + \frac{r_{o3} \parallel r_{o4}}{(g_{m1} + g_{m2})(r_{\pi 1} \parallel r_{\pi 2})}$$

Example 13.10: Biasing

➤ Compute the required bias current.

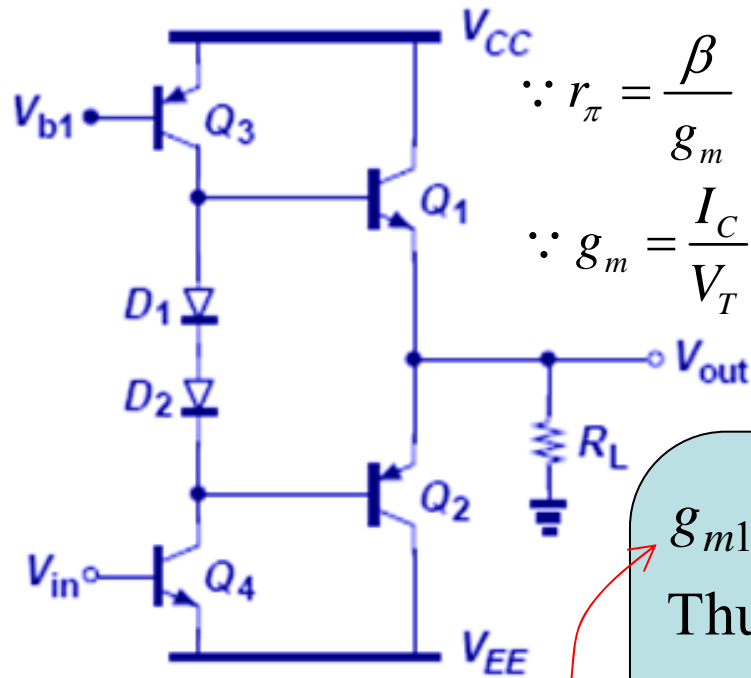

$$\therefore r_{\pi} = \frac{\beta}{g_m}$$

$$\therefore g_m = \frac{I_C}{V_T}$$

Predriver (CE stage): $A_V = 5$

Output Stage: $A_V = 0.8$ for $R_L = 8 \Omega$

$\beta_{npn} = 2\beta_{pnp} = 100$, $I_{C1} \approx I_{C2}$

$$g_{m1} + g_{m2} = (2 \Omega)^{-1} \Rightarrow g_{m1} \approx g_{m2} \approx (4 \Omega)^{-1}$$

Thus, $I_{C1} \approx I_{C2} \approx 6.5 \text{ mA}$


$$r_{\pi1} \parallel r_{\pi2} = 400 \Omega \parallel 200 \Omega = 133 \Omega$$

$$g_{m4} \cdot (r_{\pi1} \parallel r_{\pi2}) \cdot [1 + (g_{m1} + g_{m2}) \cdot R_L] = 4$$

$$\Rightarrow g_{m4} = (133 \Omega)^{-1} \Rightarrow I_{C3} \approx I_{C4} \approx 195 \mu\text{A}$$


$$0.8 = \frac{8}{8 + \frac{1}{g_{m1} + g_{m2}}}$$

Problem of Base Current

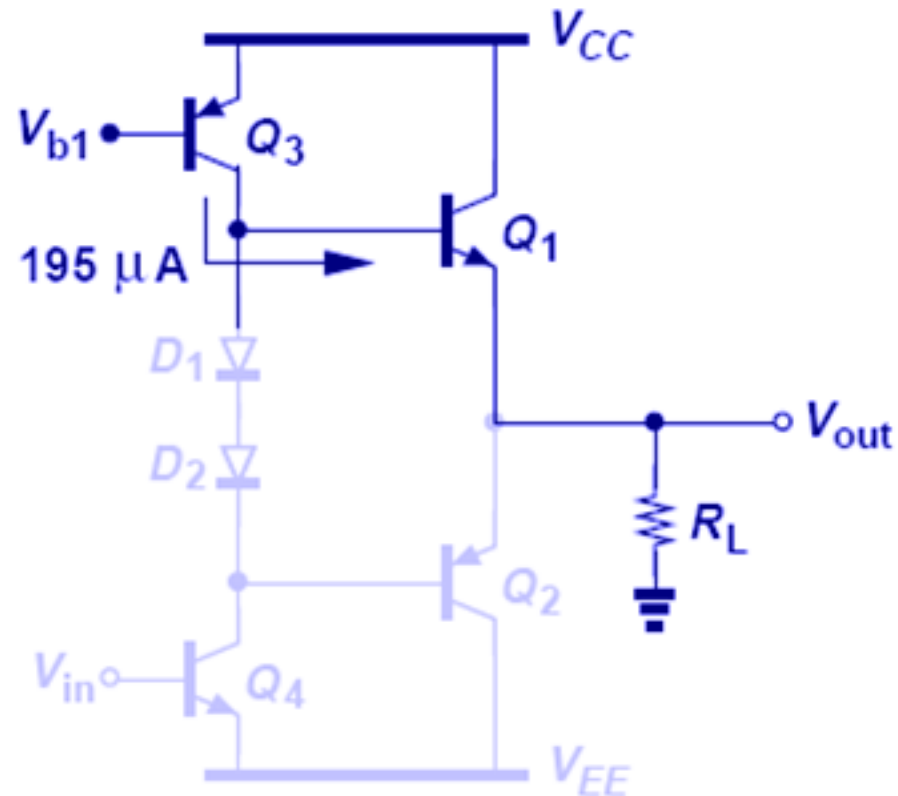

- **195 μA of base current in Q_1 can only support 19.5 mA of collector current, insufficient for high current operation (500 mA for 4 V on 8 Ω).**


Modification of the PNP Emitter Follower

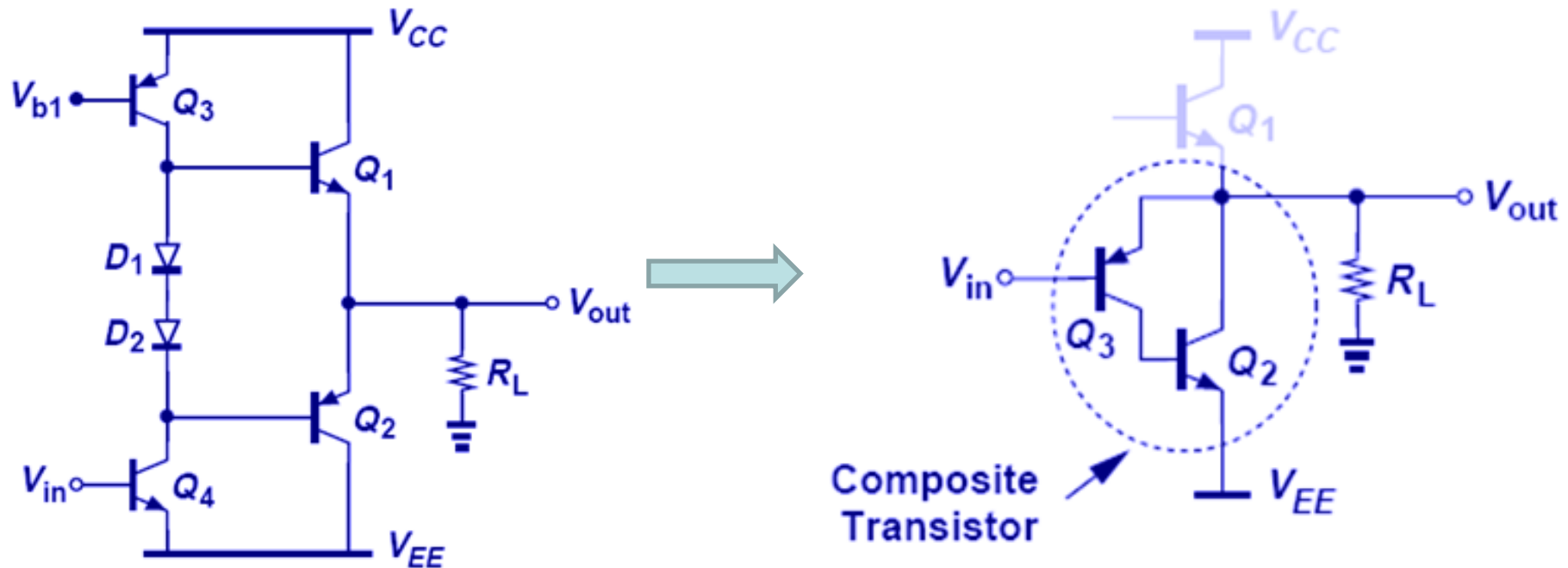

$$R_{out} \approx \frac{1}{(\beta_2 + 1) g_{m3}}$$


- Instead of having a single PNP as the emitter-follower, it is now combined with an NPN (Q_2), providing a lower output resistance.

Gain

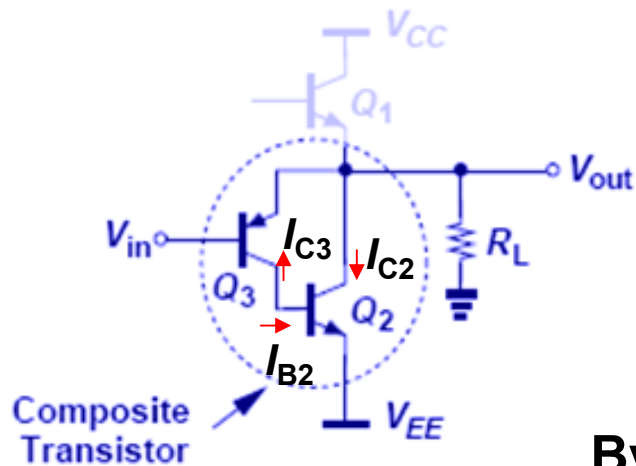

$$I_{C2} = \beta_2 I_{B2} = -\beta_2 I_{C3}$$
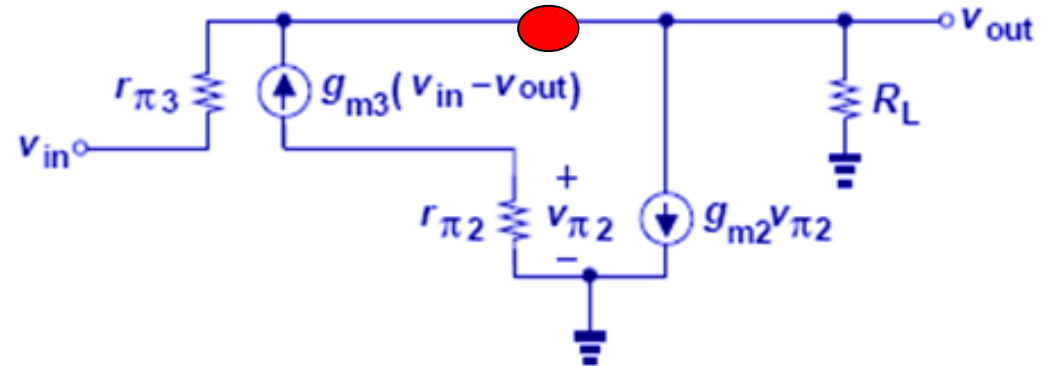
$$g_{m2} v_{\pi 2} = -\beta_2 g_{m3} (v_{in} - v_{out})$$




By KCL

$$-g_{m3} (v_{in} - v_{out}) \beta_2 + \frac{v_{out} - v_{in}}{r_{\pi 3}} - g_{m3} (v_{in} - v_{out}) = -\frac{v_{out}}{R_L}$$

$$\frac{v_{out}}{v_{in}} = \frac{R_L}{R_L + \frac{1}{(\beta_2 + 1) g_{m3} + \frac{1}{r_{\pi 3}}}}$$

Output Resistance

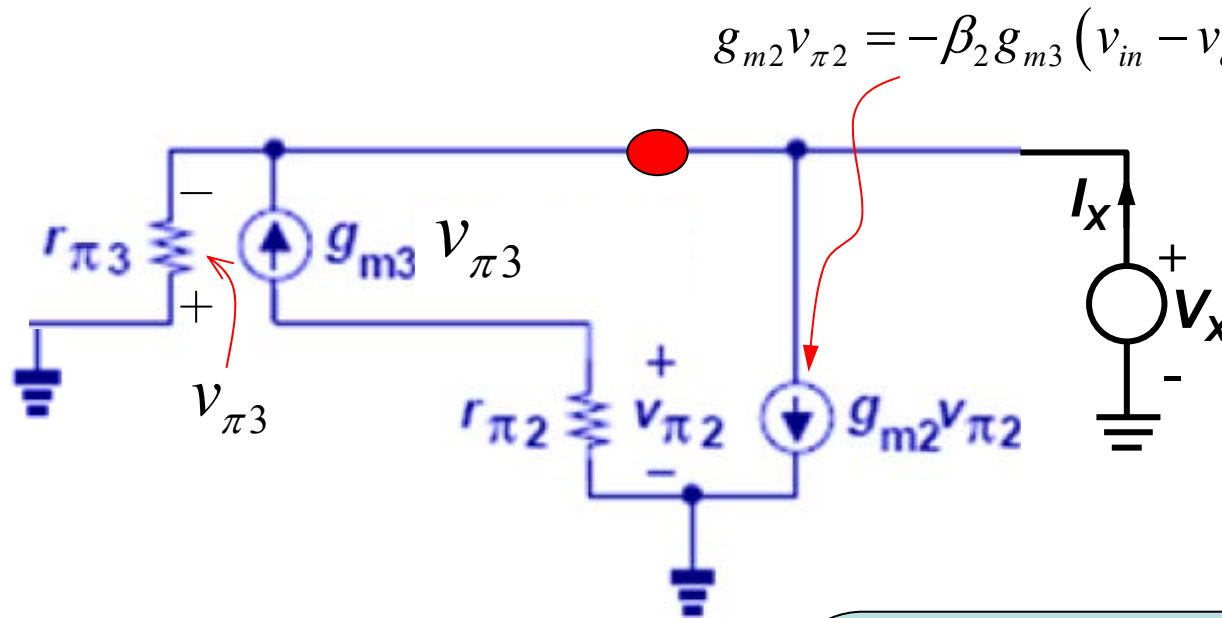


By KCL

$$-I_X + \frac{V_X}{r_{\pi 3}} + g_{m3}V_X + \beta_2 g_{m3}V_X = 0$$

Comparing with the standard EF,

$$r_{out} = \frac{1}{(\beta_2 + 1)g_{m3} + \frac{1}{r_{\pi 3}}} \approx \frac{1}{(\beta_2 + 1)g_{m3}}$$


Example 13.11: Input Resistance

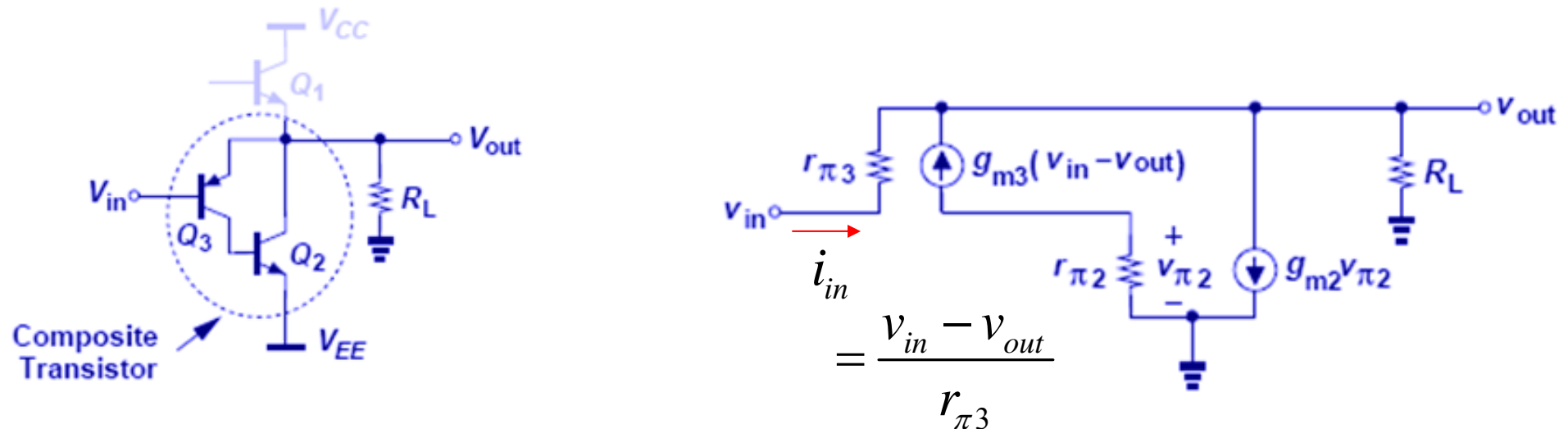

$$i_{in} = \frac{1}{r_{\pi 3}} \left(v_{in} - v_{in} \frac{R_L}{R_L + \frac{1}{(\beta_2 + 1)g_{m3}}} \right)$$

$$r_{in} = \beta_3(\beta_2 + 1)R_L + r_{\pi 3}$$


Additional Bias Current

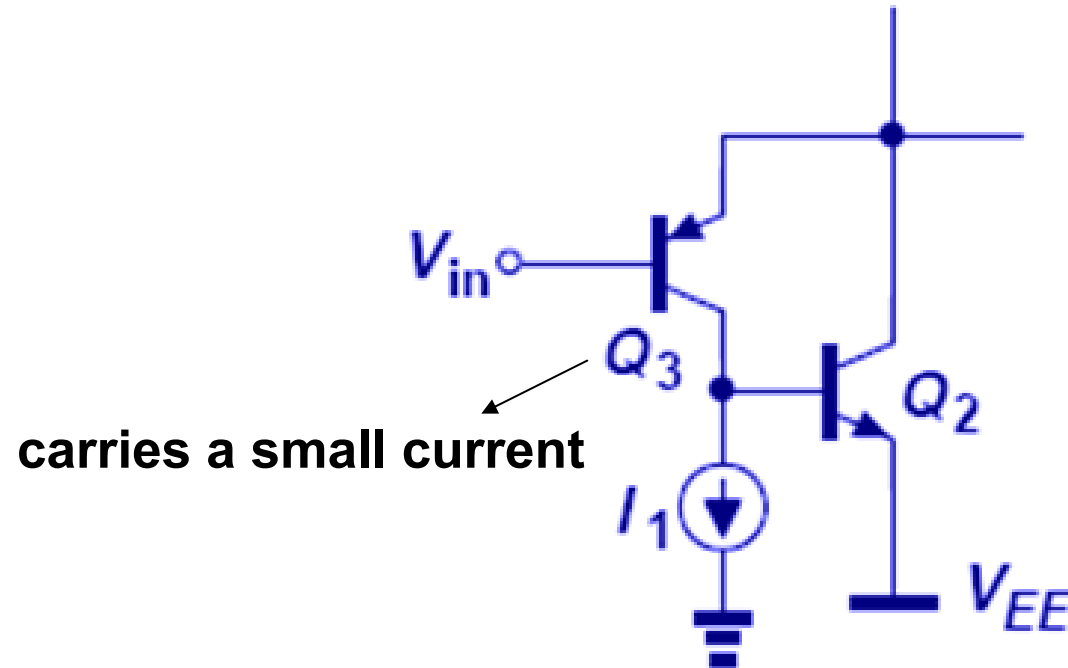

- I_1 is added to the base of Q_2 to provide an additional bias current to Q_3 so the capacitance at the base of Q_2 can be charged/discharged quickly. Additional pole at the base of Q_2 .

Example 13.12: Minimum V_{in}


Requirement: no saturation

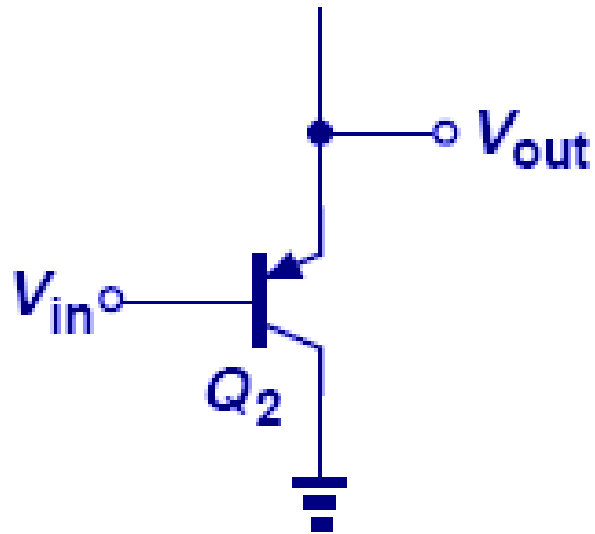

(a)

$$\text{Min } V_{in} \approx 0$$

$$V_{out} \approx |V_{EB2}|$$

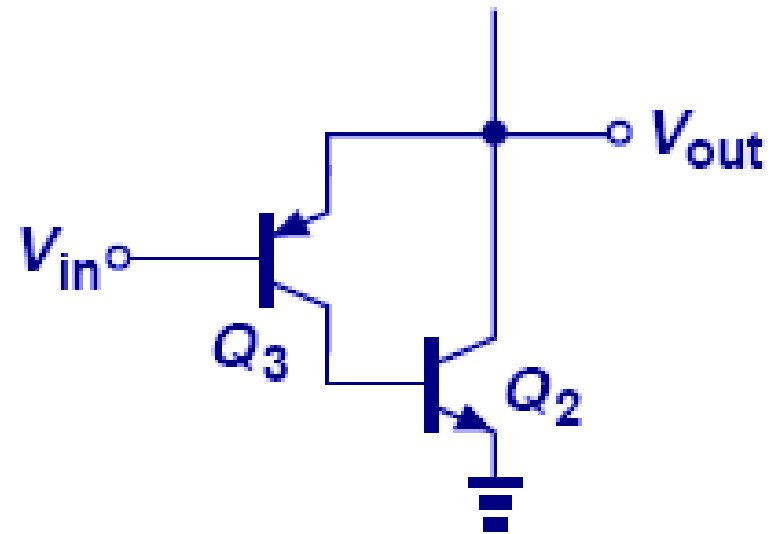


(b)

$$\text{Min } V_{in} \approx V_{BE2}$$

$$V_{out} \approx |V_{EB3}| + V_{BE2}$$

HiFi Design

$$\therefore g_m = \frac{I_C}{V_T}$$

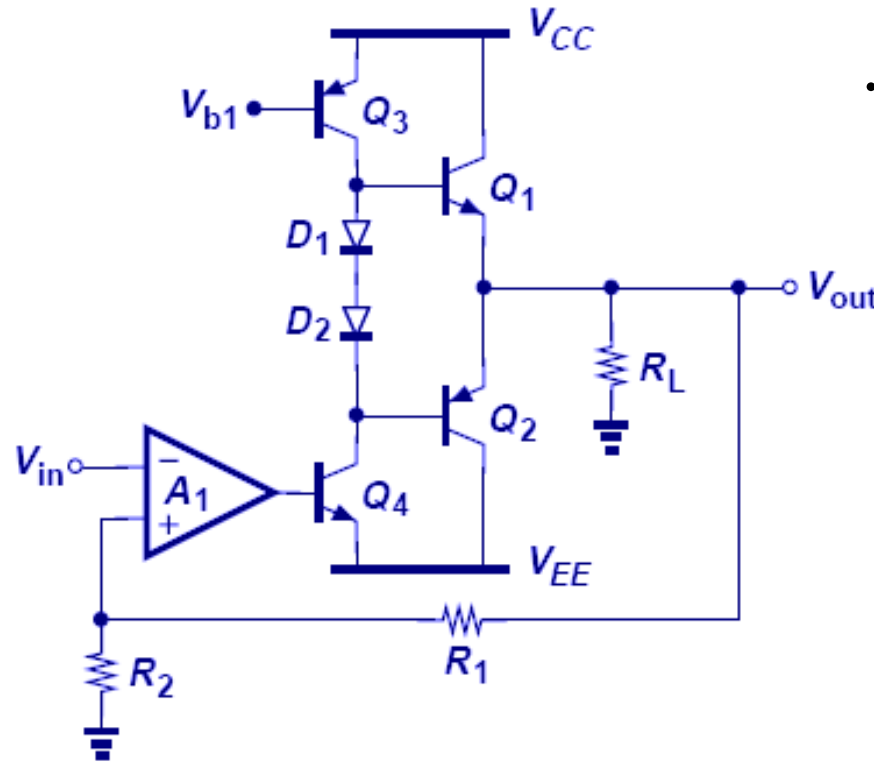


$$\therefore \frac{v_{out}}{v_N} = \frac{R_L}{R_L + \frac{1}{g_{m1} + g_{m2}}}$$

$$\therefore \frac{V_{out}}{V_{in}} \approx 1 + \frac{R_1}{R_2}$$

- As V_{out} becomes more positive, g_m rises and A_v comes closer to unity, resulting in nonlinearity.
- Using negative feedback, linearity is improved, providing higher fidelity.

Short-Circuit Protection

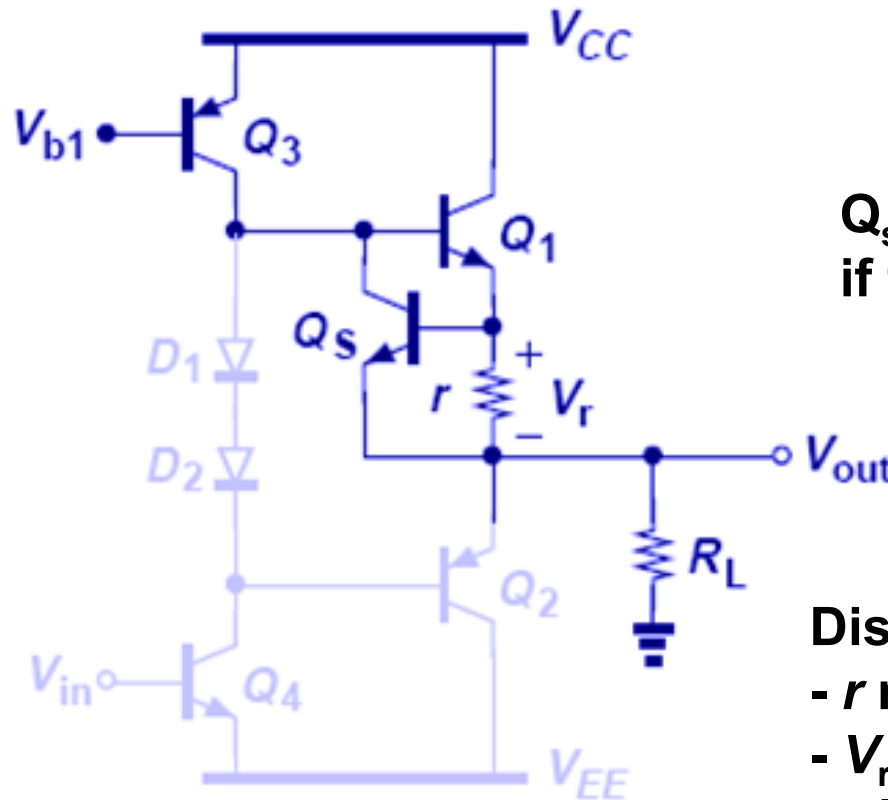

r : small resistance

Q_s reduces the base drive of Q_1
if the current exceeds a certain level


$$V_r \rightarrow 0.7 \text{ V}$$

Disadvantages:

- r raises the output impedance
- V_r under normal operating condition reduces the maximum output swing

➤ Q_s and r are used to “steal” some base current away from Q_1 when the output is accidentally shorted to ground, preventing short-circuit damage.

Emitter Follower Power Rating

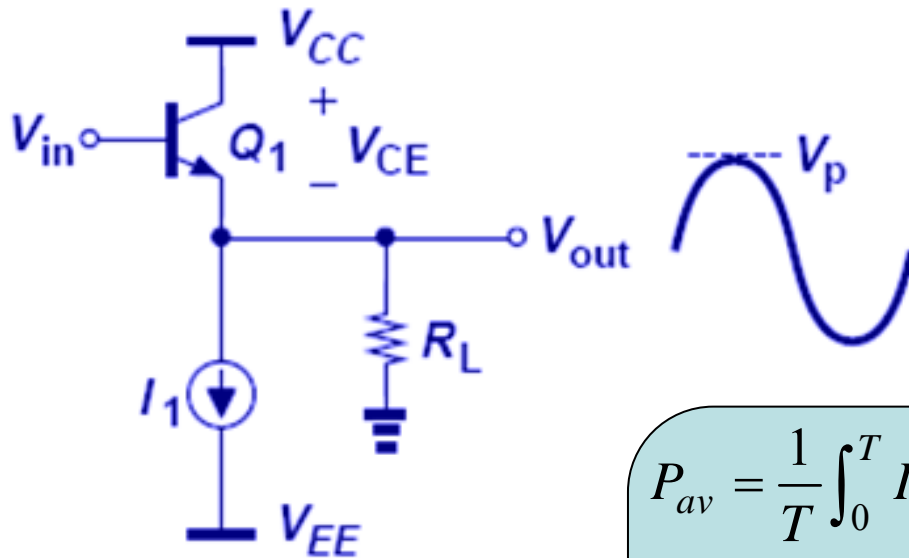


$$\sin^2 \omega t = (1 - \cos 2\omega t) / 2$$

$$\begin{aligned}
 P_{av} &= \frac{1}{T} \int_0^T I_C \cdot V_{CE} dt \\
 &= \frac{1}{T} \int_0^T \left(I_1 + \frac{V_P \sin \omega t}{R_L} \right) \cdot (V_{CC} - V_P \sin \omega t) dt \\
 &= I_1 \cdot V_{CC} - \frac{V_P^2}{R_L} = I_1 \left(V_{CC} - \frac{V_P}{2} \right) \text{ if } I_1 = \frac{V_P}{R_L}
 \end{aligned}$$

➤ **Maximum power dissipated across Q_1 occurs in the *absence* of a signal, i.e. with $V_p=0$: $P_{av,max} = I_1 V_{CC}$**

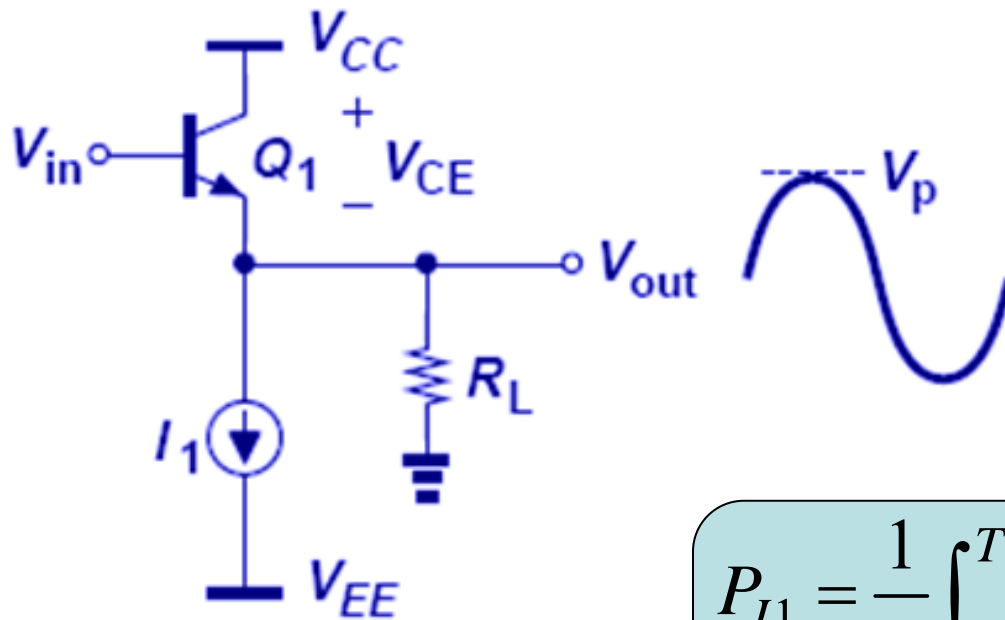Example 13.13: Power Dissipation

➤ Avg Power Dissipated in the Current Source I_1



$$P_{I1} = \frac{1}{T} \int_0^T I_1 (V_p \sin \omega t - V_{EE}) dt$$
$$= -I_1 \cdot V_{EE}$$


Push-Pull Stage Power Rating

$$\cos 2\omega t = \sin^2 \omega t - \cos^2 \omega t$$

$$\cos^2 \omega t = 1 - \sin^2 \omega t$$

$$\sin^2 \omega t = (1 - \cos 2\omega t) / 2$$

$$\int_0^{T/2} \cos 2\omega t dt = 0$$

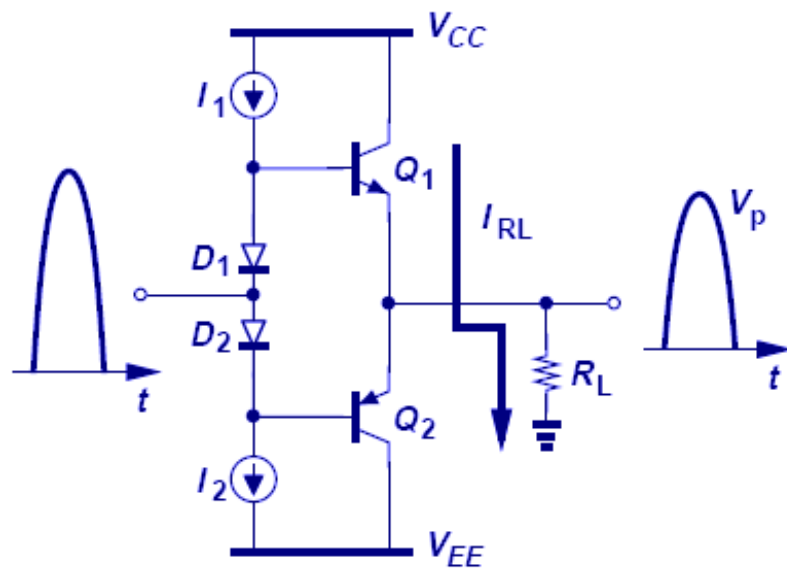


(a)

$$\begin{aligned}
 P_{av,NPN} &= \frac{1}{T} \int_0^{T/2} I_C \cdot V_{CE} dt \\
 &= \frac{1}{T} \int_0^{T/2} (V_{CC} - V_P \sin \omega t) \cdot \frac{V_P \sin \omega t}{R_L} dt \\
 &= \frac{V_{CC} \cdot V_P}{\pi R_L} - \frac{V_P^2}{4R_L} = \frac{V_P}{R_L} \left(\frac{V_{CC}}{\pi} - \frac{V_P}{4} \right)
 \end{aligned}$$

For $V_p \approx 0$ or $V_p \approx 4V_{CC}/\pi$, the power dissipated in Q_1 approaches zero

➤ No power for half of the period.

Push-Pull Stage Power Rating

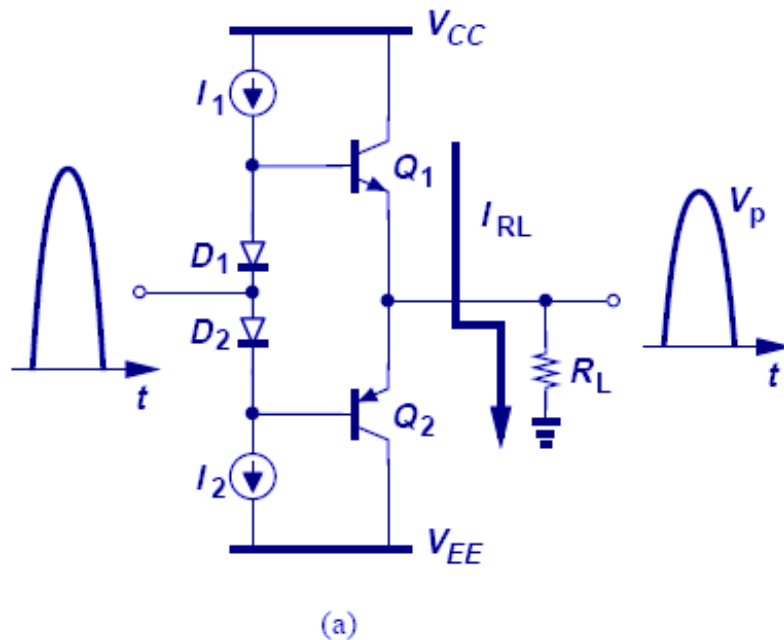


$$\begin{aligned}
 P_{av,NPN} &= \frac{1}{T} \int_0^{T/2} I_C \cdot V_{CE} dt \\
 &= \frac{1}{T} \int_0^{T/2} (V_{CC} - V_P \sin \omega t) \cdot \frac{V_P \sin \omega t}{R_L} dt \\
 &= \frac{V_{CC} \cdot V_P}{\pi R_L} - \frac{V_P^2}{4R_L} = \frac{V_P}{R_L} \left(\frac{V_{CC}}{\pi} - \frac{V_P}{4} \right)
 \end{aligned}$$

- No power for half of the period.
- Maximum power occurs between $V_p=0$ and $4V_{cc}/\pi$.

$$P_{av,max} = \frac{V_{CC}^2 \cdot V_P}{\pi^2 R_L} \text{ when } V_P = 2 \cdot \frac{V_{CC}}{\pi}$$

Push-Pull Stage Power Rating


$$\begin{aligned}
 P_{av,PNP} &= \frac{1}{T} \int_{T/2}^T |I_C| \cdot |V_{CE}| dt \\
 &= \frac{1}{T} \int_{T/2}^T (V_P \sin \omega t - V_{EE}) \cdot \left(-\frac{V_P \sin \omega t}{R_L} \right) dt \\
 &= \frac{-V_{EE} \cdot V_P}{\pi R_L} - \frac{V_P^2}{4R_L} = \frac{V_P}{R_L} \left(\frac{-V_{EE}}{\pi} - \frac{V_P}{4} \right)
 \end{aligned}$$

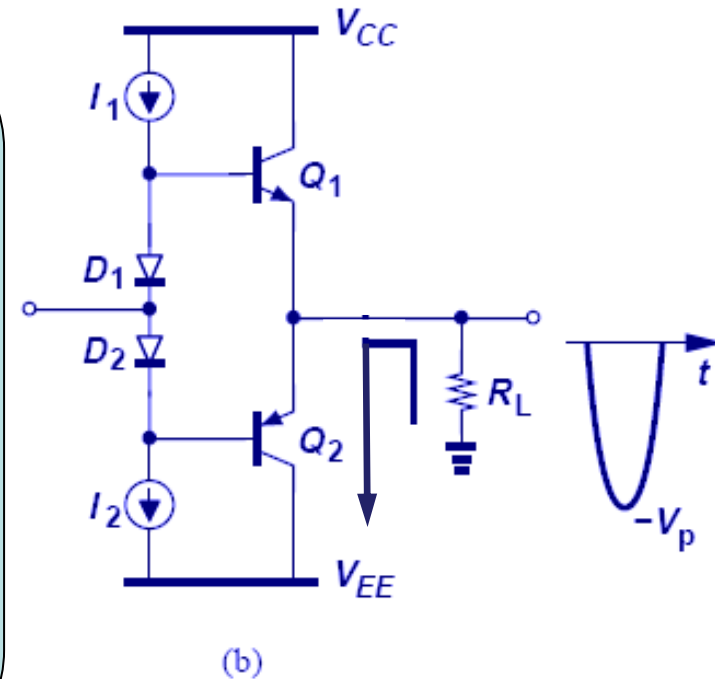

➤ Maximum power occurs between $V_p=0$ and $4V_{CC}/\pi$.


$$P_{av,max} = \frac{V_{CC}^2 \cdot V_P}{\pi^2 R_L} \text{ when } V_P = 2 \cdot \frac{V_{CC}}{\pi}$$

Heat Sink

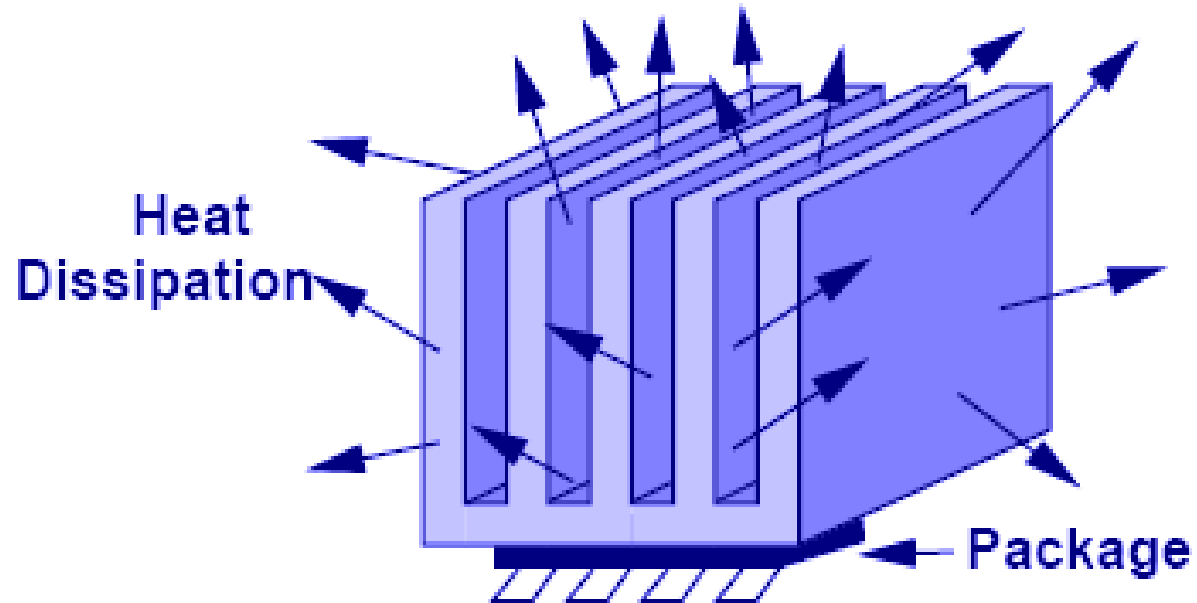

- **Heat sink, provides large surface area to dissipate heat from the chip.**

Thermal Runaway Mitigation

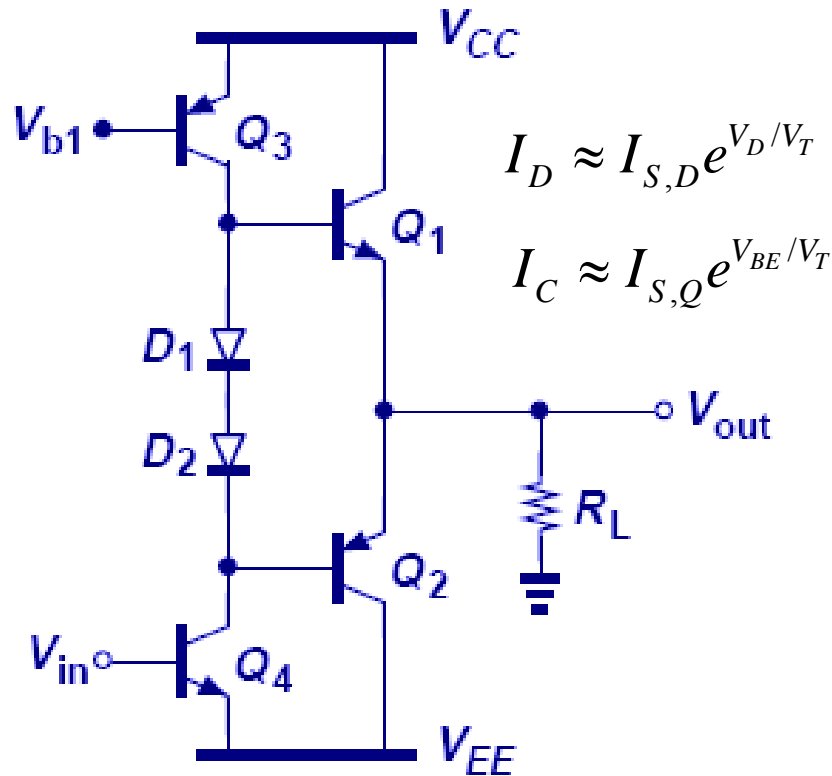

$$V_{D1} + V_{D2} = V_T \ln \frac{I_{D1}}{I_{S,D1}} + V_T \ln \frac{I_{D2}}{I_{S,D2}}$$

$$= V_T \ln \frac{I_{D1} I_{D2}}{I_{S,D1} I_{S,D2}}$$

$$V_{BE1} + V_{BE2} = V_T \ln \frac{I_{C1}}{I_{S,Q1}} + V_T \ln \frac{I_{C2}}{I_{S,Q2}}$$

$$= V_T \ln \frac{I_{C1} I_{C2}}{I_{S,Q1} I_{S,Q2}}$$

With the same V_T ,

$$\frac{I_{D1} I_{D2}}{I_{S,D1} I_{S,D2}} = \frac{I_{C1} I_{C2}}{I_{S,Q1} I_{S,Q2}}$$

- Using diode biasing prevents thermal runaway since the currents in Q_1 and Q_2 will track those of D_1 and D_2 as long as their I_s 's track with temperature.

Efficiency

- Efficiency is defined as the average power delivered to the load divided by the power drawn from the supply

$$\eta = \frac{\text{Power Delivered to Load}}{\text{Power Drawn From Supply Voltage}} = \frac{P_{out}}{P_{out} + P_{ckt}}$$

Emitter Follower

$$\eta_{EF} = \frac{V_P^2 / 2R_L}{V_P^2 / 2R_L + I_1 (V_{CC} - V_P / 2) - I_1 \cdot V_{EE}}$$


Load ←
 Tr. ←
 ← Current source

$$= \frac{V_P}{4V_{CC}} \text{ if } I_1 = \frac{V_P}{R_L} \text{ and } -V_{EE} = V_{CC}$$

- Maximum efficiency for EF is 25% if V_P approaches V_{CC} .

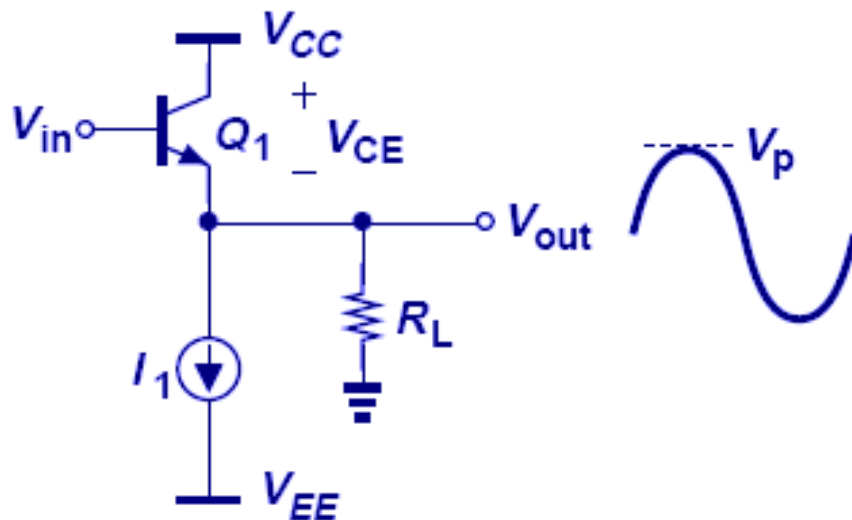Example 13.15: Efficiency of EF

➤ EF designed for full swing operates with half swing.



$$\text{With } I_1 = \frac{V_P}{R_L} = \frac{V_{CC}}{R_L} \text{ and } -V_{EE} = V_{CC}$$

$$\eta_{EF} = \frac{V_P^2 / 2R_L}{V_P^2 / 2R_L + I_1(V_{CC} - V_P/2) - I_1 \cdot V_{EE}}$$

$$= \frac{V_P^2 / 2R_L}{V_P^2 / 2R_L + \frac{V_{CC}}{R_L}(V_{CC} - V_P/2) + \frac{V_{CC}}{R_L} \cdot V_{CC}}$$

Thus,

$$\eta_{EF} \Big|_{V_P = V_{CC}/2} = \frac{1}{15}$$

Efficiency

Push-Pull Stage

$$\eta_{PP} = \frac{\frac{V_P^2}{2R_L}}{\frac{V_P^2}{2R_L} + \frac{2V_P}{R_L} \left(\frac{V_{CC}}{\pi} - \frac{V_P}{4} \right)}$$
$$= \frac{\pi V_P}{4 V_{CC}}$$

➤ **Maximum efficiency for PP is 78.5% for $V_P \approx V_{CC}$.**


Example 13.16: Efficiency incl. Predriver

$$I_1 = (V_P / R_L) / \beta$$


$$\eta = \frac{\frac{V_P^2}{2R_L}}{\frac{2V_P V_{CC}}{\pi R_L} + (V_{CC} - V_{EE}) \frac{V_P}{\beta R_L}}$$

$$= \frac{1}{4} \frac{V_P}{V_{CC} / \pi + V_{CC} / \beta}$$
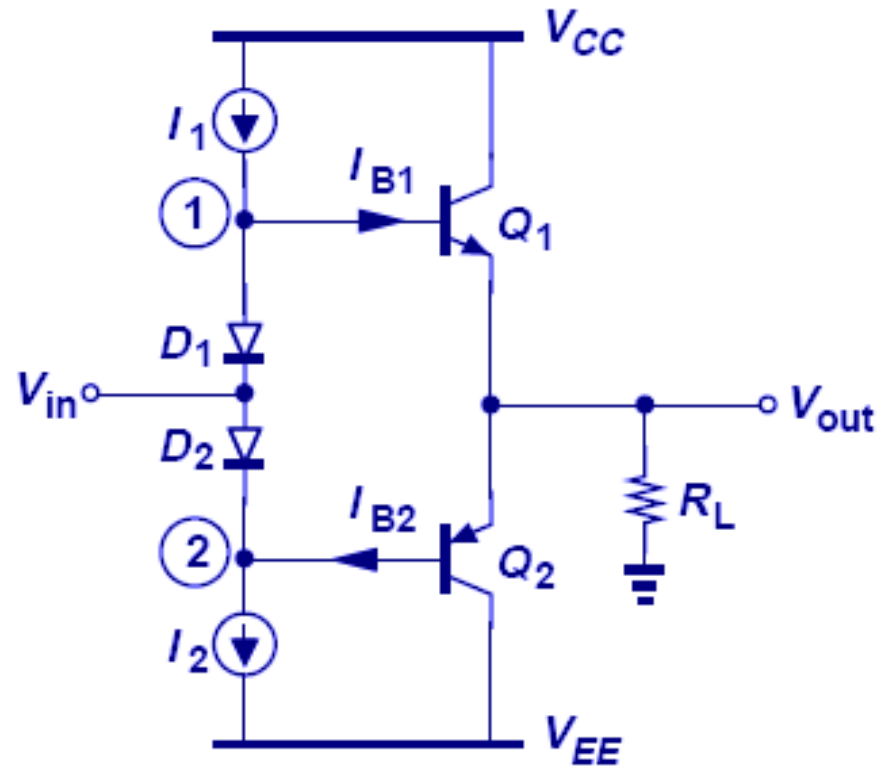
$$= \frac{1}{4} \frac{1}{\frac{1}{\pi} + \frac{1}{\beta}} \frac{V_P}{V_{CC}}$$




Power Amplifier Classes

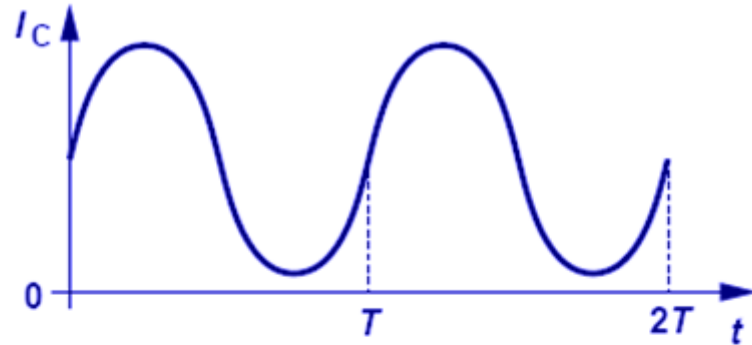


(a)

Class A: High linearity, low efficiency

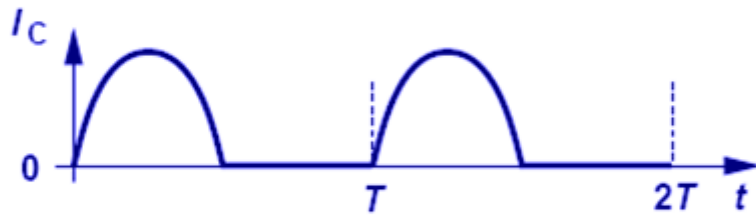

(b)

Class B: High efficiency, low linearity

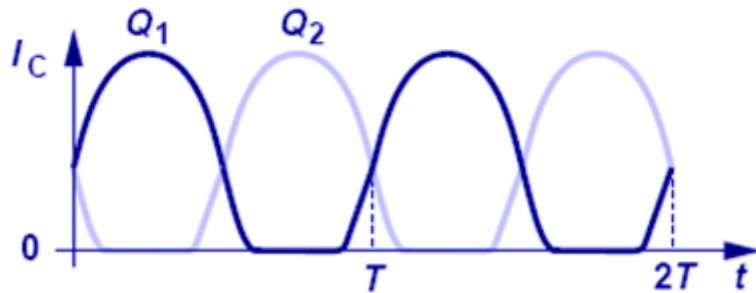

(c)

Class AB: Compromise between Class A and B

Summary

- **Small signal analysis push-pull stage: gain, R_{in} , and R_{out} .**
- **Composite transistor: lower R_{out} and higher R_{in}**
- **Using negative feedback, linearity is improved, providing higher fidelity**
- **Power rating of devices.**
- **Efficiency is defined as the average power delivered to the load divided by the power drawn from the supply:
Emitter Follower (25%), Push-Pull (78.5%)**
- **Amplifier classes: Class A, Class B, and Class AB**