



# CHAPTER 8. Transmission Lines

*Reading assignments:* Cheng Ch.8, Ulaby Ch.7, Hayt Ch.11

## 1. Transmission-Line Types and General Equations

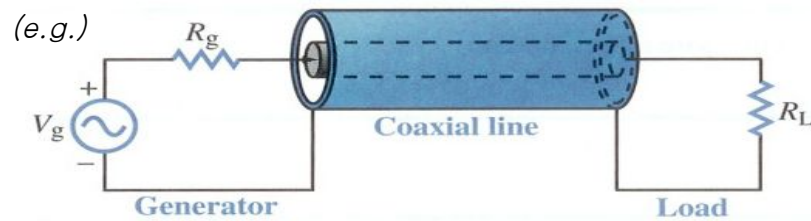
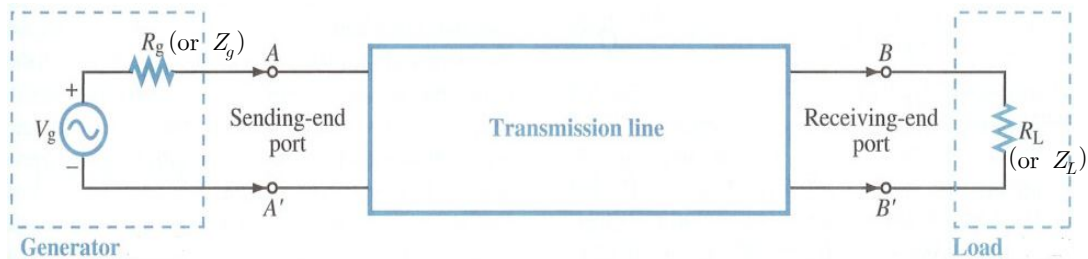
### A. Types of Transmission Lines

**Transmission line** = A four-terminal device (a two-port network) for transmitting or guiding power (for lighting, heating, or performing work) and information (audio, video, data, signal, etc) from a generator to a load



### 1) TEM-mode type [Both $E$ and $H$ are transverse ( $E, H \perp k$ or $\beta$ )]


Two-conductor transmission lines:

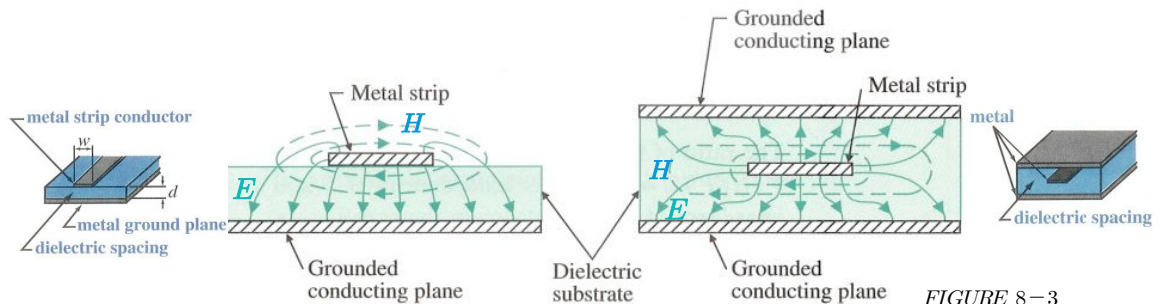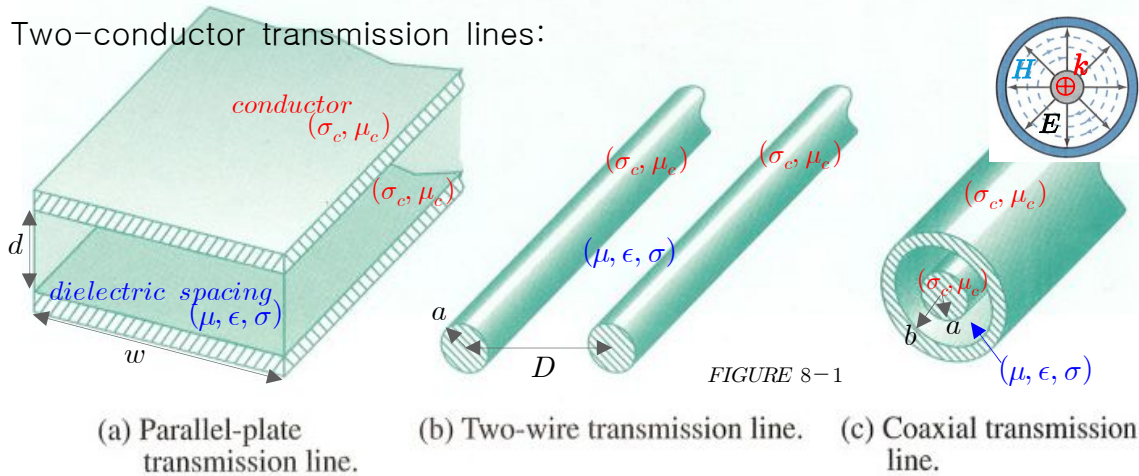


(d) Microstrip lines

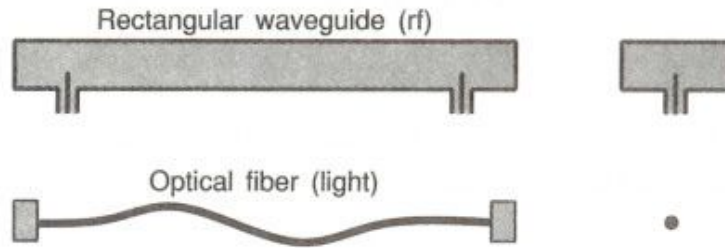- 2) Higher-mode type [ $E$  and/or  $H$  have components of transmission direction  
(TE or TM mode,  $E$  or  $H \parallel k$  or  $\beta$ )]


Hollow single-conductor waveguides (rectangular, circular, ... ),  
Optical fibers, Dielectric rods



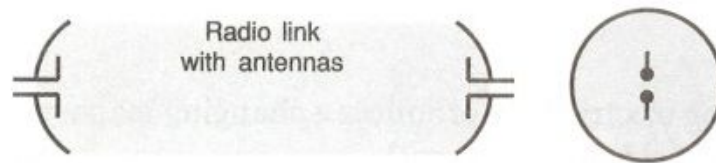- 3) TEM space waves between antennas of a radio link


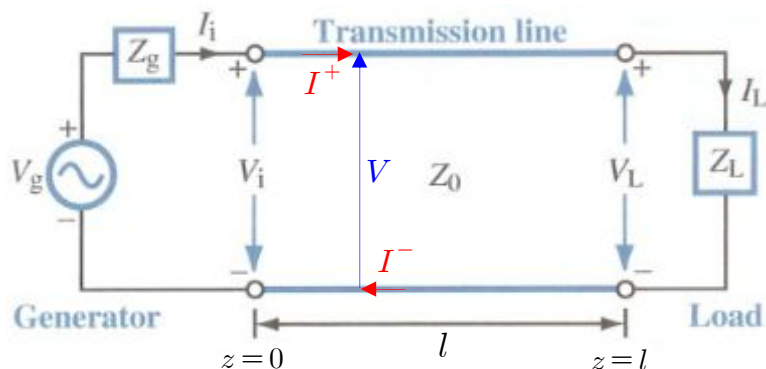
### B. Circuit Model for a Two-Conductor Transmission Line



Voltage between conductors and current along the lines are closely related with TEM fields by

$$V = - \int \mathbf{E} \cdot d\mathbf{l} \quad (3-28)$$

$$I = \oint \mathbf{H} \cdot d\mathbf{l} = \int_S \mathbf{J} \cdot d\mathbf{s} \quad (5-63) \quad (4-5)$$

- 1) Lumped circuit analysis : Two-terminal systems

If  $L_{syst.}$  or  $l \ll \lambda$ , no appreciable change of  $V(z)$ ,  $I(z)$  at any  $z$ .

no reflected signal, no standing waves

$\Rightarrow$  can be represented by discrete lumped parameters ( $R$ ,  $L$ ,  $C$ )

$$\left\{ \begin{array}{l} \text{localized energy dissipation } (R) \\ \text{localized magnetic energy storage } (L) \\ \text{localized electric energy storage } (C) \end{array} \right.$$

## 2) Distributed circuit analysis : Four-terminal systems

If  $L_{syst.}$  or  $l \gg \lambda$ ,

$\cos(\omega t - kl) = \cos(\omega t - 2\pi \frac{l}{\lambda}) \Rightarrow$  appreciable phase shift at the load

Reflected signals (Standing waves), Power loss on the line,

Dispersive (distortion) effects by different  $u_p$

$\Rightarrow$  completely described by distributed circuit parameters, whose value per unit length are constant everywhere on the line.

Transmission-line parameters:

- $R$  = series resistance of both conductors per unit length ( $\Omega/m$ )
- $L$  = series inductance of both conductors per unit length (H/m)
- $G$  = shunt conductance of dielectric medium per unit length (S/m)
- $C$  = shunt capacitance of two conductors per unit length (F/m)

Equivalent circuit of a differential length  $\Delta z$  :

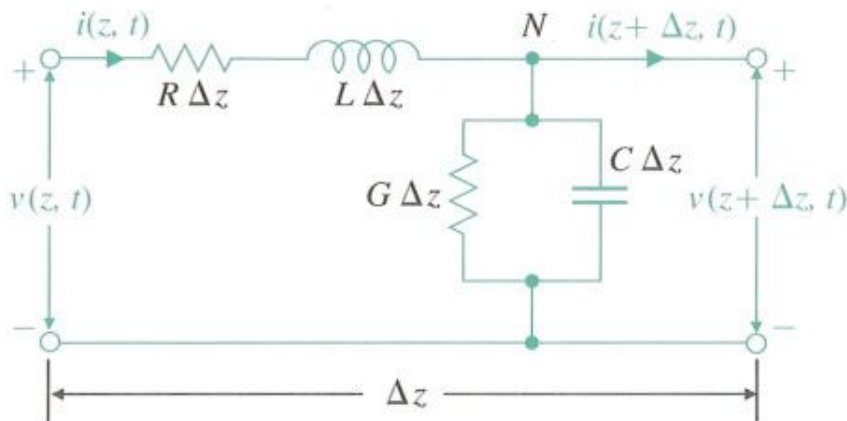


FIGURE 8-2

### C. Transmission-Line Equations

#### 1) General transmission-line equations

Kirchhoff's voltage law

$$\Rightarrow v(z, t) - R\Delta z i(z, t) - L\Delta z \frac{\partial i(z, t)}{\partial t} - v(z + \Delta z, t) = 0 \quad (8-1)$$

$$\lim_{\Delta z \rightarrow 0} \frac{(8-1)}{\Delta z} \Rightarrow -\frac{\partial v(z, t)}{\partial z} = Ri(z, t) + L\frac{\partial i(z, t)}{\partial t} \quad (8-3)$$

Kirchhoff's current law at N

$$\Rightarrow i(z, t) - G\Delta z v(z + \Delta z, t) - C\Delta z \frac{\partial v(z + \Delta z, t)}{\partial t} - i(z + \Delta z, t) = 0 \quad (8-4)$$

$$\lim_{\Delta z \rightarrow 0} \frac{(8-4)}{\Delta z} \Rightarrow -\frac{\partial i(z, t)}{\partial z} = Gv(z, t) + C\frac{\partial v(z, t)}{\partial t} \quad (8-5)$$

## 2) Time-harmonic transmission-line equations

For cosine-reference time-harmonic dependence,

$$v(z,t) = \text{Re}[V(z)e^{j\omega t}], \quad i(z,t) = \text{Re}[I(z)e^{j\omega t}] \quad (8-6, 8-7)$$

$\frac{\partial}{\partial t} \rightarrow j\omega$  in (8-3) and (8-5):

$$-\frac{dV(z)}{dz} = (R + j\omega L)I(z) = ZI(z) \quad (\leftarrow \text{Faraday's law}) \quad (8-8)$$

$$-\frac{dI(z)}{dz} = (G + j\omega C)V(z) = YV(z) \quad (\leftarrow \text{Ampere's law}) \quad (8-9)$$

where

$$Z \equiv R + j\omega L = R + jX \quad \text{series impedance} \quad (1)$$

$$Y \equiv G + j\omega C = G + jB \quad \text{shunt admittance} \quad (2)$$

Combining (8-8) and (8-9) yields Helmholtz-type equations:

$$\frac{d^2 V(z)}{dz^2} - \gamma^2 V(z) = 0 \quad [\leftarrow (7-45b)] \quad (8-10)$$

$$\frac{d^2 I(z)}{dz^2} - \gamma^2 I(z) = 0 \quad (8-11)$$

$$\text{where } \gamma = \alpha + j\beta = \sqrt{(R + j\omega L)(G + j\omega C)} = \sqrt{ZY} \quad (\text{m}^{-1}) [\leftarrow (7-43)] \quad (8-12)$$

### D. Transmission-Line Parameters

$R, L, G, C$  in (8-12) are functions of **physical dimensions** ( $d, w, a, D, b$ ) and **constitutive parameters** ( $\mu, \epsilon, \sigma, \mu_c, \sigma_c$ ).

For  $\sigma_c \rightarrow \infty$  in usual cases,  $R \rightarrow 0$  and TEM wave along the transmission line. Then, (8-12) becomes

$$\gamma = j\omega \sqrt{LC} \left(1 + \frac{G}{j\omega C}\right)^{1/2} \quad (8-13)$$

For a TEM wave in a medium with  $(\mu, \epsilon, \sigma)$ , from (7-43)


$$\gamma = j\omega \sqrt{\mu\epsilon} \left(1 + \frac{\sigma}{j\omega\epsilon}\right)^{1/2} \quad (8-14)$$

$$\text{Using (4-38), } \frac{G}{C} = \frac{\sigma}{\epsilon} \quad (8-15)$$

comparison of (8-13) with (8-14) gives

$$LC = \mu\epsilon \quad (8-16)$$

## 1) Parallel-plate transmission line

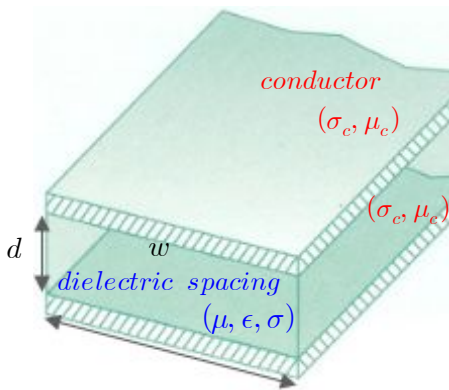

$$(3-87) \Rightarrow C = \epsilon w/d \quad (8-17)$$

(8-17) in (8-16, 15):

$$L = \mu d/w \quad (8-18)$$

$$G = \sigma w/d \quad (8-19)$$

For good conductor (not strictly TEM),


$$(4-16) \Rightarrow R = 1/\sigma_c S \quad (7-56)$$

$$\Rightarrow R = \frac{2}{\sigma_c w \delta} = \frac{2}{w} \sqrt{\frac{\pi f \mu_c}{\sigma_c}} = \frac{2}{w} R_s \quad (8-22)$$



$$\text{from which } \eta_c = (1+j) \sqrt{\frac{\pi f \mu_c}{\sigma_c}} \equiv R_s + jX_s \quad (7-53)$$

Notes) i)  $E_{1n} \gg E_{1t}$  since  $E_{1t} = E_{2t} = \frac{J_{2t}}{\sigma_2} = \frac{\text{finite}}{\text{large}} \rightarrow \text{small}$

ii) Skin depth  $\delta$

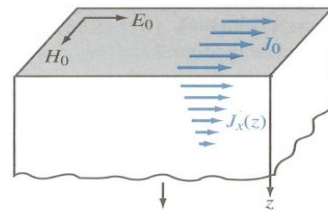


(a) Exponentially decaying  $J_x(z)$

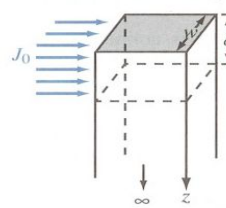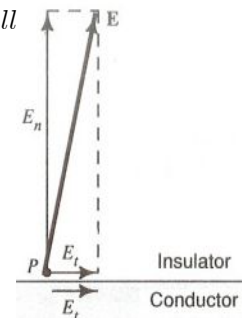

(b) Equivalent  $J_0$  over skin depth  $\delta$

## 2) Two-wire transmission line

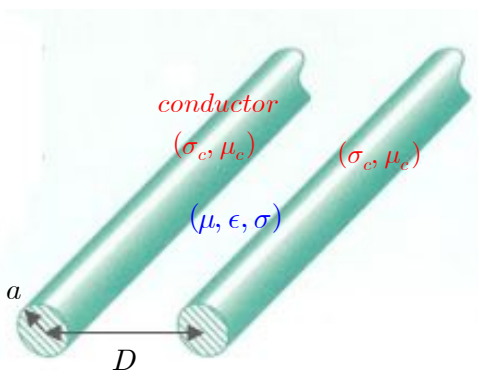

$$(3-165) \Rightarrow C = \frac{\pi \epsilon}{\cosh^{-1}(D/2a)} \quad (8-23)$$

(8-23) in (8-16, 15):

$$L = \frac{\mu}{\pi} \cosh^{-1}\left(\frac{D}{2a}\right) \quad (8-24)$$


$$G = \frac{\pi \sigma}{\cosh^{-1}(D/2a)} \quad (8-25)$$

$$R = \frac{2}{\sigma_c (2\pi a \delta)} = \frac{1}{\pi a} \sqrt{\frac{\pi f \mu_c}{\sigma_c}} = \frac{R_s}{\pi a} \quad (8-27)$$



equivalent one conducting wire

### 3) Coaxial transmission line

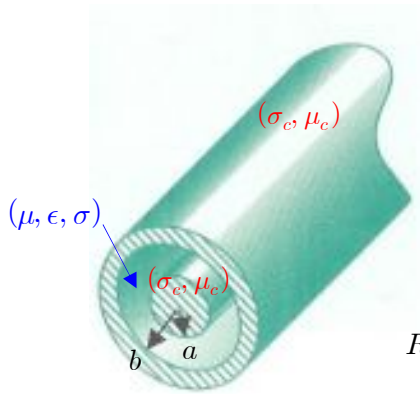

$$(3-90) \Rightarrow C = \frac{2\pi\epsilon}{\ln(b/a)} \quad (8-28)$$

(8-28) in (8-16, 15):

$$L = \frac{\mu}{2\pi} \ln \frac{b}{a} \quad (8-29)$$

$$G = \frac{2\pi\sigma}{\ln(b/a)} \quad (8-30)$$

$$R = \frac{1}{\sigma_c(2\pi a\delta)} + \frac{1}{\sigma_c(2\pi b\delta)} = \frac{1}{2\pi} \left( \frac{1}{a} + \frac{1}{b} \right) \sqrt{\frac{\pi f \mu_c}{\sigma_c}} \quad (8-32)$$

$$= \frac{R_s}{2\pi} \left( \frac{1}{a} + \frac{1}{b} \right)$$

TABLE 8-1 Summary of Distributed Transmission-Line Parameters

Parameter	Parallel-Plate Line	Two-Wire Line	Coaxial Line	Unit
$R$	$\frac{2}{w} R_s$	$\frac{R_s}{\pi a}$	$\frac{R_s}{2\pi} \left( \frac{1}{a} + \frac{1}{b} \right)$	$\Omega/\text{m}$
$L$	$\mu \frac{d}{w}$	$\frac{\mu}{\pi} \cosh^{-1} \left( \frac{D}{2a} \right)$	$\frac{\mu}{2\pi} \ln \frac{b}{a}$	$\text{H}/\text{m}$
$G$	$\sigma \frac{w}{d}$	$\frac{\pi\sigma}{\cosh^{-1}(D/2a)}$	$\frac{2\pi\sigma}{\ln(b/a)}$	$\text{S}/\text{m}$
$C$	$\epsilon \frac{w}{d}$	$\frac{\pi\epsilon}{\cosh^{-1}(D/2a)}$	$\frac{2\pi\epsilon}{\ln(b/a)}$	$\text{F}/\text{m}$

Note:  $R_s = \sqrt{\pi f \mu_c / \sigma_c}$ ;  $\cosh^{-1}(D/2a) \cong \ln(D/a)$  if  $(D/2a)^2 \gg 1$ . Internal inductance is not included.