

3. Smith Chart and Impedance Matching

A. Construction and Applications of the Smith Chart

Smith Chart :

A graphical chart of normalized impedance (or admittance) in the Γ plane for analyzing and designing both lossless and lossy transmission-line circuits (P.H. Smith, 1939)

1) Parametric equations for the chart construction

For a lossless transmission line,

$$\Gamma = \frac{Z_L - Z_o}{Z_L + Z_o} = |\Gamma| e^{j\theta_\Gamma} = \Gamma_r + j\Gamma_i = \frac{z_L - 1}{z_L + 1} \quad (8-88, 97) \quad (8-99)$$

where the normalized impedance w.r.t. $Z_o = R_o = \sqrt{L/C}$ is

$$z_L \equiv \frac{Z_L}{Z_o} = \frac{R_L}{R_o} + j \frac{X_L}{R_o} = r + jx \quad (8-98)$$

Inverse relation of (8-99) with (8-97, 98) :

$$z_L = \frac{1 + \Gamma}{1 - \Gamma} = \frac{1 + |\Gamma| e^{j\theta_\Gamma}}{1 - |\Gamma| e^{j\theta_\Gamma}} = \frac{(1 + \Gamma_r) + j\Gamma_i}{(1 - \Gamma_r) - j\Gamma_i} = r + jx \quad (8-100)(8-101)$$

$$(8-101) \times \frac{(1 - \Gamma_r) + j\Gamma_i}{(1 - \Gamma_r) - j\Gamma_i}:$$

$$r = \frac{1 - \Gamma_r^2 - \Gamma_i^2}{(1 - \Gamma_r)^2 + \Gamma_i^2} \quad (8-102)$$

$$x = \frac{2\Gamma_i}{(1 - \Gamma_r)^2 + \Gamma_i^2} \quad (8-103)$$

Rearrangements of (8-102, 103) yield the parametric equations of constant- r and constant- x circles in the $\Gamma_r - \Gamma_i$ plane, respectively

$$\underline{\left(\Gamma_r - \frac{r}{1+r}\right)^2 + \Gamma_i^2 = \left(\frac{1}{1+r}\right)^2} \quad (8-104)$$

: Eqn. of const.- r circle of a radius $\frac{1}{1+r}$ centered at $\left(\frac{r}{1+r}, 0\right)$

$$\underline{(\Gamma_r - 1)^2 + \left(\Gamma_i - \frac{1}{x}\right)^2 = \left(\frac{1}{x}\right)^2} \quad (8-105)$$

: Eqn. of const.- x circle of a radius $\frac{1}{x}$ centered at $\left(1, \frac{1}{x}\right)$

2) Construction of the Smith Chart

a) Smith Chart with $\Gamma_r - \Gamma_i$ rectangular coordinates

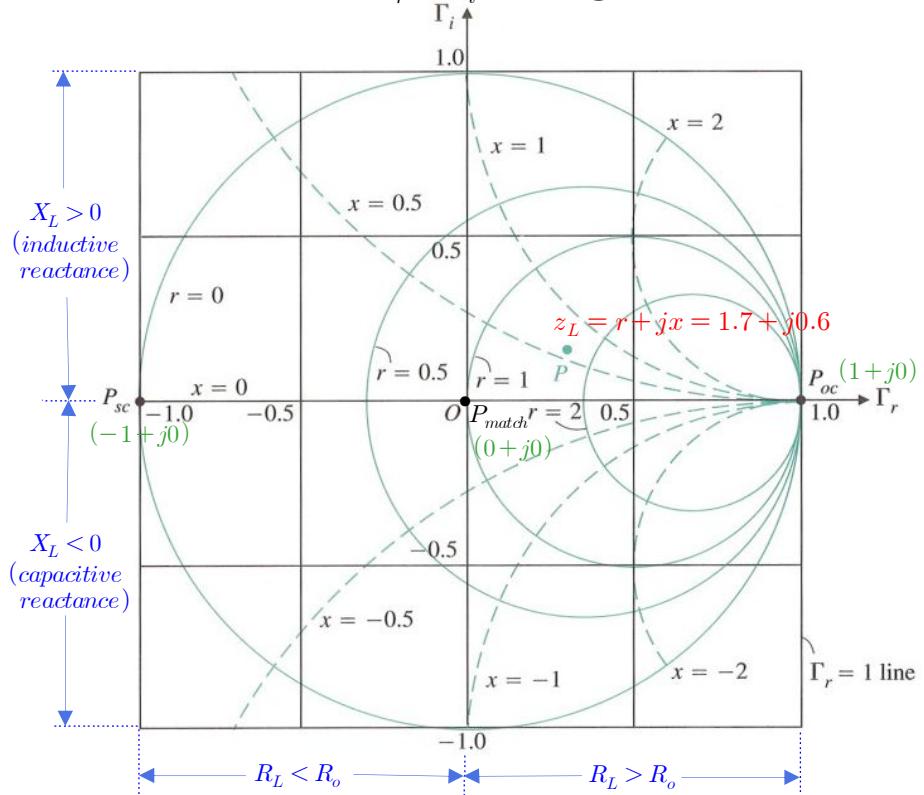


FIGURE 8-6

b) Smith Chart with $|\Gamma| - \theta_\Gamma$ polar coordinates

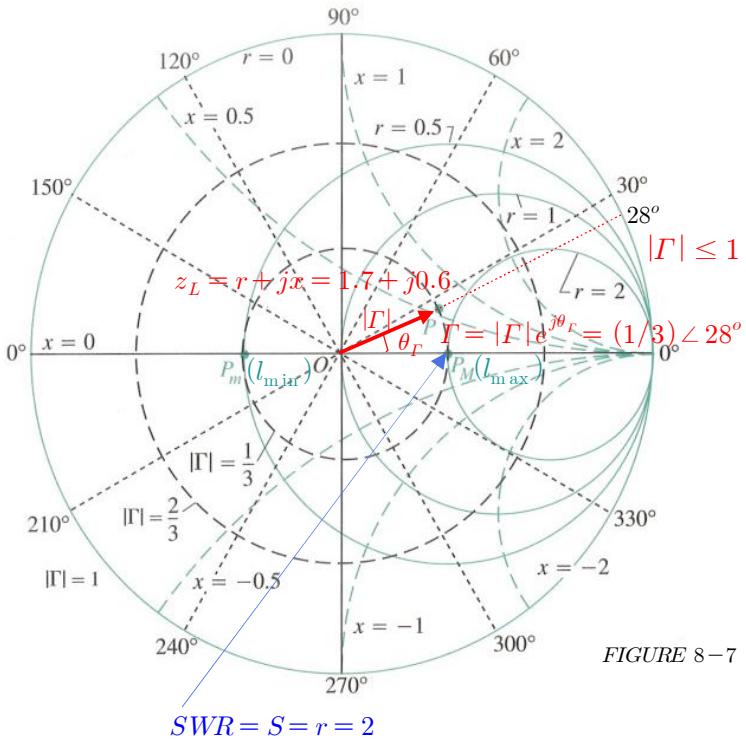


FIGURE 8-7

c) Commercially available Smith Chart


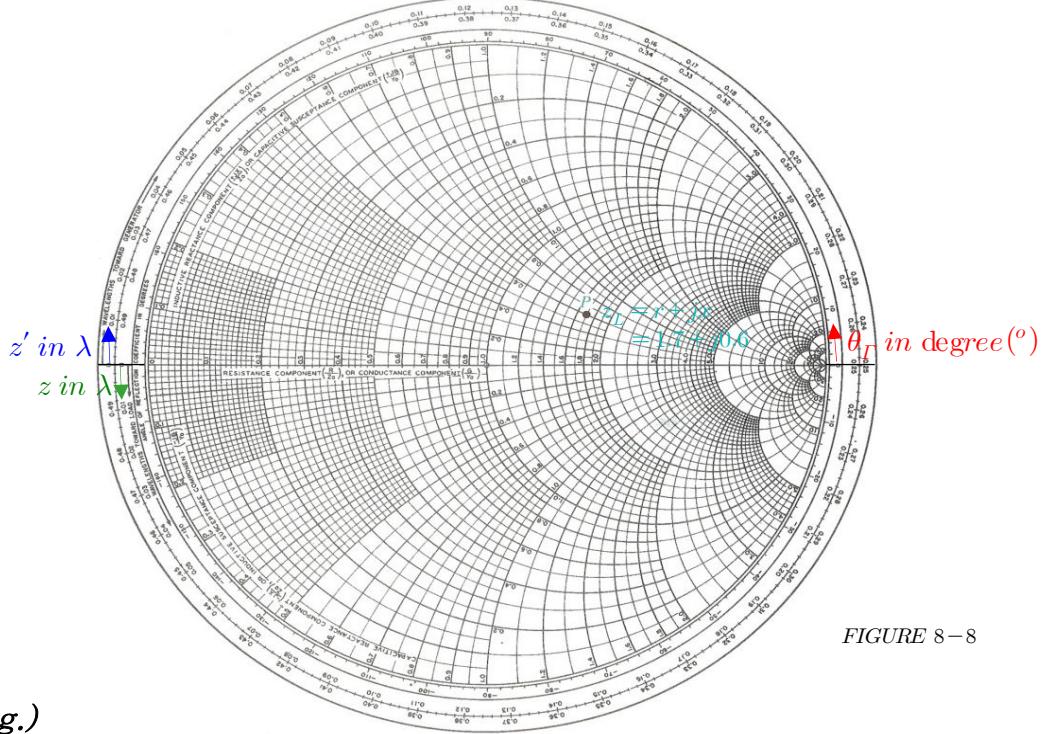


FIGURE 8-8

(e.g.)

Case $z_L = r + jx$

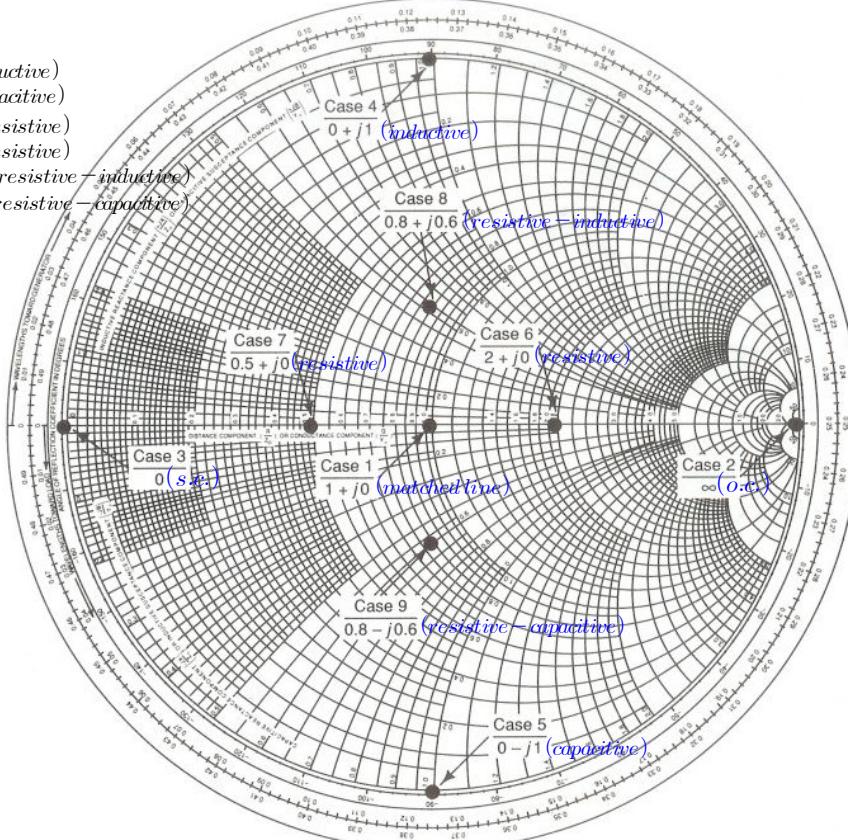- 1 $1 + j0$ (matched line)
- 2 ∞ (o.c.)
- 3 0 (s.c.)
- 4 $0 + j1$ (inductive)
- 5 $0 - j1$ (capacitive)
- 6 $2 + j0$ (resistive)
- 7 $0.5 + j0$ (resistive)
- 8 $0.8 + j0.6$ (resistive-inductive)
- 9 $0.8 - j0.6$ (resistive-capacitive)



3) Applications of the Smith Chart

a) SWR(S) and locations(l_{\min} & l_{\max}) of V_{\min} and V_{\max} on Smith Chart

Along the real Γ axis ($x = 0, X_L = 0$), $z_L = r$ ($Z_L = R_L$) in (8-99) :

$$\Gamma = \frac{R_L - R_o}{R_L + R_o} = \frac{r - 1}{r + 1} \xrightarrow{(8-91)} \frac{S - 1}{S + 1} \quad (8-106)$$

$$\Rightarrow S = r = R_L/R_o \text{ for } R_L > R_o$$

$$\Rightarrow S \text{ is numerically equal to the value of } r \text{ at } P_M$$

[SWR circle (constant- $|\Gamma|$ circle) intersects the real Γ axis at P_M]

The points P_m and P_M also represent the first distances,


l_{\min} and l_{\max} , from the load for V_{\min} and V_{\max} , respectively.

(7) and (8) on p.13 :

$$1st \ min. \ position: l_{\min} = \left(\frac{\theta_{\Gamma}}{\pi} + 1 \right) \frac{\lambda}{4} \quad (7)$$

$$1st \ max. \ position: l_{\max} = \frac{\theta_{\Gamma} \lambda}{4\pi} \text{ (for } \theta_{\Gamma} > 0 \text{) or } \frac{\theta_{\Gamma} \lambda}{4\pi} + \frac{\lambda}{2} \text{ (for } \theta_{\Gamma} < 0 \text{)} \quad (8)$$

(e.g.)

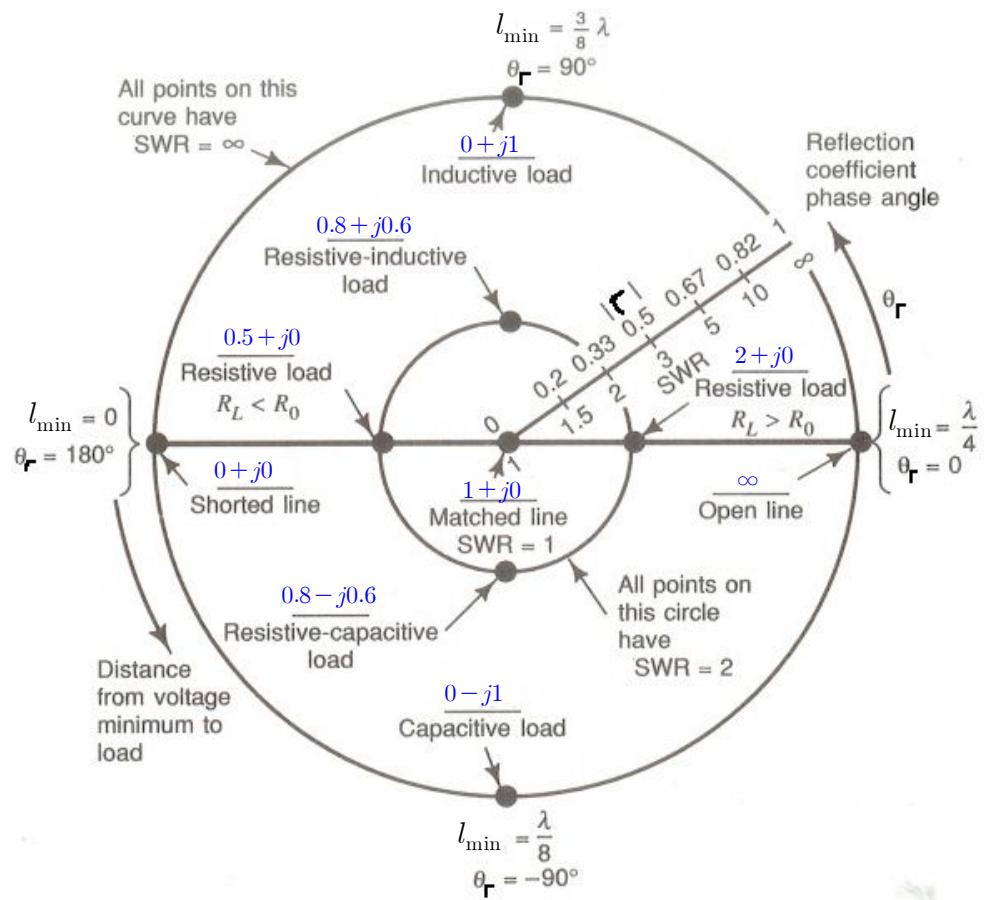

b) Normalized input impedance on Smith Chart

$$(8-77) \Rightarrow Z_i(z') = R_o \frac{1 + \Gamma e^{-j2\beta z'}}{1 - \Gamma e^{-j2\beta z'}} \quad (8-107)$$

Normalized input impedance:

$$z_i(z') \equiv \frac{Z_i}{Z_o} = \frac{1 + \Gamma e^{-j2\beta z'}}{1 - \Gamma e^{-j2\beta z'}} = \frac{1 + |\Gamma| e^{j\phi}}{1 - |\Gamma| e^{j\phi'}} \quad (8-108)$$

$$\text{where } \phi = \theta_\Gamma - 2\beta z' \quad (8-109)$$

$$(cf) (8-108) \text{ for } z' = 0 \text{ becomes } z_L = \frac{1 + |\Gamma| e^{j\theta_\Gamma}}{1 - |\Gamma| e^{j\theta_\Gamma}} \quad (8-100)$$

Similarity in form of (8-108) and (8-100)

- $\Rightarrow z_L$ can be transformed into z_i if Γ is transformed maintaining $|\Gamma|$ constant and decreasing the phase θ_Γ by $2\beta z' = 4\pi(z'/\lambda)$.
- \Rightarrow Wavelength Toward Generator (WTG) in cw direction ($z' \uparrow$)
= Outermost scale in units of λ around the perimeter
Wavelength Toward Load (WTL) in ccw direction ($z' \downarrow$)
= Inner scale in units of λ around the perimeter

Note) $\Delta z' = \lambda/2$ in $\phi \Rightarrow 2\beta\Delta z' = 4\pi(\lambda/2/\lambda) = 2\pi$
: one complete rotation around the chart

(e.g. 8-7)

Given s.c. ($z_L = 0$), lossless $R_o = 50 \ (\Omega)$, $z' = l = 0.1 \lambda$.


Find $Z_i = ?$ using the Smith Chart.

(cf) Analytical solution:

$$\begin{aligned} \text{From (8-82), } Z_{isc} &= jR_o \tan \beta l = jR_o \tan(2\pi l/\lambda) \\ &= j50 \tan\left(\frac{2\pi \times 0.1\lambda}{\lambda}\right) = j50 \tan 36^\circ = j36.3 \ (\Omega) \end{aligned}$$

Graphical solution by using Smith Chart:

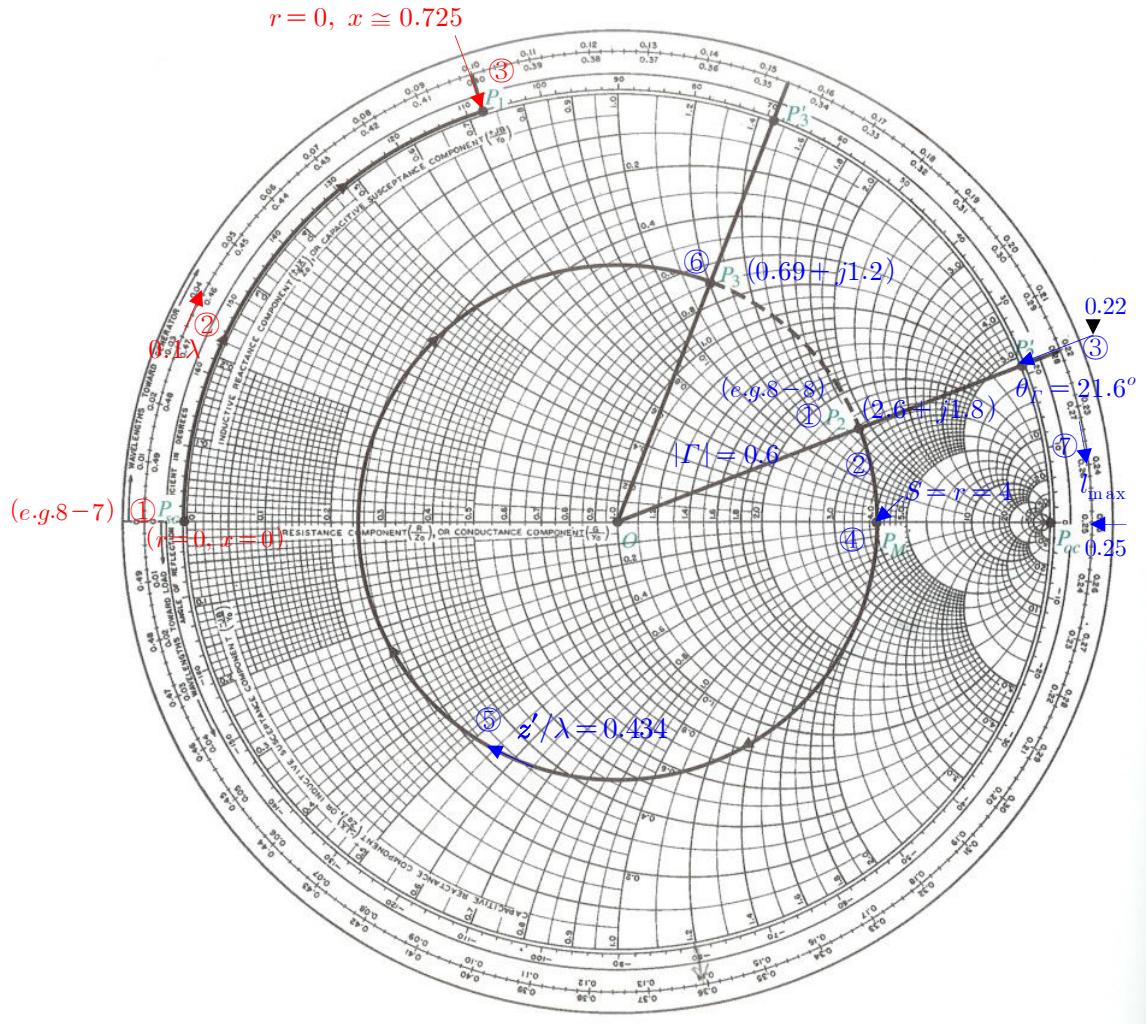- ① Start at P_{sc} ($r = 0, x = 0$)
- \rightarrow ② Move along WTG by 0.1 to P_1
- \rightarrow ③ At P_1 , read $r = 0, x \cong 0.725$
- $\Rightarrow \therefore z_i = r + jx = 0 + j0.725$
- $\Rightarrow Z_i = R_o z_i = 50(j0.725) = j36.3 \ (\Omega)$



(e.g. 8-8)

FIGURE 8-9 Smith-chart calculations for Examples 8-7 and 8-8.

Given lossless $Z_o = R_o = 100 \Omega$, $z' = l = 0.434 \lambda$, $Z_L = 260 + j180 \Omega$.

Find (a) Γ , (b) S , (c) Z_i , (d) l_{\max} using the Smith Chart.

(cf) Analytical solutions:

$$\begin{aligned}
 (a) \quad (8-88) \Rightarrow \Gamma &= \frac{Z_L - Z_o}{Z_L + Z_o} = |\Gamma| e^{j\theta_r} \\
 \Rightarrow \Gamma &= \frac{(260 + j180) - 100}{(260 + j180) + 100} = \frac{16 + j18}{36 + j18} = \frac{(16 + j18)(36 - j18)}{36^2 + 18^2} \\
 &= \frac{900 + j360}{1620} = 0.5556 + j0.2222 \cong 0.6 \angle 21.6^\circ
 \end{aligned}$$

$$(b) \quad (8-90) \Rightarrow S = \frac{1 + |\Gamma|}{1 - |\Gamma|} = \frac{1 + 0.6}{1 - 0.6} = 4$$

$$\begin{aligned}
 (c) \quad (8-79) \Rightarrow Z_i &= R_o \frac{Z_L + jR_o \tan \beta l}{R_o + jZ_L \tan \beta l} = 100 \frac{(260 + j180) + j100 \tan(2\pi \times 0.434\lambda / \lambda)}{100 + j(260 + j180) \tan(2\pi \times 0.434\lambda / \lambda)} \\
 &= 100 \frac{260 + j[180 + 100 \tan(0.864\pi)]}{[100 - 180 \tan(0.868\pi)] + j260 \tan(0.868\pi)} = 69 + j120 \Omega
 \end{aligned}$$

$$(d) \quad (8) \text{ on p.13} \Rightarrow l_{\max} = \frac{\theta_r \lambda}{4\pi} = \frac{21.6^\circ \lambda}{4 \times 180^\circ} = 0.03 \lambda$$

Graphical solution by using Smith Chart:

(a) ① Start at $P_2(z_L = Z_L/R_o = 2.6 + j1.8)$

→ ② Draw a circle of radius $\overline{OP_2} : \frac{\overline{OP_2}}{\overline{OP'_2}} = |\Gamma| = 0.6$

→ ③ At P'_2 , read $\theta_\Gamma = 21.6^\circ$

(or $z'/\lambda = 0.220 \Rightarrow (0.25 - 0.22) \times 4\pi = 0.12\pi = 21.6^\circ$)

$$\Rightarrow \therefore \Gamma = |\Gamma| e^{j\theta_\Gamma} = 0.6 \angle 21.6^\circ$$

(b) ④ Read r at P_M where the $|\Gamma| = 0.6$ circle intersects with the positive-real axis

$$\Rightarrow \therefore S = r = \underline{4}$$

(c) ⑤ Move P_2 or P'_2 along WTG by $z'/\lambda = 0.434$ up to P_3 or P'_3

→ ⑥ At P_3 , read $r = 0.69, x = 1.2$

$$\Rightarrow Z_i = R_o z_i = 100(0.69 + j1.2) = \underline{69 + j120 \ (\Omega)}$$

(d) ⑦ At P_M where the voltage is a maximum,

distance from the load: $l_{\max} = (0.25 - 0.22)\lambda = \underline{0.03\lambda}$

c) Normalized admittance on Smith Chart

Admittance corresponding to Z :

$$Y = \frac{1}{Z} = \frac{1}{R+jX} = \frac{R-jX}{R^2+X^2} = G+jB \quad (\text{S}) \quad (16)$$

where $G = R/(R^2+X^2)$ (S) : conductance (17)

$B = -X/(R^2+X^2)$ (S) : susceptance (18)

Normalized load admittance:

$$y_L \equiv \frac{Y_L}{Y_o} = \frac{1}{z_L} = \frac{Z_o}{Z_L} = Z_o Y_L = g + jb \quad (8-112, 113)$$

$$(8-100) z_L = \frac{1+\Gamma}{1-\Gamma} \quad \text{in} \quad (8-112) : y_L = \frac{1}{z_L} = \frac{1-\Gamma}{1+\Gamma} \quad (19)$$

Normalized input impedance of a quarter-wave lossless line:

$$(8-78) Z_i = Z_o \frac{1+\Gamma e^{-2\gamma l}}{1-\Gamma e^{-2\gamma l}} \quad (19)$$

$$\Rightarrow z_i(l = \lambda/4) = \frac{1+\Gamma e^{-j2\beta l}}{1-\Gamma e^{-j2\beta l}} = \frac{1+\Gamma e^{-j\pi}}{1-\Gamma e^{-j\pi}} = \frac{1-\Gamma}{1+\Gamma} \downarrow y_L \quad (20)$$

$$\text{Note)} \quad (8-111) Z_i = \frac{Z_o^2}{Z_L} \Rightarrow \frac{Z_i}{Z_o} = \frac{Z_o}{Z_L} \Rightarrow z_i = y_L \quad (20)$$

Therefore, z_L can be transformed into y_L by rotating $\lambda/4$ (180°) on the Smith Chart.

$\Rightarrow z_L$ and y_L are diametrically opposite to each other on the $|\Gamma|$ -circle
 $(r \rightarrow g, x \rightarrow b, o.c. \leftrightarrow s.c. \Rightarrow admittance chart)$

(e.g. 8-9)

Given $Z = 95 + j20$ (Ω), find Y .

Assume $Z_o = R_o = 50$ (Ω),
then $z = (95 + j20)/50 = 1.9 + j0.4$

$$\begin{aligned} \Rightarrow Y &= y/R_o \\ &= (0.5 - j0.1)/50 \\ &= 0.01 - j0.002 \text{ (S)} \end{aligned}$$

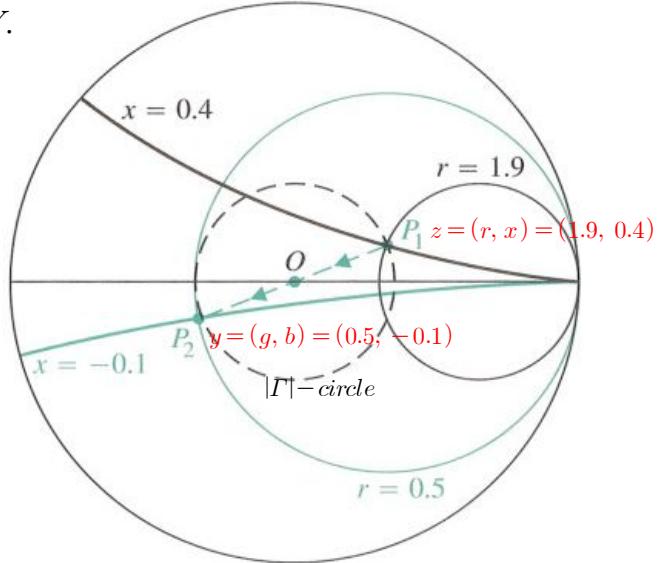


FIGURE 8-10

(e.g. 8-10)

Given lossless o.c. $Z_o = R_o = 300$ (Ω), $z' = l = 0.04\lambda$, find Y_i .

$$\begin{aligned} Y_i &= y_i/Z_o \\ &= (0 + j0.26)/300 \\ &\cong j0.00087 \text{ (S)} \\ &= j0.87 \text{ (mS)} \end{aligned}$$

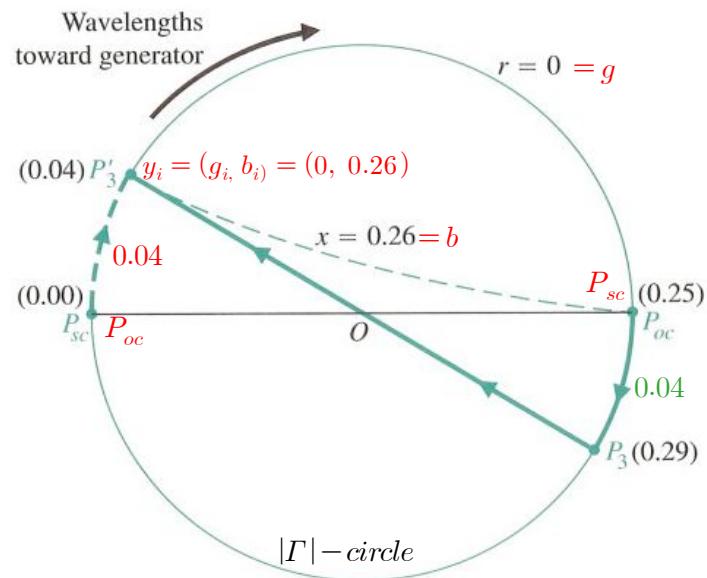


FIGURE 8-11

B. Transmission-Line Impedance Matching

1) Impedance-Matching Network


$Z_L = Z_o \Rightarrow$ Matched line

(No reflection, no distortion, no power loss at the load)

In general, $Z_L \neq Z_o$

\Rightarrow needs an **impedance-matching network** having $Z_i = Z_o$

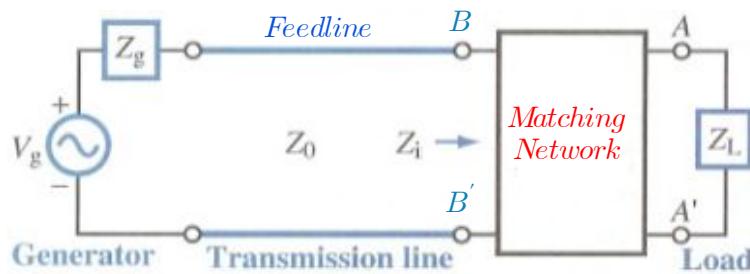
[No reflection at the line terminal BB', usually consists of inductors(L) and capacitors(C) to avoid ohmic losses]



For a lossless line ($Z_o = R_o + j0$), $Z_L = R_L + jX_L = R_o$ for matching
i.e., $X_L = 0$ for matching.

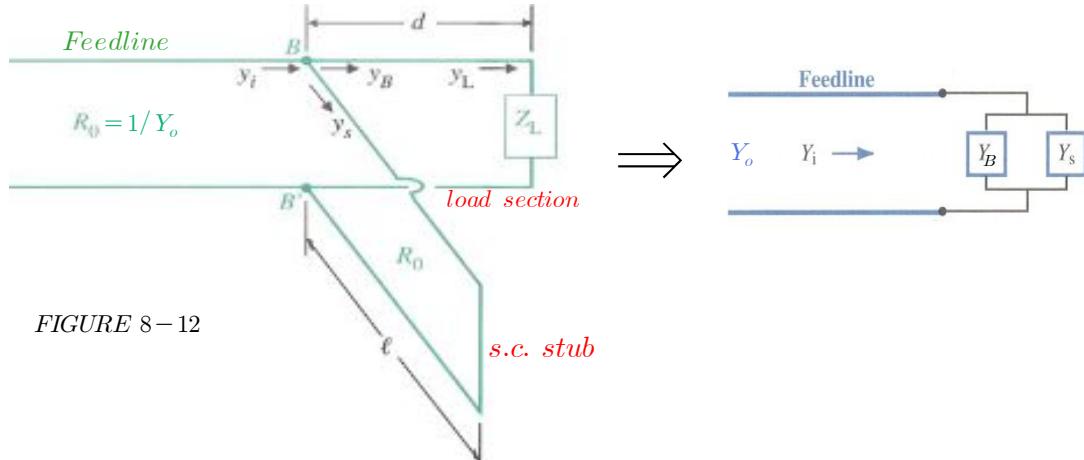2) Single-stub method for impedance matching

= short circuit (or open circuit) connected at a lossless transmission line in parallel with another line connecting the load.



Wish to determine the location d and the length l for impedance- (or admittance) matching such that

$$Y_i = Y_o = Y_B + Y_s \quad (8-114) \quad \Rightarrow \quad 1 = y_B + y_s \quad (8-115)$$

where $y_B = 1 + jb_B$ (find d) and $y_s = -jb_B$ (find l) $\quad (8-116, 117)$

Procedure for single-stub impedance-matching:

- ① Start at $z_L \rightarrow y_L$
- ② Find intersections of the $|I|$ -circle and the $g=1$ circle.
 $y_{B1} = 1 + jb_{B1}$ and $y_{B2} = 1 + jb_{B2}$
- ③ Determine d_1, d_2 from the angles between y_L and y_{B1}, y_{B2}
- ④ Determine l_1, l_2 from the angles between P_{sc} (extreme right) and $y_{s1} = -jb_{B1}, y_{s2} = -jb_{B2}$

(e.g. 8-11)

Given lossless $Z_o = R_o = 50 \Omega$, $Z_L = 35 - j47.5 \Omega$, find d and l .

① $z_L = Z_L/R_o = 0.70 - j0.95$

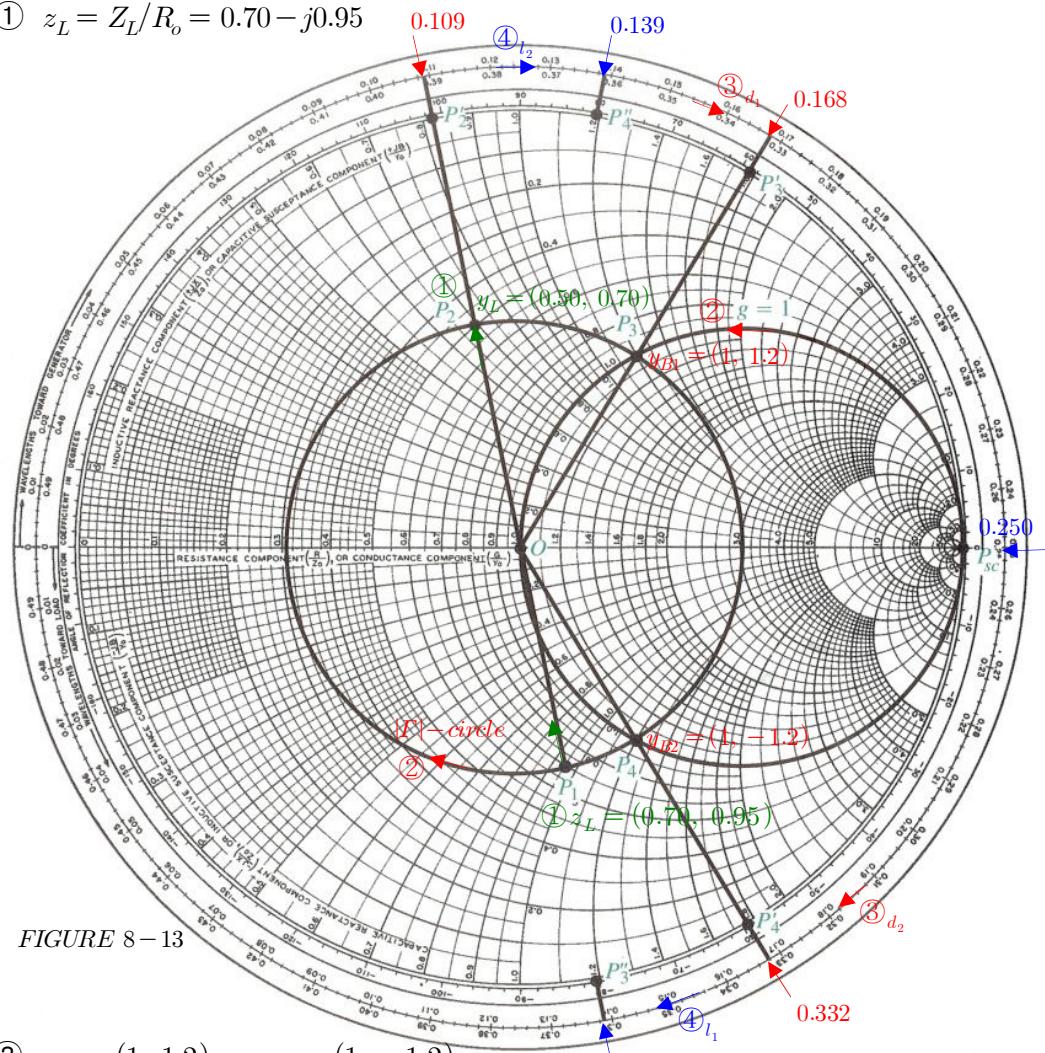


FIGURE 8-13

② $y_{B1} = (1, 1.2), y_{B2} = (1, -1.2)$

③ $d_1 = (0.168 - 0.109)\lambda = 0.059\lambda$ and $d_2 = (0.332 - 0.109)\lambda = 0.223\lambda$

④ $l_1 = (0.361 - 0.250)\lambda = 0.111\lambda$ and $l_2 = (0.139 + 0.250)\lambda = 0.389\lambda$

Homework Set 5

- 1) P.8-18
- 2) P.8-20
- 3) P.8-21
- 4) P.8-24
- 5) P.8-27