

Chapter 2: Structural Modeling

Prof. Soo-Ik Chae

Objectives

After completing this chapter, you will be able to:

- ❖ Describe what is the structural modeling
- ❖ Describe how to instantiate gate primitives
- ❖ Describe how to model a design in gate primitives
- ❖ Describe inertial and transport delays
- ❖ Describe how to specify delays in gates
- ❖ Describe hazards and their effects in gate networks

Structural Modeling

- ❖ **Structural style:** Modeled as a set of interconnected components.
 - **Modules/UDPs**
 - Modules/UDPs may or may not be synthesized.
 - A gate-level module is usually synthesizable.
 - **Gate primitives:** There are 12 gate primitives.
 - Gate primitives are synthesizable.
 - **Switch primitives:** There are 16 switch primitives.
 - Will **not be covered**
 - They are usually used to model a **new logic gate circuit** at switch level.
 - They are not synthesizable, in general.

Gate Primitives

❖ and/or gates

- have one scalar output and multiple scalar inputs
- are used to realize the basic logic operations
- include



and or xor nand nor xnor

❖ buf/not gates

- have one scalar input and one or **multiple** scalar outputs
- are used to realize the **not** operation,
- are used to buffer the output of an **and/or gate**,
- are used as **controlled buffers**
- include

buf not bufif0 notif0 bufif1 notif1



and/nand Gates

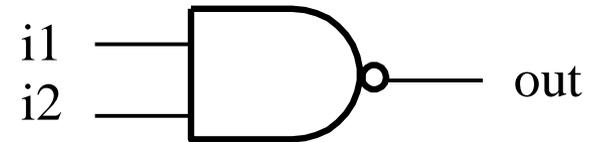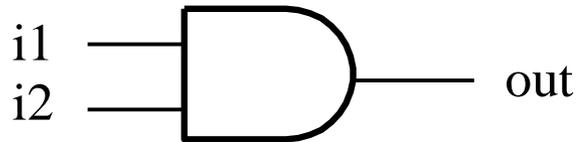

and		i2			
		0	1	x	z
i1	0	0	0	0	0
	1	0	1	x	x
	x	0	x	x	x
	z	0	x	x	x

nand		i2			
		0	1	x	z
i1	0	1	1	1	1
	1	1	0	x	x
	x	1	x	x	x
	z	1	x	x	x



or/nor Gates

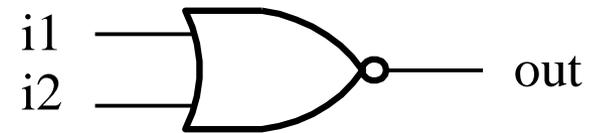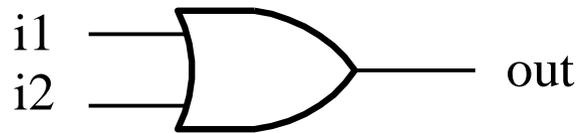

or		i2			
		0	1	x	z
i1	0	0	1	x	x
	1	1	1	1	1
	x	x	1	x	x
	z	x	1	x	x

nor		i2			
		0	1	x	z
i1	0	1	0	x	x
	1	0	0	0	0
	x	x	0	x	x
	z	x	0	x	x


xor/xnor Gates

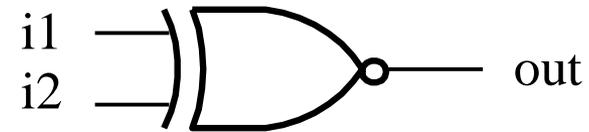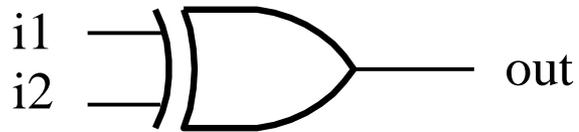


xor		i2			
		0	1	x	z
i1	0	0	1	x	x
	1	1	0	x	x
	x	x	x	x	x
	z	x	x	x	x

xnor		i2			
		0	1	x	z
i1	0	1	0	x	x
	1	0	1	x	x
	x	x	x	x	x
	z	x	x	x	x

buf/not Gates


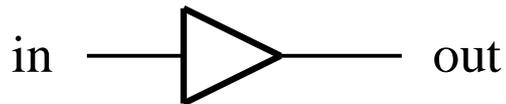


in	out
0	0
1	1
x	x
Z	x

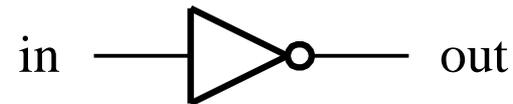

in	out
0	1
1	0
x	x
Z	x

bufif0/notif0 Gates

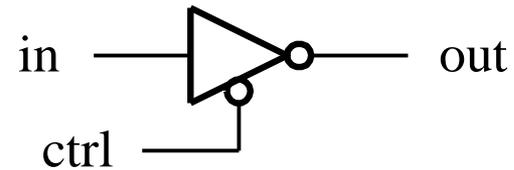
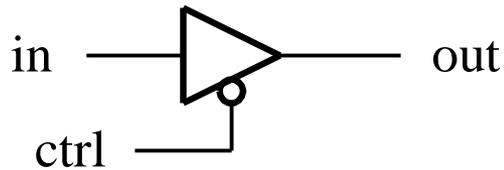


bufif0		ctrl			
		0	1	x	z
in	0	0	z	L	L
	1	1	z	H	H
	x	x	z	x	x
	z	x	z	x	x

notif0		ctrl			
		0	1	x	z
in	0	1	z	H	H
	1	0	z	L	L
	x	x	z	x	x
	z	x	z	x	x

Note that: **L** represents 0 or z and
H represents 1 or z.

bufif1/notif1 Gates

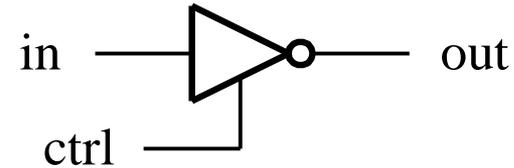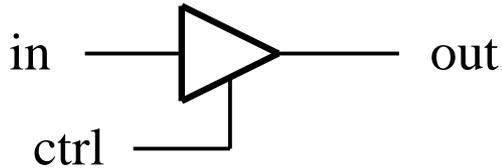

bufif1		ctrl			
		0	1	x	z
in	0	z	0	L	L
	1	z	1	H	H
	x	z	x	x	x
	z	z	x	x	x

notif1		ctrl			
		0	1	x	z
in	0	z	1	H	H
	1	z	0	L	L
	x	z	x	x	x
	z	z	x	x	x

Note that: **L** represents **0** or **z** and
H represents **1** or **z**.


Instantiation of Basic Gates

❖ To instantiate and/or gates

```
gatename [instance_name](output, input1, input2, ..., inputn);
```

- `instance_name` is **optional**.
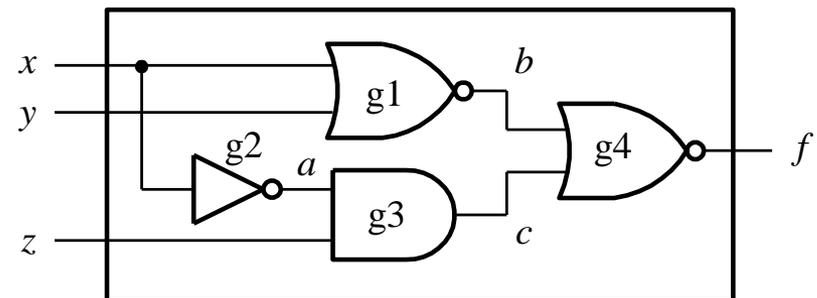
```
module basic_gates (x, y, z, f) ;
input  x, y, z;
output f;
wire a, b, c; // internal nets
// Structural modeling using basic gates.
nor g1 (b, x, y);
not g2 (a, x);
and g3 (c, a, z);
nor g4 (f, b, c);
endmodule
```



Array of Instances

- ❖ Array instantiations may be a synthesizer dependent!
 - **Suggestion:** you had better to check this feature before using the synthesizer.


```
wire [3:0] out, in1, in2;  
// basic array instantiations of nand gate.  
nand n_gate[3:0] (out, in1, in2);  
  
// this is equivalent to the following:  
nand n_gate0 (out[0], in1[0], in2[0]);  
nand n_gate1 (out[1], in1[1], in2[1]);  
nand n_gate2 (out[2], in1[2], in2[2]);  
nand n_gate3 (out[3], in1[3], in2[3]);
```

An Example --- A 1-Bit Full Adder

```

module full_adder_structural(x, y, c_in, s, c_out);
// I/O port declarations
input  x, y, c_in;
output s, c_out;
wire  s1, c1, c2, c3;
// Structural modeling of the 1-bit full adder.
xor  xor_s1(s1, x, y);    // compute sum.
xor  xor_s2(s, s1, c_in);
and  and_c1(c1, x, y);    // compute carry out.
and  and_c2(c2, x, c_in);
and  and_c3(c3, y, c_in);
or   or_cout(c_out, c1, c2, c3);
endmodule

```

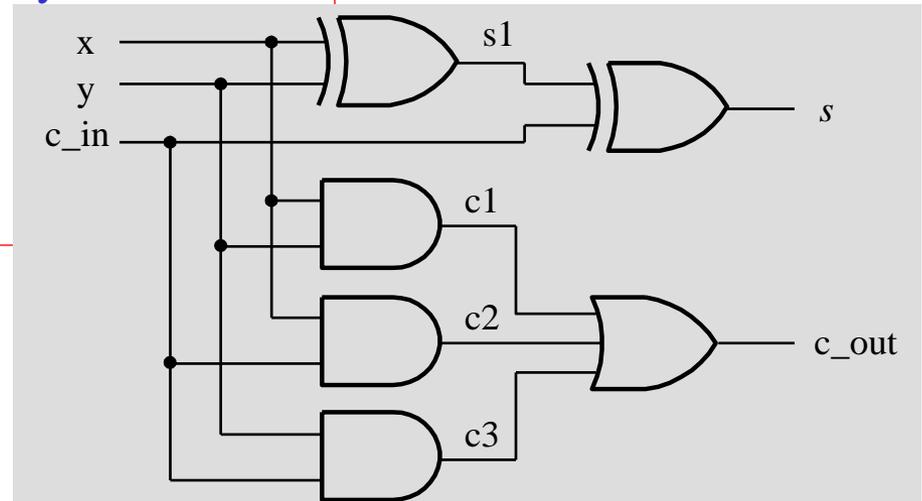


An Example --- A 4-to-1 Multiplexer


```

module mux4_to_1_structural (i0, i1, i2, i3, s1, s0, out);
input  i0, i1, i2, i3, s1, s0;
output out;
wire  s1n, s0n; // Internal wire declarations
wire  y0, y1, y2, y3;
// Gate instantiations
not (s1n, s1); // Create s1n and s0n signals.
not (s0n, s0);
and (y0, i0, s1n, s0n); // 3-input and gates instantiated
and (y1, i1, s1n, s0);
and (y2, i2, s1, s0n);
and (y3, i3, s1, s0);
or (out, y0, y1, y2, y3); // 4-input or gate instantiated
endmodule

```

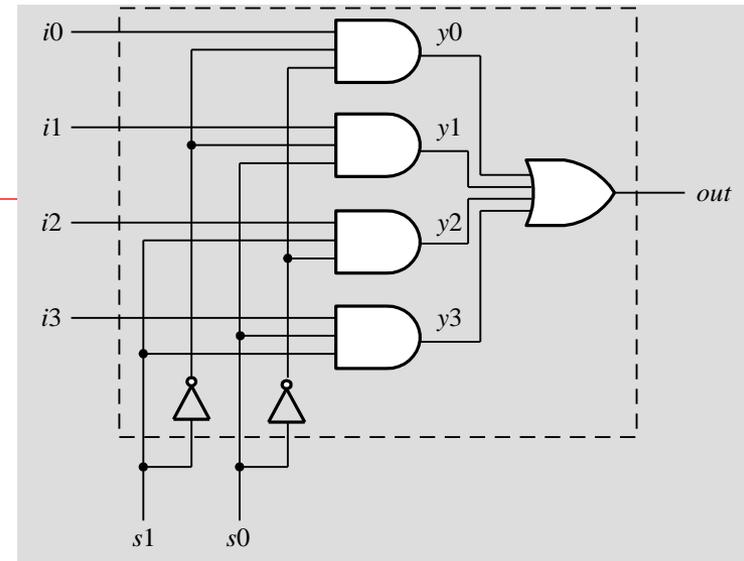

An Example --- A 9-Bit Parity Generator

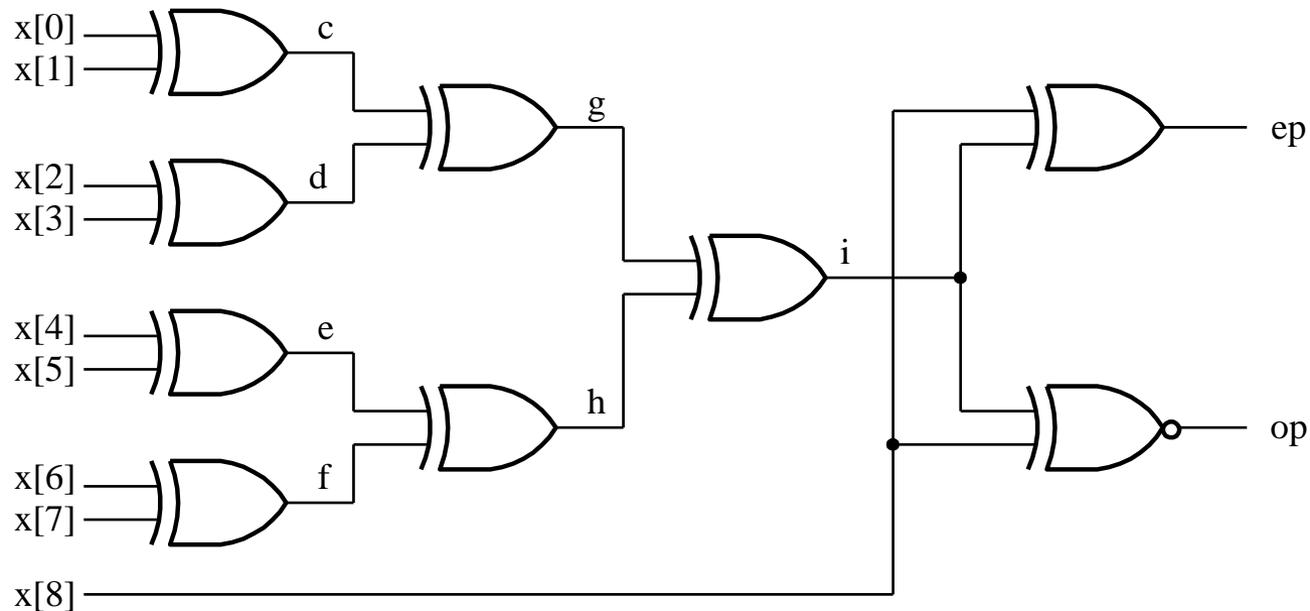

An Example --- A 9-Bit Parity Generator


```
module parity_gen_9b_structural(x, ep, op);  
// I/O port declarations  
input  [8:0] x;  
output ep, op;  
wire   c, d, e, f, g, h, j;  
  xor xor_11(c, x[0], x[1]); // first level  
  xor xor_12(d, x[2], x[3]);  
  xor xor_13(e, x[4], x[5]);  
  xor xor_14(f, x[6], x[7]);  
  xor xor_21(g, c, d);      // second level  
  xor xor_22(h, e, f);  
  xor xor_31(i, g, h);     // third level  
  xor xor_ep(ep, i, x[8]); // fourth level  
  xnor xnor_op(op, i, x[8]);  
endmodule
```

Applications of Tristate Buffers

❖ To instantiate tristate buffers

```
buf_name[instance_name](output, input, control);
```

- The instance_name is **optional**.

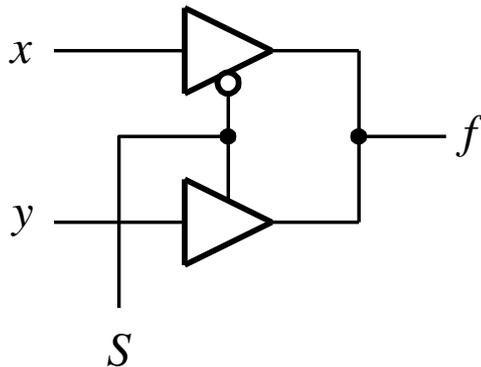

```
// Data selector – 2-to-1 mux
module two_to_one_mux_tristate (x, y, s, f);
input  x, y, s;
output f;
// internal declaration
tri  f;
// data selector body
    bufif0 b1 (f, x, s); // enable if s = 0
    bufif1 b2 (f, y, s); // enable if s = 1
endmodule
```

Inertial and Transport Delay Models


❖ Inertial delay model

- The signal events do not persist long enough will not be propagated to the output.
- It is used to model gate delays (**RC** delays).
- It is the default delay model for HDL (Verilog HDL and VHDL).

❖ Transport delay model

- Any signal events will be propagated to the output.
- It is used to model net (i.e. wires) delays.
- The default delay of a net is zero.


The Effects of Inertial Delays

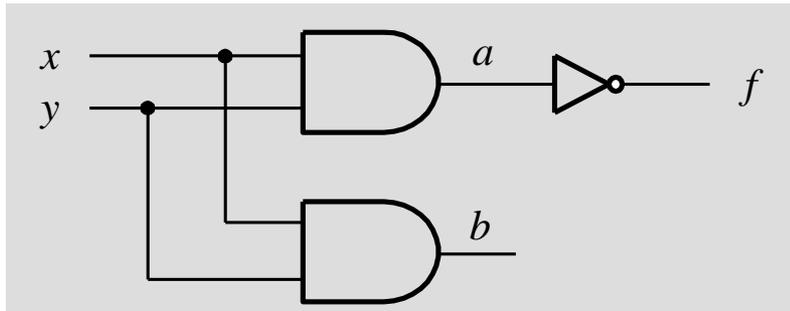


```

wire a;
and #4 (b, x, y); // Inertial delay
and #4 (a, x, y);
not #1 (f, a);
    
```

↔ Inertial delay

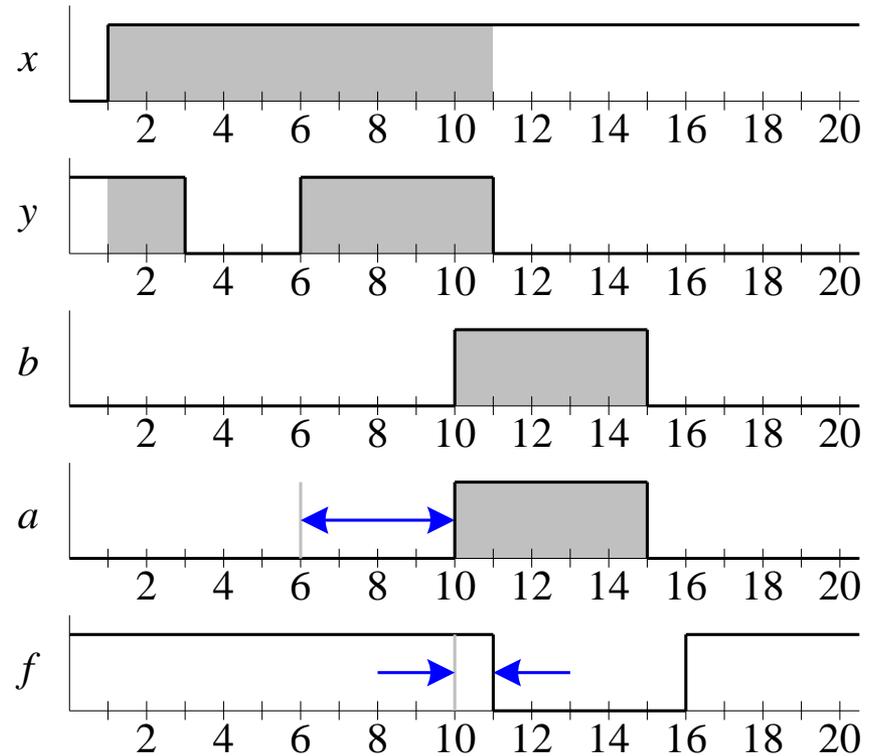

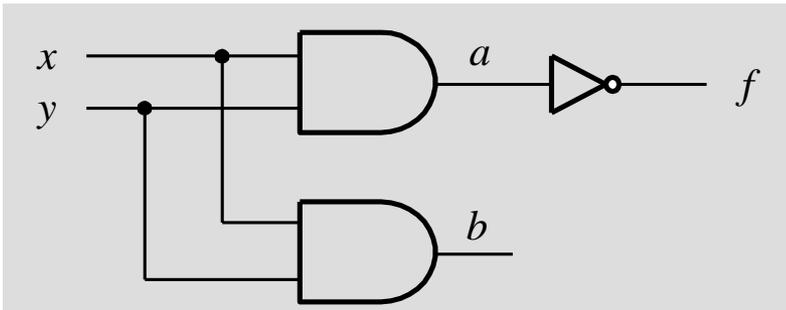
The Effects of Transport and Inertial Delays



```

wire #2 a;      // Transport delay
and #4 (b, x, y); // Inertial delay
and #4 (a, x, y);
not #1 (f, a);
    
```

 Inertial delay
 Transport delay

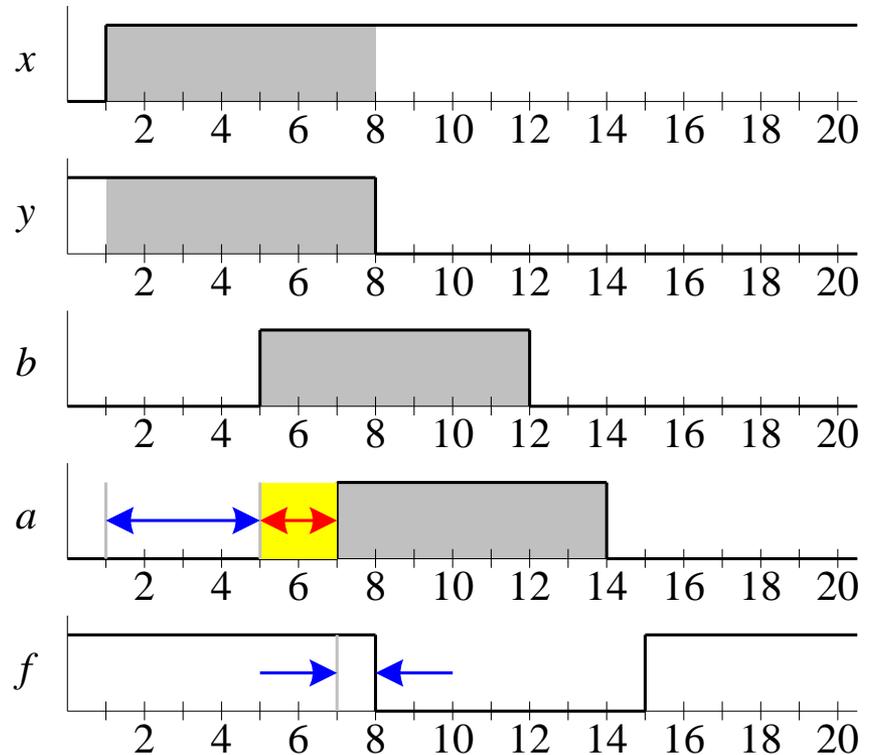

Gate Delay Specifications

❖ Gate Delay Specifications

- Specify propagation delay only:
 - `gatename #(prop_delay) [instance_name](output, in_1, in_2,...);`
- Specify both rise and fall times:
 - `gatename #(t_rise, t_fall) [instance_name](output, in_1, in_2,...);`
- Specify rise, fall, and turn-off times:
 - `gatename #(t_rise, t_fall, t_off) [instance_name](output, in_1, in_2,...);`
 - Turn-off time: transition to high-impedance value
 - When a value changes to x, the delay is the smallest of the two or three delays

Delay specifier: `min:typ:max`

Gate Delay Specifications

Table 7-9—Rules for propagation delays

From value:	To value:	Delay used if there are	
		2 delays	3 delays
0	1	d1	d1
0	x	min(d1, d2)	min(d1, d2, d3)
0	z	min(d1, d2)	d3
1	0	d2	d2
1	x	min(d1, d2)	min(d1, d2, d3)
1	z	min(d1, d2)	d3
x	0	d2	d2
x	1	d1	d1
x	z	min(d1, d2)	d3
z	0	d2	d2


- `gatename #(d1) [instance_name](output, in_1, in_2,...);`
- `gatename #(d1, d2) [instance_name](output, in_1, in_2,...);`
- `gatename #(d1, d2, d3) [instance_name](output, in_1, in_2,...);`

Gate Delays Specifications


```
// Only specify one delay  
and #(5) a1 (b, x, y);  
  
// Only specify one delay using min:typ:max  
not #(10:12:15) n1 (a, x);  
  
// Specify two delays using min:typ:max  
and #(10:12:15, 12:15:20) a2 (c, a, z);  
  
// Specify three delays using min:typ:max  
or #(10:12:15, 12:15:20, 12:13:16) o2 (f, b, c);
```

Hazards and Their Effects

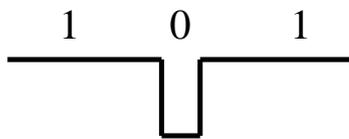
- ❖ A hazard is an unwanted short-width output signal when the inputs to a combinational circuit changes.
- ❖ These unwanted signals are generated when different paths from input to output have different propagation delays.
 - Static hazard
 - Dynamic hazard



(a) static-1 hazard

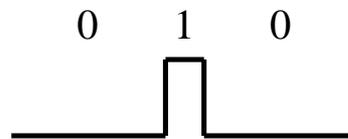


(b) static-0 hazard

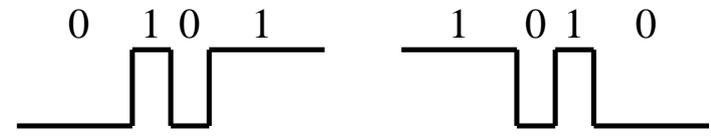

(c) dynamic hazard


A Static Hazard Example

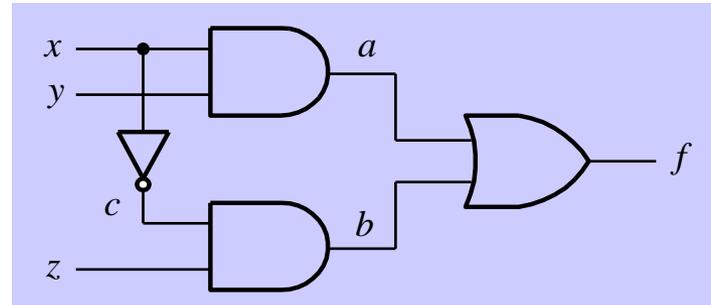

```

module hazard_static (x, y, z, f);
input  x, y, z;
output f;
// internal declaration
wire a, b, c; // internal net
// logic circuit body
    and #5  a1 (a, x, y);
    not #5  n1 (c, x);
    and #5  a2 (b, c, z);
    or #5   o2 (f, b, a);
endmodule

```

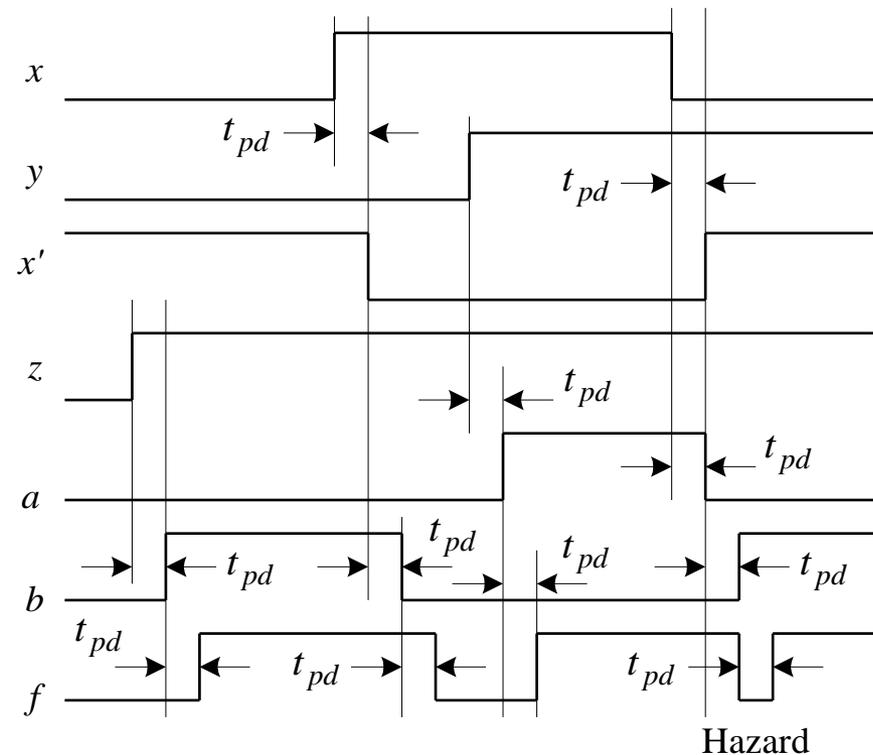

A Dynamic Hazard Example

