

Chapter 15: Design Examples


Prof. Soo-Ik Chae

Objectives

After completing this chapter, you will be able to:

- ❖ Describe basic structures of μ P systems
- ❖ Understand the basic operations of bus structures
- ❖ Understand the essential operations of data transfer
- ❖ Understand the design principles of GPIOs
- ❖ Understand the design principles of timers
- ❖ Understand the design principles of UARTs
- ❖ Describe the design principles of CPUs

A Basic μ P System

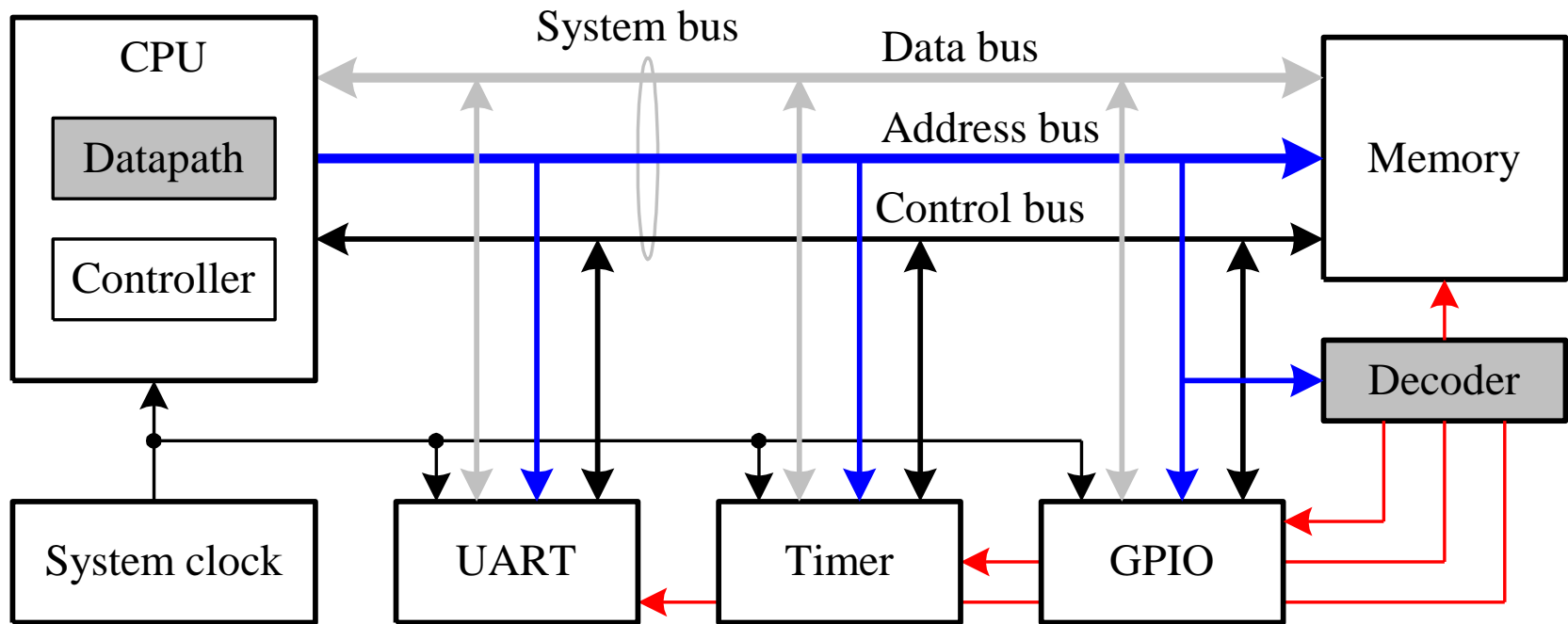


Bus Structures

- ❖ A bus is a set of wires used to transport information between two or more devices in a digital system.
- ❖ Types of buses:
 - **tristate bus**
 - When realizing by using tristate buffers.
 - **multiplexer-based bus**
 - When realizing by using multiplexers.
- ❖ The tristate bus is often called bus for short.

A Tristate Bus

❖ Tristate bus

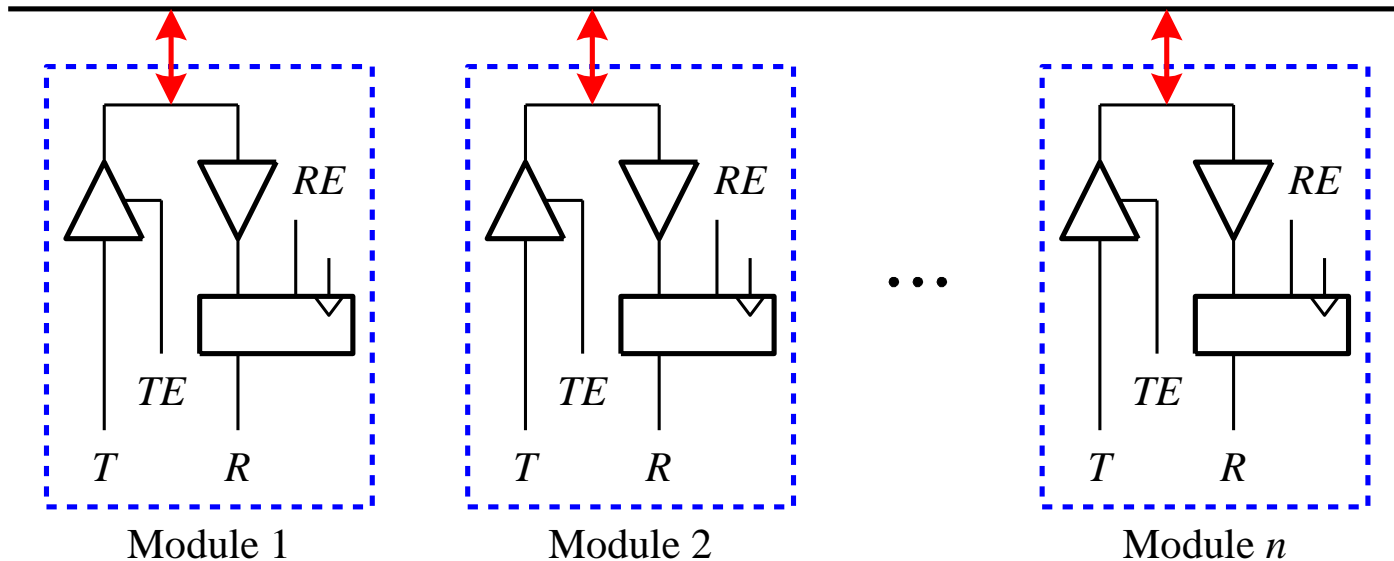
- A bidirectional interface drives a signal T to the bus and samples a signal on the bus onto an internal signal R .
- Only one module is allowed to transmit signal on the bus.




A Tristate Bus Example

```
// a tristate bus example
module tristate_bus (data, enable, qout);
parameter N = 2; // define bus width
input  enable;
input  [N-1:0] data;
output [N-1:0] qout;
wire   [N-1:0] qout;

 // the body of tristate bus
assign qout = enable ? data : {N{1'bz}};
endmodule
```



A Bidirectional Bus Example

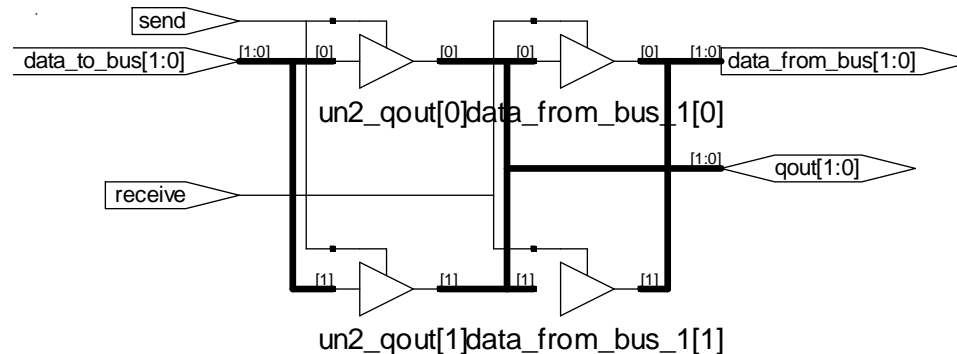


```
// a bidirectional bus example
module bidirectional_bus (data_to_bus, send, receive, data_from_bus, qout);
parameter N = 2;          // define bus width
input  send, receive;
input  [N-1:0] data_to_bus;
output [N-1:0] data_from_bus;
inout  [N-1:0] qout;      // bidirectional bus
wire   [N-1:0] qout, data_from_bus;
// the body of tristate bus
assign data_from_bus = receive ? qout : {N{1'bz}};
assign          qout = send ? data_to_bus : {N{1'bz}};
endmodule
```

A Multiplexer-Based Bus

❖ Multiplexer-based bus

 - It can avoid the large amount of capacitive load.
- It has much less the propagation delay than the tristate bus when the number of modules attached to it is large enough.




Bus Arbitration


- ❖ The operation that chooses one transmitter from multiple ones attempting to transmit data on the bus is called a **bus arbitration**.
- ❖ The device used to perform the function of bus arbitration is known as a **bus arbiter**.

Daisy-Chain Arbitration

 
- ❖ 소자가 직렬로 연결되고 신호가 한 소자에서 다른 소자로 통과하는 버스를 따라 신호를 전달하는 방식. 데이지 체인(daisy chain) 체계는 버스 상의 소자의 전기적 위치에 기반하여 소자의 우선 순위를 할당한다.



(a) Daisy-chain arbitration

 


Centralized arbitration

 


Daisy-Chain Arbitration

 Fixed priority: composed of a priority encoder and a decoder



(a) A bit cell

 

(b) A 4-request daisy-chain arbiter

Figure 15.6: The logic diagram of a 4-request daisy-chain bus arbiter.

Round-Robin Arbitration

$$\text{next_}p_i = \text{anyg}' \cdot p_i + g_{(i-1)} \text{ mod } n$$

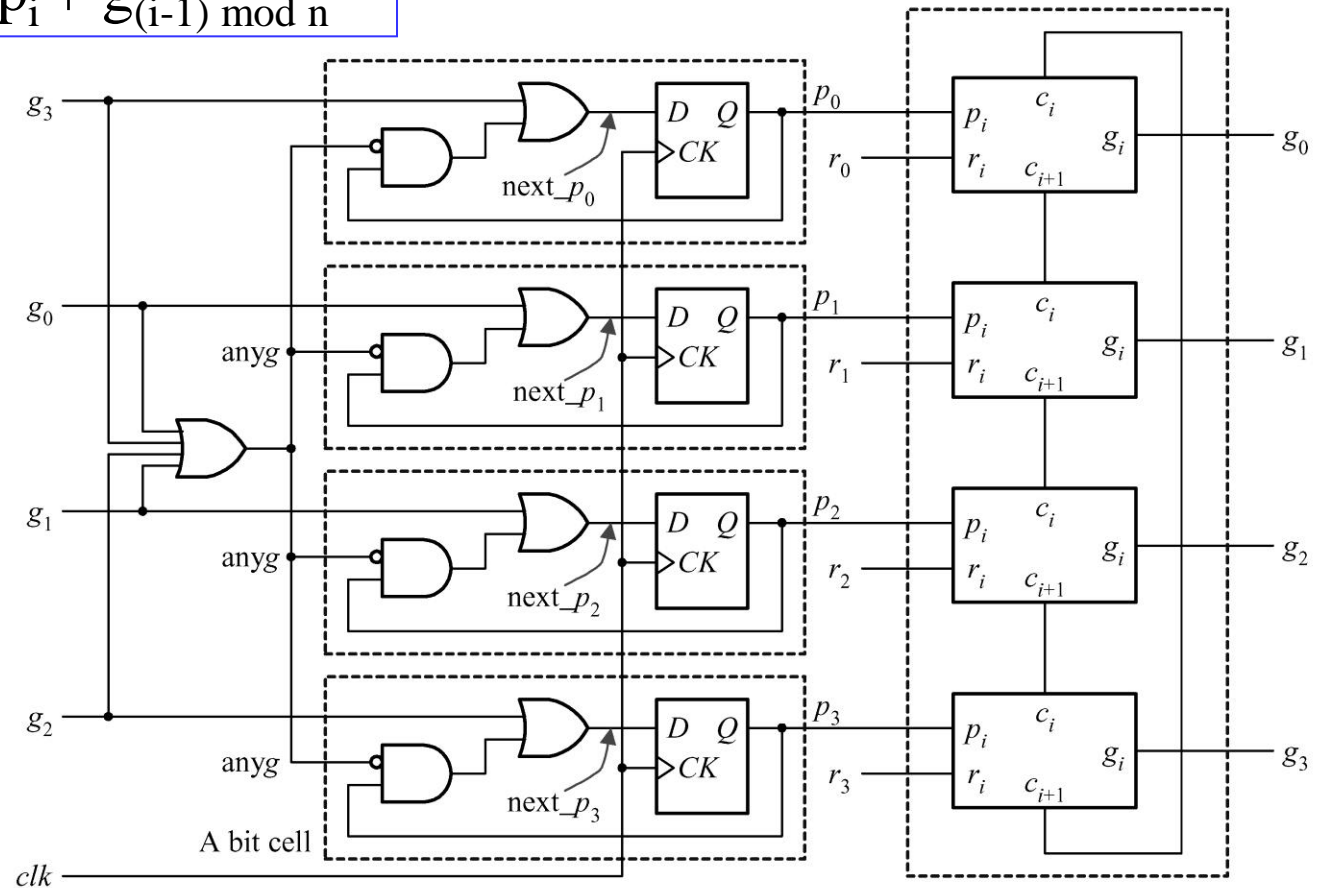


Figure 15.8: The logic diagram of a 4-request round-robin bus arbiter.


Data Transfer Modes

- ❖ Data transfer modes:
 - **synchronous** mode
 - **asynchronous** mode
- ❖ Regardless of data transfer modes, the actual data can be transferred in:
 - **parallel**: a bundle of signals in parallel
 - **serial**: a stream of bits


Synchronously Parallel Data Transfers

- ❖ Each data transfer is in synchronism with clock signal.
 - **Bus master:** A device generates address and command.
 - **Bus slave:** A device receives the address and the command from the bus.
- ❖ Synchronous bus transfers can be further divided into two types:
 - **Single-clock** bus cycle
 - **Multiple-clock** bus cycle

Synchronously Parallel Data Transfers

 

(a) Single-clock bus cycle

 


(b) Multiple-clock bus cycle

Synchronously Serial Data Transfers


- ❖ In synchronous serial data transfer, the clock signal is sending along with the data.
 - **Explicitly clocking scheme**
 - The clock signal is sent along with data explicitly as a separate signal.
 - **Implicitly clocking scheme**
 - The clock signal is encoded into the data stream.
 - The clock signal is then extracted at the receiver before sampling the data.

Synchronously Serial Data Transfers

 ❖ Examples of synchronously serial data transfer



 (a) Serial data transfer with explicitly clocking





(b) Serial data transfer with implicitly clocking (NRZ code)

Asynchronous Data Transfers

- ❖ Each data transfer occurs at random
- ❖ The data transfer may be controlled by using:
 - **strobe scheme**
 - **handshaking scheme**
- ❖ Both strobe and handshaking are used extensively on numerous occasions that require the transfer of data between two asynchronous devices.



Strobe

  - ❖ Only one control signal known as strobe is needed.
- ❖ The strobe signal is enabled by either the source device or destination device, depending on the actual application.



—→ : source's action

(a) Source-initiated transfer

  

- - - - -→ : destination's action

(b) Destination-initiated transfer


It presumes that the requested device is ready for transferring data once it receives the request, which is not the case in reality.

Handshaking

- ❖ In the handshaking transfer, four events are proceeded in a cycle order:
 1. ready (request):
 2. data valid:
 3. data acceptance:
 4. acknowledge:

Source-initiated transfer


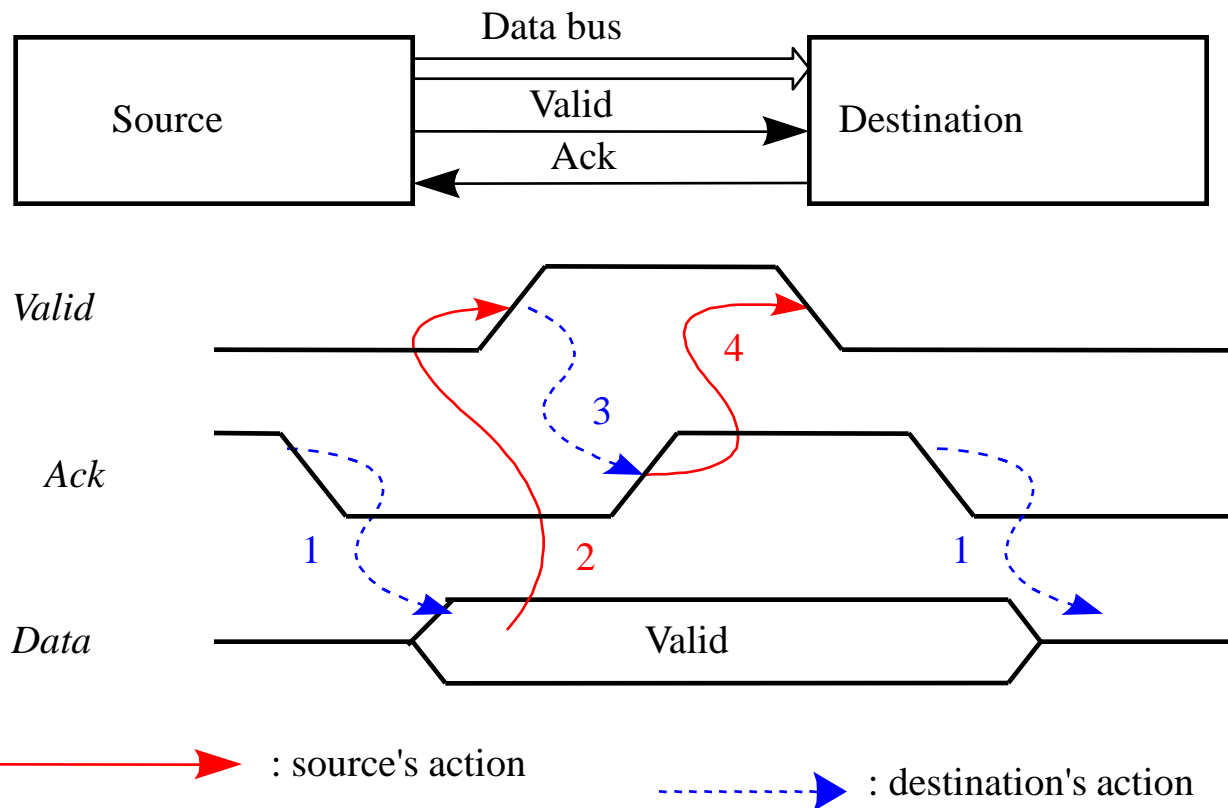
1. ready:
2. data valid:
3. data acceptance:
4. acknowledge:



Source-initiated transfer

- ❖ In the handshaking transfer, four events are proceeded in a cycle order:
 1. **ready**: The destination device deasserts the acknowledge signal and is ready to accept the next data.
 2. **data valid**: The source device places the data onto the data bus and asserts the valid signal to notify the destination device that the data on the data bus is valid.
 3. **data acceptance**: The destination device accepts (latches) the data from the data bus and asserts the acknowledge signal.
 4. **acknowledge**: The source device invalidates data on the data bus and deasserts the valid signal

Destination-initiated transfer

  

→ : source's action


→ : destination's action

Destination-initiated transfer

- ❖ In the handshaking transfer, four events are proceeded in a cycle order:
 1. **request**: The destination device asserts the request signal to request data from the source device.
 2. **data valid**: The source device places the data on the data bus and asserts the valid signal to notify the destination device that the data is valid now.
 3. **data acceptance**: The destination device accepts (latches) the data from the data bus and asserts the request signal.
 4. **acknowledge**: The source device invalidates data on the data bus and deasserts the valid signal **to notify** the destination device that it has removed the data from the data bus


Asynchronously Serial Data Transfers

 - ❖ The clock signal is not sent with data.
- ❖ The receiver generates its local clock that is then used to capture the data being received.
- ❖ When there is no data to be sent, the transmitter continuously sends 1s in order to maintain a continuous communication channel.
- ❖ The receiver monitors the channel continuously until the start bit is detected.




Asynchronously Serial Data Transfers

❖ Sampling at the same frequency

 

❖ Sampling using 4 times frequency

 


Timers


- ❖ Important applications:
 - time-delay creation
 - event counting
 - time measurement
 - period measurement
 - pulse-width measurement
 - time-of-day tracking
 - waveform generation
 - periodic interrupt generation

Timers

 The latch register stores the initial value to be loaded into the timer for counting down.



(a) Hardware model

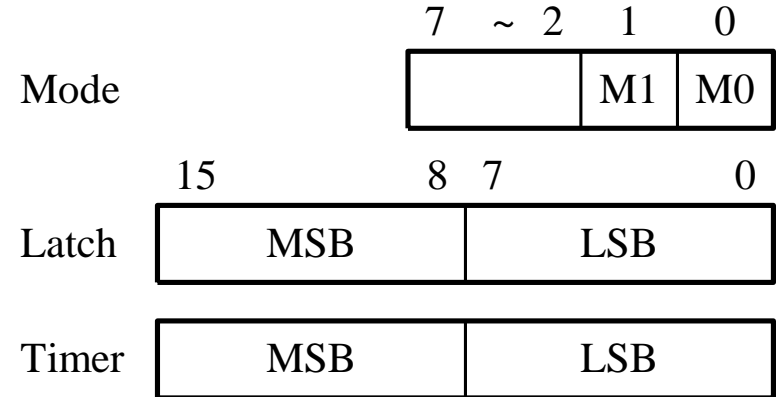

(b) Programming model


| cs | r_w | A1 | A0 | Function |
|----|--------|--------|--------|----------------------|
| 0 | ϕ | ϕ | ϕ | Chip unselected |
| 1 | 1 | 0 | 0 | Read Latch register |
| 1 | 1 | 0 | 1 | Read timer register |
| 1 | 0 | 0 | 0 | Write Latch register |
| 1 | 0 | 1 | 0 | Write mode register |

(c) Function table


Basic Timer Operations

- ❖ A counter is called a timer if it is operated at a known clock of fixed frequency.
- ❖ In practice, the timers used in most μC systems are counters with programmable operation modes.
- ❖ The basic operation modes of a timer are as follows:
 - terminal count (binary/BCD event counter)
 - rate generation
 - (digital) monostable (or called one-shot)
 - square-wave generation

Terminal Count

 


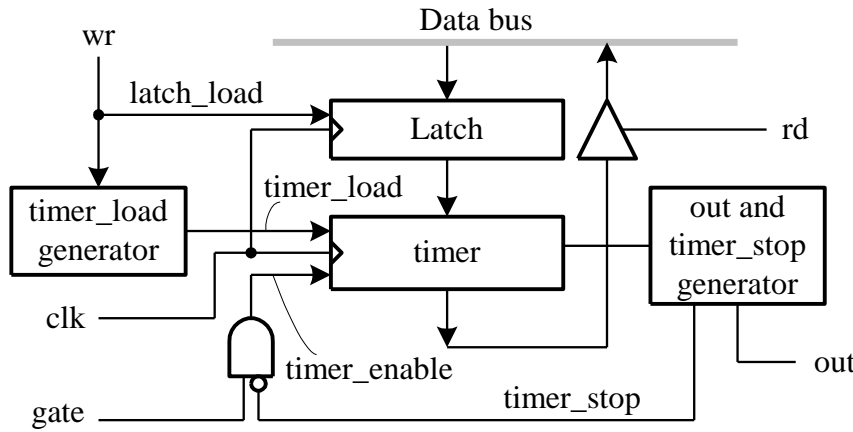(a) A waveform example of terminal-count mode




(b) Block diagram of terminal-count mode

(c) Generate one-cycle timer_load pulse

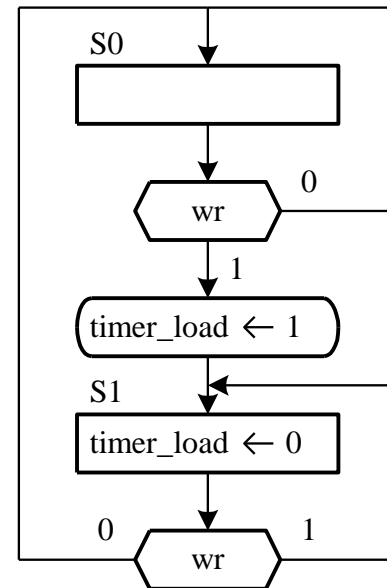


Rate Generation

 
- ❖ The out terminal outputs one clock pulse for every N clock pulses.
- ❖ The gate input should be fixed at the logic 1 to enable the timer.
- ❖ It is implemented by being reloaded the timer register from latch register whenever the terminal count is reached.



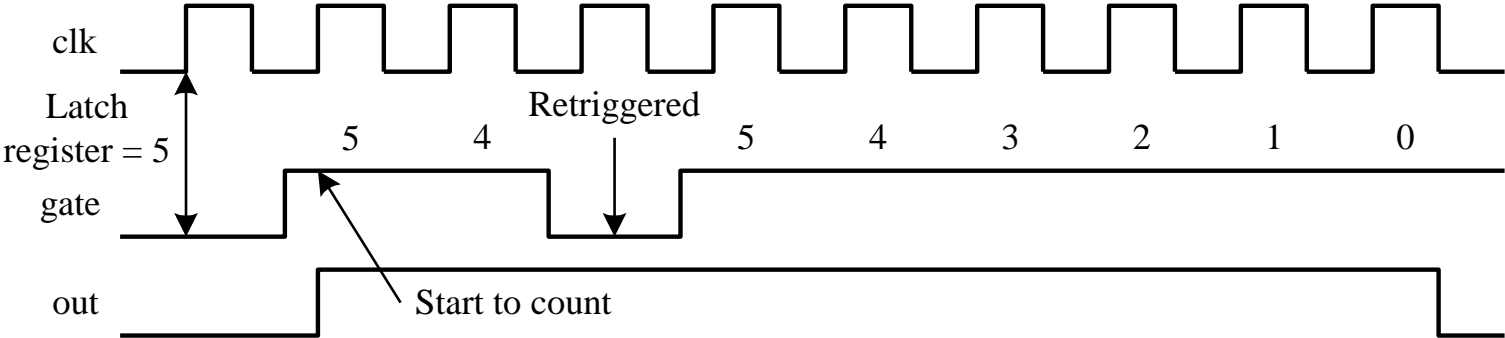Retriggerable Monostable (One-Shot) Operation



(a) A waveform example of one-shot mode


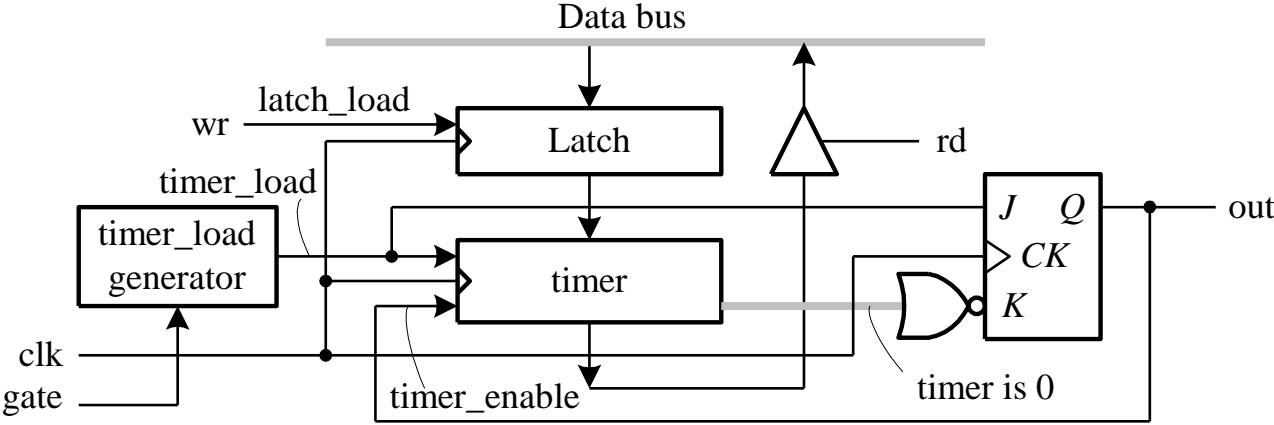


(b) Block diagram of one-shot mode

UART

❖ Universal Asynchronous Receiver Transmitter

▪ Serial Data Transmission

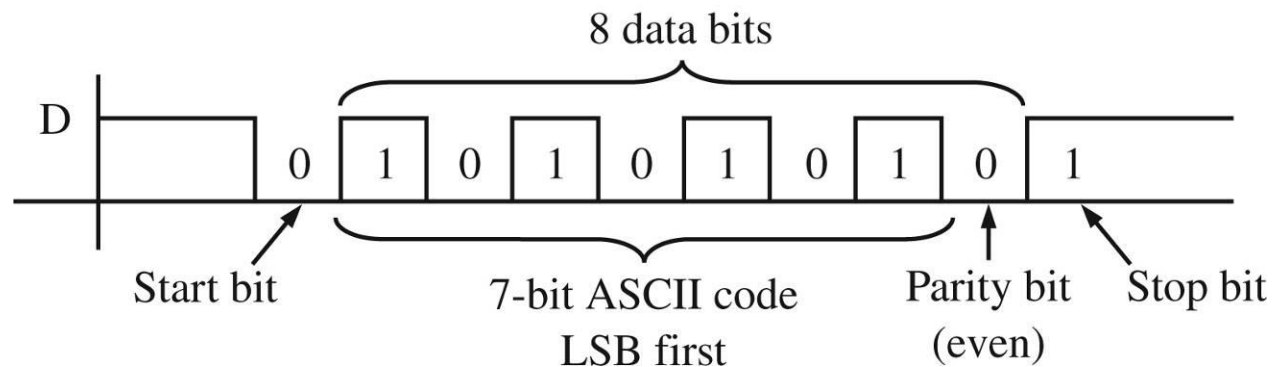 

68HC11 Microcontroller


❖ UART Registers

- **RSR** **Receive Shift Register**
- RDR Receive Data Register
- TDR Transmit Data Register
- **TSR** **Transmit Shift Register**
- SCCR Serial Communications Control Register
- SCSR Serial Communications Status Register

❖ UART Flags

- TDRE Transmit Data Register Empty
- RDRF Receive Data Register Full


UART Block Diagram

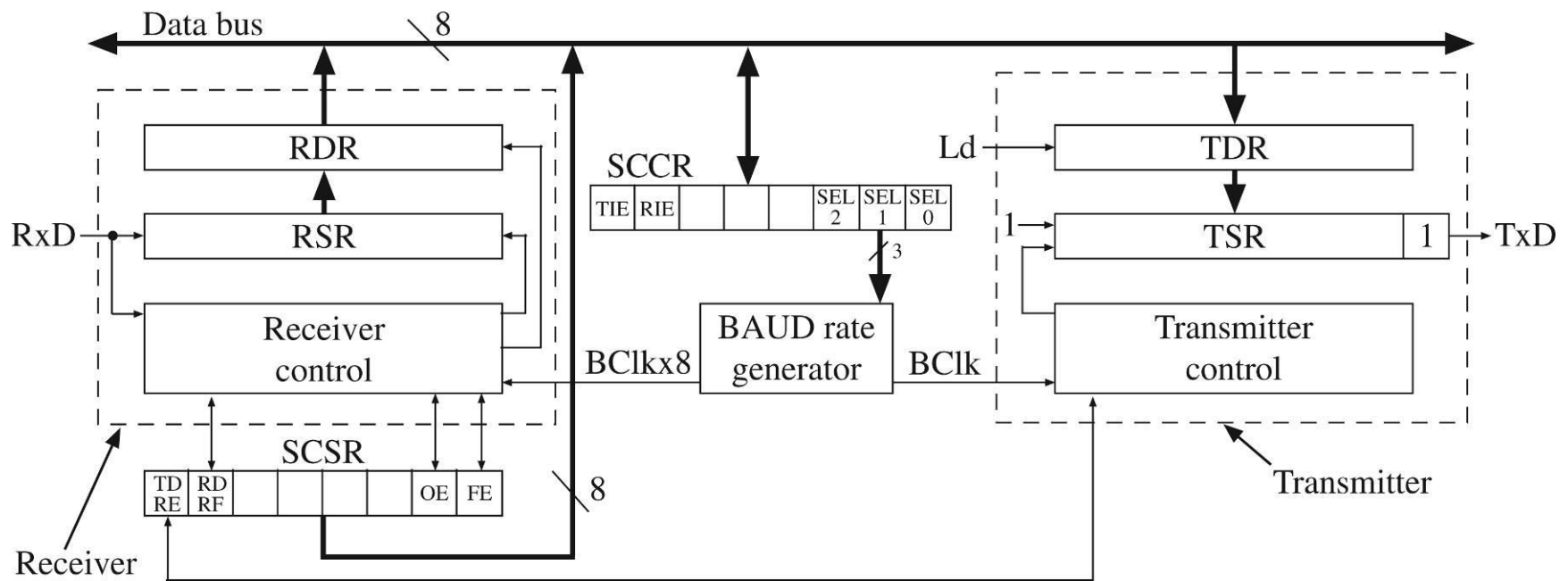

UARTs

- ❖ UART is a device used to provide serial data ports used to communicate with serial devices.
- ❖ The hardware model includes
 - the CPU interface
 - the I/O interface
- ❖ The software model consists of four registers:
 - receiver data register (RDR)
 - transmitter data register (TDR)
 - status register (SR)
 - control register (CR)



UARTs

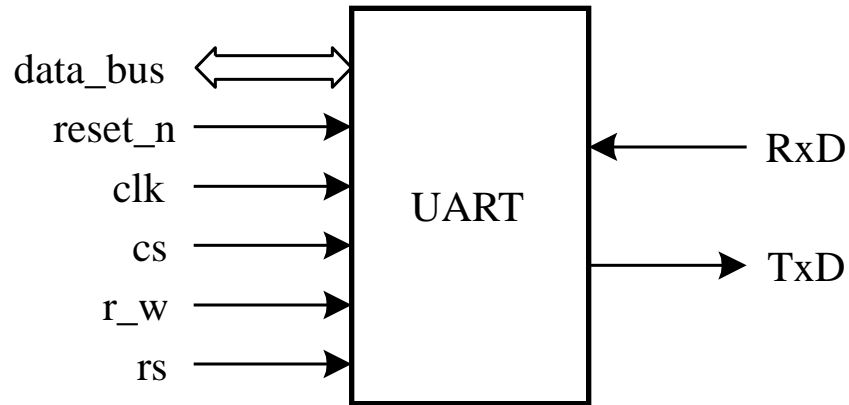

(a) Hardware model

| cs | r_w | rs | Function |
|----|--------|--------|-----------------|
| 0 | ϕ | ϕ | Chip unselected |
| 1 | 1 | 0 | Read SR |
| 1 | 0 | 0 | Write CR |
| 1 | 1 | 1 | Read RDR |
| 1 | 0 | 1 | Write TDR |

(b) Function table

  

(c) Programming model

UARTs


❖ Design issues

- baud rate: 300 to 19200, or even more
- sampling clock frequency: $RxC = n TxC$ ($n = 1, 4, 16, 64$)
- stop bits: 1, 1.5, 2 bits
- parity check
 - Even: the number of 1s of information and parity is even.

Transmitter Operation


- ❖ Microcontroller waits until TDRE = '1'
 - Loads data into TDR
 - Clears TDRE
- ❖ UART transfers data from TDR to TSR
 - Sets TDRE
- ❖ UART outputs start bit ('0') then shifts TSR right eight times followed by a stop bit ('1')

Transmitter SM Chart

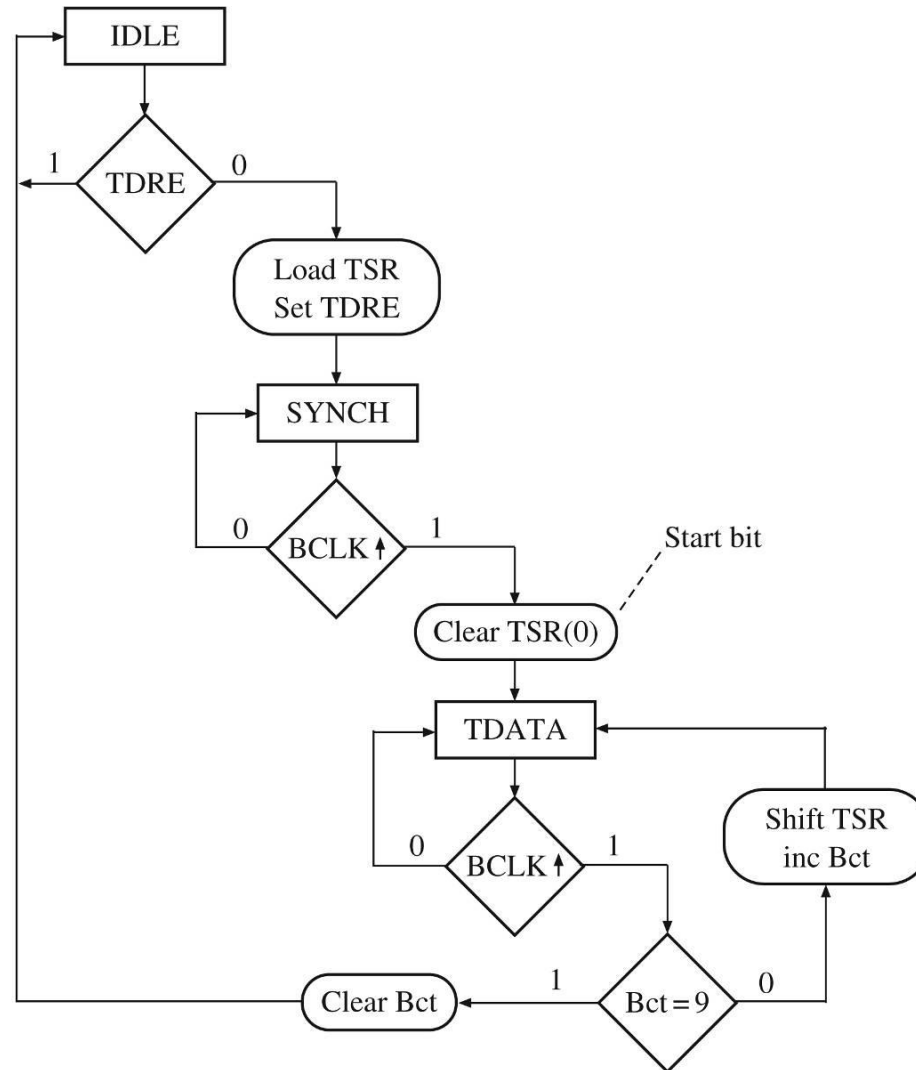


A Transmitter of UARTs

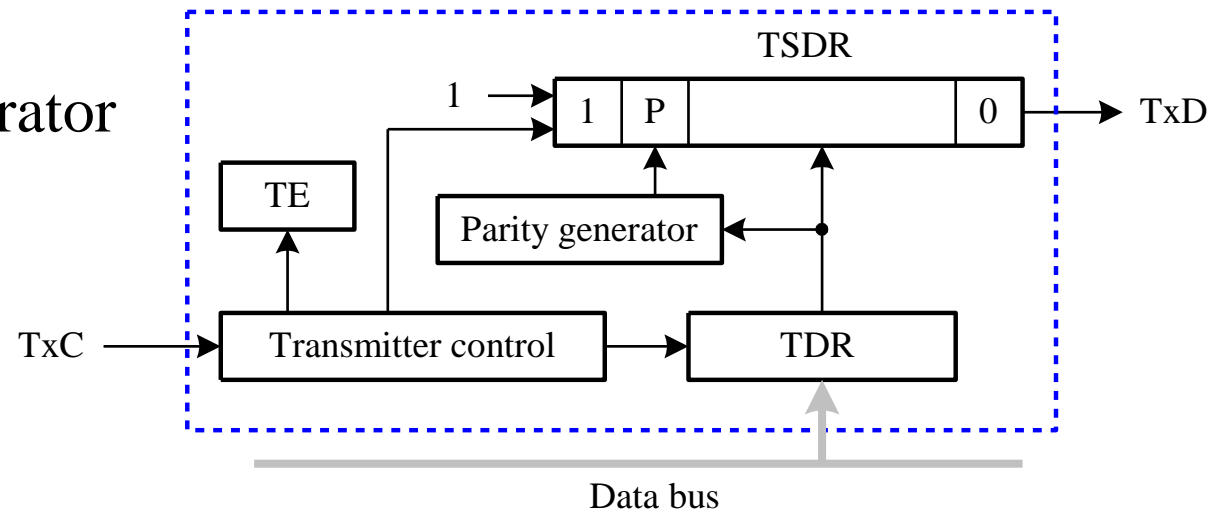
- ❖ The essential component of the transmitter is a shift register.
- ❖ The transmitter is composed of
 - a transmitter shift data register (TSDR)
 - a TDR empty flag (TE)
 - a transmitter control circuit
 - a TDR
 - parity generator



A Transmitter of UARTs

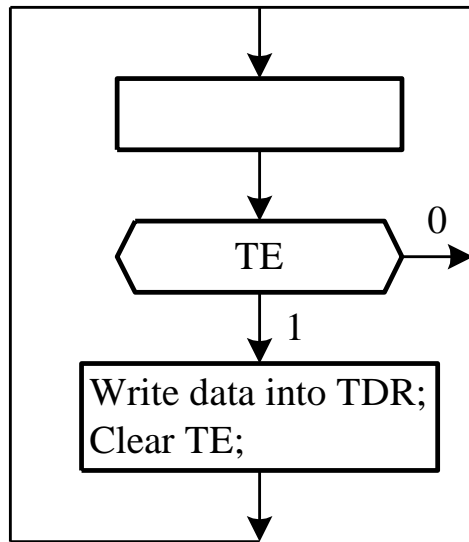

(a) CPU operations

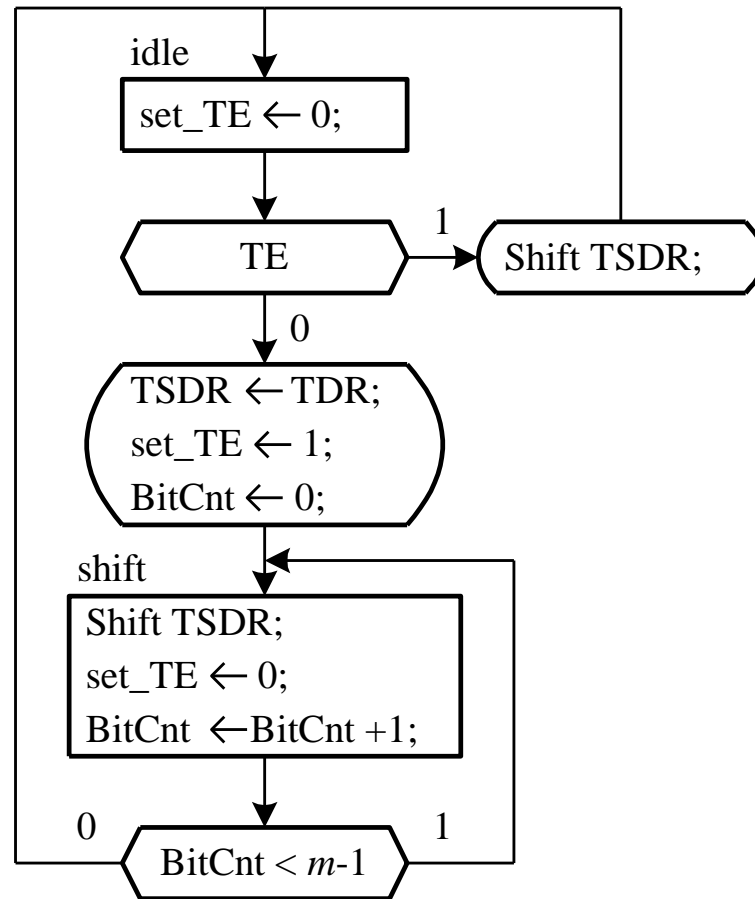

(b) TSDR operations

UART transmitter

```

// an example of UART transmitter
module UART_transmitter(clk, reset_n, load_TDR, data_bus,
                        TE, TxC, TxD);
parameter M = 10; //the frame size excluding the stop bit
input clk, reset_n, TxC, load_TDR;
input [7:0] data_bus;
output TxD, TE;
// internal used registers
reg [7:0] TDR;
reg [M-1:0] TSDR;
reg [3:0] BitCnt;
reg ps, ns, set_TE, TE;
localparam idle = 1'b0, shift = 1'b1;
// load TDR when load_TDR is activated
always @(posedge clk or negedge reset_n)
    if (!reset_n) TDR <= 8'b0;
    else if (load_TDR) TDR <= data_bus;
// update TDR empty flag (TE)
always @(posedge clk or negedge reset_n)
    if (!reset_n) TE <= 1'b1;
    else TE <= (set_TE && !TE) || (!load_TDR && TE);
// load TSDR from TDR and perform data transmission
// step 1: initialize and update state registers
always @(posedge TxC or negedge reset_n)

```

UART transmitter

```

    if (!reset_n) ps <= idle;
    else ps <= ns;
// step 2: compute next state
always @(*)
    case (ps)
        idle: if (TE == 1) ns = idle;
              else ns = shift;
        shift: if (BitCnt < M - 1) ns = shift;
              else ns = idle;
    endcase
// step 3: execute RTL operations
always @(posedge TxC or negedge reset_n)
    if (!reset_n) begin TSDR <= {M{1'b1}};
        BitCnt <= 0; set_TE <= 1'b0; end
    else case (ps)
        idle: begin set_TE <= 1'b0;
            if (TE == 1) TSDR <= {1'b1, TSDR[M-1:1]};
            else begin
                TSDR <= {^TDR, TDR, 1'b0};
                set_TE <= 1'b1;
                BitCnt <= 0; end end
        shift: begin
            TSDR <= {1'b1, TSDR[M-1:1]};
            set_TE <= 1'b0;
            BitCnt <= BitCnt + 1; end
    endcase
assign TxD = TSDR[0] & (ps == shift) | (ps == idle);
endmodule

```


even parity

start bit

Receiver Operation



- ❖ UART waits for start bit
 - Shifts bits into RSR
- ❖ When all data bits and stop bit are received
 - RSR loaded into RDR
 - Set RDRF
- ❖ Microcontroller waits until RDRF is set
 - Read RDR
 - Clear RDRF

Sampling RxD

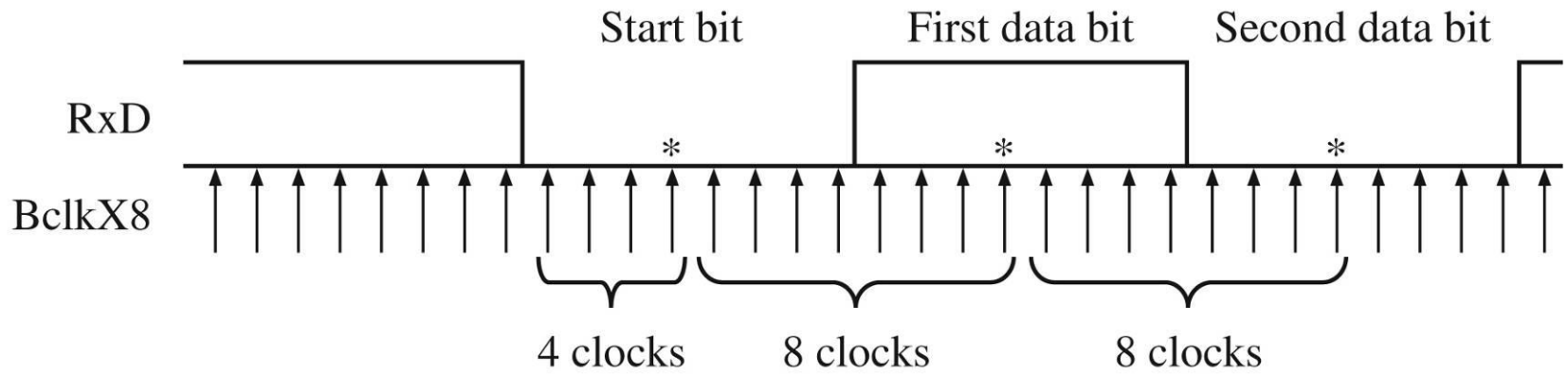


*Read data at these points

Receiver SM Chart

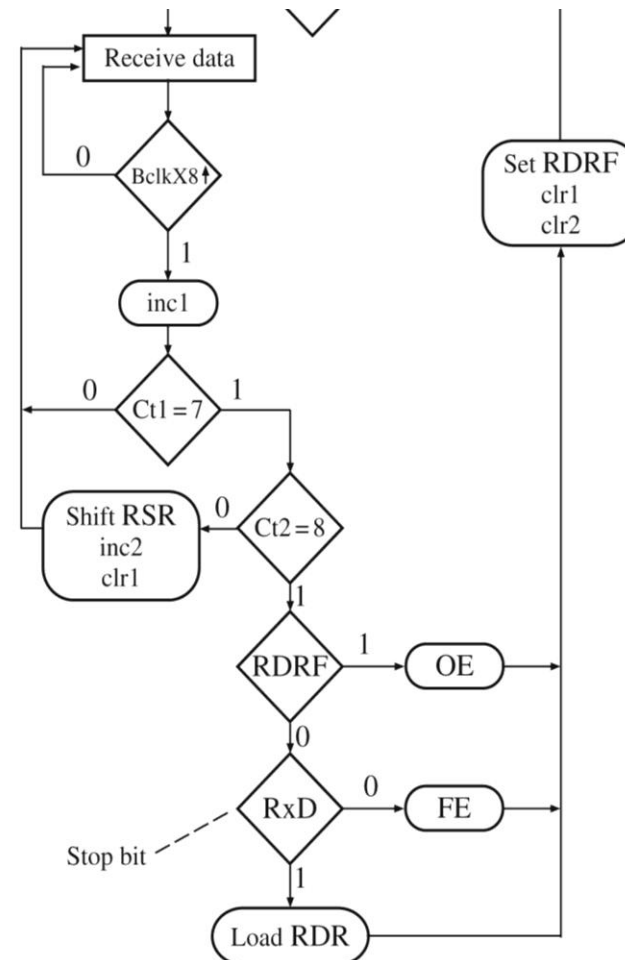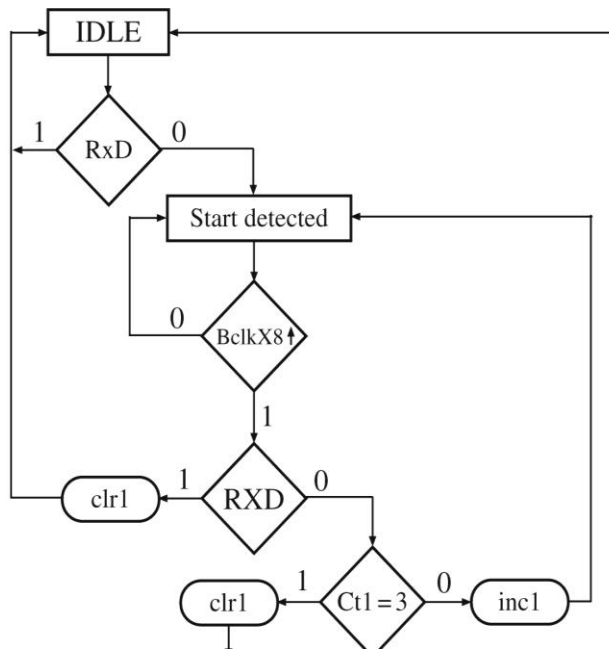


A Receiver of UARTs

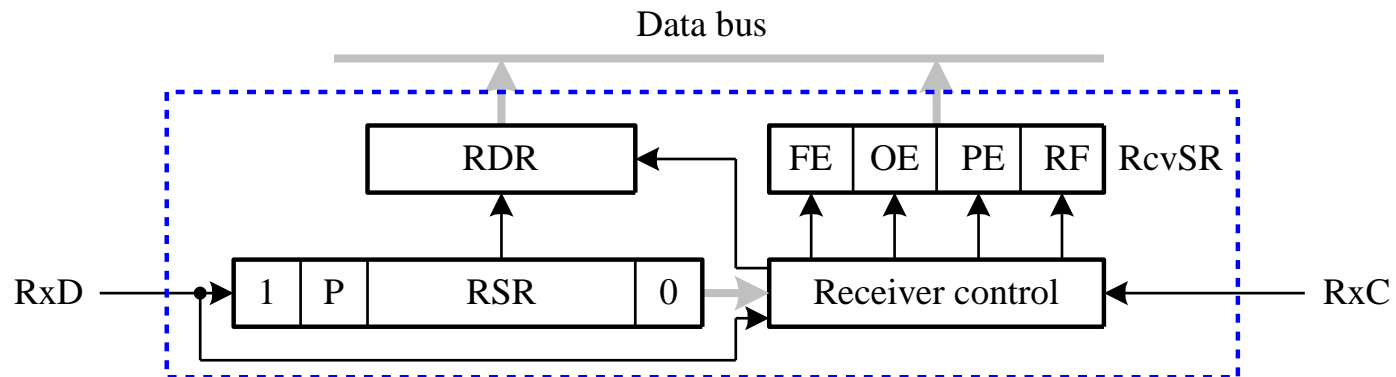
- ❖ The essential component of the receiver is also a shift register.
- ❖ The receiver is composed of
 - a RDR
 - a receiver shift data register (RSDR)
 - a status register
 - a receiver control circuit



A Receiver of UARTs

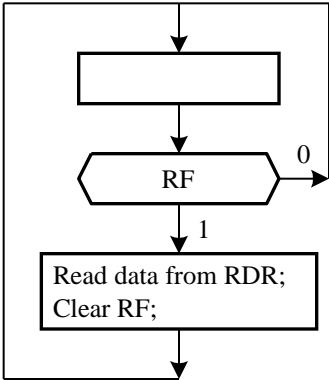

(a) CPU operations

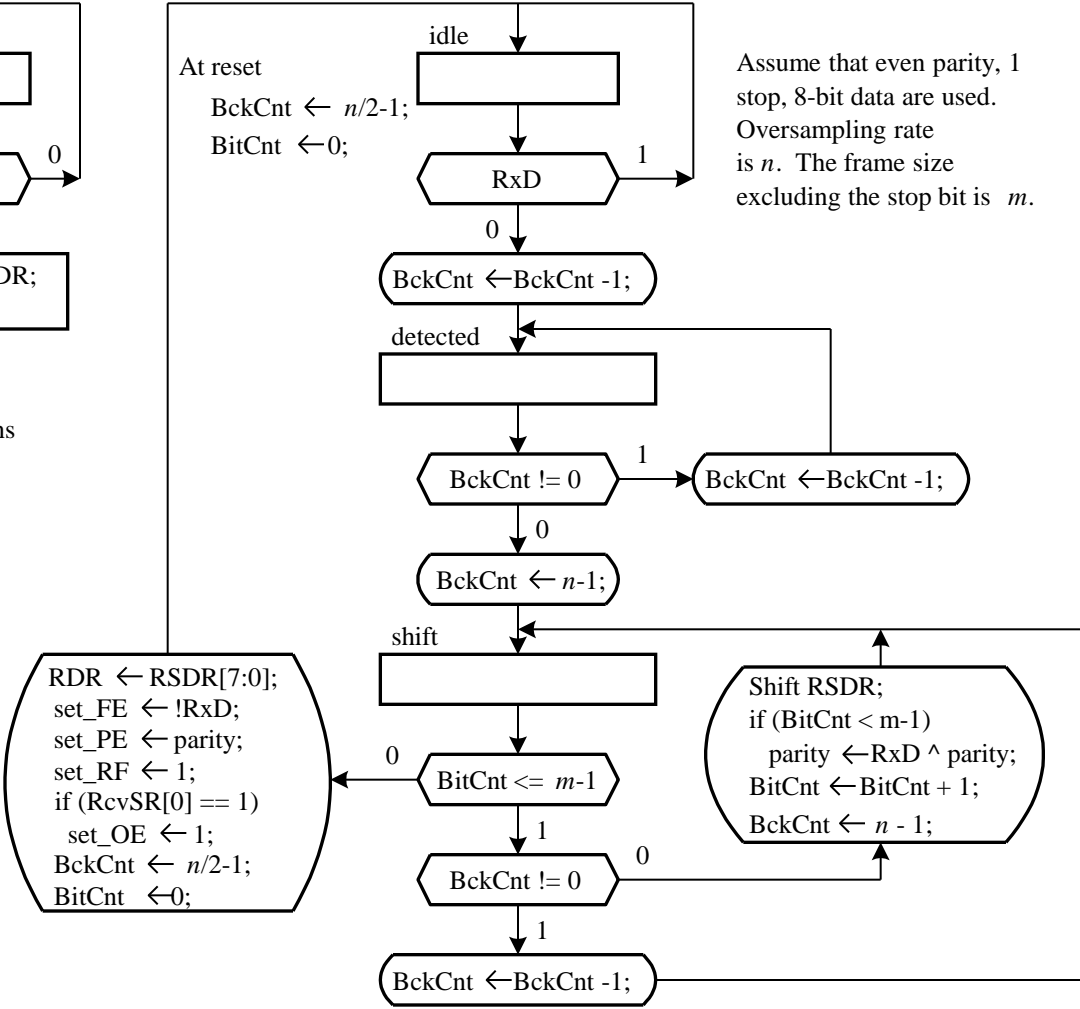

Assume that even parity, 1 stop, 8-bit data are used. Oversampling rate is n . The frame size excluding the stop bit is m .

(b) RSDR operations

UART receiver

```
// an example of UART receiver -- RxC is 8 times TxC
// 1 stop, 8-bit data, and even parity are used
module UART_receiver(clk, reset_n, read_RDR, RDR, RcvSR,
                    RxC, RxD);
parameter M = 10; // default frame size excluding the
                // stop bit
parameter N = 8; // default sampling clock frequency
localparam K = 3; // K = log2 N
localparam L = 4; // L = log2 M
input  clk, reset_n, read_RDR, RxC, RxD;
output reg [3:0] RcvSR;
output reg [7:0] RDR; // receiver data register
// internal used registers
reg [M-1:0] RSDR; // receiver shift data register
reg [L-1:0] BitCnt; // number of bits received
reg [K-1:0] BckCnt; // number of TxC clocks elapsed
reg [1:0] ps, ns;
wire RcvSR_reset;
reg parity, set_FE, set_OE, set_PE, set_RF, set_RF_1clk;
```

UART receiver

```

localparam idle = 2'b00, detected = 2'b01, shift = 2'b10;
// update status register (RcvSR)
assign RcvSR_reset = !reset_n || read_RDR;
always @(posedge clk or posedge RcvSR_reset)
    if (RcvSR_reset) RcvSR <= 4'b0000;
    else if (set_RF_1clk) RcvSR <= {set_FE, set_OE, set_PE,
                                   set_RF};

// generate set_RF_1clk signal from set_RF
reg state;
localparam S0 = 1'b0, S1 = 1'b1;
always @(posedge clk or negedge reset_n)
    if (!reset_n) begin set_RF_1clk <= 1'b0;
                        state <= S0; end

    else case (state)
        S0: if (set_RF) begin state <= S1;
                    set_RF_1clk <= 1'b1; end
            else state <= S0;
        S1: begin set_RF_1clk <= 1'b0;
                    if (set_RF) state <= S1; else state <= S0; end
    endcase

// receive data and load RSDR into RDR
// step 1: initialize and update state registers
always @(posedge RxC or negedge reset_n)
    if (!reset_n) ps <= idle;
    else ps <= ns;
// step 2: compute next state

```

UART receiver

```
always @(*)
  case (ps)
    idle: if (RxD == 1) ns = idle;
          else ns = detected;
    detected: if (BckCnt != 0) ns = detected;
              else ns = shift;
    shift: if (BitCnt <= M-1) ns = shift;
           else ns = idle;
    default: ns = idle;
  endcase
// step 3: execute RTL operations
always @(posedge RxC or negedge reset_n)
  if (!reset_n) begin RSDR <= {M{1'b0}};
    RDR <= 8'b00000000;
    BckCnt <= N/2-1; BitCnt <= 0; set_FE <= 1'b0;
    set_OE <= 1'b0; set_PE <= 1'b0;
    set_RF <= 1'b0; parity <= 0; end
  else case (ps)
```

UART receiver

```

idle: begin set_FE <= 1'b0; set_OE <= 1'b0;
      set_PE <= 1'b0;
      set_RF <= 1'b0; parity <= 1'b0;
      if (RxD == 0) BckCnt <= BckCnt - 1; end
detected: if (BckCnt != 0) BckCnt <= BckCnt - 1;
      else BckCnt <= N - 1;
shift: begin
      if (BitCnt <= M - 1) begin
        if (BckCnt != 0)
          BckCnt <= BckCnt - 1;
        else begin
          RSDR <= {RxD, RSDR[M-1:1]};
          if (BitCnt < M-1)
            parity <= RxD ^ parity;
          BitCnt <= BitCnt + 1;
          BckCnt <= N - 1; end end
      else begin RDR <= RSDR[7:0];
        set_FE <= !RxD; set_PE <= parity;
        BckCnt <= N/2 - 1; set_RF <= 1'b1;
        if (RcvSR[0] == 1) set_OE <= 1'b1;
        BitCnt <= 0; end
      end
    endcase
endmodule

```


shift

Baud-Rate Generators

- ❖ The baud-rate generator provides both clock sources: TxC and RxC, for transmitter and receiver modules, respectively.
- ❖ Two most widely used approaches to designing baud-rate generators:
 - Multiplexer-based approach
 - timer-based approach


Baud Rate Generator

| Select Bits | BAUD Rate |
|-------------|-----------|
| 000 | 38,462 |
| 001 | 19,231 |
| 010 | 9615 |
| 011 | 4808 |
| 100 | 2404 |
| 101 | 1202 |
| 110 | 601 |
| 111 | 300.5 |

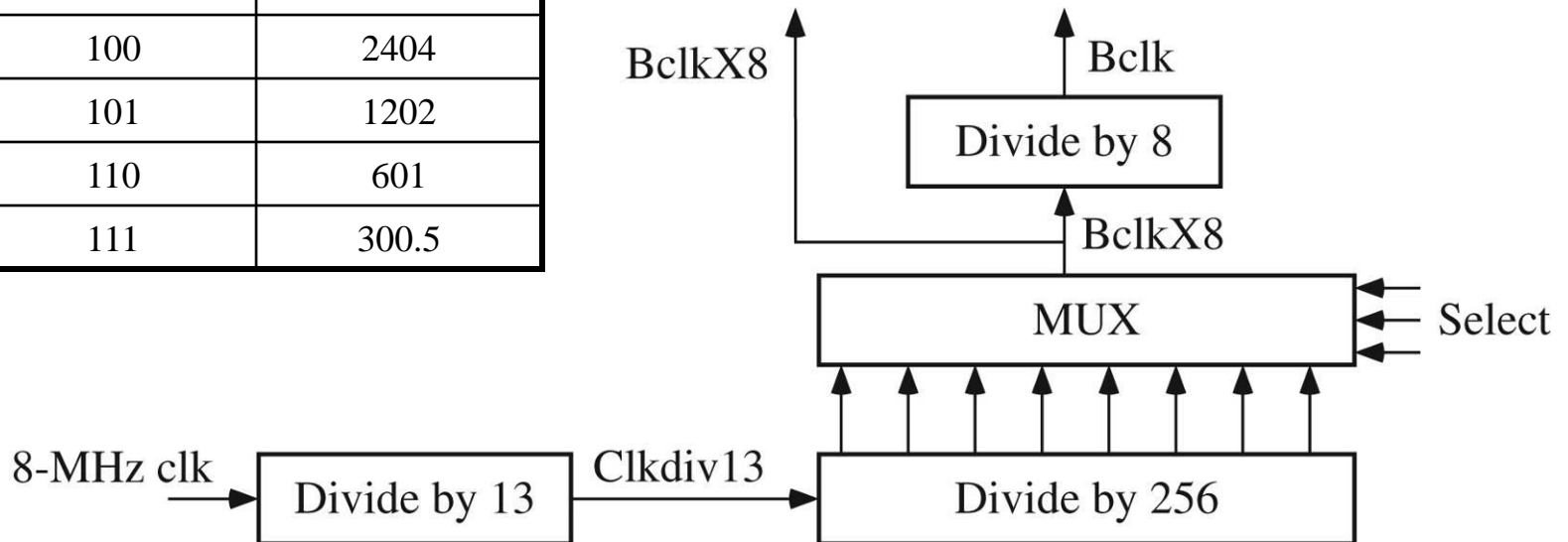


$$300.5 \times 8 \times 256 \times 13 = 8000512$$

Baud-Rate Generators

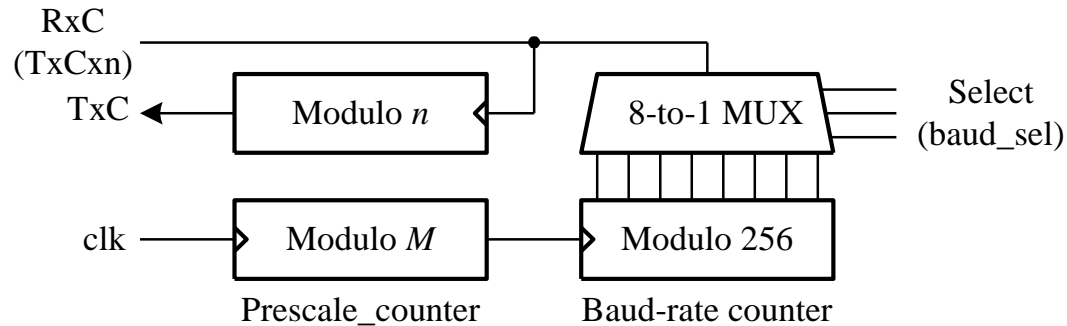

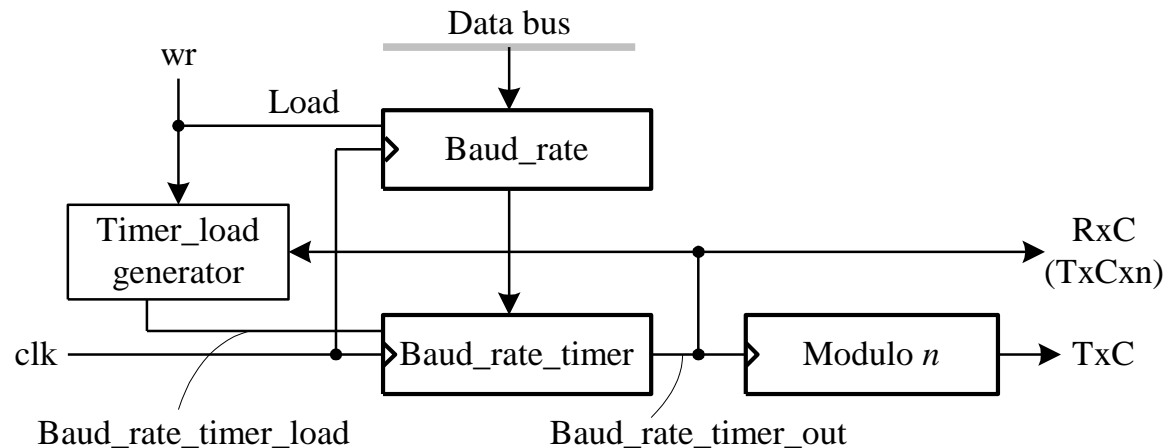(a) Multiplexer-based baud-rate generator



(b) Timer-based baud-rate generator

Baud-rate generator

```
// an example of multiplexer-based baud-rate generator
module UART_baud_rate(clk, reset_n, baud_sel, TxC, TxCx8);
parameter BD_STEPS = 8; // default number of baud-rate
                        // steps
input clk, reset_n;
input [2:0] baud_sel;
output TxC, TxCx8;
reg TxCx8;
integer i;
// internal used reg variables
wire prescale_out, TxC, TxCx8_clk;
reg [2:0] prescale_counter;
reg [BD_STEPS-1:0] baud_rate_counter;
```

Baud-rate generator

```

reg [2:0] mod8_counter;
// describe the prescale_counter, a presetable down
// counter
always @(posedge clk or negedge reset_n)
    if (!reset_n) prescale_counter <= 0;
    else prescale_counter <= prescale_counter + 1;
assign prescale_out = &prescale_counter;
// describe the a modulo-256 up counter
always @(posedge clk or negedge reset_n)
    if (!reset_n) baud_rate_counter <= 0;
    else if (prescale_out)
        baud_rate_counter <= baud_rate_counter + 1;
// describe the 8-to-1 multiplexers for selecting the
// required baud rate
always @(baud_sel or baud_rate_counter) begin
    TxCx8 = 0;
    for (i = 0; i < BD_STEPS; i = i + 1)
        if (baud_sel == i) TxCx8 = baud_rate_counter[i];
    end
assign TxCx8_clk = TxCx8;
// describe the modulo8_counter
always @(posedge TxCx8_clk or negedge reset_n)
    if (!reset_n) mod8_counter <= 0;
    else mod8_counter <= mod8_counter + 1;
assign TxC = mod8_counter[2];
endmodule

```

UART top

```
// instantiate transmitter, receiver, and baud-rate
// generator modules
UART_transmitter my_transmitter (.clk(clk), .reset_n
    (reset_n), .load_TDR(load_TDR), .data_bus(data_bus),
    .TE(TE), .TxC(TxC), .TxD(TxD));
UART_receiver my_receiver (.clk(clk), .reset_n(reset_n),
    .read_RDR(read_RDR), .RDR(RDR), .RcvSR (RcvSR),
    .RxC(RxC), .RxD(RxD));
UART_baud_rate my_baud_rate(.clk(clk), .reset_n(reset_n),
    .baud_sel(CR[2:0]), .TxC(TxC), .TxCx8(RxC));

// generate interface control signals
assign read_UART = (cs == 1) && (r_w == 1),
    write_UART = (cs == 1) && (r_w == 0);
assign read_RDR = read_UART && (rs == 1'b1),
    load_TDR = write_UART && (rs == 1'b1),
    read_SR = read_UART && (rs == 1'b0),
    load_CR = write_UART && (rs == 1'b0);
```

| cs | r_w | rs | Function |
|----|--------|--------|-----------------|
| 0 | ϕ | ϕ | Chip unselected |
| 1 | 1 | 0 | Read SR |
| 1 | 0 | 0 | Write CR |
| 1 | 1 | 1 | Read RDR |
| 1 | 0 | 1 | Write TDR |

(b) Function table

UART top

```
// read RDR or SR
assign data_bus = (read_RDR) ? RDR :
                  ((read_SR) ? {3'b000, RcvSR, TE}: 8'bz);
// define the control register
always @(posedge clk or negedge reset_n)
  if (!reset_n) CR <= 8'b0000_0000; // control register
  else if (load_CR) CR <= data_bus;
```

```
// irq generation logic
always @(posedge clk or negedge reset_n)
  if (!reset_n) IRQ <= 1'b0;
```


```
    else if (((CR[7] == 1) && (RcvSR[0] == 1 ||
      RcvSR[2] == 1)) ||
      (CR[6] == 1) && (TE == 1)) IRQ <= 1'b1;
    else IRQ <= 1'b0;
endmodule
```

RIE


RF

TIE

CPU Basic Operations

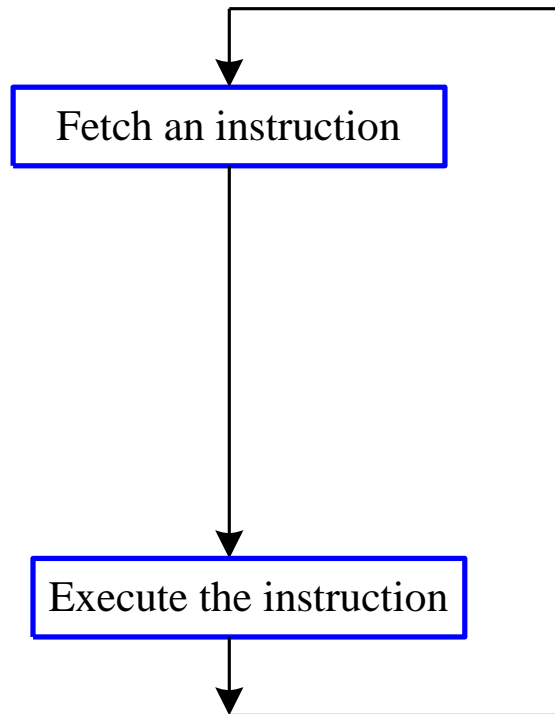

(a) CPU basic operations

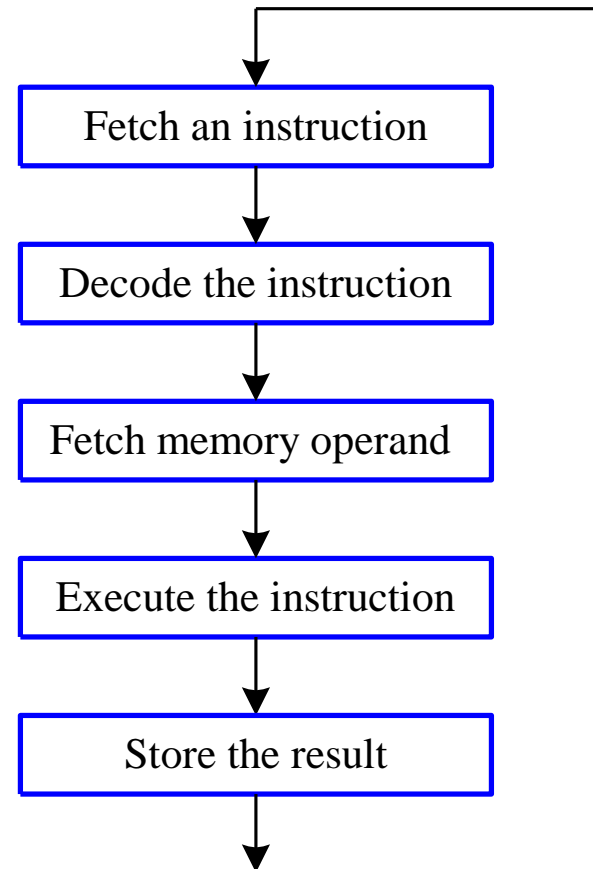


(b) More detailed CPU operations

The Software Model of CPU

- ❖ The software model of CPU:
 - the programming model
 - instruction formats
 - addressing modes
 - instruction set


The Programming Mode

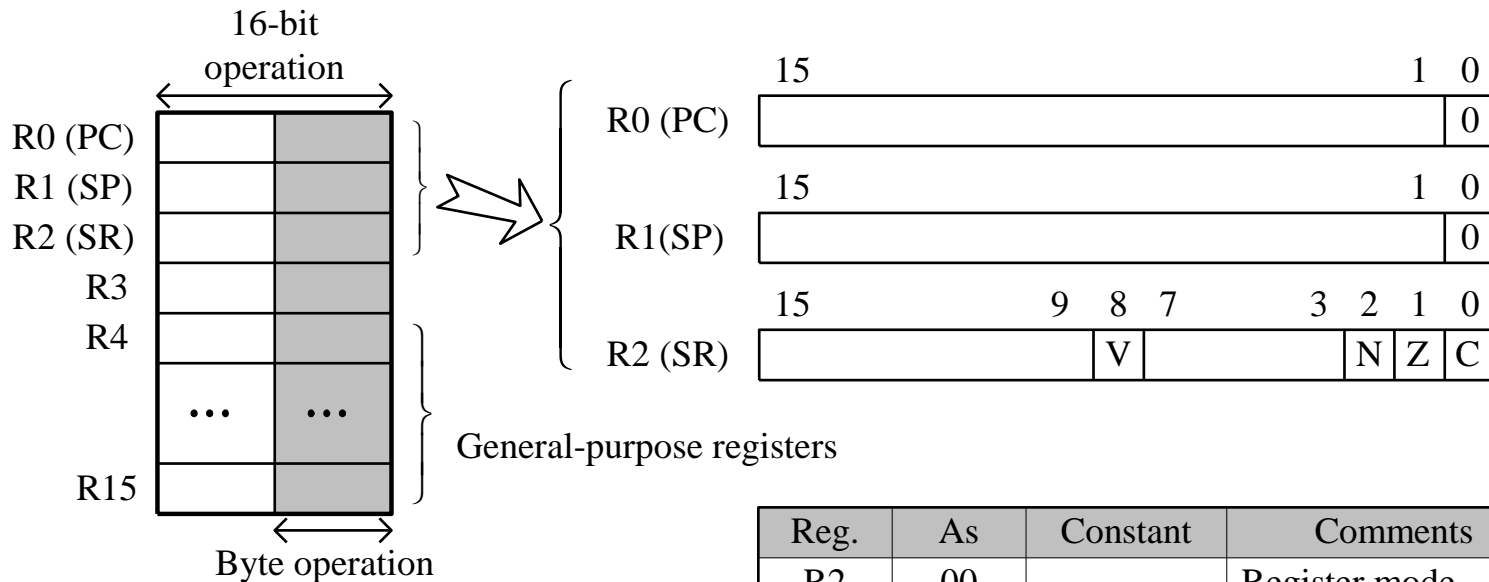


| Reg. | As | Constant | Comments |
|------|----|----------|-----------------------|
| R2 | 00 | --- | Register mode |
| R2 | 01 | (0) | Absolute address mode |
| R2 | 10 | 0x0004 | +4, bit processing |
| R2 | 11 | 0x0008 | +8, bit processing |
| R3 | 00 | 0x0000 | 0, word processing |
| R3 | 01 | 0x0001 | +1, bit processing |
| R3 | 10 | 0x0010 | +2, bit processing |
| R3 | 11 | 0xFFFF | -1, word processing |

Instruction Formats

 
- ❖ Any instruction is composed of two major parts:
 - Opcode defines the operations of the instruction.
 - Operand specifies the operands to be operated by the instruction.



(a) Double-operand instruction format

 

(b) Single-operand instruction format

 

(c) Jump instruction format

Addressing Modes

- ❖ Addressing modes are the ways that operands are fetched.
 - register
 - indexed
 - register indirect
 - immediate

| As/Ad | Addressing mode | Syntax | Comments |
|-------|------------------------|--------|---|
| 00/0 | Register mode | Rn | Register contents are operand. |
| 01/1 | Indexed mode | X(Rn) | (Rn+X) points to the operand. |
| | Symbolic mode | ADDR | (PC+X) points to the operand. |
| | Absolute mode | &ADDR | X(SR) points to the operand. |
| 10/- | Register indirect mode | @Rn | Rn points to the operand. |
| | Autoincrement mode | @Rn+ | Rn points to the operand and increments 1 or 2. |
| 11/- | Immediate mode | #N | @PC+. |

The Instruction Set

❖ Double-operand instruction set

| Mnemonic | Operation | N | Z | V | C | Op code |
|-------------------|---|---|---|---|---|---------|
| MOV(.B) src, dst | $dst \leftarrow src$ | - | - | - | - | 0x4xxx |
| ADD(.B) src, dst | $dst \leftarrow src + dst$ | * | * | * | * | 0x5xxx |
| ADDC(.B) src, dst | $dst \leftarrow src + dst + C$ | * | * | * | * | 0x6xxx |
| SUB(.B) src, dst | $dst \leftarrow \text{.not.}src + dst + 1$ | * | * | * | * | 0x8xxx |
| SUBC(.B) src, dst | $dst \leftarrow \text{.not.}src + dst + C$ | * | * | * | * | 0x7xxx |
| CMP(.B) src, dst | $dst - src$ | * | * | * | * | 0x9xxx |
| DADD(.B) src, dst | $dst \leftarrow src + dst + C$ (decimal) | * | * | * | * | 0xAxxx |
| BIT(.B) src, dst | $dst \text{ .and. } src$ | * | * | 0 | * | 0xBxxx |
| BIC(.B) src, dst | $dst \leftarrow \text{.not.}src \text{ .and. } dst$ | - | - | - | - | 0xCxxx |
| BIS(.B) src, dst | $dst \leftarrow src \text{ .or. } dst$ | - | - | - | - | 0xDxxx |
| XOR(.B) src, dst | $dst \leftarrow src \text{ .xor. } dst$ | * | * | * | * | 0xExxx |
| AND(.B) src, dst | $dst \leftarrow src \text{ .and. } dst$ | * | * | 0 | * | 0xFxxx |

The Instruction Set

❖ Single-operand instruction set


| Mnemonic | Operation | N | Z | V | C | Op code |
|--------------|--|---|---|---|---|---------|
| RRA(.B) dst | Arithmetic shift right, $C \leftarrow \text{LSB}$ | * | * | 0 | * | 0x110x |
| RRC(.B) dst | Rotate right through carry | * | * | * | * | 0x100x |
| PUSH(.B) src | $SP \leftarrow SP - 2, @SP \leftarrow \text{src}$ | - | - | - | - | 0x120x |
| SWAPB | Swap bytes | - | - | - | - | 0x108x |
| CALL dst | $SP \leftarrow SP - 2, @SP \leftarrow PC + 2,$ $PC \leftarrow \text{dst}$ | - | - | - | - | 0x128x |
| RETI | $SR \leftarrow \text{TOS}, SP \leftarrow SP + 2,$ $PC \leftarrow \text{TOS}, SP \leftarrow SP + 2,$ | * | * | * | * | 0x130x |
| SXT dst | $\text{dst}[15:8] \leftarrow \text{dst}[7]$ | * | * | 0 | * | 0x118x |

The Instruction Set

❖ Jump instruction set

| Mnemonic | Operation | N | Z | V | C | Op code |
|---------------|---|---|---|---|---|---------|
| JNE/JNZ label | Jump to label if zero bit is reset | - | - | - | - | 0x20xx |
| JEQ/JZ label | Jump to label if zero bit is set | - | - | - | - | 0x24xx |
| JC label | Jump to label if carry bit is set | - | - | - | - | 0x2Cxx |
| JNC label | Jump to label if carry bit is reset | - | - | - | - | 0x28xx |
| JN label | Jump to label if negative bit is set | - | - | - | - | 0x30xx |
| JGE label | Jump to label if $(N \text{ .xor. } V) = 0$ | - | - | - | - | 0x34xx |
| JL label | Jump to label if $(N \text{ .xor. } V) = 1$ | - | - | - | - | 0x38xx |
| JMP label | Jump to label unconditionally | - | - | - | - | 0x3Cxx |

A Datapath Design

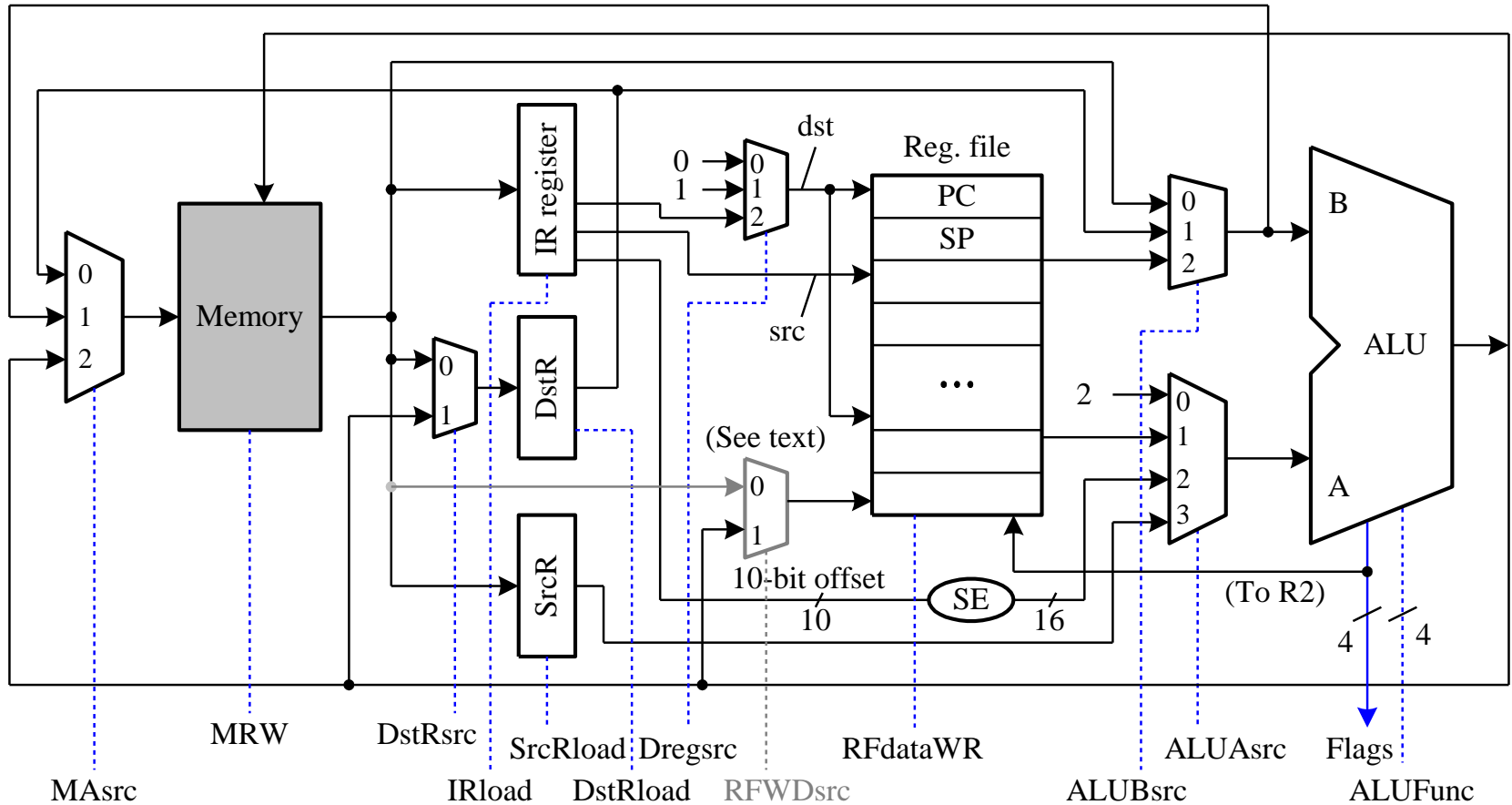


ALU Functions

| Instruction | ALU function | Mode selection | | | | | Mnemonic |
|------------------|-------------------------------------|----------------|----|----|----|-----|--------------|
| | | m3 | m2 | m1 | m0 | B/W | |
| MOV(.B) | $F \leftarrow A$ | 0 | 0 | 0 | 0 | - | pass A |
| MOV(.B) | $F \leftarrow B$ | 0 | 0 | 0 | 1 | - | pass B |
| ADD(.B) | $A+B$ | 0 | 0 | 1 | 0 | 0/1 | add(b/w) |
| ADDC(.B) | $A+B+C$ | 0 | 0 | 1 | 1 | 0/1 | addc(b/w) |
| SUB(.B), CMP(.B) | $A + \text{not } B + 1$ | 0 | 1 | 0 | 0 | 0/1 | sub(b/w) |
| SUBC(.B) | $A + \text{not } B + \text{not } C$ | 0 | 1 | 0 | 1 | 0/1 | subc(b/w) |
| DADD(.B) | $A+6H, A+60H$ conditional | 0 | 1 | 1 | 0 | 0/1 | dadd(b/w) |
| AND(.B), BIT(.B) | A and B | 0 | 1 | 1 | 1 | 0/1 | and(b/w) |
| BIC(.B) | not A and B | 1 | 0 | 0 | 0 | 0/1 | bic(b/w) |
| BIS(.B) | A or B | 1 | 0 | 0 | 1 | 0/1 | or(b/w) |
| XOR(.B) | $A \text{ xor } B$ | 1 | 0 | 1 | 0 | 0/1 | xor(b/w) |
| RRA(.B) | Arithmetic shift right into C | 1 | 0 | 1 | 1 | 0/1 | asrc(b/w) |
| RRC(.B) | Rotate right through C | 1 | 1 | 0 | 0 | 0/1 | rotatec(b/w) |
| SWAP | Swap byte | 1 | 1 | 0 | 1 | 0 | swap |

A Control Unit


❖ The decoder-based approach

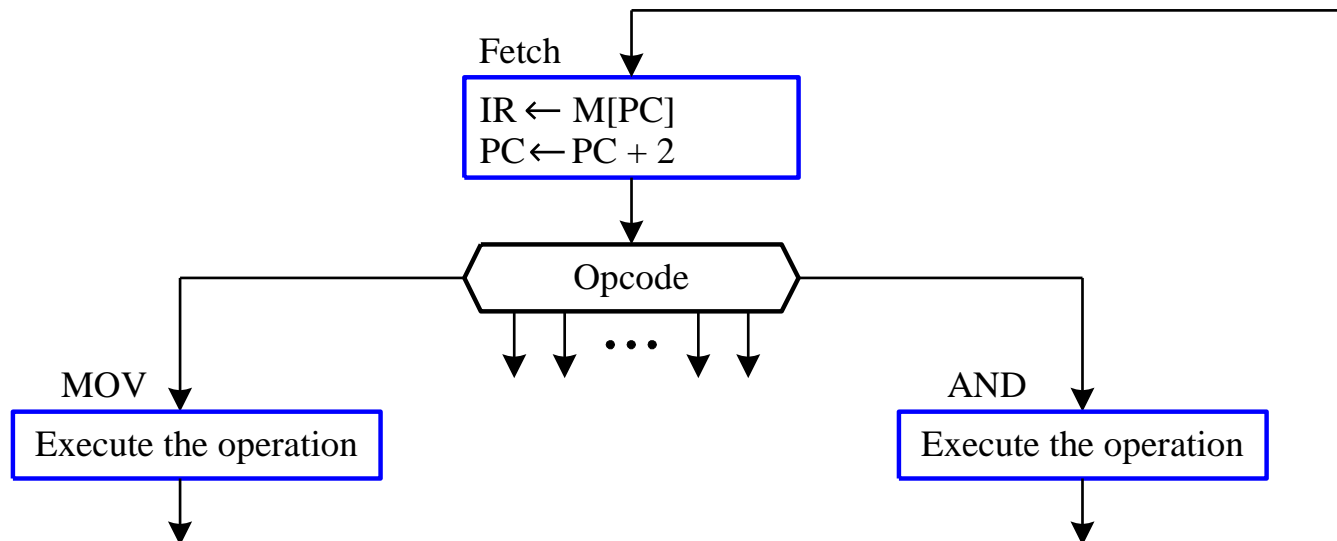- An opcode decoder is used after the instruction fetch phase.
- Each instruction is then executed accordingly.
- The resulting states required is rather large.



A Control Unit

❖ Single-operand instruction

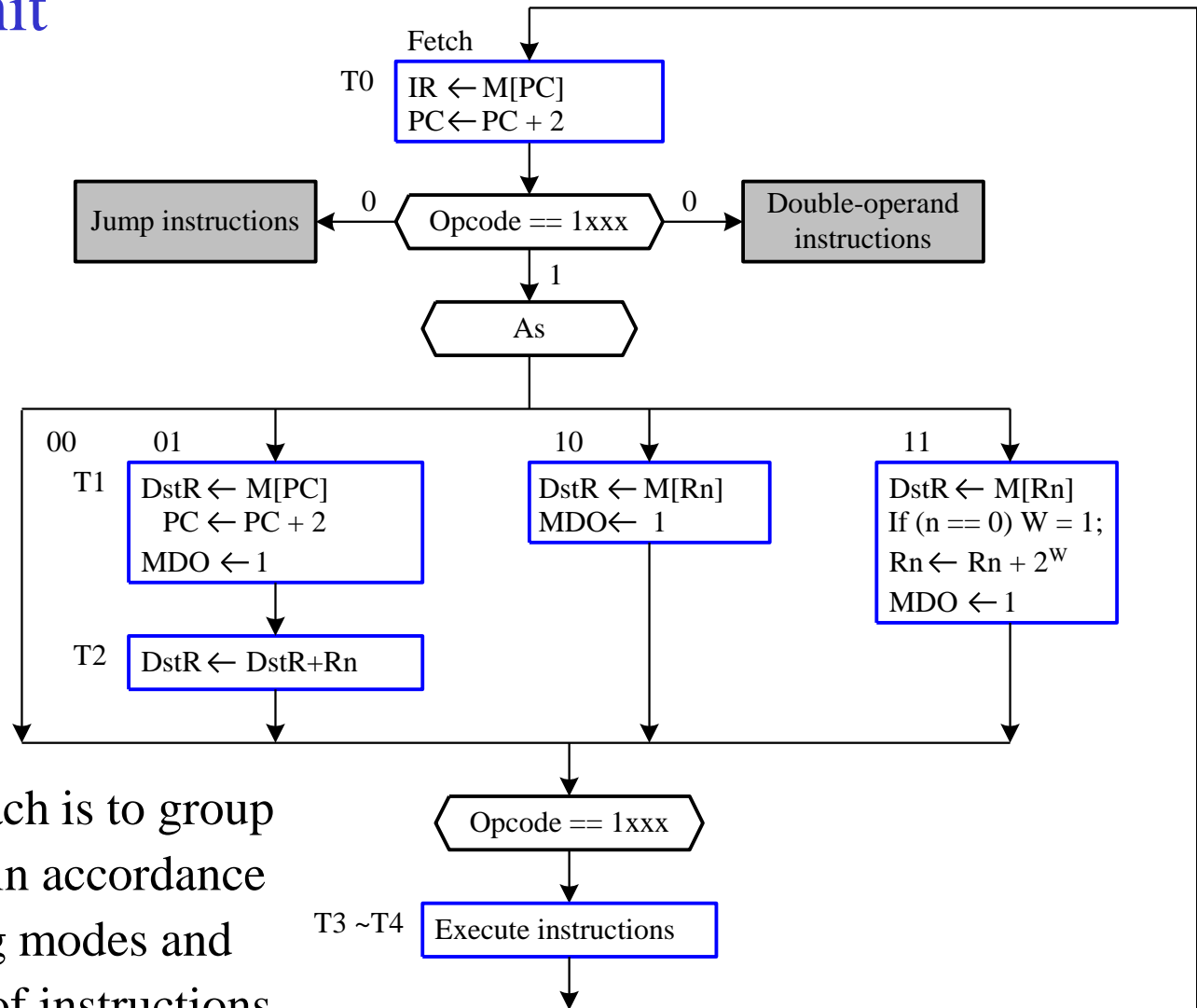

❖ A better approach is to group the instruction in accordance with addressing modes and the operations of instructions.

A Control Unit

- ❖ The operations of T3 and T4 are determined separately by each instruction.

| | | T3 | T4 |
|------------------------|--------|--|-----------------------------------|
| RRA (0001_0001_00) | MDO =0 | $Rd \leftarrow ARS(Rd)$ | |
| | MDO =1 | $SrcR \leftarrow M[DstR]$ | $M[DstR] \leftarrow ARS(SrcR)$ |
| RRC (0001_0000_00) | MDO =0 | $Rd \leftarrow Rotate(Rd)$ | |
| | MDO =1 | $SrcR \leftarrow M[DstR]$ | $M[DstR] \leftarrow Rotate(SrcR)$ |
| PUSH (0001_0010_00) | MDO =0 | $SP \leftarrow SP -2$ | $M[SP] \leftarrow Rs$ |
| | MDO =1 | $SP \leftarrow SP -2$ $SrcR \leftarrow M[DstR]$ | $M[SP] \leftarrow SrcR$ |