

Digital Logic Design

4190.201.001

2010 Spring Semester

3. Combinational Logic

Naehyuck Chang
Dept. of EECS/CSE
Seoul National University
naehyuck@snu.ac.kr



Introduction

- Combinational logic
 - Whose output is solely determined by their inputs
- Representation of a function
 - Truth table
 - Boolean equation
 - Sum of products, a two-level form
 - Unique way to represent a logic like a finger print
 - Alternative form is product of sums
 - Can be done in many ways
 - Highly desirable to find the simplest implementation
 - Gates and wires
- Boolean minimization
 - Karnaugh map, etc.
 - Fundamental tradeoff between time and space (speed and area: gates and wires)
 - Two-level logic and multi-leveled logic



Introduction

- Time response of in digital network
 - Non-zero propagation delay



Introduction

- Definition
 - Output behavior depends on the current input
 - Memoryless
 - Example: adder
 - The output changes shortly after the input changes, but the previous input has nothing to do with the current output
- Comparison with sequential logic
 - There is memory or state
 - Whose output depends both the input and the state
 - Example: traffic light
- Simple combinational circuits representing with truth tables

X	Y	Equal
0	0	1
0	1	0
1	0	0
1	1	1

Comparator

X	Y	Zero	One	Two
0	0	1	0	0
0	1	0	1	0
1	0	0	1	0
1	1	0	0	1

Tally circuit



Introduction


- More examples
 - Half adder: output the carry but cannot be chained
 - Full adder: can be chained
- Truth table
 - Suitable with a modest number of inputs
 - 2^n number of rows where n is the number of inputs

A	B	Carry	Sum
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

Half adder

Introduction

Full adder

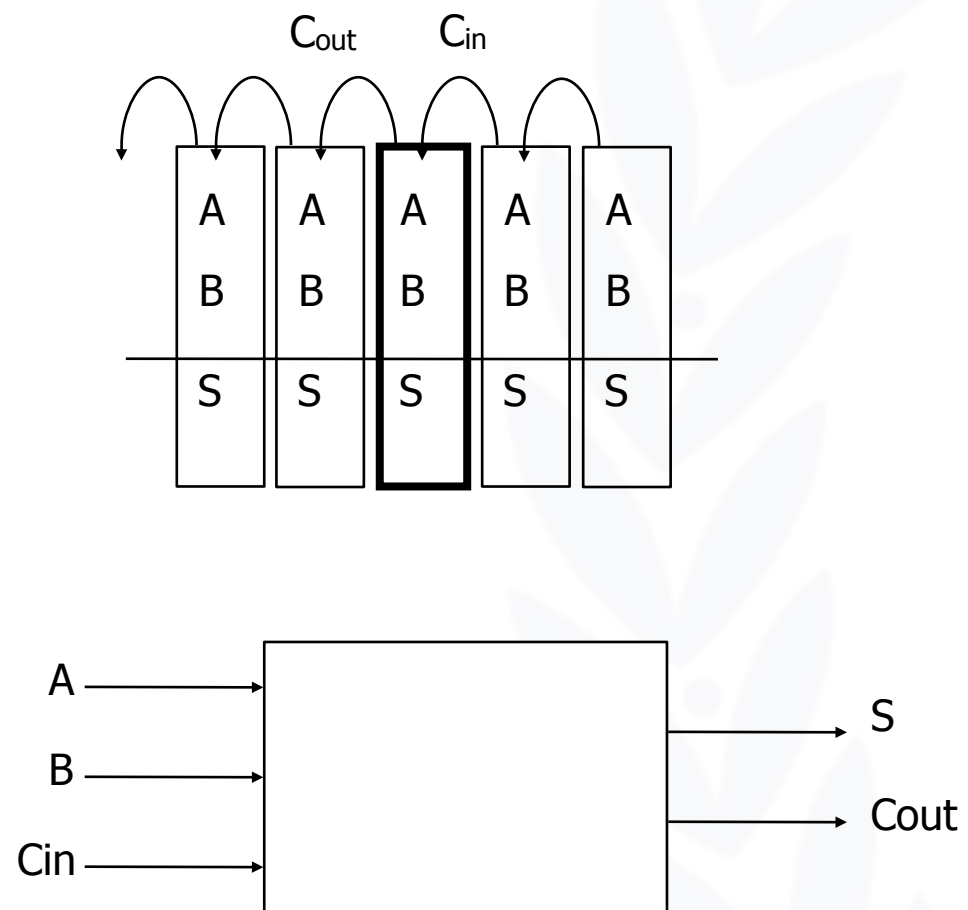

A	A	Cin	Carry	Sum
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

Full adder

An Algebraic Structure

- An algebraic structure consists of
 - A set of elements B
 - Binary operations $\{ +, \cdot \}$
 - And a unary operation $\{ ' \}$
 - Such that the following axioms hold:

- 1. The set B contains at least two elements a, b such that a is not equal to b
- 2. Closure: $a + b \in B, a \cdot b \in B$
- 3. Commutativity: $a + b = b + a, a \cdot b = b \cdot a$
- 4. Associativity: $a + (b + c) = (a + b) + c, a \cdot (b \cdot c) = (a \cdot b) \cdot c$
- 5. Identity: $a + 0 = a, a \cdot 1 = a$
- 6. Distributivity: $a + (b \cdot c) = (a + b) \cdot (a + c), a \cdot (b + c) = (a \cdot b) + (a \cdot c)$
- 7. Complementarity: $a + a' = 1, a \cdot a' = 0$

- Order of operations
 - Complement, AND and then OR
- AND and OR are not the same to the arithmetic operations MULTIPLY and PLUS



Truth Tables

- Any logic function that can be expressed as a truth table can be written as an expression in Boolean algebra using the operators: $'$, $+$, and \bullet
- Equivalence of Boolean expressions and truth tables
 - Can be readily derived from each other

X	Y	$X \bullet Y$
0	0	0
0	1	0
1	0	0
1	1	1

X	Y	X'	$X' \bullet Y$
0	0	1	0
0	1	1	1
1	0	0	0
1	1	0	0

X	Y	X'	Y'	$X \bullet Y$	$X' \bullet Y'$	$(X \bullet Y) + (X' \bullet Y')$
0	0	1	1	0	1	1
0	1	1	0	0	0	0
1	0	0	1	0	0	0
1	1	0	0	1	0	1

$$(X \bullet Y) + (X' \bullet Y') \equiv X = Y$$

X, Y are Boolean algebra variables

Boolean expression that is true when the variables X and Y have the same value and false, otherwise

Truth Tables

- Reduced carry out full adder expression

- $C_{out} = (AC_{in}) + (BC_{in}) + (AB)$

A	A	C _{in}	AC _{in}	BC _{in}	AB	C _{out}
0	0	0	0	0	0	0
0	0	1	0	0	0	0
0	1	0	0	0	0	0
0	1	1	0	1	0	1
1	0	0	0	0	0	0
1	0	1	1	0	0	1
1	1	0	0	0	1	1
1	1	1	1	1	1	1

Truth Tables

Deriving expressions from truth tables

$S =$

$C_{out} =$

A	B	C_{in}	C_{out}	Sum
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

Theorems of Boolean Algebra

- Duality

- A dual of a Boolean expression is derived by replacing
 - by +, + by •, 0 by 1, and 1 by 0, and leaving variables unchanged
- Any theorem that can be proven is thus also proven for its dual!
- A meta-theorem (a theorem about theorems)

- Duality:

- $X + Y + \dots \Leftrightarrow X \cdot Y \cdot \dots$

- Generalized duality:

- $f(X_1, X_2, \dots, X_n, 0, 1, +, \cdot) \Leftrightarrow f(X_1, X_2, \dots, X_n, 1, 0, \cdot, +)$

- Different from deMorgan's Law

- This is a statement about theorems
- This is not a way to manipulate (re-write) expressions



Theorems of Boolean Algebra

- Identity

- 1. $X + 0 = X$

- 1D. $X \cdot 1 = X$

- Null

- 2. $X + 1 = 1$

- 2D. $X \cdot 0 = 0$

- Idempotency:

- 3. $X + X = X$

- 3D. $X \cdot X = X$

- Involution:

- 4. $(X')' = X$

- Complementarity:

- 5. $X + X' = 1$

- 5D. $X \cdot X' = 0$

- Commutativity:

- 6. $X + Y = Y + X$

- 6D. $X \cdot Y = Y \cdot X$

- Associativity:

- 7. $(X + Y) + Z = X + (Y + Z)$

- 7D. $(X \cdot Y) \cdot Z = X \cdot (Y \cdot Z)$



Theorems of Boolean Algebra

• Distributivity:

$$\bullet \text{ 8. } X \bullet (Y + Z) = (X \bullet Y) + (X \bullet Z) \quad \text{8D. } X + (Y \bullet Z) = (X + Y) \bullet (X + Z)$$

• Uniting:

$$\bullet \text{ 9. } X \bullet Y + X \bullet Y' = X \quad \text{9D. } (X + Y) \bullet (X + Y') = X$$

• Absorption:

$$\bullet \text{ 10. } X + X \bullet Y = X \quad \text{10D. } X \bullet (X + Y) = X$$
$$\bullet \text{ 11. } (X + Y') \bullet Y = X \bullet Y \quad \text{11D. } (X \bullet Y') + Y = X + Y$$

• Factoring:

$$\bullet \text{ 12. } (X + Y) \bullet (X' + Z) = X \bullet Z + X' \bullet Y \quad \text{12D. } X \bullet Y + X' \bullet Z = (X + Z) \bullet (X' + Y)$$

• Consensus:

$$\bullet \text{ 13. } (X \bullet Y) + (Y \bullet Z) + (X' \bullet Z) = X \bullet Y + X' \bullet Z \quad \text{13D. } (X + Y) \bullet (Y + Z) \bullet (X' + Z) = (X + Y) \bullet (X' + Z)$$



Proving Theorems (Rewriting)

- Using the axioms of Boolean algebra:

- e.g., prove the theorem:

$$X \bullet Y + X \bullet Y' = X$$

distributivity (8)
complementarity (5)
identity (1D)

$$\begin{aligned} X \bullet Y + X \bullet Y' &= X \bullet (Y + Y') \\ X \bullet (Y + Y') &= X \bullet (1) \\ X \bullet (1) &= X \end{aligned}$$

- e.g., prove the theorem:

$$X + X \bullet Y = X$$

identity (1D)
distributivity (8)
identity (2)
identity (1D)

$$\begin{aligned} X + X \bullet Y &= X \bullet 1 + X \bullet Y \\ X \bullet 1 + X \bullet Y &= X \bullet (1 + Y) \\ X \bullet (1 + Y) &= X \bullet (1) \\ X \bullet (1) &= X \end{aligned}$$

Activity

● Prove the following using the laws of Boolean algebra:

● $(X \bullet Y) + (Y \bullet Z) + (X' \bullet Z) = X \bullet Y + X' \bullet Z$

identity

$$(X \bullet Y) + (Y \bullet Z) + (X' \bullet Z)$$

$$(X \bullet Y) + (1) \bullet (Y \bullet Z) + (X' \bullet Z)$$

complementarity

$$(X \bullet Y) + (X' + X) \bullet (Y \bullet Z) + (X' \bullet Z)$$

distributivity

$$(X \bullet Y) + (X' \bullet Y \bullet Z) + (X \bullet Y \bullet Z) + (X' \bullet Z)$$

commutativity

$$(X \bullet Y) + (X \bullet Y \bullet Z) + (X' \bullet Y \bullet Z) + (X' \bullet Z)$$

commutativity

$$(X \bullet Y) + (X \bullet Y) \bullet Z + (X' \bullet Z) + (X' \bullet Z) \bullet Y$$

absorption

$$(X \bullet Y) + (X' \bullet Z)$$



Activity

- Full adder example

- $C_{out} = A'BC_{in} + AB'C_{in} + ABC_{in}' + ABC_{in}$

- Idempotent (introduces a redundant term)

- $C_{out} = A'BC_{in} + AB'C_{in} + ABC_{in}' + ABC_{in} + ABC_{in}$

- Commutative (rearranges terms)

- $C_{out} = A'BC_{in} + ABC_{in} + AB'C_{in} + ABC_{in}' + ABC_{in}$

- Distributed (factors out common literals)

- $C_{out} = (A' + A)BC_{in} + AB'C_{in} + ABC_{in}' + ABC_{in}$

- Complementarity (replaces $A' + A$ to 1)

- $C_{out} = (1)BC_{in} + AB'C_{in} + ABC_{in}' + ABC_{in}$

- Identity (replaces $1X$ to X)

- $C_{out} = BC_{in} + AB'C_{in} + ABC_{in}' + ABC_{in}$

- Finally

- $C_{out} = BC_{in} + AC_{in} + AB$



DeMorgan's Law

- DeMorgan's law

- Establishes relationship between \bullet and $+$

- Theorem:

- 14. $(X + Y + \dots)' = X' \bullet Y' \bullet \dots$

- 14D. $(X \bullet Y \bullet \dots)' = X' + Y' + \dots$

- Generalized DeMorgan's:

- 15. $f'(X_1, X_2, \dots, X_n, 0, 1, +, \bullet) = f(X_1', X_2', \dots, X_n', 1, 0, \bullet, +)$

- Purpose

- Negative logic



Proving Theorems (Perfect Induction)

- Using perfect induction (complete truth table):
 - e.g., de Morgan's:

$(X + Y)' = X' \cdot Y'$
NOR is equivalent to AND
with inputs complemented

X	Y	X'	Y'	$(X + Y)'$	$X' \cdot Y'$
0	0	1	1	1	1
0	1	1	0	0	0
1	0	0	1	0	0
1	1	0	0	0	0

$(X \cdot Y)' = X' + Y'$
NAND is equivalent to OR
with inputs complemented

X	Y	X'	Y'	$(X \cdot Y)'$	$X' + Y'$
0	0	1	1	1	1
0	1	1	0	1	1
1	0	0	1	1	1
1	1	0	0	0	0

Possible Logic Functions of Two Variables

- There are 16 possible functions of 2 input variables:
 - In general, there are 2^{2^n} functions of n inputs



		16 possible functions (F0–F15)															
X	Y	0	0	0	0	0	0	0	0	0	0	1	1	1	1	1	1
		0	1	0	1	0	1	0	1	0	1	0	0	1	0	1	1
0	0	0	0	0	0	0	0	0	0	0	0	1	1	1	1	1	1
0	1	0	0	0	0	1	1	1	1	1	1	0	0	0	0	0	0
1	0	0	0	1	1	0	0	1	1	0	0	0	1	1	0	1	1
1	1	0	1	0	1	0	1	0	1	1	1	0	1	0	1	0	1
		0		X		Y		X <u>xor</u> Y		X <u>or</u> Y		X <u>nor</u> Y not (X <u>or</u> Y)		X = Y		not Y	
		X and Y														not X	
																X nand Y not (X and Y)	
																1	

Cost of Different Logic Functions

- Different functions are easier or harder to implement
 - Each has a cost associated with the number of switches needed
 - 0 (F0) and 1 (F15): require 0 switches, directly connect output to low/high
 - X (F3) and Y (F5): require 0 switches, output is one of inputs
 - X' (F12) and Y' (F10): require 2 switches for "inverter" or NOT-gate
 - X nor Y (F4) and X nand Y (F14): require 4 switches
 - X or Y (F7) and X and Y (F1): require 6 switches
 - $X = Y$ (F9) and $X \oplus Y$ (F6): require 16 switches
- Thus, because NOT, NOR, and NAND are the cheapest they are the functions we implement the most in practice
- But if we consider the target technology (logic structure), the story is different
 - To be learned from electronics circuit, semiconductor and advanced digital system design



Minimal Set of Functions

- Can we implement all logic functions from NOT, NOR, and NAND?
 - For example, implementing X and Y is the same as implementing $\text{not } (X \text{ nand } Y)$
- In fact, we can do it with only NOR or only NAND
 - NOT is just a NAND or a NOR with both inputs tied together

X	Y	X nor Y
0	0	1
1	1	0

X	Y	X nand Y
0	0	1
1	1	0

- And NAND and NOR are "duals", that is, its easy to implement one using the other

$$\begin{aligned} X \text{ nand } Y &\equiv \text{not } (\text{not } X \text{ nor } \text{not } Y) \\ X \text{ nor } Y &\equiv \text{not } (\text{not } X \text{ nand } \text{not } Y) \end{aligned}$$

- But lets not move too fast . . .
 - Let's look at the mathematical foundation of logic




From Boolean Expressions to Logic Gates

● NOT

X'

\overline{X}

$\sim X$

 


X	Y
0	1
1	0

● AND

$X \bullet Y$

XY

$X \wedge Y$

 


X	Y	Z
0	0	0
0	1	0
1	0	0
1	1	1

● OR

$X + Y$

$X \vee Y$

 

X	Y	Z
0	0	0
0	1	1
1	0	1
1	1	1


From Boolean Expressions to Logic Gates

● NAND




X	Y	Z
0	0	1
0	1	1
1	0	1
1	1	0

● NOR

 

X	Y	Z
0	0	1
0	1	0
1	0	0
1	1	0


● XOR
 $X \oplus Y$

 

X	Y	Z
0	0	0
0	1	1
1	0	1
1	1	0

$X \text{ xor } Y = X Y' + X' Y$
X or Y but not both
("inequality", "difference")

● XNOR
 $X \equiv Y$

 

X	Y	Z
0	0	1
0	1	0
1	0	0
1	1	1



$X \text{ xnor } Y = X Y + X' Y'$
X and Y are the same
("equality", "coincidence")



From Boolean Expressions to Logic Gates

- More than one way to map expressions to gates

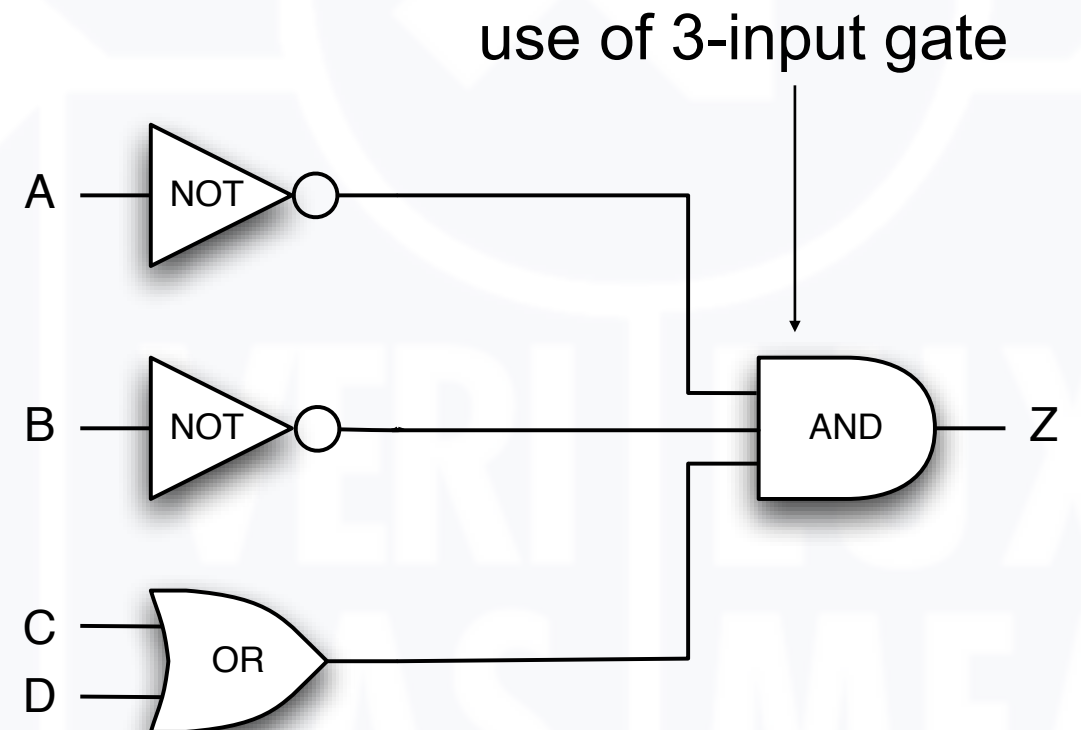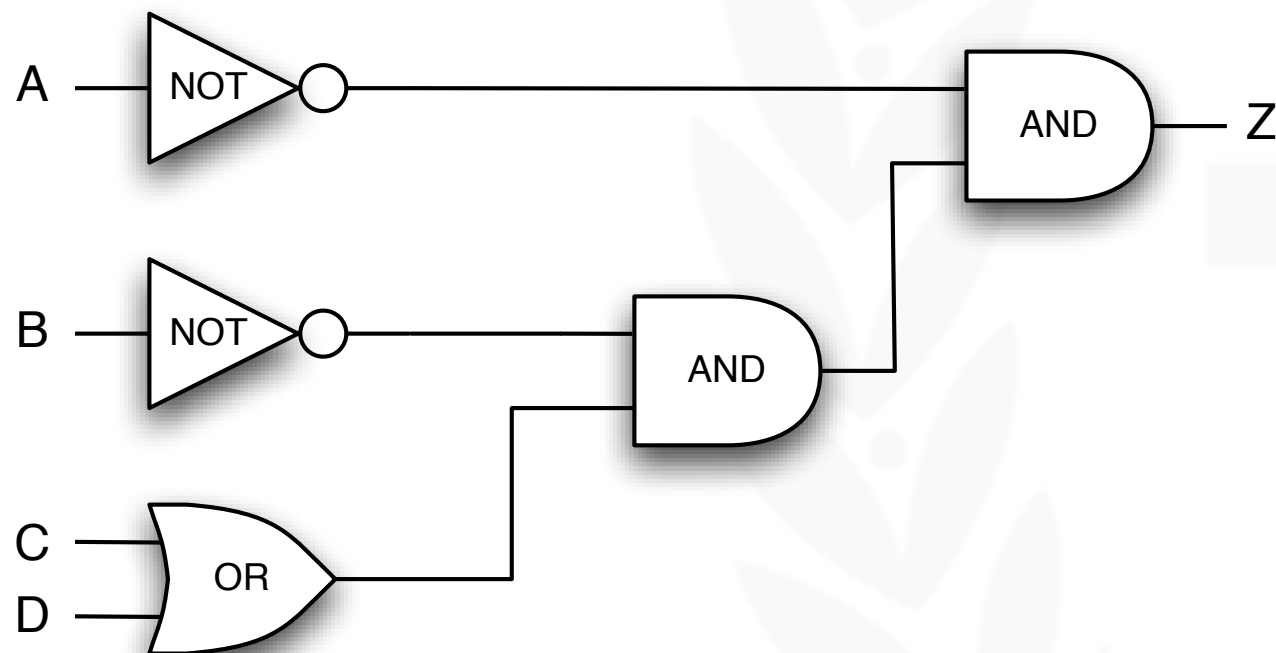e.g., $Z = A' \cdot B' \cdot (C + D) = (A' \cdot (B' \cdot (C + D)))$



From Boolean Expressions to Logic Gates

- Implication


- X implies Y: $X \Rightarrow Y$

- Is false only when X is true and Y is false




Logic Blocks and Hierarchy

Half adder

 


A	B	Carry	Sum
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

Full adder

 


Logic Blocks and Hierarchy

2 bit full adder

 

Waveform View of Logic Functions

 
- Just a sideways truth table
 - But note how edges don't line up exactly
 - It takes time for a gate to switch its output!



Change in Y takes time to "propagate" through gates

Time and Space Tradeoff

A	B	C	Z
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	0

 

Two-level realization
(We don't count NOT gates)

Multi-level realization
(Gates with fewer inputs)

XOR gate (easier to draw
but costlier to build)

Which Realization is Best?

- Reduce number of inputs
 - Literal: input variable (complemented or not)
 - Can approximate cost of logic gate as 2 transistors per literal
 - Why not count inverters?
 - Fewer literals means less transistors
 - Smaller circuits
 - Fewer inputs implies faster gates
 - Gates are smaller and thus also faster
 - Fan-ins (# of gate inputs) are limited in some technologies
- Reduce number of gates
 - Fewer gates (and the packages they come in) means smaller circuits
 - Directly influences manufacturing costs




Which Is the Best Realization?

- Reduce number of levels of gates
 - Fewer level of gates implies reduced signal propagation delays
 - Minimum delay configuration typically requires more gates
 - Wider, less deep circuits
- How do we explore tradeoffs between increased circuit delay and size?
 - Automated tools to generate different solutions
 - Logic minimization: reduce number of gates and complexity
 - Logic optimization: reduction while trading off against delay



Are All Realizations Equivalent?

 - Under the same input stimuli, the three alternative implementations have almost the same waveform behavior
 - Delays are different
 - Glitches (hazards) may arise – these could be bad, it depends
 - Variations due to differences in number of gate levels and structure
- The three implementations are functionally equivalent



Implementing Boolean Functions

- Technology independent
 - Canonical forms
 - Two-level forms
 - Multi-level forms
- Technology choices
 - Packages of a few gates
 - Regular logic
 - Two-level programmable logic
 - Multi-level programmable logic



Canonical Forms

- Truth table is the unique signature of a Boolean function
- The same truth table can have many gate realizations
- Canonical forms
 - Standard forms for a Boolean expression
 - Provides a unique algebraic signature



Sum-of-Products Canonical Forms

- Also known as disjunctive normal form
- Also known as minterm expansion
 - Minterm contains one version of every literal
 - Each minterm covers only one row
 - Minterms are ORed together to form the complete function

$F = 001 \quad 011 \quad 101 \quad 110 \quad 111$
 $F = A'B'C + A'BC + AB'C + ABC' + ABC$

A	B	C	F	F'
0	0	0	0	1
0	0	1	1	0
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	0

$F' = A'B'C' + A'BC' + AB'C'$

35

Sum-of-Products Canonical Form

- Product term and minterm
 - AB is a product term but not a minterm
 - ABC is a product term and a minterm
 - ANDed product of literals – input combination for which output is true
 - Each variable appears exactly once, true or inverted (but not both)

A	B	C	minterms
0	0	0	$A'B'C'$ m0
0	0	1	$A'B'C$ m1
0	1	0	$A'BC'$ m2
0	1	1	$A'BC$ m3
1	0	0	$AB'C'$ m4
1	0	1	$AB'C$ m5
1	1	0	ABC' m6
1	1	1	ABC m7

Short-hand notation for
minterms of 3 variables

F in canonical form:

$$\begin{aligned}F(A, B, C) &= \Sigma m(1,3,5,6,7) \\&= m1 + m3 + m5 + m6 + m7 \\&= A'B'C + A'BC + AB'C + ABC' + ABC\end{aligned}$$

Canonical form \neq minimal form

$$\begin{aligned}F(A, B, C) &= A'B'C + A'BC + AB'C + ABC + ABC' \\&= (A'B' + A'B + AB' + AB)C + ABC' \\&= ((A' + A)(B' + B))C + ABC' \\&= C + ABC' \\&= ABC' + C \\&= AB + C\end{aligned}$$



Product-of-Sums Canonical Form

- Also known as conjunctive normal form
- Also known as maxterm expansion
 - Maxterm contains one version of every literal
 - Each maxterm covers all but one row
 - Maxterms are ANDed together and form the complete function

A	B	C	F	F'
0	0	0	0	1
0	0	1	1	0
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	0

$$A+B+C$$

A	B	C	F	F'
0	0	0	0	1
0	0	1	1	0
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	0

$$A+B'+C$$

A	B	C	F	F'
0	0	0	0	1
0	0	1	1	0
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	0

$$A'+B+C$$

A	B	C	F	F'
0	0	0	0	1
0	0	1	1	0
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	0

$$F=(A+B+C)(A+B'+C)(A'+B+C)$$

Product-of-Sums Canonical Form (cont'd)

- Sum term and maxterm

- A+B is a sum term but not a maxterm
- A+B+C is a sum term and a maxterm
- ORed sum of literals – input combination for which output is false
- Each variable appears exactly once, true or inverted (but not both)

A	B	C	maxterms	
0	0	0	$A+B+C$	M0
0	0	1	$A+B+C'$	M1
0	1	0	$A+B'+C$	M2
0	1	1	$A+B'+C'$	M3
1	0	0	$A'+B+C$	M4
1	0	1	$A'+B+C'$	M5
1	1	0	$A'+B'+C$	M6
1	1	1	$A'+B'+C'$	M7

Short-hand notation for maxterms of 3 variables

F in canonical form:

$$\begin{aligned}
 F(A, B, C) &= \prod M(0, 2, 4) \\
 &= M0 \cdot M2 \cdot M4 \\
 &= (A + B + C) (A + B' + C) (A' + B + C)
 \end{aligned}$$

Canonical form \neq minimal form

$$\begin{aligned}
 F(A, B, C) &= (A + B + C) (A + B' + C) (A' + B + C) \\
 &= (A + B + C) (A + B' + C) \\
 &\quad (A + B + C) (A' + B + C) \\
 &= (A + C) (B + C)
 \end{aligned}$$



S-o-P, P-o-S, and de Morgan's Theorem

- Sum-of-products

- $F' = A'B'C' + A'BC' + AB'C'$

- Apply de Morgan's

- $(F')' = (A'B'C' + A'BC' + AB'C')'$

- $F = (A + B + C)(A + B' + C)(A' + B + C)$

- Product-of-sums

- $F' = (A + B + C')(A + B' + C')(A' + B + C')(A' + B' + C)(A' + B' + C')$


- Apply de Morgan's

- $(F')' = ((A + B + C')(A + B' + C')(A' + B + C')(A' + B' + C)(A' + B' + C'))'$

- $F = A'B'C + A'BC + AB'C + ABC' + ABC$




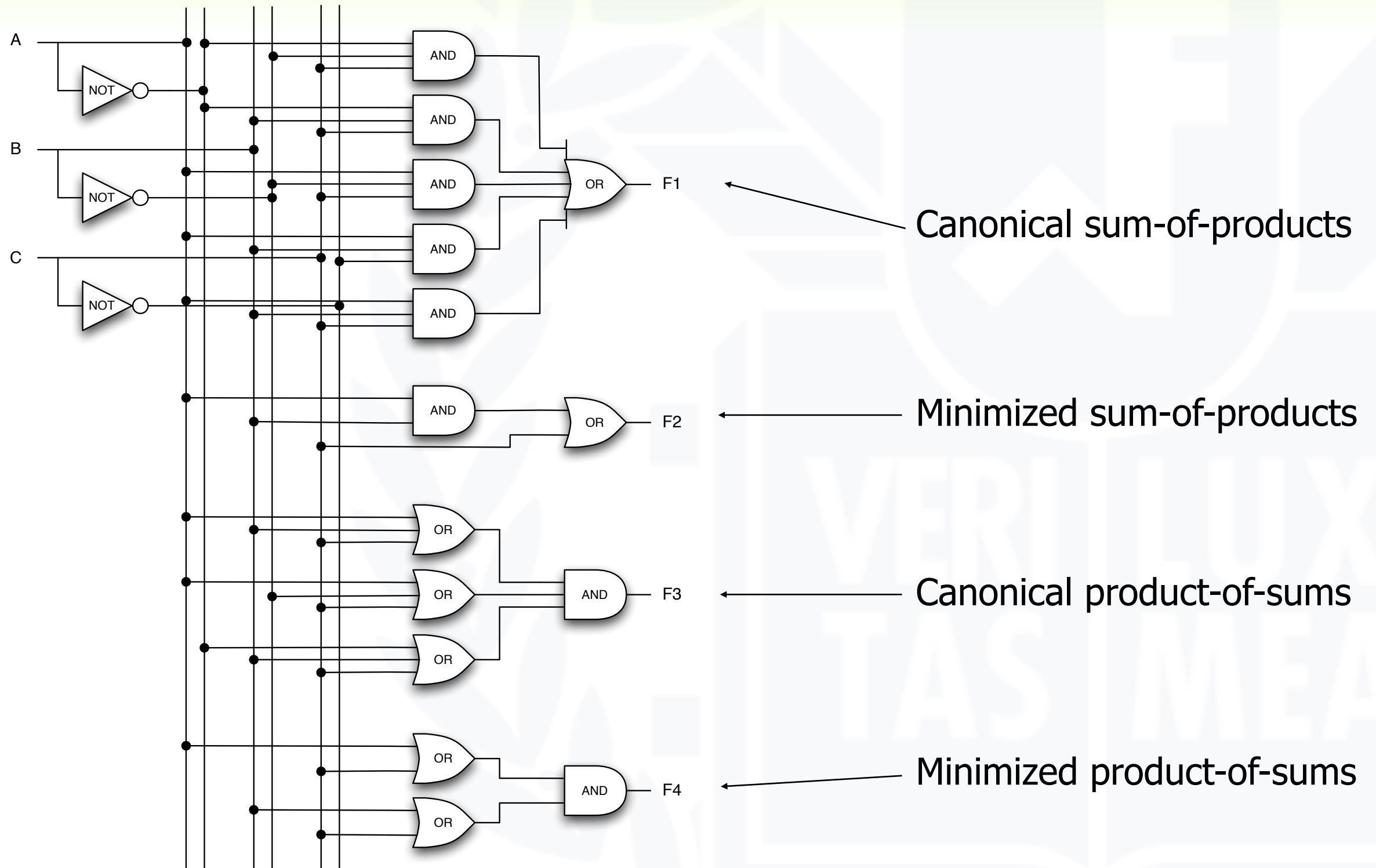Four Alternative Two-Level Implementations of $F = AB + C$



Waveforms for the Four Alternatives

 - Waveforms are essentially identical
 - Except for timing hazards (glitches)
 - Delays almost identical (modeled as a delay per level, not type of gate or number of inputs to gate)




Mapping Between Canonical Forms

- Minterm to maxterm conversion
 - Use maxterms whose indices do not appear in minterm expansion
 - e.g., $F(A,B,C) = \sum m(1,3,5,6,7) = \prod M(0,2,4)$
- Maxterm to minterm conversion
 - Use minterms whose indices do not appear in maxterm expansion
 - e.g., $F(A,B,C) = \prod M(0,2,4) = \sum m(1,3,5,6,7)$
- Minterm expansion of F to minterm expansion of F'
 - Use minterms whose indices do not appear
 - e.g., $F(A,B,C) = \sum m(1,3,5,6,7)$ $F'(A,B,C) = \sum m(0,2,4)$
- Maxterm expansion of F to maxterm expansion of F'
 - Use maxterms whose indices do not appear
 - e.g., $F(A,B,C) = \prod M(0,2,4)$ $F'(A,B,C) = \prod M(1,3,5,6,7)$

Incompletely Specified Functions

 - Binary and BCD (decimal) representation



A3	A2	A1	A0	S3	S2	S1	S0
0	0	0	0	0	0	0	0
0	0	0	1	0	0	0	1
0	0	1	0	0	0	1	0
0	0	1	1	0	0	1	1
0	1	0	0	0	1	0	0
0	1	0	1	1	0	0	0
0	1	1	0	1	0	0	1
0	1	1	1	1	0	1	0
1	0	0	0	1	0	1	1
1	0	0	1	1	1	0	0
1	0	1	0	X	X	X	X
1	0	1	1	X	X	X	X
1	1	0	0	X	X	X	X
1	1	0	1	X	X	X	X
1	1	1	0	X	X	X	X
1	1	1	1	X	X	X	X

Incompletely Specified Functions

- Binary coded decimal increment by 1
 - BCD digits encode the decimal digits 0 – 9 in the bit patterns 0000 – 1001

A	B	C	D	W	X	Y	Z
0	0	0	0	0	0	0	1
0	0	0	1	0	0	1	0
0	0	1	0	0	0	1	1
0	0	1	1	0	1	0	0
0	1	0	0	0	1	0	1
0	1	0	1	0	1	1	0
0	1	1	0	0	1	1	1
0	1	1	1	1	0	0	0
1	0	0	0	1	0	0	1
1	0	0	1	0	0	0	0
1	0	1	0	X	X	X	X
1	0	1	1	X	X	X	X
1	1	0	0	X	X	X	X
1	1	0	1	X	X	X	X
1	1	1	0	X	X	X	X
1	1	1	1	X	X	X	X

Off-set of W

On-set of W

Don't care (DC) set of W


These inputs patterns should never be encountered in practice – **"don't care"** about associated output values, can be exploited in minimization

Notation For Incompletely Specified Functions



- Don't cares and canonical forms
 - So far, only represented on-set
 - Also represent don't-care-set
 - Need two of the three sets (on-set, off-set, dc-set)
- Canonical representations of the BCD increment by 1 function:
 - $Z = m_0 + m_2 + m_4 + m_6 + m_8 + d_{10} + d_{11} + d_{12} + d_{13} + d_{14} + d_{15}$
 - $Z = \Sigma [m(0,2,4,6,8) + d(10,11,12,13,14,15)]$
 - $Z = M_1 \bullet M_3 \bullet M_5 \bullet M_7 \bullet M_9 \bullet D_{10} \bullet D_{11} \bullet D_{12} \bullet D_{13} \bullet D_{14} \bullet D_{15}$
 - $Z = \Pi [M(1,3,5,7,9) \bullet D(10,11,12,13,14,15)]$

Examples

- BCD (decimal) to seven segment decoder

 

Seven segment LED

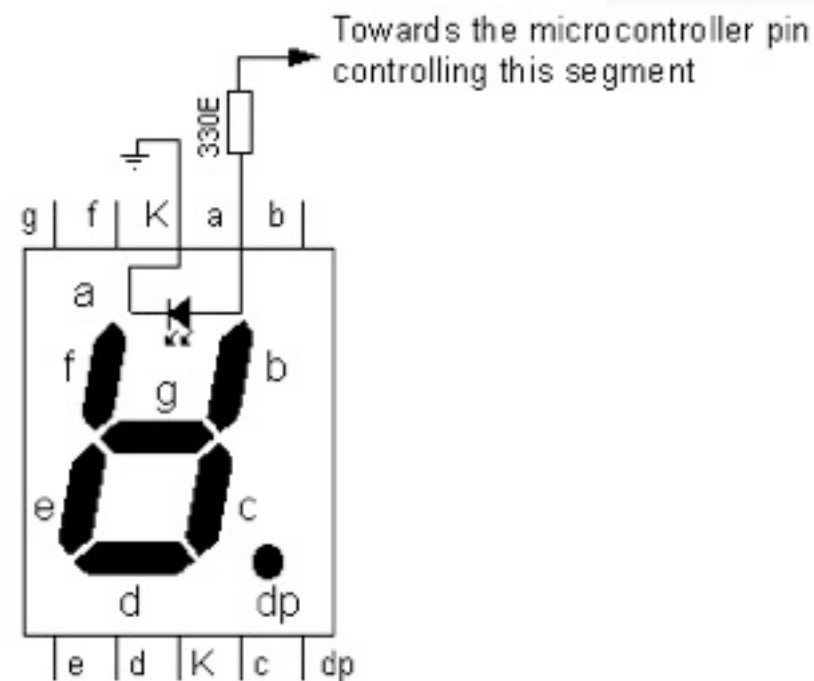 

Examples

- BCD to seven segment decoder
 - Truth table



Simplification of Two-Level Combinational Logic

- Motivation: is the following optimization is easy and systematic?

- $C_{out} = A'BC_{in} + AB'C_{in} + ABC_{in}' + ABC_{in}$
- Idempotent (introduces a redundant term)
 - $C_{out} = A'BC_{in} + AB'C_{in} + ABC_{in}' + ABC_{in} + ABC_{in}$
- Commutative (rearranges terms)
 - $C_{out} = A'BC_{in} + ABC_{in} + AB'C_{in} + ABC_{in}' + ABC_{in}$
- Distributed (factors out common literals)
 - $C_{out} = (A' + A)BC_{in} + AB'C_{in} + ABC_{in}' + ABC_{in}$
- Complementarity (replaces $A' + A$ to 1)
 - $C_{out} = (1)BC_{in} + AB'C_{in} + ABC_{in}' + ABC_{in}$
- Identity (replaces $1X$ to X)
 - $C_{out} = BC_{in} + AB'C_{in} + ABC_{in}' + ABC_{in}$
- Finally
 - $C_{out} = BC_{in} + AC_{in} + AB$

Simplification of Two-Level Combinational Logic

- Finding a minimal sum of products or product of sums realization
 - Exploit don't care information in the process
- Algebraic simplification
 - Not an algorithmic/systematic procedure
 - How do you know when the minimum realization has been found?
- Computer-aided design tools
 - Precise solutions require very long computation times, especially for functions with many inputs (> 10)
 - Heuristic methods employed – "educated guesses" to reduce amount of computation and yield good if not best solutions
- Hand methods still relevant
 - To understand automatic tools and their strengths and weaknesses
 - Ability to check results (on small examples)



The Uniting Theorem

- Key tool to simplification: $A(B' + B) = A$
- Essence of simplification of two-level logic
 - Find two element subsets of the ON-set where only one variable changes its value – this single varying variable can be eliminated and a single product term used to represent both elements

$$F = A'B' + AB' = (A' + A)B' = B'$$

A	B	F
0	0	1
0	1	0
1	0	1
1	1	0


B has the same value in both on-set rows
– B remains

A has a different value in the two rows
– A is eliminated


Boolean Cubes

- Visual technique for identifying when the uniting theorem can be applied
- n input variables = n -dimensional "cube"


1-cube

 


2-cube

 

3-cube

 


4-cube

 

Mapping Truth Tables onto Boolean Cubes

- Uniting theorem combines two "faces" of a cube into a larger "face"
- Example:


A	B	F
0	0	1
0	1	0
1	0	1
1	1	0

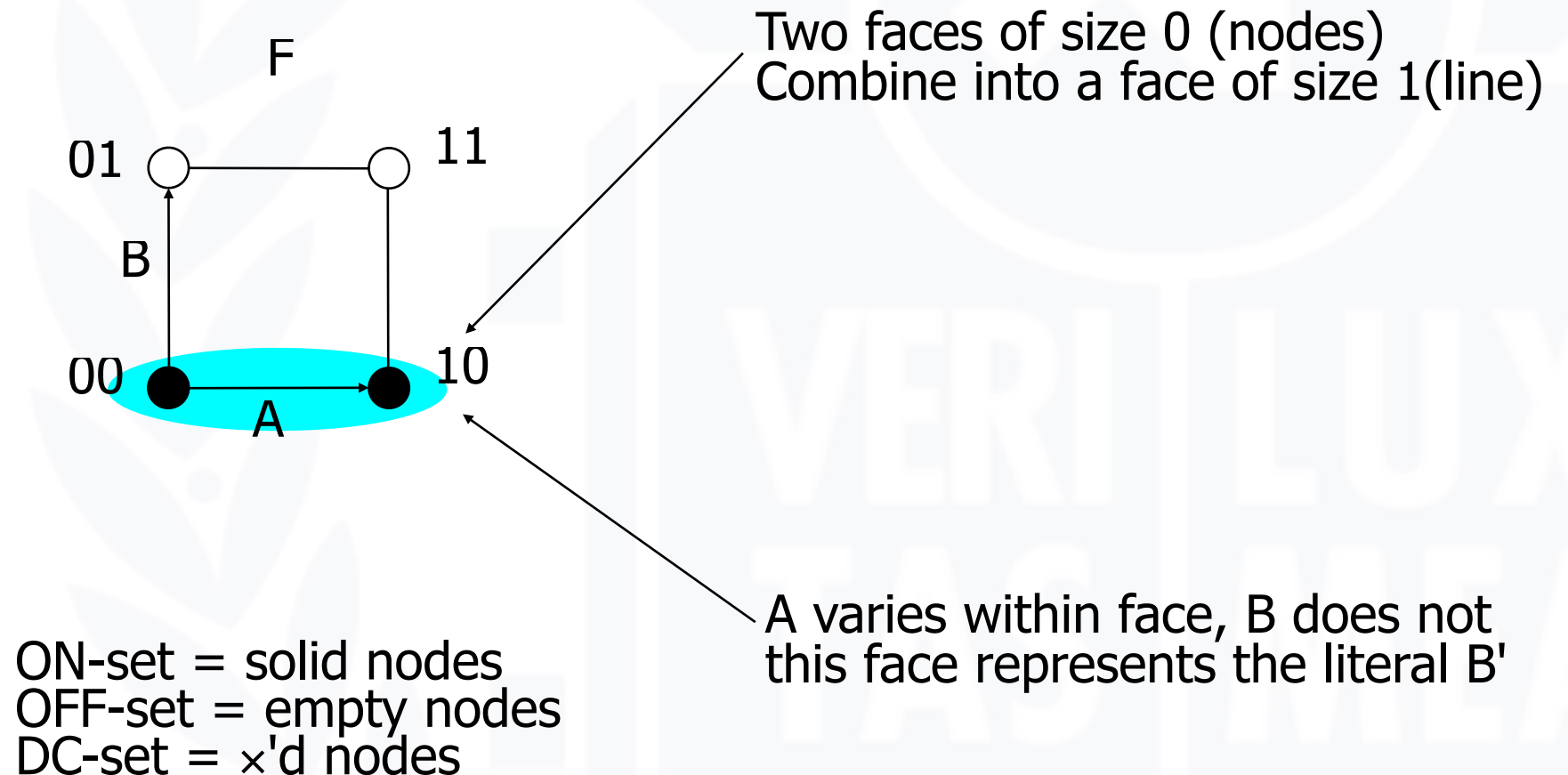

Three Variable Example

- Binary full-adder carry-out logic

A	B	Cin	Cout
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

 


The on-set is completely covered by the combination (OR) of the subcubes of lower dimensionality - note that "111" is covered three times

$$Cout = BCin + AB + ACin$$

Higher Dimensional Cubes

- Sub-cubes of higher dimension than 2

 

$$F(A,B,C) = \sum m(4,5,6,7)$$

On-set forms a square
i.e., a cube of dimension 2

Represents an expression in one variable
i.e., 3 dimensions – 2 dimensions

A is asserted (true) and unchanged
B and C vary

This subcube represents the
literal A

m-Dimensional Cubes in a n-Dimensional Boolean Space

- In a 3-cube (three variables):
 - A 0-cube, i.e., a single node, yields a term in 3 literals
 - A 1-cube, i.e., a line of two nodes, yields a term in 2 literals
 - A 2-cube, i.e., a plane of four nodes, yields a term in 1 literal
 - A 3-cube, i.e., a cube of eight nodes, yields a constant term "1"
- In general,
 - An m-subcube within an n-cube ($m < n$) yields a term with $n - m$ literals



Karnaugh Maps

- Flat map of Boolean cube
 - Wrap-around at edges
 - Hard to draw and visualize for more than 4 dimensions
 - Virtually impossible for more than 6 dimensions
- Alternative to truth-tables to help visualize adjacencies
 - Guide to applying the uniting theorem
 - On-set elements with only one variable changing value are adjacent unlike the situation in a linear truth-table

		A	
		0	1
B	0	0 1	2 1
	1	1 0	3 0

A	B	F
0	0	1
0	1	0
1	0	1
1	1	0



Karnaugh Maps (cont'd)

- Numbering scheme based on Gray-code
 - e.g., 00, 01, 11, 10
 - Only a single bit changes in code for adjacent map cells

C \ AB	A			
	00	01	11	10
0	0	2	6	4
1	1	3	7	5



C	A			
	0	2	6	4
1	1	3	7	5

C	A			
	0	4	12	8
1	1	5	13	9
3	3	7	15	11
2	2	6	14	10

$$13 = 1101 = ABC'D$$

Adjacencies in Karnaugh Maps

  - Wrap from first to last column
- Wrap top row to bottom row



Karnaugh Map Examples

● $F =$

● $Cout =$

● $f(A,B,C) = \Sigma m(0,4,5,7)$

	A		
	0	1	B'
B	1	1	
	0	0	

	A				
	0	0	1	0	
Cin	0	1	1	1	
					B

$$AB + ACin + BCin$$

obtain the complement of the function by covering 0s with subcubes

	A				
	1	0	0	1	
C	0	0	1	1	
					B

$$AC + B'C' + \cancel{AB'}$$



More Karnaugh Map Examples

		A		
	0	0	1	1
C	0	0	1	1
	B			

$$G(A,B,C) = A$$

		A		
	1	0	0	1
C	0	0	1	1
	B			

$$F(A,B,C) = \sum m(0,4,5,7) = AC + B'C'$$

		A		
	0	1	1	0
C	1	1	0	0
	B			

F' simply replace 1's with 0's and vice versa


$$F'(A,B,C) = \sum m(1,2,3,6) = BC' + A'C$$

Karnaugh Map: 4-Variable Example

● $F(A,B,C,D) = \sum m(0,2,3,5,6,7,8,10,11,14,15)$

$$F = C + A'BD + B'D'$$

	A				
	1	0	0	1	
	0	1	0	0	
C	1	1	1	1	D
	1	1	1	1	
B					

 

Find the smallest number of the largest possible subcubes to cover the ON-set
(fewer terms with fewer inputs per term)

Karnaugh Maps: Don't Cares

- $f(A,B,C,D) = \sum m(1,3,5,7,9) + d(6,12,13)$

- Without don't cares

- $f = A'D + B'C'D$

		A			
		0	0	X	0
		1	1	X	1
		1	1	0	0
C		0	X	0	0
		B		D	

Karnaugh Maps: Don't Cares

- $f(A,B,C,D) = \sum m(1,3,5,7,9) + d(6,12,13)$

- $f = A'D + B'C'D$

Without don't cares

- $f = A'D + C'D$

With don't cares

	A			
	0	0	X	0
	1	1	X	1
	1	1	0	0
C	0	X	0	0
	B			

D

By using don't care as a "1" a 2-cube can be formed rather than a 1-cube to cover this node

Don't cares can be treated as 1s or 0s depending on which is more advantageous

Activity

- Minimize the function $F = \sum m(0, 2, 7, 8, 14, 15) + d(3, 6, 9, 12, 13)$



Combinational Logic Summary

- Logic functions, truth tables, and switches
 - NOT, AND, OR, NAND, NOR, XOR, . . ., minimal set
- Axioms and theorems of Boolean algebra
 - Proofs by re-writing and perfect induction
- Gate logic
 - Networks of Boolean functions and their time behavior
- Canonical forms
 - Two-level and incompletely specified functions
- Simplification
 - A start at understanding two-level simplification
- Later
 - Automation of simplification
 - Multi-level logic
 - Time behavior
 - Hardware description languages
 - Design case studies

