

Lecture 8.

Introduction to RF Simulation

Jaeha Kim

Mixed-Signal IC and System Group (MICS)

Seoul National University

jaeha@ieee.org




Overview

- Readings:
 - K. Kundert, "Introduction to RF Simulation and Its Application," JSSC, Sept. 1999.
 - L. Zadeh, "Frequency Analysis of Variable Networks," Proc. I.R.E., Mar. 1950, pp. 291-299.
- Background:
 - This lecture introduces advanced class of simulation algorithms that perform linear, periodically time-varying (LPTV) analyses on circuits. These simulations are commonly referred to as "RF simulations", but once you understand the underlying principles, there are a myriad of ways to utilize them for broad classes of circuits beyond RF.




RF Transceiver

Direct Conversion Transmitter

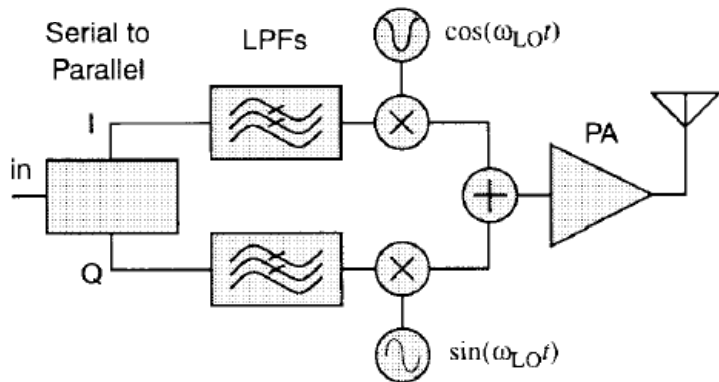

Super-Heterodyne Receiver

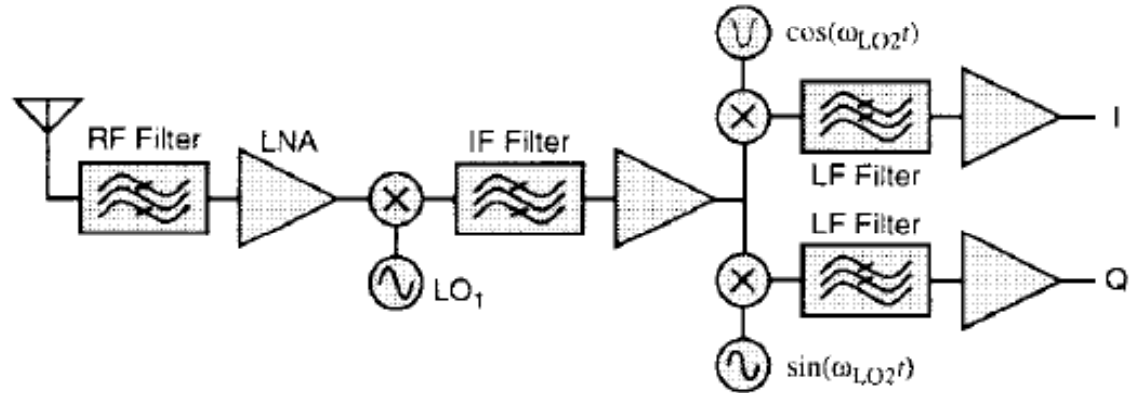

- Identify the key circuit blocks and their purposes
 - Filters, LNA, LO, mixers, PA, ...
- Which ones would have difficulties in characterizing their functionalities/performances using conventional SPICE?

SPICE Analysis Modes: TRAN

- TRAN: time-domain analysis
 - Most versatile way of simulating a circuit – measures the output time-waveforms for given inputs' time-waveforms
 - Note: when digital folks say “simulation”, they always mean this transient analysis (e.g. Verilog only runs in time-domain)


- Which blocks can you verify/characterize with TRAN?
 - Check each of filter, LNA, LO, mixer, PA, ...
 - Yes, you can simulate any circuits with TRAN but you can never completely verify the circuit with it
 - This is why digital people ask for “formal verification tools”

RF Characteristics I: Narrowband Signals

- RF signals are expressed as *modulated carriers*, e.g.,


$$y(t) = m(t) \times A_c \cdot \cos(\omega_c t)$$

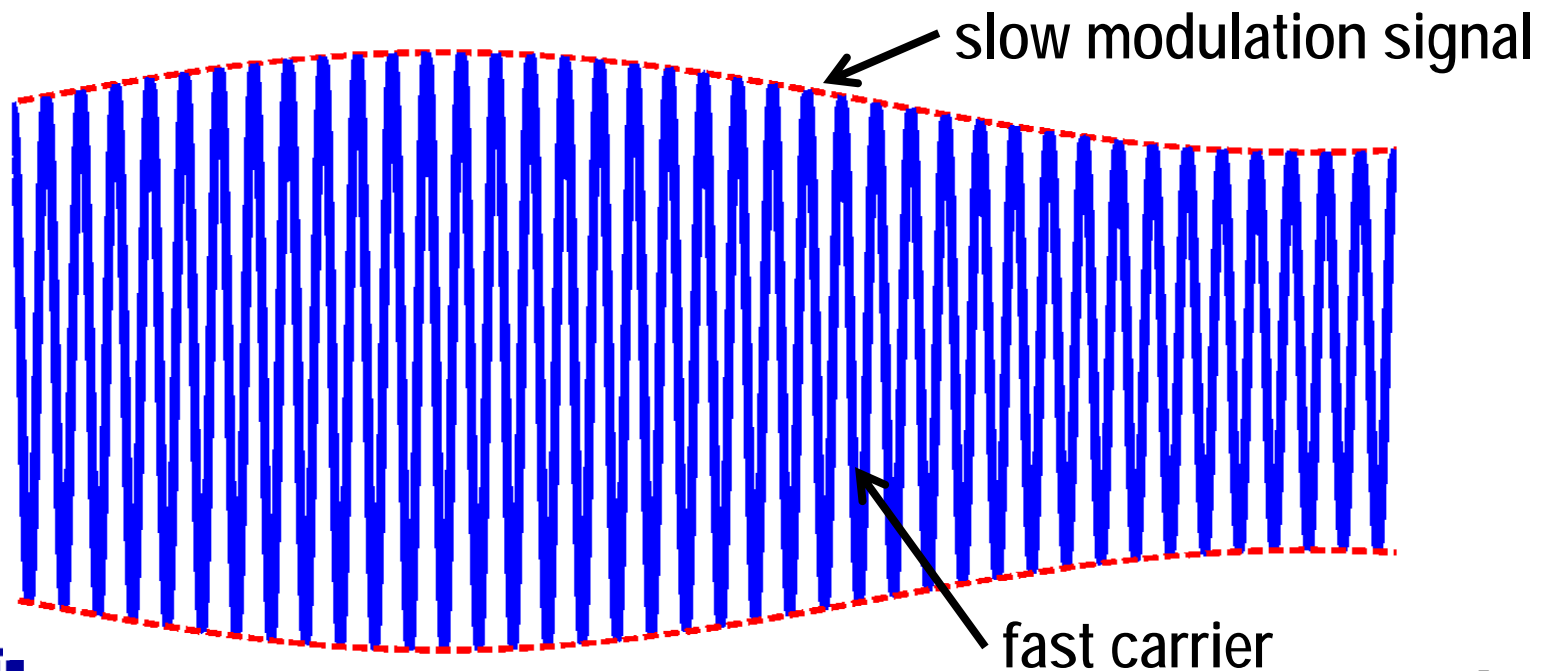- Amplitude, phase, or frequency can be modulated




RF Characteristics I: Narrowband Signals

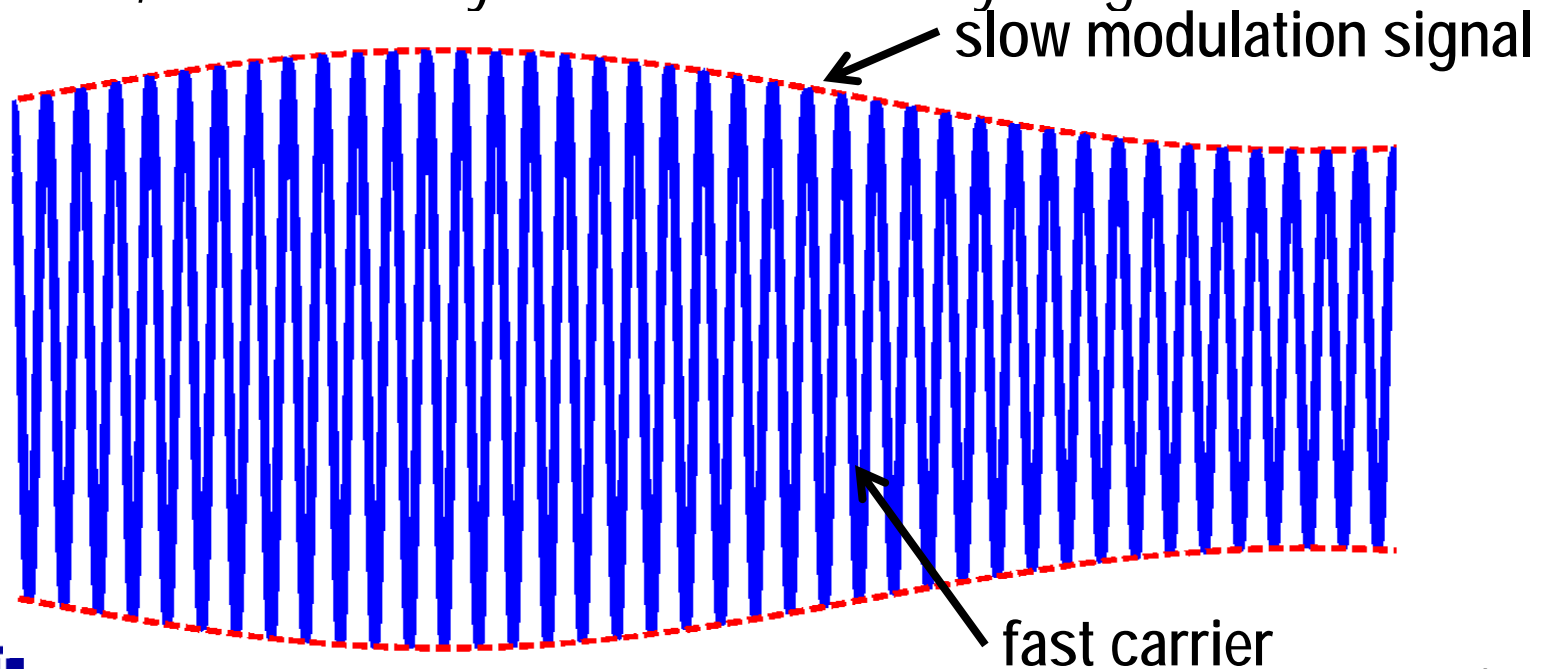- To measure RF circuit responses with TRAN analysis
 - We need fine time steps due to the high-frequency carrier
 - Also, long time span due to the low-frequency signal
- Hence, TRAN analysis can take a very long time



RF Analysis Modes: Envelope-Following

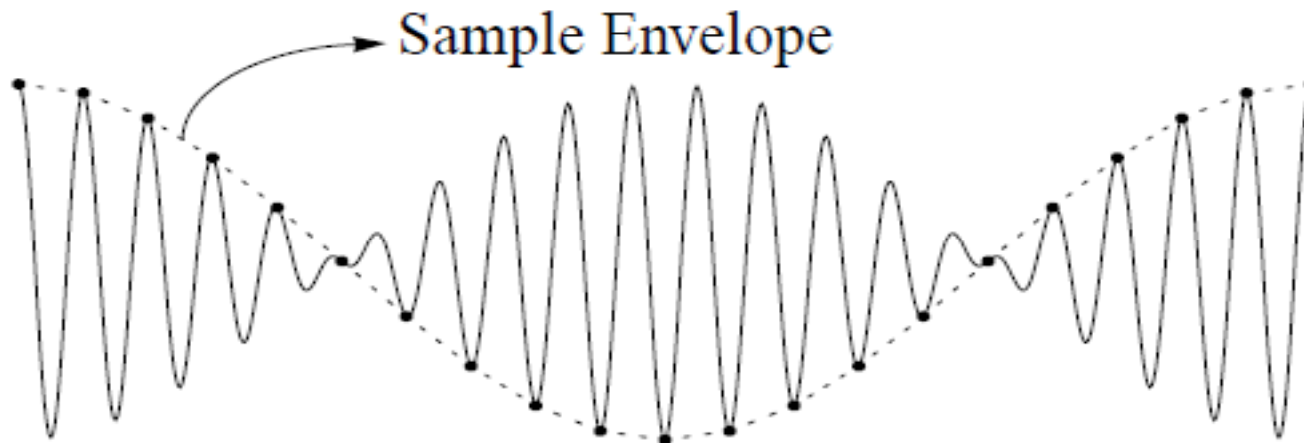- Accelerates transient simulation assuming that the response is a slowly-modulated periodic waveform
 - Once the periodic waveform (i.e. the carrier) is found, only the small changes between the cycles are computed
 - e.g. for simulating initial transients of phase-locked loops



SPICE Basics


- SPICE is basically a nonlinear ODE solver, which formulates an arbitrary circuit into:

$$\text{KCL: } f(v(t), t) = \underbrace{i(v(t))}_{\substack{\text{nonlinear} \\ \text{conductors}}} + \underbrace{\frac{dq(v(t))}{dt}}_{\substack{\text{nonlinear} \\ \text{capacitors}}} + \underbrace{u(t)}_{\substack{\text{current} \\ \text{sources}}} = 0$$

- One reason for SPICE's success was its reliable equation formulation algorithm
 - called modified nodal analysis (MNA)

SPICE Basics (2)

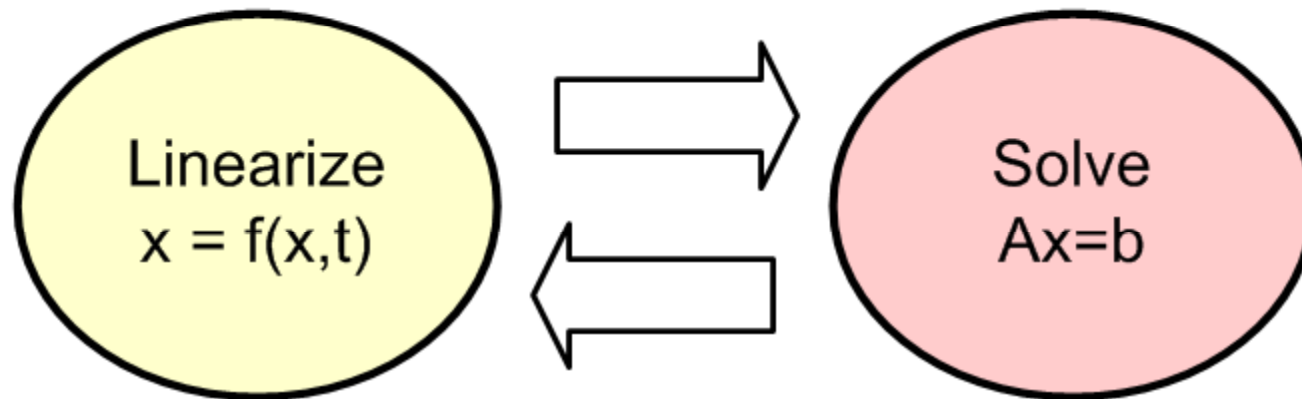- Once the equation is formed, its solution is found by iterating between linearization and solving
 - Linearize the nonlinear ODE around its temporary solution
 - Solve the linear ODE
 - Repeat until the solution converges



SPICE Analysis Modes: DC, AC

- SPICE offers two kinds of steady-state analysis
- DC: finds the DC steady-state response of a circuit
 - Assuming the circuit reaches a DC state at $t=\infty$, solve:
$$f(v(t = \infty), t = \infty) = i(v_{DC}) + u_{DC} = 0$$
 - Solving this eq is actually the most difficult task in SPICE!
 - Note: it finds "a" solution but not all the solutions...
- AC: calculates the steady-state response to a small-signal, sinusoidal perturbation
 - Linearizes the system and use phasor analysis to compute the transfer functions
 - Extremely efficient computation – the fastest in SPICE!




Characterization with DC/AC Analyses

- Which blocks can you verify/characterize with DC/AC?
 - Your choices: filter, LNA, LO, mixer, PA, ...
- The ones with linear, time-invariant (LTI) behaviors
 - Filters (LPF, BPF), LNA, and PA fall into this category
 - A frequency-domain transfer function completely describes their functional behavior (filtering, narrow-band amplification)
- But what about others?
 - Mixers and oscillators – are they just nonlinear?

RF Characteristics II: Linear Time-Varying

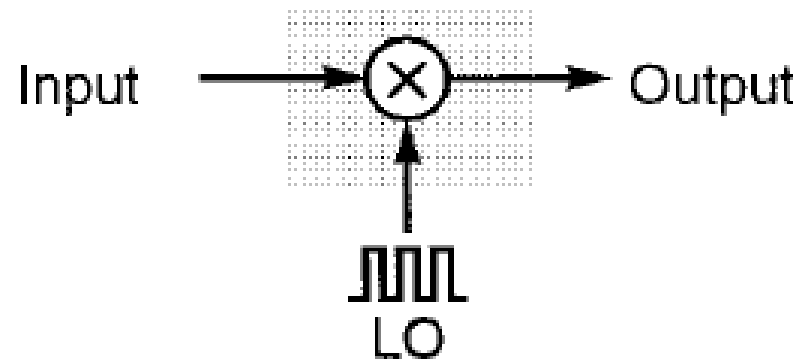- Mixers, just like other RF circuits, are designed to be as linear as possible from its input to output while minimizing distortion/nonlinearities
- Mixer circuit itself exhibits strong nonlinearity and typically driven by a large-signal LO clock:




RF Characteristics II: Linear Time-Varying

- However, the LO clock does not bear any information
 - It is more like part of the circuit (i.e. the circuit wouldn't function correctly – frequency translation – without it)

- Then mixer+clock can be perceived as a LPTV system:

$$v_{in}(t) = m(t) \cdot \cos(\omega_c t)$$

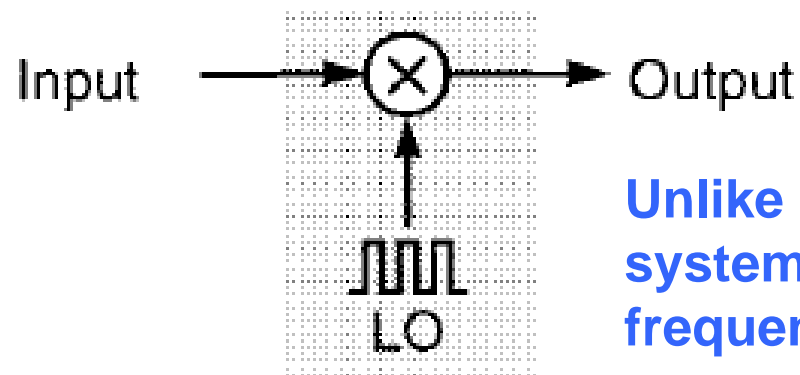
$$v_{out}(t) = LPF\{\cos(\omega_{LO}t) \cdot v_{in}(t)\} = m(t) \cdot \cos((\omega_c - \omega_{LO})t)$$



Unlike LTI systems, LPTV systems can translate frequencies!

RF Characteristics II: Linear Time-Varying

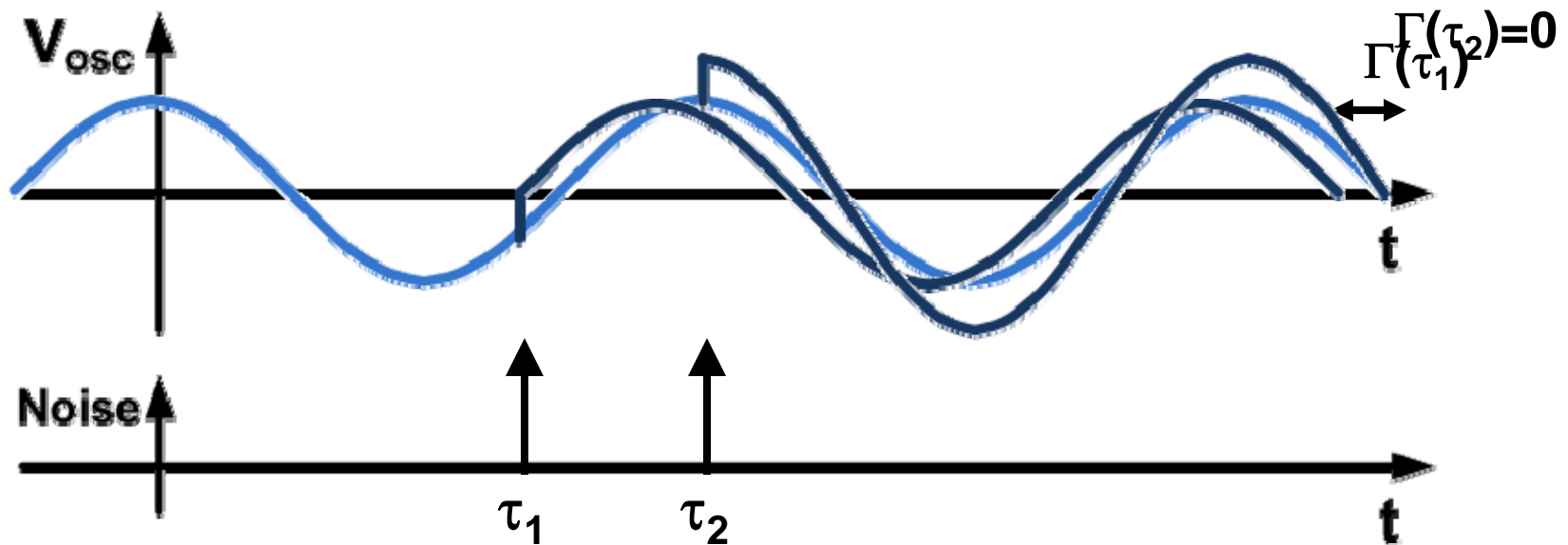- Oscillators are time-varying systems since:
 - Its steady-state is a time-varying waveform (periodic)
 - Its response to external noises varies with time



* A. Hajimiri and T. H. Lee, "A General Theory of Phase Noise in Electrical Oscillators," IEEE JSSC, Feb. 1998.

Periodic Steady-State (PSS) Analysis

- Finds a steady-state response of a periodic circuit
 - The circuit may be driven by periodic, large-signal excitations
 - The resulting response is a large-signal one, but must be periodic
 - e.g. output of a mixer with DC input, oscillator output clock
- PSS is an extension of DC analysis to periodic circuits
 - Finds the final waveforms after infinite period of time
 - Useful for:
 - Measuring the steady-state frequency of a VCO
 - Measuring the steady-state phase-offset of a locked PLL
 - However, as with DC, PSS is the most difficult analysis
 - Can have convergence issues if care is not taken



PSS Method 1: Harmonic Balance

- Harmonic balance directly finds the PSS solution in frequency domain
 - Assuming that the PSS solution is T-periodic, it can be expressed in a Fourier series:

$$f(v(t), t) \rightarrow \sum_{k=-\infty}^{\infty} F_k(V) \cdot e^{j2\pi kt/T} = 0$$

$$F_k(V) = I_k(V) + \frac{j2\pi k}{T} Q_k(V) + U_k = 0$$


- Solve a system of equations for $k=0, \pm 1, \dots, \pm K$
- Accuracy/speed depends on the choice of K

PSS Method 2: Shooting Newton

- Shooting solves a boundary value problem to find a T-periodic solution:

$$v(T) - v(0) = 0$$

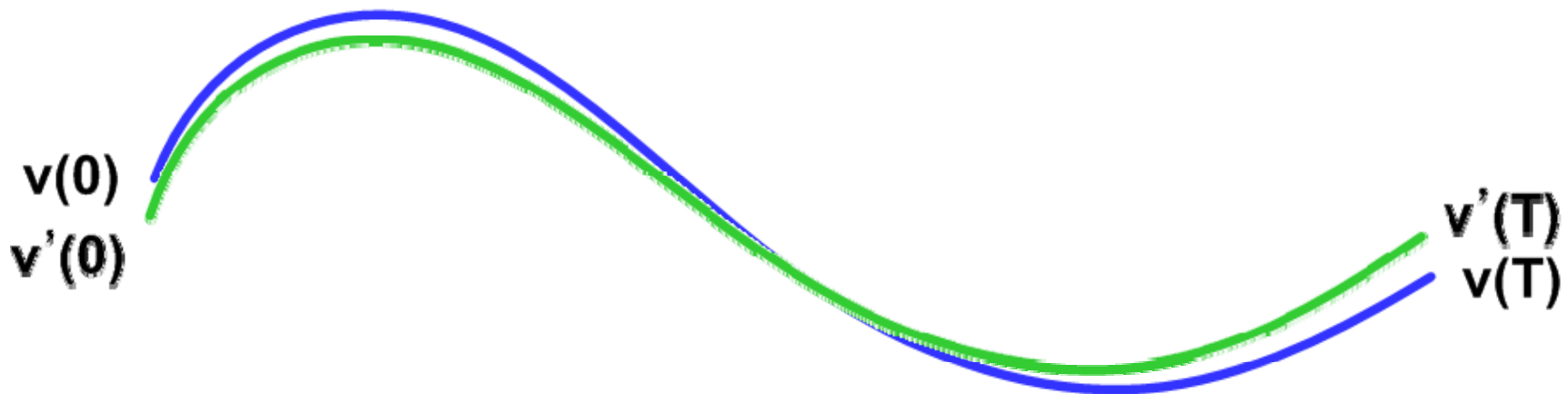- In other words, find a circuit state $v(0)$ that makes the state after T identical to $v(0)$
- Requires to calculate the sensitivity of $v(T)$ w.r.t. $v(0)$



Harmonic Balance vs. Shooting

- Harmonic Balance (e.g. Agilent ADS)
 - A frequency-domain method
 - Easily handles frequency-domain models (e.g. S-parameters)
 - Its accuracy is limited by the number of harmonics used – not suitable for simulating strongly nonlinear responses
- Shooting (e.g. Cadence SpectreRF)
 - A time-domain method
 - Need not choose the number of harmonics – however, the time step should be fine enough to simulate the max frequency AC response
 - Can't handle frequency-domain models directly

SpectreRF Syntax for PSS

- To find its full description (in fact, it works on any Spectre commands):

```
unix> spectre -h pss
```

- For example:

```
PSS_Shooting pss fund=1G tstab=100n  
+ errpreset=conservative
```

```
PSS_HB pss fund=1G harms=10 harmonicbalance=yes  
+ errpreset=conservative
```

- Tip: use 'simulator lang=spice' and 'simulator lang=spectre' to switch the languages within a deck




Dealing with PSS Convergence Issues


- Before SPICE became mature enough, circuit designers used to encounter “DC convergence failure” error a lot
 - These days, you may get the equivalent messages with PSS
- However, convergence problems are usually the designers’ faults – the circuit isn’t really periodic!
 - Remember, the *entire* circuit must be *perfectly periodic* at the prescribed fundamental frequency
 - Common pitfalls (e.g. for a PLL)
 - Some part of the circuit has longer periods (e.g. divider, prbs)
 - The PD has hysteresis or deadzone near the locked point and the PLL doesn’t lock to a single point

Output of PSS Analysis

- A unit-period time-domain waveform

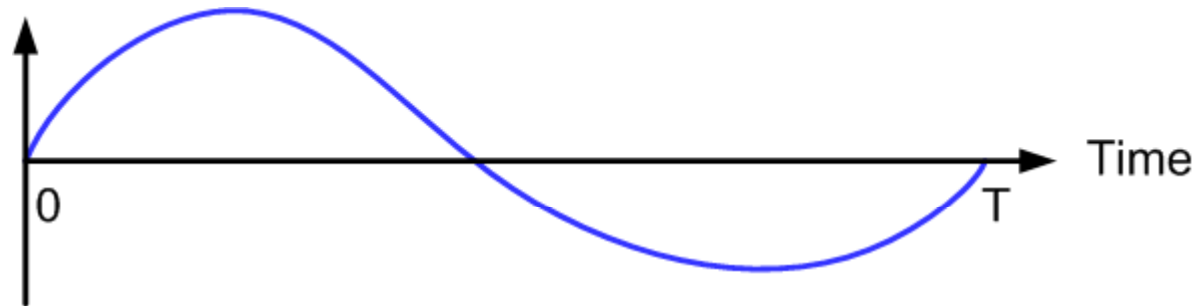

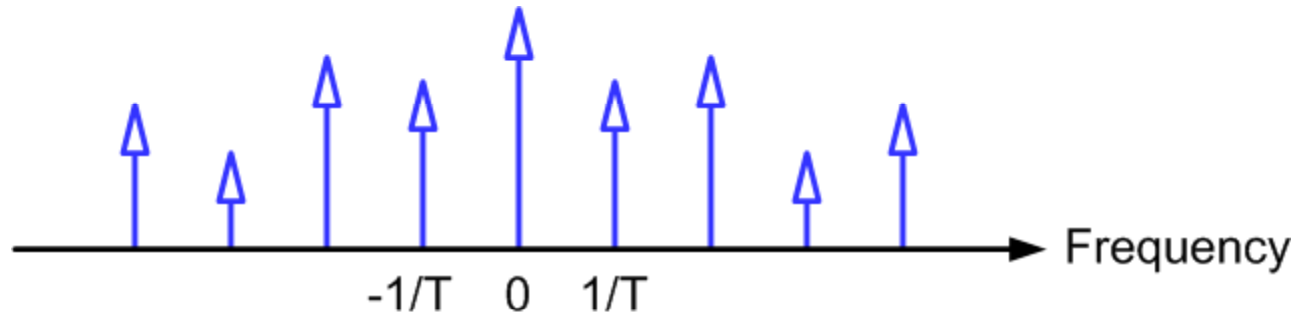- A collection of Fourier series component



Quasi Periodic Steady State (QPSS)



- A circuit driven by two large-signal excitations may have two fundamental tones:

$$x(t) = \sum_{k=-\infty}^{\infty} \sum_{l=-\infty}^{\infty} X_{kl} \cdot e^{j2\pi(kf_1+lf_2)t}$$

- Its steady-state response (i.e., a periodically modulated periodic signal) can be found either by harmonic balance or by shooting


PSS vs. DISTO

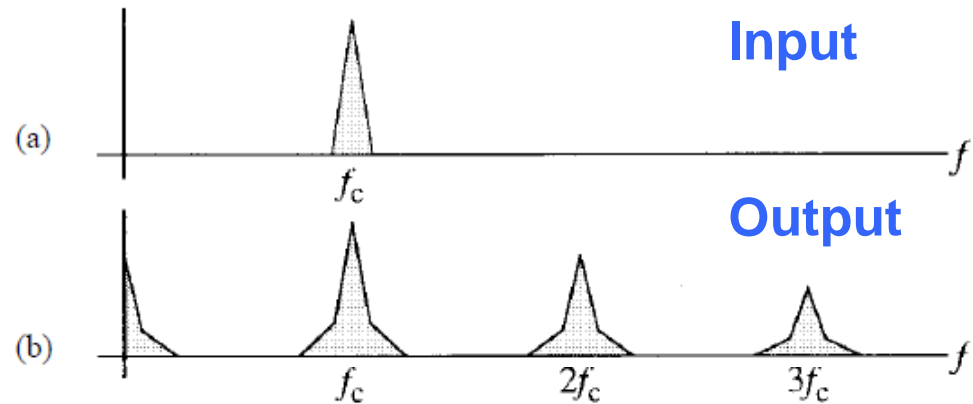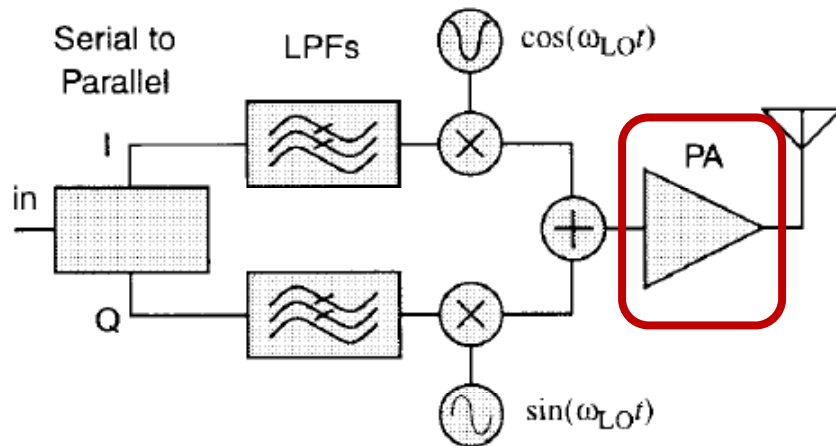- Consider a PA driven by a large, periodic signal at f_c
 - The PSS output waveform may have spectrums at $k \cdot f_c$ due to the PA's nonlinearities (i.e. harmonic distortion)
- Comparison with SPICE's distortion analysis (DISTO)
 - DISTO computes the harmonic distortions due to "small-signal" inputs while PSS does for "large-signal" inputs




RF Analysis Modes: Periodic AC (PAC)

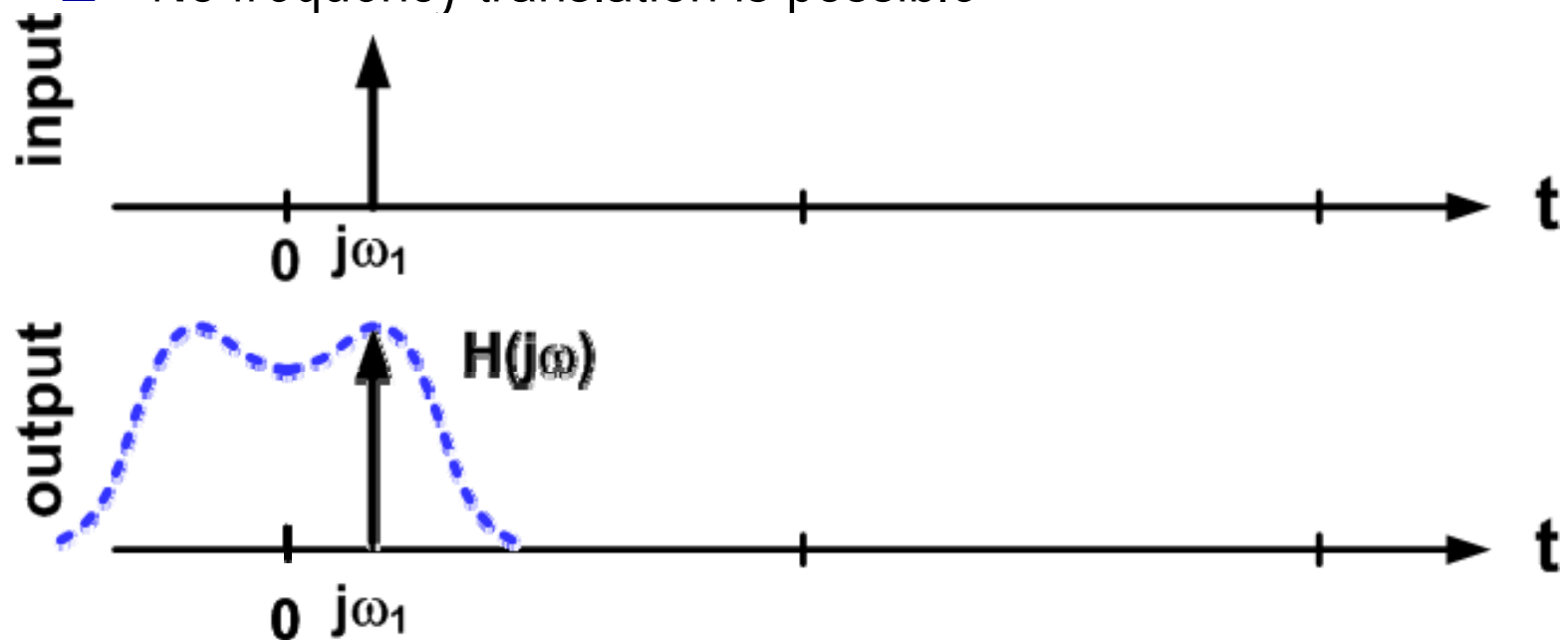- Computes the steady-state response to a small-signal sinusoid excitation of a circuit about its PSS
- For LTI systems, AC analysis returns $X(j\omega_1) \cdot H(j\omega_1)$
 - No frequency translation is possible



RF Analysis Modes: Periodic AC (PAC)

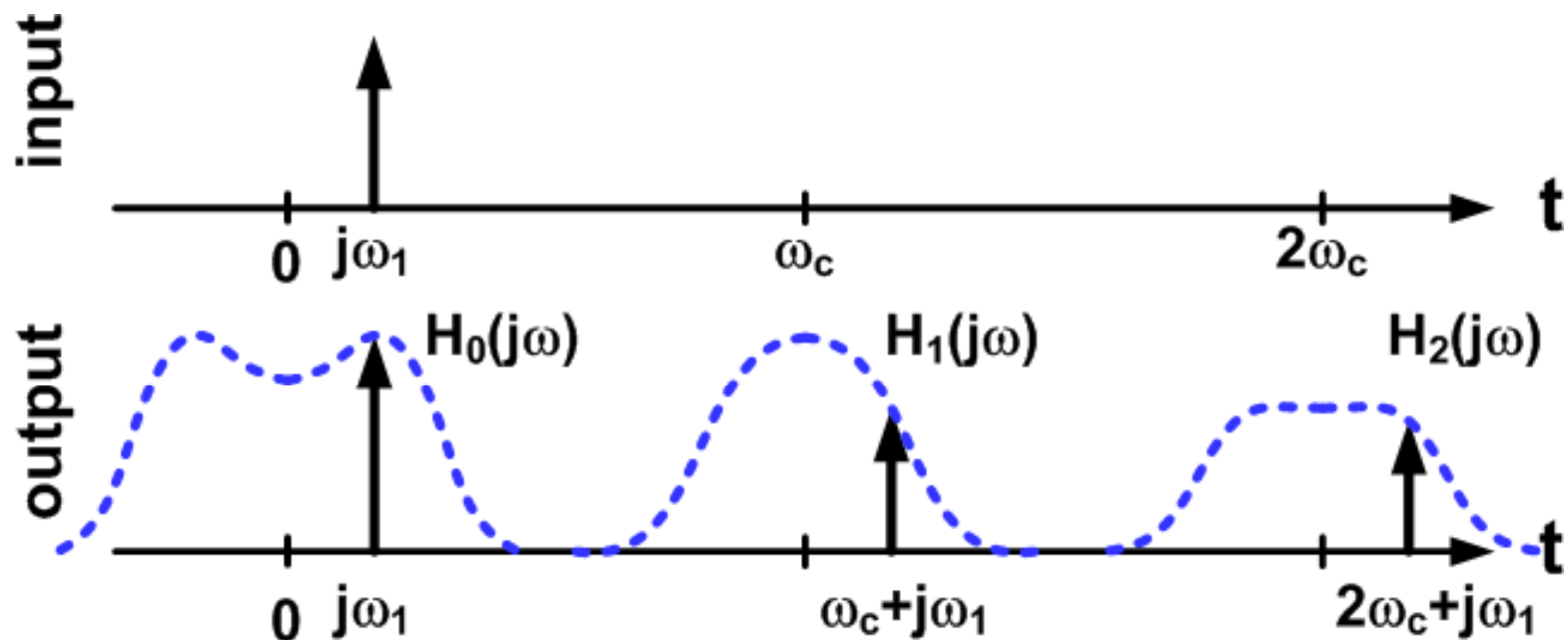- For LPTV systems, a sinusoid input at ω_1 can excite the output at multiple frequencies of $\omega_1 + m \cdot \omega_c$
 - $H_m(\omega_c)$ is the transfer function mapping to the m-th sideband
 - In PAC, you specify which $H_m(\omega_c)$ to be reported



Linear Time-Varying System Basics

- Time-varying impulse response $h(t, \tau)$:

$$y(t) = \int_{-\infty}^t h(t, \tau) \cdot x(\tau) d\tau$$

- Time-varying transfer function $H(j\omega; t)$:

$$Y(j\omega)e^{j\omega t} = H(j\omega; t) \cdot X(j\omega)e^{j\omega t}$$

- Relationship between $h(t, \tau)$ and $H(j\omega; t)$:

$$H(j\omega; t) = \int_{-\infty}^{\infty} h(t, \tau) \cdot \exp(-j\omega(t - \tau)) d\tau$$

- For LPTV system $H(j\omega; t) = H(j\omega; t+T)$:


$$H(j\omega; t) = \sum_{m=-\infty}^{\infty} H_m(j\omega) \cdot e^{jm\omega t}$$



* L. Zadeh, "Frequency Analysis of Variable Networks," Proc. I.R.E. Mar. 1950.

A Mixer Example

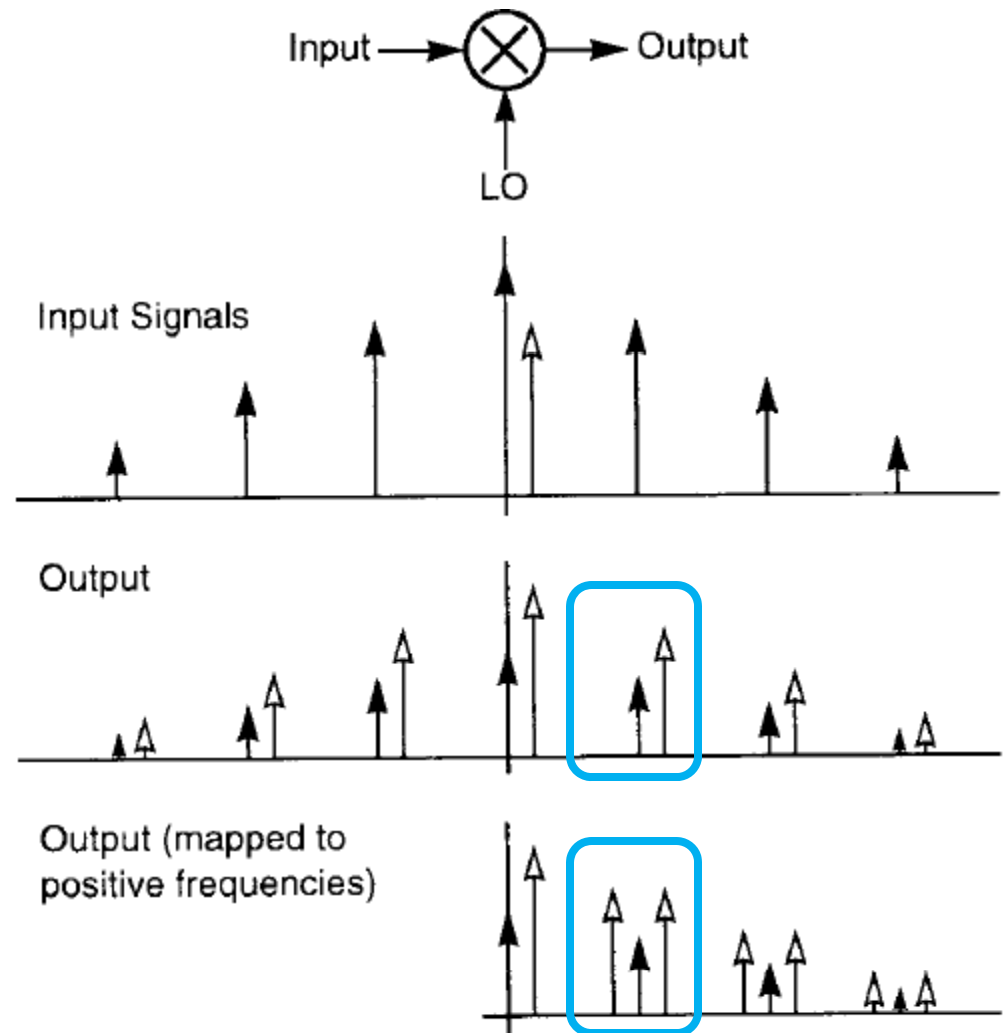- Consider a up-conversion mixer
- TF to which sideband would you be interested in?
- That TF describes the conversion gain, bandwidth, etc.




PM vs. AM

- Based on narrowband angle modulation approximation, one can derive whether the input perturbation modulates the phase or the amplitude of the carrier:

$$PM = \frac{j}{A_c} \cdot (H_{-1}e^{j\phi_c} - H_1e^{-j\phi_c})$$
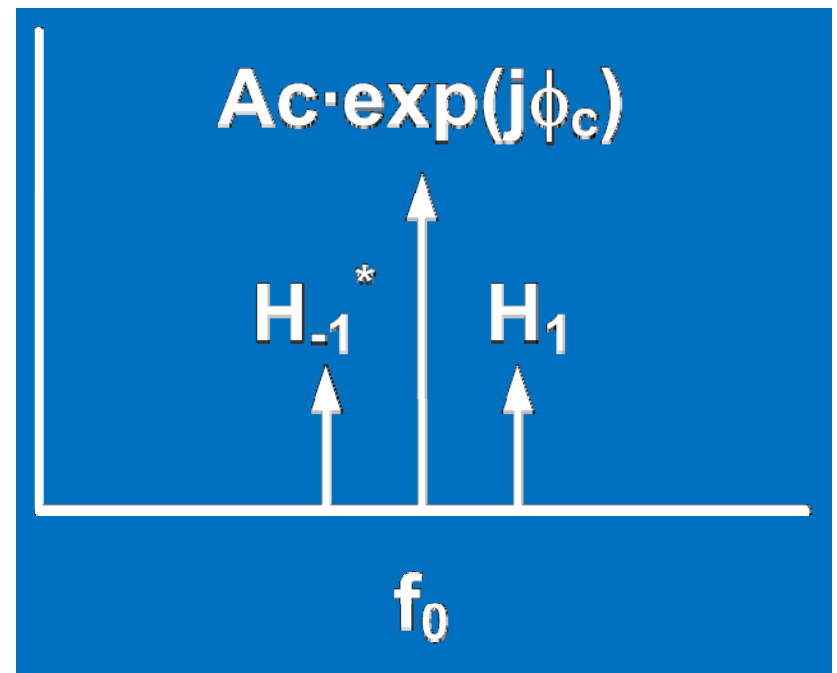
$$AM = \frac{1}{A_c} \cdot (H_{-1}e^{j\phi_c} + H_1e^{-j\phi_c})$$



SpectreRF Syntax for PAC

- First, you need a PAC stimulus:

```
Vin ( in gnd ) vsource dc=0 pacmag=1 pacphase=0
```


- Then the analysis statement:

```
sim_PAC pac start=1k stop=.1G dec=10 maxsideband=10  
freqaxis=in
```

- **sidebands**: array of relevant sidebands for the analysis.
- **maxsideband**: equivalent to sidebands = [-maxsideband ... 0 ... +maxsideband
- **freqaxis**: specifies whether the results should be output versus the input frequency (in), the output frequency (out), or the absolute value of the output frequency (absout)


SPICE Analysis Modes: NOISE

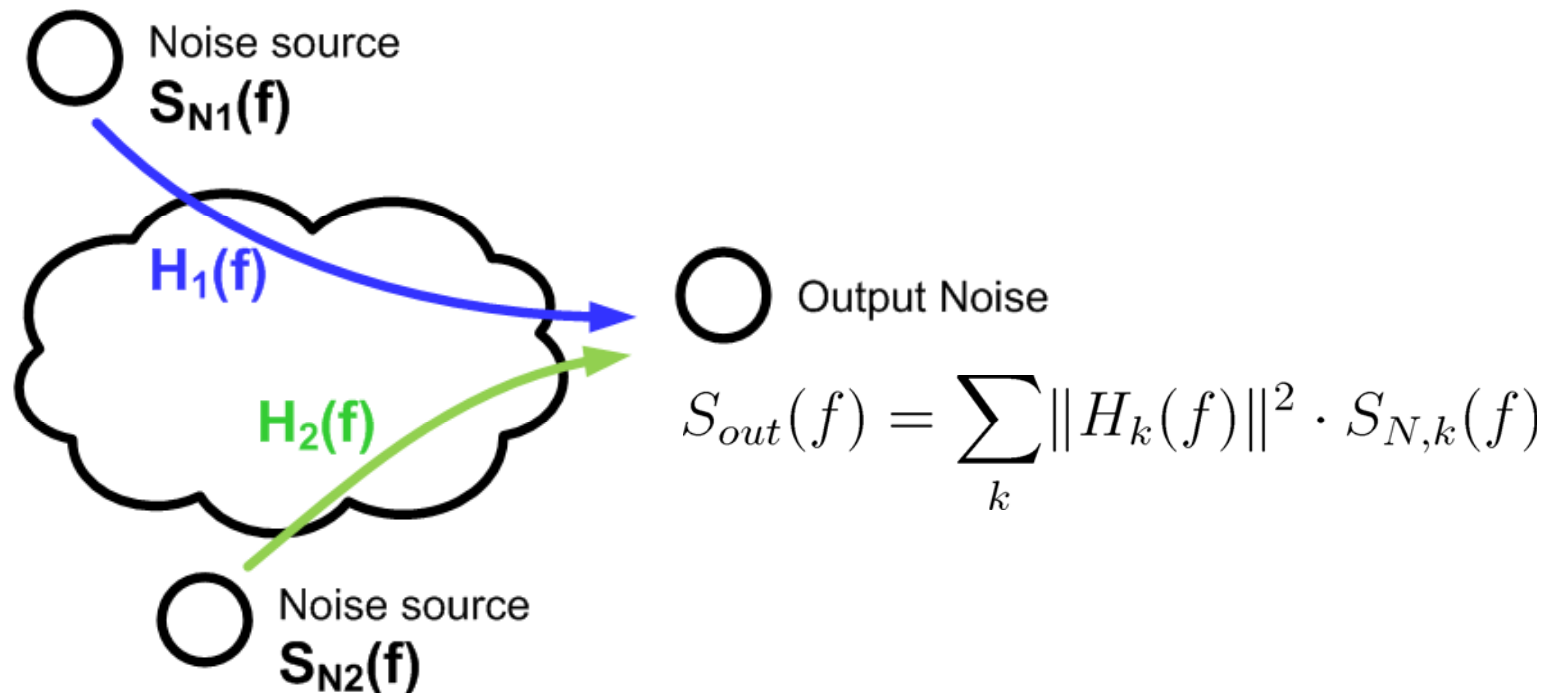- Computes output noise PSD contributed by multiple noise sources
- Based on the TFs obtained by small-signal AC analysis



RF Analysis Modes: Periodic Noise

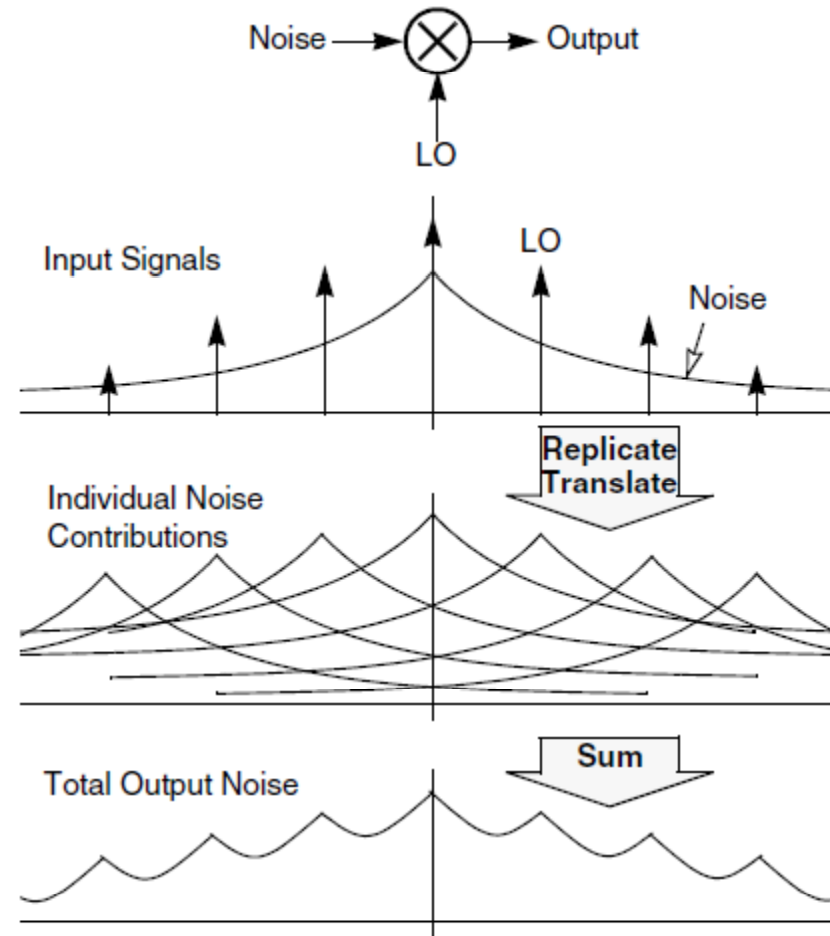- Since in LPTV systems a single-frequency input can give rise to outputs at multiple frequencies, noise folding may occur
- The resulting noise is in general cyclostationary



SpectreRF Syntax for PNOISE

- Reporting time-averaged PSD of the output noise

```
sim_PNOISE ( outp outn ) pnoise
+         start=1 stop=0.5G dec=20
+         maxsideband=50 noisetype=sources
```

- **maxsideband** specifies the # of sidebands in the noise TF to be considered

- Reporting the output noise PSD at specific time (hence, cyclostationary noise):

```
sim_PNOISE ( outp outn ) pnoise
+         start=1 stop=0.5G dec=20
+         maxsideband=50 noisetype=timedomain
+         noisetimepoints=[0.5n] numberofpoints=1
```