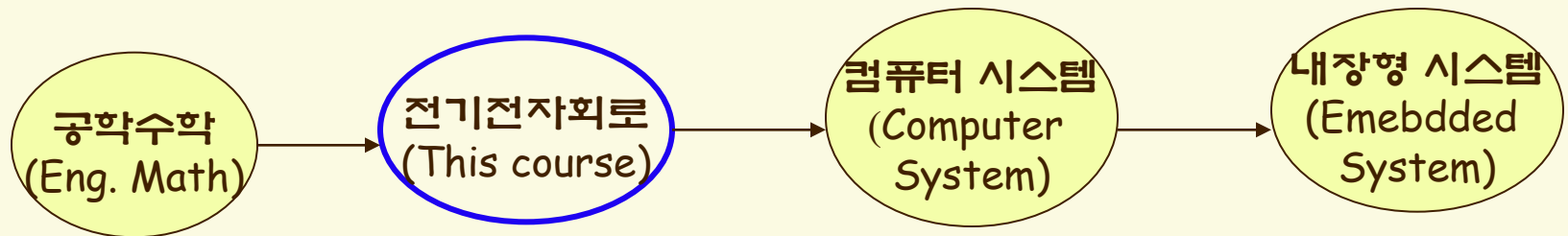


# Electrical and Electronics Circuits (2010)

- 📄 Lecturer: Prof. Soonhoi Ha (301-408, x8382)  
sha@snu.ac.kr, <http://peace.snu.ac.kr/sha>
- 📄 Textbook: Foundations of Analog and Digital Electronic Circuits
- 📄 Course homepage: <http://peace.snu.ac.kr/courses> & ETL
- 📄 Grades: 3 exams 30, 30, 30% homework + attendance: 10%

# Tips for the course

- Do not leave the class until you understand the contents.
- Exercise is the best way to learn the key concepts.
- Better if you can prepare and review the class
- Why do you need this course
  - Pre-requisite for advanced system courses
  - Broad knowledge on IT-related issues



# Chap. 1 Circuit Abstraction

Lumped Circuit Abstraction

Practical Two-Terminal Elements

Electric power

i-v characteristics

Resistors: Ohm's law

# Abstraction

Physics laws or "abstractions"

- Maxwell's
- Ohm's

$$V = R I$$

abstraction for  
tables of data

Lumped circuit abstraction



Simple amplifier abstraction




Operational  
amplifier abstraction  
abstraction



Digital abstraction



Combinational logic

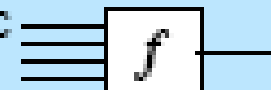



Filters




Clocked digital abstraction



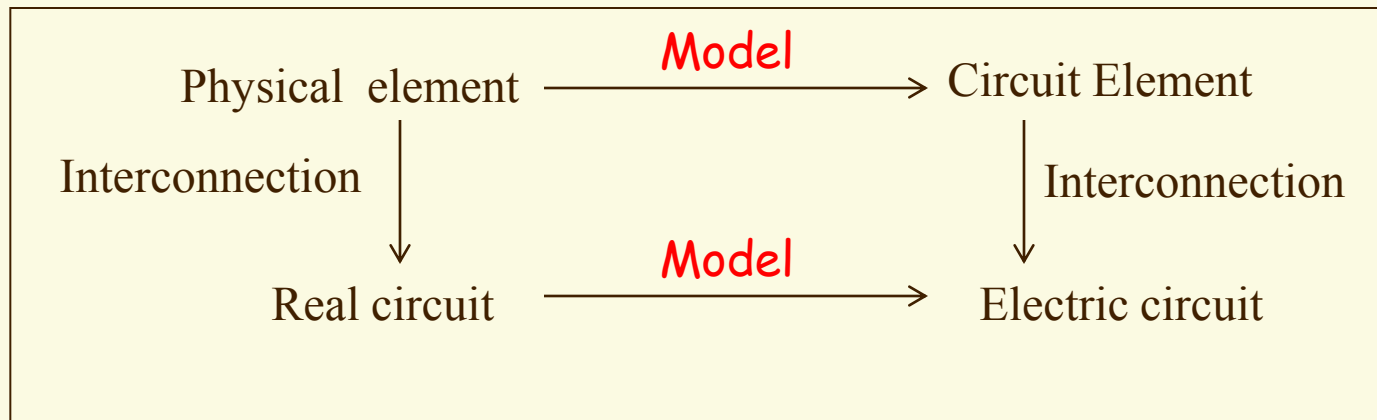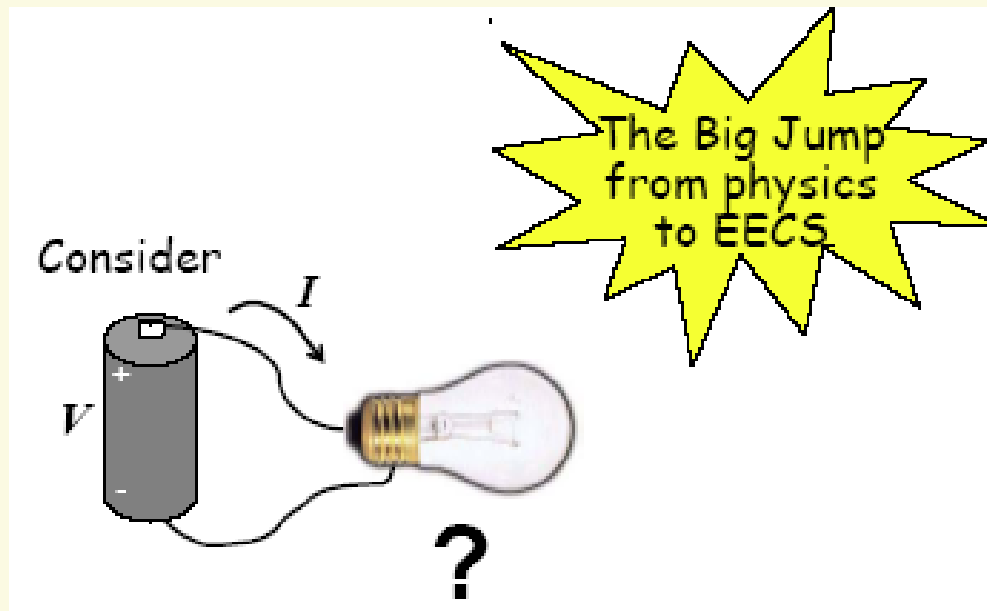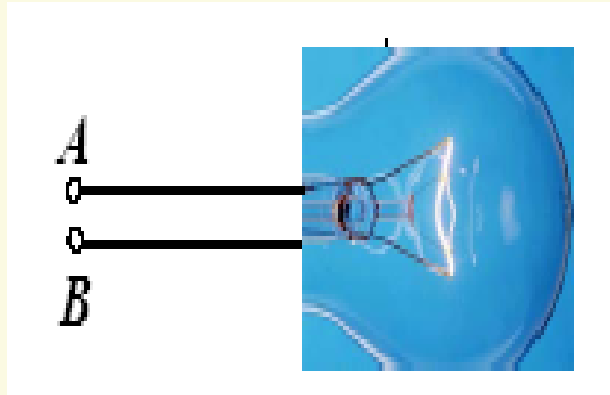
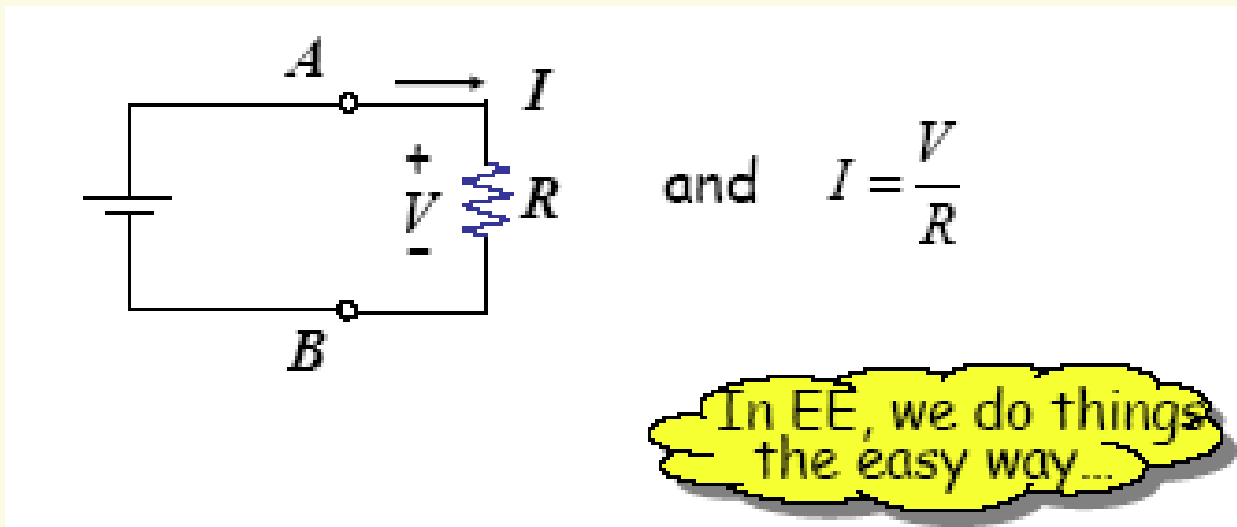
# Lumped Circuit Abstraction




# The Easy Way ...



 R is the “lumped circuit abstraction” of the bulb.



# Lumped Circuit Abstraction Assumption

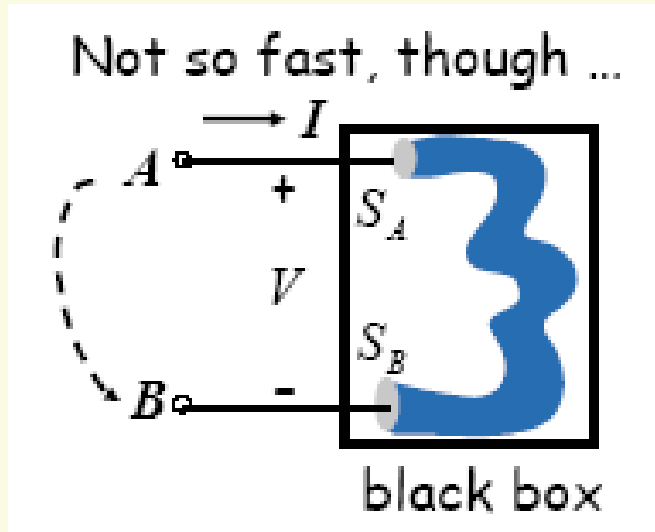

- 📄  $V$  and  $I$  must be defined for the element
- 📄 Element behavior is completely captured by its I-V relationship.



When you measure the current of a circuit, the measured value turns out to be 10 times higher than the analyzed one. What happens?




# Charge and Current

 Charge  $Q$

 Current  $I = dq/dt$  ( $C/sec = A$ )

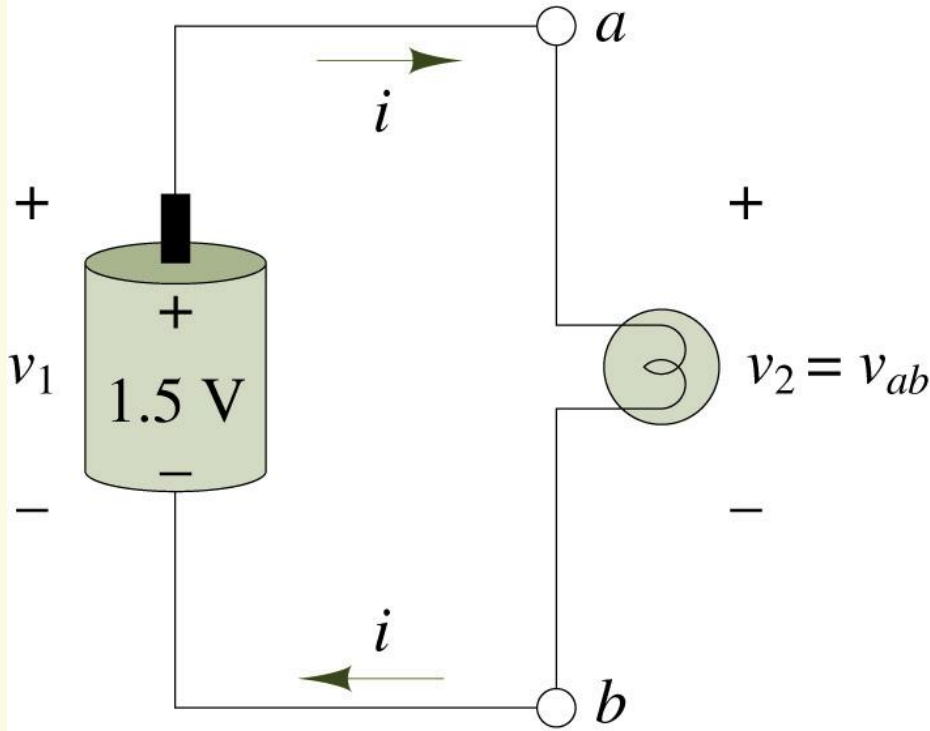
# Voltages around a circuit

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.




 Voltage = Joule/Coulomb

# Direction of Current and Voltage

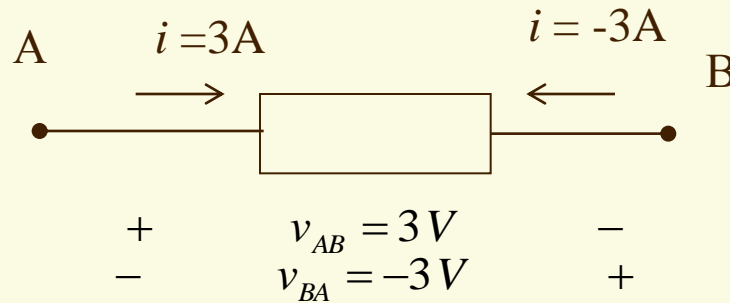

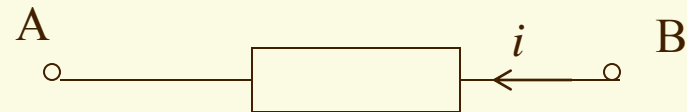
5A Current flows from A to B. What is the value of current  $i$ ?



# Power and Energy

📄 Power = work/time = work/charge \* charge/time  
= voltage \* current

📄  $P = VI$

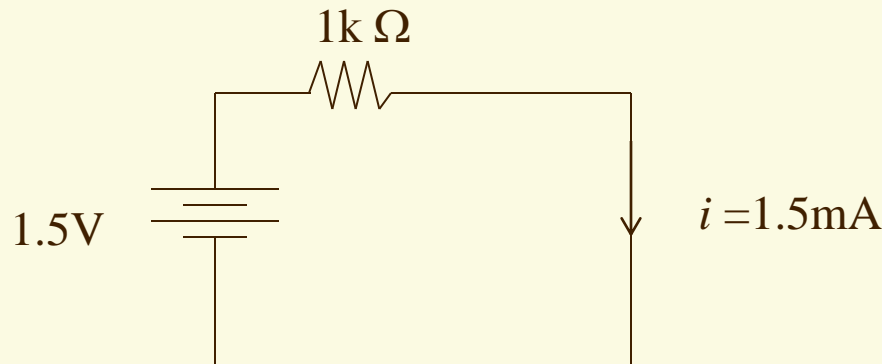


Power consumed by the resistor: 2.25 mW

Power consumed by the battery? -2.25 mW


$$\text{Energy} = \int \text{power } dt$$
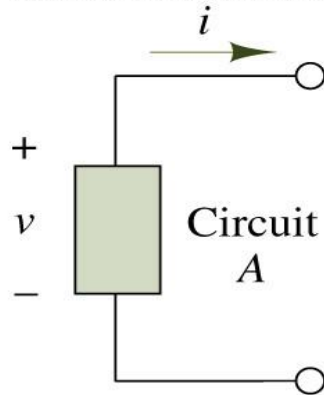
# The passive sign convention

Copyright © The McGraw-Hill Companies, Inc.  
Permission required for reproduction or display.



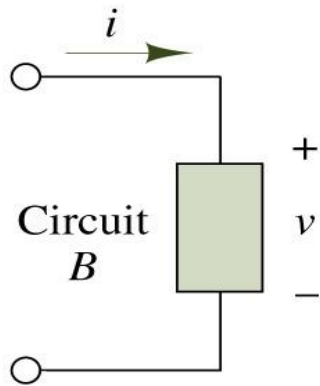
$$\text{Power dissipated} = v(-i) = (-v)i = -vi$$
$$\text{Power generated} = vi$$



$$\text{Power dissipated} = vi$$
$$\text{Power generated} = v(-i) = (-v)i = -vi$$

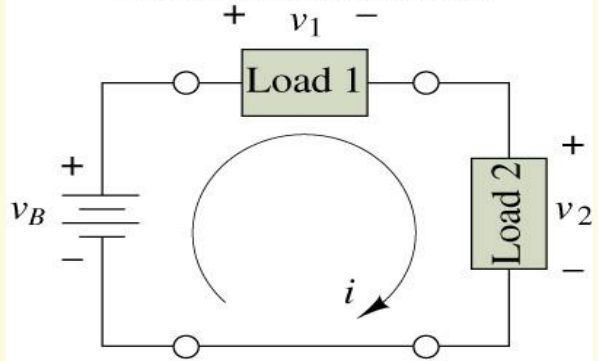
# Find power dissipated by each element

Copyright © The McGraw-Hill Companies, Inc.  
Permission required for reproduction or display.



$$\begin{aligned} v_B &= 12 \text{ V} & v_1 &= 8 \text{ V} \\ i &= 0.1 \text{ A} & v_2 &= 4 \text{ V} \end{aligned}$$

(a)

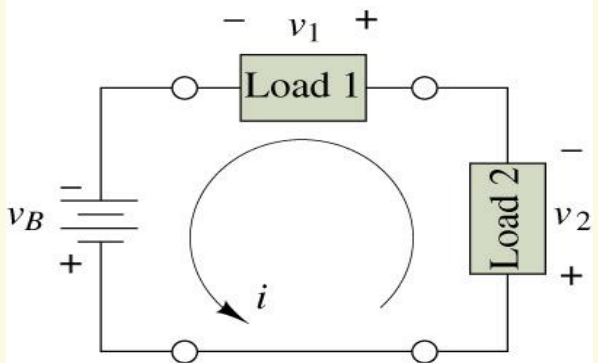


$$\begin{aligned} v_B &= -12 \text{ V} & v_1 &= -8 \text{ V} \\ i &= -0.1 \text{ A} & v_2 &= -4 \text{ V} \end{aligned}$$

(b)

# i – v characteristics

## 📄 Generalized circuit element

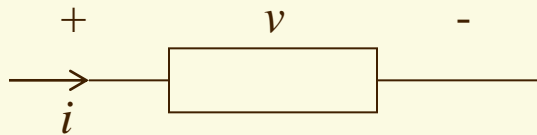

Resistor:  $i = f(v)$ ,  $v = g(i)$


In general,  $F(v,i,t) = 0$

## 📄 i-v characteristics


- Voltage source
- Current source
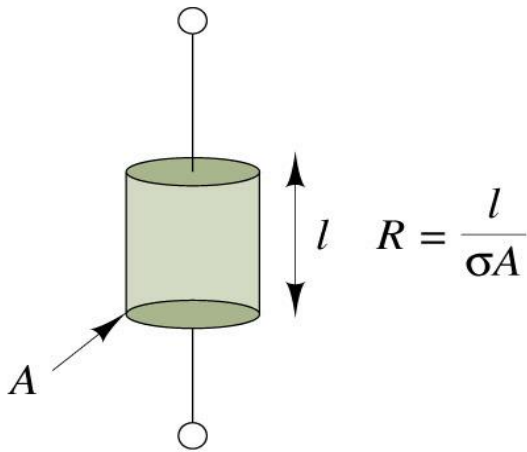
# The resistance element: Ohm's law


Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.



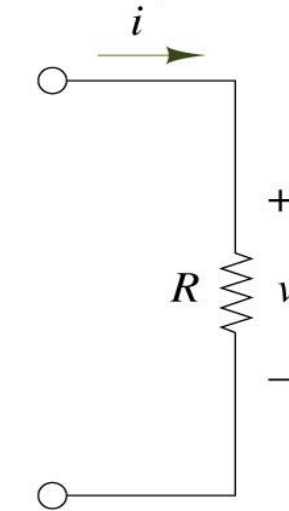Physical resistors with resistance  $R$ . Typical materials are carbon, metal film.



Circuit symbol

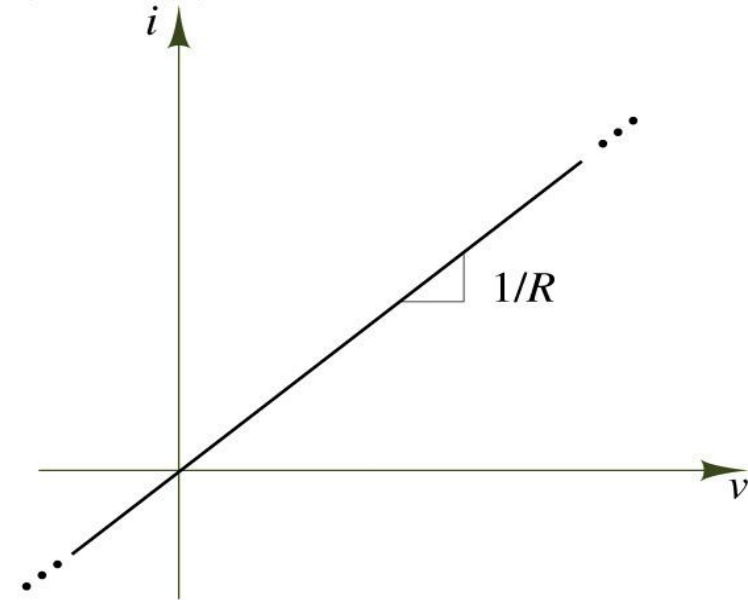


$i$ - $v$  characteristic

Conductance =  $1 / \text{resistance}$

$$P = VI$$




# Diode: non-linear resistor

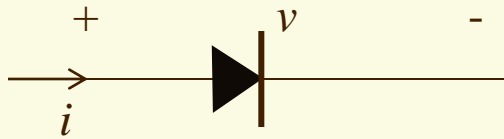


(a) Diode circuit symbol

$$i = I_0 \left( e^{\frac{v}{V_T}} - 1 \right)$$

(b) Characteristic equation

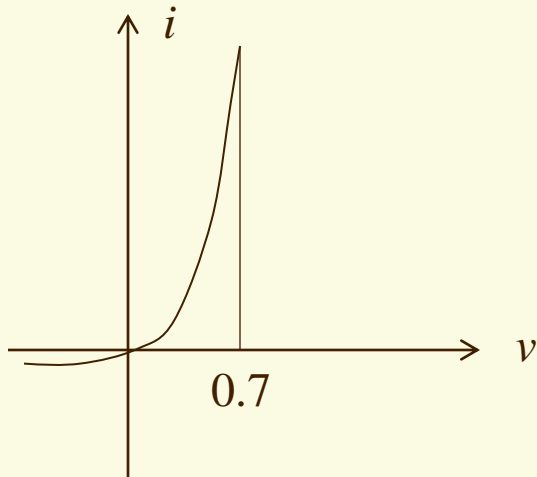


(c) i-v characteristic

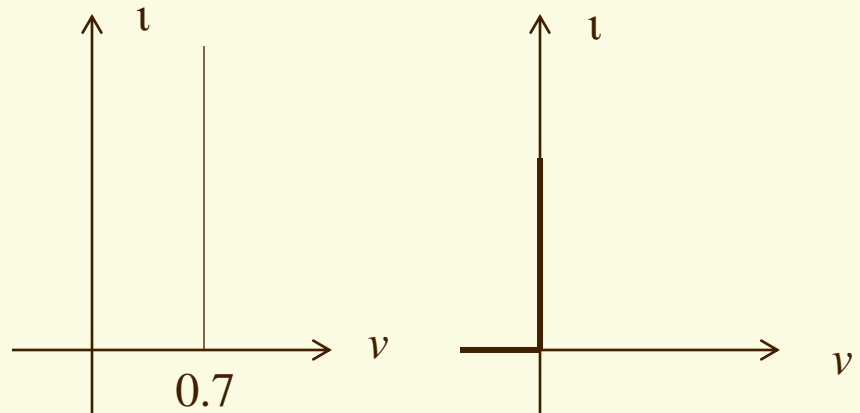

(d) simplified i-v characteristic


# Open and short circuits

 Open circuit

 Short circuit
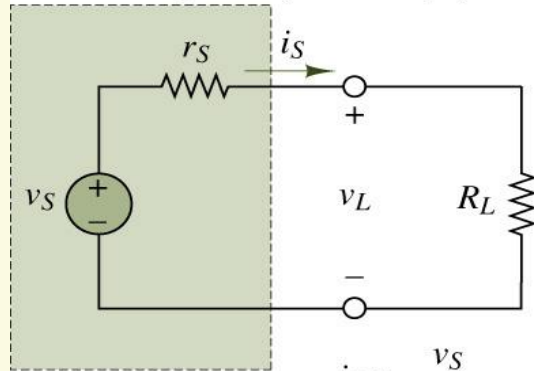
# Practical voltage source


Copyright © The McGraw-Hill Companies, Inc.  
Permission required for reproduction or display.



Practical voltage  
source

$$i_S = \frac{v_S}{r_S + R_L}$$
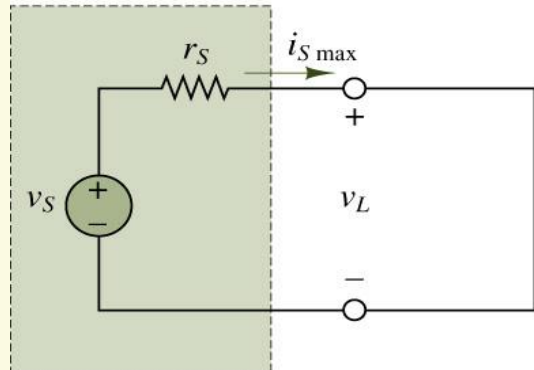
$$\lim_{R_L \rightarrow 0} i_S = \frac{v_S}{r_S}$$




The maximum (short circuit)  
current which can be supplied  
by a practical voltage source is


$$i_{S \max} = \frac{v_S}{r_S}$$
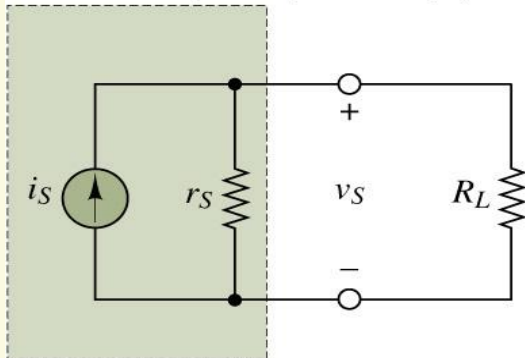
# Practical current source

Copyright © The McGraw-Hill Companies, Inc.  
Permission required for reproduction or display.



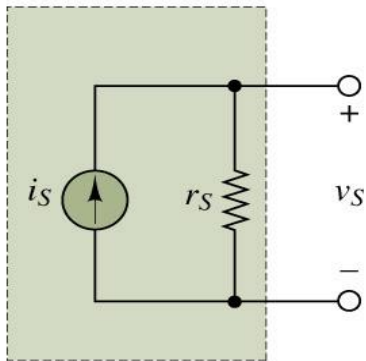A model for practical current sources consists of an ideal source in *parallel* with an internal resistance.




Maximum output voltage for practical current source with open-circuit load:

$$v_{S \max} = i_S r_S$$

# Ohmmeter and measurement of resistance

Figure 2.48

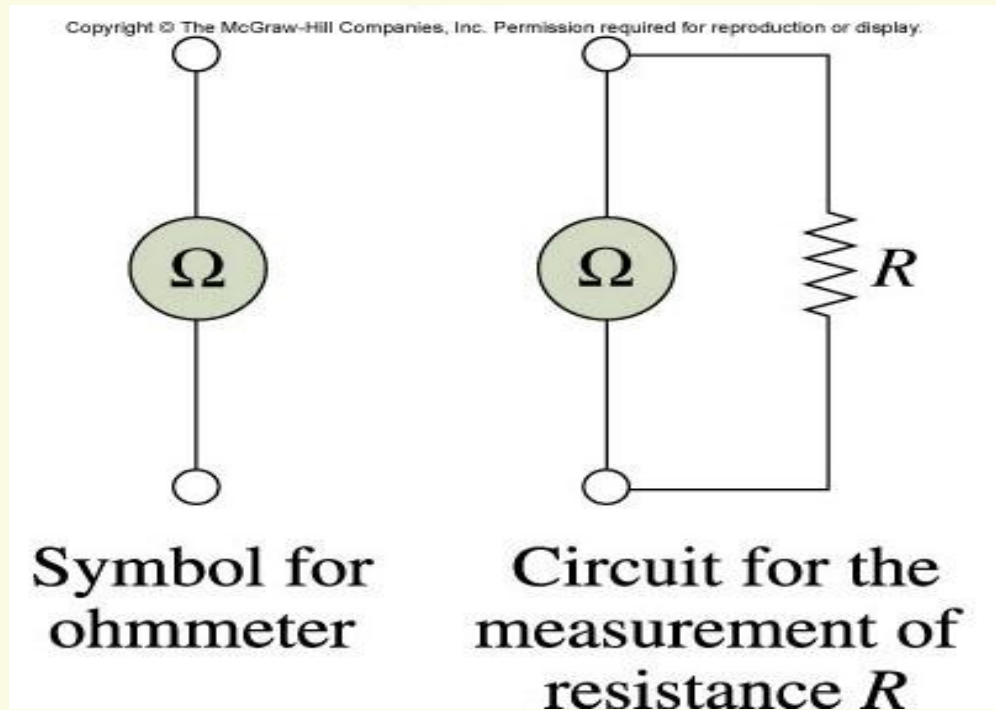


# Measurement of current


Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.



Symbol for ideal ammeter

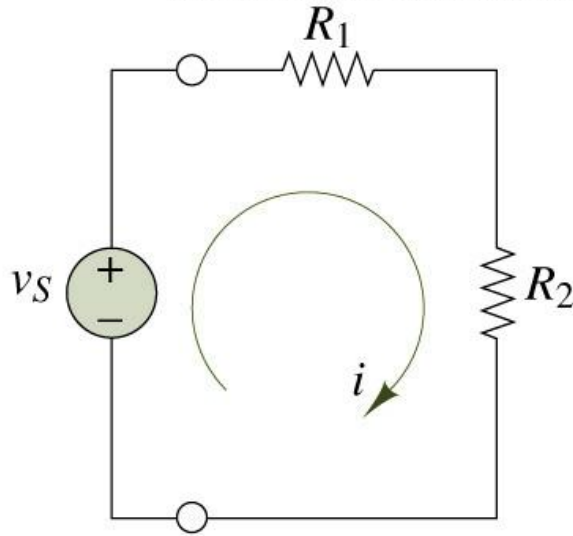


A series circuit

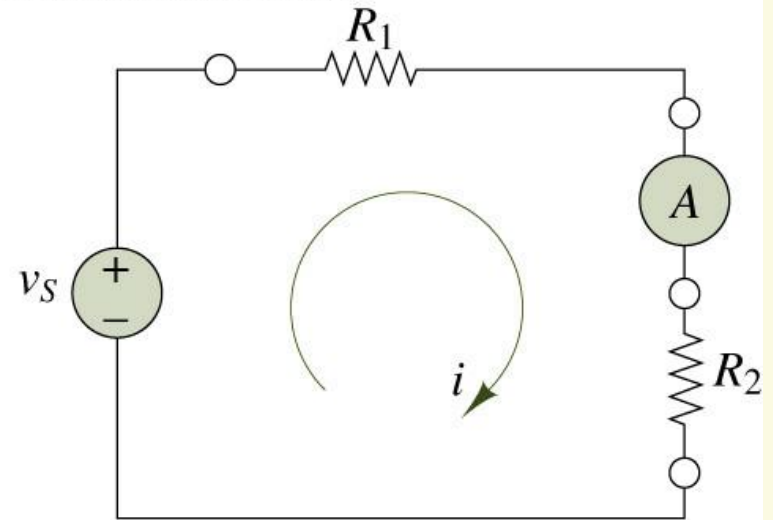

Circuit for the measurement of the current  $i$
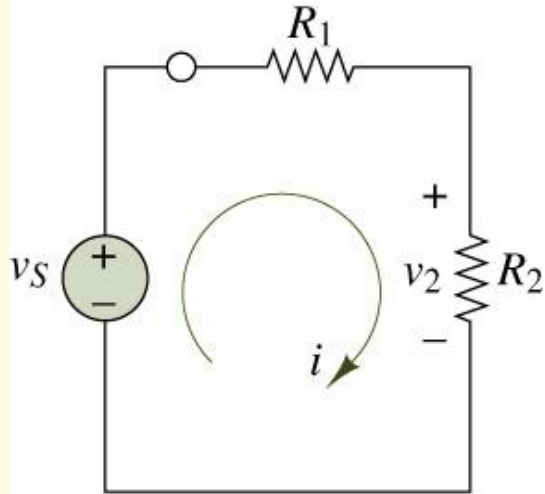
# Measurement of voltage


Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.



A series circuit




Ideal voltmeter

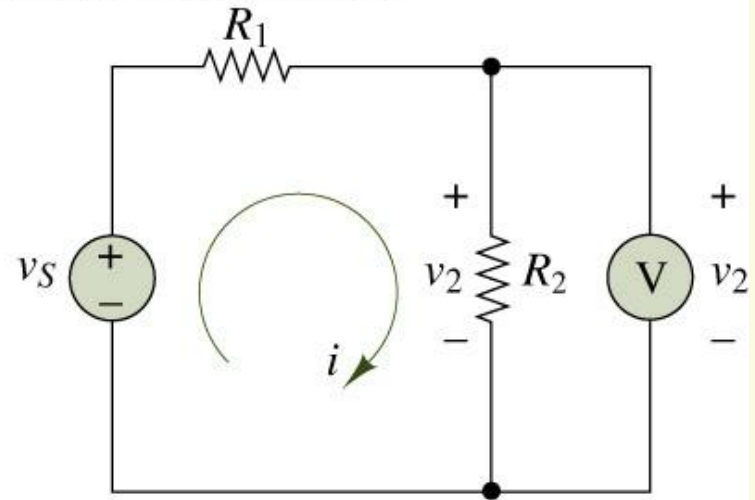

Circuit for the measurement of the voltage  $v_2$
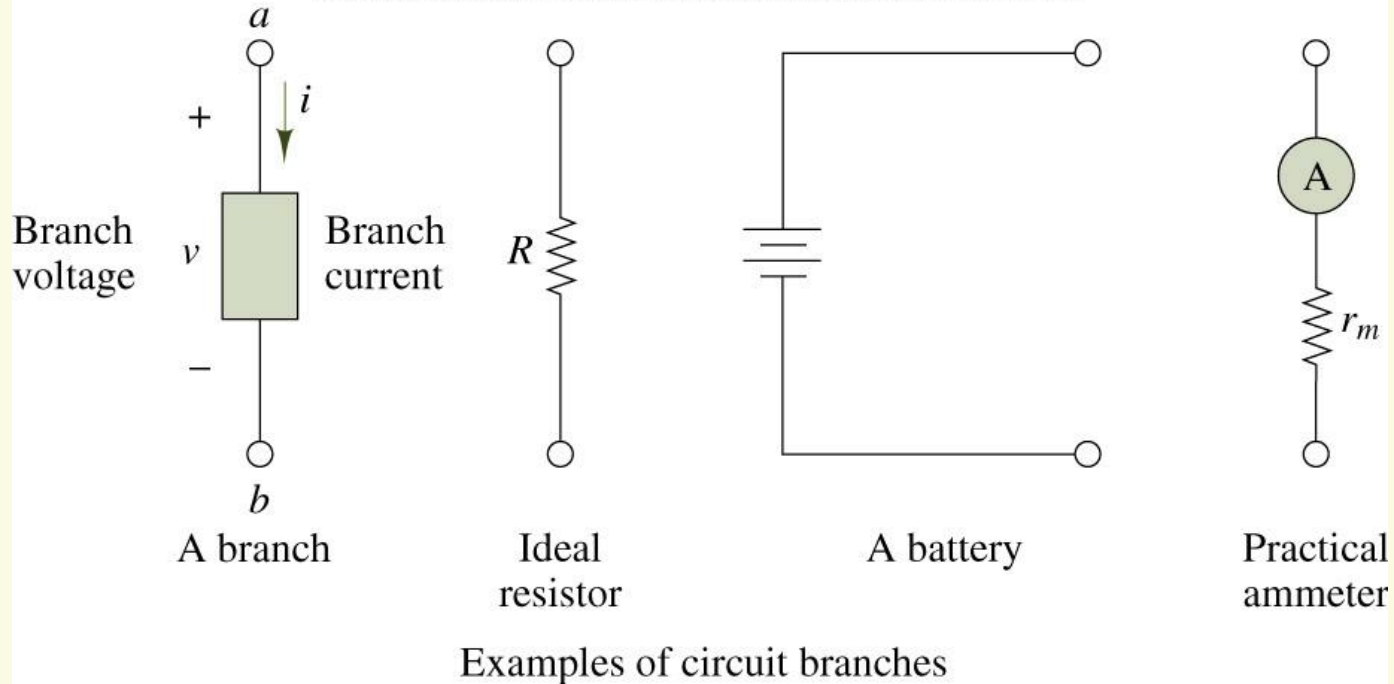
# Definition of a branch





Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.





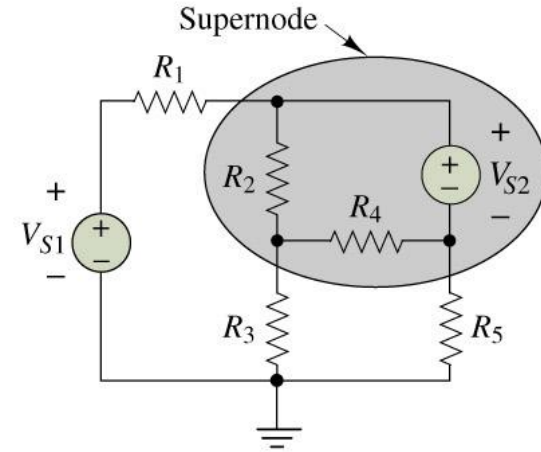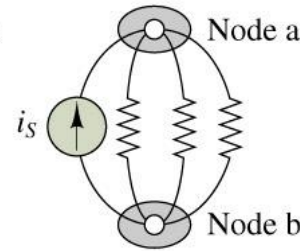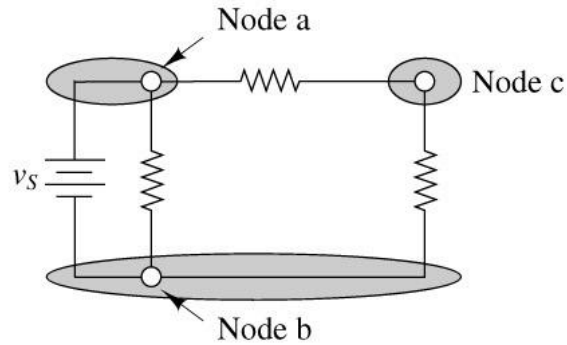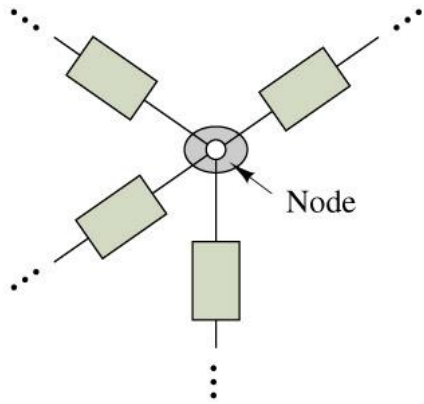
# Definitions of node and supernode

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.




Examples of nodes in practical circuits

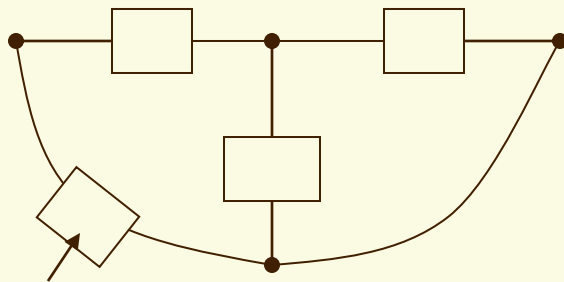

Circuit element


(a)

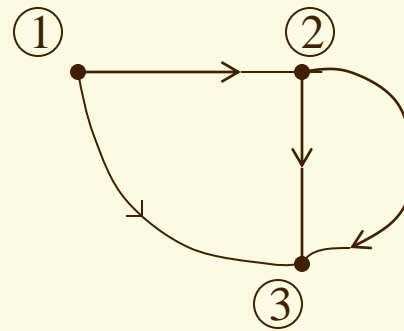


(b)
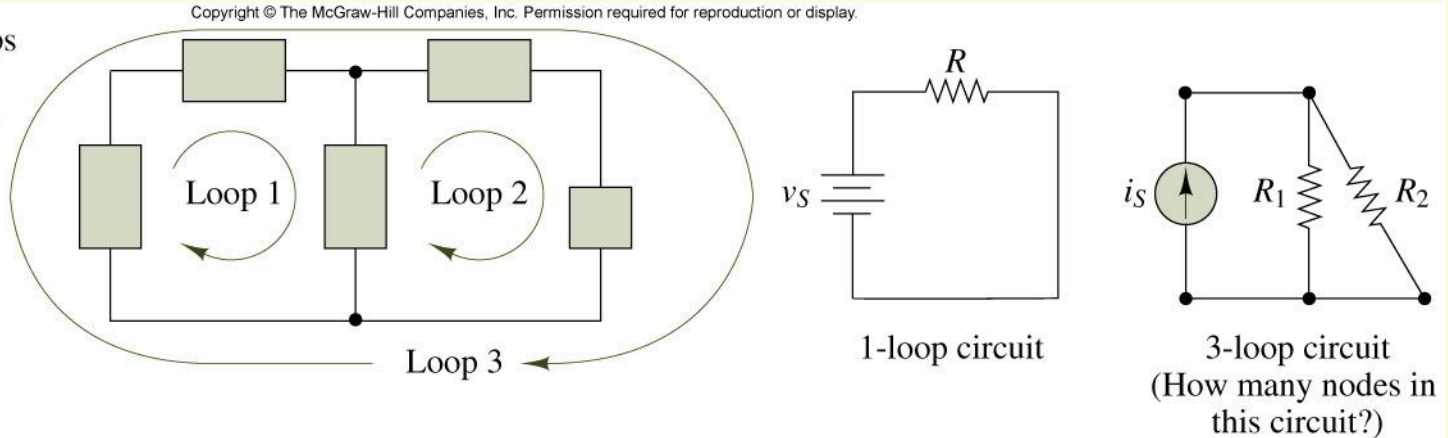
# Definition of a loop and a mesh

Note how two different loops in the same circuit may include some of the same elements or branches.




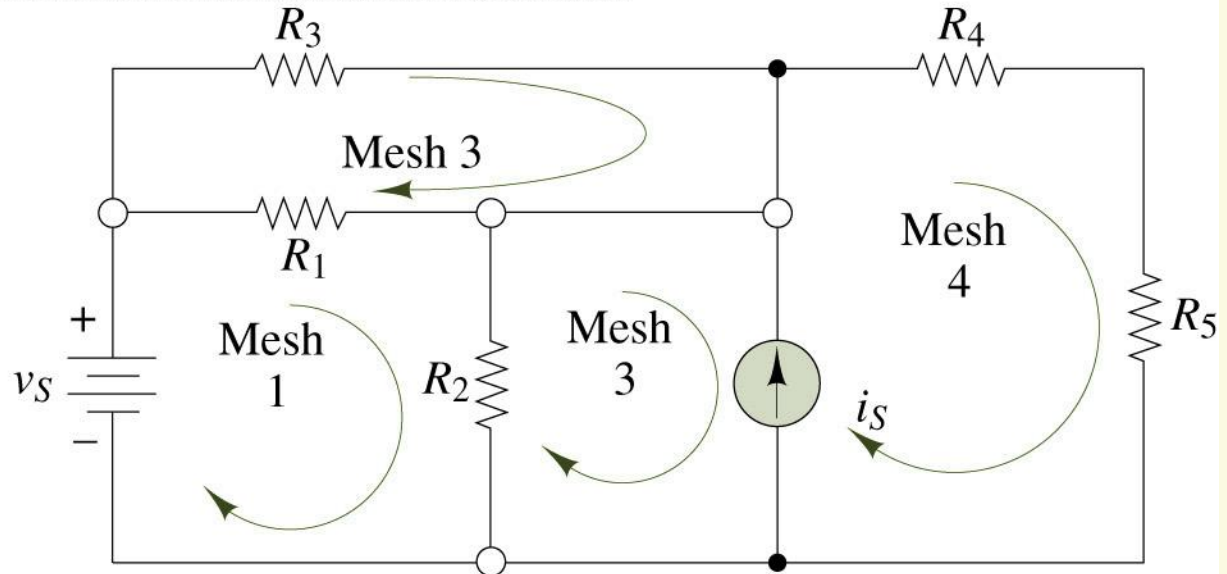
Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.



How many loops can you identify in this four-mesh circuit? (Answer: 14)



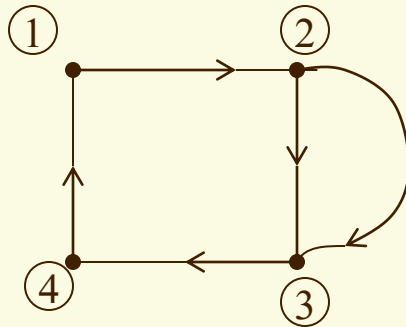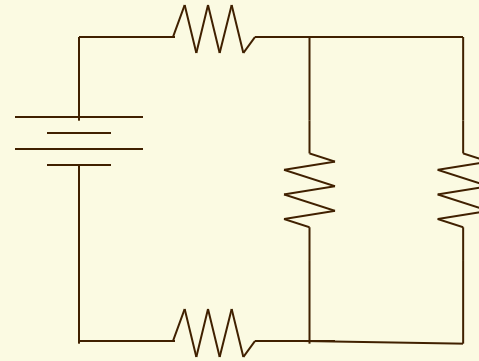Draw the directed graph. How many nodes and edges exist?



# Conclusion

- 📄 Lumped Circuit Abstraction
- 📄 Circuit Elements
- 📄 Power and Energy
- 📄 Circuit Graph: Branch and Node