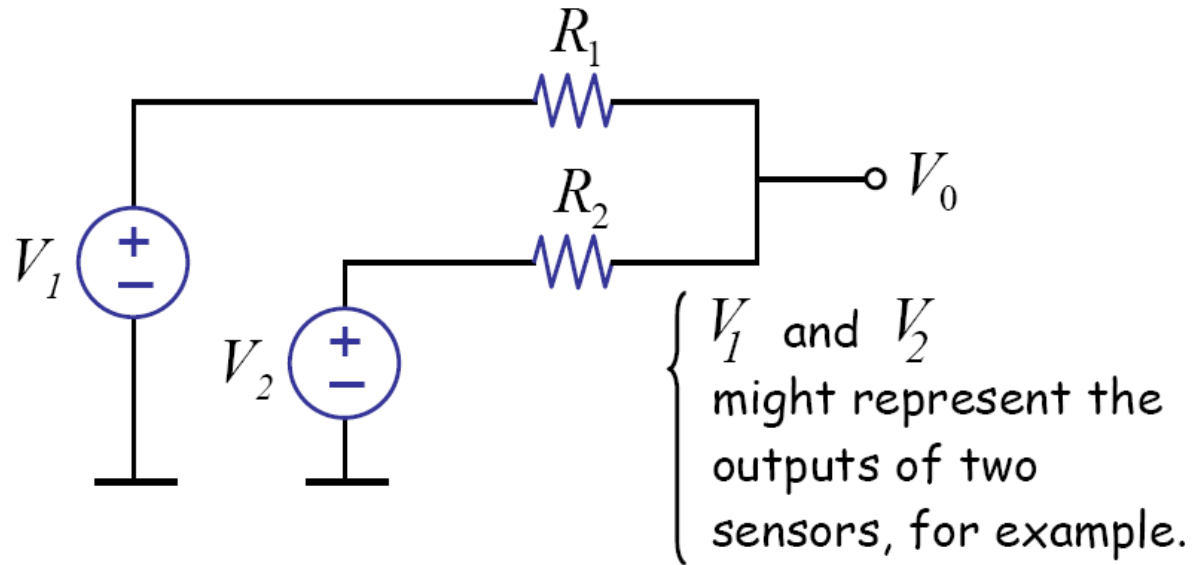




# **Chap. 5 The Digital Abstraction**


Voltage Levels and the Static Discipline



# Analog Signal Processing



# Noise Problem

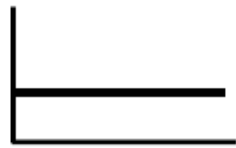
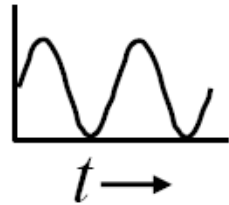


add noise on  
this wire 

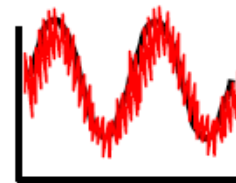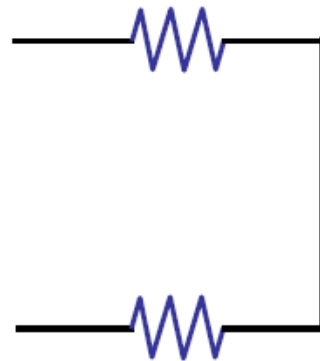


Receiver:  
huh?

# Digital System: Noise immunity !!

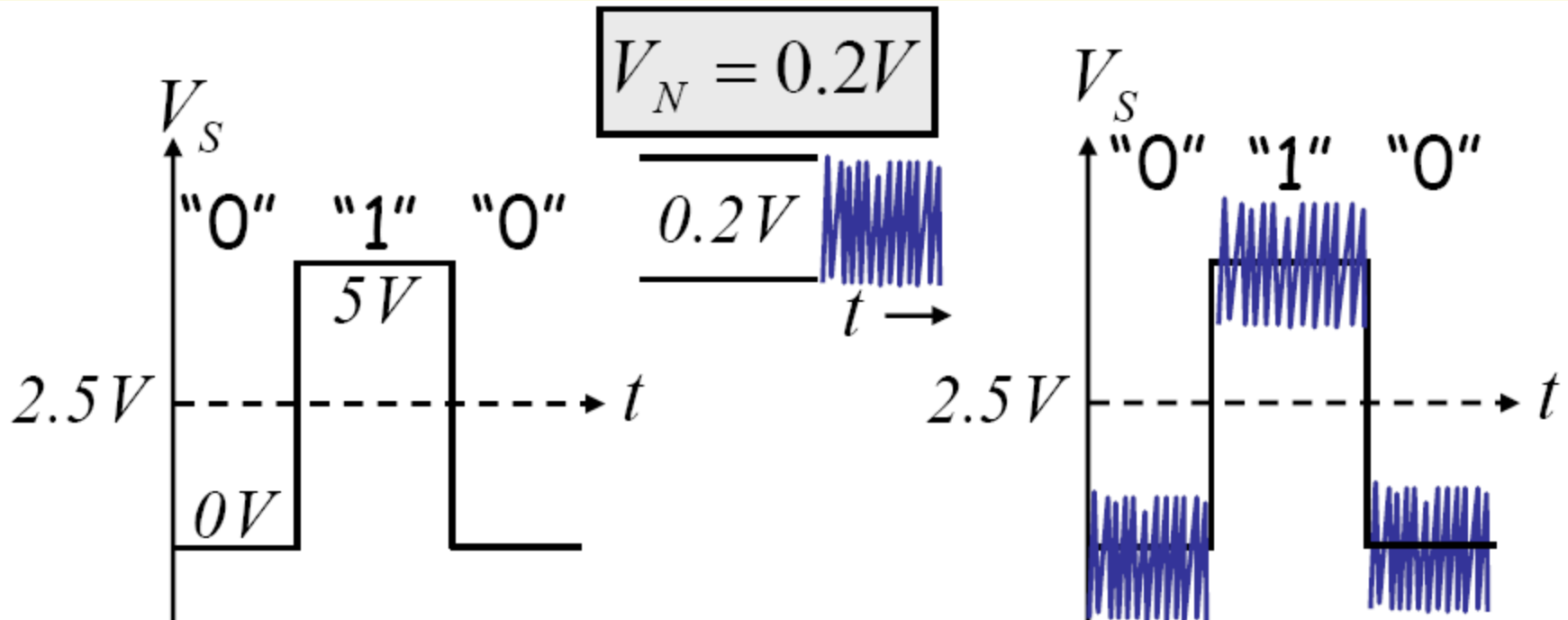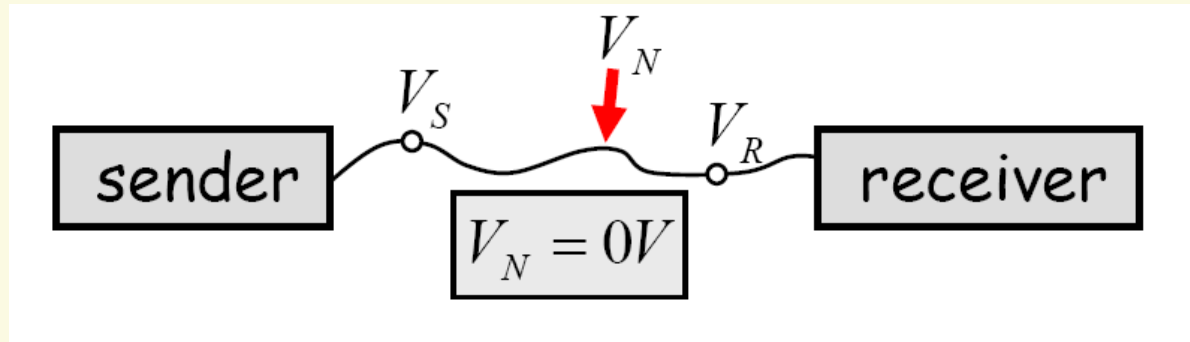


# Value Discretization

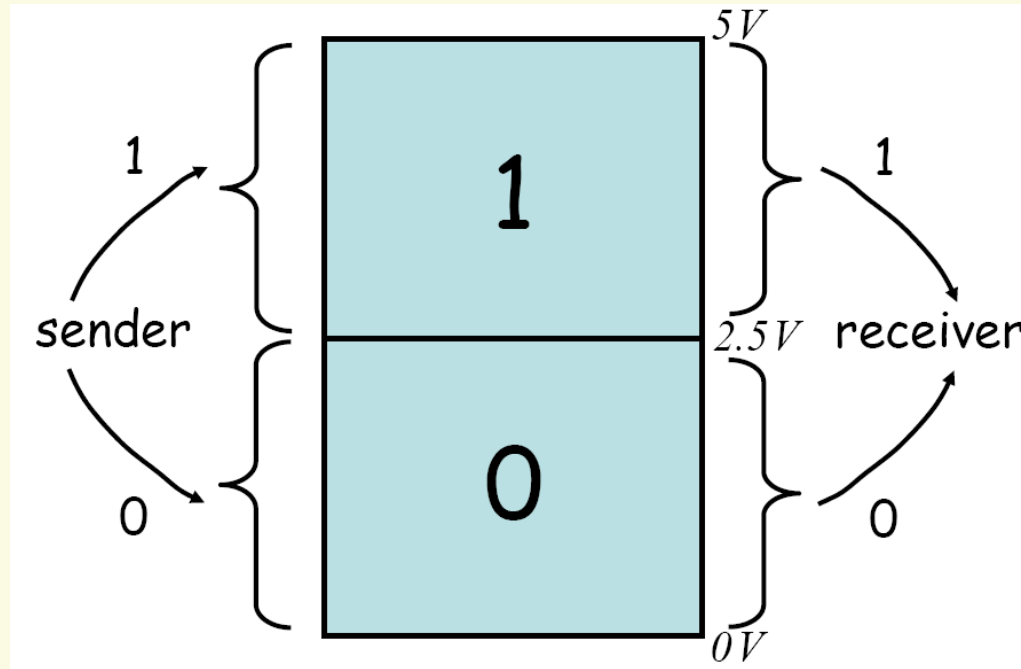


📄 What about 2.5 V ?

# Forbidden Region

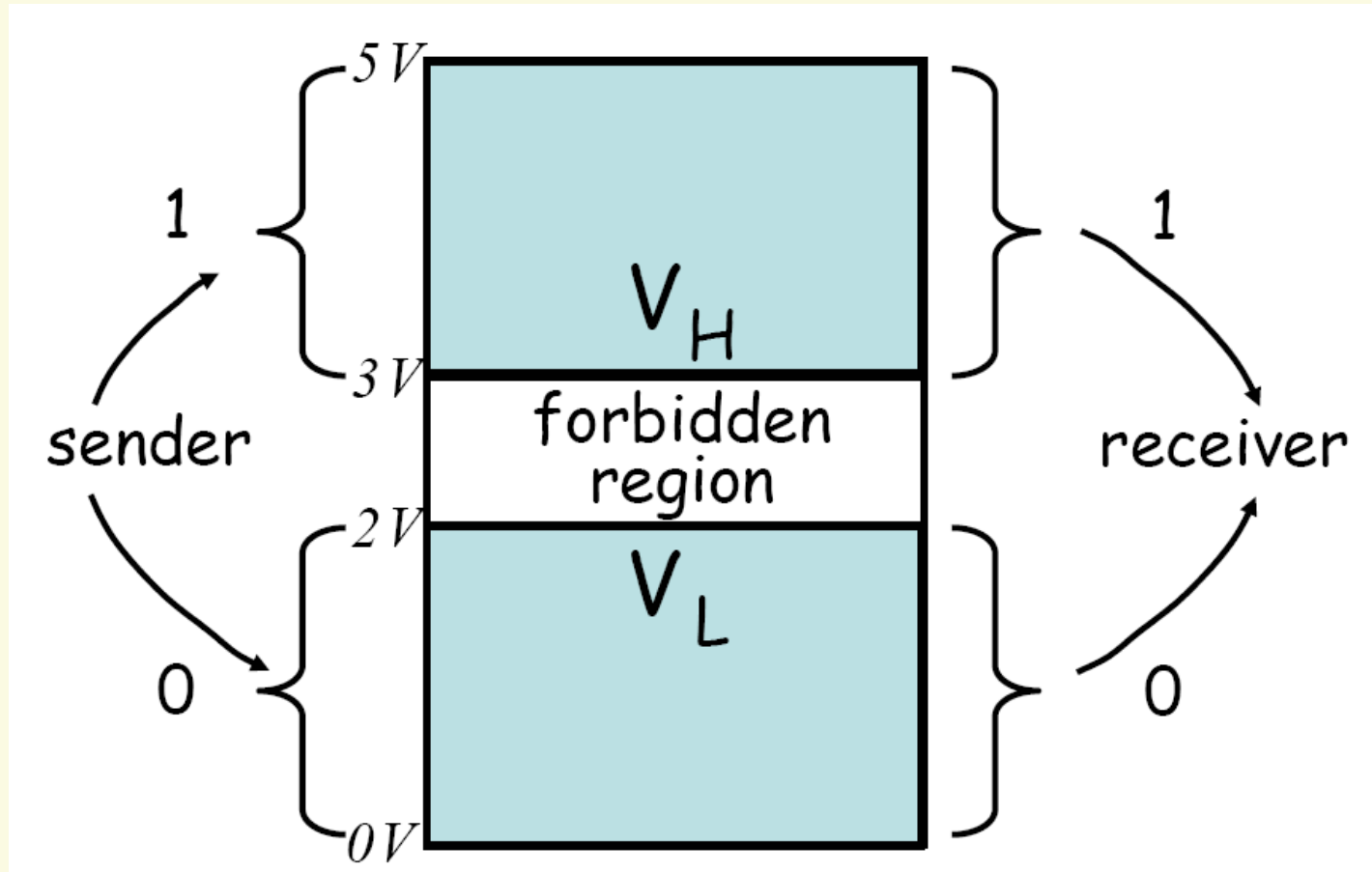

Where is the noise margin?

# Actual Value Discretization

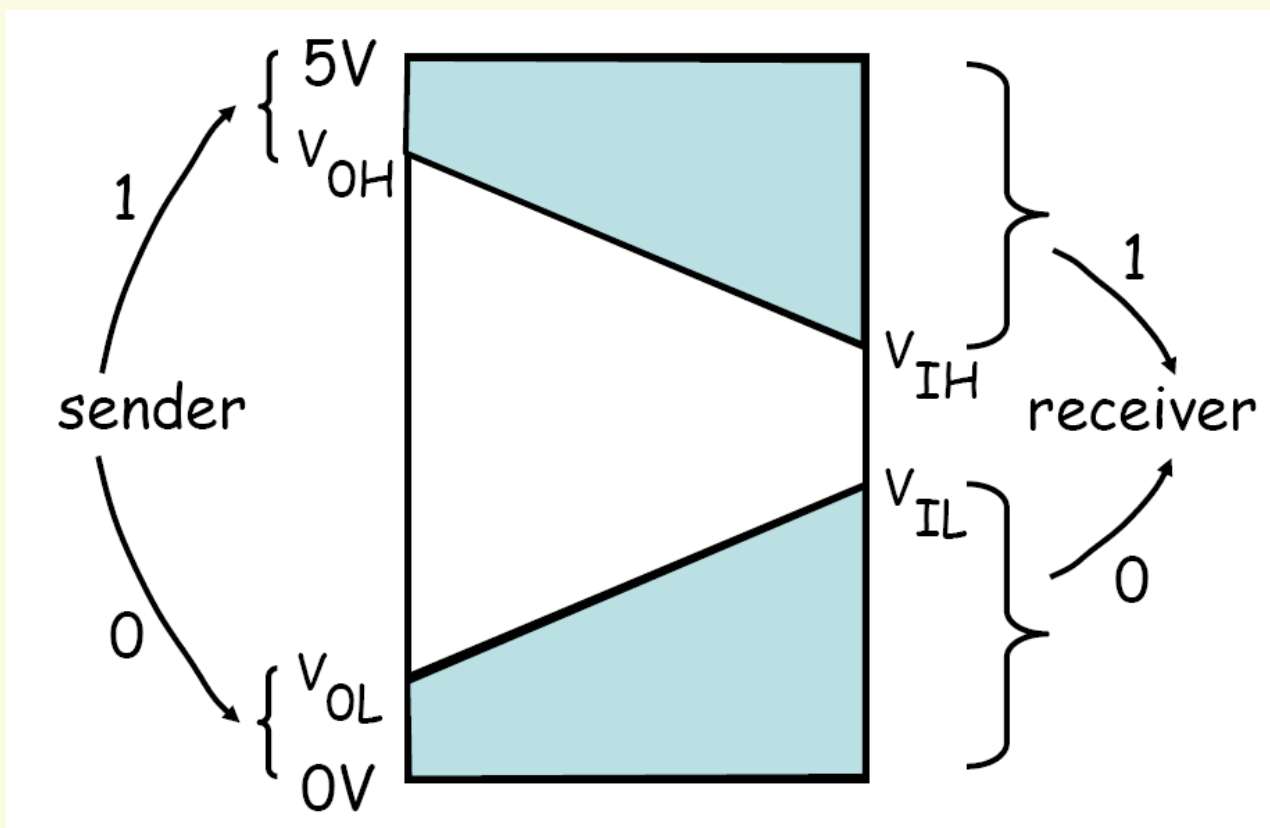

📄 Noise margin

$$NM_0 = V_{IL} - V_{OL}$$




$$NM_1 = V_{OH} - V_{IH}$$

# Static Discipline

- 📄 If inputs to a digital system meet valid input thresholds, the system guarantees that its outputs will meet valid output thresholds.



# Conclusion

-  Value discretization
-  Noise margin
-  Static discipline

# Chap. 6 The MOSFET Switches


MOSFET and Switch(S) Model

Static Analysis Using S Model


SR Model of MOSFET

Static Analysis

# Switch Logic

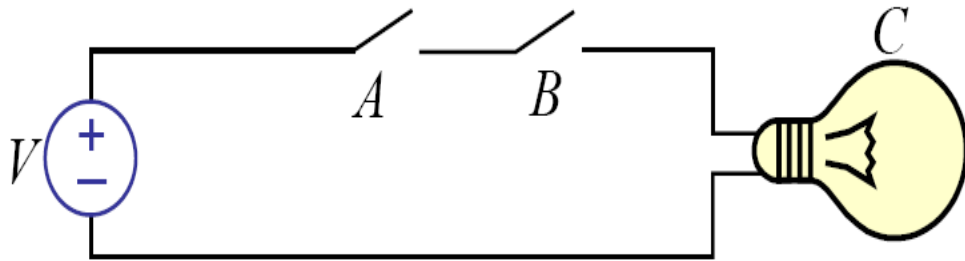


📄 Key: switch device

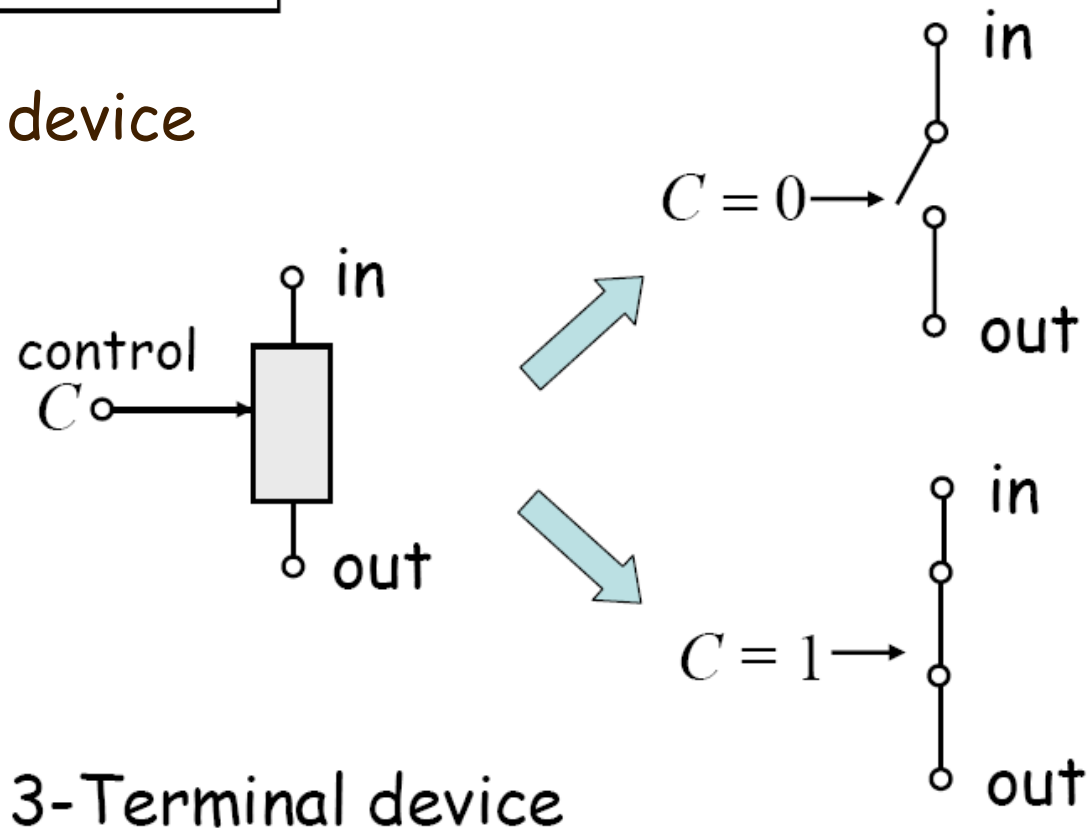


3-Terminal device

# Logic Inverter

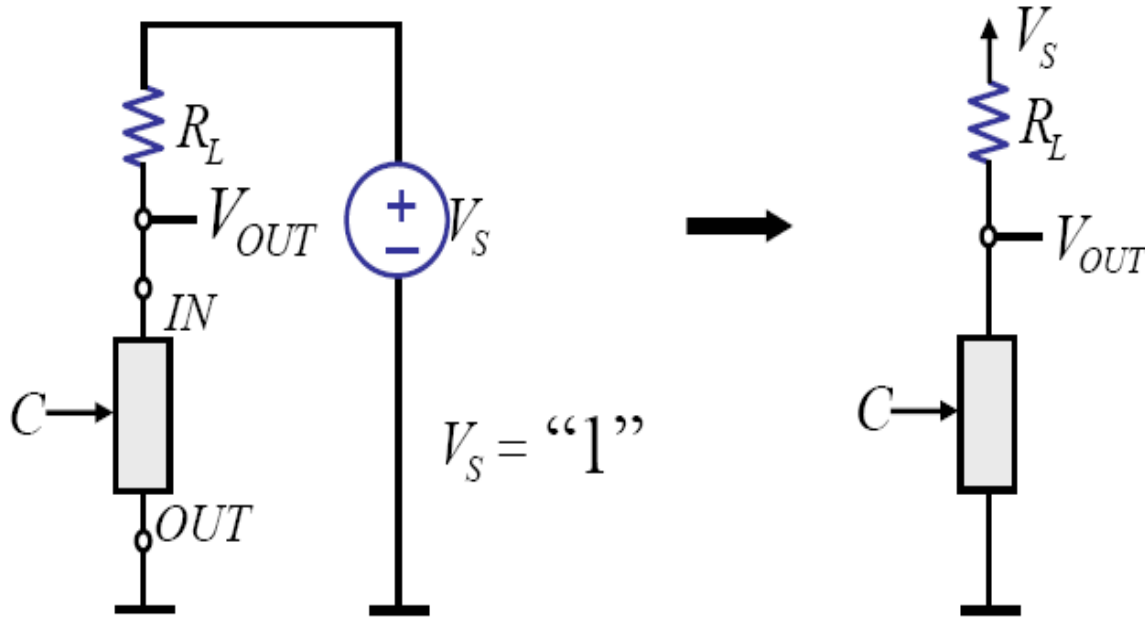


Truth table for

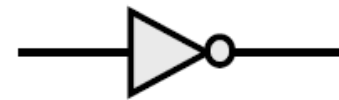

$C$	$V_{OUT}$
0	1
1	0

# Example

1. Find the logic of this circuit.


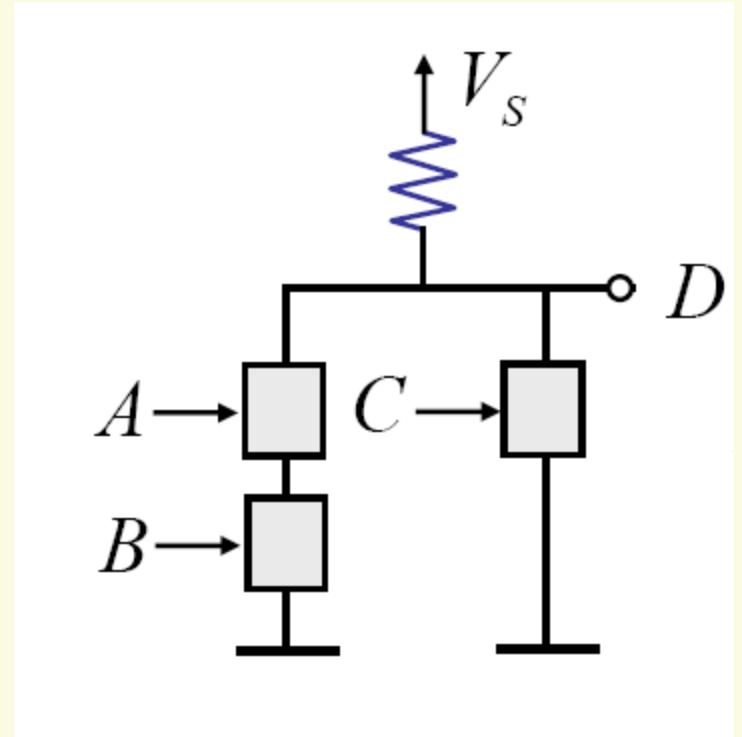


2. Draw the following logic circuit:



$$Y = \overline{A(B + C)}$$
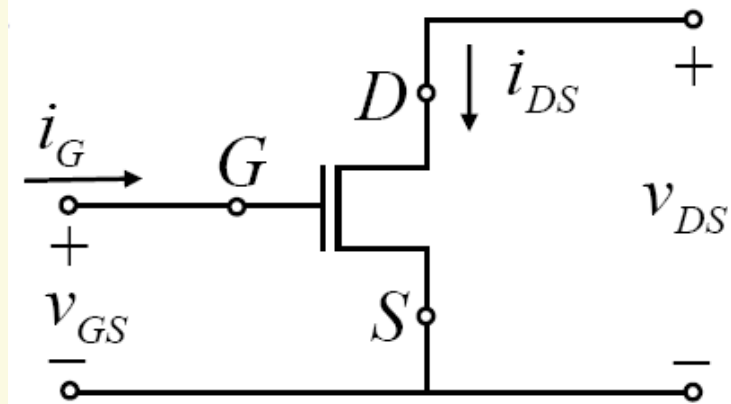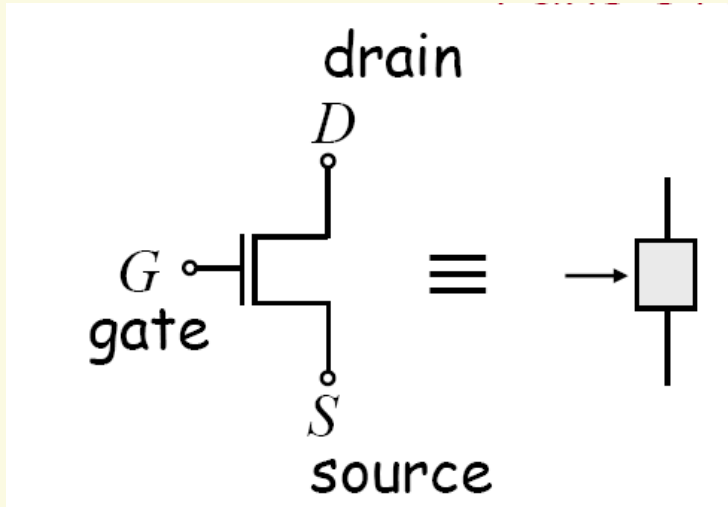
# MOSFET


☞ Metal Oxide Semiconductor Field-Effect Transistor




# Switch (S) Model of MOSFET

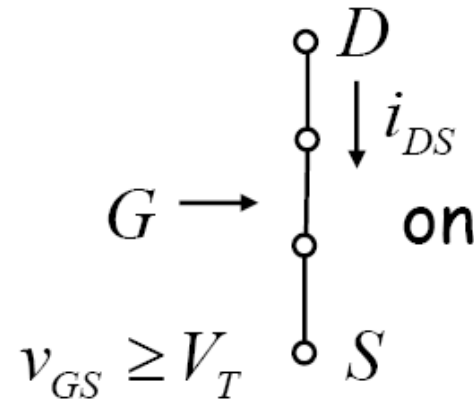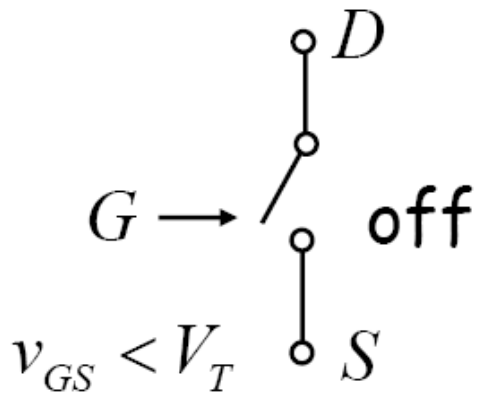

$V_T \approx 1V$  typically

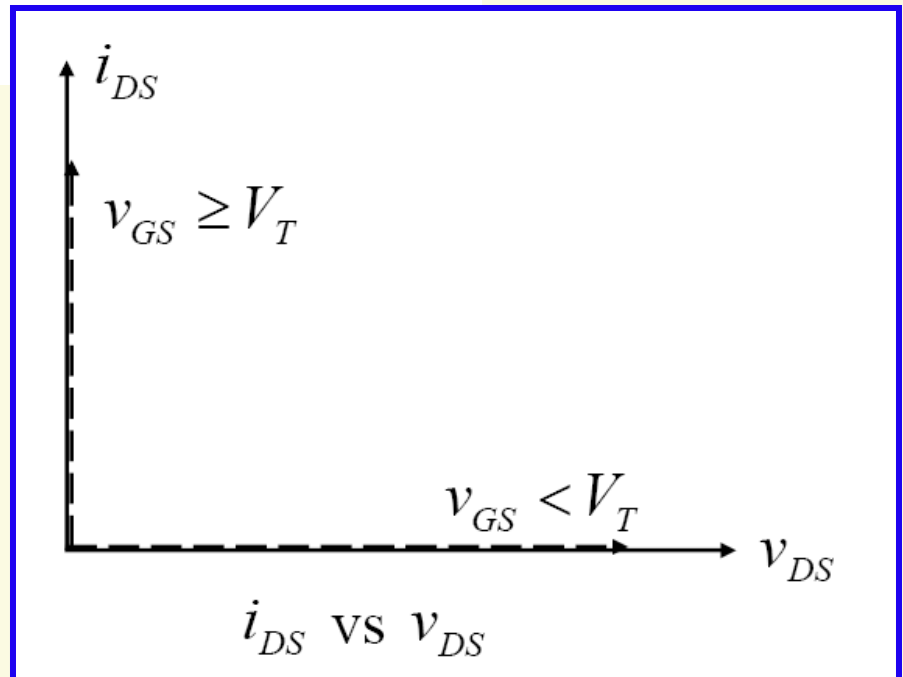


# MOS Inverter

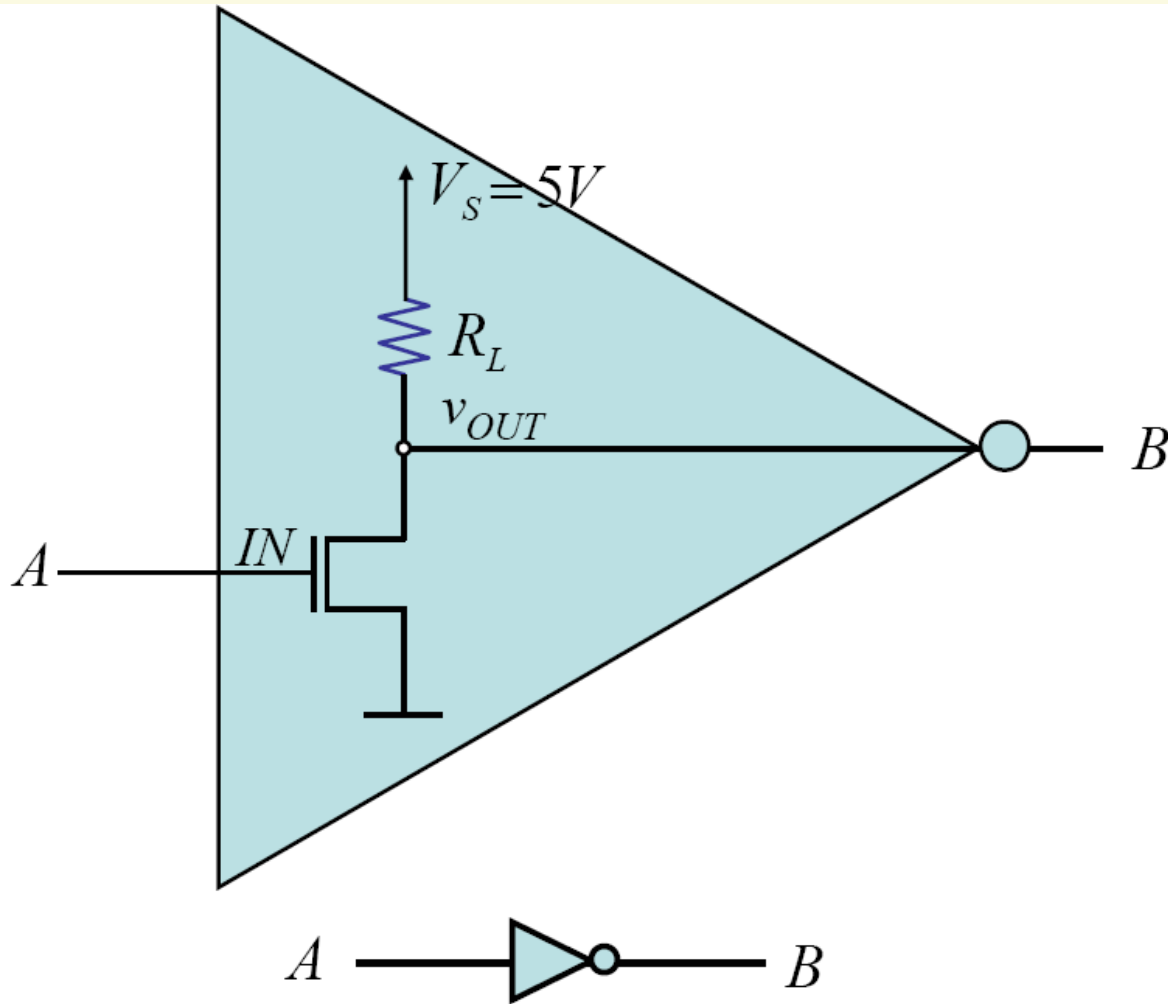



# Voltage Transfer Characteristics




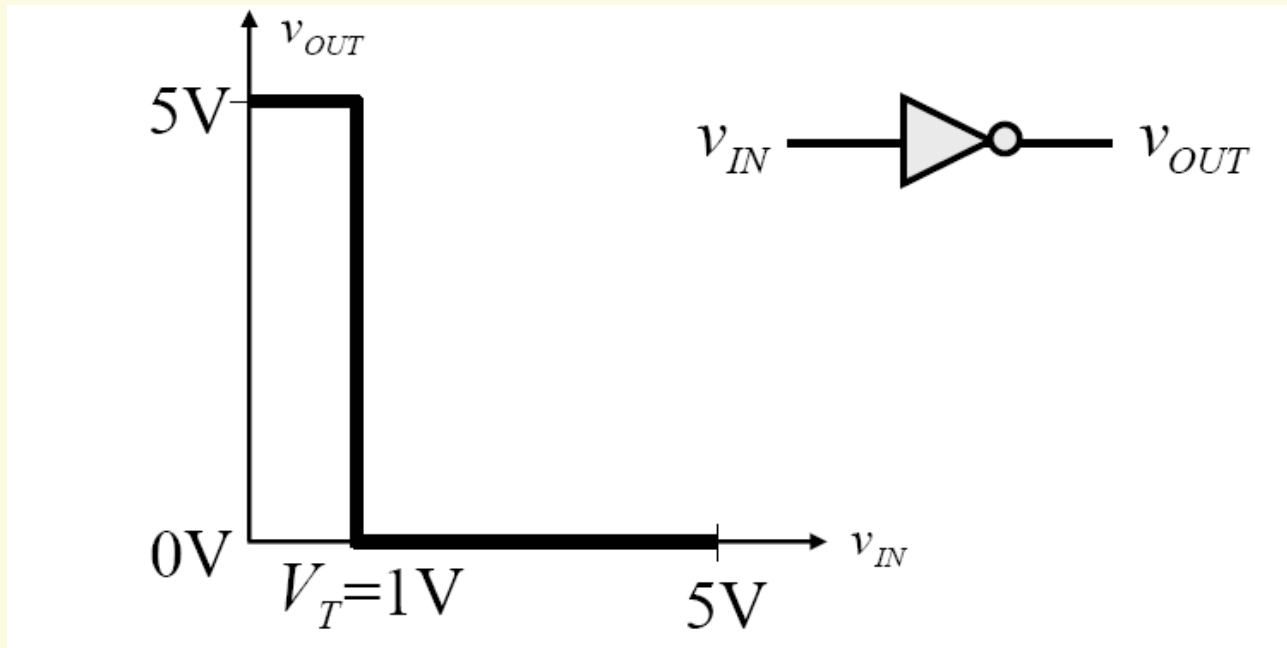


Does it satisfy the following static discipline?



- (1)  $V_{OH} = 4.5V$ ,  $V_{OL} = 0.5V$ ,  $V_{IH} = 4V$ ,  $V_{IL} = 0.9V$
- (2)  $V_{OH} = 4V$ ,  $V_{OL} = 1V$ ,  $V_{IH} = 3.5V$ ,  $V_{IL} = 1.5V$

# Switch Resistor (SR) Model of MOSFET

📄 Better approximation

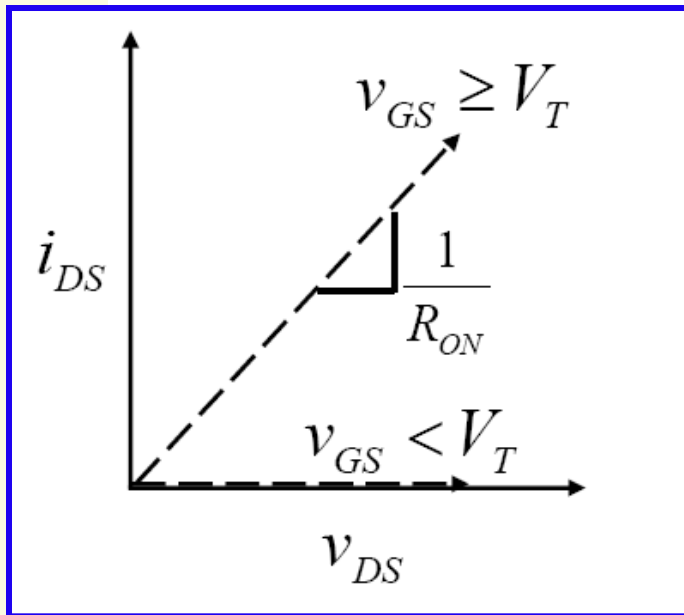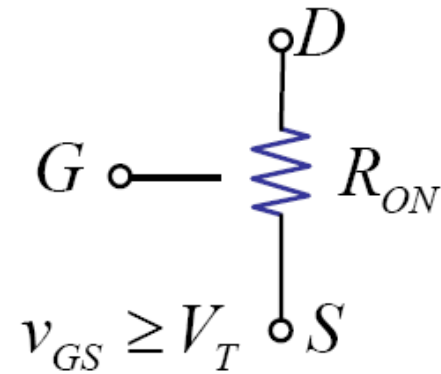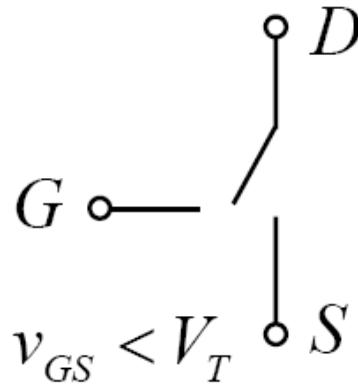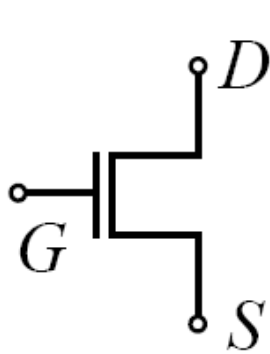

# MOSFET Inverter: Revisted

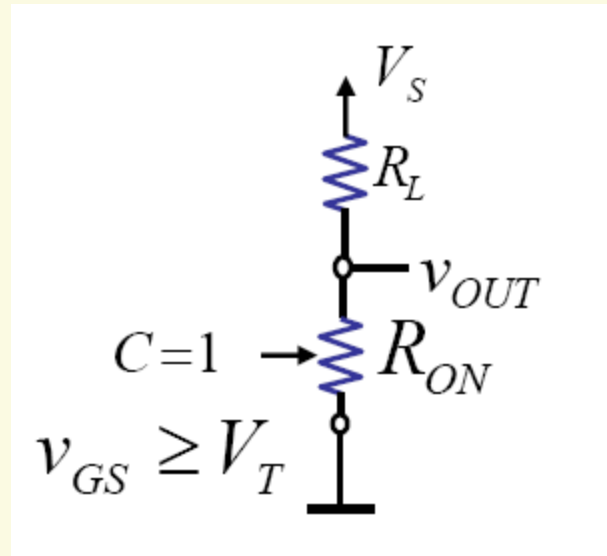
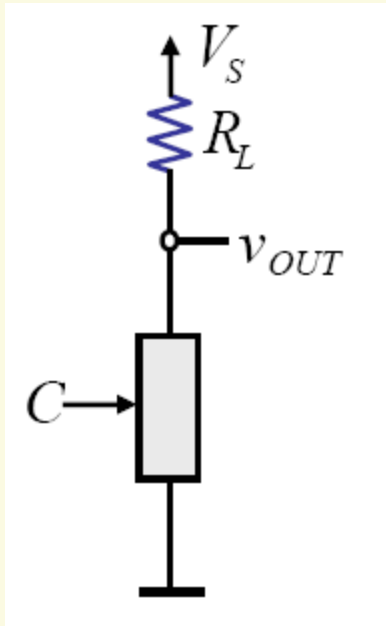


Choose  $R_L$ ,  $R_{ON}$ ,  $V_S$  such that:

$$v_{OUT} = \frac{V_S R_{ON}}{R_{ON} + R_L} \leq V_{OL}$$

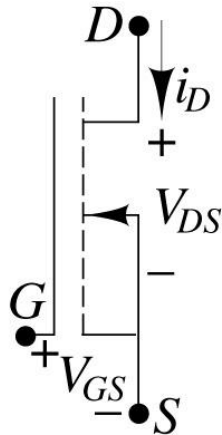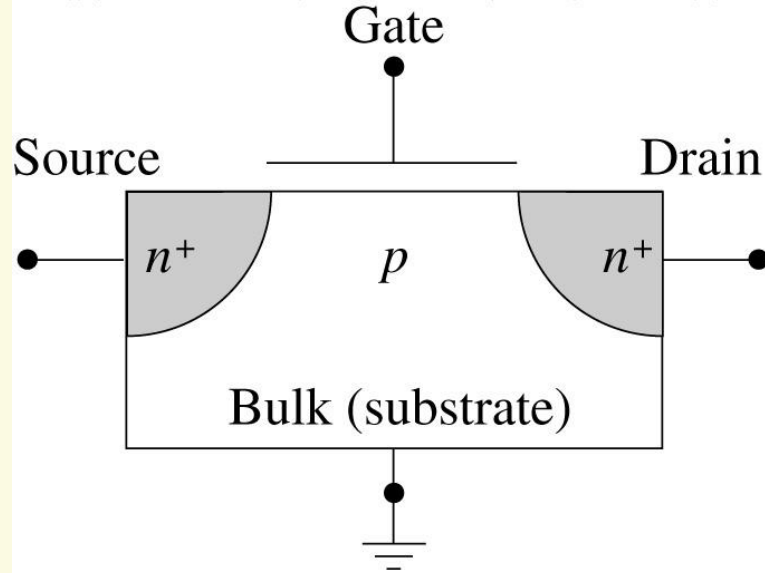
# Physical Structure of MOSFET

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.



# Regions of operation of NMOS transistor

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.

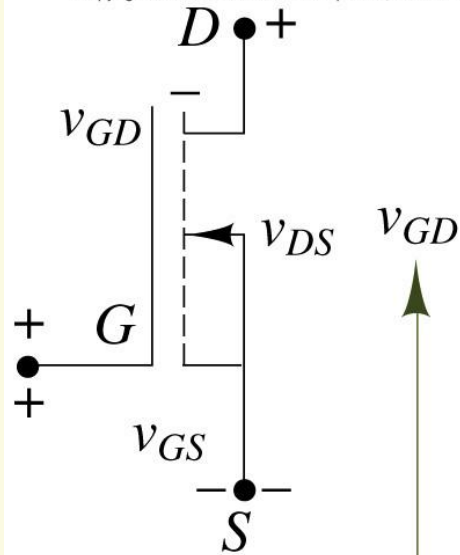

**Region 3:  
Triode**

$$V_{GS} \geq V_T, \quad V_{GD} \geq V_T$$

$$i_D = K[2(V_{GS} - V_T)V_{DS} - V_{DS}^2]$$

**Region 2:  
Saturation**

$$V_{GS} \geq V_T, \quad V_{GD} < V_T$$

$$i_D = K(V_{GS} - V_T)^2 \left(1 + \frac{V_{DS}}{V_A}\right)$$

$$\approx K(V_{GS} - V_T)^2$$

**Region 1:  
Cutoff**


$$V_{GS} < V_T, \quad V_{GD} < V_T$$

$$i_D = 0$$
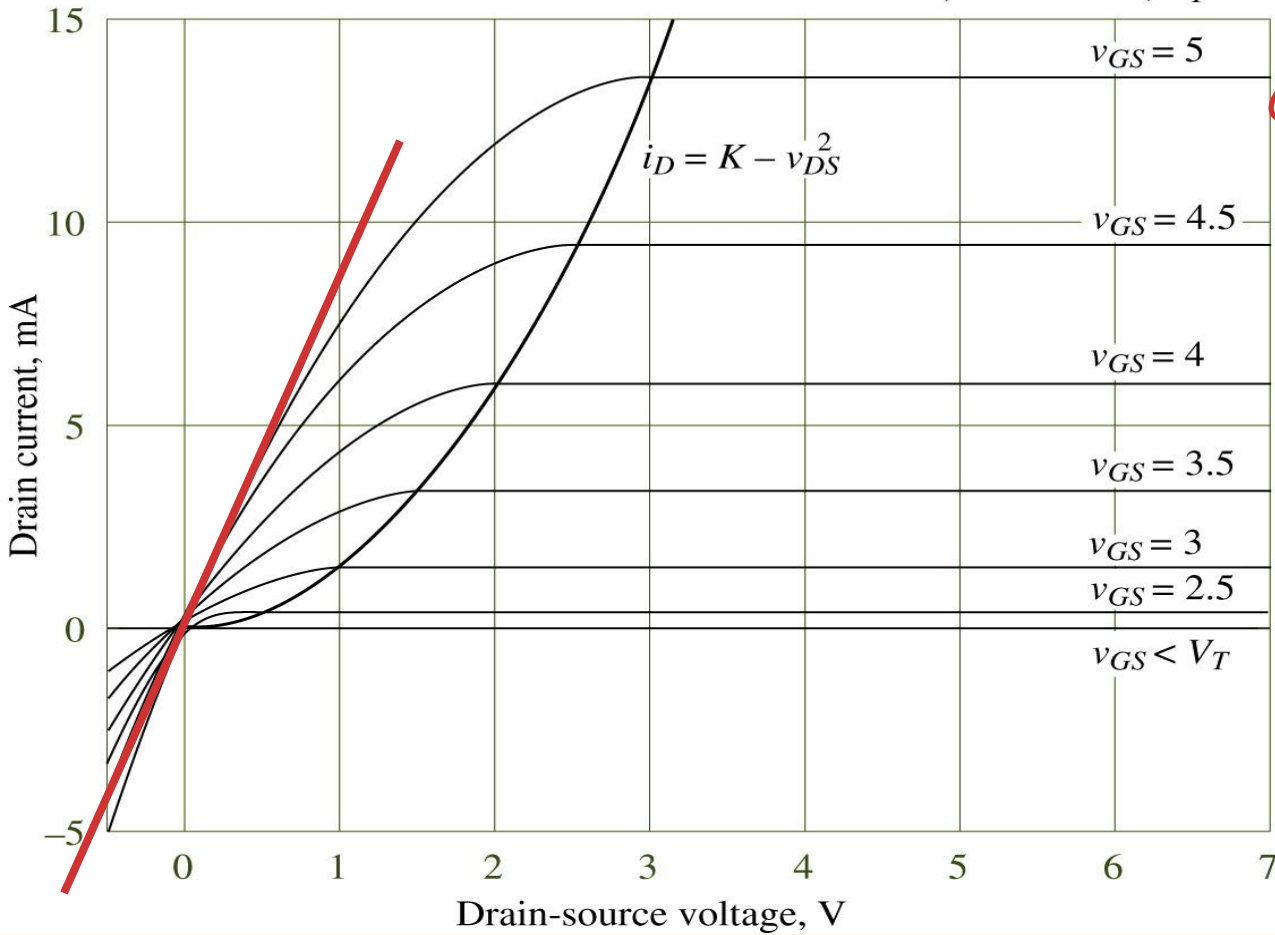
# I-V Characteristic of NMOS

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.

Drain curves for  $n$ -channel enhancement MOSFET;  $K = 0.0015$ ,  $V_T = 2$




Conductance parameter

$$K = \frac{1}{2} \mu C_{OX} \left( \frac{W}{L} \right)$$


$$R_{ON} = R_n \frac{L}{W}$$

# MOS Circuit Analysis

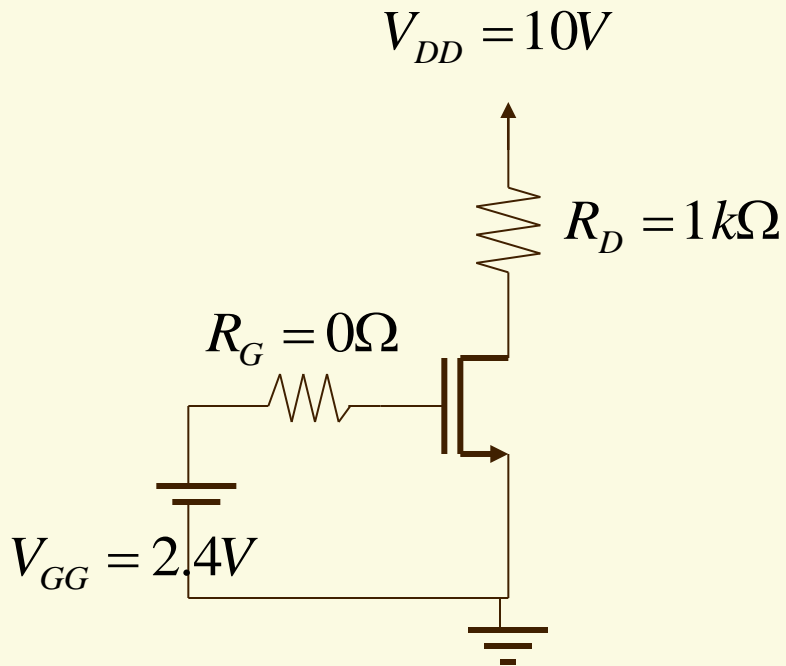


$$V_T = 1.4V, K = 10mA/V$$

# Inverter Characteristics: SR Model

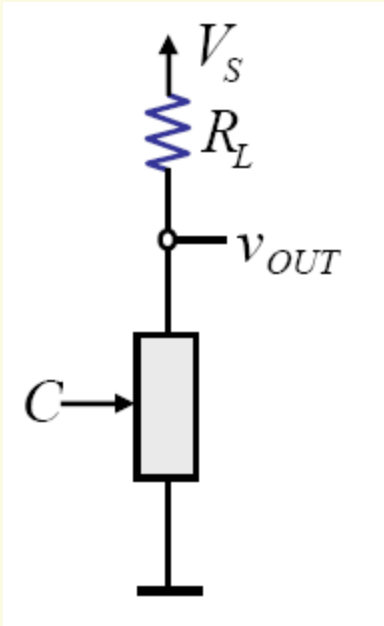
 
$$V_S = 5V, \quad V_T = 1V, \quad R_L = 14k\Omega, \quad R_{ON} = 1k\Omega$$






## Example 6.5

 Determine  $W/L$  for correct inverter operation


$$V_S = 5V, \quad V_T = 1V, \quad R_L = 10k\Omega, \quad R_n = 5k\Omega$$

## Example 6.6

 To satisfy the following static discipline redesign the inverter.


$$V_S = 5V, \quad V_T = 1V, \quad R_L = 10k\Omega, \quad R_n = 5k\Omega$$

# Static Analysis of NAND Gate: SR Model

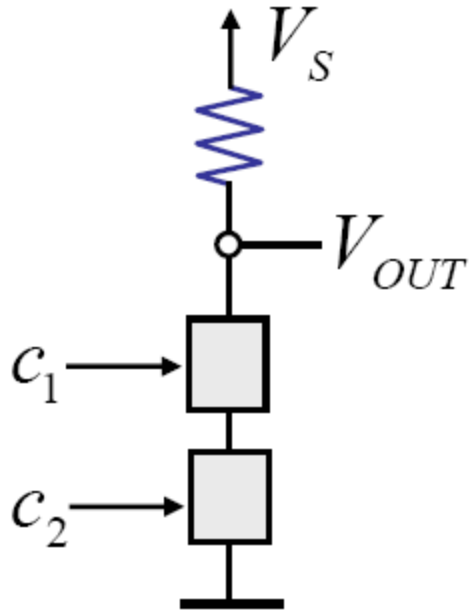

$$V_S = 5V, \quad V_T = 1V, \quad R_L = 14k\Omega, \quad R_{ON} = 1k\Omega$$

# Signal Restoration and Gain

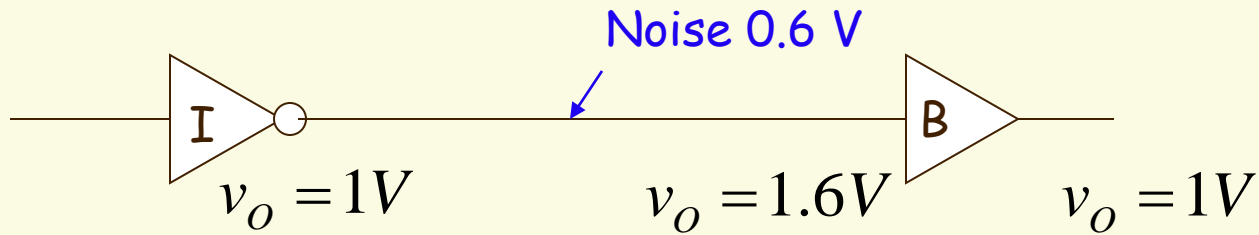


📄 Buffer restores the signal level (example)


$$V_{IL} = 2V, \quad V_{IH} = 3V, \quad V_{OL} = 1V, \quad V_{OH} = 4V$$

$$\text{Gain} = \frac{V_{OH} - V_{OL}}{V_{IH} - V_{IL}}$$
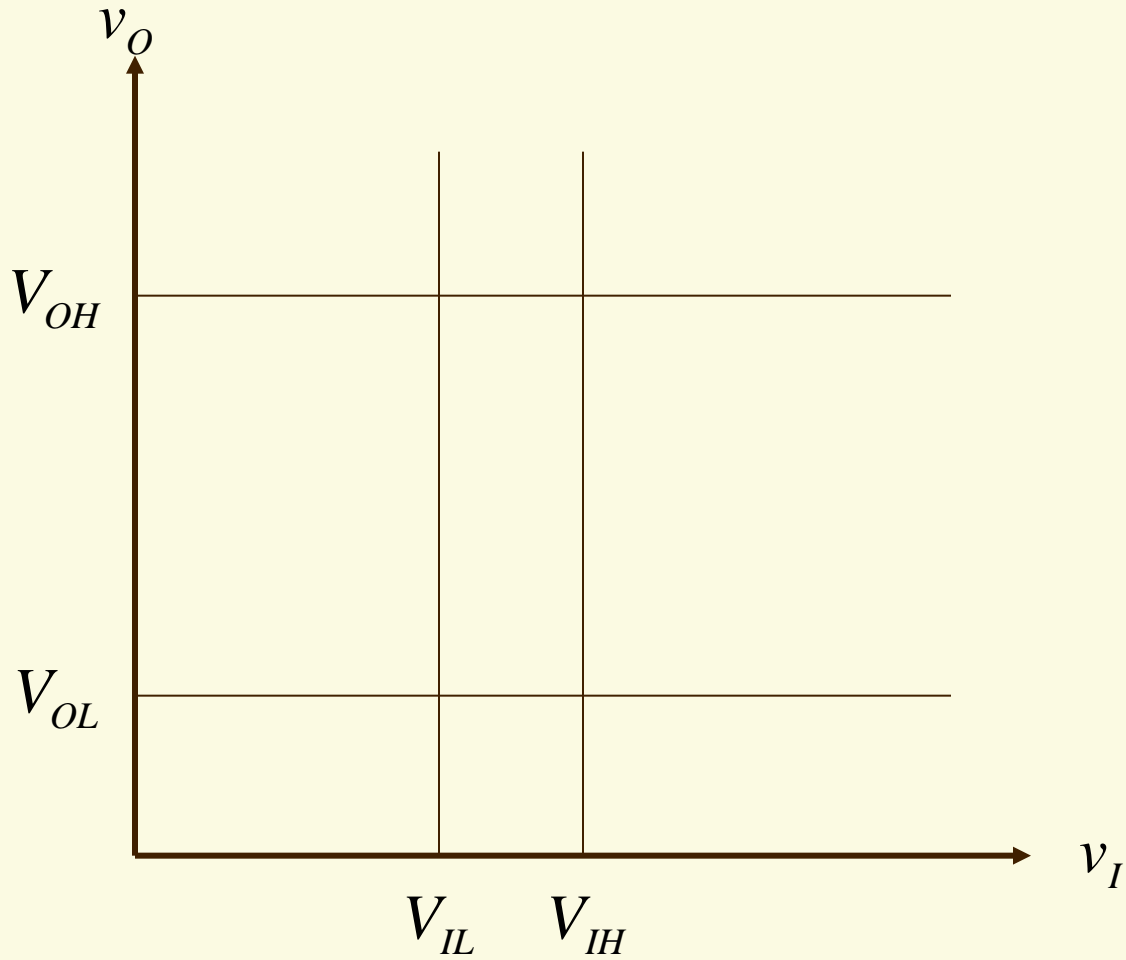
# Buffer Voltage Transfer Characteristics (VTC)



# Inverter VTC

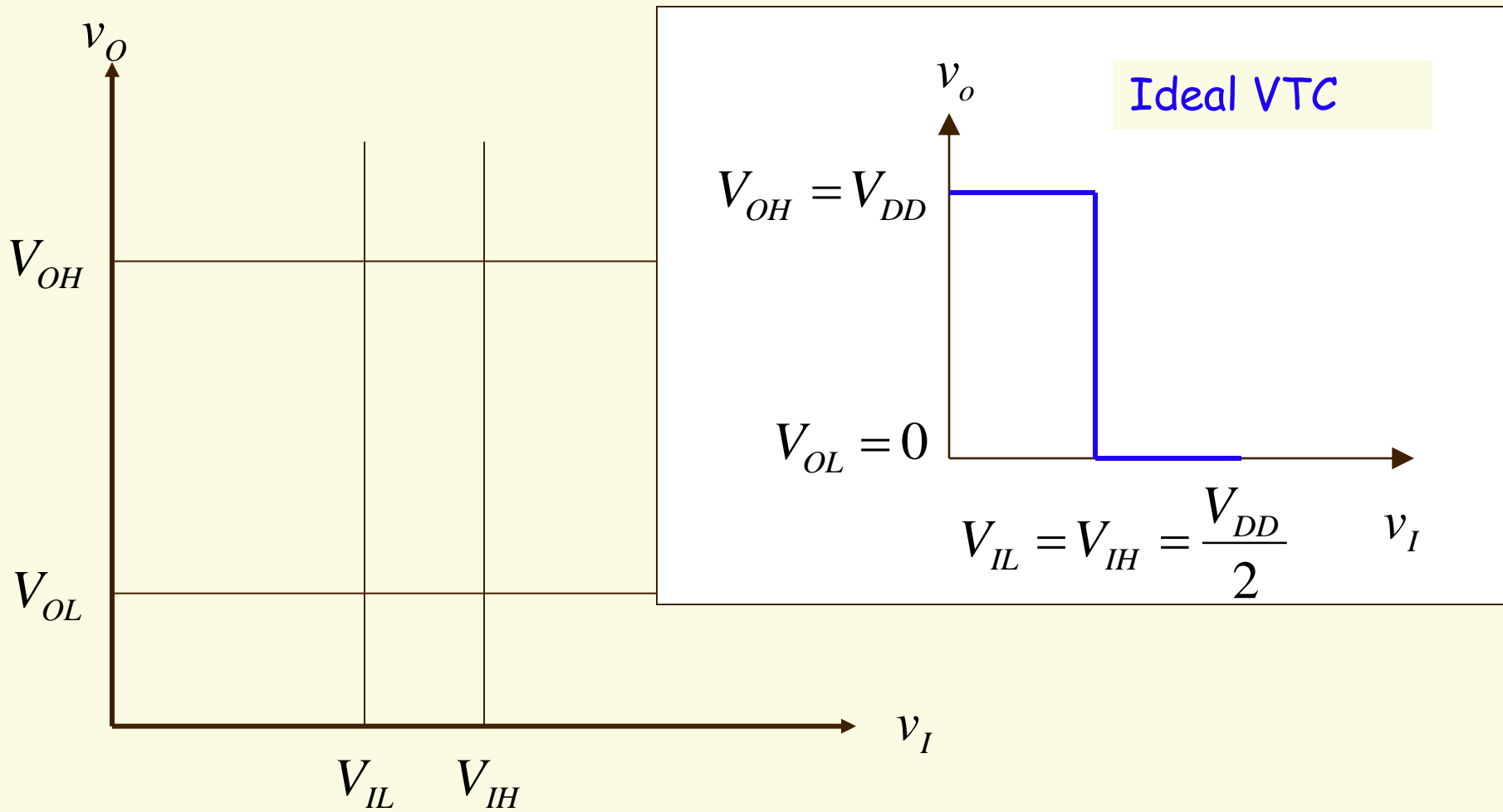

# Conclusion

- 📄 MOSFET and S Model
- 📄 MOSFET and SR Model
- 📄 MOSFET Analysis
- 📄 Signal Restoration and Gain