

# Chap. 9 Energy Storage Elements



Capacitors and Inductors

Series and Parallel Connections



Simple Circuit Examples

Energy, Charge, and Flux Conservation

# Motivation

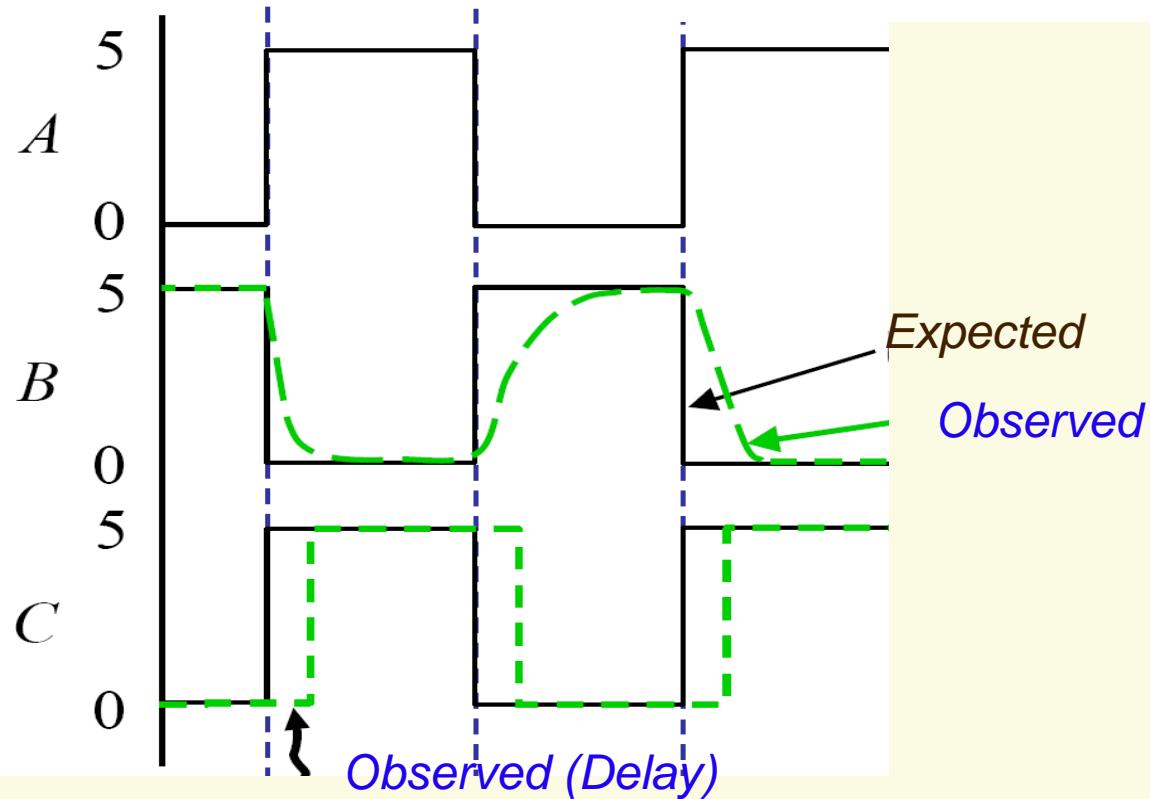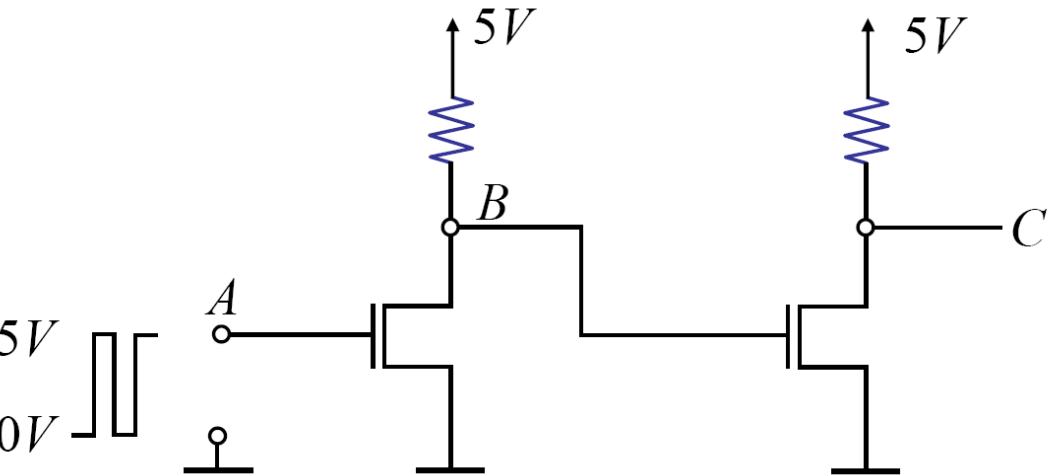


# MOSFET Modeling

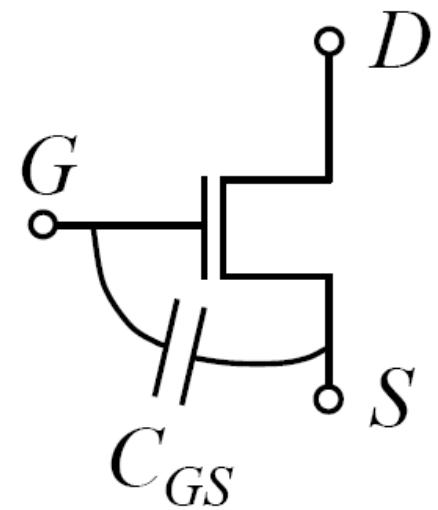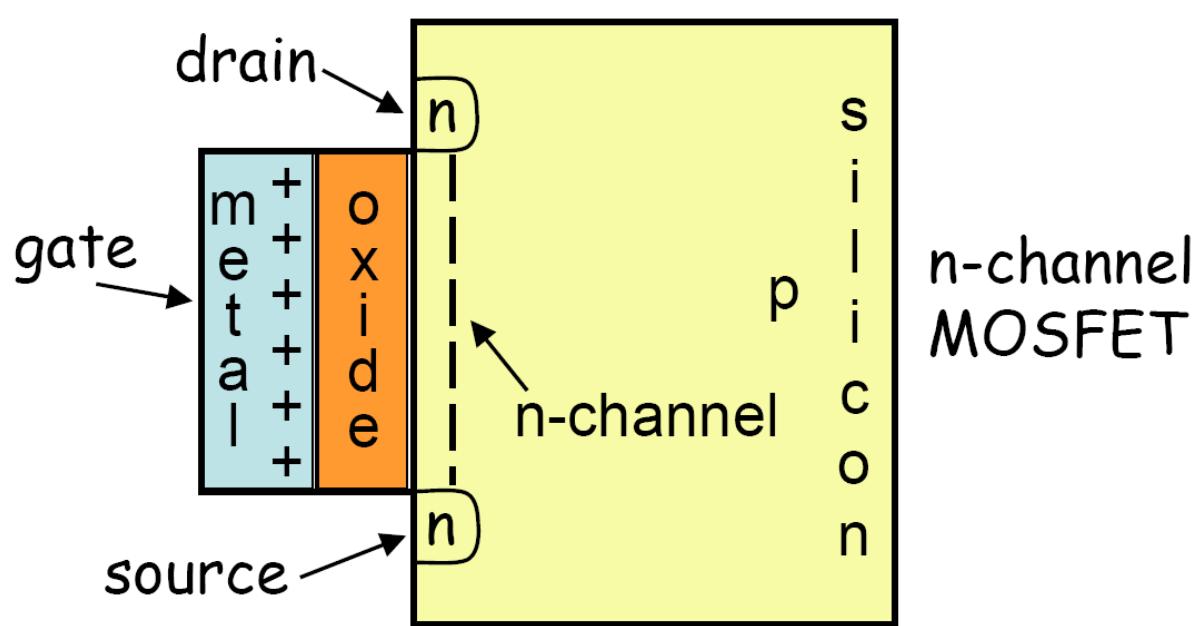
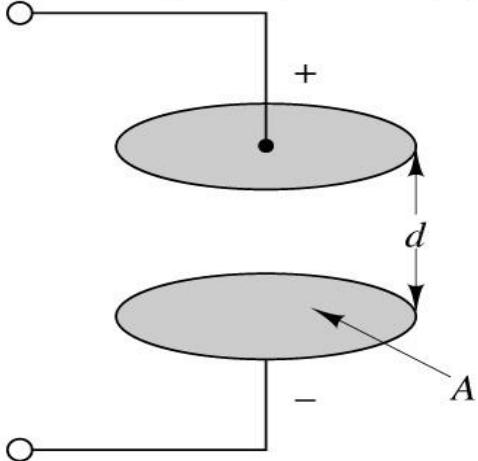
# Ideal Linear Capacitor

Copyright © The McGraw-Hill Companies, Inc.  
Permission required for reproduction or display.



Parallel-plate capacitor with air gap  $d$  (air is the dielectric)

The circuit symbol for a capacitor, which is a capacitor plate icon with a value  $C$  written next to it.

$$C = \frac{\epsilon A}{d}$$

$\epsilon$  = permittivity of air  
 $= 8.854 \times 10^{-12} \text{ F/m}$

Circuit symbol

A circuit diagram showing a capacitor symbol (two parallel lines) with a voltage  $v$  indicated across it. A current  $i$  is shown entering the top terminal. Below the capacitor, there is a minus sign (-).



$$q = Cv$$
$$\frac{dq}{dt} \equiv i = C \frac{dv}{dt}$$

$$v(t) =$$

# Observations from $i = C \ dv/dt$




- For DC voltage: Capacitor is an open circuit
- For  $i$  to be finite,  $v(t)$  must be continuous
- Typical units:  $\mu F \sim pF$

# Current Source and Capacitor

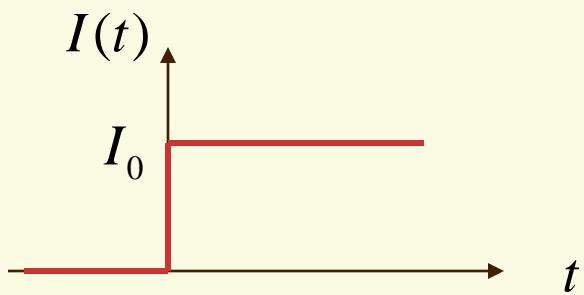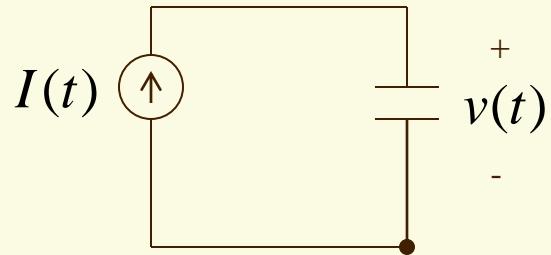


*Step input*

# Voltage Source and Capacitor

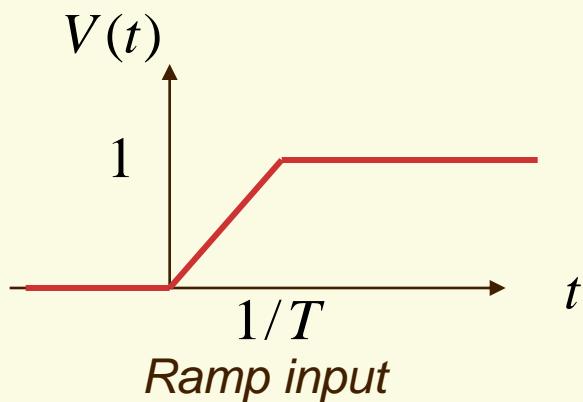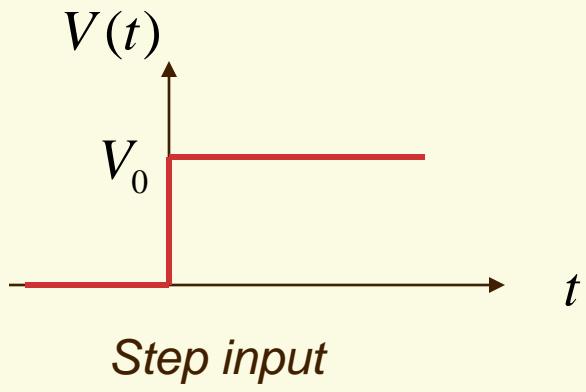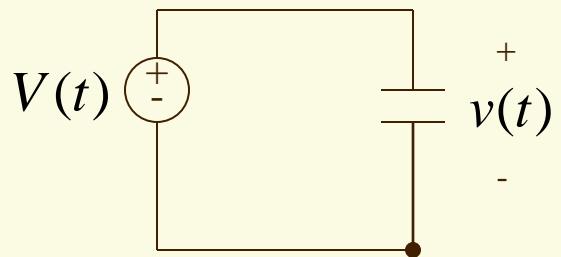

# Unit Impulse Function

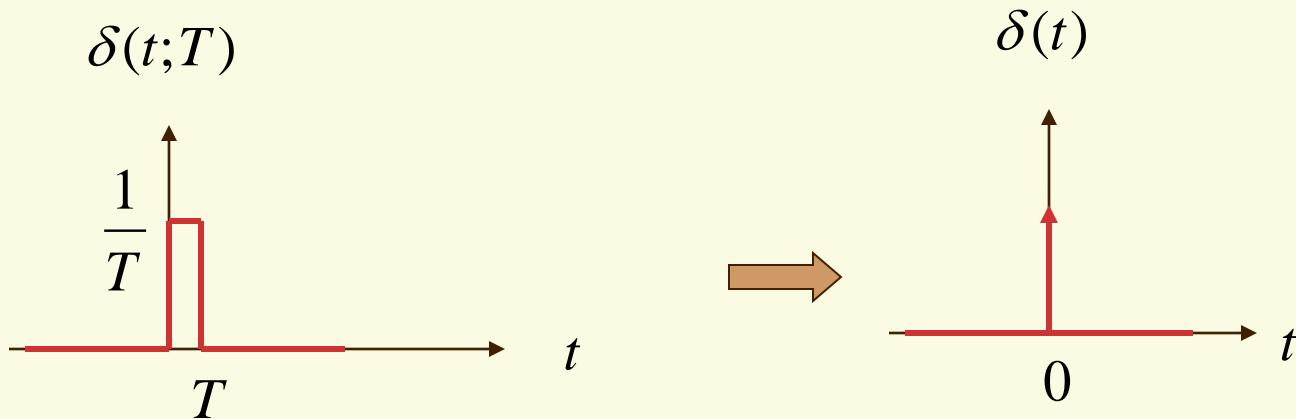


$$\delta(t) = 0 \quad \text{for} \quad t \neq 0$$

$$\int_{-\infty}^t \delta(t) dt = u(t) \Leftrightarrow \delta(t) = \frac{du(t)}{dt}$$

$$\int_{-\infty}^{+\infty} \delta(t) dt = 1$$

# Capacitor Voltage is continuous

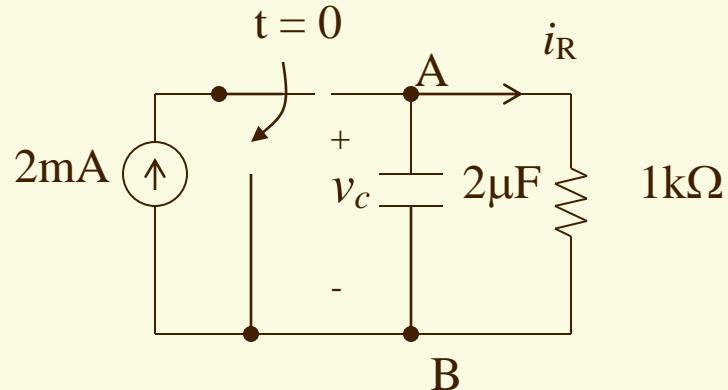


$$i_R(0-) = 1mA$$

$$\frac{dv_C}{dt}(0-) = ? \quad \frac{dv_C}{dt}(0+) = ?$$
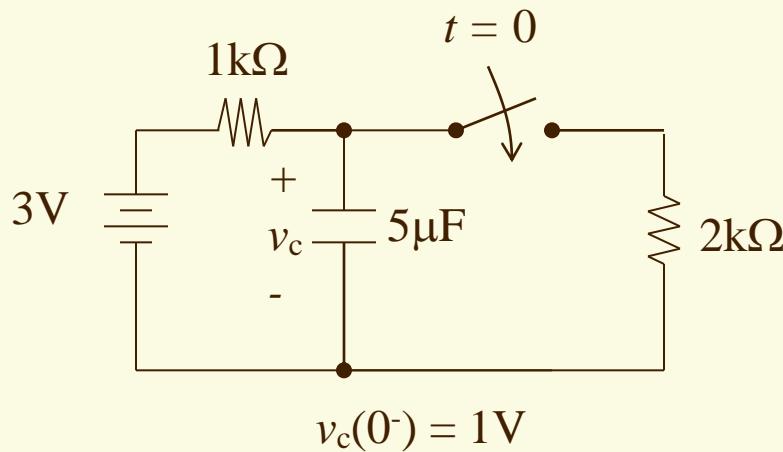
# Exercise



Switch is closed at  $t=0$ . Find  $\frac{dv_c}{dt}(0+)$ .




# Energy Storage – memory device


$$\frac{d\omega_E(t)}{dt} = i(t)v(t)$$

$$d\omega_E(t) = v(t)(i(t)dt) = v(t)dq(t)$$
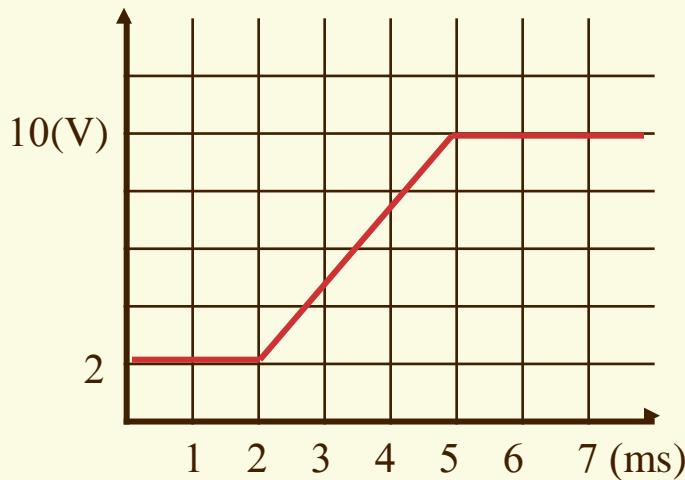
$$\omega_E = \int_0^q v \, dx = \frac{q^2(t)}{2C} = \frac{Cv(t)^2}{2}$$




# Capacitor Loop: Charge Conservation

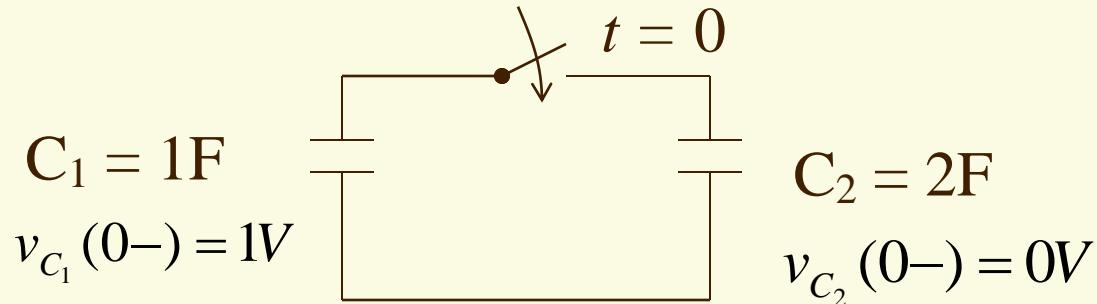

Question: Is energy conserved?

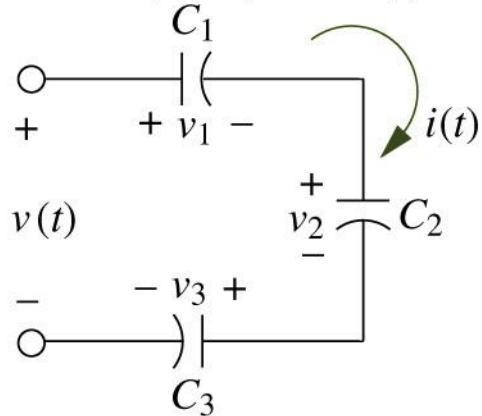
# Combining capacitors in a circuit

Copyright © The McGraw-Hill Companies, Inc.  
Permission required for reproduction or display.



$$C_{EQ} = \frac{1}{\frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3}}$$

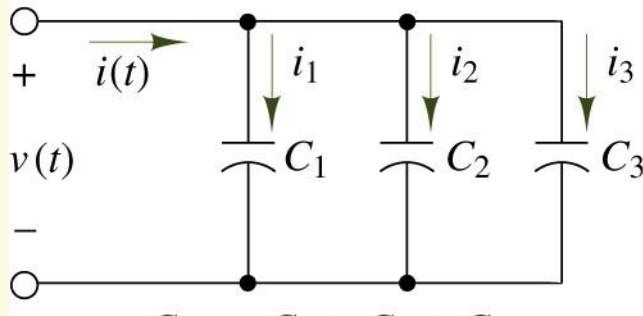Capacitances in series combine  
like resistors in parallel



$$C_{EQ} = C_1 + C_2 + C_3$$


Capacitances in parallel add

## Series connection:


## Parallel connection:
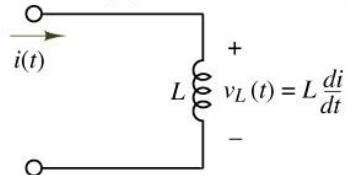
# Inductance and practical inductors


Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.




(a) Circuit symbol

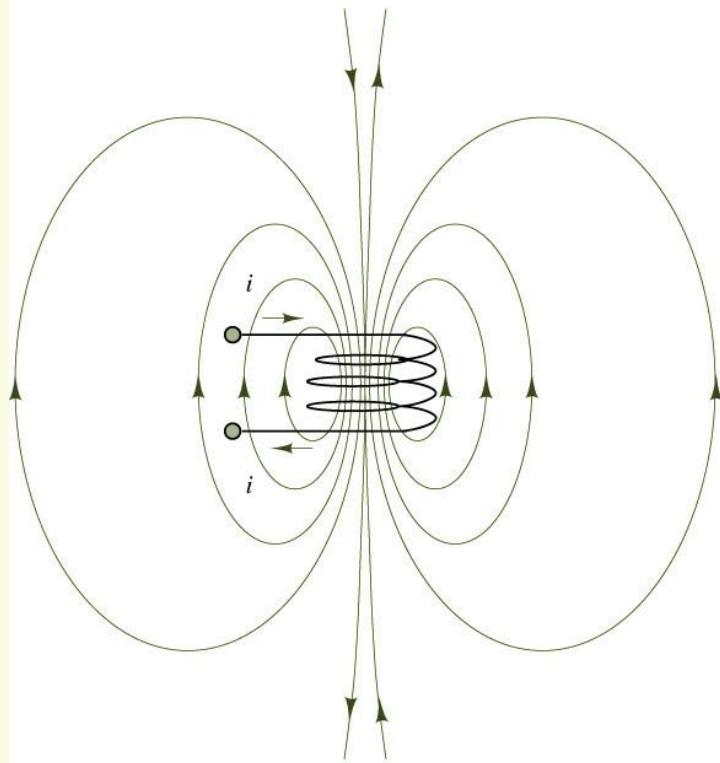

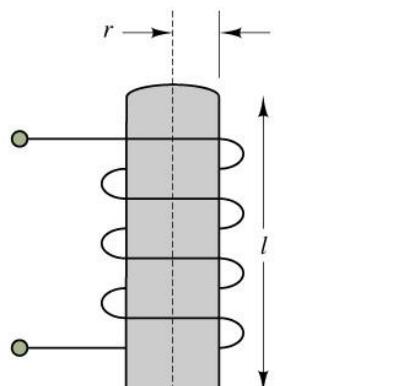(b) Magnetic flux lines in the vicinity of a current-carrying coil



Iron-core inductor

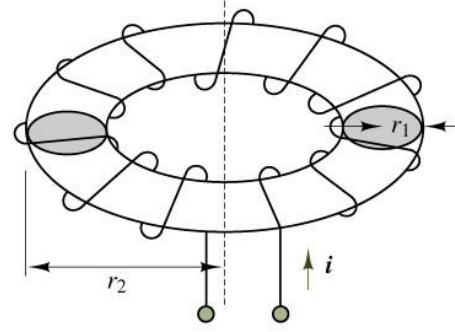

Toroidal inductor

(c) Practical inductors

$$V = L \frac{di}{dt}$$





$$i(t) =$$

# Observations from $v = L \frac{di}{dt}$

- For DC current: inductor is a short circuit
- For  $v$  to be finite,  $i(t)$  must be continuous
- Typical units: mH ~ H


Inductor circuit is dual to Capacitor circuit

# Voltage/Current Source and Inductor

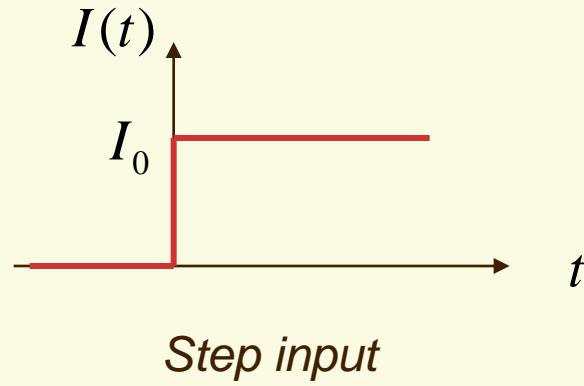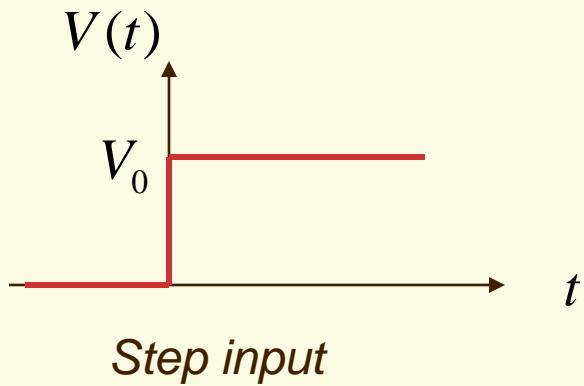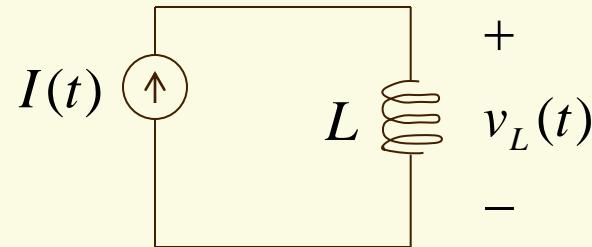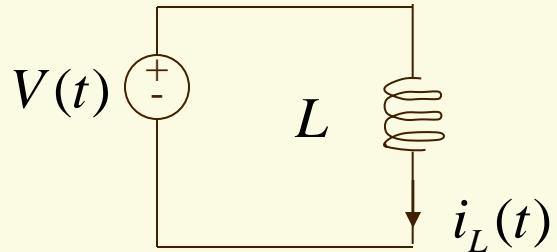


# Energy Storage in an Inductor

☰  $W_L = \frac{1}{2} L i_L^2$

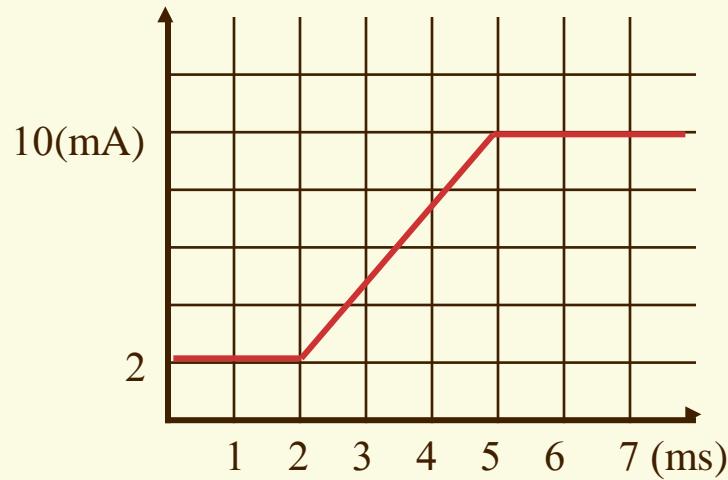

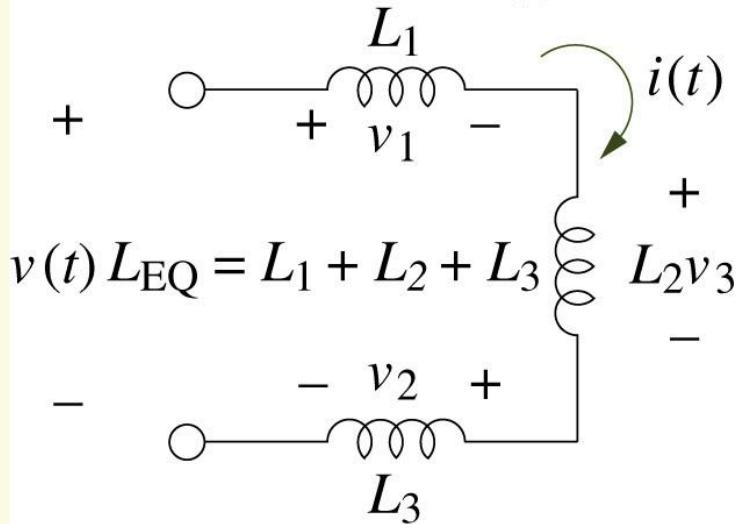
# Combining inductors in a circuit

Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.



Inductances in series add

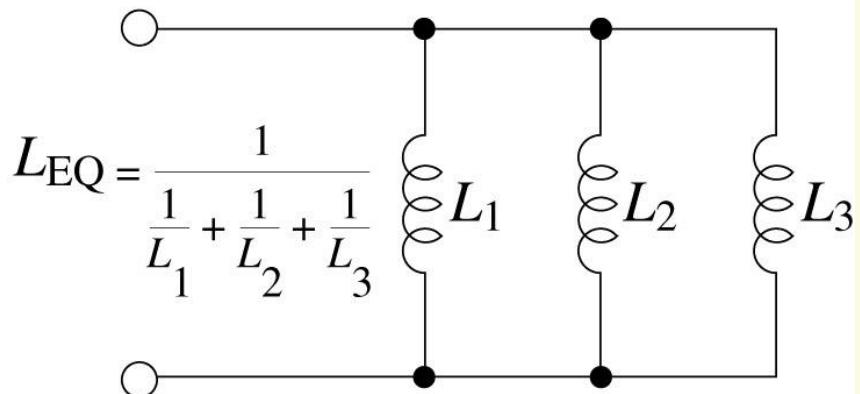


Inductances in parallel combine  
like resistors in parallel
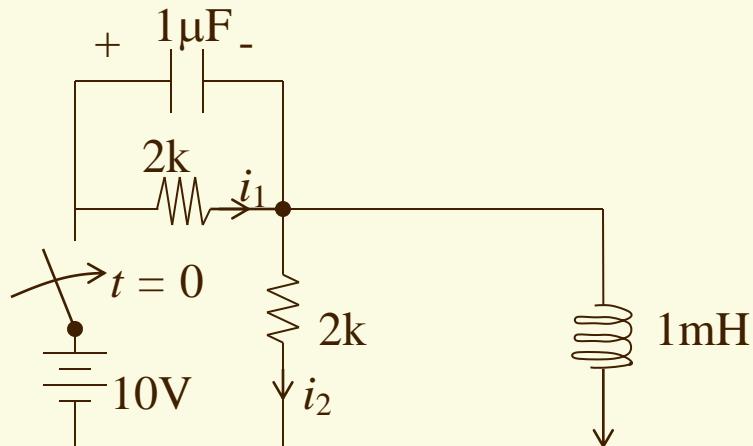
# Exercise





Switch is closed at  $t = 0$ . Find the following:

$$i_2(0+), \frac{dv_c}{dt}(0+), \frac{di_2}{dt}(0+)$$



$$v_c(0^-) = 5V, i_L(0^-) = 5mA$$


# Transformer

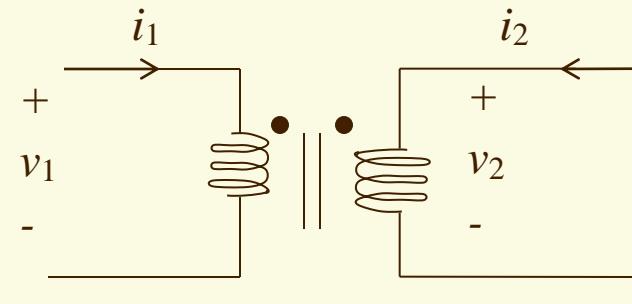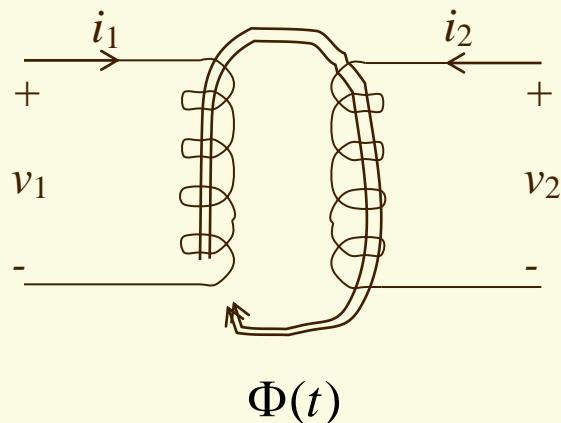

$N_1 : N_2$

$$\frac{v_1(t)}{N_1} = \frac{v_2(t)}{N_2}, \quad N_1 i_1(t) = -N_2 i_2(t)$$

# Transformer Circuit

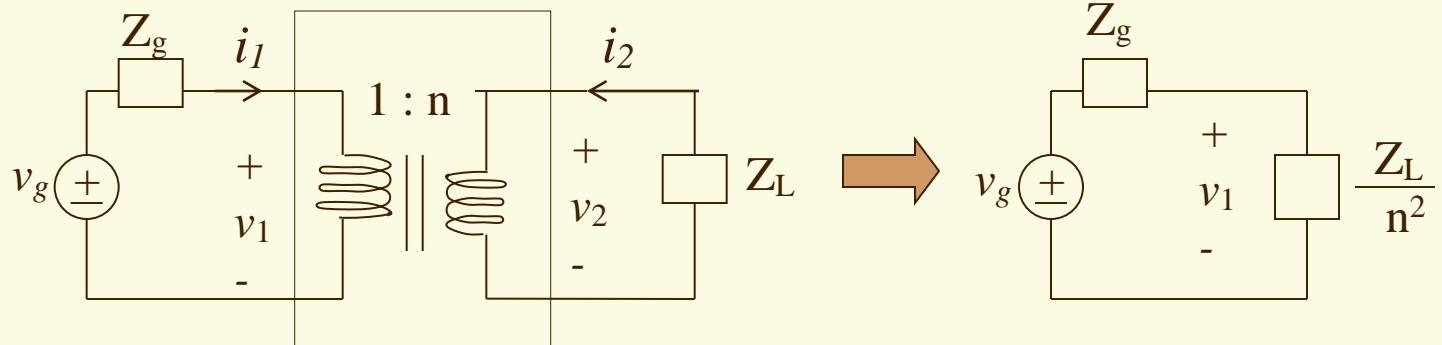

# Chap. 10 First-Order Transients in Linear Electrical Networks

Analysis of RC/RL Circuits

Intuitive Analysis

Propagation Delay


State and State Variables

Additional Examples

Digital Memory

# Simple RC Circuit: Series RC Circuit

Thévenin Equivalent:

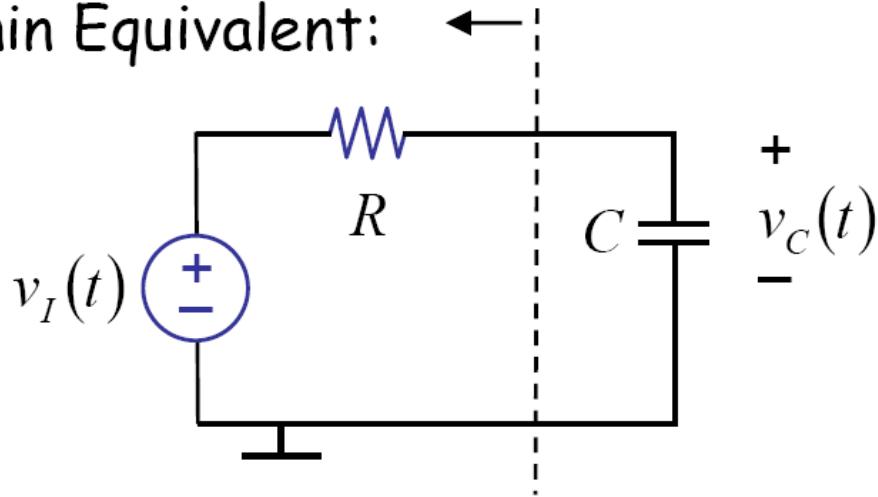

$$\frac{v_C - v_I}{R} + C \frac{dv_C}{dt} = 0$$

$$v_C(t) = v_{CH}(t) + v_{CP}(t)$$


$$(RC) \frac{dv_C}{dt} + v_C = v_I$$

total homogeneous particular

# Solutions

- Find the particular solution
- Find the form of homogeneous solution
- Use initial condition to obtain the total solution

< example >

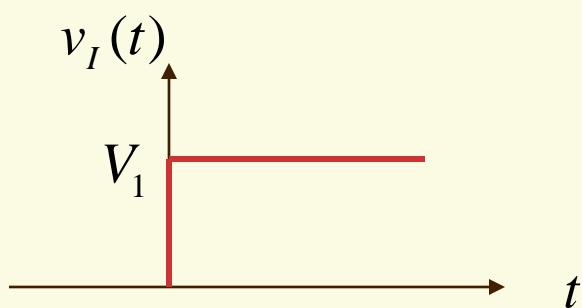


Particular Solution:
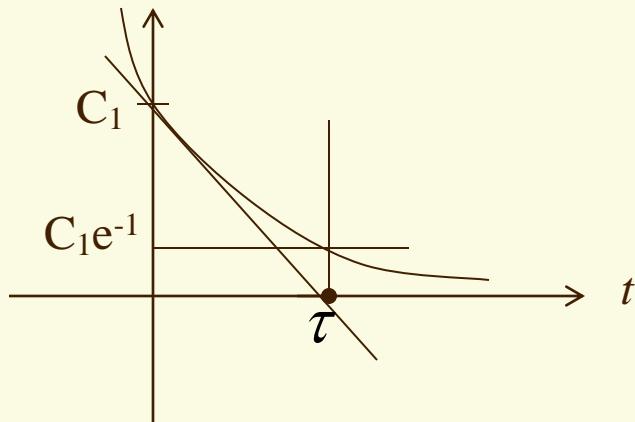
# Homogeneous Solution

General Form:  $v_{CH}(t) = Ae^{st}$

$$v_{CH}(t) = Ae^{-t/RC} = Ae^{-t/\tau}$$



Time constant:  $\tau = RC$


# Total Solution

☰ Assume the following initial condition

Given,  $v_C = V_0$  at  $t = 0$


☰ The total solution becomes

## Total Solution (2)

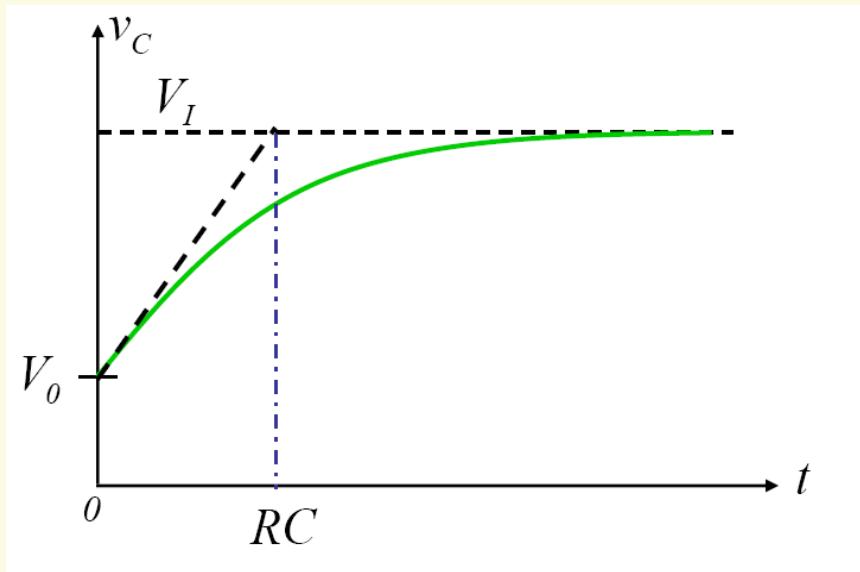

General form:  $x(t) = [x(0+) - x(\infty)]e^{-\frac{t}{\tau}} + x(\infty) \quad t \geq 0$


# Response to Square Wave

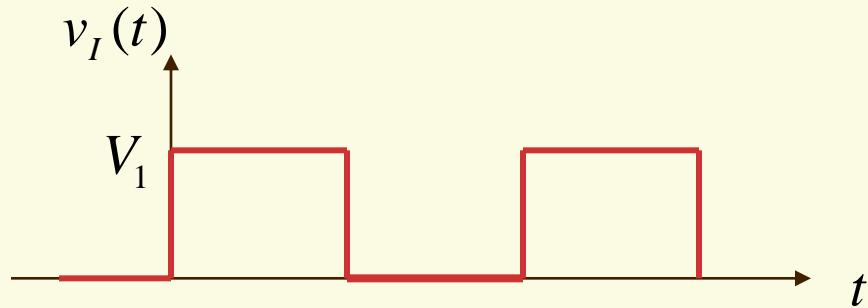

At steady state:
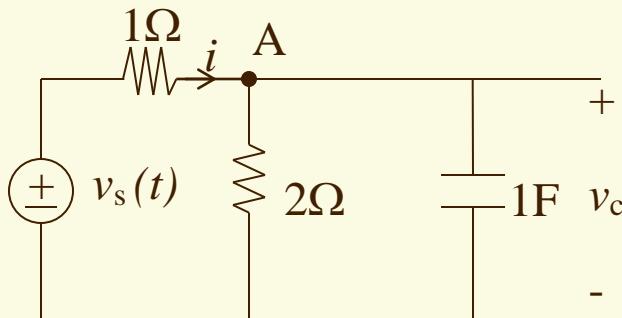
# Exercise

Find the differential equation to obtain  $v_c$



# DC Steady state

☰ DC voltage or DC current source

☰ After a long time:


$$t \rightarrow \infty$$

☰ Capacitor: open circuit



☰ Inductor: closed circuit
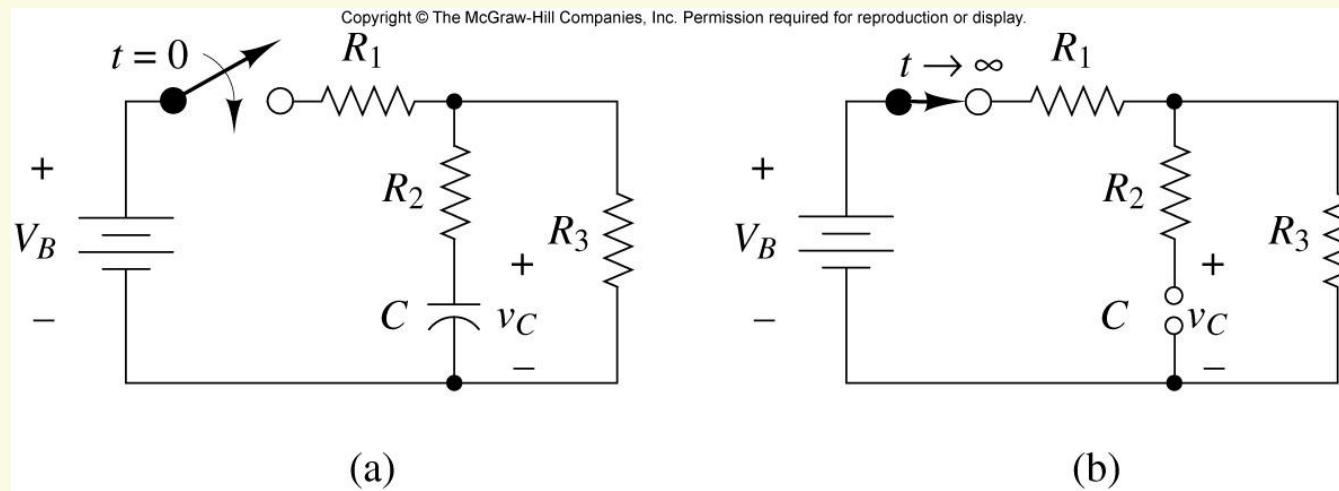
# Circuit Example

a long time after the switch is closed: final solution




# Parallel RC Circuit: Do it yourself !

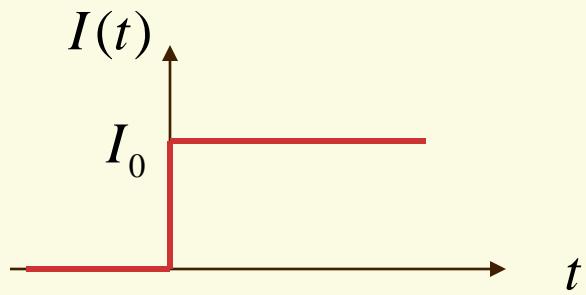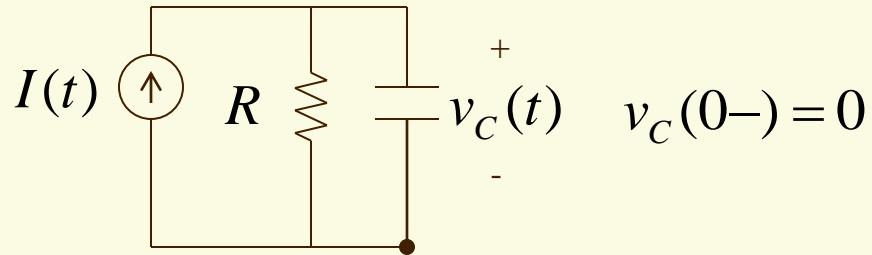


*Step input*

# RC Transient

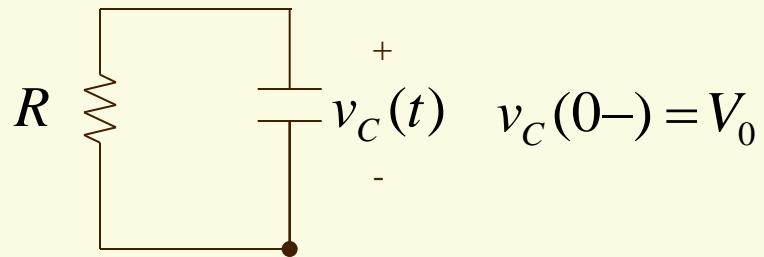
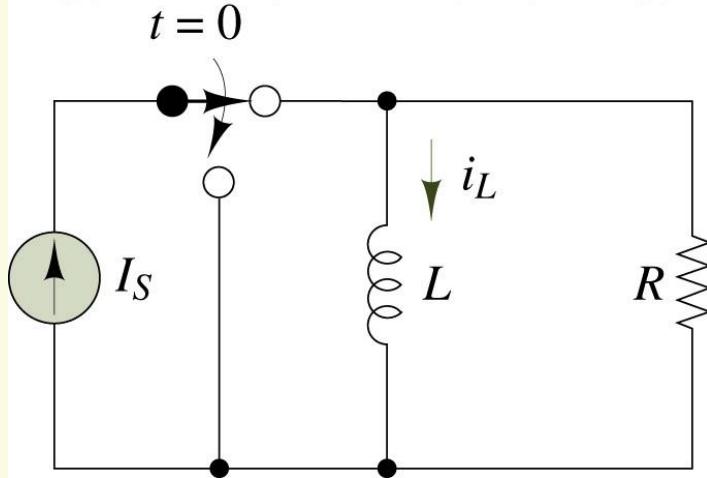
# Exercise






Copyright © The McGraw-Hill Companies, Inc. Permission required for reproduction or display.




$$i_S = 10mA$$

Find  $i_L$  at  $t = 0+$  and  $t \rightarrow \infty$

# Digital Logic Again

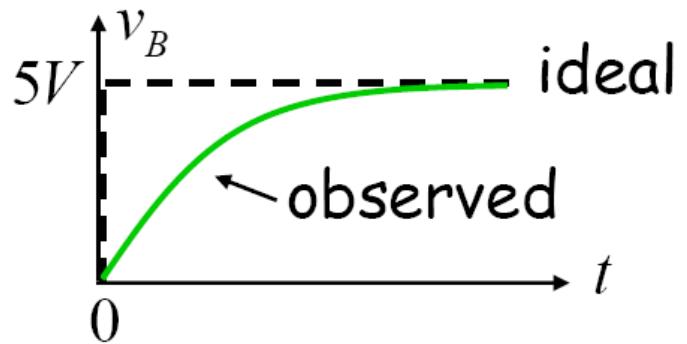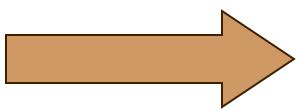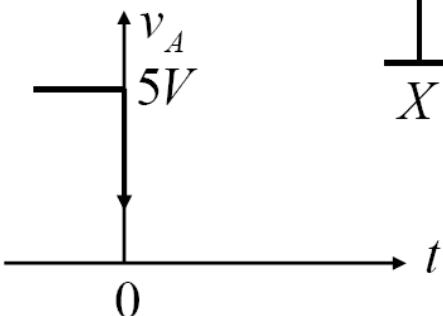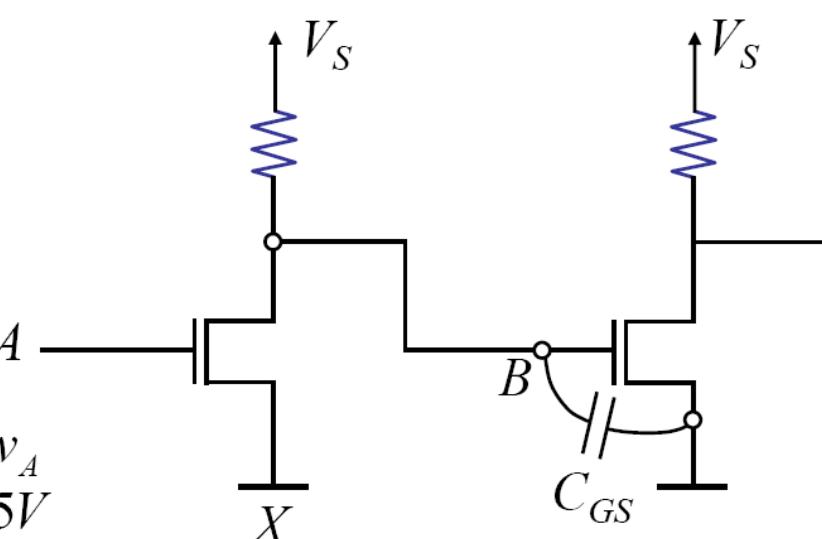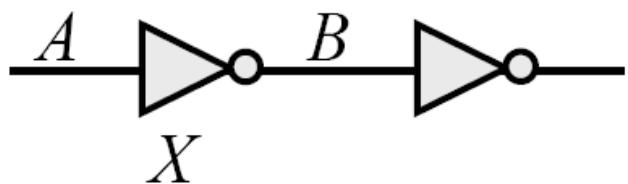


# Propagation Delay

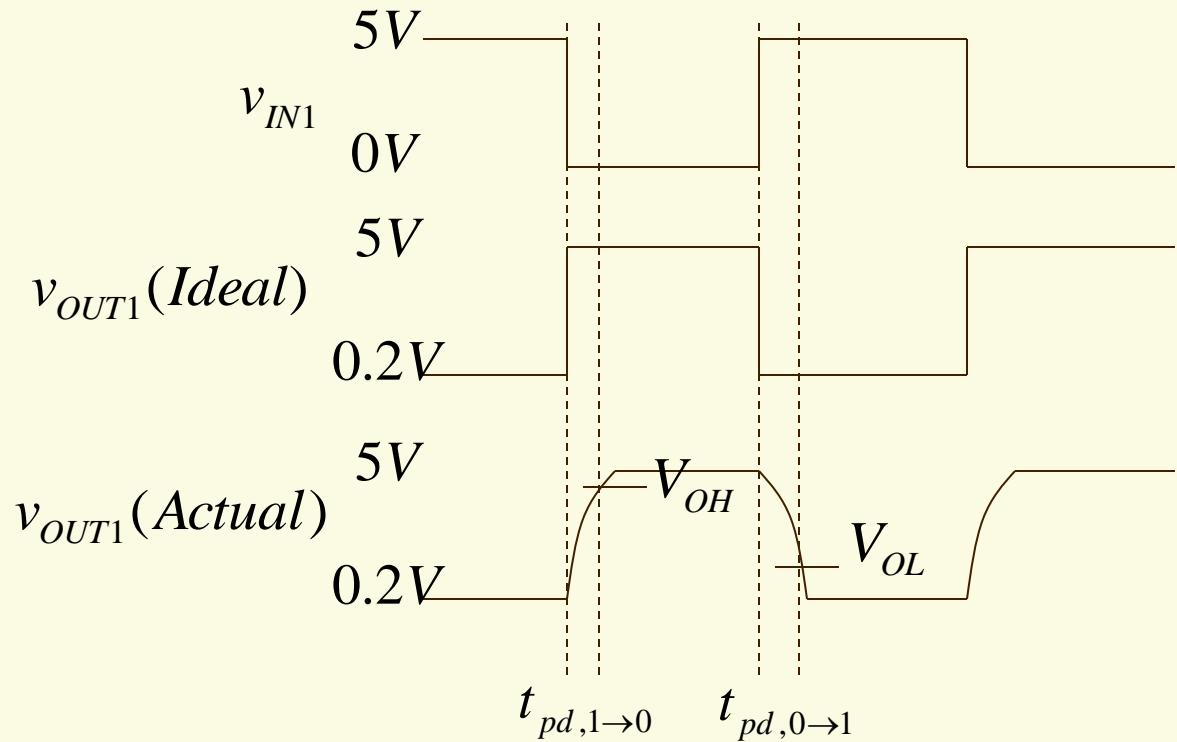

Propagation delay  $t_{pd} = \max(t_{pd,1 \rightarrow 0}, t_{pd,0 \rightarrow 1})$


# Rise time (vs. Fall time)

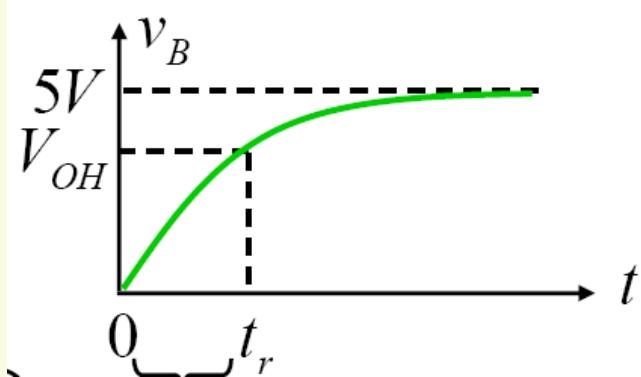

Rise time

( $V_{OL}$  to  $V_{OH}$ )

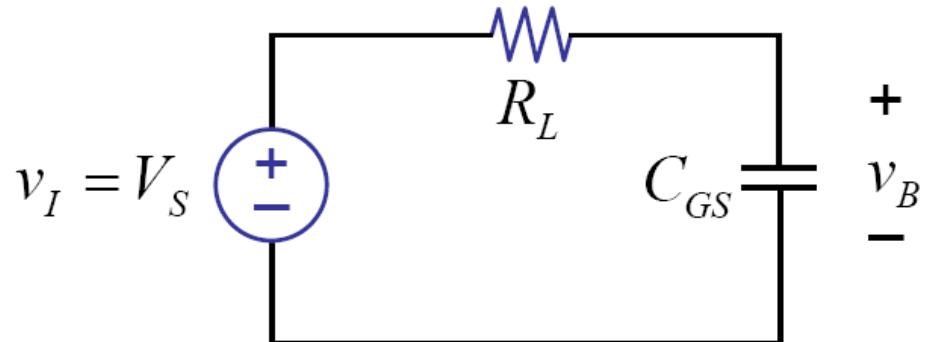Equivalent Circuit:  $t_{pd,1 \rightarrow 0}$



$$v_I = V_S \quad \text{for } t \geq 0$$
$$v_B(0) = 0$$

# Rise time Computation

$$v_B = V_S + (0 - V_S) e^{\frac{-t}{R_L C_{GS}}}$$

$v_B = V_{OH}$  at  $t = t_r$  ?

example


$$R_L = 1K$$

$$V_S = 5V$$


$$C_{GS} = 0.1 \text{ } pF$$

$$V_{OH} = 4V$$

# Fall Time: from the SRC Model

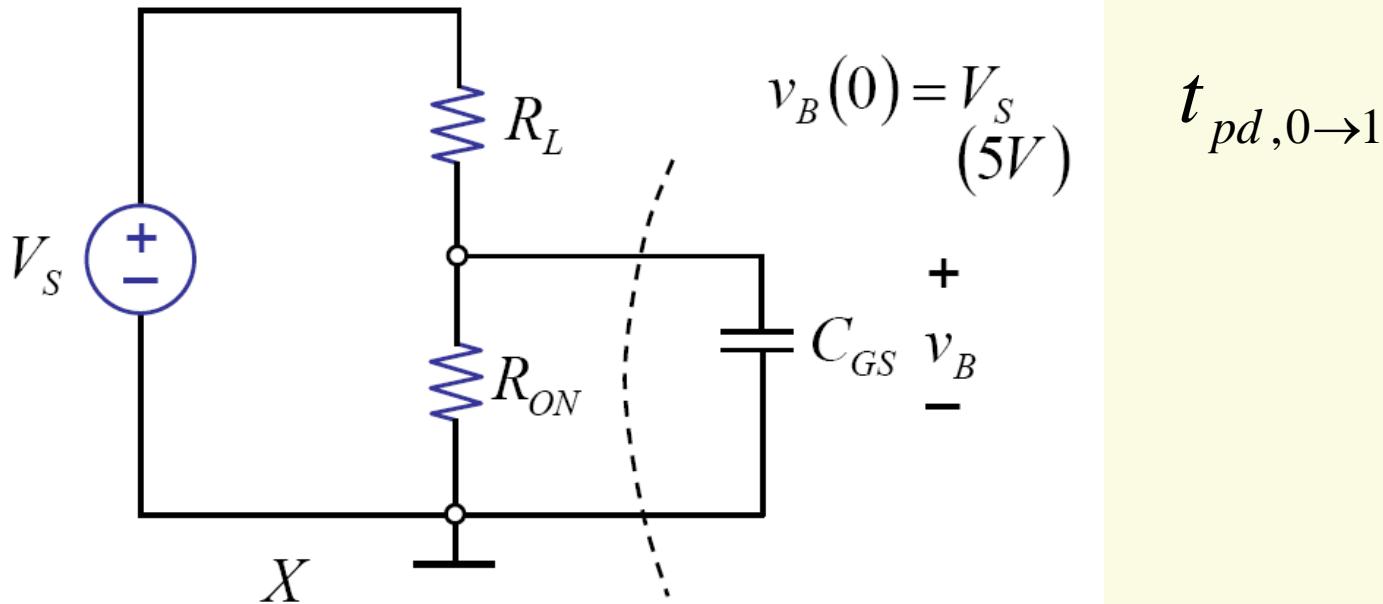

Thévenin replacement ...

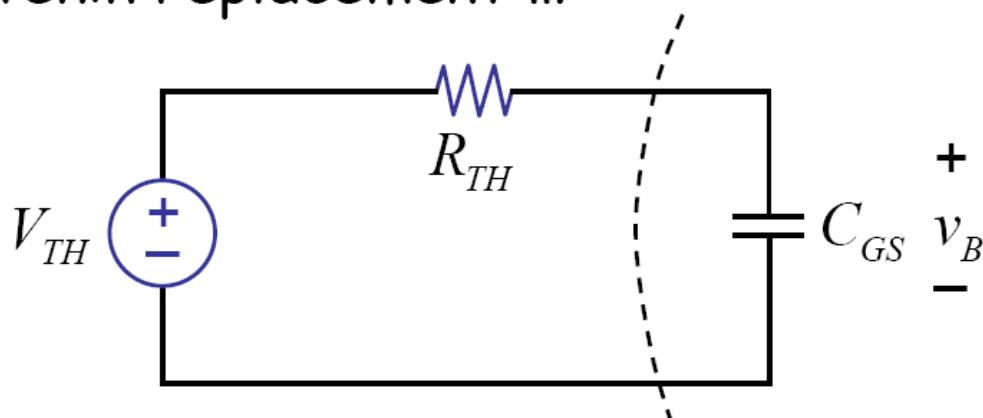

# Fall Time Computation

From 5V to  $V_{OL}$

$$V_{OL} = 1V, R_L = 10k\Omega, R_{ON} = 1k\Omega, C_{GS} = 0.1pF$$

# Propagation Delay Computation

$$t_{pd} = \max(t_{pd,1 \rightarrow 0}, t_{pd,0 \rightarrow 1})$$


$$R_L = 1K \quad V_S = 5V \quad R_{ON} = 10\Omega$$

$$C_{GS} = 0.1\text{ }pF \quad V_{OL} = 1V$$

# State and State variables
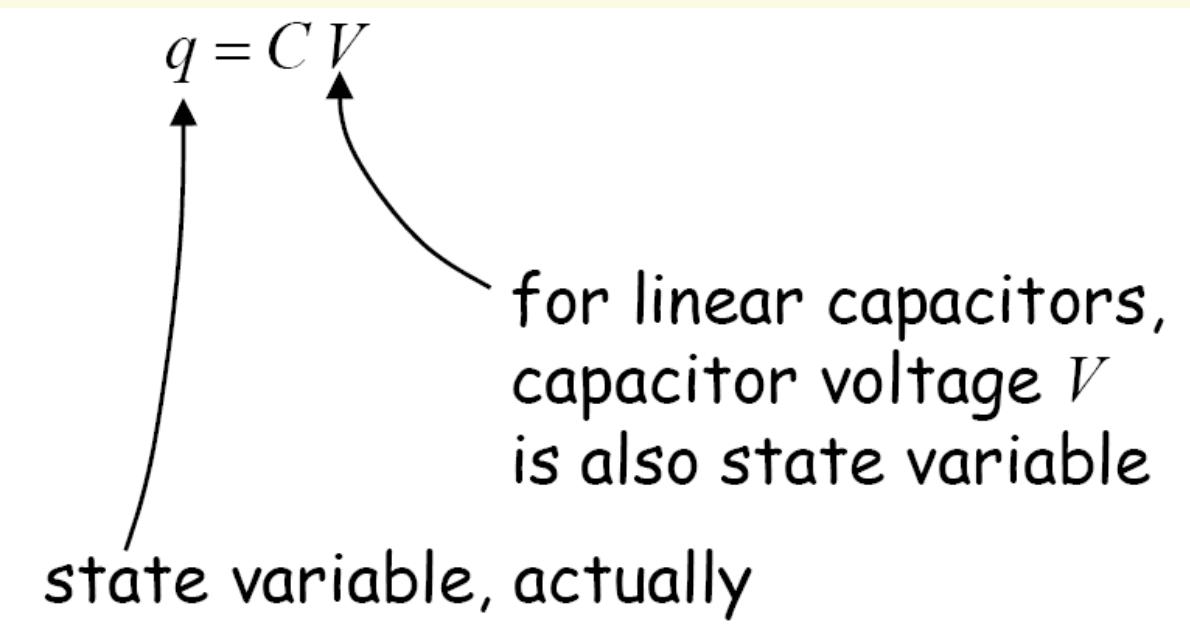
## State

- Summary of past inputs relevant to predicting the future



# Another Interpretation

$$\frac{dv_C}{dt} = -\frac{v_C}{RC} + \frac{v_I(t)}{RC}$$

$\frac{d}{dt}$  (state variable) =  $K_1$  (State variable present value) +  $K_2$  (input variable)

Total Solution = zero-input response + zero-state response

# Total Solution



$$\frac{dv_C}{dt} = -\frac{v_C}{RC} + \frac{v_I(t)}{RC}$$

Zero-input response:  $\frac{dv_C}{dt} = -\frac{v_C}{RC}$

Zero-state response:  $\frac{dv_C}{dt} = -\frac{v_C}{RC} + \frac{v_I(t)}{RC}$


# Ramp Input As an Example

Thévenin Equivalent:

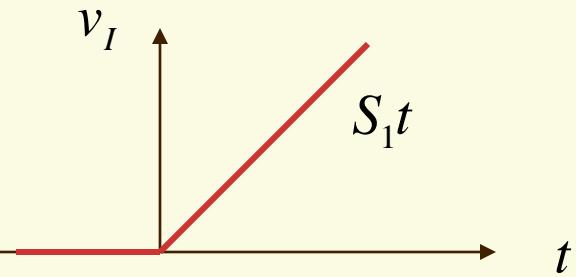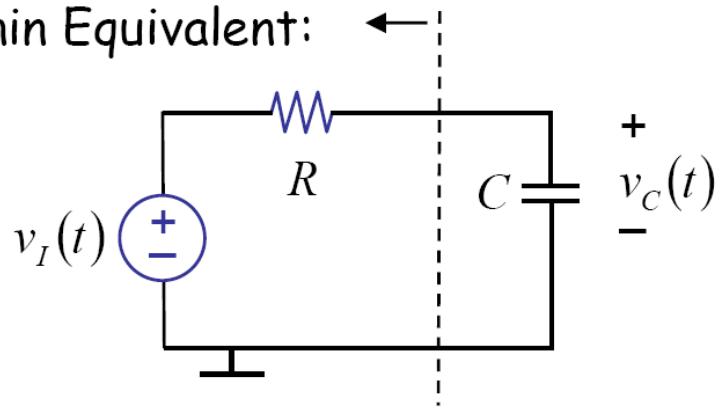

*Ramp input*

# Sine wave input


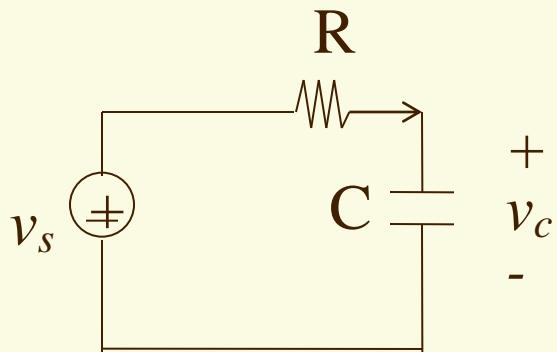


Sinusoidal signal waveform:

$$v_s(t) = V \cos(\omega t)$$

# Impulse Response

Thévenin Equivalent:

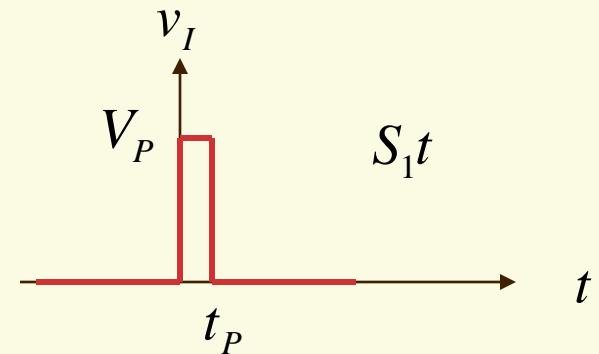
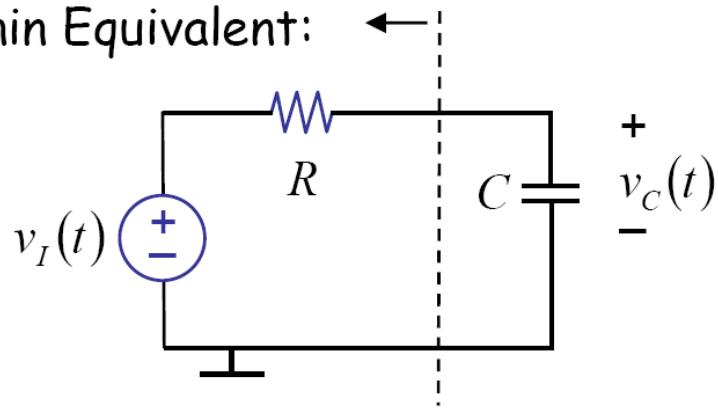


Pulse input  $\rightarrow$  impulse input



$$t_P \rightarrow 0, V_P t_p = A \Rightarrow A\delta(t)$$

# Memory Abstraction


A 1-bit memory element

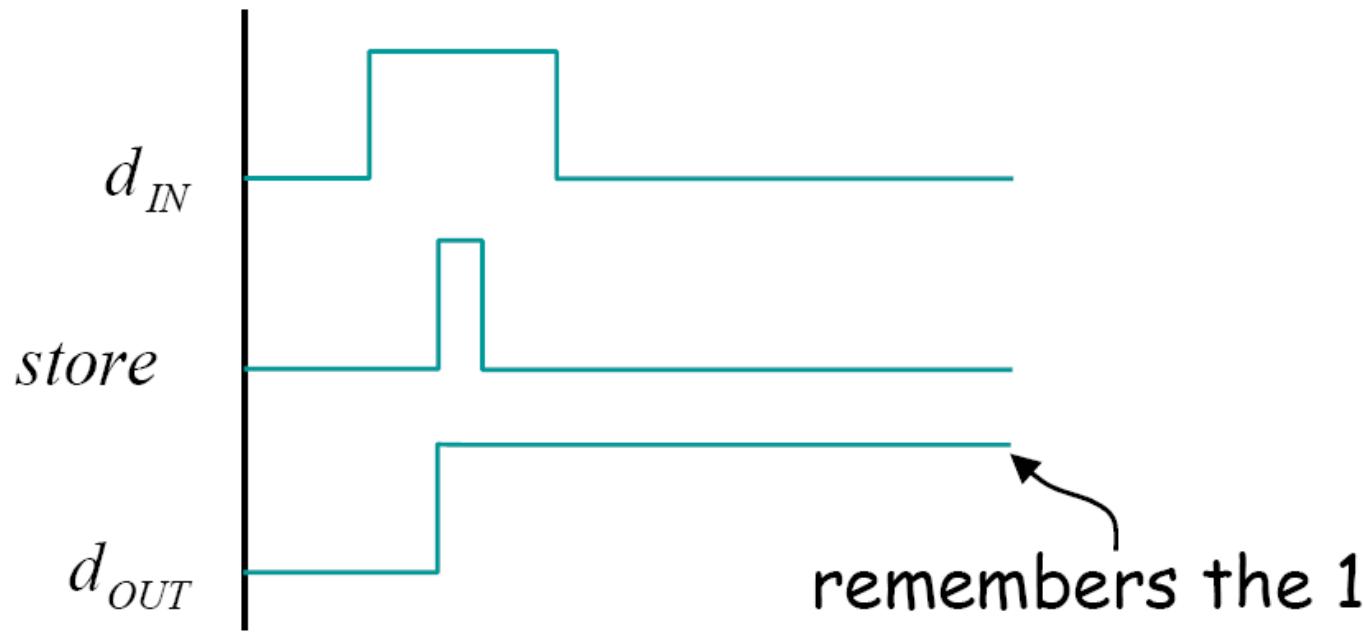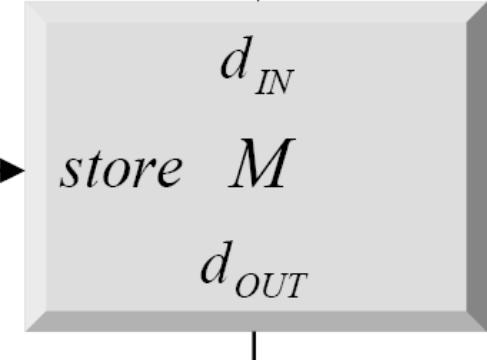

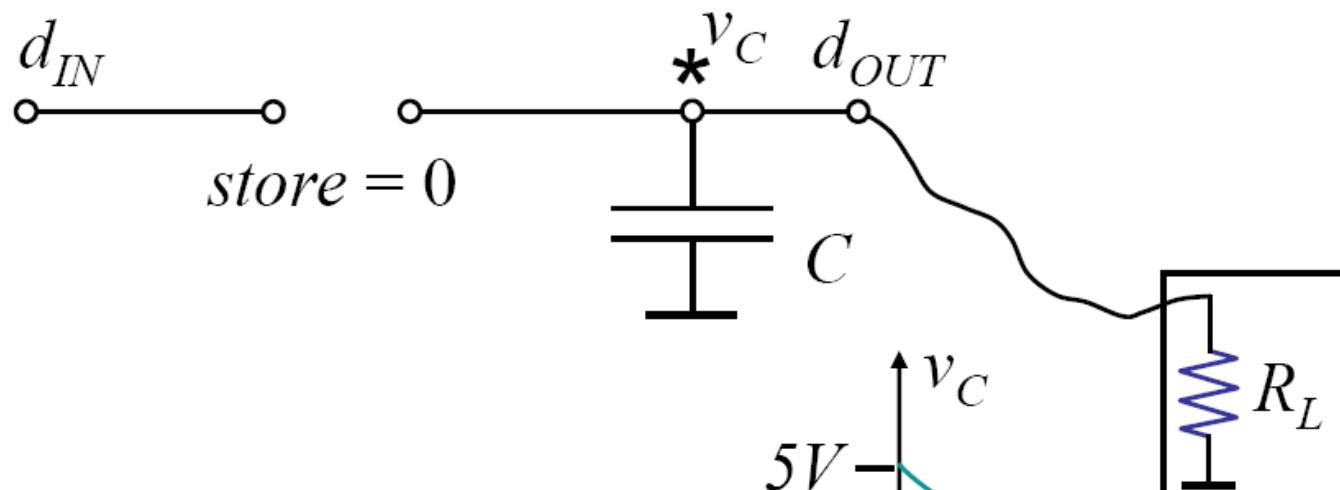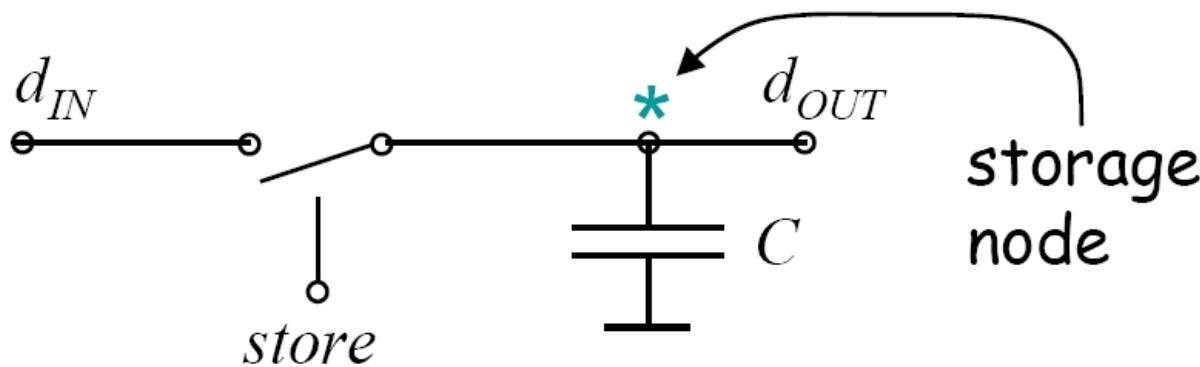
# Building a memory element: First Attempt



Stored value leaks away

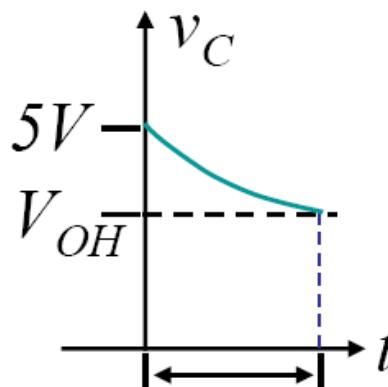


## Second Attempt: buffer

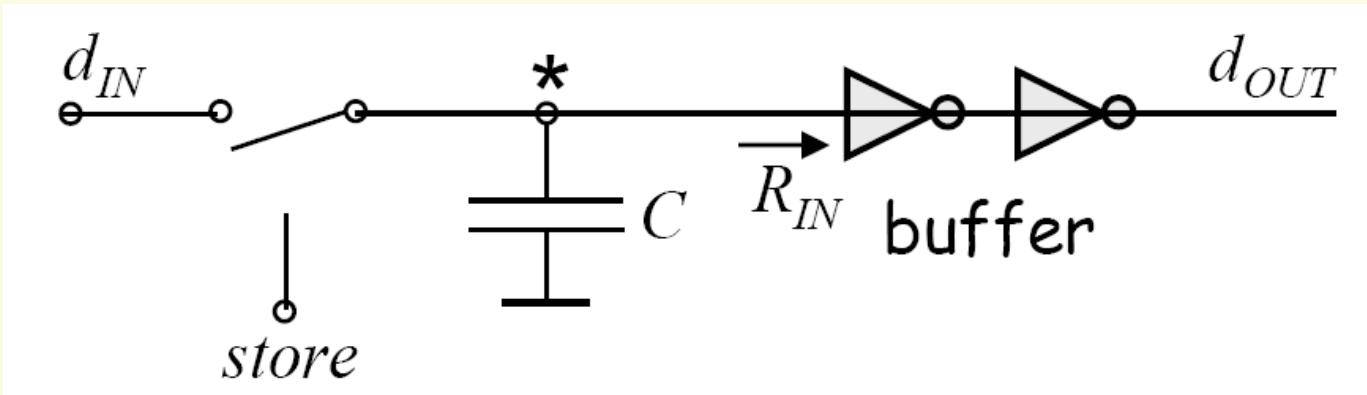


$R_{IN}$  is much larger than  $R_L$

# Third attempt: buffer + refresh

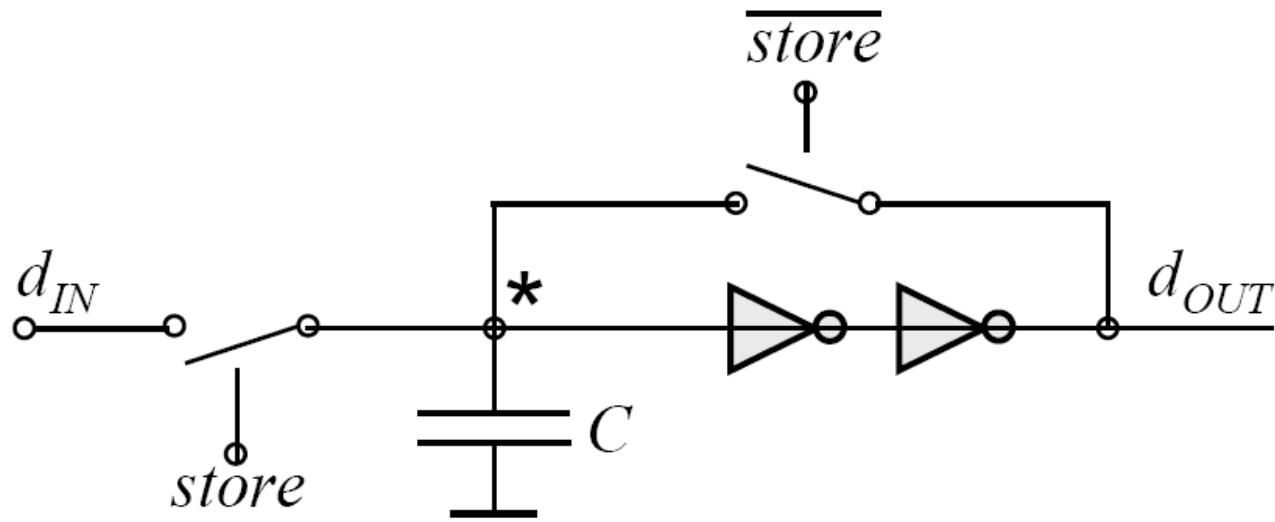

Does this work?

# Finally: buffer + decoupled refresh

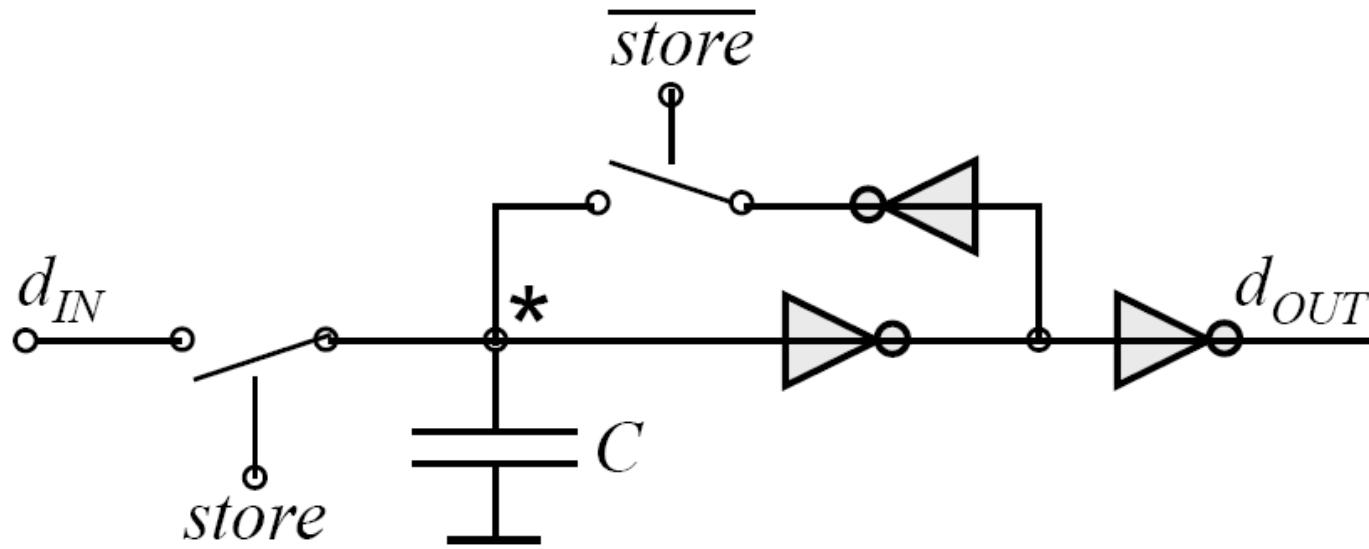

Refresh Period?

# Conclusion

## First order circuit

- Time constant
- DC steady state

## Propagation delay

- Rise time and fall time

## State and state variables

## Memory element