

Chapter 16: Design for Testability

Prof. Soo-Ik Chae

Objectives

After completing this chapter, you will be able to:



- ❖ Describe various fault models
- ❖ Understand the fundamentals of fault detection
- ❖ Understand the difficulties of sequential circuit tests
- ❖ Understand the basic principles of test vector generation
- ❖ Describe the basic principles of testable circuit design
- ❖ Understand the principle of boundary scan standard (IEEE1149.1)

Terminology Definition

- ❖ A **defect** means the unintended difference between the implemented hardware and its design.
 - Process defects
 - Material defects
 - Age defects
 - Package defects
- ❖ An **error** is the wrong output signal produced by a defective circuit.
- ❖ A **fault** is a representation of a defect at an abstracted function level.

Fault Models --- Stuck-at/Bridge Faults

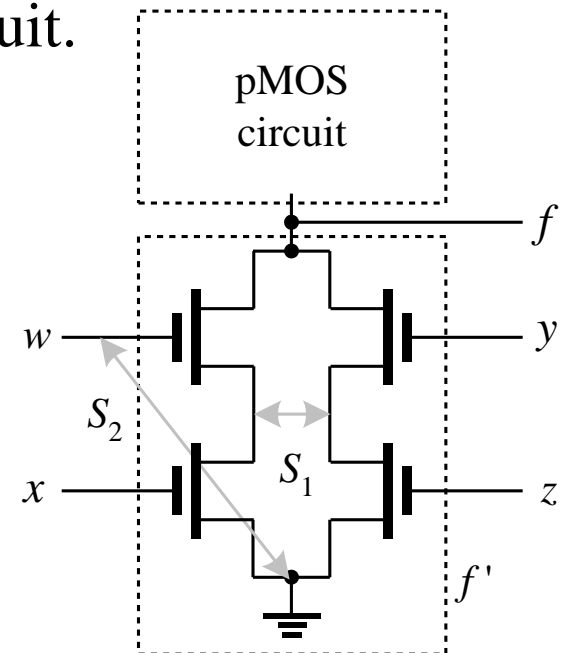 
- ❖ The most common fault models used today:
 - A **stuck-at-0** fault is modeled by assigning a fixed value of 0 to a signal line or net in the circuit.
 - A **stuck-at-1** fault is modeled by assigning a fixed value of 1 to a signal line or net in the circuit.
 - A **bridge fault** is a shorting between any set of lines (nets).



Fault Models --- Stuck-Open/Closed Faults

- A stuck-open fault is modeled as a switch being permanently in open state.
- A stuck-closed (stuck-on) fault is modeled as a switch being permanently in shorted state.

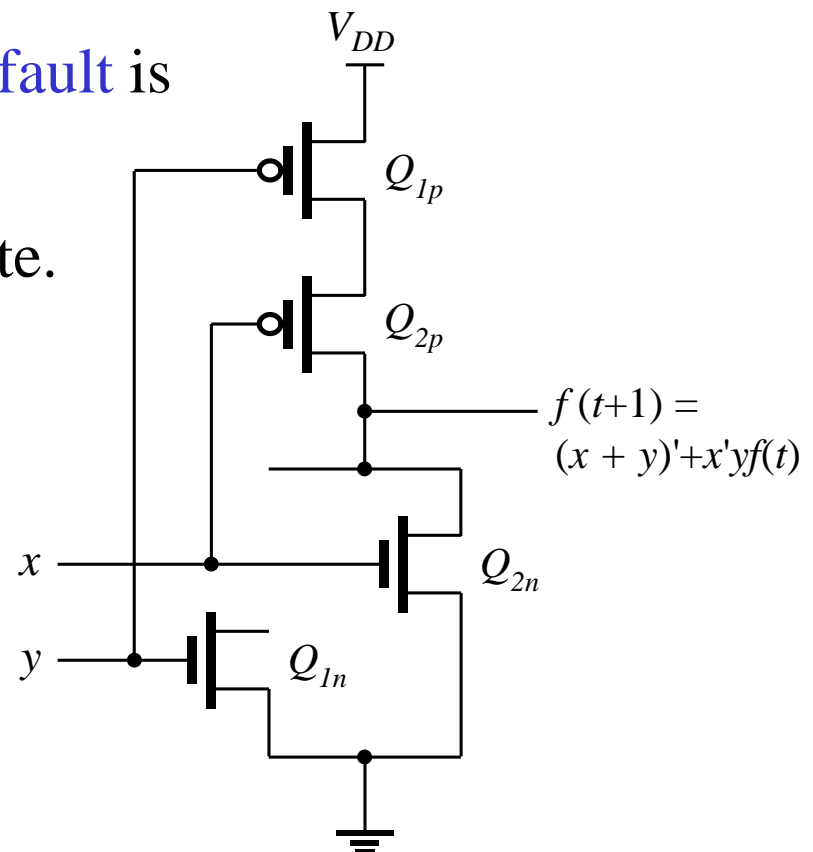- The effect of stuck-open fault is to produce a floating state at the output of the faulty logic circuit.
- The effect of stuck-closed fault is produce a power supply to ground conducting path.



Fault Equivalence/Collapse/Coverage


- ❖ **Fault equivalence** means two faults of a logic circuit transform the circuit such that two faulty circuits have the same output functions.
- ❖ **Fault collapse** means the process to select one fault from each equivalence set.

$$\text{Collapse ratio} = |\text{set of collapsed faults}| / |\text{set of faults}|$$

- ❖ To achieve a world-class quality level, the fault coverage of a circuit has in excess of 98.5%.


$$\text{Fault coverage} = \text{number of detected faults} / \text{total number of faults}$$

Defect level

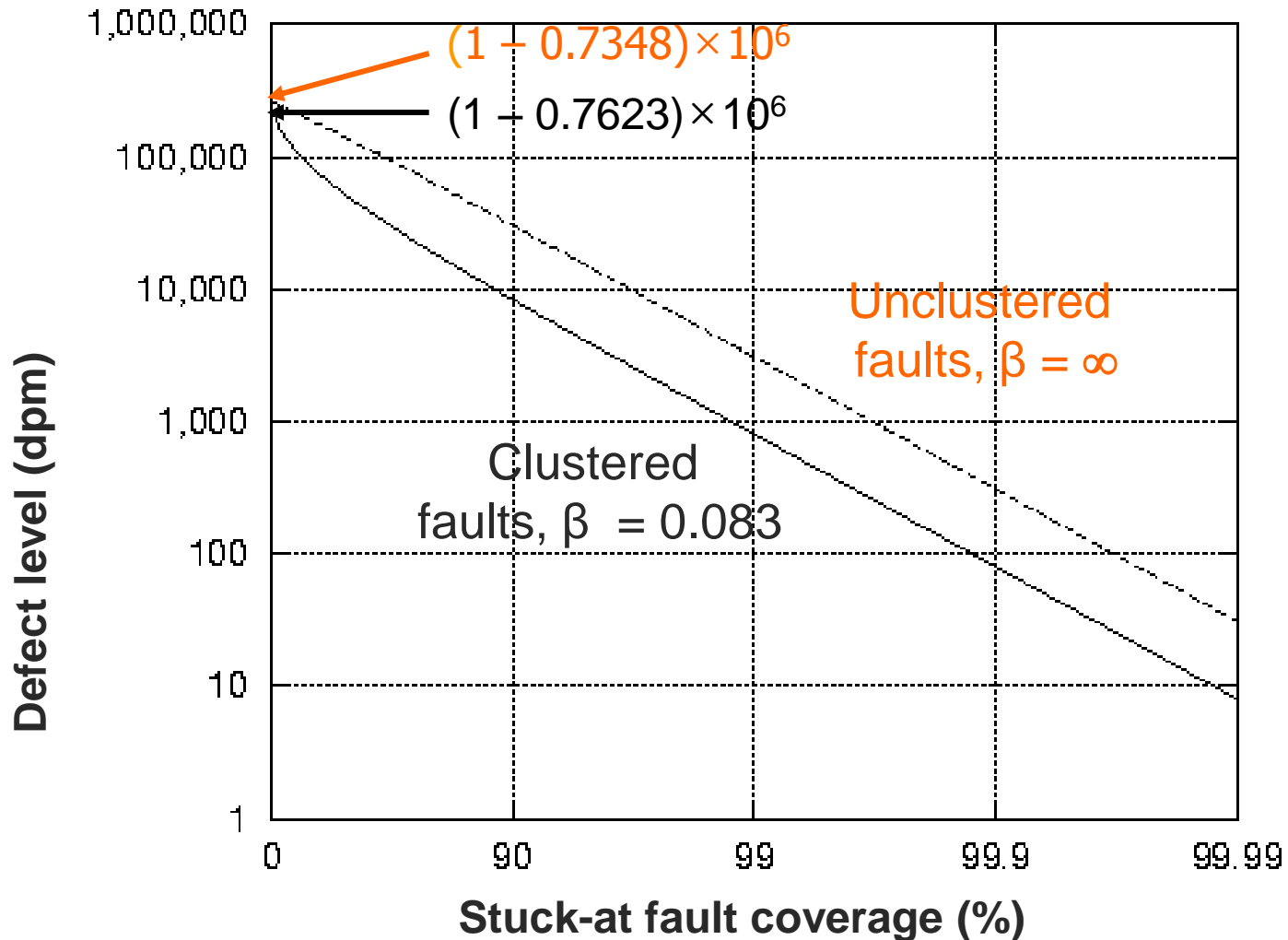


Fault Detection --- A Basic Model of CUT

 - ❖ The **controllability** of a particular node in a logic circuit is a measure of the ease of setting the node to a 1 or a 0 from the inputs.
- ❖ The **observability** of a particular node in a logic circuit is the degree to which you can observe the node at the outputs.




Fault Detection --- Detectable and Undetectable Faults

 
- ❖ A **testable fault** means that at least one input assignments can be found to make the outputs different between the fault-free and faulty circuits.
- ❖ An **untestable fault** means a fault for which no test can be found.
 - A **redundant** gate will cause some nets associated with it to be untestable.



 Fault Detection --- An Example of Complete Test Set



(a)

 

(b)

a	b	f_{fault_free}	f_{faulty}	Detectable faults
0	0	1	0	$\gamma/0$
0	1	1	0	$\alpha/1, \gamma/0$
1	0	1	0	$\beta/1, \gamma/0$
1	1	0	1	$\alpha/0, \beta/0, \gamma/1$

(c)

- ❖ With test vectors of $\{(0,1), (1,0), (1,1)\}$, all stuck-at faults can be tested.

Difficulty of Sequential Circuit Test

- ❖ Verification of state table
 - Transfer the machine into a known state: a homing sequence
 - Test all transitions from that state

- ❖ Verify each transition by first taking the machine to a specific **initial** state, applying the input to perform the transition and then verifying the **final** state.

Homing Sequence


- ❖ A **homing sequence** is an input sequence that produces an output response that **uniquely** indicates the state of a machine after the homing sequence has been applied.
- ❖ A **preset homing sequence** is a homing sequence that **does not employ the output response to determine subsequent inputs in the sequence.**

Example

<i>PS</i>	<i>NS, z</i>	
	<i>x</i> 0	1
<i>A</i>	<i>B,0</i>	<i>A,1</i>
<i>B</i>	<i>B,0</i>	<i>A,0</i>
<i>C</i>	<i>D,0</i>	<i>C,1</i>
<i>D</i>	<i>B,0</i>	<i>C,1</i>

Example: Homing Sequence


<i>PS</i>	<i>NS, z</i>	
	<i>x</i> 0	1
<i>A</i>	<i>B,0</i>	<i>A,1</i>
<i>B</i>	<i>B,0</i>	<i>A,0</i>
<i>C</i>	<i>D,0</i>	<i>C,1</i>
<i>D</i>	<i>B,0</i>	<i>C,1</i>

 

Initial state	Input sequence					
	00		01		11	
<i>A</i>	00	<i>B</i>	00	<i>A</i>	11	<i>A</i>
<i>B</i>	00	<i>B</i>	00	<i>A</i>	01	<i>A</i>
<i>C</i>	00	<i>B</i>	01	<i>C</i>	11	<i>C</i>
<i>D</i>	00	<i>B</i>	00	<i>A</i>	10	<i>C</i>

Difficulty of Sequential Circuit Test

<i>PS</i>	<i>NS, z</i>	
	<i>x</i> 0	1
<i>A</i>	<i>B</i> ,0	<i>A</i> ,1
<i>B</i>	<i>B</i> ,0	<i>A</i> ,0
<i>C</i>	<i>D</i> ,0	<i>C</i> ,1
<i>D</i>	<i>B</i> ,0	<i>C</i> ,1

 

Initial state	Input sequence					
	00		01		11	
<i>A</i>	00	<i>B</i>	00	<i>A</i>	11	<i>A</i>
<i>B</i>	00	<i>B</i>	00	<i>A</i>	01	<i>A</i>
<i>C</i>	00	<i>B</i>	01	<i>C</i>	11	<i>C</i>
<i>D</i>	00	<i>B</i>	00	<i>A</i>	10	<i>C</i>

Difficulty of Sequential Circuit Test

- ❖ A **transfer sequence** for state S_i and S_j of a sequential machine is the **shortest input sequence** that will take the machine from state S_i to S_j .
- ❖ A circuit is **strongly connected** if and only if there exists for **each ordered pair of states** (S_i, S_j) of the circuit an input sequence that will transfer the circuit from state S_i to S_j .
- ❖ So what are the **difficulties** of testing sequential circuits?

Sequential Circuit Test

- ❖ For a strongly connected state diagram, a proper sequence can transfer the state diagram from one to another state.

- ❖ What if not strongly connected?
 - Difficult to test it


- ❖ Adding extra circuit that directly sets the state of the circuit.

Test Vector Generation

- ❖ Four basic test vector generation approaches:
 - Fault tables
 - Fault simulation
 - Boolean differences
 - Path sensitization

Fault Tables

 - ❖ A fault table is a table that displays a set of faults and a set of test inputs.



x	y	z	f	f_{x0}	f_{x1}	f_{y0}	f_{y1}	f_{z0}	f_{z1}	f_{a0}	f_{a1}	f_{f0}	f_{f1}
0	0	0	1	1	1	1	1	1	0	1	0	0	1
0	0	1	0	0	0	0	0	1	0	0	0	0	1
0	1	0	1	1	0	1	1	1	0	1	0	0	1
0	1	1	0	0	0	0	0	1	0	0	0	0	1
1	0	0	1	1	1	1	0	1	0	1	0	0	1
1	0	1	0	0	0	0	0	1	0	0	0	0	1
1	1	0	0	1	0	1	0	0	0	1	0	0	1
1	1	1	0	0	0	0	0	0	0	0	0	0	1

Truth table

Single stuck-at-fault truth table

Fault Tables

- ❖ A fault detection table is a table that identifies which input combinations detect a certain faults.
 - It is formed by performing the XOR of each output column in fault table with the output of fault-free circuit.

x	y	z	f	x_0	x_1	y_0	y_1	z_0	z_1	a_0	a_1	f_0	f_1
0	0	0	1	0	0	0	0	0	1	0	1	1	0
0	0	1	0	0	0	0	0	1	0	0	0	0	1
0	1	0	1	0	1	0	0	0	1	0	1	1	0
0	1	1	0	0	0	0	0	1	0	0	0	0	1
1	0	0	1	0	0	0	1	0	1	0	1	1	0
1	0	1	0	0	0	0	0	1	0	0	0	0	1
1	1	0	0	1	0	1	0	0	0	1	0	0	1
1	1	1	0	0	0	0	0	0	0	0	0	0	1

May delete two rows

Equivalent faults

Equivalent faults

Fault Tables

- ❖ A reduced fault table is a fault table that combines equivalent faults and deletes the redundant rows in the fault detection table.

x	y	z	f	\hat{g}	\hat{x}_1	\hat{y}_1	\hat{z}_0	\hat{h}	\hat{f}_1
0	0	0	1	0	0	0	0	1	0
0	0	1	0	0	0	0	①	0	1
0	1	0	1	0	①	0	0	1	0
1	0	0	1	0	0	①	0	1	0
1	1	0	0	①	0	0	0	0	1
1	1	1	0	0	0	0	0	0	1


$$g = \{x_0, y_0, a_0\}$$

$$h = \{z_1, a_1, f_0\}$$

- ❖ The test vectors are: $\{(0,0,1), (0,1,0), (1,0,0), (1,1,0)\}$.

Fault Simulation

 - ❖ The basic concept of fault simulation approach to test pattern generation is to select a primary input combination and determine its fault detection capabilities by simulation. The process is repeated until:
 - All faults are covered,
 - At least an acceptable number of faults are covered, **or**
 - Some predefined stopping point is reached.




Fault Simulation

❖ Types of fault simulation:

- The row method
- The column method

Fault Simulation

❖ The row method

 

x	y	z	f	f_{x0}	f_{x1}	f_{y0}	f_{y1}	f_{z0}	f_{z1}	f_{a0}	f_{a1}	f_{f0}	f_{f1}	Faults detected
0	0	0	1	1	1	1	1	1	0	1	0	0	1	$z1, a1, f0$
0	0	1	0	0	0	0	0	1	*	0	*	*	1	$z0, f1$
0	1	0	1	1	0	1	1	*	*	1	*	*	*	$x1$
0	1	1	0	0	*	0	0	*	*	0	*	*	*	
1	0	0	1	1	*	1	0	*	*	1	*	*	*	$y1$
1	0	1	0	0	*	0	*	*	*	0	*	*	*	
1	1	0	0	1	*	1	*	*	*	1	*	*	*	$x0, y0, a0$
1	1	1	0	*	*	*	*	*	*	*	*	*	*	


Truth table

* --- not simulated for this input pattern.

❖ Test vectors = $\{(0,0,0), (0,0,1), (0,1,0), (1,0,0), (1,1,0)\}$.

Fault Simulation

❖ The column method

 

x	y	z	f	f_{x0}	f_{x1}	f_{y0}	f_{y1}	f_{z0}	f_{z1}	f_{a0}	f_{a1}	f_{f0}	f_{f1}	Faults detected
0	0	0	1	1	1	*	1	*	0	1	0	0	1	z1, a1, f0
0	0	1	0	0	0	*	0	*	*	0	*	*	1	f1
0	1	0	1	1	0	1	1	*	*	1	*	*	*	x1
0	1	1	0	0	*	0	0	*	*	0	*	*	*	
1	0	0	1	1	*	1	0	1	*	1	*	*	*	y1
1	0	1	0	0	*	0	*	1	0	0	*	*	*	z0
1	1	0	0	1	0	1	0	*	0	1	0	*	*	x0, y0, a0
1	1	1	0	*	0	*	0	*	0	*	0	*	*	

Truth table

* --- not simulated for this input pattern.

❖ Test vectors = $\{(0,0,0), (0,0,1), (0,1,0), (1,0,0), (1,0,1), (1,1,0)\}$.

Boolean Differences

- ❖ Boolean difference of a switching function $f(x_{n-1}, \dots, x_1, x_0)$ is defined as:

$$\begin{aligned}\frac{df(X)}{dx} &= f(x_{n-1}, \dots, x_{i+1}, 0, x_{i-1}, \dots, x_0) \oplus f(x_{n-1}, \dots, x_{i+1}, 1, x_{i-1}, \dots, x_0) \\ &= f_i(0) \oplus f_i(1)\end{aligned}$$

- Boolean difference sometimes is called Boolean partial derivative.
- Boolean difference is **not an effective way to compute test patterns for large circuits.**

Boolean Differences

❖ Example: $f(X) = x_1x_2 + x_3$

$$\begin{aligned}\frac{df(X)}{dx_1} &= (1 \cdot x_2 + x_3) \oplus (0 \cdot x_2 + x_3) = (x_2 + x_3) \oplus x_3 \\ &= (x_2 + x_3)'x_3 + (x_2 + x_3)x_3' = x_2x_3'\end{aligned}$$

❖ To test stuck-at-0 fault at net x_i , it is required to compute:

$$x_i \frac{df(X)}{dx_i} = 1$$


$x_i=1$ 일 때 output이 다른 경우가 test vector

❖ To test stuck-at-1 fault at net x_i , it is required to compute:

$$x_i' \frac{df(X)}{dx_i} = 1$$

$x_i=0$ 일 때 output이 다른 경우가 test vector

Boolean Differences

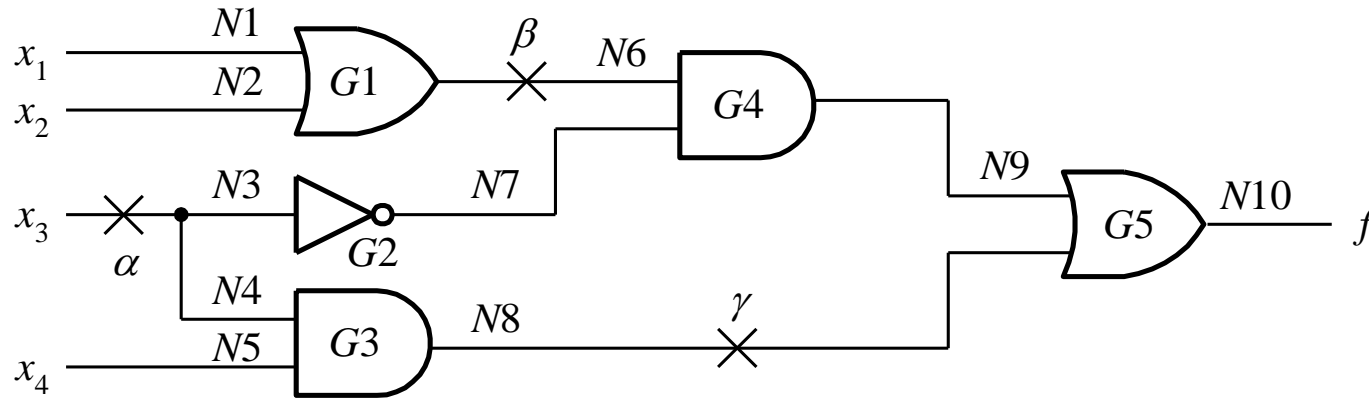


$$f(X) = (x_1 + x_2)x'_3 + x_3x_4$$

- ❖ Stuck-at-0 fault at net α is

$$\begin{aligned} x_3 \frac{df(X)}{dx_3} &= 1 = x_3 [f_3(0) \oplus f_3(1)] \\ &= x'_1 x'_2 x_3 x_4 + x_1 x_3 x'_4 + x_2 x_3 x'_4 \end{aligned}$$

- ❖ The test vector set is $\{(0, 0, 1, 1), (1, \phi, 1, 0), (\phi, 1, 1, 0)\}$.

Boolean Differences

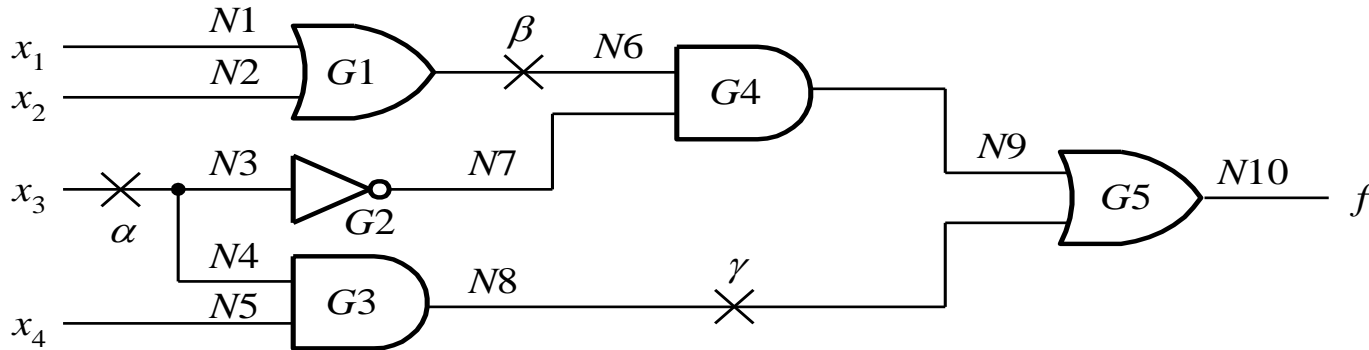

❖ Stuck-at-0 fault at net β is

$$y = x_1 + x_2$$

$$f(X, y) = yx'_3 + x_3x_4$$

$$y \cdot \frac{df(X, y)}{dy} = y[x_3x_4 \oplus (x'_3 + x_3x_4)] = yx'_3$$

$$= (x_1 + x_2)x'_3 = x_1x'_3 + x_2x'_3$$

❖ The test vector set is $\{(1, \phi, 0, \phi), (\phi, 1, 0, \phi)\}$.

Path Sensitization

- ❖ Basic operations of path sensitization method:
 - **Fault sensitization:** A stuck-at fault is activated by forcing the signal driving it to an opposite value from the fault value.
 - **Fault propagation:** The fault effect is propagated through one or more paths to a primary output of the circuit.
 - **Line justification (Consistency operation):** The internal signal assignments previously made to sensitize a fault or propagate its effect are justified by setting primary inputs of the circuit.


Path Sensitization

- ❖ Sensitized path is a path that can propagate the net value of the primary inputs with a consistency operation for a stuck-at-fault


- ❖ Otherwise, unsensitized path

Path Sensitization


❖ Sensitized path

 


❖ Unsensitized path

 

Path Sensitization

 

(a) Single sensitized path

 

(b) Multiple sensitized paths

A Simplified D Algorithm

- ❖ pdcf (primitive D -cube of fault) of the five most commonly used gates.

x	y	z	Faults covered
0	0	D'	$z/1$
0	1	D'	$x/1, z/1$
1	0	D'	$y/1, z/1$
1	1	D	$x/0, y/0, z/0$

(a) AND gate

x	y	z	Faults covered
0	0	D'	$x/1, y/1, z/1$
0	1	D	$x/0, z/0$
1	0	D	$y/0, z/0$
1	1	D	$z/0$

(b) OR gate

x	y	z	Faults covered
0	0	D	$z/0$
0	1	D	$x/1, z/0$
1	0	D	$y/1, z/0$
1	1	D'	$x/0, y/0, z/1$

(c) NAND gate

x	y	z	Faults covered
0	0	D	$x/1, y/1, z/0$
0	1	D'	$x/0, z/1$
1	0	D'	$y/0, z/1$
1	1	D'	$z/1$

(d) NOR gate

	z	Faults covered
0	D	$x/1, z/0$
1	D'	$x/0, z/1$

(e) NOT gate

A Simplified D Algorithm

❖ pdc (propagation of D-cube): error propagation

AND gate			OR gate			NAND gate			NOR gate			NOT gate	
x	y	z	x	y	z	x	y	z	x	y	z	x	z
D'	1	D'	D'	0	D'	D'	1	D	D	0	D'	D'	D
1	D'	D'	0	D'	D'	1	D'	D	0	D	D'		
D	1	D	D	0	D	D	1	D'	D	0	D'	D	D'
1	D	D	0	D	D	1	D	D'	0	D	D'		

❖ sc (singular cover): fixed output

AND gate			OR gate			NAND gate			NOR gate			NOT gate	
x	y	z	x	y	z	x	y	z	x	y	z	x	z
0	ϕ	0	1	ϕ	1	0	ϕ	1	1	ϕ	0	1	0
ϕ	0	0	ϕ	1	1	ϕ	0	1	ϕ	1	0	0	1
1	1	1	0	0	0	1	1	0	0	0	1		

A Simplified D Algorithm

❖ A simplified D algorithm

1. **Fault sensitization**: Select a **pdf** for the fault for which a test pattern is to be generated.
2. **D -drive**: Use **pdfs** to propagate the D signal to at least one primary outputs of the circuit.
3. **Consistency operations**: Use the **sc** of each logic module to perform the consistency operation.

Testable Circuit Design


- ❖ Testable circuit design is also called design for testability (DFT).
- ❖ Ad hoc testing
 - uses **some means** to increase both observability and controllability of the circuits.
- ❖ Scan-path methods
 - provide the observability and controllability at each register.
- ❖ Built-in self-test (BIST)
 - relies on augmenting circuits to allow them to perform operations so as to prove the correct operation of the circuit.

Ad hoc Testing

- ❖ Basic principles are to increase both the observability and controllability of circuits.
 - Providing more control and test points
 - Using multiplexers to increase the number of internal control and test points
 - Breaking feedback paths
 - Using state registers to reduce the additional of I/O pins required for testing signals.


Ad hoc Testing

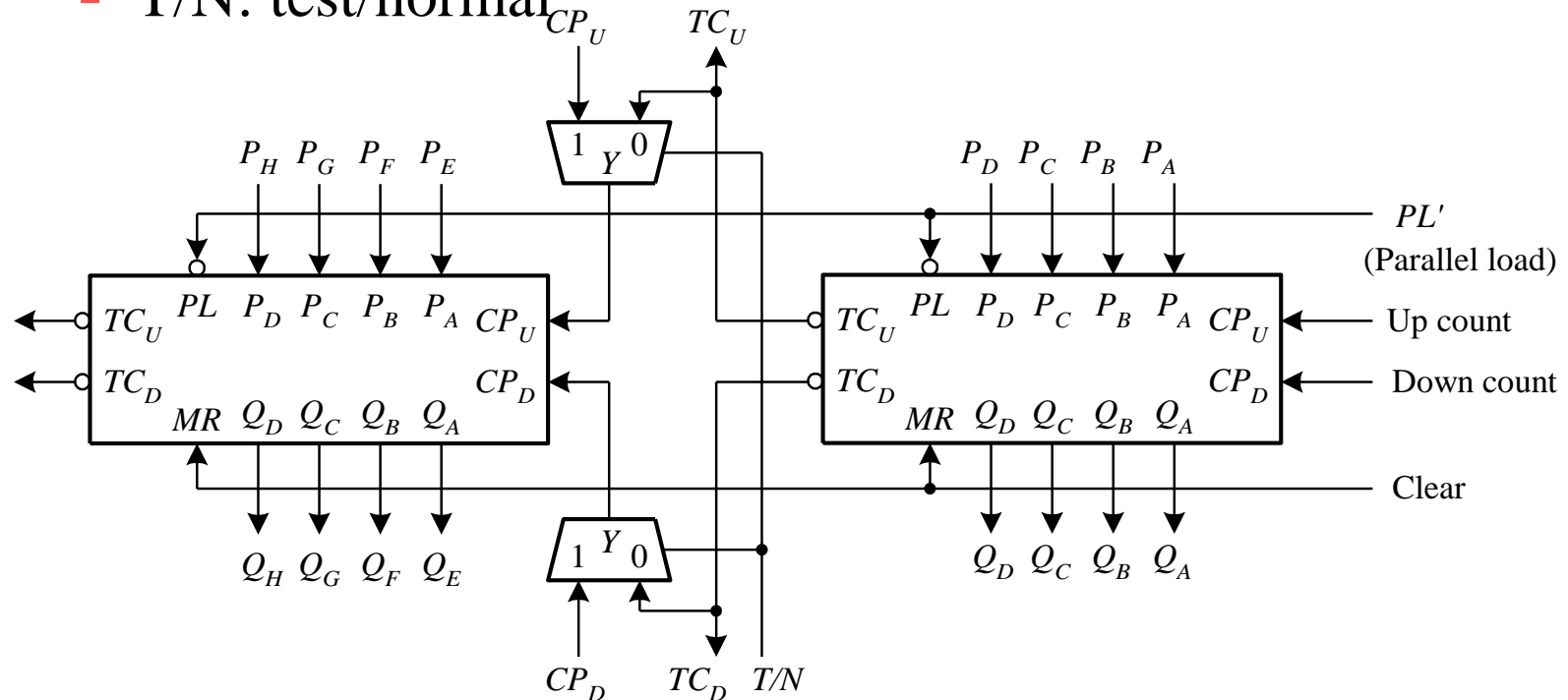- ❖ An example of exhaustive test: 8-bit up/down counter with two 4-bit up/down counters
 - 256 cycles vs 16 cycles
 - T/N: test/normal




Scan-Path Methods


❖ An example of scan-path method

 

BIST Principles

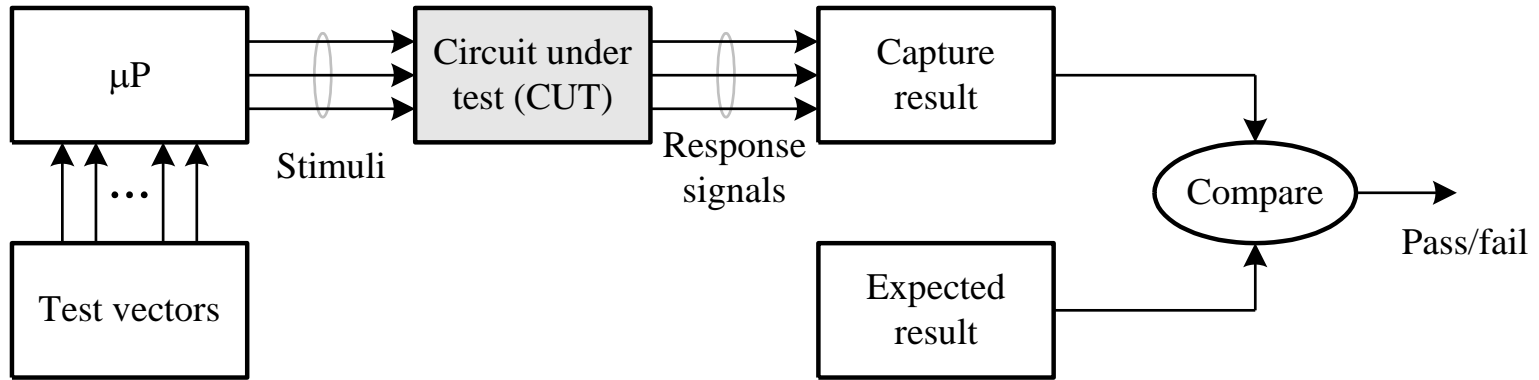


(a) ATE (Automatic test equipment)

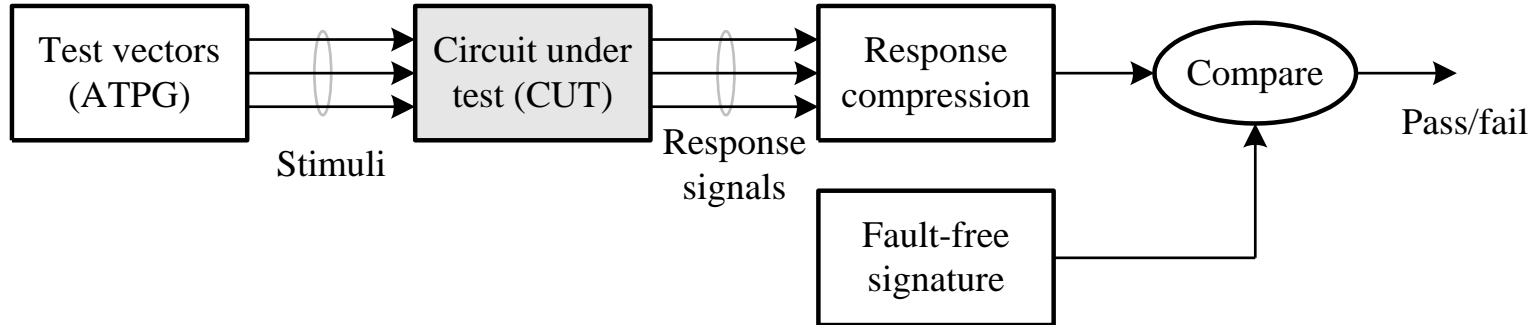


(b) Built-in self test (BIST)

Automatic Test Pattern Generation (ATPG)(ALFSR)

❖ PR-sequence generator

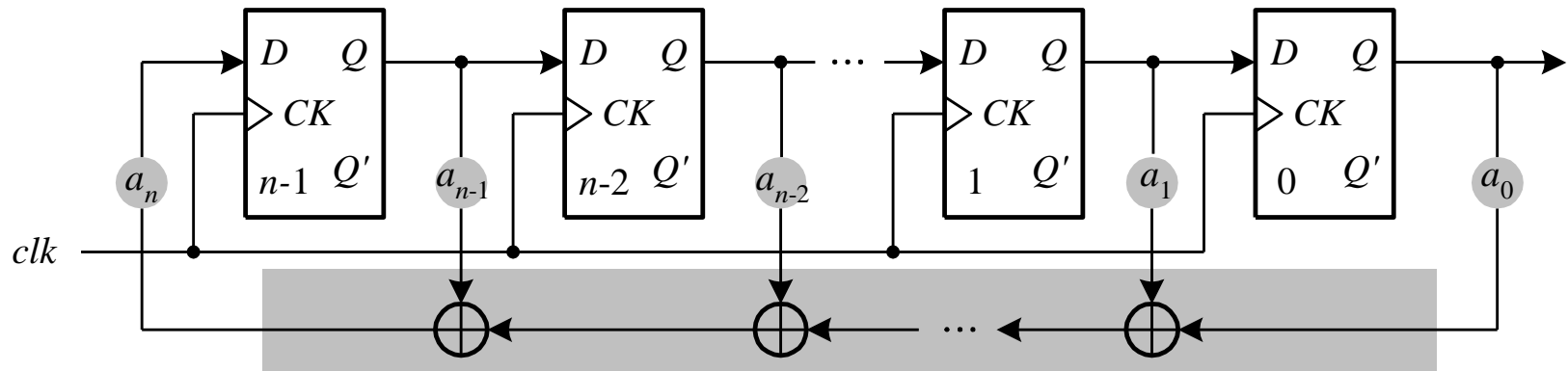

(a) Standard format

 

(b) Modular format


Autonomous linear feedback shift register (ALFSR)

❖ A sample primitive polynomials for n from 1 to 60.


n	$f(x)$	n	$f(x)$	n	$f(x)$
1, 2, 3, 4, 6, 7, 15, 22, 60	$1+x+x^n$	24	$1+x+x^2+x^7+x^n$	43	$1+x+x^5+x^6+x^n$
		26	$1+x+x^2+x^6+x^n$	44, 50	$1+x+x^{26}+x^{27}+x^n$
5, 11, 21, 29	$1+x^2+x^n$	30	$1+x+x^2+x^{23}+x^n$	45	$1+x+x^3+x^4+x^n$
10, 17, 20, 25, 28, 31, 41, 52	$1+x^3+x^n$	32	$1+x+x^2+x^{22}+x^n$	46	$1+x+x^{20}+x^{21}+x^n$
		33	$1+x^{13}+x^n$	48	$1+x+x^{27}+x^{28}+x^n$
9	$1+x^4+x^n$	34	$1+x+x^{14}+x^{15}+x^n$	49	$1+x^9+x^n$
23, 47	$1+x^5+x^n$	35	$1+x^2+x^n$	51, 53	$1+x+x^{15}+x^{16}+x^n$
18	$1+x^7+x^n$	36	$1+x^{11}+x^n$	54	$1+x+x^{36}+x^{37}+x^n$
8	$1+x^2+x^3+x^4+x^n$	37	$1+x^2+x^{10}+x^{12}+x^n$	55	$1+x^{24}+x^n$
12	$1+x+x^4+x^6+x^n$	38	$1+x+x^5+x^6+x^n$	56, 59	$1+x+x^{21}+x^{22}+x^n$
13	$1+x+x^3+x^4+x^n$	39	$1+x^4+x^n$	57	$1+x^7+x^n$
14, 16	$1+x^3+x^4+x^5+x^n$	40	$1+x^2+x^{19}+x^{21}+x^n$	58	$1+x^{19}+x^n$
19, 27	$1+x+x^2+x^5+x^n$	42	$1+x+x^{22}+x^{23}+x^n$		

Signature Generators

 Serial input signature register
Multiple input signature register




(a) SISR Circuit example

 

(b) MISR circuit example

A Signature Application Example

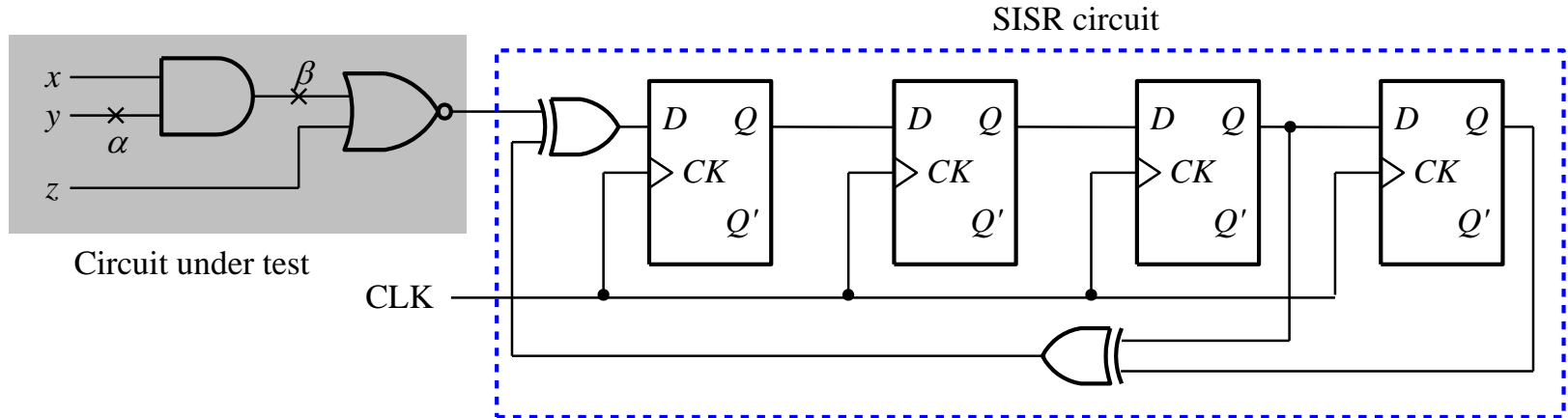

(a) Logic diagram

Input			Fault-free output f	Faulty output		
x	y	z		$f_{\alpha/0}$ and $f_{\beta/0}$	$f_{\alpha/1}$	$f_{\beta/1}$
0	0	1	0	0	0	0
0	1	0	1	1	1	0
1	0	0	1	1	0	0
1	0	1	0	0	0	0
1	1	0	0	1	0	0
1	1	1	0	0	0	0
			0101	0001	1100	0000

(b) A numerical example of signature


Signature Capability

- ❖ For a particular fault-response, there are $2^{m-n} - 1$ erroneous bit streams that will produce the same signature.
- ❖ **Theorem:** For an input data stream of length m , if all possible error patterns are equally likely, then the probability that an n -bit signature generator will not detect an error is

$$P(M) = \frac{2^{m-n}}{2^m - 1}$$

where $2^m - 1$ is the total possible erroneous streams. For $m \gg n$, $P(M)$ will approach 2^{-n} .

 
A BILBO (built-in block observer) Example



(a) Logic diagram

M1	M0	Function
0	0	Scan mode
0	1	MISR
1	0	Clear register
1	1	Parallel load

(b) Function selection

 


(c) Application example

IEEE 1149.1 --- The Boundary Scan Standard

- ❖ The goals of the boundary scan standard are to :
 - provide a data transfer standard between ATE and the devices on a PCB,
 - provide a method of interconnecting devices on a PCB,
 - provide a way of using test bus standard or BIST hardware to find the faulty devices on a PCB.
- ❖ Functions of boundary scan standard:
 - interconnection test
 - normal operation data observation
 - each device test

IEEE 1149.1 --- An Application Example

- ❖ A boundary scan architecture used to test the entire board-level module.

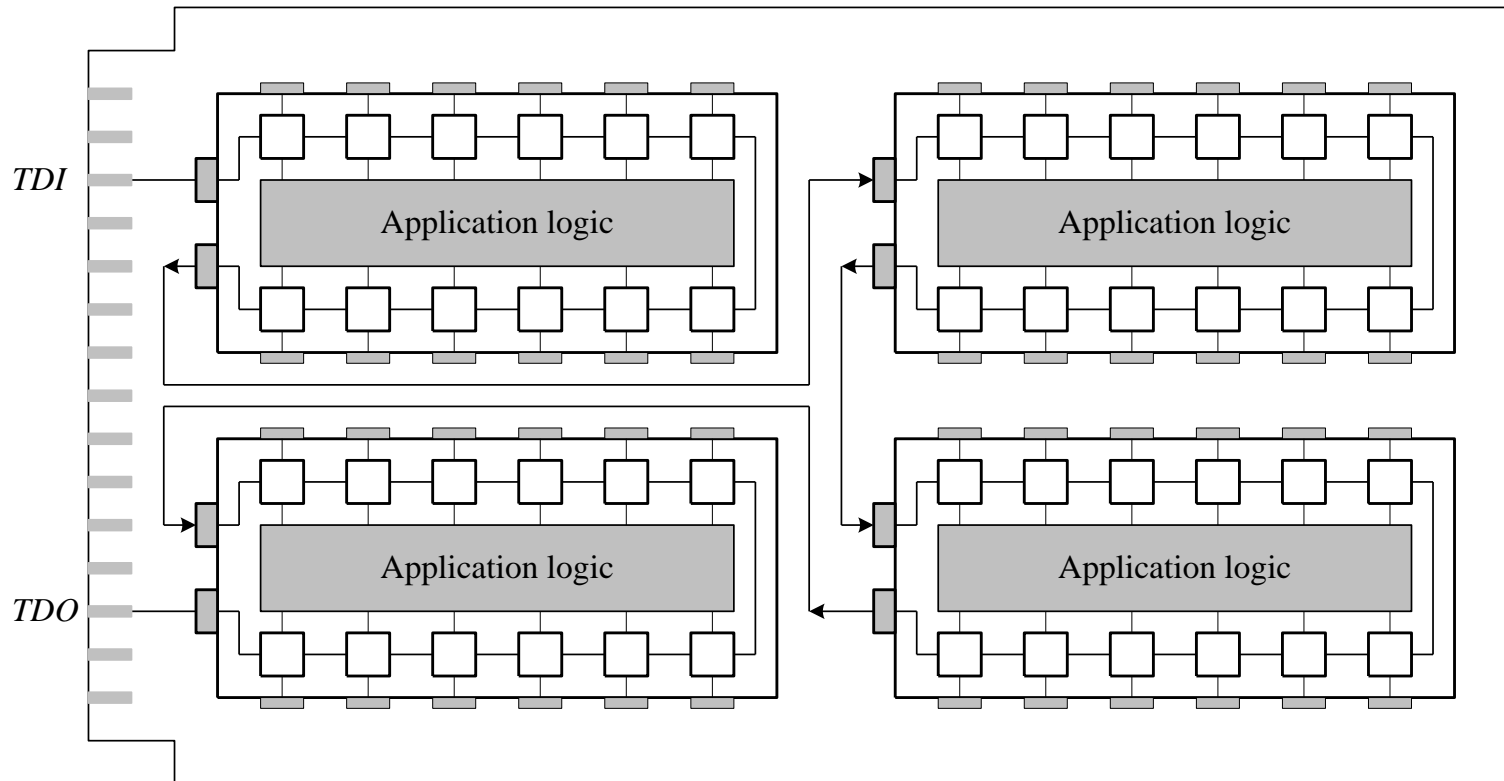


IEEE 1149.1 --- The Structure

- ❖ The boundary scan standard mainly include five parts:
 - test access port (TAP),
 - data registers,
 - TDO driver,
 - instruction register and decoder
 - TAP controller.

IEEE 1149.1 --- The TAP Structure

- ❖ TAP (test access port) consists of:
 - Test data registers (test DRs)
 - Instruction register and decoder
 - TAP controller
 - TDO driver

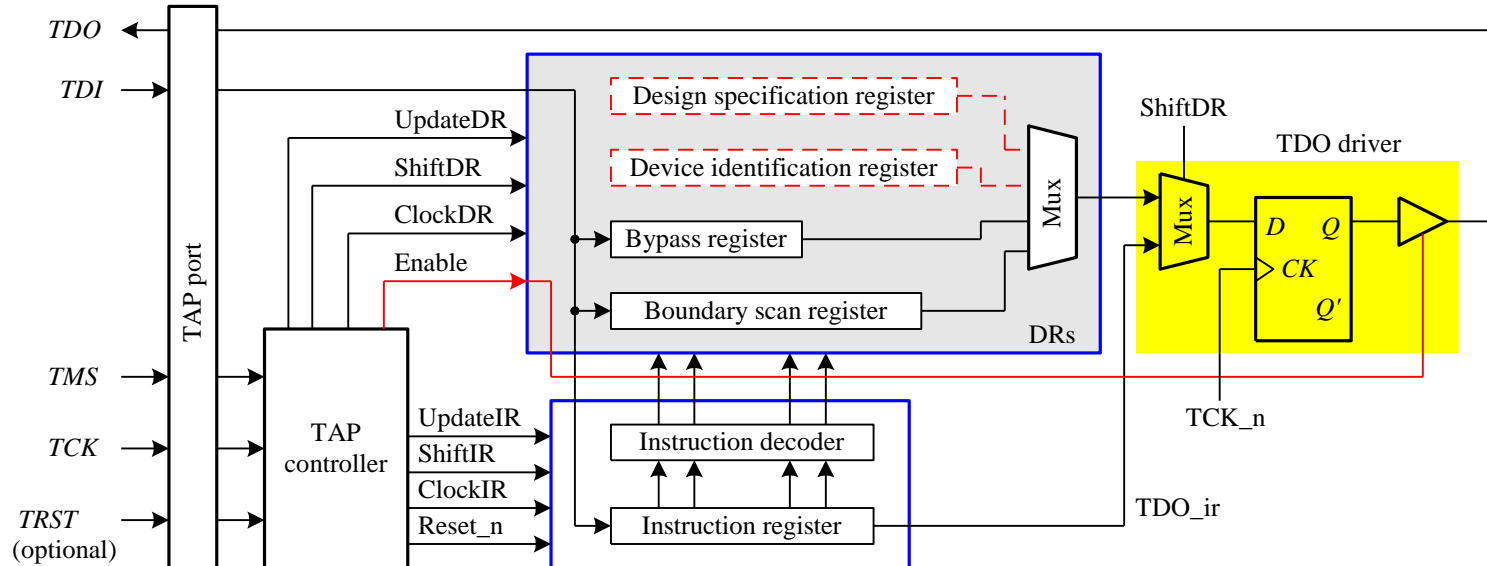

IEEE 1149.1 --- Control Signals

❖ Four control signals:

- TCK (test clock, input) clocks tests into and out of the chip.
- TDI (test data input, input) input test data into the chip.
- TDO (test data output, output) output test data out of the chip.
- TMS (test mode select, input) controls the test operations.


❖ One optional reset signal

- TRST_n (test reset) is an optional active-low asynchronous reset signal, used to reset TAP controller externally.

IEEE 1149.1 --- Control Signals

- ❖ In the normal mode, TRST_n and TCK are held low and TMS is held high to disable boundary scan.
- ❖ To prevent race conditions, inputs are sampled on the positive edge of TCK and output toggle on the negative edge.


IEEE 1149.1 --- The State Machine

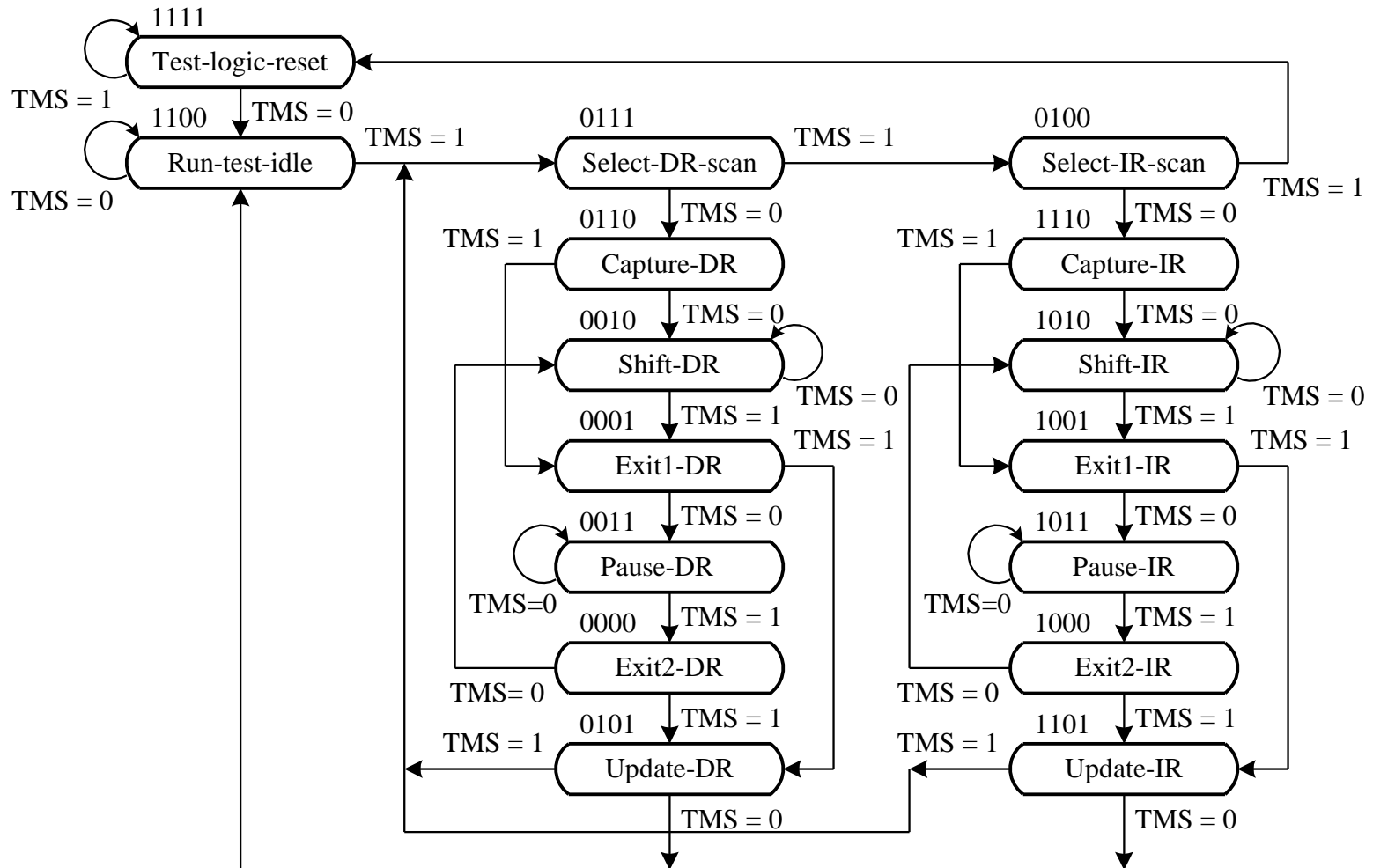


IEEE 1149.1 --- Instruction and Bypass Registers

❖ Instruction register cell

- Shift register
- Instruction register

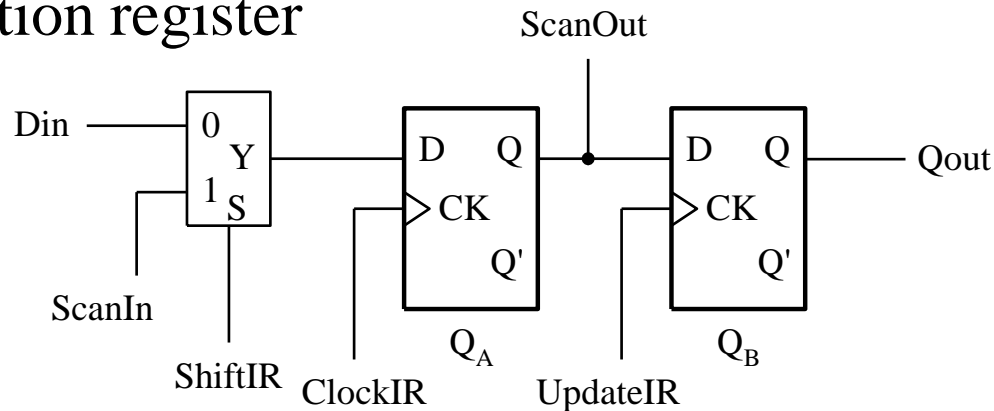


❖ Bypass register structure

 

IEEE 1149.1 --- A TDO Driver

❖ TDO Driver



- TMS is sampled at the positive edge of TCK.
- TDO is sampled at the negative edge of TCK.

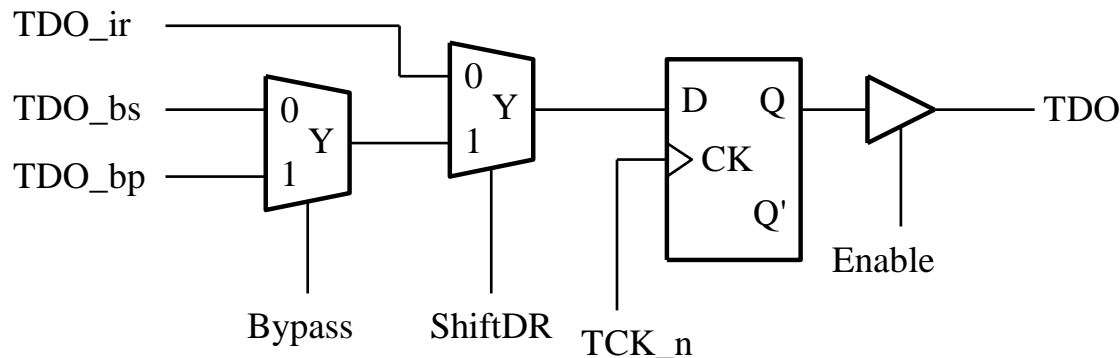

IEEE 1149.1 --- A Boundary Scan Cell


❖ Operation modes of boundary scan cell (BSC):

- Normal mode
- Capture mode
- Scan mode
- Update mode

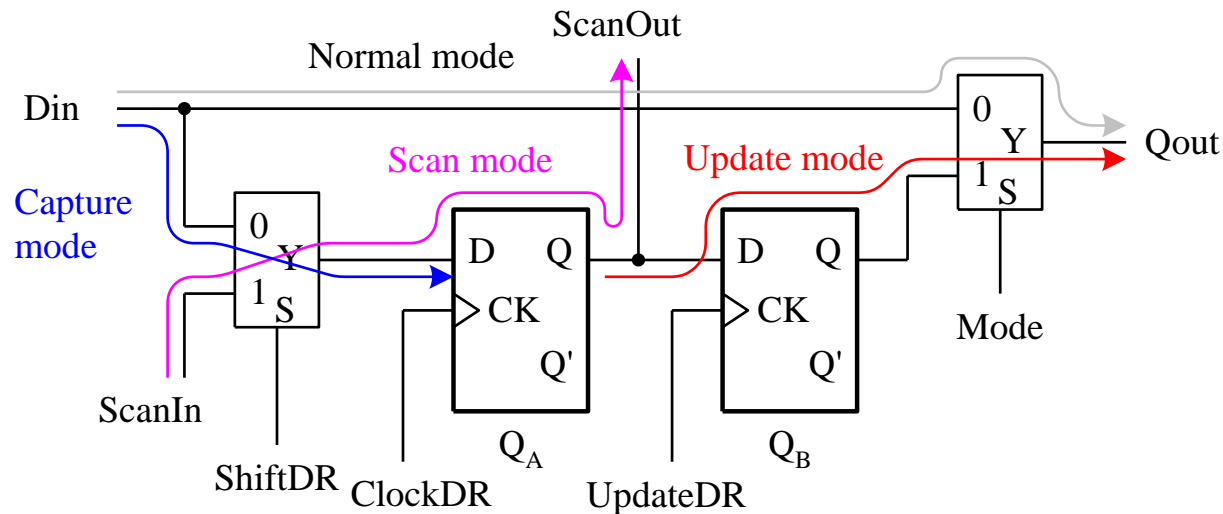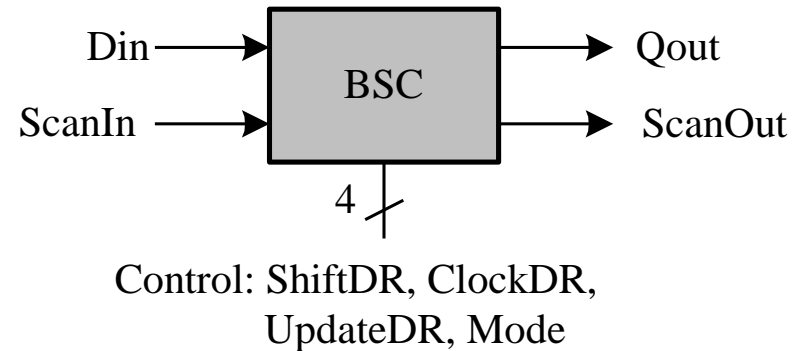


IEEE 1149.1 --- A Boundary Scan Cell

❖ Boundary scan input pad configuration

 


❖ Boundary scan output pad configuration

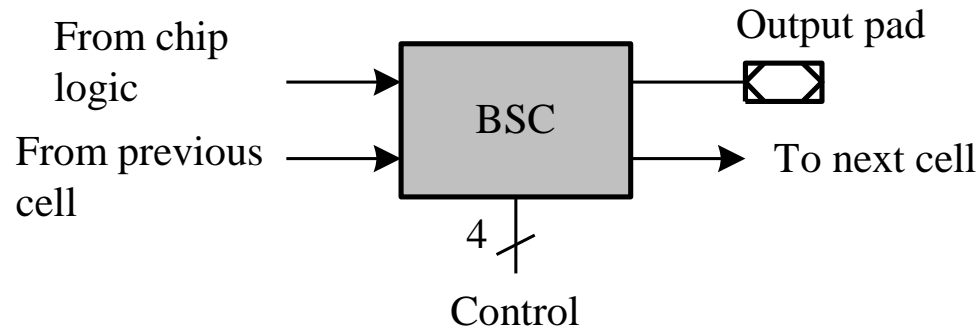


IEEE 1149.1 --- A Boundary Scan Cell

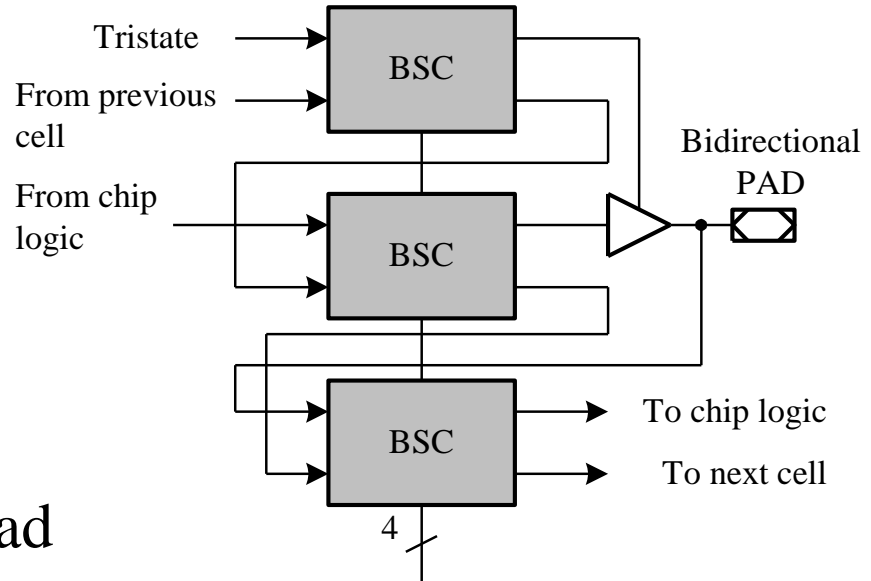❖ Boundary scan
bidirectional pad
configuration



❖ Boundary scan tri-state pad
configuration

 

IEEE 1149.1 --- A Complete Example

