
Ch 2. Combinational Logic

Combinational logic

- Define
 - The kind of digital system whose output behavior depends only on the current inputs
 - memoryless: its outputs are independent of the historical sequence of values presented to it as inputs
 - (cf.) Sequential logic
- Many ways to describe combination logic
 - Boolean algebra expression
 - wired up logic gates
 - truth tables tabulating input and output combinations
 - graphical maps
 - program statements in a hardware description language

Examples of combinational logic

■ The equivalence circuit

X	Y	equal
0	0	1
0	1	0
1	0	0
1	1	1

■ The tally circuit

X	Y	Zero	One	Two
0	0	1	0	0
0	1	0	1	0
1	0	0	1	0
1	1	0	0	1

■ Binary Adder

X	Y	Cout	S
0	0	0	0
0	1	0	1
1	0	0	1
1	1	1	0

< Half-adder >

X	Y	Cin	Cout	S
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

< Full-adder >

Laws and theorems of Boolean logic

■ Basic concept

- Boolean algebra is the mathematical foundation of digital systems
- laws (axioms) : The property to which the operations of Boolean algebra must adhere
- Axioms can be used to prove more general laws

■ Boolean operations

- Operation order
 - COMPLEMENT → AND → OR
- Parentheses : change the default order of evaluation
- examples :

$$1) \bar{A} \bullet B + C = \left(\left(\bar{A} \right) \bullet B \right) + C$$

$$2) \bar{A} + B \bullet C = \left(\bar{A} \right) + \left(B \bullet C \right)$$

Axioms of Boolean algebra

■ A Boolean algebra consists of

- a set of elements B
- binary operations $\{ + , \cdot \}$
- and a unary operation $\{ ' \}$
- such that the following axioms hold (Huntington's postulates):

1. the set B contains at least two elements: a, b

2. closure: $a + b$ is in B $a \cdot b$ is in B

3. identity: $a + 0 = a$ $a \cdot 1 = a$

4. complementarity: $a + a' = 1$ $a \cdot a' = 0$

5. commutativity: $a + b = b + a$ $a \cdot b = b \cdot a$

6. distributivity: $a + (b \cdot c) = (a + b) \cdot (a + c)$ $a \cdot (b + c) = (a \cdot b) + (a \cdot c)$

7. associativity: $a + (b + c) = (a + b) + c$ $a \cdot (b \cdot c) = (a \cdot b) \cdot c$
(redundant) $= a + b + c$ $= a \cdot b \cdot c$

Axioms/theorems of Boolean algebra

■ Operations with 0 and 1:

1. $X \cdot 1 = X$

1D. $X + 0 = X$

2. $X + 1 = 1$

2D. $X \cdot 0 = 0$

■ Idempotent theorem:

3. $X + X = X$

3D. $X \cdot X = X$

■ Involution theorem:

4. $(X')' = X$

■ Theorem of complementarity:

5. $X + X' = 1$

5D. $X \cdot X' = 0$

■ Commutative law:

6. $X + Y = Y + X$

6D. $X \cdot Y = Y \cdot X$

■ Associative law:

7. $(X + Y) + Z = X + (Y + Z)$
 $= X + Y + Z$

7D. $(X \cdot Y) \cdot Z = X \cdot (Y \cdot Z)$
 $= X \cdot Y \cdot Z$

Axioms/theorems of Boolean algebra (cont'd)

- Distributive law:

$$8. X \cdot (Y + Z) = (X \cdot Y) + (X \cdot Z)$$

$$8D. X + (Y \cdot Z) = (X + Y) \cdot (X + Z)$$

- Simplification theorems:

$$9. X \cdot Y + X \cdot Y' = X$$

$$9D. (X + Y) \cdot (X + Y') = X$$

$$10. X + X \cdot Y = X$$

$$10D. X \cdot (X + Y) = X$$

$$11. (X + Y') \cdot Y = X \cdot Y$$

$$11D. (X \cdot Y') + Y = X + Y$$

- DeMorgan's law:

$$12. (X + Y + Z + \dots)' \\ = X' \cdot Y' \cdot Z' \cdot \dots$$

$$12D. (X \cdot Y \cdot Z \cdot \dots)' \\ = X' + Y' + Z' + \dots$$

- General form:

$$13. \{f(X_1, X_2, \dots, X_n, 0, 1, +, \cdot)\}' = \{f(X_1', X_2', \dots, X_n', 1, 0, \cdot, +)\}$$

Axioms/theorems of Boolean algebra (cont'd)

- Duality:

$$14. (X + Y + Z + \dots)^D \\ \rightarrow X \cdot Y \cdot Z \cdot \dots$$

$$14D. (X \cdot Y \cdot Z \cdot \dots)^D \\ \rightarrow X + Y + Z + \dots$$

- General form:

$$15. \{f(X_1, X_2, \dots, X_n, 0, 1, +, \cdot)\}^D \rightarrow f(X_1, X_2, \dots, X_n, 1, 0, \cdot, +)$$

- Theorem for multiplying and factoring

$$16. (X + Y) \cdot (X' + Z) \\ = X \cdot Z + X' \cdot Y$$

$$16D. X \cdot Y + X' \cdot Z \\ = (X + Z) \cdot (X' + Y)$$

- Consensus theorem:

$$17. X \cdot Y + Y \cdot Z + X' \cdot Z \\ = X \cdot Y + X' \cdot Z$$

$$17D. (X + Y) \cdot (Y + Z) \cdot (X' + Z) \\ = (X + Y) \cdot (X' + Z)$$

Axioms/theorems of Boolean algebra (cont'd)

- Verifying the Boolean theorems using the axioms of Boolean algebra:

- e.g., the Uniting theorem(9): $X \cdot Y + X \cdot Y' = X?$

Distributive law (8)	$X \cdot (Y + Y')$	=	X
Complementarity theorem (5)	$X \cdot (1)$	=	X
Identity (1D)	X	=	$X \checkmark$

- e.g., the Simplification theorem(10): $X + X \cdot Y = X?$

Identity (1D)	$X \cdot 1 + X \cdot Y$	=	X
Distributive law (8)	$X(1 + Y)$	=	X
Commutative law (6)	$X(Y + 1)$	=	X
Identity (2)	$X(1)$	=	X
Identity (1)	X	=	$X \checkmark$

Duality and DeMorgan's law

■ Duality

- a dual of a Boolean expression is derived by replacing
 - by +, + by •, 0 by 1, and 1 by 0, and leaving variables unchanged
- any theorem that can be proven is thus also proven for its dual!
- a meta-theorem (a theorem about theorems)
- allow to derive new theorems

: (e.g.) the dual of the Uniting theorem(9), $X \bullet Y + X \bullet Y' = X$, is $(X + Y) \bullet (X + Y') = X$. The proof of the dual follows step-by-step, simply using the duals of the laws used in the original proof.

$$(X + Y) \bullet (X + Y') = X?$$

$$X + (Y \bullet Y') = X \quad \text{Distributive law (8D)}$$

$$X + 0 = X \quad \text{Complementarity theorem (5D)}$$

$$X = X \quad \checkmark \quad \text{Identity (1)}$$

Duality and DeMorgan's law

■ DeMorgan's law

- Give a procedure for complementing a complex function
- The complemented expression is derived by replacing
All literals by their complements, 0 by 1, 1 by 0, • by + and + by •

- (e.g.) the complement of $Z = \bar{A}\bar{B}C + \bar{A}BC + A\bar{B}C + ABC\bar{C}$


$$\bar{Z} = \overline{(\bar{A}\bar{B}C + \bar{A}BC + A\bar{B}C + ABC\bar{C})}$$

$$\bar{Z} = \overline{\bar{A}\bar{B}C} \cdot \overline{\bar{A}BC} \cdot \overline{A\bar{B}C} \cdot \overline{ABC\bar{C}}$$

$$\bar{Z} = (A + B + \bar{C}) (A + \bar{B} + \bar{C}) (\bar{A} + B + \bar{C}) (\bar{A} + \bar{B} + C)$$

Possible logic functions of two variables

 - There are 16 possible functions of 2 input variables:



X	Y	16 possible functions (F0-F15)																
0	0	0	0	0	0	0	0	0	0	0	1	1	1	1	1	1	1	1
0	1	0	0	0	0	1	1	1	1	0	0	0	0	1	1	1	1	1
1	0	0	0	1	1	0	0	1	1	0	0	1	1	0	0	1	1	1
1	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1	0	1	1

Labels for the 16 functions (F0-F15) from left to right:

 F0: X and Y

 F1: NOT (X implies Y)

 F2: X

 F3: NOT (Y implies X)

 F4: Y

 F5: X xor Y

 F6: X or Y

 F7: X nor Y

 F8: X = Y

 F9: not (X or Y)

 F10: not Y

 F11: Y implies X

 F12: not X

 F13: X implies Y

 F14: X nand Y


 F15: not (X and Y)

Cost of different logic functions

- Different functions are easier or harder to implement
 - each has a cost associated with the number of switches needed
 - 0 (F0) and 1 (F15): require 0 switches, directly connect output to low/high
 - X (F3) and Y (F5): require 0 switches, output is one of inputs
 - X' (F12) and Y' (F10): require 2 switches for "inverter" or NOT-gate
 - X nor Y (F4) and X nand Y (F14): require 4 switches
 - X or Y (F7) and X and Y (F1): require 6 switches
 - X = Y (F9) and X \oplus Y (F6): require 16 switches
- thus, because NOT, NOR, and NAND are the cheapest they are the functions we implement the most in practice

Realizing Boolean formulas (logic gates)

■ NAND

 


X	Y	Z
0	0	1
0	1	1
1	0	1
1	1	0

■ NOR



X	Y	Z
0	0	1
0	1	0
1	0	0
1	1	0

■ XOR $X \oplus Y$

 

X	Y	Z
0	0	0
0	1	1
1	0	1
1	1	0

$X \text{ xor } Y = X Y' + X' Y$
 X or Y but not both
 ("inequality", "difference")

■ XNOR $X = Y$






X	Y	Z
0	0	1
0	1	0
1	0	0
1	1	1

$X \text{ xnor } Y = X Y + X' Y'$
 X and Y are the same
 ("equality", "coincidence")



Realizing Boolean formulas (logic blocks and hierarchy)

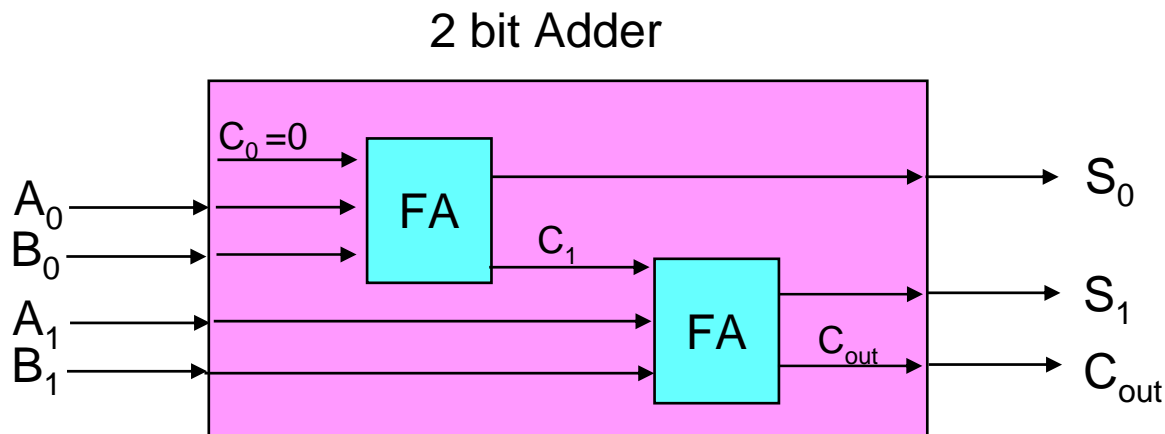  - Complex logic function can be constructed from more primitive functions by wiring up logic gates
- example : 2-bit adder



Time behavior and waveforms

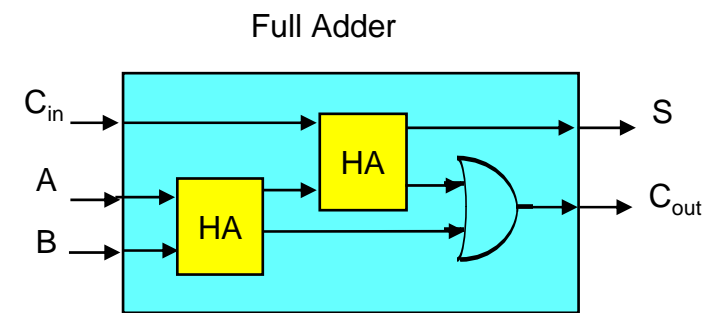 - Waveform: represent signal propagation over time
 - x-axis: the time step
 - y-axis: the logical value
- Unit delay model: considering the delay through any gate as taking exactly one time unit for a simplifying assumption




Minimizing the number of gates and wires

- Different implementations of one function

A	B	C	Z
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	0

$$Z = A'B'C + A'BC + AB'C + ABC'$$

 

two-level realization
($Z1 = ABC' + A'C + B'C$)

multi-level realization
(simple gates but long path;
 $Z2 = TC' + T'C$, $T = AB$)

XOR gate (lowest gate count
but the worst delay;
 $Z3 = (AB) \oplus C$)

Two-level logic

- Canonical form
 - Standard form for a Boolean expression
 - Unique algebraic signature of the function
 - Two alternative forms
 - sum-of-products
 - product-of-sums
- Incompletely specified function
 - consider one more set: don't care set

Sum-of-products canonical forms

- Also known as disjunctive normal form
- Also known as minterm expansion


					$F = 001 \quad 011 \quad 101 \quad 110 \quad 111$
					$F = A'B'C + A'BC + AB'C + ABC' + ABC$
A	B	C	F	F'	
0	0	0	0	1	↖
0	0	1	1	0	↖
0	1	0	0	1	↖
0	1	1	1	0	↖
1	0	0	0	1	↖
1	0	1	1	0	↖
1	1	0	1	0	↖
1	1	1	1	0	↖
					$F' = A'B'C' + A'BC' + AB'C'$

Sum-of-products canonical form (cont'd)

- Product term (or minterm)
 - ANDed product of literals – input combination for which output is true
 - each variable appears exactly once, true or inverted (but not both)

A	B	C	minterms	
0	0	0	$A'B'C'$	m0
0	0	1	$A'B'C$	m1
0	1	0	$A'BC'$	m2
0	1	1	$A'BC$	m3
1	0	0	$AB'C'$	m4
1	0	1	$AB'C$	m5
1	1	0	ABC'	m6
1	1	1	ABC	m7

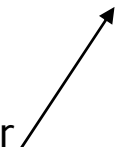short-hand notation for
minterms of 3 variables



F in canonical form:

$$\begin{aligned}F(A, B, C) &= \Sigma m(1,3,5,6,7) \\ &= m1 + m3 + m5 + m6 + m7 \\ &= A'B'C + A'BC + AB'C + ABC' + ABC\end{aligned}$$

canonical form \neq minimal form

$$\begin{aligned}F(A, B, C) &= A'B'C + A'BC + AB'C + ABC + ABC' \\ &= (A'B' + A'B + AB' + AB)C + ABC' \\ &= ((A' + A)(B' + B))C + ABC' \\ &= C + ABC' \\ &= ABC' + C \\ &= AB + C\end{aligned}$$

Product-of-sums canonical form

- Also known as conjunctive normal form
- Also known as maxterm expansion

			$F =$	000	010	100
			$F =$	$(A + B + C)$	$(A + B' + C)$	$(A' + B + C)$

A	B	C	F	F'
0	0	0	0	1
0	0	1	1	0
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	0


$$F' = (A + B + C') (A + B' + C') (A' + B + C') (A' + B' + C) (A' + B' + C')$$

Product-of-sums canonical form (cont'd)

- Sum term (or maxterm)
 - ORed sum of literals – input combination for which output is false
 - each variable appears exactly once, true or inverted (but not both)

A	B	C	maxterms	
0	0	0	$A+B+C$	M0
0	0	1	$A+B+C'$	M1
0	1	0	$A+B'+C$	M2
0	1	1	$A+B'+C'$	M3
1	0	0	$A'+B+C$	M4
1	0	1	$A'+B+C'$	M5
1	1	0	$A'+B'+C$	M6
1	1	1	$A'+B'+C'$	M7

short-hand notation for maxterms of 3 variables




F in canonical form:

$$\begin{aligned}F(A, B, C) &= \prod M(0,2,4) \\ &= M0 \cdot M2 \cdot M4 \\ &= (A + B + C) (A + B' + C) (A' + B + C)\end{aligned}$$

canonical form \neq minimal form


$$\begin{aligned}F(A, B, C) &= (A + B + C) (A + B' + C) (A' + B + C) \\ &= (A + B + C) (A + B' + C) \\ &\quad (A + B + C) (A' + B + C) \\ &= (A + C) (B + C)\end{aligned}$$

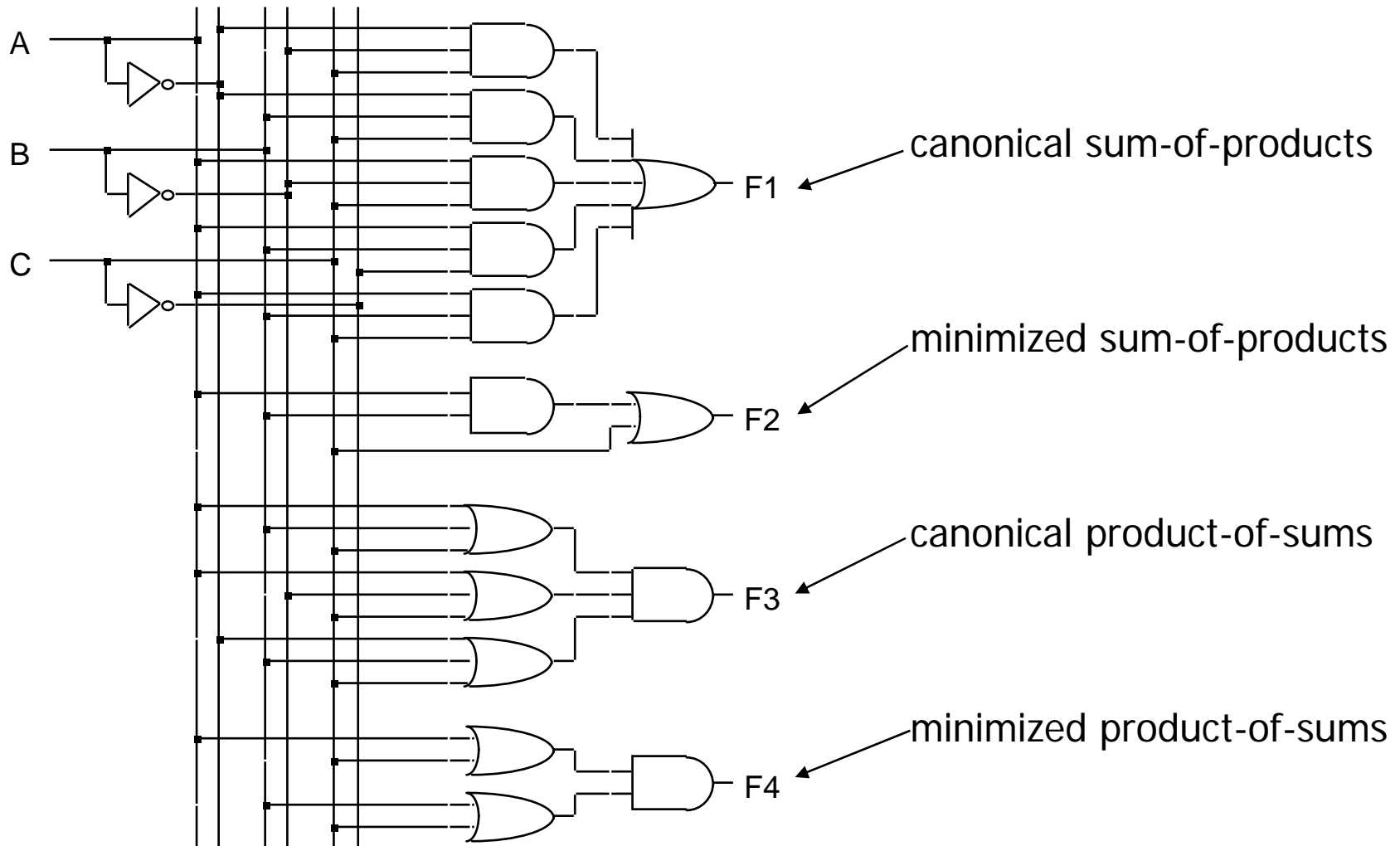Four alternative two-level implementations of F



Waveforms for the four alternatives

 - Waveforms are essentially identical
 - except for timing hazards (glitches)
 - delays almost identical (modeled as a delay per level, not type of gate or number of inputs to gate)



S-o-P, P-o-S, and DeMorgan's theorem

■ Sum-of-products

- $F' = A'B'C' + A'BC' + AB'C'$

■ Apply DeMorgan's

- $(F')' = (A'B'C' + A'BC' + AB'C')$

- $F = (A + B + C)(A + B' + C)(A' + B + C)$

■ Product-of-sums

- $F' = (A + B + C')(A + B' + C')(A' + B + C')(A' + B' + C)(A' + B' + C')$

■ Apply DeMorgan's

- $(F')' = ((A + B + C')(A + B' + C')(A' + B + C')(A' + B' + C)(A' + B' + C'))'$

- $F = A'B'C + A'BC + AB'C + ABC' + ABC$

Conversion between canonical forms

- Minterm to maxterm conversion
 - use maxterms whose indices do not appear in minterm expansion
 - e.g., $F(A,B,C) = \sum m(1,3,5,6,7) = \prod M(0,2,4)$
- Maxterm to minterm conversion
 - use minterms whose indices do not appear in maxterm expansion
 - e.g., $F(A,B,C) = \prod M(0,2,4) = \sum m(1,3,5,6,7)$
- Minterm expansion of F to minterm expansion of F'
 - use minterms whose indices do not appear
 - e.g., $F(A,B,C) = \sum m(1,3,5,6,7) \quad F'(A,B,C) = \sum m(0,2,4)$
- Maxterm expansion of F to maxterm expansion of F'
 - use maxterms whose indices do not appear
 - e.g., $F(A,B,C) = \prod M(0,2,4) \quad F'(A,B,C) = \prod M(1,3,5,6,7)$

Incompletely specified functions

- Example: binary coded decimal increment by 1
 - BCD digits encode the decimal digits 0 – 9 in the bit patterns 0000 – 1001

A	B	C	D	W	X	Y	Z
0	0	0	0	0	0	0	1
0	0	0	1	0	0	1	0
0	0	1	0	0	0	1	1
0	0	1	1	0	1	0	0
0	1	0	0	0	1	0	1
0	1	0	1	0	1	1	0
0	1	1	0	0	1	1	1
0	1	1	1	1	0	0	0
1	0	0	0	1	0	0	1
1	0	0	1	0	0	0	0
1	0	1	0	X	X	X	X
1	0	1	1	X	X	X	X
1	1	0	0	X	X	X	X
1	1	0	1	X	X	X	X
1	1	1	0	X	X	X	X
1	1	1	1	X	X	X	X

off-set of W
 on-set of W
 don't care (DC) set of W

these inputs patterns should never be encountered in practice – **"don't care"** about associated output values, can be exploited in minimization

Notation for incompletely specified functions

- Don't cares and canonical forms
 - so far, only represented on-set
 - also represent don't-care-set
 - need two of the three sets (on-set, off-set, dc-set)
- Canonical representations of the BCD increment by 1 function:
 - $Z = m_0 + m_2 + m_4 + m_6 + m_8 + d_{10} + d_{11} + d_{12} + d_{13} + d_{14} + d_{15}$
 - $Z = \Sigma [m(0,2,4,6,8) + d(10,11,12,13,14,15)]$
 - $Z = M_1 \cdot M_3 \cdot M_5 \cdot M_7 \cdot M_9 \cdot D_{10} \cdot D_{11} \cdot D_{12} \cdot D_{13} \cdot D_{14} \cdot D_{15}$
 - $Z = \Pi [M(1,3,5,7,9) \cdot D(10,11,12,13,14,15)]$

Simplification of two-level combinational logic

- Finding a minimal sum of products or product of sums realization
- Algebraic simplification
 - not an algorithmic/systematic procedure
 - how do you know when the minimum realization has been found?
- Computer-aided design tools
 - precise solutions require very long computation times, especially for functions with many inputs (> 10)
 - heuristic methods employed – "educated guesses" to reduce amount of computation and yield good if not best solutions
- Hand methods still relevant
 - to understand automatic tools and their strengths and weaknesses
 - ability to check results (on small examples)

The essence of Boolean simplification

- Key tool to simplification: the Uniting theorem

$$\rightarrow A (B' + B) = A$$

- Essence of simplification of two-level logic

- find two element subsets of the ON-set where only one variable changes its value – this single varying variable can be eliminated and a single product term used to represent both elements

$$F = A'B' + AB' = (A' + A)B' = B'$$





A	B	F
0	0	1
0	1	0
1	0	1
1	1	0

B has the same value in both on-set rows
– B remains

A has a different value in the two rows
– A is eliminated

Boolean cubes

    
- Visual technique for identifying when the uniting theorem can be applied
- n input variables = n -dimensional "cube"



Mapping truth tables onto Boolean cubes

- Uniting theorem combines two "faces" of a cube into a larger "face"
- adjacency plane
 - circled elements of the on-set that are directly adjacent
 - each adjacency plane corresponds to a product term
- Example:

A	B	G
0	0	1
0	1	0
1	0	1
1	1	0

 

two faces of size 0 (nodes) combine into a face of size 1 (line)


A varies within face, B does not this face represents the literal B'

ON-set = solid nodes
 OFF-set = empty nodes
 DC-set = x'd nodes

Three variable example

Binary full-adder carry-out logic

A	B	Cin	Cout
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

 


the on-set is completely covered by the combination (OR) of the subcubes of lower dimensionality - note that "111" is covered three times

$$Cout = BCin + AB + ACin$$

Higher dimensional cubes

- Sub-cubes of higher dimension than 1

 

$$F(A,B,C) = \Sigma m(4,5,6,7)$$

on-set forms a square
i.e., a cube of dimension 2

*represents an expression in one variable
i.e., 3 dimensions – 2 dimensions*

A is asserted (true) and unchanged
B and C vary

This subcube represents the
literal A

m-dimensional cubes in an n-dimensional Boolean space

- In a 3-cube (three variables):
 - a 0-dimensional plane, i.e., a single node, yields a term in 3 literals
 - example : $101 = AB'C$
 - a 1-dimensional plane, i.e., a line of two nodes, yields a term in 2 literals
 - example : $100-101 = AB'$
 - a 2-dimensional plane, i.e., a plane of four nodes, yields a term in 1 literal
 - example : $100-101-111-110 = A$
 - a 3-dimensional plane, i.e., a cube of eight nodes, yields a constant logic "1"
- In general,
 - an m-dimensional adjacency plane within an n-cube ($m < n$) yields a term with $n - m$ literals

Karnaugh maps

- The problem for humans
 - difficulty of visualizing adjacencies in more than 3 dimensional cubes
- Karnaugh maps
 - Alternative reformulation of the truth table
 - at least for expressions up to six variables
 - wrap-around at edges
 - on-set elements with only one variable changing value are adjacent unlike the situation in a linear truth-table

		A	
		0	1
B	0	1	1
	1	0	0

A	B	F
0	0	1
0	1	0
1	0	1
1	1	0

Karnaugh maps (cont'd)

- Numbering scheme based on Gray-code
 - e.g., 00, 01, 11, 10
 - only a single bit changes in code for adjacent map cells

		A			
		00	01	11	10
C	0				
	1				
		B			



		A			
		0	2	6	4
C	0				
	1				
		B			

		A			
		0	4	12	8
C	0				
	1				
		B			

$$13 = 1101 = ABC'D$$

Adjacencies in Karnaugh maps

  
- Wrap from first to last column
- Wrap top row to bottom row



Karnaugh map examples


- 2-variable maps
 - $F = AB' + AB = A$

A	B	F
0	0	0
0	1	0
1	0	1
1	1	1

 

- $G = A'B' + AB' = B'$

A	B	G
0	0	1
0	1	0
1	0	1
1	1	0

 


Karnaugh map examples (cont'd)

- 3-variable maps


- Full adder

A	B	Cin	Cout
0	0	0	0
0	0	1	0
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	1
1	1	1	1

 

$$AB + Bcin + ACin$$


- $F(A,B,C) = \Sigma m(0,4,5,7)$

 


$$AC + B'C' + \cancel{AB'}$$

obtain the complement of the function by covering 0s with subcubes (see next page)


More Karnaugh map examples

 

$$G(A,B,C) = A$$

 
 
$$F(A,B,C) = \sum m(0,4,5,7) = AC + B'C'$$





Complement of $F(A,B,C) = m(0,4,5,7)$
 F' simply replace 1's with 0's and vice versa

$$F'(A,B,C) = \sum m(1,2,3,6) = BC' + A'C$$

Karnaugh map: 4-variable example

- $F(A,B,C,D) = \Sigma m(0,2,3,5,6,7,8,10,11,14,15)$

$$F = C + A'BD + B'D'$$

  

find the smallest number of the largest possible subcubes to cover the ON-set
(fewer terms with fewer inputs per term)

Karnaugh maps: don't cares


- $f(A,B,C,D) = \Sigma m(1,3,5,7,9) + d(6,12,13)$
 - without don't cares
 - $f = A'D + B'C'D$

		A		
	0	0	X	0
	1	1	X	1
	1	1	0	0
C	0	X	0	0
		B		

The Karnaugh map is a 4x4 grid with variables A and B as columns and C and D as rows. The cells contain values: (A=0, B=0, C=0, D=0) is 0; (A=0, B=0, C=1, D=0) is 1; (A=0, B=0, C=1, D=1) is 1; (A=0, B=1, C=0, D=0) is 0; (A=0, B=1, C=0, D=1) is X; (A=0, B=1, C=1, D=0) is 1; (A=0, B=1, C=1, D=1) is 1; (A=1, B=0, C=0, D=0) is 0; (A=1, B=0, C=0, D=1) is X; (A=1, B=0, C=1, D=0) is 0; (A=1, B=0, C=1, D=1) is 0; (A=1, B=1, C=0, D=0) is 0; (A=1, B=1, C=0, D=1) is 0; (A=1, B=1, C=1, D=0) is 0; (A=1, B=1, C=1, D=1) is 0. Circles group the 1s at (0,0,1,0), (0,0,1,1), (0,1,1,0), and (0,1,1,1). A thick border highlights the 1s at (0,0,1,0), (0,0,1,1), (0,1,1,0), and (0,1,1,1).

Karnaugh maps: don't cares (cont'd)

 - $f(A,B,C,D) = \Sigma m(1,3,5,7,9) + d(6,12,13)$
 - $f = A'D + B'C'D$ without don't cares
 - $f = A'D + C'D$ with don't cares



by using don't care as a "1"
a 2-cube can be formed
rather than a 1-cube to cover
this node

don't cares can be treated as
1s or 0s
depending on which is more
advantageous

Multilevel Logic

- Comparison with 2-level logic

- gain: reduce the number of wires, gates and inputs to each gate
- lose: add up more combined delay because of the increased levels of logic

- Example

- 2-level logic

$$Z = ADF + AEF + BDF + BEF + CDF + CEF + G$$

→ six 3-input AND gates and one 7-input OR gate

- multilevel logic

$$Z = (AD + AE + BD + BE + CD + CE)F + G$$

$$Z = [(A + B + C)D + (A + B + C)E]F + G$$

$$Z = (A + B + C)(D + E)F + G$$

→ one 3-input OR gate, two 2-input OR gates and one 3-input AND gate

Chapter review

- Variety of primitive logic building blocks
 - NOT, AND, OR, NAND, NOR, XOR and XNOR gates
- Axioms and theorems of Boolean algebra
 - proofs by re-writing and perfect induction
- Two-level logic
 - canonical forms: sum-of-products and product-of-sums
 - incompletely specified functions
- Simplification
 - a start at understanding two-level simplification
 - Boolean cubes
 - K-Map