


---

# Microelectronics Circuits 1 Review

Prof. Y.Kwon

# Electronic Circuits

---

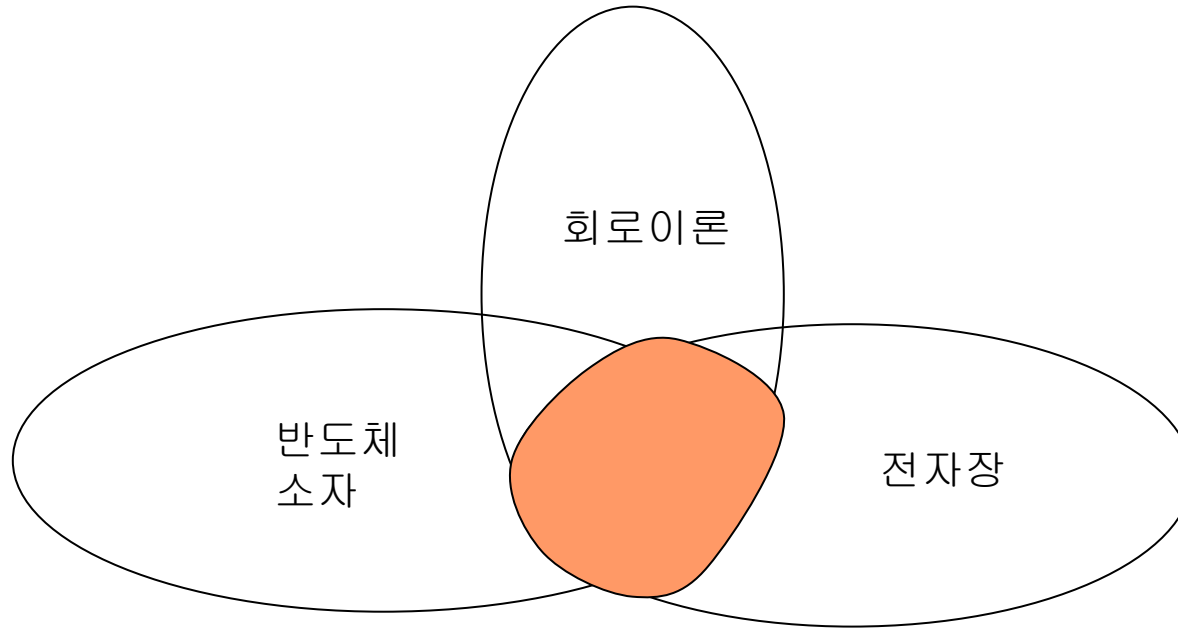


- Static phenomenon only
- Simplified transistor model : MOSFET and BJT
- Interested in “voltage” gain rather than “power” gain
- Consists of “analog” integrated circuit and “digital” integrated circuit

# Contents to Cover in this Course and Evaluation

---

- Chap 8 : Feedback Amplifier
- Chap 9 : Operational Amplifier
- Chap 12 : Filters and Tuned Amplifier (12.1 ~ 12.7)
- Chap 13 : Signal Generators and Waveform-Shaping Circuits (13.1~13.5)
- Chap 14 : Output Stage and Power Amplifiers (14.1 ~ 14.5)
- Chap 10 & 11 : Basics of Digital Circuits
  
- Evaluation
  - Two mid terms and One final exam
  - Attendance
  - Homework

# Physical understanding of STC

 

$$V_o = \frac{Q}{C}$$

$$Q(t = 0^-) = 0 \rightarrow V_o(t = 0^-) = 0$$

$$V_o(t = \infty) = V_s \rightarrow Q(t = \infty) = C * V_s$$

$$Q(t) = \int_0^t I(\tau) d\tau \rightarrow \text{requires large } I \text{ to reduce } t$$

$$I = \frac{V_i - V_s}{R} \rightarrow \text{requires small } R$$

$$\text{Time Constant} = RC$$

takes more charge to raise voltage level

# Comparison of the MOSFET & the BJT



**TABLE 6.3**

Comparison of the MOSFET and the BJT

NMOS

nnp

Circuit Symbol

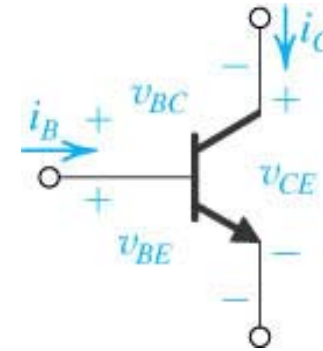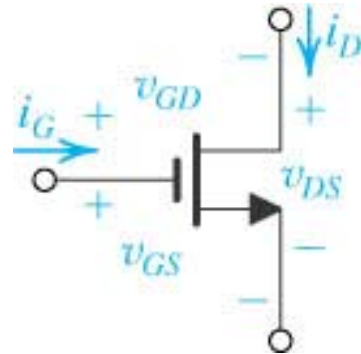

To Operate in the Active Mode, Two Conditions Have To Be Satisfied

(1) Induce a channel;

$$V_{GS} \geq V_t, V_t = 0.5 - 0.7 \text{ V}$$

Let  $V_{GS} = V_t + v_{ov}$

(2) Pinch-off channel at drain;

$$V_{GD} < V_t$$

or equivalently,

$$v_{DS} \geq V_{OV}, V_{ov} = 0.2 - 0.3 \text{ V}$$

(1) Forward-bias EBJ;

$$v_{BE} \geq V_{BEon}, V_{BEon} \cong 0.5 \text{ V}$$

(2) Reverse-bias CBJ;

$$v_{BC} < V_{BCon}, V_{BCon} \cong 0.4 \text{ V}$$

or equivalently

$$v_{CE} \geq 0.3 \text{ V}$$

# Comparison of the MOSFET & the BJT

## Current-Voltage Characteristics in the Active Region

$$i_D = \frac{1}{2} \mu_n C_{ox} \frac{W}{L} (v_{GS} - V_t)^2 \left( 1 + \frac{v_{DS}}{V_A} \right)$$


$$i_C = I_S e^{v_{BE}/V_T} \left( 1 + \frac{v_{CE}}{V_A} \right)$$

$$= \frac{1}{2} \mu_n C_{ox} \frac{W}{L} v_{ov}^2 \left( 1 + \frac{v_{DS}}{V_A} \right)$$

$$i_G = 0$$

$$i_B = i_C / \beta$$

## Low-Frequency Hybrid- $\pi$ Model

 

# Comparison of the MOSFET & the BJT

---

## Transconductance

$g_m$

$$g_m = I_D / (V_{ov} / 2)$$

$$g_m = I_C / V_T$$

$$g_m = (\mu_n C_{ox}) \left( \frac{W}{L} \right) V_{ov}$$

$$g_m = \sqrt{2(\mu_n C_{ox}) \left( \frac{W}{L} \right) I_D}$$

---

## Output resistance

$r_0$

$$r_0 = V_A / I_D = \frac{V'_A L}{I_D}$$

$$r_0 = V_A / I_C$$

$\Rightarrow r_0$  is inversely proportional to the bias current.

---

## Input Resistance with Source

(Emitter)

Grounded

$\infty$

$$r_\pi = \beta / g_m$$

# Comparison of the MOSFET & the BJT

## Intrinsic Gain


$$A_0 = g_m r_o$$

$$A_0 = V_A / (V_{OV} / 2)$$

$$A_0 = g_m r_o = \frac{I_C}{V_T} \cdot \frac{V_A}{I_C} = V_A / V_T$$

$$A_0 = \frac{2V_A' L}{V_{OV}}$$
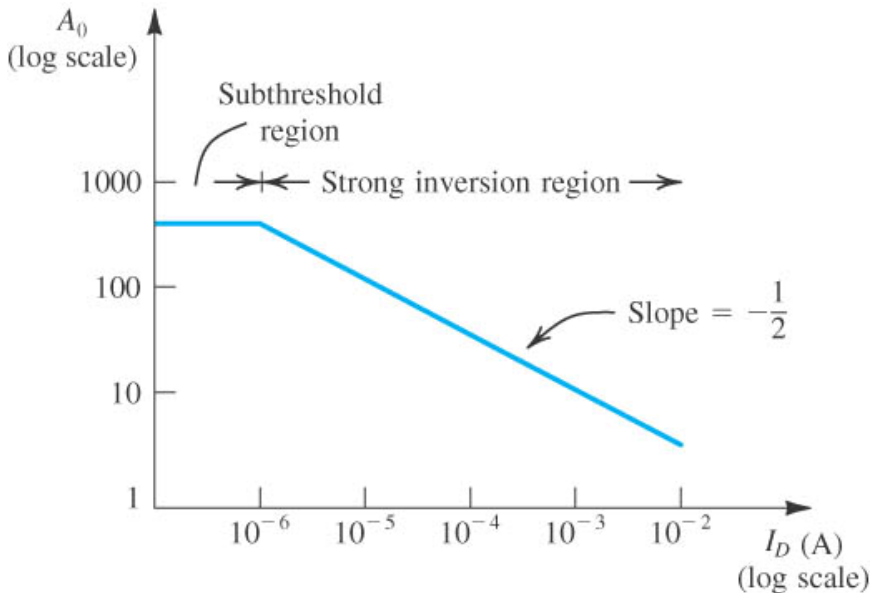
$$A_0 = \frac{V_A' \sqrt{2\mu_n C_{ox} WL}}{\sqrt{I_D}}$$




$$A_0 = 1000 \sim 5000 V/V$$


 
# Current Mirror Circuit

Transistor  $Q_1$  : Drain is shorted to its gate.  $\Rightarrow$  Saturation mode

$$i_{D1} = \frac{1}{2} \mu_n C_{ox} \left( \frac{W}{L} \right)_1 (V_{GS} - V_{tn})^2$$



Since the gate currents are zero,

$$I_{D1} = I_{REF} = \frac{V_{DD} - V_{GS}}{R}$$

$R$  : In most cases, outside the IC chip


Assuming  $Q_2$  in the saturation mode,

$$I_O = I_{D2} = \frac{1}{2} k_n' \left( \frac{W}{L} \right)_2 (V_{GS} - V_{tn})^2$$

$$\Rightarrow \frac{I_O}{I_{REF}} = \frac{\left( \frac{W}{L} \right)_2}{\left( \frac{W}{L} \right)_1}$$

$I_O / I_{REF}$  is solely determined by the geometries of the transistors.

# Current Mirror Circuit

 


To ensure that  $Q_2$  is saturated,  
 $V_O \geq V_{GS} - V_t$  or equivalently  $V_O \geq V_{OV}$ .

At  $V_O = V_{GS}$ ,  $I_O = I_{REF}$ .

As  $V_O$  increases above  $V_{GS}$ ,  
 $I_O$  will increase according to  
the incremental output resistance  $r_{o2}$  of  $Q_2$ .

# Current Mirror Circuit

 


As  $V_O$  is increases above  $V_{GS}$ ,  $I_O$  will increase according to the incremental output resistance  $r_{o2}$  of  $Q_2$ .

$$R_o \equiv \frac{\Delta V_O}{\Delta I_O} = r_{o2} = \frac{V_{A2}}{I_O}$$

$$I_O = \frac{(W/L)_2}{(W/L)_1} I_{REF} \left( 1 + \frac{V_O - V_{GS}}{V_{A2}} \right)$$
 
# Current Steering Circuit

Once a constant current is generated, it can be replicated to provide dc bias currents for various amplifier stages in an IC.



# $F_H$ Estimation : Open-circuit time constant Method

---

- High Frequency Gain Function :  $A(s) = A_M F_H(s)$        $A_M$  : Midband Gain

$$F_H(s) = \frac{(1 + s/\omega_{z1})(1 + s/\omega_{z2}) \cdots (1 + s/\omega_{zn})}{(1 + s/\omega_{p1})(1 + s/\omega_{p2}) \cdots (1 + s/\omega_{pn})} = \frac{1 + a_1s + a_2s^2 + \cdots + a_ns^n}{1 + b_1s + b_2s^2 + \cdots + b_ns^n}$$

$$b_1 = \frac{1}{\omega_{p1}} + \frac{1}{\omega_{p2}} + \cdots + \frac{1}{\omega_{pn}}$$

- Practical Bandwidth is determined by 3dB roll-off point ( $\omega_H$ )

- When dominant pole exists,  $F_H(s) \cong \frac{1}{1 + s/\omega_{p1}}$       &       $\omega_H \cong \omega_{p1}$

- Gray and Searle  $\rightarrow$        $b_1 = \sum_i C_i R_{io}$


- IF there is dominant pole,

$$b_1 \cong \frac{1}{\omega_{p1}} \rightarrow \omega_H \approx \omega_{p1} \approx \frac{1}{b_1} = \frac{1}{\left| \sum_i C_i R_{io} \right|}$$

- This result are very good even if no dominant pole exists.



 
# Miller's Theorem

- When the circuit conditions remain to make  $V_1 = KV_2$



- Proof : derive the same I/V relationship at both ports
- $(1 - K) \rightarrow$  Miller multiplication (“Miller Effect”) for conductance or susceptance
   
# The MOSFET internal capacitances and high-frequency model



## Five capacitance

$C_{gs}$ ,  $C_{gd}$ ,  $C_{gb}$ ,  $C_{sb}$  and  $C_{db}$

# The MOSFET internal capacitances and high-frequency model

- The gate capacitive effect

- Triode region

- $C_{gs} = C_{gd} = 1/2WLC_{ox}$

- Saturation region

- $C_{gs} = 2/3WLC_{ox}$

- $C_{gd} = 0$



- Cutoff

- $C_{gs} = C_{gd} = 0$

- $C_{gb} = WLC_{ox}$

- The junction capacitances

  
$$C_{sb} = \frac{C_{sbo}}{\sqrt{1 + \frac{V_{SB}}{V_o}}}, \quad C_{db} = \frac{C_{dbo}}{\sqrt{1 + \frac{V_{DB}}{V_o}}}$$






# The MOSFET internal capacitances and high-frequency model


- The high-frequency MOSFET model

 

(a)

 

(c)

 


(b)

- (a) High-frequency equivalent circuit model for the MOSFET.
- (b) The equivalent circuit for the case in which the source is connected to the substrate (body).
- (c) The equivalent circuit model of (b) with  $C_{db}$  neglected (to simplify analysis).
 
# The MOSFET internal capacitances and high-frequency model

- The MOSFET unity-gain frequency ( $f_T$ )

The frequency at which the short-circuit current-gain of the common-source configuration becomes unity.



Determining the short-circuit current gain  $I_o/I_i$ .

$$I_o = g_m V_{gs} - sC_{gd} V_{gs}$$

$$I_o \cong g_m V_{gs}$$

$$V_{gs} = I_i / s(C_{gs} + C_{gd})$$

$$\frac{I_o}{I_i} = \frac{g_m}{s(C_{gs} + C_{gd})}$$


For physical frequencies  $s = j\omega$

$$\omega_T = g_m / (C_{gs} + C_{gd})$$

$$f_T = \frac{g_m}{2\pi(C_{gs} + C_{gd})}$$

Typically,  $f_T$  ranges from about 100MHz for the older technologies (e.g., a 5-um CMOS process) to many GHz for newer high-speed technologies (e.g., a 0.13-um CMOS process).

# CS Amplifier

 


(1) The current source can be implemented using a PMOS transistor.

→ Active load

(2) Obviously,  $Q_1$  is biased at  $I_D = I$ .  
But what are  $V_{DS}$  and  $V_{GS}$ ?

→ We just assume that the MOSFET is biased to operate in the saturation region throughout this chapter.

# CS Amplifier

 



$$R_i = \left. \frac{v_i}{i_i} \right|_{RL=\infty} = \infty$$

$$A_{vo} = \left. \frac{v_o}{v_i} \right|_{RL=\infty} = -g_m r_o$$

$$R_o = \left. \frac{v_x}{i_x} \right|_{v_i=0} = r_o$$

$A_0 = g_m r_o$  : Intrinsic gain of MOSFET

# CS Amplifier

  


The value of  $V_{SG}$  is set by passing the reference bias current  $I_{REF}$  through  $Q_3$ .

When  $v = v_{SD}$  exceeds  $(V_{SG} - |V_{tp}|)$ ,  $Q_2$  operates in saturation.


When  $Q_2$  operates in saturation,  $Q_2$  behaves as a current source.

When  $Q_2$  is in saturation, it exhibits a finite incremental resistance :  $r_{o2} = \frac{|V_{A2}|}{I_{REF}}$




# CS Amplifier

 

 When the amplifier is biased  
 at a point in region III,  
 small signal voltage gain  
 can be determined  
 by replacing  $Q_1$  with its  
 small signal model  
 and  $Q_2$  with its  
 output resistance  $r_{o2}$ .



# CS Amplifier

   

$$A_{vo} = -g_m r_o$$

$$R_o = \left. \frac{v_x}{i_x} \right|_{v_i=0} = r_o$$

# CS Amplifier

---

$$A_v \equiv \frac{v_o}{v_i} = A_{vo} \frac{R_L}{R_L + R_O}, \text{ and in this case } A_{vo} = -(g_{m1} r_{o1}), R_O = r_{o1}, \text{ and } R_L = r_{o2}.$$

$$A_v = -(g_{m1} r_{o1}) \frac{r_{o2}}{r_{o2} + r_{o1}} = -g_{m1} (r_{o1} \parallel r_{o2})$$

Or from the other circuit,  $v_o = -(g_{m1} v_i) (r_{o1} \parallel r_{o2})$



# CS Amplifier

---


CMOS common-source amplifier

- (1) Voltage gain of 15 to 100
- (2) Very high input resistance
- (3) Output resistance is also high.


Two final comments

- (1) The circuit is not affected by the body effect since the source terminals of both  $Q_1$  and  $Q_2$  are at signal ground.
- (2) The circuit operates in region III, which is ensured by the negative feedback: the circuit is usually part of a larger amplifier (Chapters 7 and 9).

# Common-Gate Amplifier

 

(a)

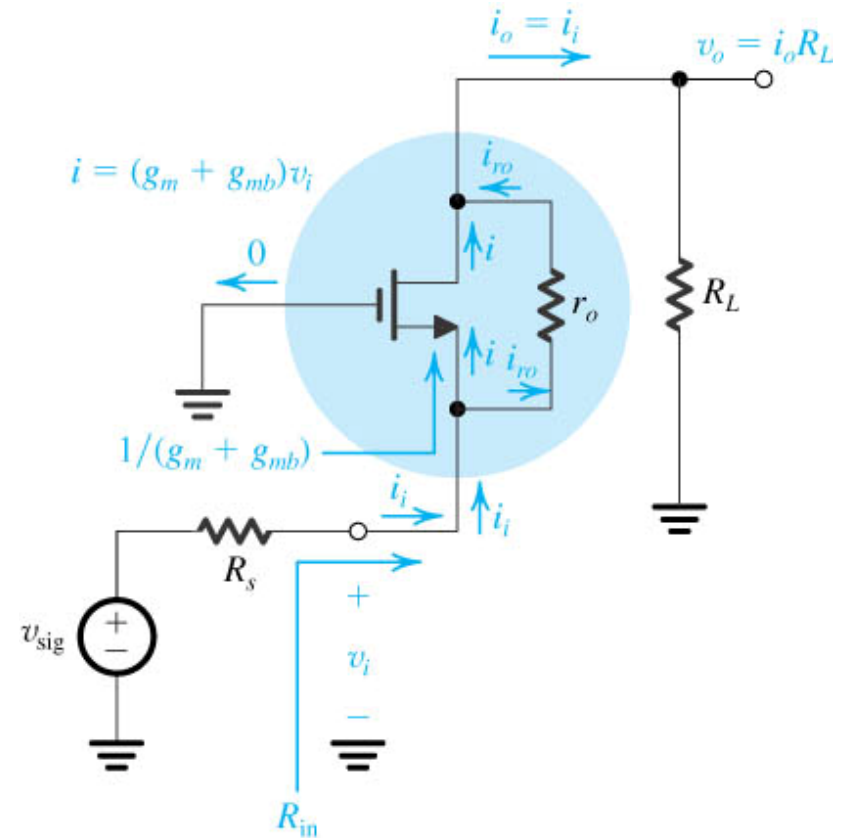


(c)

- $V_b$  is different from  $V_s$ .

- Circuits to calculate  $R_{in}$



# Common-Gate Amplifier

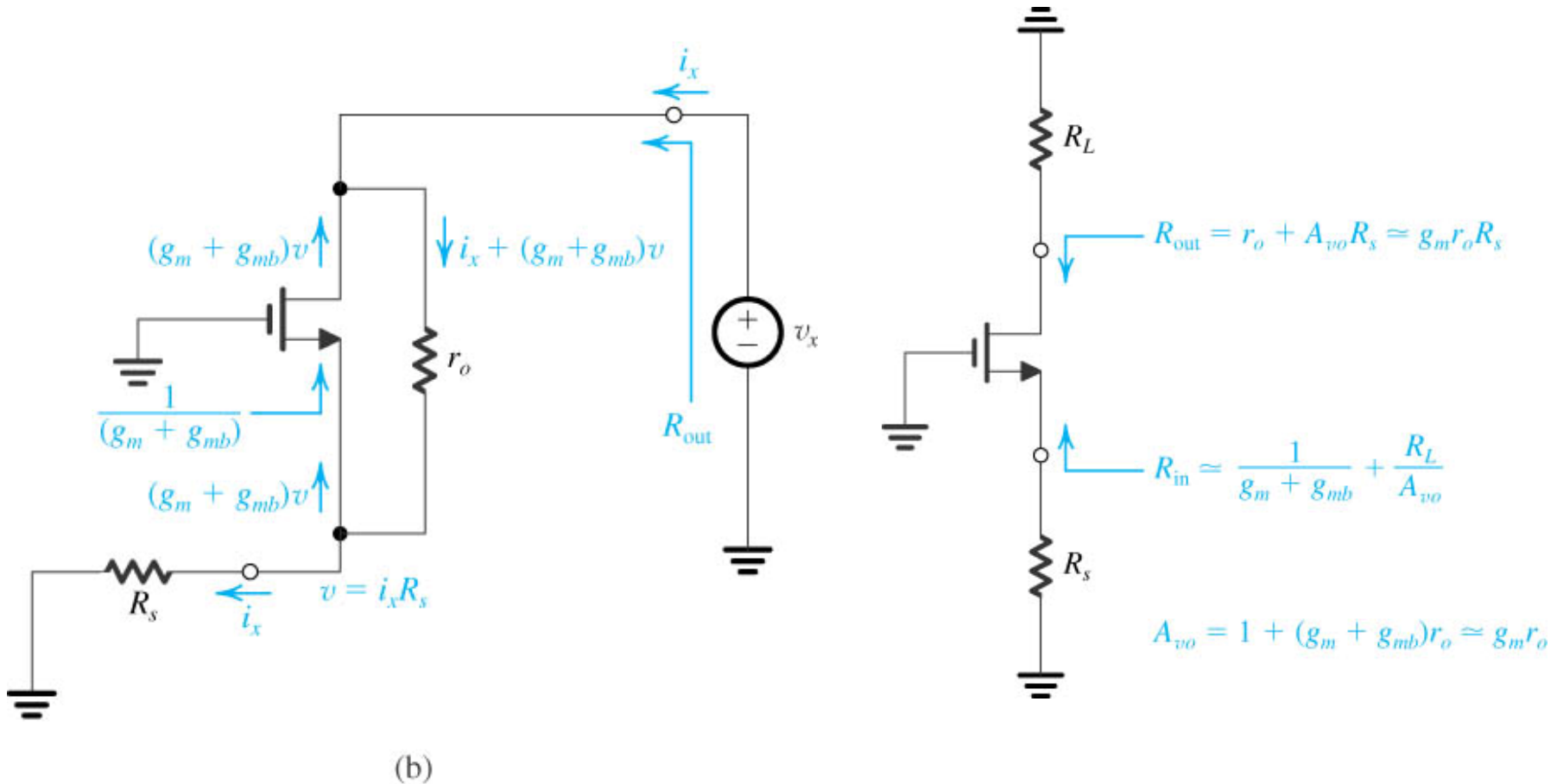

- Circuits to calculate  $R_{out}$

- Impedance transformation

# Source Follower

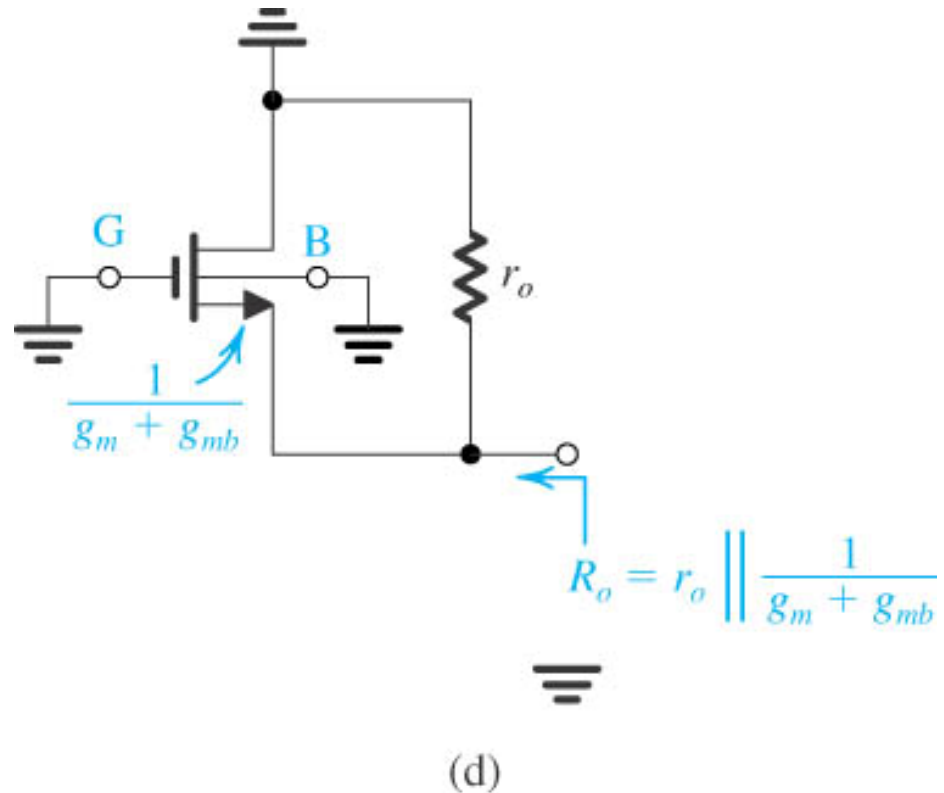 

- No voltage gain ( $\sim 1$ ).

- Circuits to calculate  $R_{out}$