

10.3.8 Transistor Sizing

 


Figure 10.16 Proper transistor sizing for a four-input NOR gate.


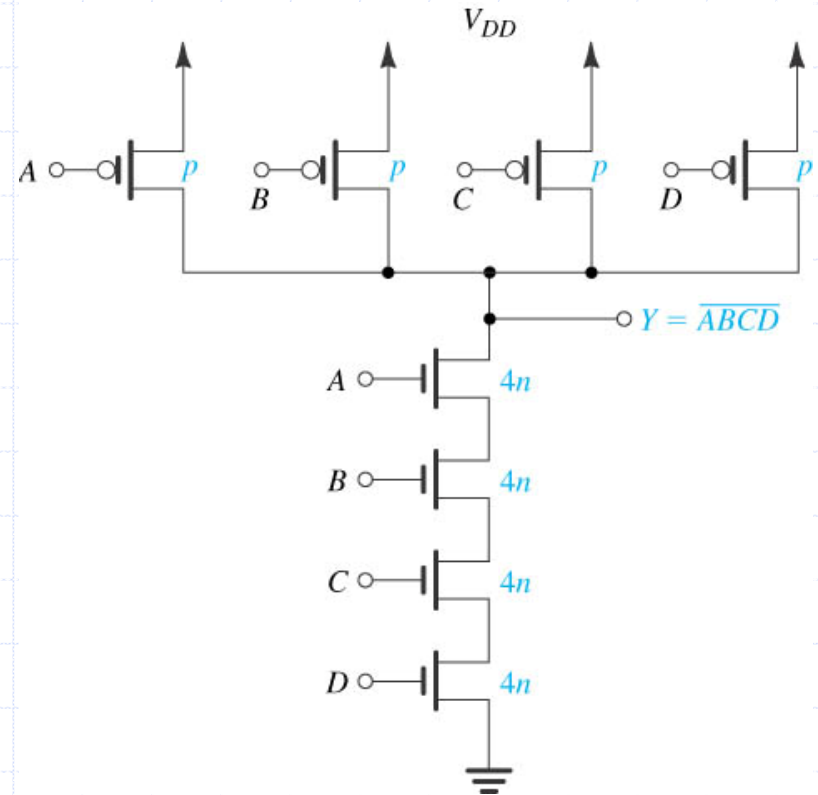






Figure 10.17 Proper transistor sizing for a four-input NAND gate.

10.4 Pseudo-NMOS Logic Circuits

MOS inverter

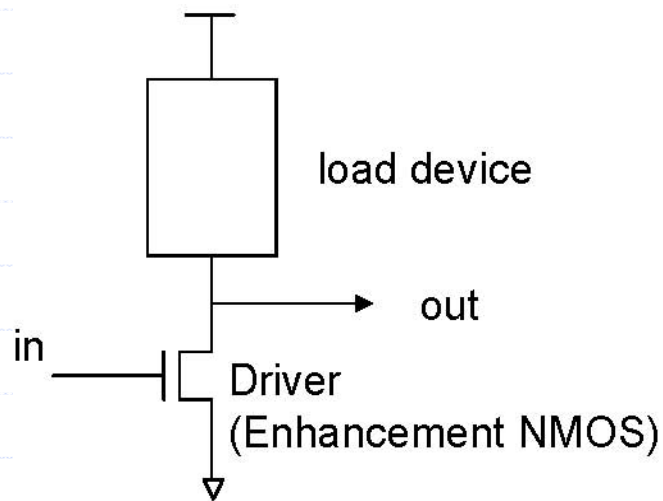

Load device

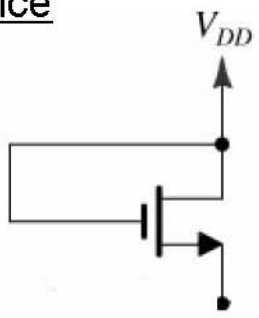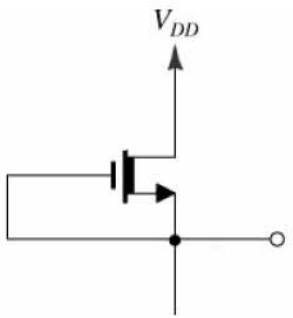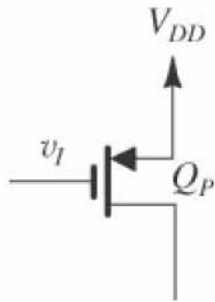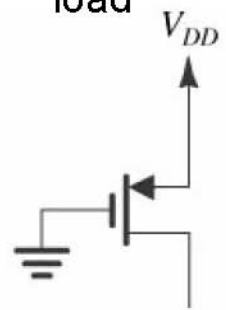- ① Enhancement NMOS load

- ② Depletion NMOS load

- ③ CMOS inverter load

- ④ Pseudo-NMOS load


10.4.1 The Pseudo-NMOS Inverter

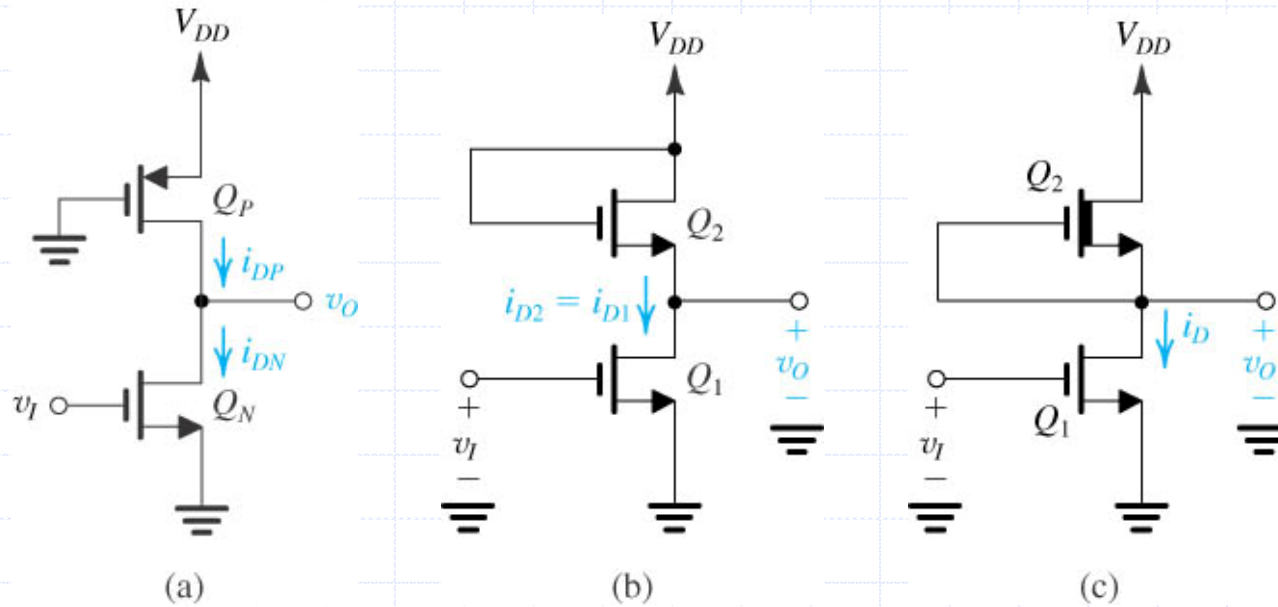


Figure 10.19 (a) The pseudo-NMOS logic inverter. (b) The enhancement-load NMOS inverter. (c) The depletion-load NMOS inverter.

10.4.2 Static Characteristics

Static Characteristics


- Load curve represents a much lower saturation current.
- k_n is usually greater than k_p by a factor of 4 to 10.
- $V_{OH} = V_{DD}$
- $V_{OL} > 0$ (nonzero V_{OL} for pseudo-NMOS)

$$i_{DN} = \frac{1}{2} k_n (v_I - V_t)^2 \quad \text{for } v_O \geq v_I - V_t \quad (\text{saturation})$$


$$i_{DN} = k_n \left[(v_I - V_t)v_O - \frac{1}{2}v_O^2 \right] \quad \text{for } v_O \leq v_I - V_t \quad (\text{triode})$$

$$i_{DP} = \frac{1}{2} k_p (V_{DD} - V_t)^2 \quad \text{for } v_O \leq V_t \quad (\text{saturation})$$
 
$$i_{DP} = k_p \left[(V_{DD} - V_t)(V_{DD} - v_O) - \frac{1}{2}(V_{DD} - v_O)^2 \right] \quad \text{for } v_O \geq V_t \quad (\text{triode})$$



10.4.3 Derivation of the VTC

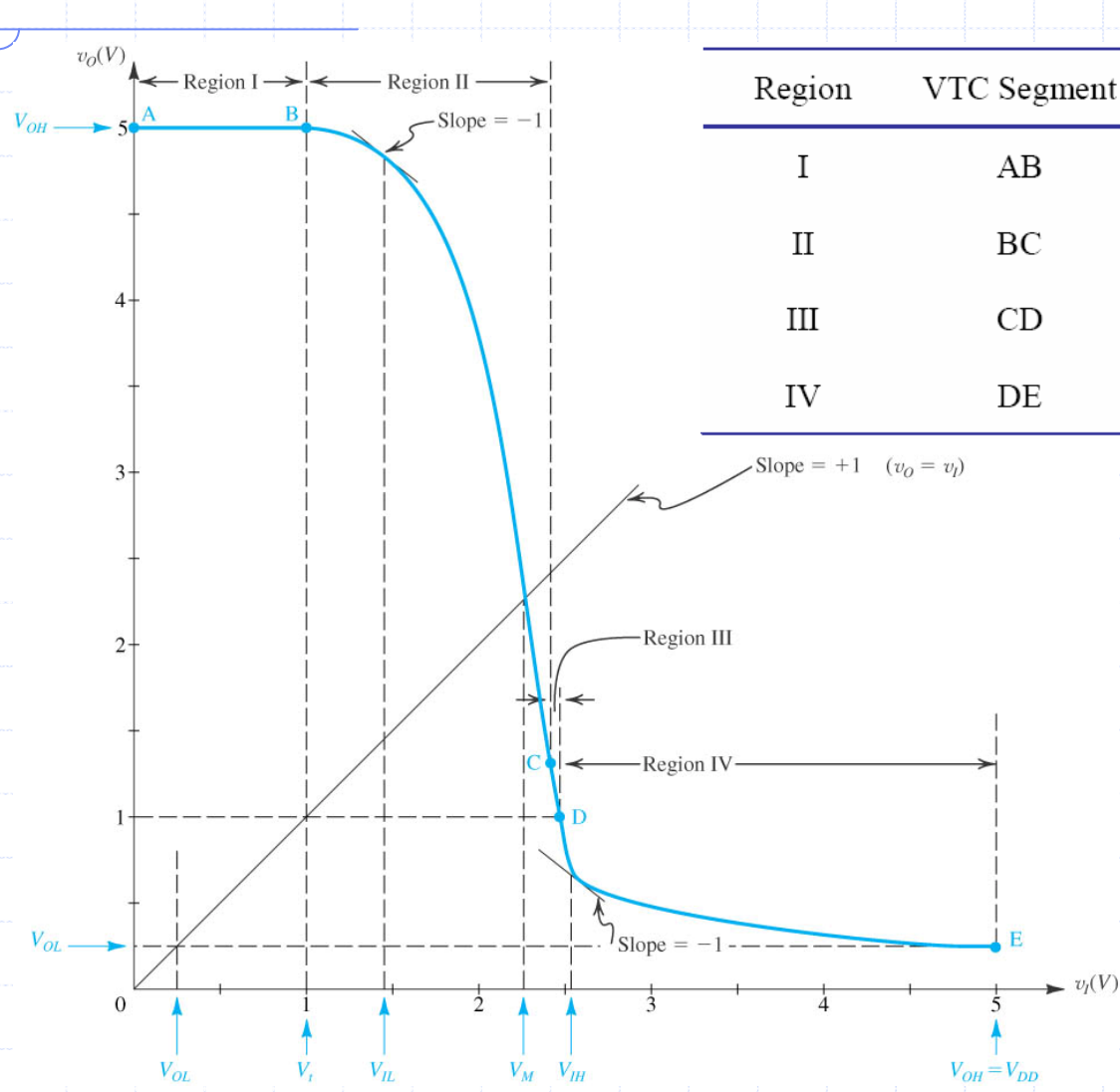

Region	VTC Segment	Q _N	Q _P	Condition
I	AB	Cut-off	Triode	$v_I < V_t$
II	BC	Saturation	Triode	$v_O > v_I - V_t$
III	CD	Triode	Triode	$V_t < v_O < v_I - V_t$
IV	DE	Triode	Saturation	$v_O < V_t$

10.4.4 Dynamic Operation

$$i_{DP}(0) = \frac{1}{2} k_P' \left(\frac{W}{L} \right)_P (V_{DD} - V_t)^2$$

$$i_{DP}(t_{PLH}) = k_P' \left(\frac{W}{L} \right)_P \left[(V_{DD} - V_t) \frac{V_{DD}}{2} - \frac{1}{2} \left(\frac{V_{DD}}{2} \right)^2 \right]$$

$$i_{DP}|_{av} = \frac{1}{2} [i_{DP}(0) + i_{DP}(t_{PLH})]$$

$$t_{PLH} = \frac{C \Delta V}{i_{DP}|_{av}} = \frac{C V_{DD} / 2}{i_{DP}|_{av}}$$

for $V_t \cong 0.2V_{DD}$,

$$t_{PLH} = \frac{1.7C}{k_P' \left(\frac{W}{L} \right)_P V_{DD}}$$

for a large value of r,

$$t_{PHL} \cong \frac{1.7C}{k_N' \left(\frac{W}{L} \right)_N V_{DD}}$$

10.4.6 Gate Circuits



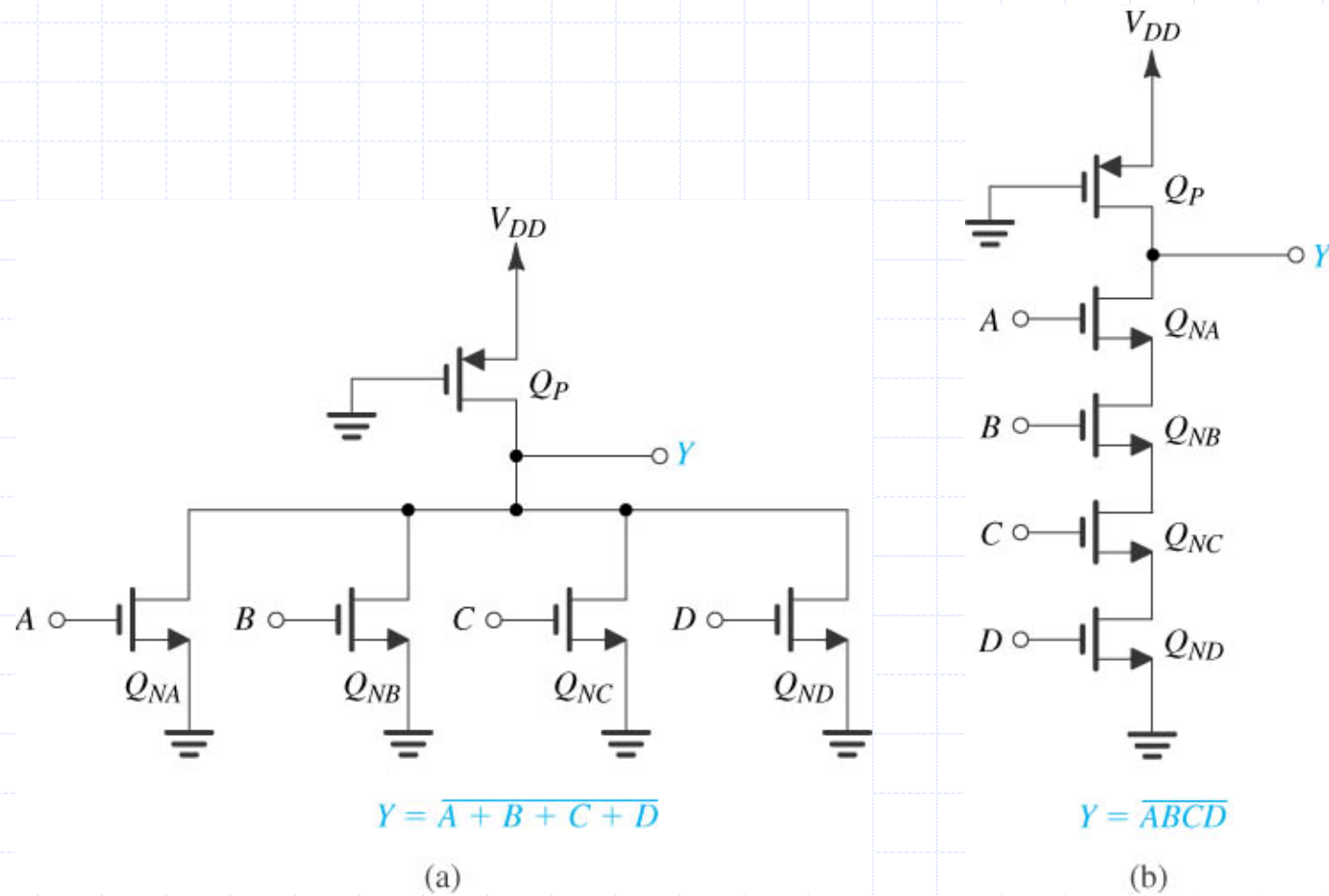


Figure 10.22 NOR and NAND gates of the pseudo-NMOS type.


10.5 Pass-Transistor Logic Circuits

 


Series $Y = ABC$

 

Parallel $Y = A(B+C)$

 


Single NMOS gate

 


Transmission gate

10.5.1 An Essential Design Requirement

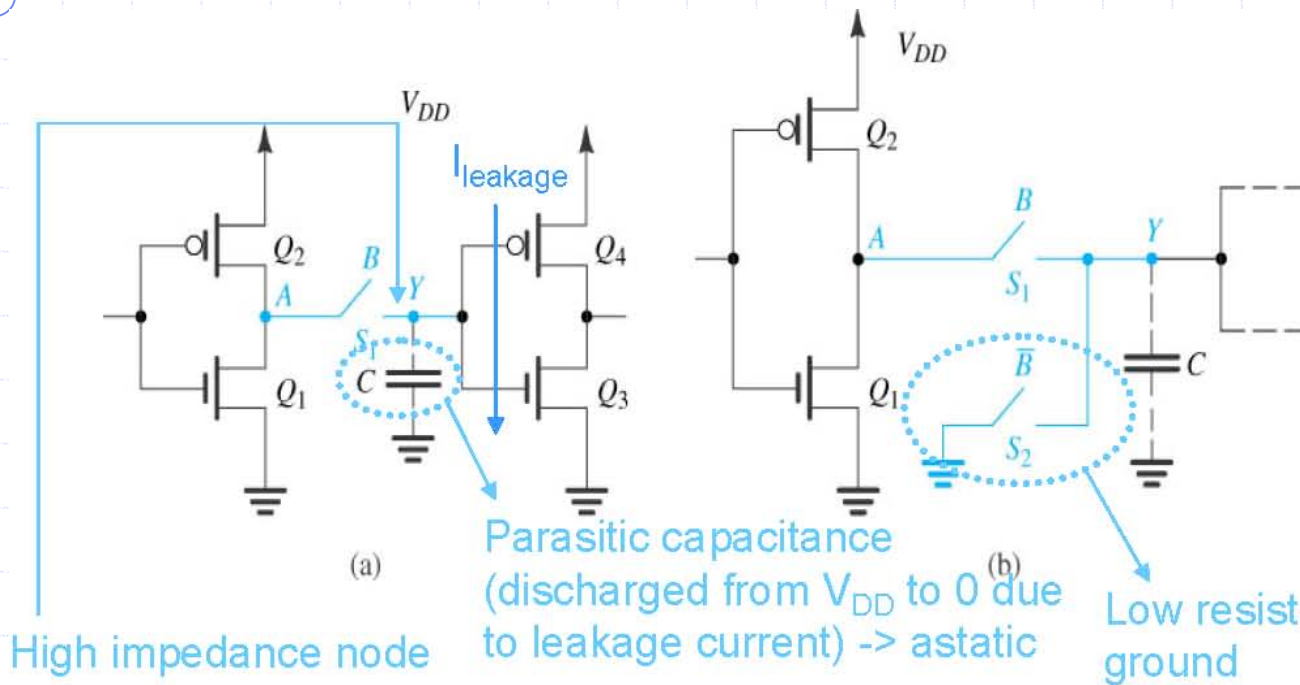

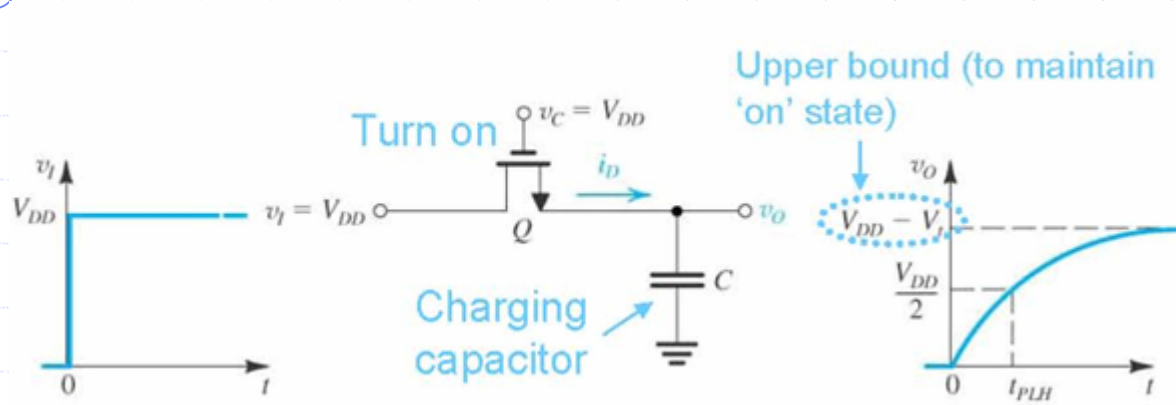
10.5.2 Operation with NMOS Transistors as Switches





Single NMOS transistor when input is high

$$i_D = \frac{1}{2} k_n (V_{DD} - v_o - V_t)^2$$


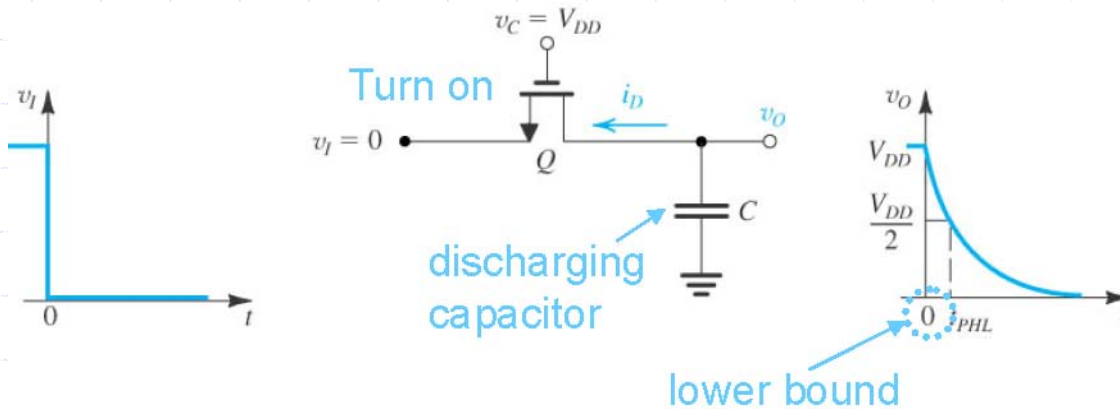
$$V_t = V_{t0} + \gamma (\sqrt{v_o + 2\phi_f} - 2\sqrt{2\phi_f})$$



  
10.5.3 The Use of CMOS Transmission Gates as Switches



 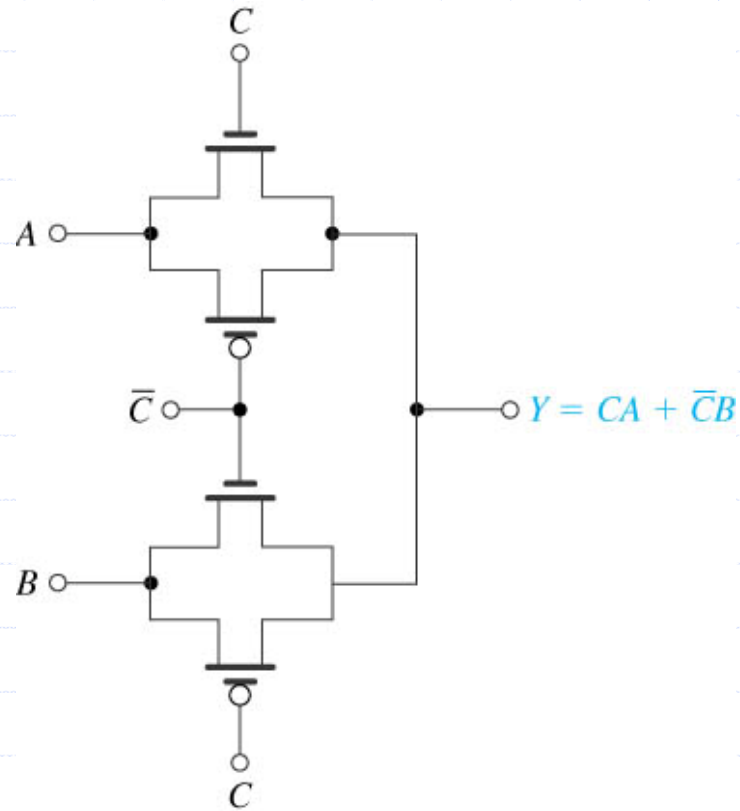10.5.4 Pass-Transistor Logic Circuit Examples



 10.5.4 Pass-Transistor Logic Circuit Examples



$$Y = AB + B\bar{B} = AB$$

$$\begin{aligned} Y &= \bar{A}B + \bar{B}\bar{B} = \bar{A}B + \bar{B} \\ &= \bar{A}B + (1 - B) = 1 - B(1 - \bar{A}) \\ \bar{Y} &= \bar{A} + \bar{B} = \overline{AB} = 1 - AB = \overline{AB} \end{aligned}$$

10.6 Dynamic Logic

 


Figure 10.33 (a) Basic structure of dynamic-MOS logic circuits. (b) Waveform of the clock needed to operate the dynamic logic circuit. (c) An example circuit.

10.6.2 Non-ideal Effects

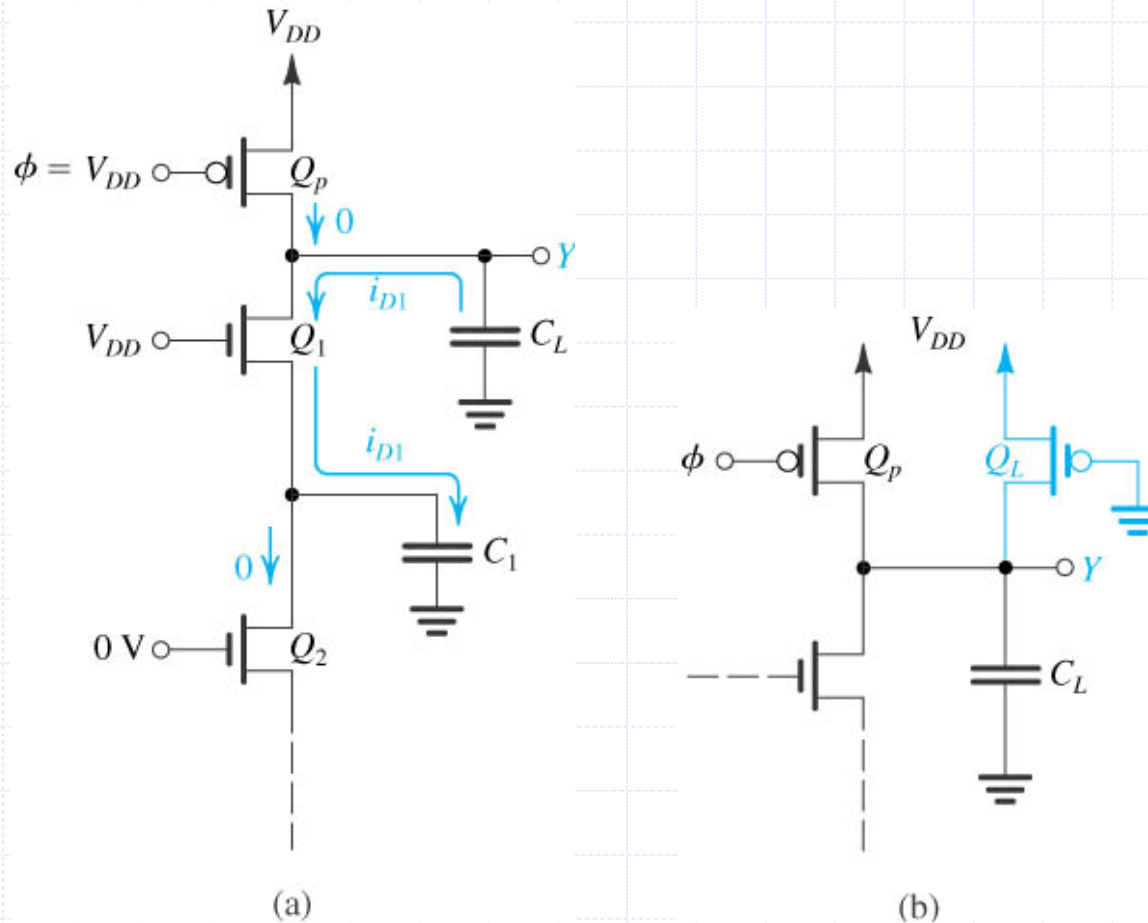


Figure 10.34 (a) Charge sharing. (b) Adding a permanently turned-on transistor Q_L solves the charge-sharing problem at the expense of static power dissipation.

10.6.2 Non-ideal Effects


 


Figure 10.35 Two single-input dynamic logic gates connected in cascade. With the input A high, during the evaluation phase C_{L2} will partially discharge and the output at Y_2 will fall lower than V_{DD} , which can cause logic malfunction.

10.6.3 Domino CMOS Logic

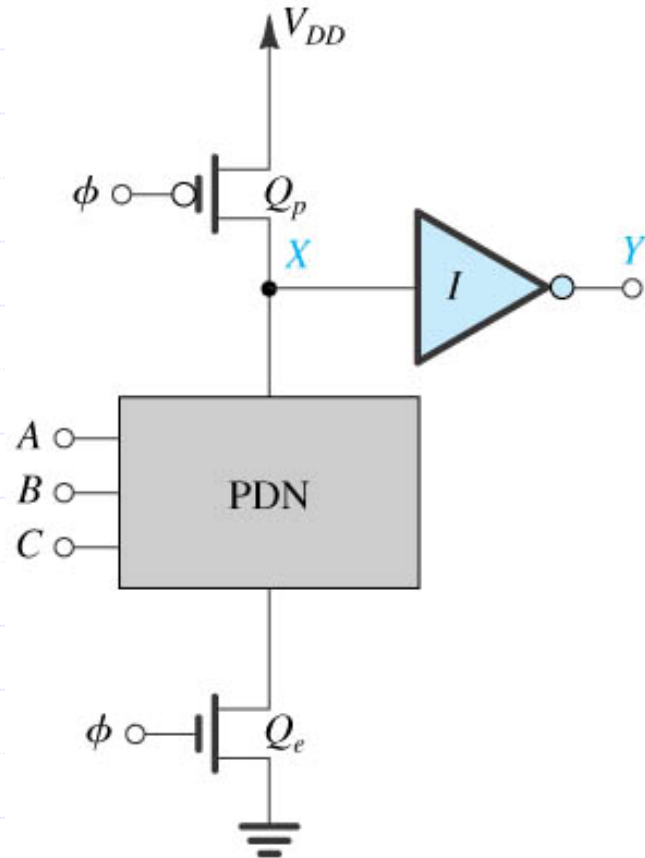

◆ Domino logic

- N-type dynamic logic + inverter
- Cascadable gates
- During the precharge, $X \rightarrow V_{DD}$, $Y \rightarrow '0'$
- During the evaluation, $Y \rightarrow V_{DD}$ or $Y \rightarrow '0'$

10.6.3 Domino CMOS Logic

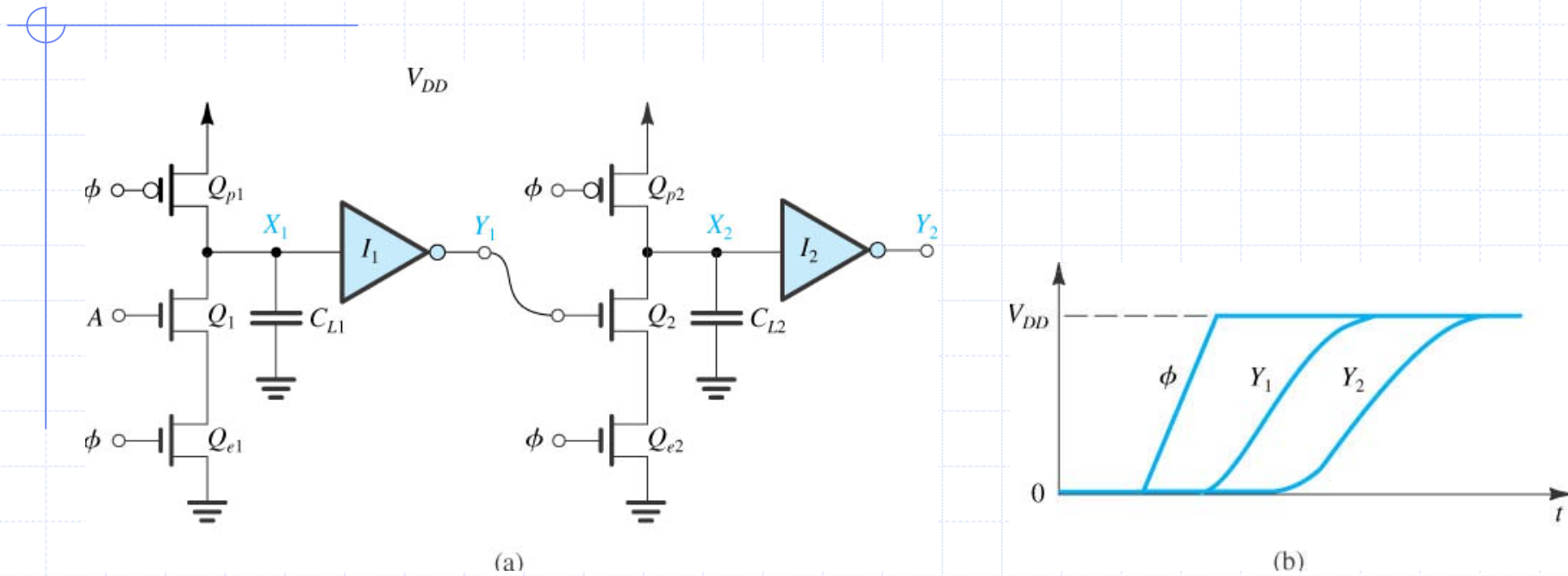


Figure 10.37 (a) Two single-input domino CMOS logic gates connected in cascade. (b) Waveforms during the evaluation phase.