

11.1 Bandgap References

Deog-Kyoon Jeong

dkjeong@snu.ac.kr

School of Electrical and Computer Engineering

Seoul National University

2020 Fall


Compliment to SeungHyun Lee

What is required of a reference?

- DC voltage or current that is
 1. Independent of the Supply variation
 - e.g.: V_{CC} : 2.7V \rightarrow 3.0V
 2. Independent of the Temperature variation
 - e.g.: T: -20°C \rightarrow 80°C
 3. Independent of the process variation
 - e.g.: β of BJTs: $\pm 30\%$

Temperature-Independent References

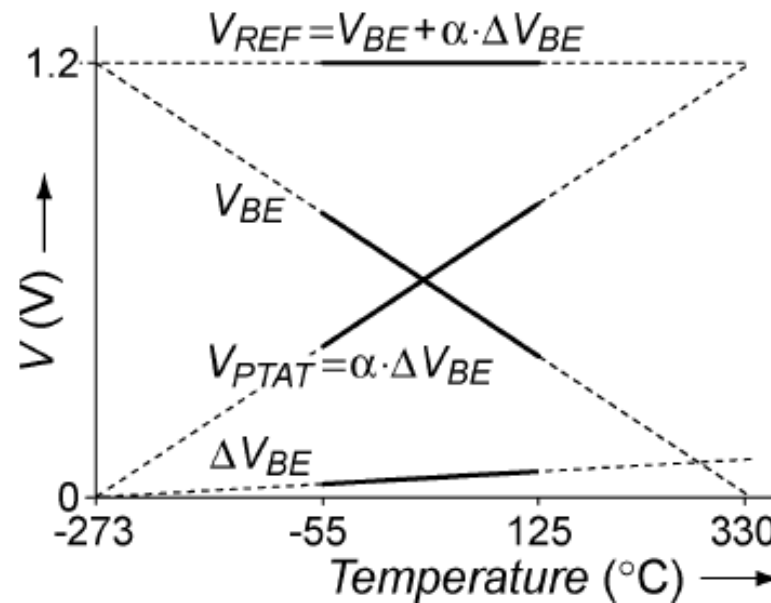- $V_{REF} = \alpha_1 V_1 + \alpha_2 V_2$ (V_1 is Proportional To Absolute Temperature, PTAT, and V_2 Complementary TAT, CTAT)



Temperature dependency of the key voltages in the sensor.

[M. Pertijs, JSSC, 2005]

Negative-TC Voltage

- The base-emitter voltage of a bipolar transistor V_{BE} exhibits a negative TC.
- For a bipolar device, $I_C = I_S \exp\left(\frac{V_{BE}}{V_T}\right)$, where $V_T = \frac{kT}{q}$ and I_S is proportional to $\mu_k T n_i^2$.
- Temperature dependence: $\mu \propto \mu_0 T^m$, where $m \approx -\frac{2}{3}$ and $n_i^2 \propto T^3 \exp\left[\frac{-E_g}{kT}\right]$, where $E_g \approx 1.12$ eV is the bandgap energy of silicon.
- Thus, $I_S = b T^{4+m} \exp\left[\frac{-E_g}{kT}\right]$ (b is a proportional factor).

Negative-TC Voltage

- Writing $V_{BE} = V_T \ln\left(\frac{I_C}{I_S}\right)$, and assuming for now that I_C is held constant,

$$\frac{\partial V_{BE}}{\partial T} = \frac{\partial V_T}{\partial T} \ln \frac{I_C}{I_S} - \frac{V_T}{I_S} \frac{\partial I_S}{\partial T}$$

- Since


$$\frac{\partial I_S}{\partial T} = b(4+m)T^{3+m} \exp\left(-\frac{E_g}{kT}\right) + bT^{4+m} \left(\exp\left(-\frac{E_g}{kT}\right)\right) \left(\frac{E_g}{kT^2}\right) \Rightarrow \frac{V_T}{I_S} \frac{\partial I_S}{\partial T} = (4+m) \frac{V_T}{T} + \frac{E_g}{kT^2} V_T$$

$$\frac{\partial V_{BE}}{\partial T} = \frac{\partial V_T}{\partial T} \ln \frac{I_C}{I_S} - \frac{V_T}{I_S} \frac{\partial I_S}{\partial T} = \frac{V_{BE} - (4+m)V_T - E_g/q}{T}$$

Thus, with $V_{BE} \approx 750$ mV and $T = 300$ K, $\partial V_{BE} / \partial T \approx -1.5$ mV/K

Positive-TC Voltage

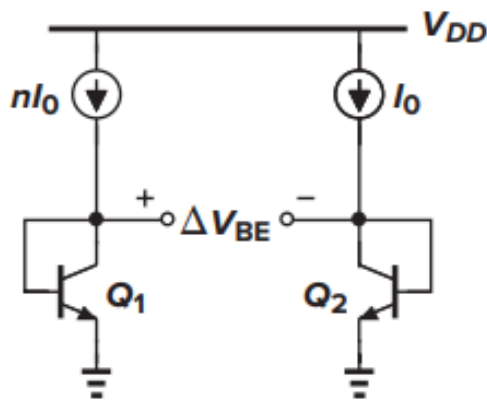- The difference between two base-emitter voltages, ΔV_{BE} exhibits a positive-TC.




$$\begin{aligned}\Delta V_{BE} &= V_{BE1} - V_{BE2} \\ &= V_T \ln \frac{nI_0}{I_{S1}} - V_T \ln \frac{I_0}{I_{S2}} \\ &= V_T \ln n \\ \frac{\partial \Delta V_{BE}}{\partial T} &= \frac{k}{q} \ln n\end{aligned}$$

- To compensate for -1.5 mV/K , $\ln n \approx 17.2$, hence $n \approx 2.95 \times 10^7$!!

Bandgap Reference

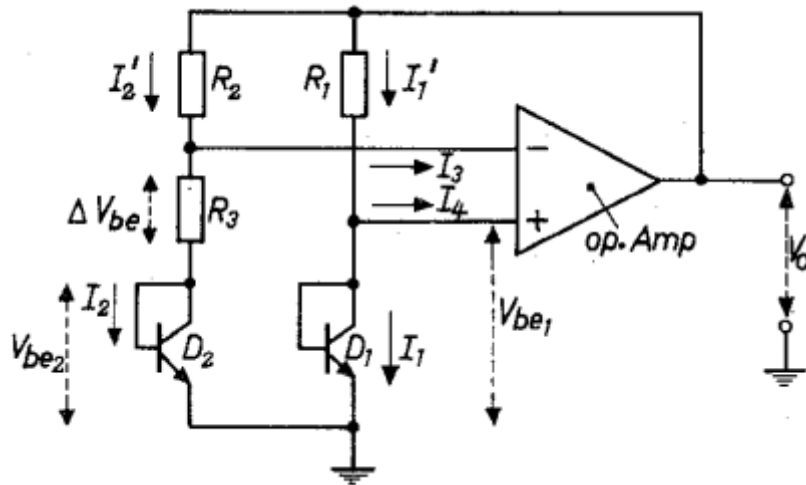- Large n can be mitigated if ΔV_{BE} is “Amplified” before it is added to V_{BE} .



$$V_{out} = V_{BE2} + \frac{V_T \ln n}{R_3} (R_3 + R_2)$$


$$= V_{BE2} + (V_T \ln n) \left(1 + \frac{R_2}{R_3} \right)$$

[K. KUIJK, JSSC, 1973]

Bipolar Bandgap Reference


Three issues

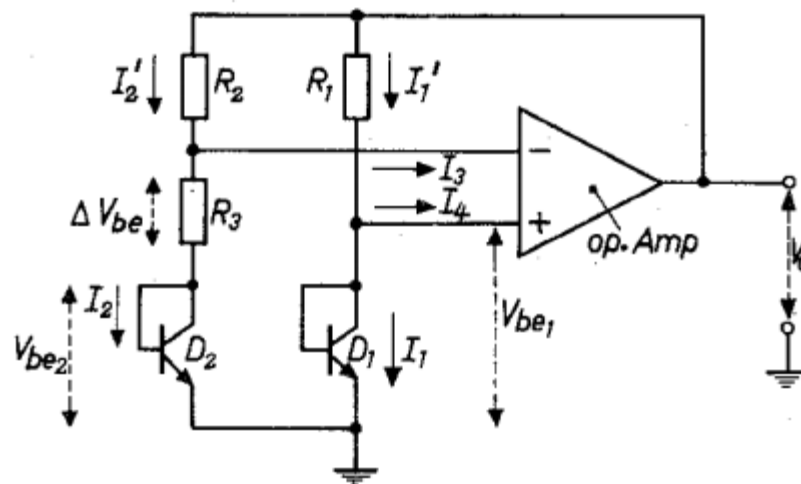1. Gain-power-stability trade-offs
2. NPN bipolar transistors
3. Op-amp offset



CMOS bandgap Reference

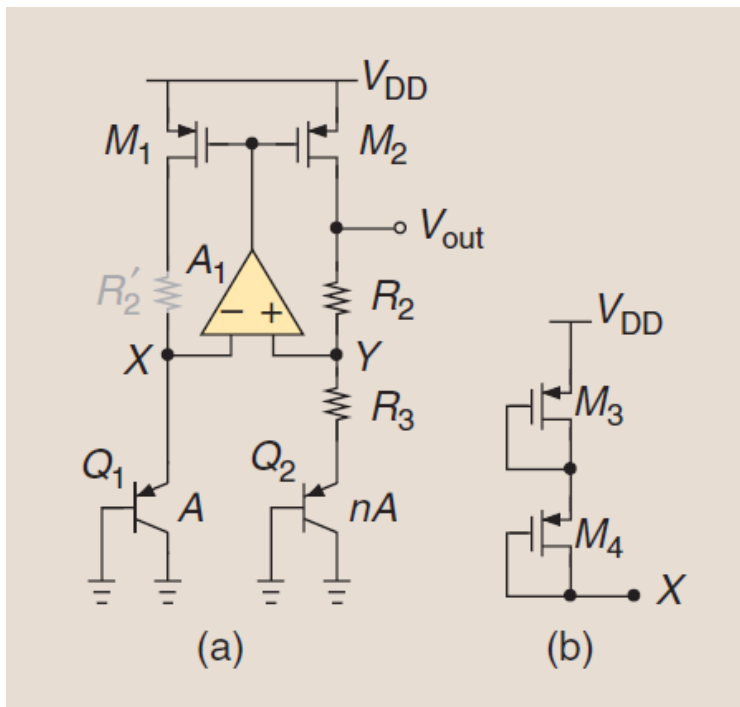- Replace resistors with controlled current sources.
- Bipolar transistors are implemented as PNP structures.
- Large n & non-unity ratio between I_{E1} and I_{E2} .




[B. Razavi, IEEE SSC Magazine , 2016]

Low-Voltage Bandgap Reference (1)

- In (a), V_{out} is still around 1.25V.
- In (b), V_{out} is arbitrarily small, about 700-800mV.

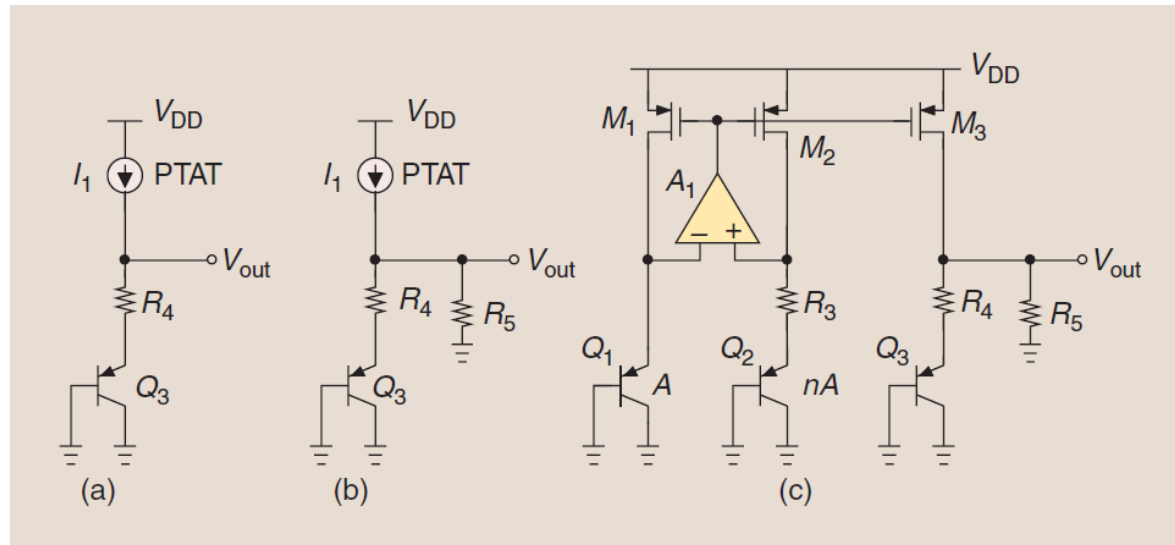
$$V_{out} = \frac{R_5}{R_5 + R_4} (R_4 I_1 + V_{BE3}),$$



[B. Razavi, IEEE SSC Magazine , 2016]

Low-Voltage Bandgap Reference (2)

- Use of shunt resistors

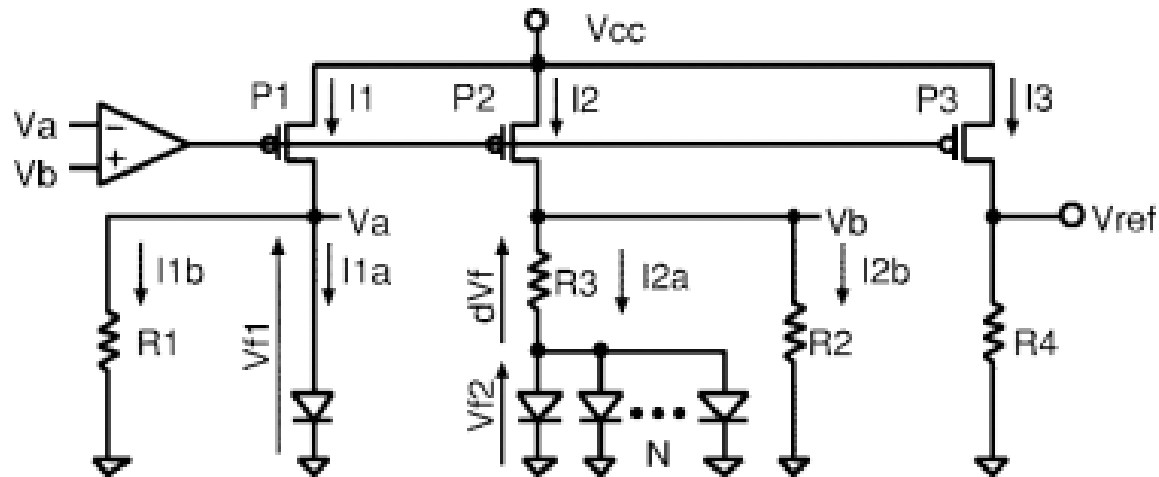


$$V_{\text{ref}} = R4 \left(\frac{V_{f1}}{R2} + \frac{dV_f}{R3} \right) \equiv V_{\text{ref-prop}}$$

$$V_{\text{ref-prop}} = \frac{R4}{R2} V_{\text{ref-conv}}$$

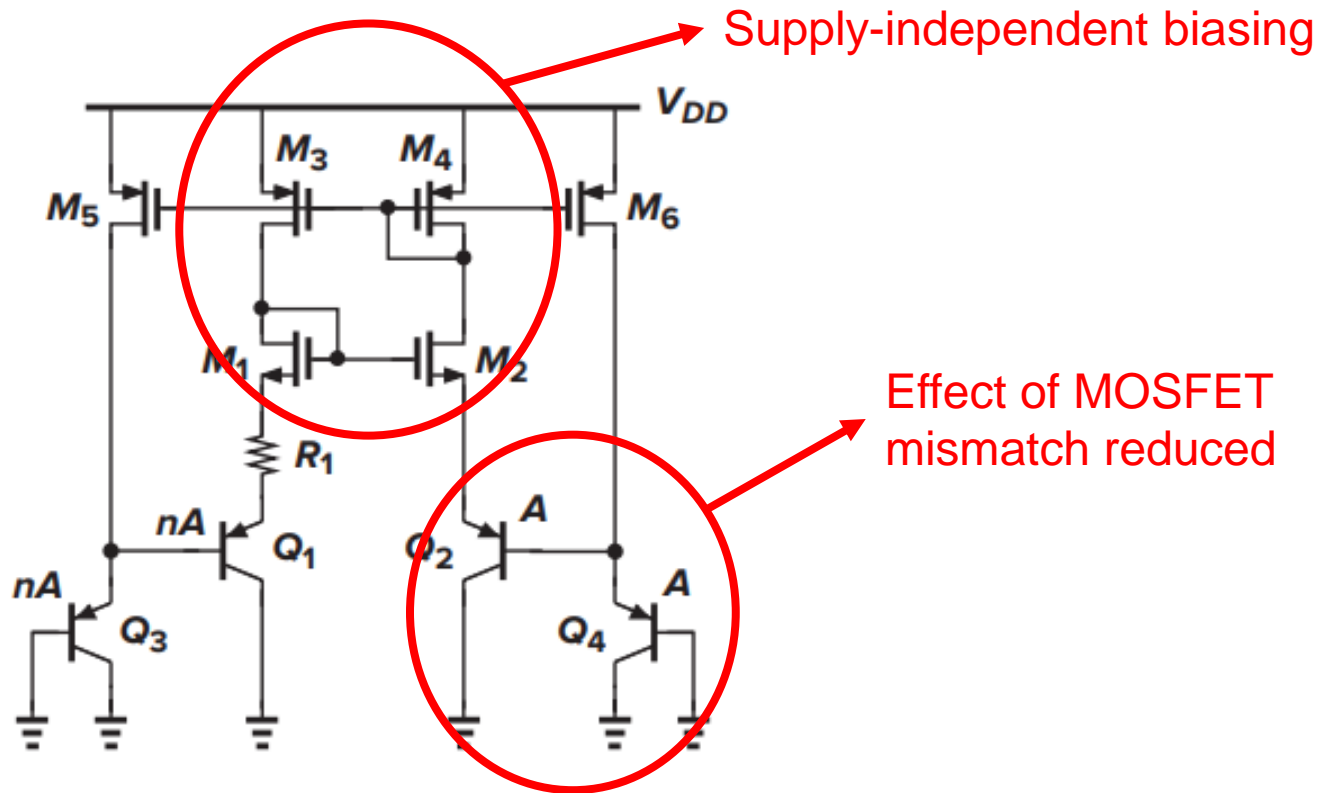[H. Banda, JSSC, 1999]

PVT-Tolerant Bandgap Reference

- Effect of device mismatches is reduced.



[T. Brooks, ISSCC , 1994]

Compatibility with CMOS Technology

- p+ diffusion inside n-well → Emitter
- n-well → Base
- p- substrate → Collector


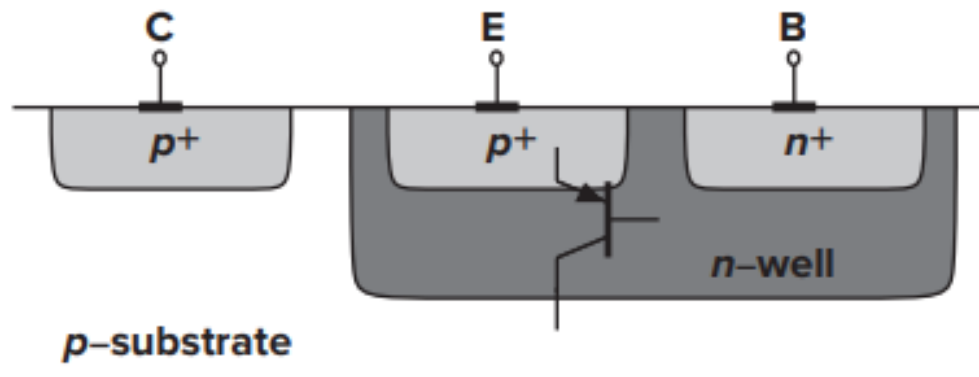


Figure 12.10 Realization of a *pnp* bipolar transistor in CMOS technology.

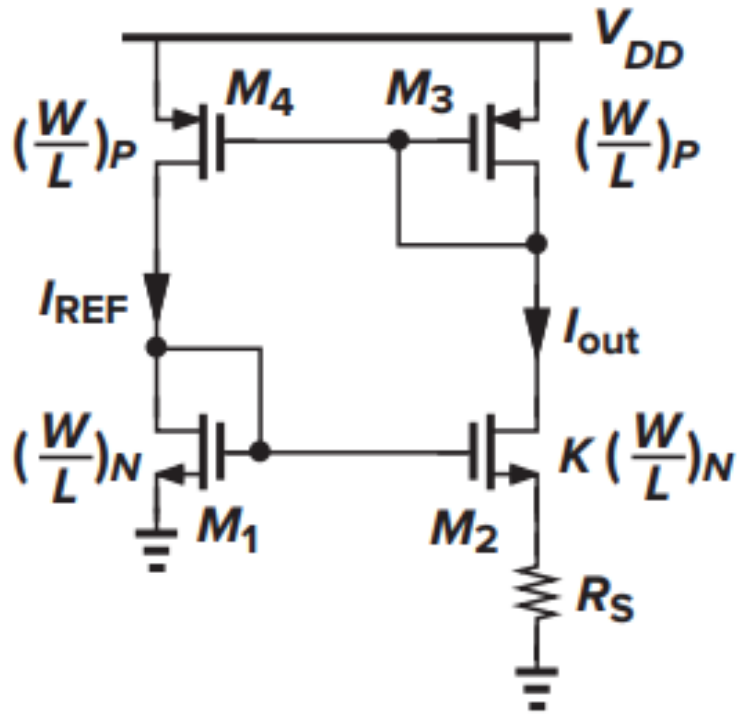[B. Razavi, Design of Analog CMOS Integrated Circuits]

Current Reference


- Use of Widlar Current Mirror.
- Current I_{out} is independent of the supply voltage.



$$I_{out} = \frac{2}{\mu_n C_{ox} (W/L)_N} \cdot \frac{1}{R_S^2} \left(1 - \frac{1}{\sqrt{K}} \right)^2$$

Current Reference with SC Resistor

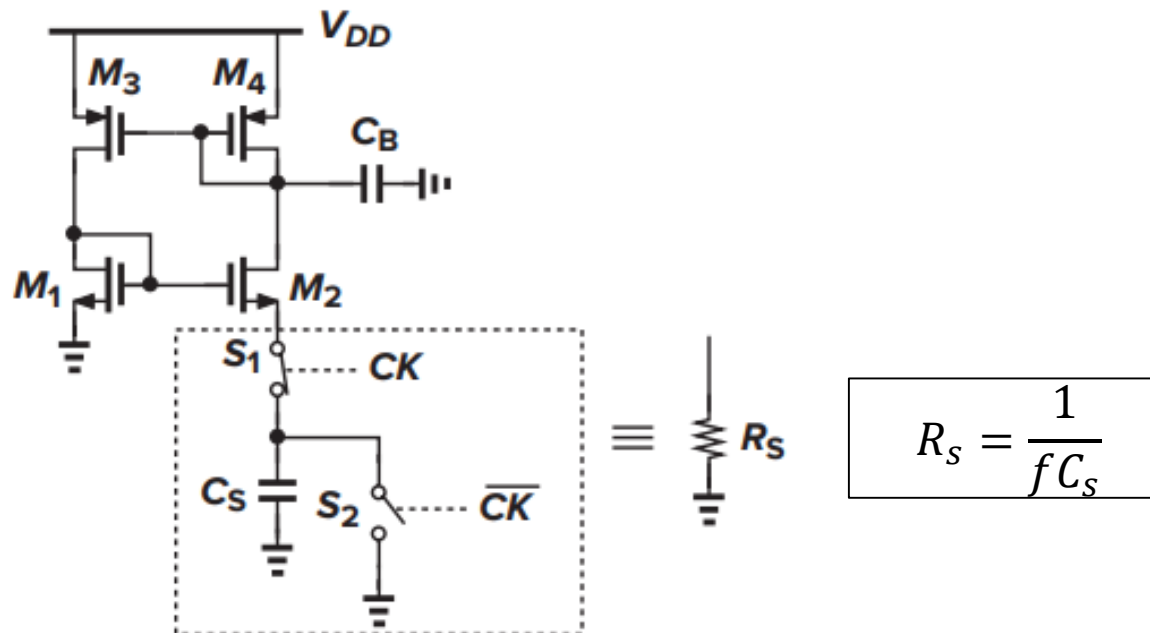- R_s can be replaced by a switched-capacitor equivalent: Temperature insensitivity.



References

- **K. E. Kujik, “A precision reference voltage source,” IEEE J. Solid-State Circuits, vol. 8, pp. 222–226, June 1973.**
- **H. Banba, H. Shiga, A. Umezawa, and T. Miyaba, “A CMOS bandgap reference circuit with sub-1-V operation,” IEEE J. SolidState Circuits,**
- **B. Razavi, “The bandgap reference,” IEEE Solid-State Circuits Mag., vol. 8, pp. 9–12, Summer 2016.**
- **B. Razavi, "Design of Analog CMOS Integrated Circuits", *Tata McGraw Hill*, 2002. , pp.509-533**
- **T. Brooks and A. L. Westwisk, “A Low-Power Differential CMOS Bandgap Reference,” ISSCC Dig. of Tech. Papers, pp. 248–249, February 1994.**