

Topics in IC Design

2.1 Introduction to Phase-Locked Loop

Deog-Kyoon Jeong
dkjeong@snu.ac.kr

School of Electrical and Computer Engineering
Seoul National University



2020 Fall

Outline

- Introduction
- Charge-Pump PLL building blocks
- Charge-Pump PLL dynamics
- Clock Synthesizers


What is PLL?

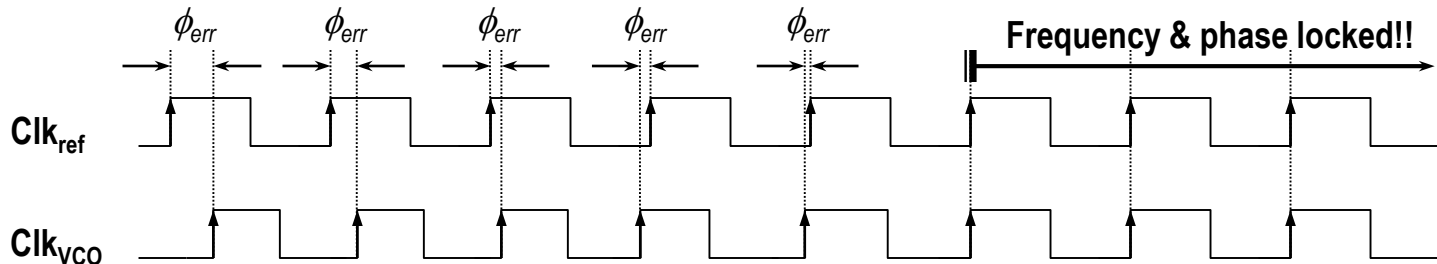 - A negative feedback system where an oscillator-generated signal is frequency and phase locked to a reference signal




PLL Applications (1)

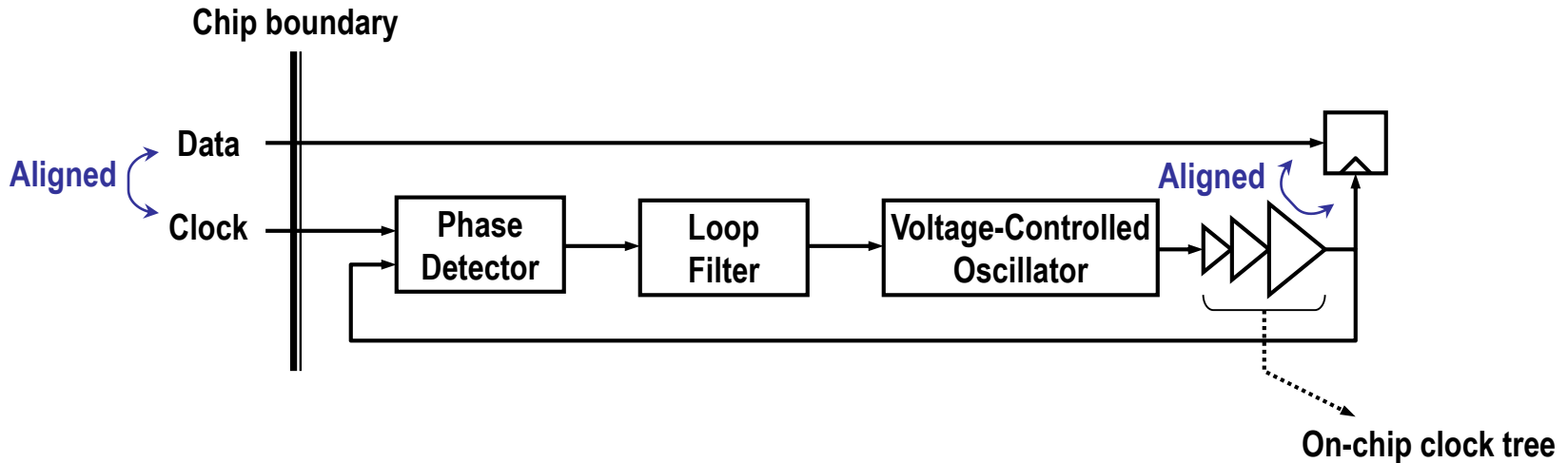- ❑ On-chip clock generator with reduced skew – Zero delay buffer
- ❑ Resolves skew problem due to on-chip clock tree




PLL Applications (2)

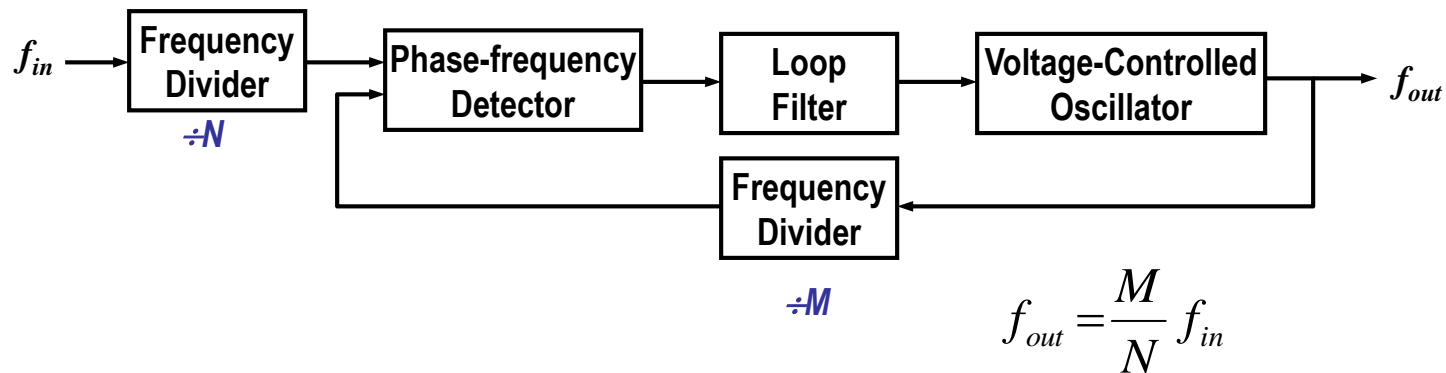- ❑ Clock frequency multiplication – On-chip clock generation
- ❑ Frequency synthesizer – Many RF applications




PLL Applications (3)

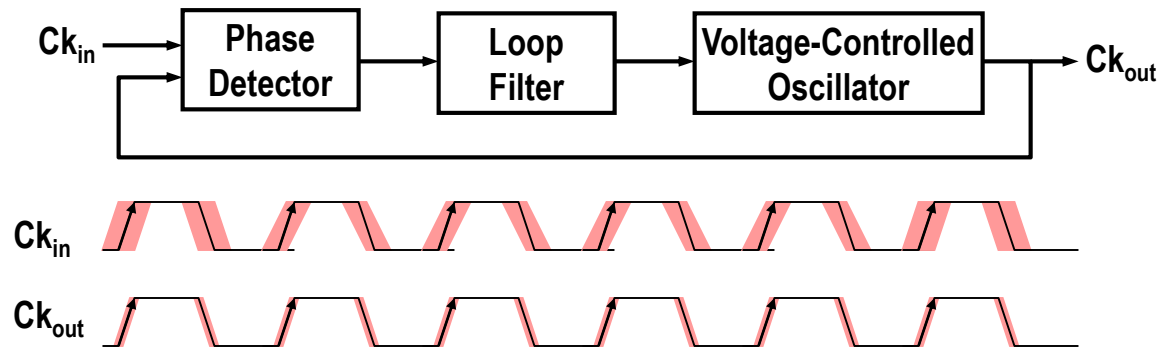- ❑ Jitter reduction
- ❑ PLL filters out low frequency jitter of input clock





PLL Applications (4)

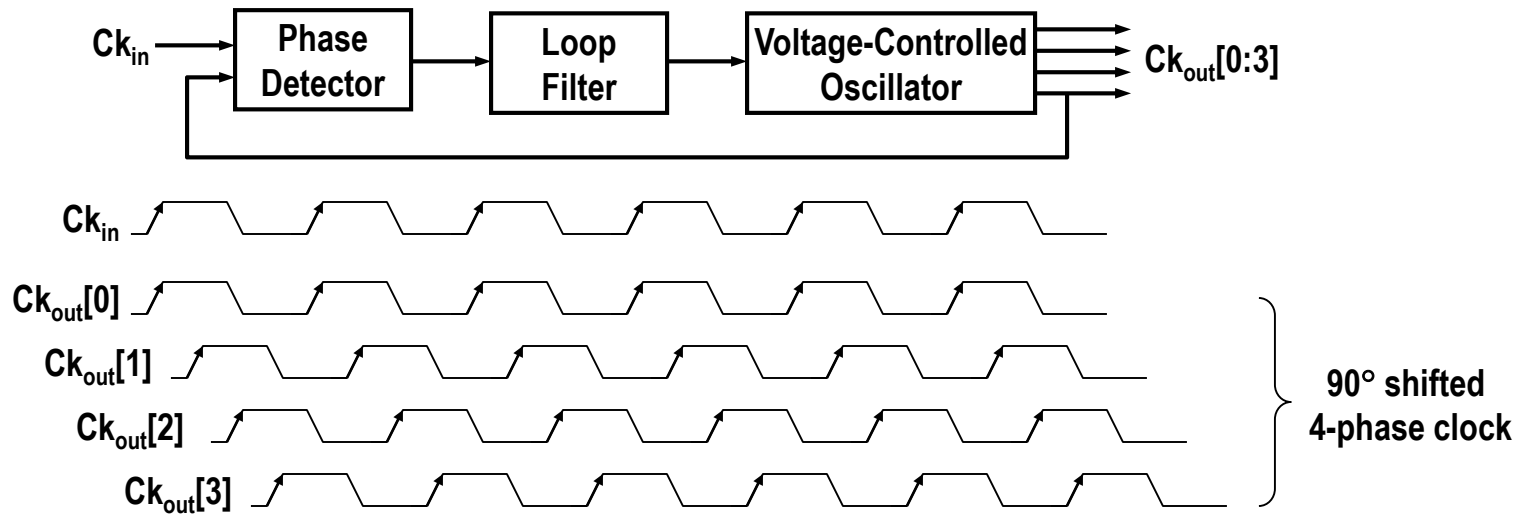- ❑ Multi-phase clock generation
- ❑ Multi-phase clock is very useful in many applications



PLL Applications (5)

  - ❑ Clock and data recovery
- ❑ Extracts timing information from NRZ data pattern




PLL aligns falling edge of Ck_{out} with data transition, so that the data is sampled at optimal point!!

PLL Building Blocks

- Voltage controlled oscillator (VCO)
- Phase detector (PD)
- Charge pump (CP)
- Loop filter (LF)
- Frequency divider



Charge-Pump PLL

 - ❑ Most of recent PLLs are of the charge-pump type
- ❑ PFD + CP – Converts digital phase-error signal to analog current
- ❑ 4 essential building blocks – VCO, PFD, CP, and loop filter
- ❑ 1 optional building block – Frequency divider





VCO

  - ❑ Self-resonating clock generator
- ❑ LC tank, ring oscillator, relaxation oscillator ...
- ❑ Performance parameters
 - ✓ Center frequency (No meaning for CP-PLL)
 - ✓ Tuning range
 - ✓ Tuning linearity
 - ✓ Power dissipation
 - ✓ Supply rejection ratio
 - ✓ Spectral purity




VCO

  - ❑ VCO gain – K_{VCO} (Hz/V or rad/s/V)
 - ✓ Large gain means wide tuning range, but more sensitive to control line noise in PLL
- ❑ Phase noise of VCO
 - ✓ If input clock is clean, VCO is a dominant noise source in PLL
 - ✓ White noise is modulated by VCO as a “skirt-like shape”



VCO Phase Noise Model

□ Leeson's model

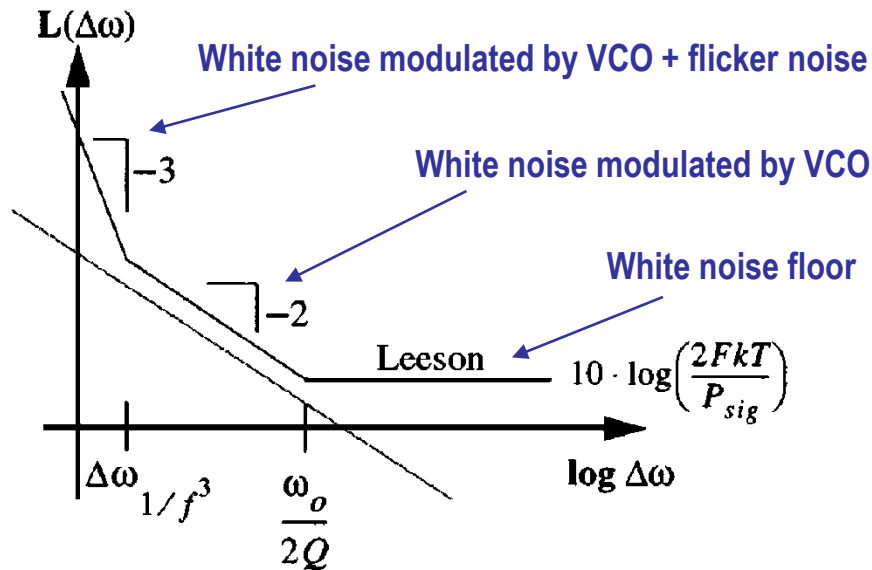

$$L\{\Delta\omega\} = 10 \log \left[\frac{2FkT}{P_{sig}} \left\{ 1 + \left(\frac{\omega_0}{2Q\Delta\omega} \right)^2 \right\} \left(1 + \frac{\Delta\omega_{1/f^3}}{|\Delta\omega|} \right) \right]$$


Low Noise VCO

- ❑ Use high-Q resonator
- ❑ Maximize signal swing – May result in more power dissipation
- ❑ Fast slew rate – Reduces signal transition time
- ❑ Symmetrical waveform
 - ❑ Robustness against flicker noise
 - ❑ Reduces low frequency phase noise

LC-Tank Oscillator

□ LC resonator as VCO

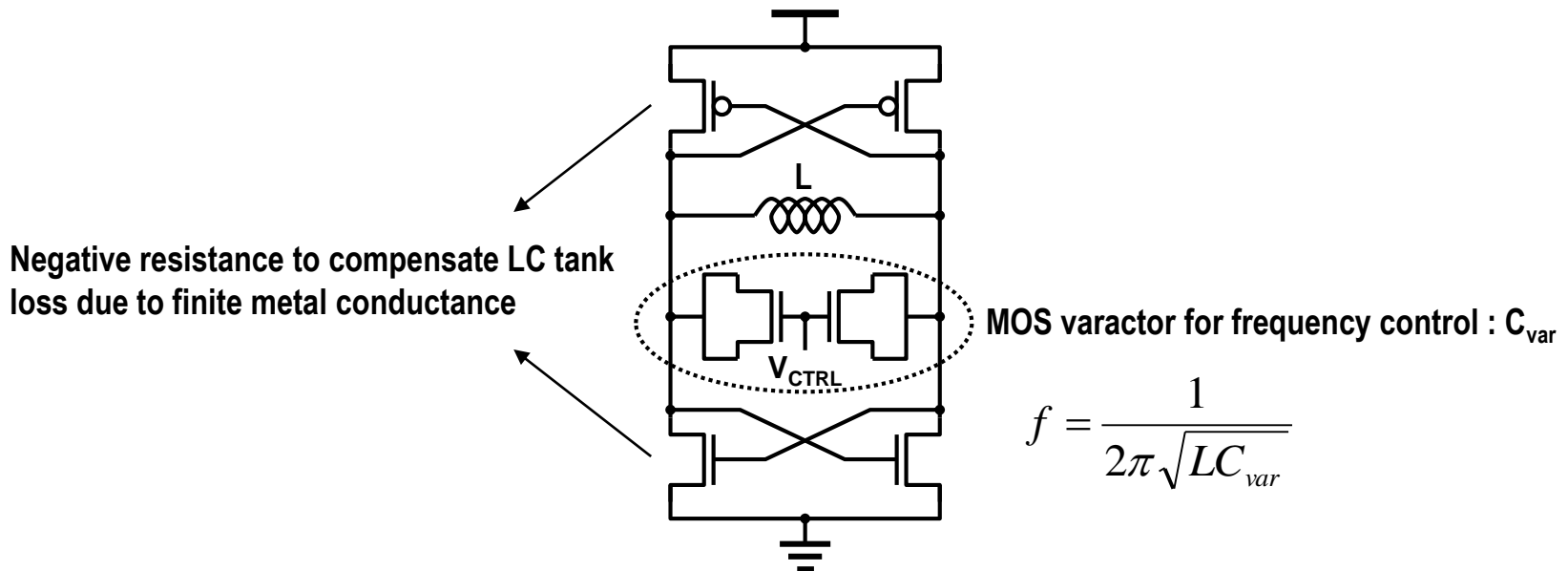
- ☺ Low noise
- ☺ Insensitive to PVT variation
- ☺ High-frequency
- ☹ Narrow tuning range
- ☹ Requires additional fabrication steps for spiral inductor – Thick top metal



Ring Oscillator

□ Chain of variable delay elements

 - ☺ Easy to implement
- ☺ Low cost
- ☺ Wide range
- ☹ Very sensitive to PVT variation
- ☹ Noisier than LC-tank




$$f = \frac{1}{2MT_d}$$


$$T_d = \frac{C\Delta V}{I} \Rightarrow$$

Single stage delay: Delay is controlled by varying C or ΔV or I


Delay Element Examples

 

(a) Capacitive tuning

 


(b) Starved inverter

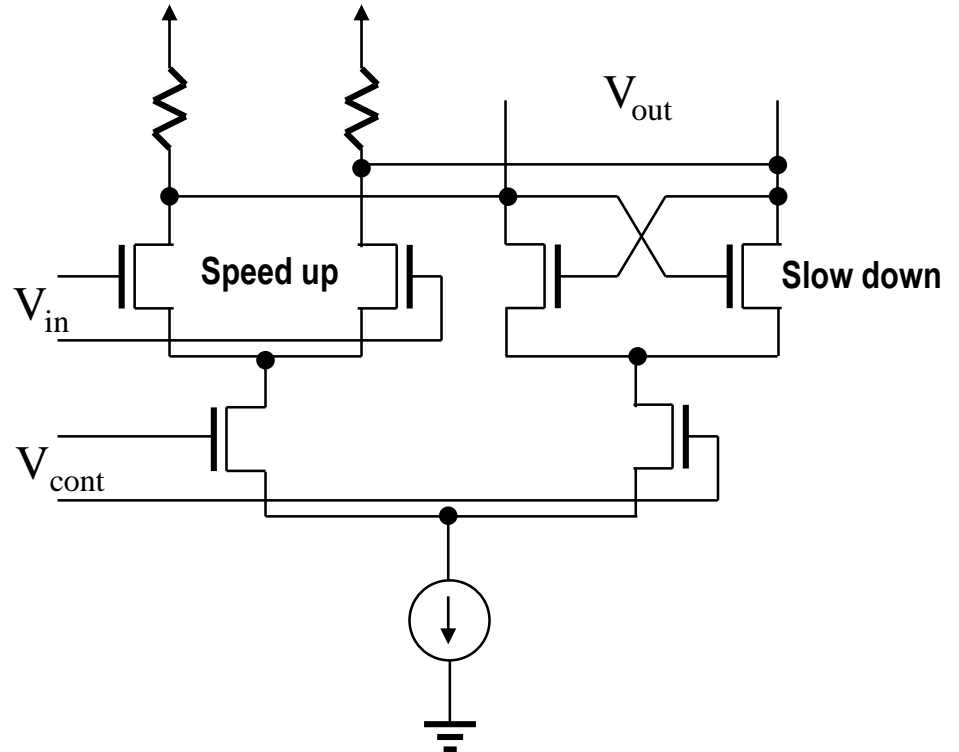

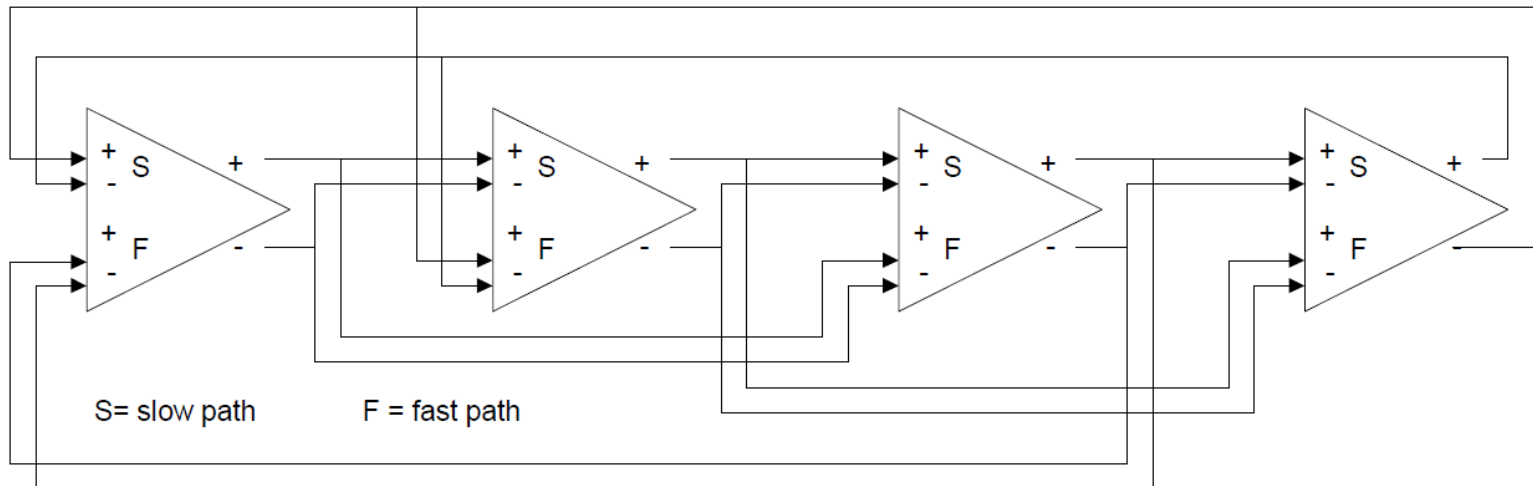(c) Delay variation by positive feedback

Multipath Oscillator

- ❑ When oscillation frequency is low. Extend the frequency by 30%.
- ❑ One input of the delay inverter comes from the previous delay stage
- ❑ Extra input comes early from the 2nd previous delay stage
- ❑ Must be careful about the false mode.
 - ❑ Check with various initial conditions




Design Tips on Ring Oscillator



- ❑ RO phase noise is too large for high precision PLL applications - the main source of PLL output jitter
- ❑ Differential structure for less supply sensitivity
- ❑ Latch added at the output for faster rise/fall times
- ❑ Too many stages can cause harmonic lock
- ❑ Symmetric rise/fall times for less phase noise against flicker noise
- ❑ Multipath RO for higher frequency
- ❑ PVT variation can cause 1:3 oscillating frequency
- ❑ Possible use of LD regulator for less variation and less jitter
- ❑ Use of supply as the control voltage
 - ❑ Level translation is required
 - ❑ Less swing might increase jitter

Phase Detector



□ Definition

 


□ XOR gate as phase detector

  


Phase Frequency Detector

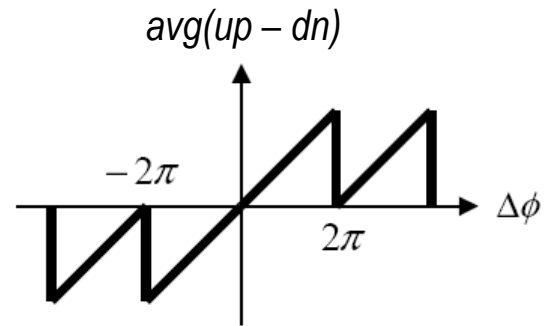 

 Different frequency (Frequency detection)





Same frequency (Phase detection)

 


PFD Non-ideality

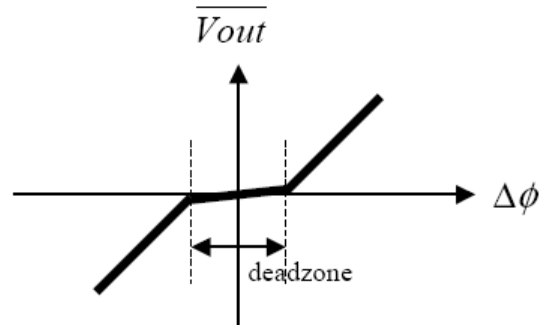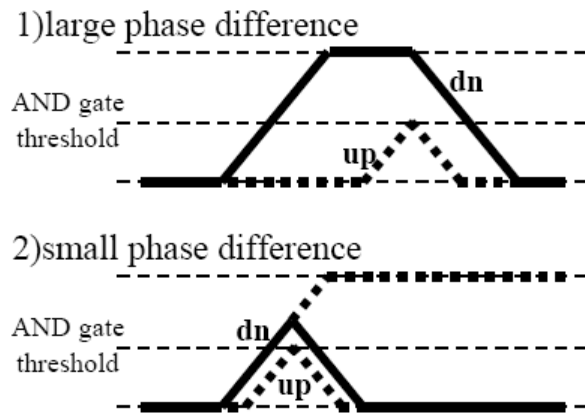- ❑ Dead zone – Occurs when PFD doesn't respond to small phase errors




DN pulse is too narrow - ignored by charge pump

 - ❑ Phase offset – Due to circuit or device mismatch



Design Tips on PFD

 
- ❑ Intentionally introduce delay by adding delay on reset path
 - ❑ Identical wide pulses on up and dn in the locked state must be cancelled in the charge pump




- ❑ Reduce delay offset in up and dn path to the charge pump
 - ❑ Reference spur appears at PLL output

Reference Spur

- In the frequency multiplier

 


Clock power spectrum

 





Charge Pump

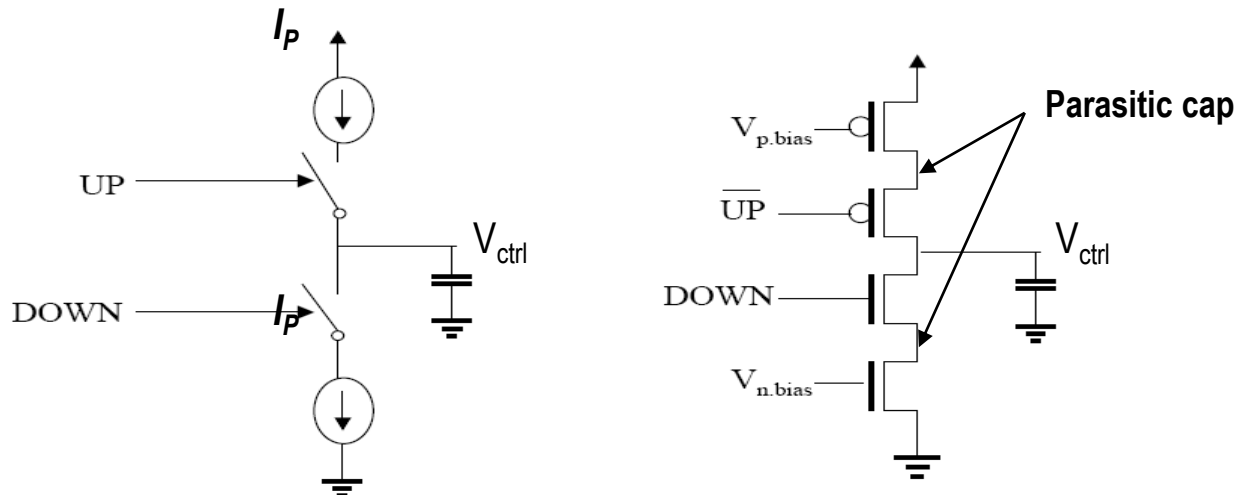- ❑ Converts PFD phase error(digital) to charge(analog)
- ❑ Issues
 - ✓ Equal up/down current over entire V_{ctrl} range
 - ✓ Minimum coupling between switching signals & V_{ctrl}
 - ✓ PVT insensitive pumping current
 - ✓ Charge sharing between loop filter cap & CP internal nodes
 - ✓ Output resistance of the transistors




Design tips on Charge Pump

 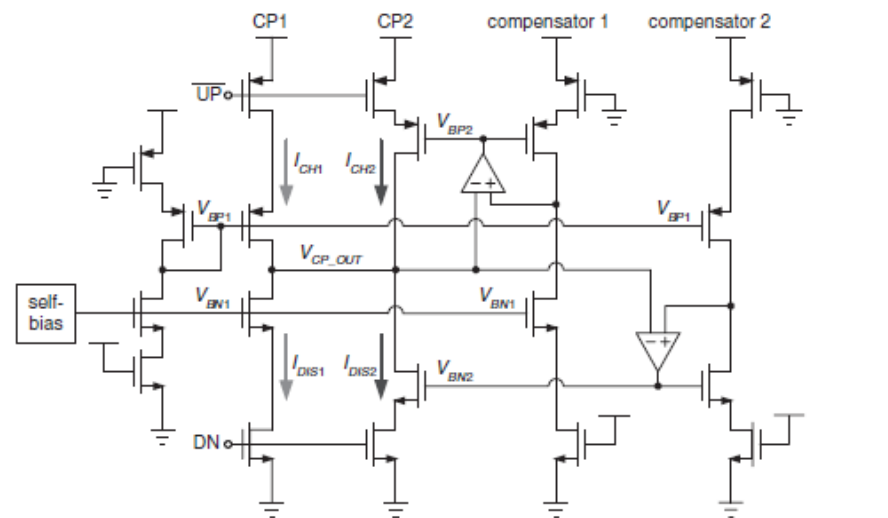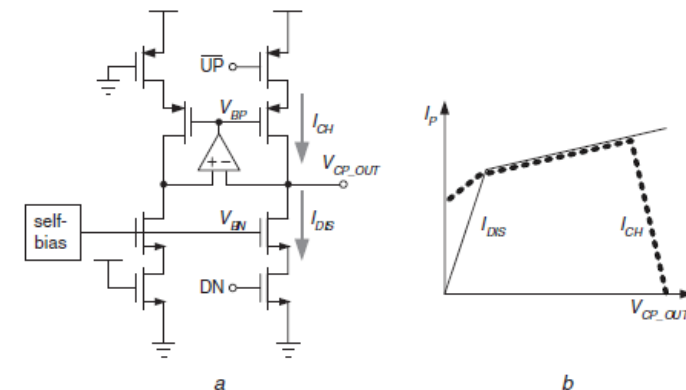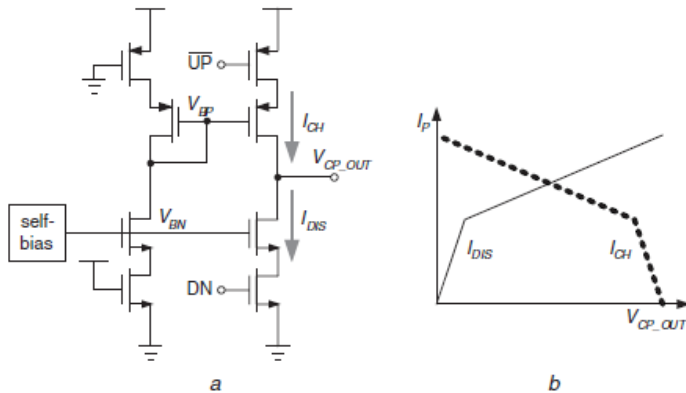- ❑ A differential charge pump is more accurate
- ❑ Equalize up/down current over the entire voltage range




Loop Filter

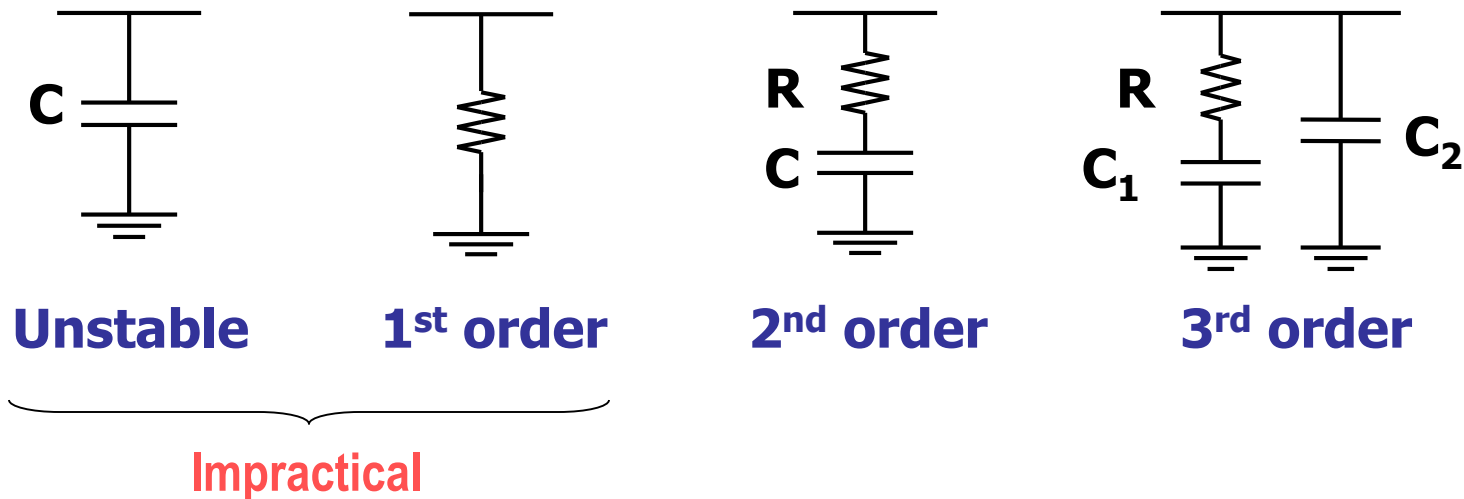- ❑ Low pass filter composed in passive RC network
- ❑ Type
 - ✓ Capacitor only – Unstable
 - ✓ Resistor only – Stable, but lock range is very narrow
 - ✓ 2nd order – Integral path (Set average VCO frequency) + proportional path (Instantaneous phase correction)
 - ✓ 3rd order – 2nd order LF + additional cap to smooth large IR ripple on Vctrl



Design tips on Loop Filter

 
- ❑ Main source of reference spur in the frequency multiplier
- ❑ Beware the leakage current of the capacitor made with thin oxide of the MOS - Causes spur



Frequency Divider

□ Type

- ✓ Cascade of div-2 – Divide by powers of 2 only
- ✓ Integer-N divider – Counter-based FSM
- ✓ Fractional-N divider – Alternates div-N & div-N+1 operation to generate fractional frequency using sigma-delta modulator
- ✓ Sigma-delta modulator
 - ✓ Keeps the average by dithering
 - ✓ Noise shaping operation moves noise to higher frequency (easily removed)
 - ✓ Prevents spur (only fractional spur present)
 - ✓ Third-order SDM can fully remove fractional spur as well

 

Design tips on Frequency Divider



- ❑ Divider operating frequency range > entire VCO oscillation frequency range under PVT variation (**NOT** functional operating oscillation frequency)
 - ❑ Use dual-modulus prescaler for high frequency division
- ❑ Minimum delay – Logic delay degrades PLL loop stability
- ❑ Try to reduce jitter with supply variation

PLL Dynamics

- PLL s-domain model
- PLL dynamics analysis using Bode plot
- Jitter in PLL
- PLL design procedure

PLL s-domain model

  - ❑ Assumption – PLL operation frequency is much higher than PLL loop responding speed
 - ✓ Loop bandwidth $\gg f_0$ by the factor of > 10
 - ✓ Can ignore sampling nature of PLL, and consequently, can be modeled in s-domain, not in z-domain
- ❑ PLL can be viewed as a linear system with phase-input & phase-output



$$H(s) = \frac{\Phi_{out}}{\Phi_{in}}$$

VCO Model


❑ Beware the unit –rad/s/V

✓ Multiply by 2π when unit is [Hz/V]



$$\omega_{\text{out}} = \omega_0 + K_{VCO} \cdot v_{\text{cont}}(t)$$


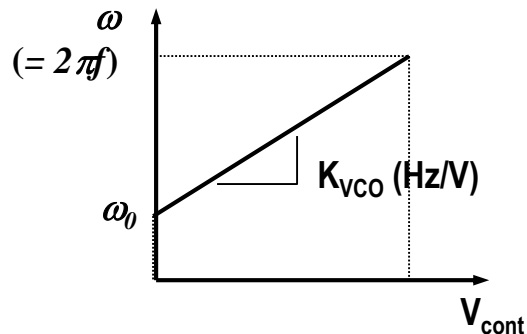
$$y(t) = A_0 \cos\left(\omega_0 t + K_{VCO} \int v_{\text{cont}}(t) dt\right)$$



$$\text{Excess phase : } \phi_{\text{out}}(t) = K_{VCO} \int v_{\text{cont}}(t) dt$$


$$\text{Transfer function : } \frac{\phi_{\text{out}}}{V_{\text{cont}}}(s) = \frac{K_{VCO}}{s}$$

PFD and Charge Pump Model

 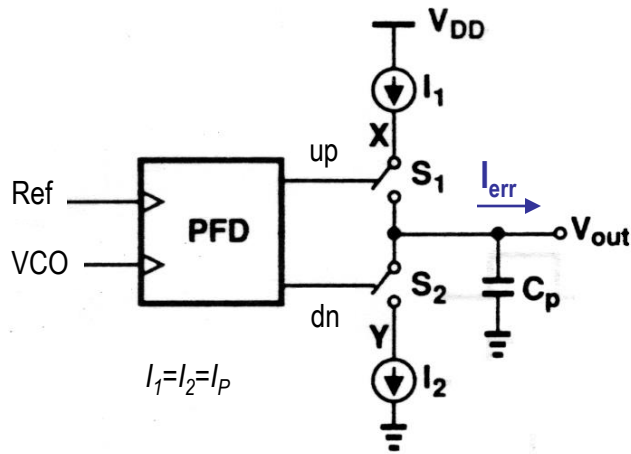


Average error current over a reference cycle: I_{err}

 
$$I_{err} = \frac{\Phi_{err}}{2\pi} \times I_P$$




Loop Filter Model

 

2nd order

 

3rd order

 


2nd order $Z_{LF}(s) = \left(R + \frac{1}{sC_1} \right) = \frac{s/\omega_z + 1}{sC_1}$

3rd order $Z_{LF}(s) = \left(R + \frac{1}{sC_1} \right) \parallel \frac{1}{sC_2} = \frac{RC_1s + 1}{RC_1C_2s^2 + (C_1 + C_2)s} = \frac{1}{(C_1 + C_2)s} \frac{s/\omega_z + 1}{s/\omega_p + 1}$


$\left(\omega_z = \frac{1}{RC_1}, \quad \omega_p = \frac{C_1 + C_2}{RC_1C_2} \right)$ Usually $C_1 > 10C_2$

Loop Filter Model

 
- ❑ Second order loop filter causes ripple on the Vcont




2nd order

 

3rd order

 



Bode Plot Premier – 2nd Order PLL

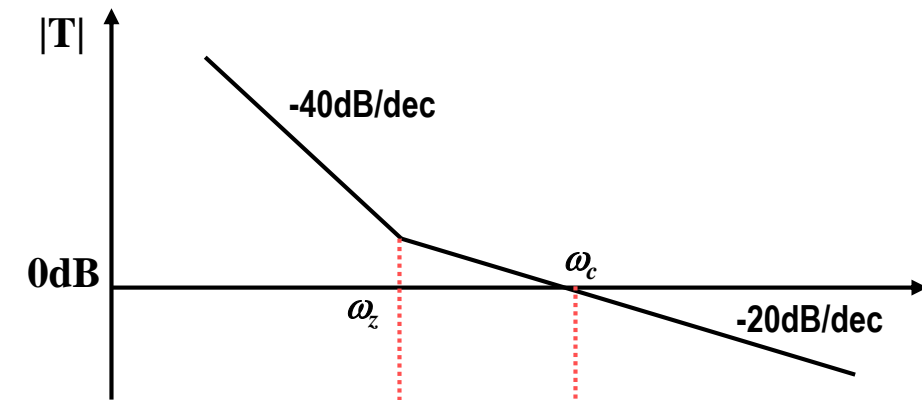


$$T(s) = K \frac{s / \omega_z + 1}{s^2}, \quad K = \frac{K_{VCO} I_p}{2\pi C_1}$$

$$|T(j\omega_c)| = 1 \Rightarrow$$
  
$$\omega_c = \frac{I_p K_{VCO} R}{2\pi} \text{ if } \omega_z \ll \omega_c$$



Bode Plot Premier – 3rd Order PLL

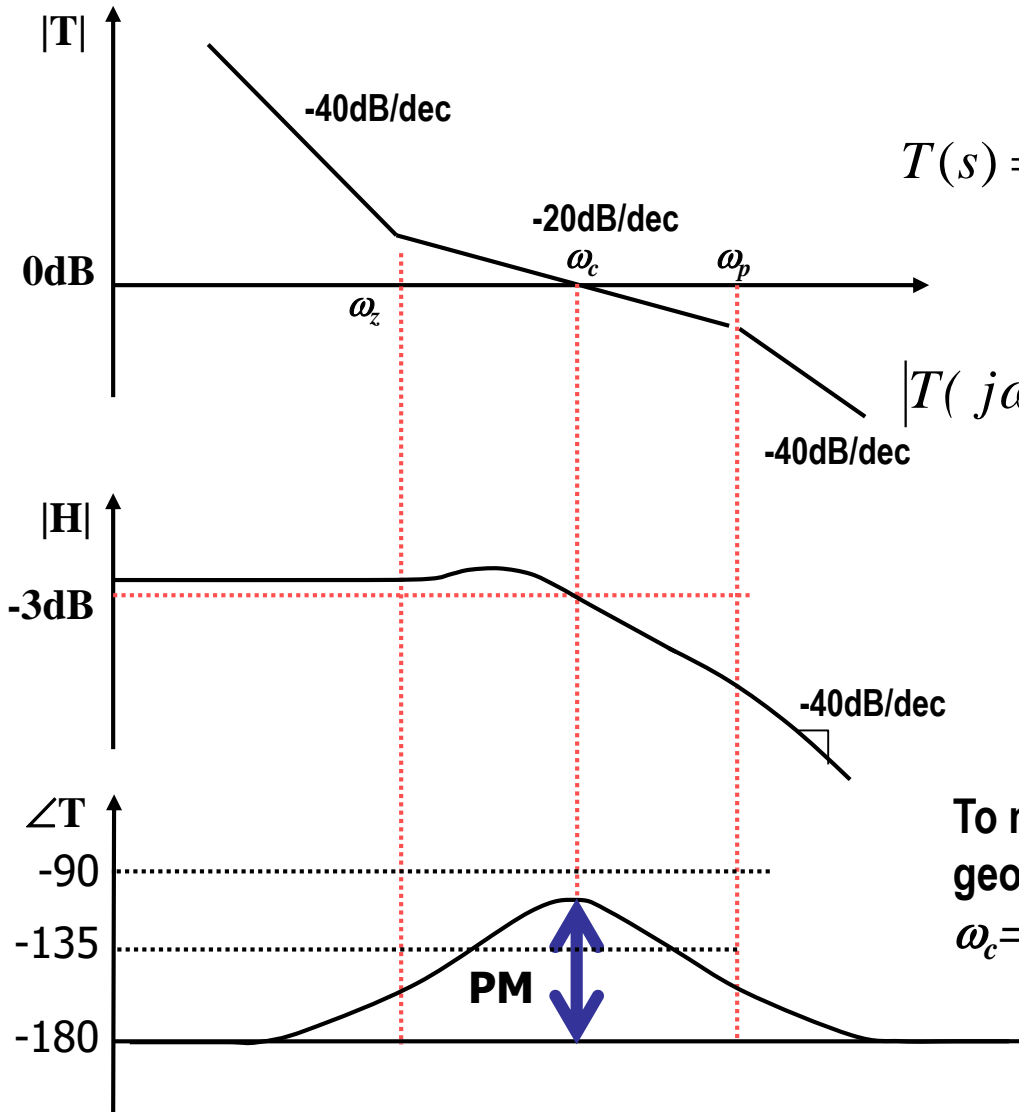


$$T(s) = K \frac{1}{s^2} \frac{s/\omega_z + 1}{s/\omega_p + 1}, \quad K = \frac{K_{VCO} I_p}{2\pi(C_1 + C_2)}$$

$$|T(j\omega_c)| = 1 \Rightarrow \omega_c = \frac{I_p K_{VCO} R}{2\pi(1 + C_2/C_1)}$$

To maximize PM, ω_c must be located at geometric mean of ω_z and ω_p , i.e.,
 $\omega_c = (\omega_z \omega_p)^{1/2}$


Tuning Design Parameters

□ Tuning of R

 


Tuning Design Parameters

□ Tuning of C

 


Tuning Design Parameters

□ Tuning of I_p

 

PLL Linear Model

- PLL linear model in s-domain

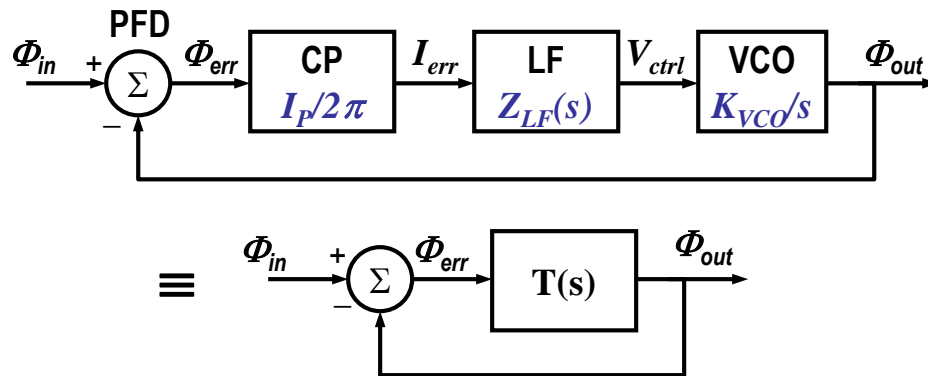

- Open loop transfer function $T(s) = \Phi_{out} / \Phi_{err}$

$$T(s) = \frac{I_P}{2\pi} \cdot Z_{LF}(s) \cdot \frac{K_{VCO}}{s}$$

- Closed loop transfer function $H(s) = \Phi_{out} / \Phi_{in}$

$$H(s) = \frac{T(s)}{1 + T(s)}$$

PLL Transfer Function of 2nd-order PLL

- Closed loop transfer function H(s)

$$H(s) = \frac{s \frac{I_p K_{VCO} R}{2\pi} + \frac{I_p K_{VCO}}{2\pi C}}{s^2 + s \frac{I_p K_{VCO} R}{2\pi} + \frac{I_p K_{VCO}}{2\pi C}} = \frac{2\zeta\omega_n s + \omega_n^2}{s^2 + 2\zeta\omega_n s + \omega_n^2}$$

$$\omega_n = \sqrt{\frac{I_p K_{VCO}}{2\pi C}} \quad \zeta = \frac{\sqrt{I_p K_{VCO} C R}}{2\sqrt{2\pi}}$$


Open-loop Transfer Function

- Open-loop unit gain frequency
 \cong Closed-loop bandwidth

$$\omega_u = \omega_n \sqrt{2\zeta^2 + \sqrt{4\zeta^4 + 1}}$$

$$\cong 2.38\zeta\omega_n$$

- Phase Margin?

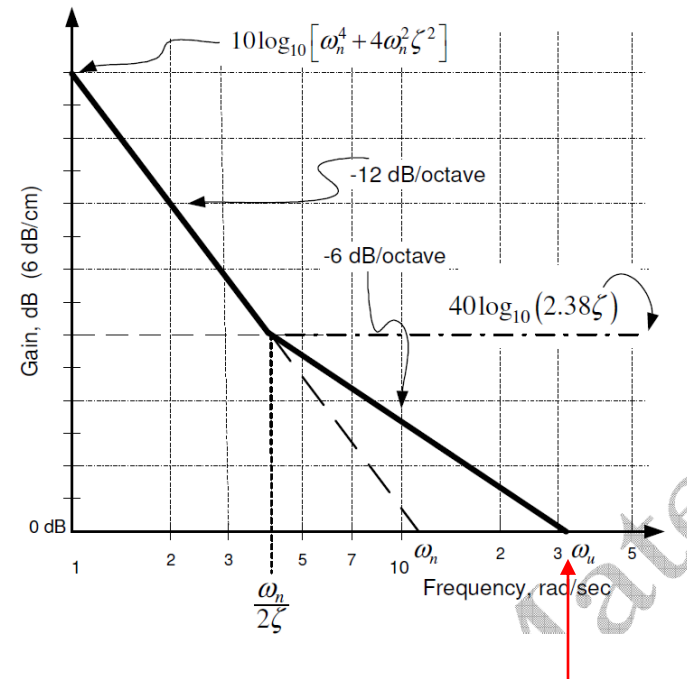

[Crawford - Advanced Phase-Lock Techniques]



PLL Jitter

- ❑ All the loop components may contribute jitter
 - ✓ PLL output jitter can be reduced through proper bandwidth selection
- ❑ Two important cases
 - ✓ When input noise is dominant
 - ✓ When VCO noise is dominant

PLL Jitter Transfer

□ Input noise

  - ✓ $\Phi_O/\Phi_N = H(s) \rightarrow$ Low pass filter!!
- ✓ Bandwidth should be lower for noise rejection



Closed-Loop Transfer Function

$$H(s) = \frac{2\zeta\omega_n s + \omega_n^2}{s^2 + 2\zeta\omega_n s + \omega_n^2}$$


$$\omega_n = \sqrt{\frac{I_p K_{VCO}}{2\pi C}} \quad \zeta = \frac{\sqrt{I_p K_{VCO} CR}}{2\sqrt{2\pi}}$$

$$F_{Pk} = \frac{1}{2\pi} \frac{\omega_n}{2\zeta} \sqrt{\sqrt{1+8\zeta^2} - 1} \text{ Hz}$$

$$F_{0dB} = \frac{1}{2\pi} \sqrt{2}\omega_n \text{ Hz}$$

$$F_{3dB} = \frac{\omega_n}{2\pi} \sqrt{1+2\zeta^2 + 2\sqrt{\zeta^4 + \zeta^2 + \frac{1}{2}}} \text{ Hz}$$
 
$$G_{Pk} = 10 \log_{10} \left(\frac{8\zeta^4}{8\zeta^4 - 4\zeta^2 - 1 + \sqrt{1+8\zeta^2}} \right) \text{ dB}$$





[Crawford - Advanced Phase-Lock Techniques]

PLL Jitter Transfer

□ VCO noise

  - ✓ $\Phi_O/\Phi_N = 1 - H(s) \rightarrow$ High pass filter!!
- ✓ Bandwidth should be higher for noise rejection
- ✓ Same ω_c



Closed-Loop Transfer Function

- VCO jitter transfer function

$$H_2(s) = 1 - H(s) = \frac{s^2}{s^2 + 2\zeta\omega_n s + \omega_n^2}$$


$$F_{H_2-3dB} = \frac{\omega_n}{2\pi} \left[\frac{2\zeta^2 - 1 + \sqrt{2 - 4\zeta^2 + 4\zeta^4}}{2} \right]^{1/2}$$

$$G_{H_2-\omega_n} = -10 \log_{10}(4\zeta^2)$$

- If $\zeta < \frac{\sqrt{2}}{2}$, peaking occurs

$$F_{H_2-max} = \frac{1}{2\pi} \frac{\omega_n}{\sqrt{1 - 2\zeta^2}}$$

 
$$G_{H_2-max} = -10 \log_{10}(4\zeta^2 - 4\zeta^4)$$



[Crawford - Advanced Phase-Lock Techniques]

PLL Linear Model with FB Divider

- PLL linear model in s-domain

 

- Open loop transfer function $T(s) = \Phi_{out} / \Phi_{err}$

$$T(s) = \frac{I_P}{2\pi} \cdot Z_{LF}(s) \cdot \frac{K_{VCO}}{s} \cdot \frac{1}{M}$$

- Closed loop transfer function $H(s) = \Phi_{out} / \Phi_{in}$

$$H(s) = M \cdot \frac{T(s)}{1 + T(s)}$$

**All the stability analysis is on the modified T(s)
Loop gain is reduced by M
Phase is multiplied by M – Frequency as well**

PLL Design Procedure

- ❑ Determine PLL spec
 - ✓ Operation range, bandwidth, power budget, jitter peaking ...
- ❑ Design VCO
 - ✓ Should have the proper operation range over PVT variation
 - ✓ Determine K_{VCO}
- ❑ Design loop filter
 - ✓ Determine proper pole-zero location
 - ✓ Determine RC values – Should be practical ($R=100 \sim 10k\Omega$, $C_{max} = 200pF$)
- ❑ Determine charge pump current
 - ✓ PM should be considered – More than 60°
 - ✓ Several $\mu A \sim 1mA$

Topics in IC Design

2.2 Fractional-N FS

Deog-Kyoon Jeong

dkjeong@snu.ac.kr

School of Electrical and Computer Engineering

Seoul National University


2020 Fall

Issues

- Background
- Architecture
- Spurious Tone
- SDM and Dithering
- Quantization Noise Analysis

Background

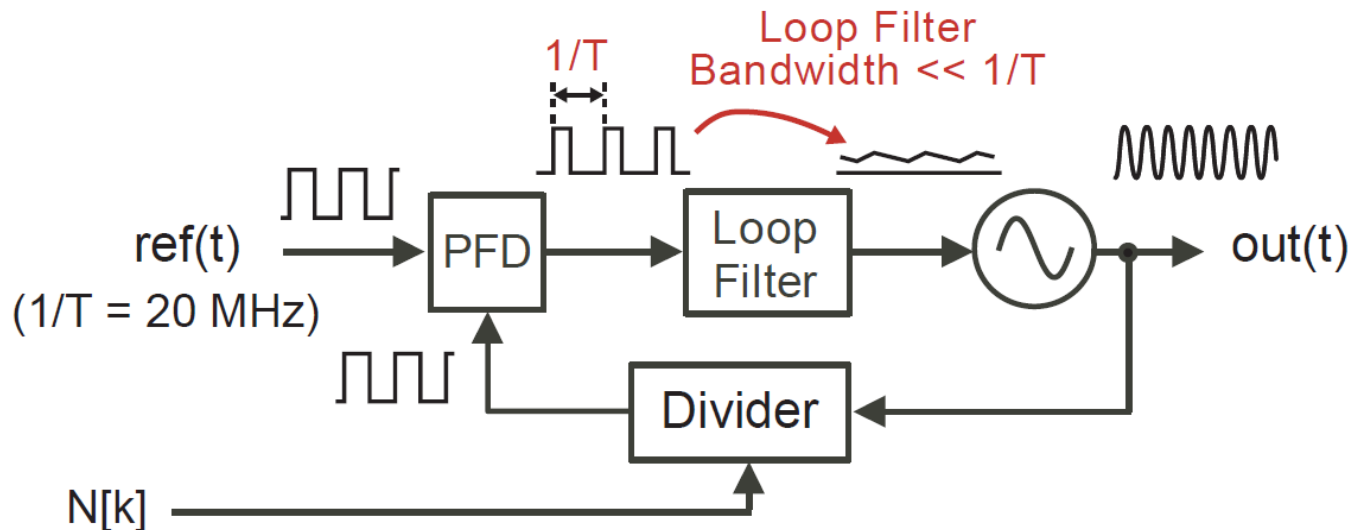
- ❑ Integer PLL gives integer * f_{REF}
- ❑ Frequency resolution = f_{REF} , too coarse.
- ❑ What if we want to have 1 MHz resolution when $f_{\text{REF}}=20$ MHz?
- ❑ Fractional divide factor is required.



[MIT Courseware: Perrott]



Fractional-N PLL Architecture

- Alternating divide factors are used

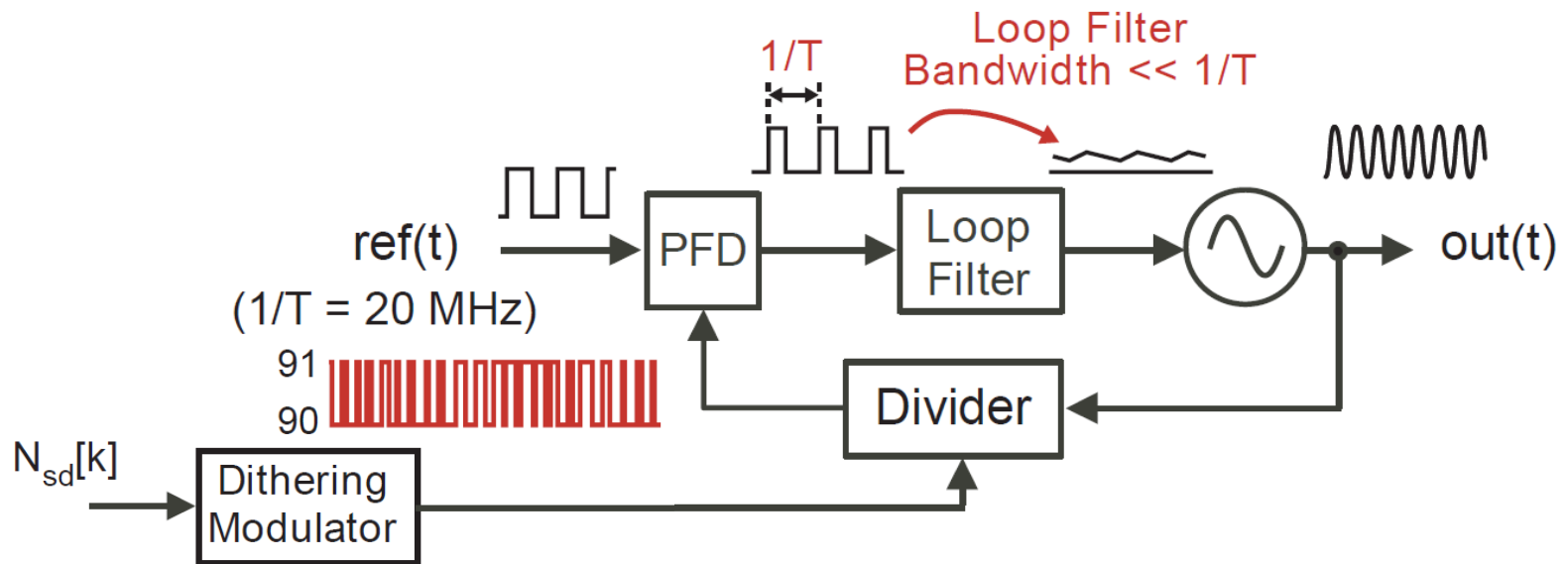


Fractional-N PLL Architecture

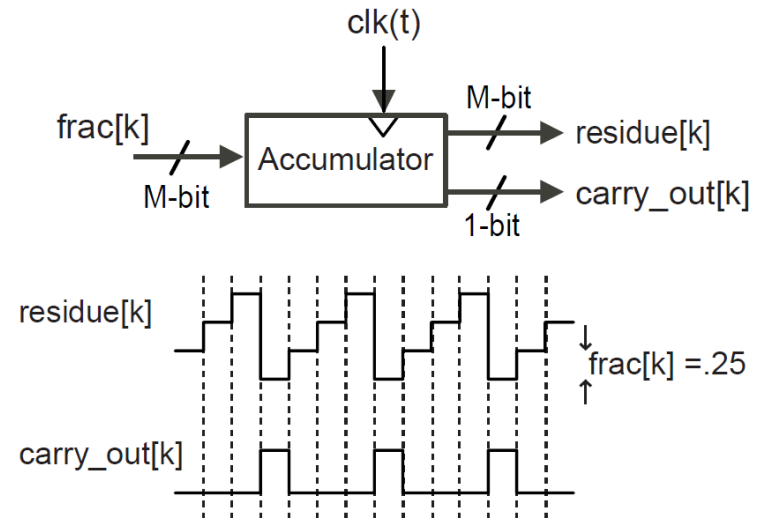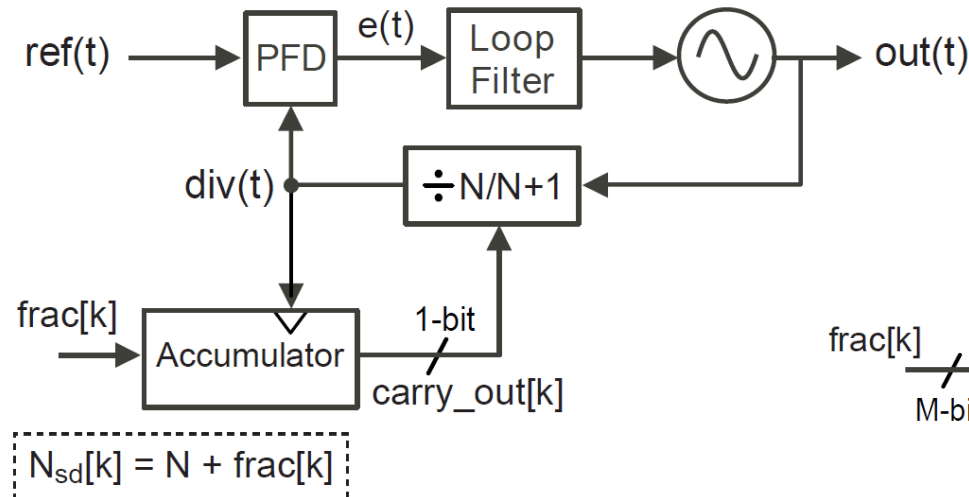- ❑ Accumulator is used for generating alternating divide factors
- ❑ Accumulator adds a fraction every cycle and carry overflow is the output




Timing Diagram

 - For fractional divide of 4.25, divide value = 4, 3 times and divide value = 5, 1 time.




Timing Diagram (corrected)

 - ❑ In fact, in steady state, average value of $e(t)=0$.
- ❑ All signals except $ref(t)$ must be shifted.



Spurious Tone

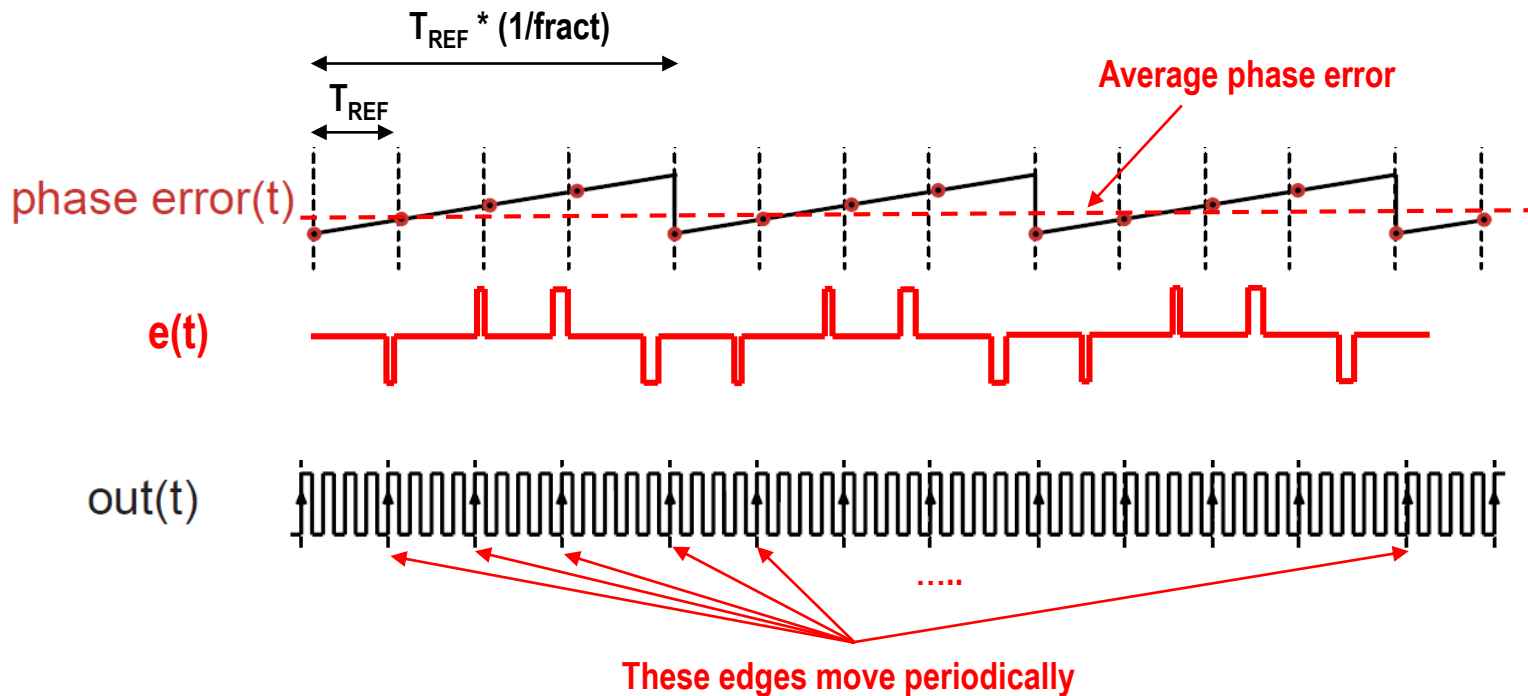- ❑ Periodic phase error appears if averaging is not perfect.
- ❑ The spurious tone frequency is about f_{REF} and $f_{REF} * \text{fract}$




Reducing Spurious Tone


- ❑ Instead of periodically alternating at 3:1 ratio, dither the ratio at random, with long-term average of 3:1.
- ❑ Fractional spur is spread ($f_{\text{REF}} * \text{fract}$)
- ❑ How? Use the **Sigma-Delta Modulator**
- ❑ **Accumulator is the 1st order SDM**
 - ❑ Output (carry) is periodically generated, no dithering (1 0 0 0 1 0 0 0 1 0 0 0 1 0 0 0 1 ...)
- ❑ **What is the 2nd order SDM?**
 - ❑ Output is dithered. (1 0 0 1 0 0 0 0 1 0 0 0 1 0 0 0 0 1 ...)

1st Order SDM


- Same as accumulator

 

Digital Implementation

 


1st order DSM Model

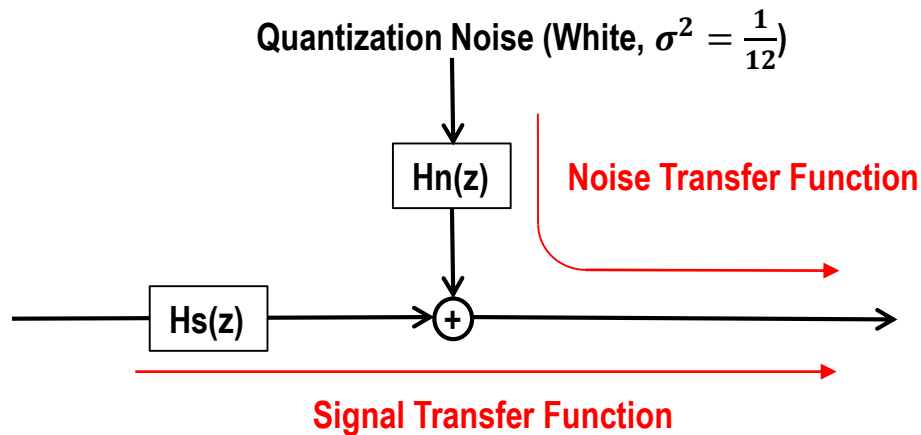

2nd Order SDM


- Noise is shaped
- Dithering added

 

2nd order DSM Model


Noise Shaping

 - Signal Transfer function $H_s(z) = 1$
- Noise Transfer Function $H_n(z) = (1 - z^{-1})^m$, $m = \text{order of DSM}$



2nd Order SDM

- Noise is shaped
- Dithering added


 


2nd order DSM Model



DSM Outputs

- For sinusoidal input $x[k] = 0.5 + 0.25 \sin\left(\frac{2\pi}{100}k\right)$



1st order

  

2nd order

  


3rd order

  

Quantization Noise in F-N FS

- Phase Noise injected at input of PFD

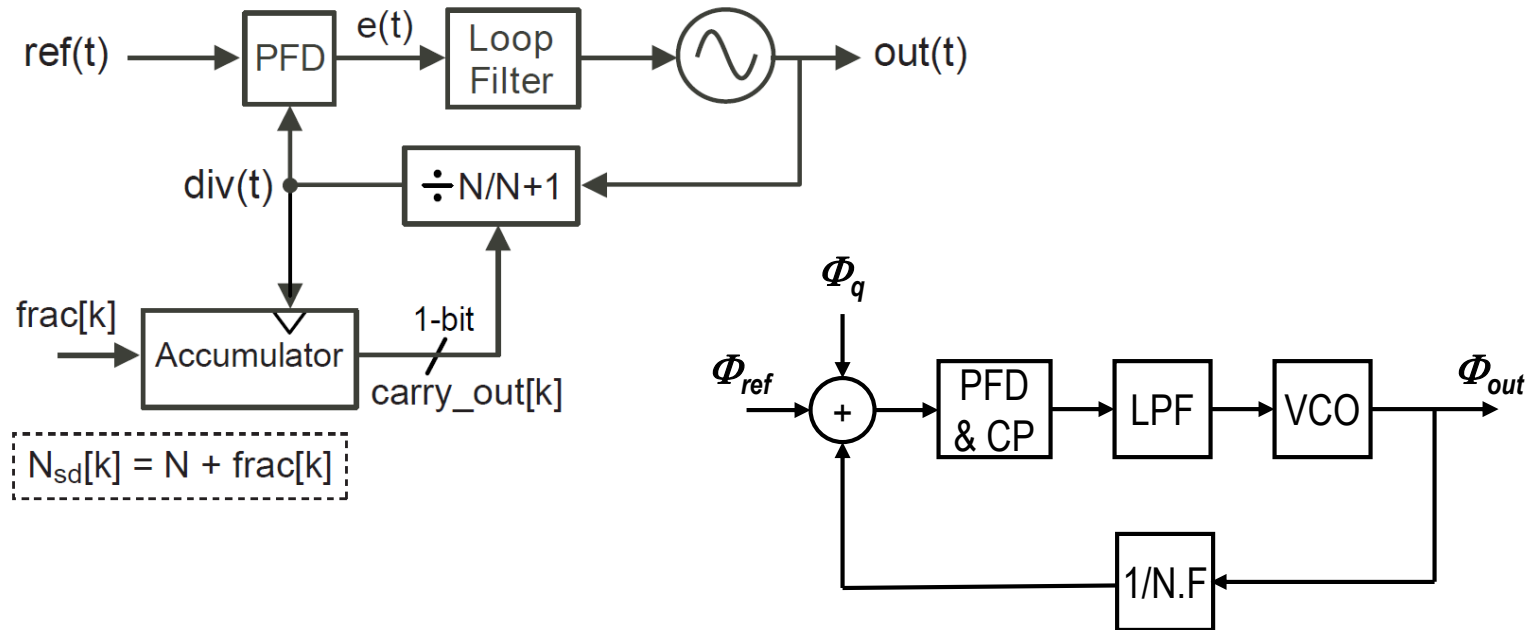


$$S_q(f) = \frac{1}{12} \cdot \frac{(2\pi)^2}{(N.F)^2 \cdot f R_{EF}} \cdot \left[2 \sin \left(\frac{\pi f}{f_{REF}} \right) \right]^{2(m-1)}$$

$$S_{qOUT}(f) = S_q(f) \cdot |H(j2\pi f)|^2$$

Phase Noise in Fractional-N FS

- Quantization noise is shaped.

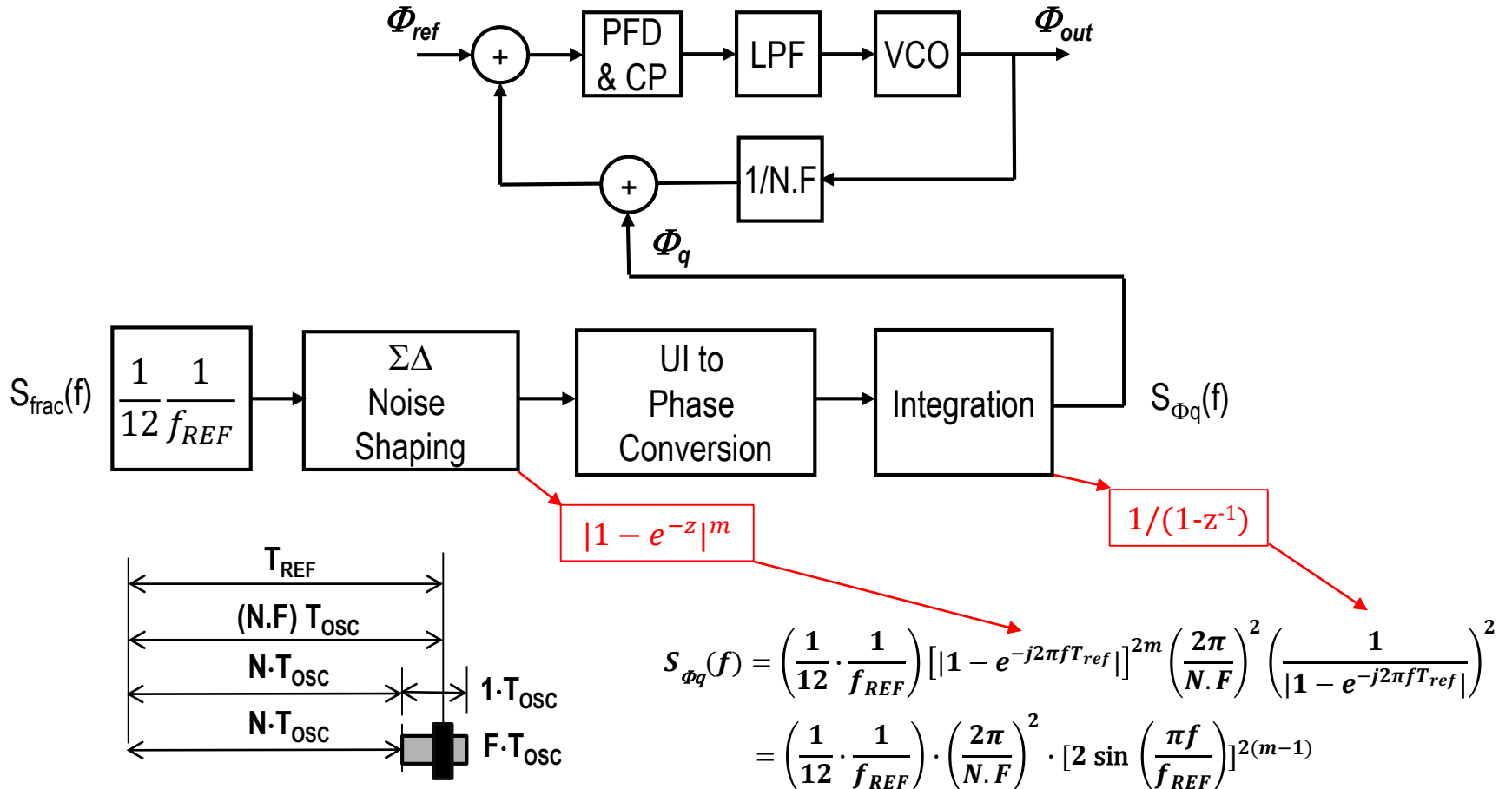

Topics in IC Design

2.3. Spread-Spectrum Frequency Synthesizer

Deog-Kyoon Jeong
dkjeong@snu.ac.kr

School of Electrical and Computer Engineering
Seoul National University



2020 Fall

Outline

- EMI issues
- Frequency Spectrum
- Architectures

Background

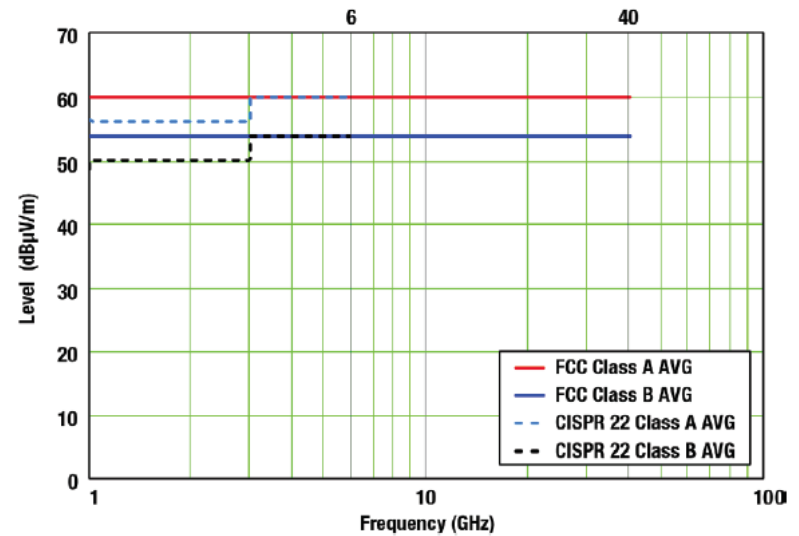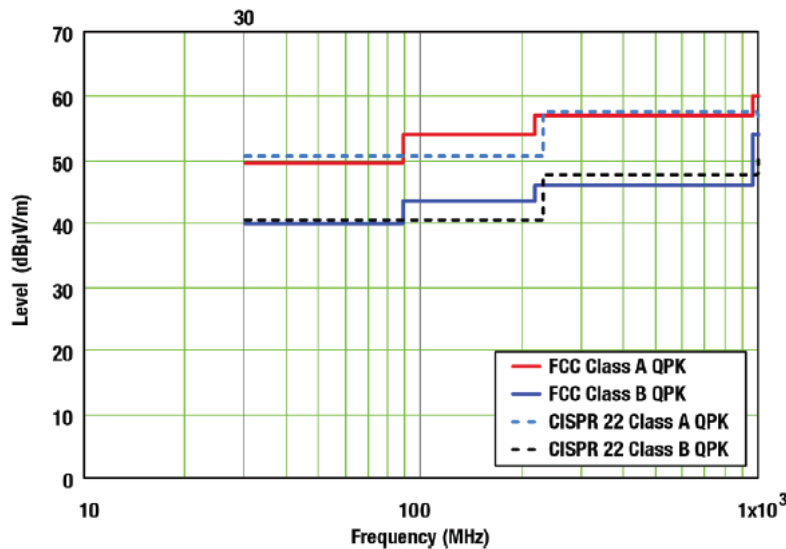
- ❑ Electromagnetic Interference
- ❑ Many standards to comply
 - ❑ FCC Class A, Class B
 - ❑ CISPR




[TI: Overview of Radiated EMI]

Background


Shield Room Test

 

Front view:

 




Side view:

 

[TI: Overview of Radiated EMI]


EMI Reduction Techniques

   - Shielding
- Edge rate reduction
- Low voltage differential signaling
- Spread-spectrum clocking
 - FM modulation of clock with triangular/Hersey-Kiss waveform
 - 30-33kHz (inaudible to human ear)
 - Down spread not to shorten clock period




Spectral Peak Reduction

- Spectral peak is reduced by 5.9dB

 

unmodulated

 


+/- 1 % modulation


[Li: ISSCC 1999: Dual-Loop SSCG]

Spectral Peak Reduction

- Spectral peak is reduced by 11.2dB

 

unmodulated

 


+/- 5 % modulation

[Li: ISSCC 1999: Dual-Loop SSCG]


Spectral Peak Reduction

 - ❑ Peak reduction factor
- ❑ $10 \log [(\text{Frequency Spread}) / (\text{Resolution Bandwidth, 100kHz})]$






Spectral Peak Reduction

 - Peak EMI reduction [dB] =
 $10 \log [(\text{Frequency Spread}) / (\text{Resolution Bandwidth, 100kHz})]$



SSCG Architectures


- Dual Loop**

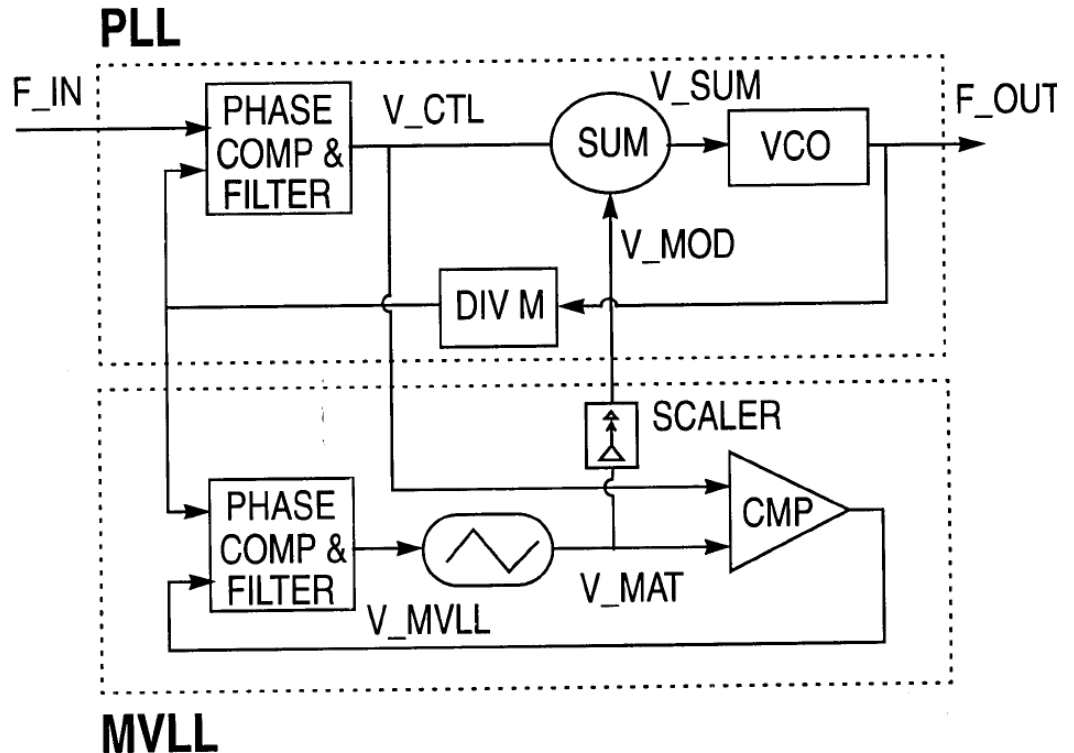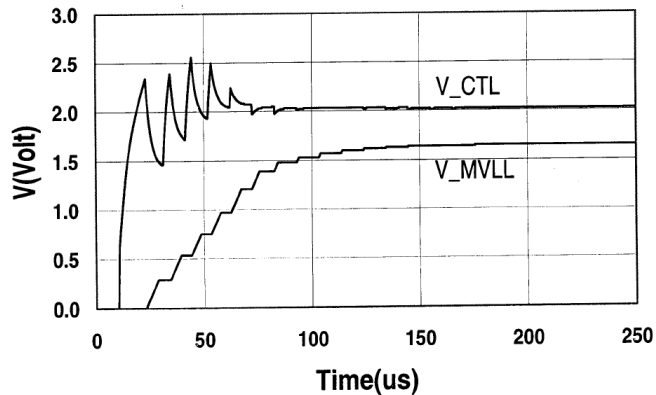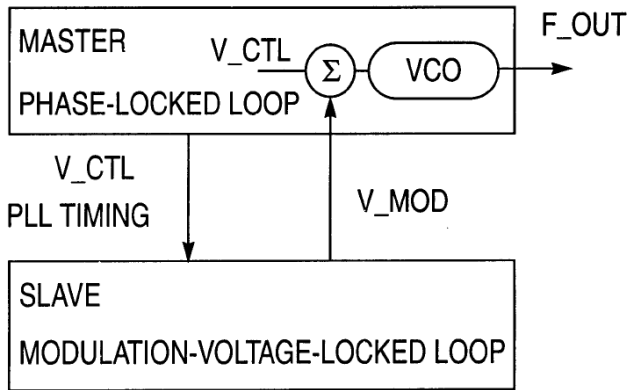

[Li: ISSCC 1999: Dual-Loop SSCG]


SSCG Architectures

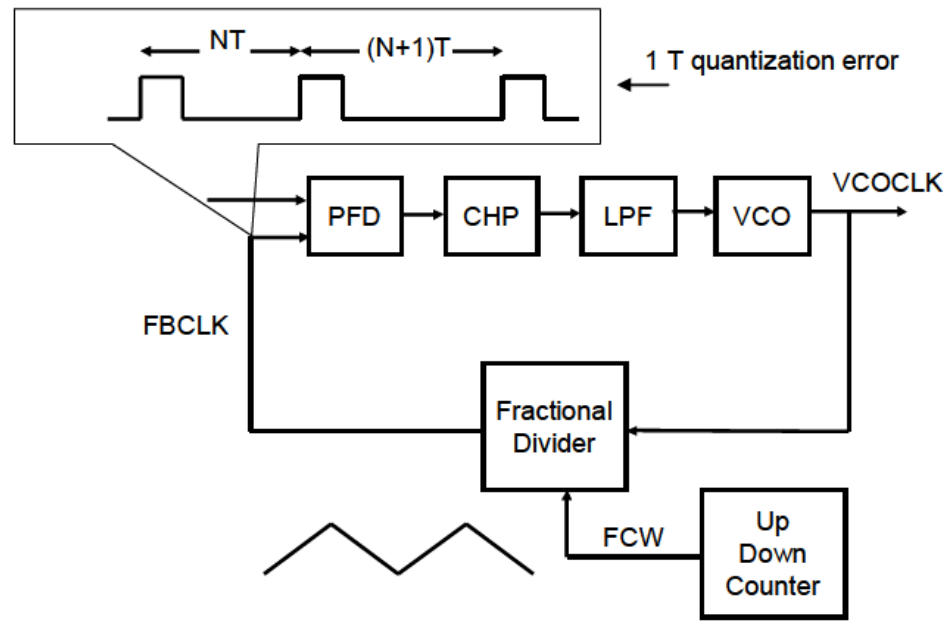- ❑ Integer feedback factor modulation
- ❑ Conflict:
 - ❑ Low bandwidth to filter quantization noise
 - ❑ Harmonic tones of the triangular will be filtered



SSCG Architectures

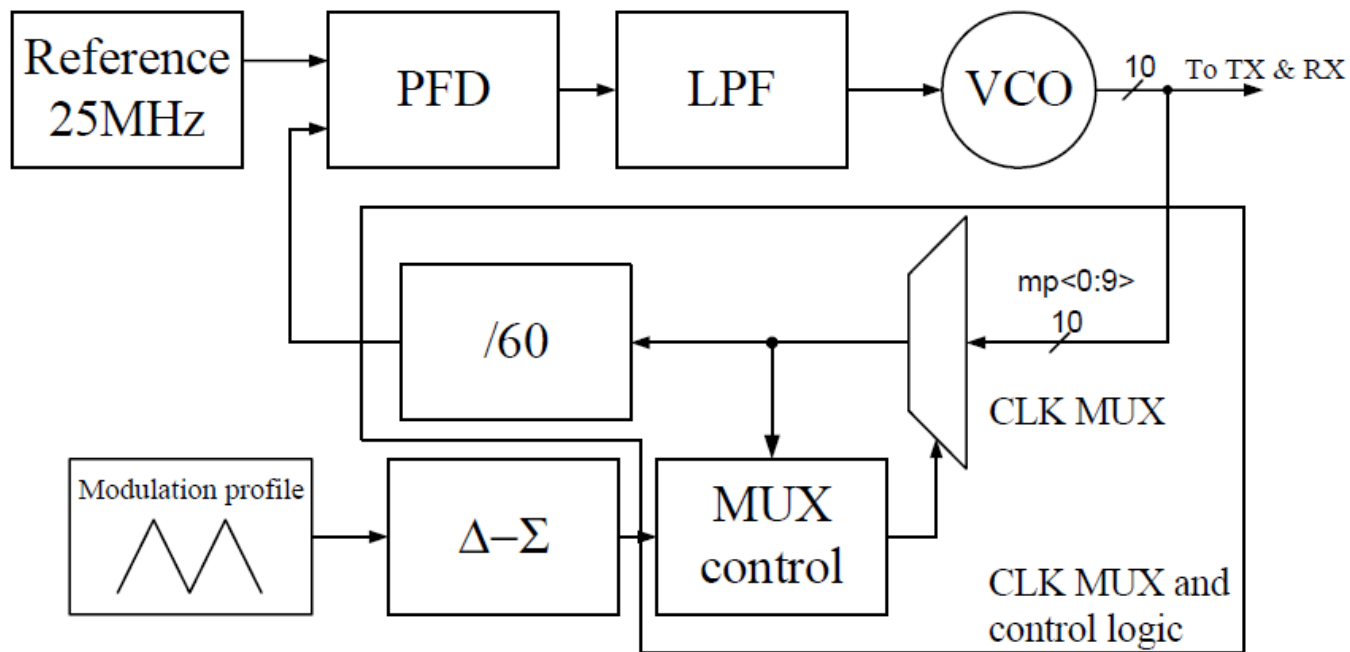
- ❑ Feedback factor modulation with fractional phase



[HR Lee: A low jitter 5000 ppm]

SSCG Architectures

- Two-point modulation

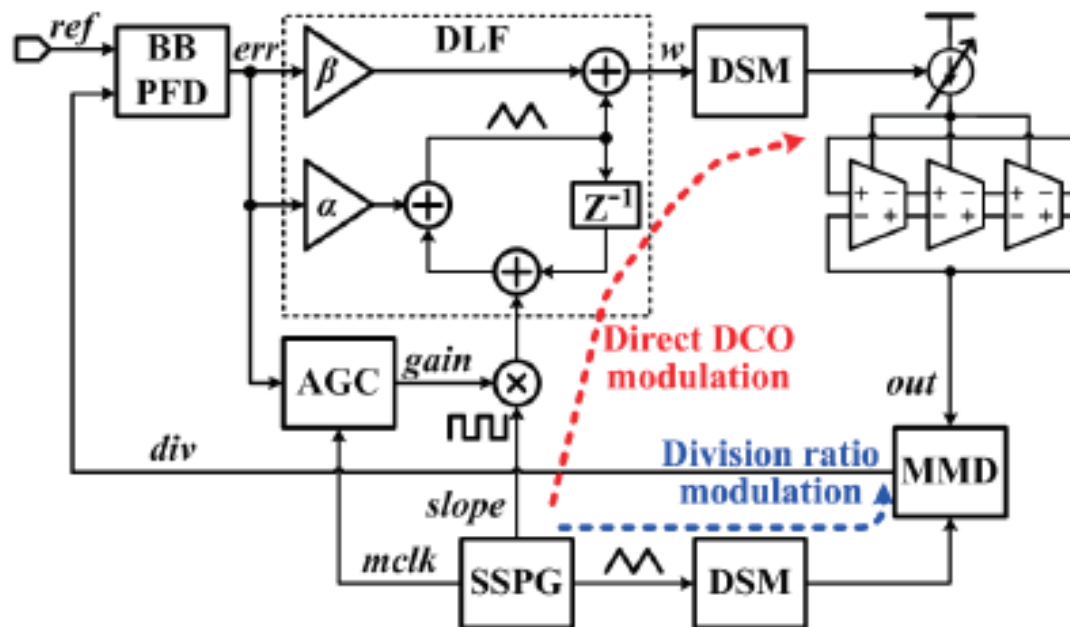

[2015_SOVC_SCJANG - An All-Digital Bang-Bang PLL Using Two-Point Modulation and Background Gain Calibration for Spread Spectrum Clock Generation]

Modulation Waveform

- Triangular vs Hersey-Kiss

 


Figure 1. Linear Profile (MDA plot)

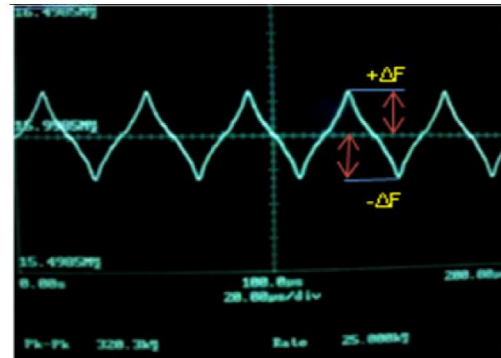


Figure 2. Hersey Kiss Profile (MDA Plot)

 


Figure 3. Linear Profile (Spectrum Plot)

 


Figure 4. Hersey Kiss Profile (Spectrum Plot)

EMI Reduction at Harmonics

- EMI Reduction is larger with harmonics

