


Topics in IC Design

7.1 Modeling of Transmission Lines

Deog-Kyoon Jeong
dkjeong@snu.ac.kr


School of Electrical and Computer Engineering
Seoul National University
2020 Spring

Serial-Link Architecture

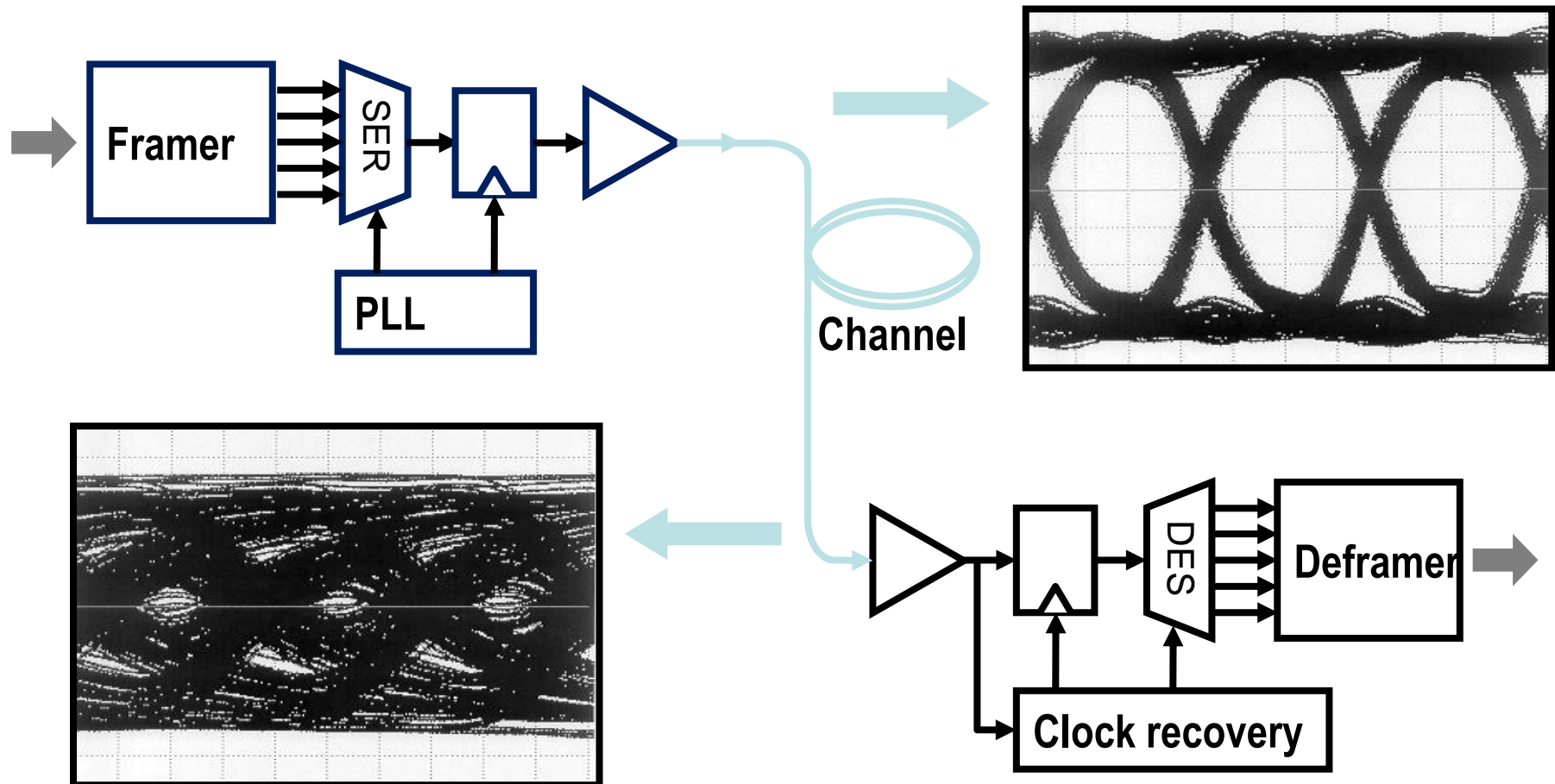

Receiver should compensate channel loss to recover transmitted signal completely!!

Distributed Parameter Channel Model

 

$$V_+(t, x) = V_+(0, 0)e^{j\omega t - \gamma x}$$

$$I_+(t, x) = I_+(0, 0)e^{j\omega t - \gamma x}$$

$$V_+(t, x) = I_+(t, x)Z_0$$

$$V_-(t, x) = V_-(0, L)e^{j\omega t + \gamma x}$$

$$I_-(t, x) = I_-(0, L)e^{j\omega t + \gamma x}$$

$$V_-(t, x) = I_-(t, x)Z_0$$

$$V(t, x) = V_+(t, x) + V_-(t, x)$$


$$I(t, x) = I_+(t, x) - I_-(t, x)$$

$$\text{Complex propagation constant: } \gamma = \alpha + j\beta = \sqrt{(R + j\omega L)(G + j\omega C)}$$

$$\text{Characteristic impedance: } Z_o = \frac{R + j\omega L}{\gamma} = \sqrt{\frac{R + j\omega L}{G + j\omega C}}$$

Skin Effect

- Skin effect is the tendency of an alternating electric current(AC) to distribute itself within a conductor so that the current density near the surface of the conductor is greater than at its core.
- The skin depth is the depth where the current has fallen off to $e^{-1}(0.381)$ of its original value.
- The effective series resistance of the cable corresponding to this depth increases with square root of frequency

 

Current Distribution
Shell Model

$$\text{Skin depth: } \delta_s = \sqrt{\frac{1}{\pi f \mu \sigma}}$$

$$\text{Surface resistance (Sheet resistance): } R_s = \frac{1}{\sigma \delta_s} = \sqrt{\frac{\pi f \mu}{\sigma}}$$

$$\text{Effective series resistance: } R_{skin} = \frac{1}{2r} \sqrt{\frac{f \mu \rho}{\pi}}$$

$$\text{Skin effect frequency } f_{skin} = \frac{\rho}{\pi \cdot \mu \cdot r^2} \text{ (skin depth = radius)}$$


Dielectric Loss

- **With some insulating materials, dielectric absorption causes frequency dependent attenuation**
 - This loss can be modeled as a conductance G between the signal wire and ground.
- **Dielectric loss for each material is usually expressed in terms of a parameter, called the loss tangent.**

$$\epsilon = \epsilon' - j\epsilon''$$

$$\tan \delta_D = \frac{\epsilon''}{\epsilon'} = \frac{G_{AC}}{\omega C}$$

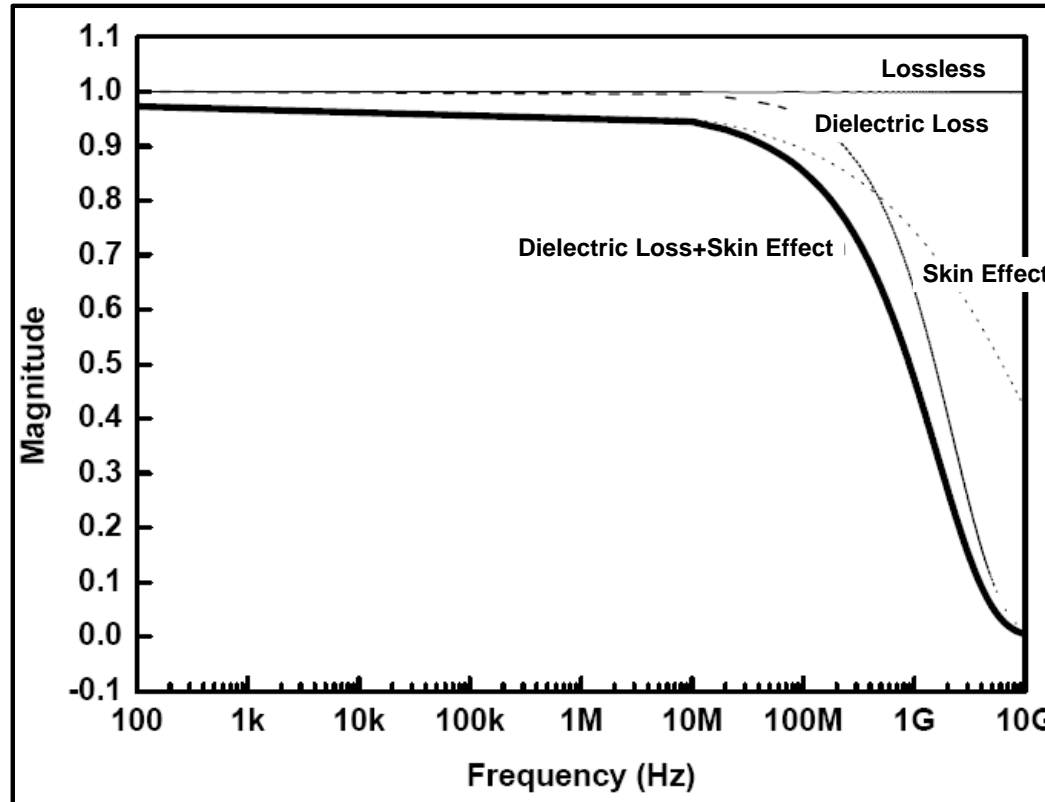Frequency Dependent Attenuation- Skin Effect + Dielectric Loss



$$R_{Skin} = \frac{1}{2r} \sqrt{\frac{f\mu\rho}{\pi}} \Rightarrow R_{skin} \propto \sqrt{f}$$

$$G_{AC} = \omega C \tan \delta_D \Rightarrow G_{AC} \propto f$$

$$\gamma = \alpha + j\beta = \sqrt{(R_{Skin} + j\omega L)(G_{AC} + j\omega C)}$$

$$\cong j\omega\sqrt{LC} + \frac{R_{Skin}}{2Z_0} + \frac{G_{AC}Z_0}{2}$$

Channel Transfer Function (1)

- When properly terminated, the transfer-function of a cable is modeled by

$$H(d, \omega) = e^{-d\gamma(\omega)} = e^{-d\alpha(\omega)} e^{-jd\beta(\omega)}$$

where propagation constant $\gamma(\omega) = \alpha(\omega) + j\beta(\omega)$

d : cable length

α, β : attenuation and phase constants

- From lossy propagation constant where $G=0$

$$\begin{aligned}\gamma(\omega) &= \sqrt{(R + j\omega L)(j\omega C)} \\ &= j\omega\sqrt{LC} \sqrt{1 + \frac{R}{j\omega L}}\end{aligned}$$

Channel Transfer Function (2)

- When you alter the path of current, you also alter the inductance.

$$Z_{AC} = Z_{real} + Z_{image}$$

- Therefore, to fully characterize skin effect, you need to consider both the changes in resistance and inductance with frequency.
- Self-inductance per length = $\mu/8\pi$.
- By Wheeler's assumption about the equality of the real and imaginary parts of conductor internal impedance.

$$Z_{AC} = R_{AC}(1+j)\sqrt{\omega} \text{ [}\Omega/\text{m]}$$

[Wheeler H. A. "Formulas for the skin-effect", Proc. IRE, Vol. 30, 412-424, 1942]

- The term $(1+j)$ signifies the real(resistive) and imaginary(inductive) parts are equal

$$R = R_{DC} + R_{AC}(1+j)\sqrt{\omega} @ R_{DC} = \frac{\rho}{A}$$

$$R_{Skin} = \frac{1}{2r} \sqrt{\frac{f\mu\rho}{\pi}} = R_{AC} \sqrt{\omega}$$

$$\therefore R_{AC} = \frac{1}{2\pi r} \sqrt{\frac{\mu\rho}{2}}$$

Channel Transfer Function (3)

- If frequency is very high

$$R \approx R_{AC}(1+j)\sqrt{\omega}$$

$$\begin{aligned}\gamma(\omega) &= j\omega\sqrt{LC}\sqrt{1+\frac{R}{j\omega L}} \\ &= j\omega\sqrt{LC}\sqrt{1+\frac{R_{AC}(1-j)}{L\sqrt{\omega}}}\end{aligned}$$

- Using approximation $(1+x)^{1/2} \approx 1+x/2$ for $x \ll 1$

$$\alpha(\omega) = \frac{R_{AC}}{2}\sqrt{\frac{\omega C}{L}} \text{ (same), } \beta(\omega) = \omega\sqrt{LC} + \frac{R_{AC}}{2}\sqrt{\frac{\omega C}{L}} \text{ (second term added)}$$

$$H_{dB}(d, f) = 20 \log_{10} |H(d, f)| = -8.68d \times R_{AC} \sqrt{\frac{\pi f C}{2L}}$$

$\therefore \text{The gain in dB} \propto -\sqrt{f}$

Coaxial Cable

- Resistance at DC

$$R = \frac{\sigma}{\pi d^2}$$

- Series resistance

$$R_{skin} = \frac{R_s}{2\pi} \left(\frac{1}{D} + \frac{1}{d} \right)$$

- External Series Inductance

$$L = \frac{\mu}{2\pi} \ln(D/d) = \frac{\mu_0 \mu_r}{2\pi} \ln(D/d)$$

- Internal Self-Inductance at DC


$$L_0 = \frac{\mu}{8\pi}$$

permittivity : $\varepsilon = \varepsilon' - j\varepsilon''$

permeability : $\mu = \mu_0 \mu_r$

Surface resistance : $R_s = 1 / \sigma \delta_s$

Coaxial Cable
Cross Section

 

Center Conductor

Dielectric

Tape

Braid

Jacket

RG58 Coaxial Cable



Coaxial Cable

- **Shunt conductance per unit length**

$$G = \frac{2\pi\omega\epsilon''}{\ln(D/d)}$$

- **Shunt capacitance per unit length**


$$C = \frac{2\pi\epsilon'}{\ln(D/d)} = \frac{2\pi\epsilon_0\epsilon_r}{\ln(D/d)}$$

permittivity : $\epsilon = \epsilon' - j\epsilon''$

permeability : $\mu = \mu_0\mu_r$

Surface resistance : $R_s = 1/\sigma\delta_s$

Coaxial Cable
Cross Section

 

Center Conductor

Dielectric

Tape


Braid

Jacket


RG58 Coaxial Cable



Channel Loss

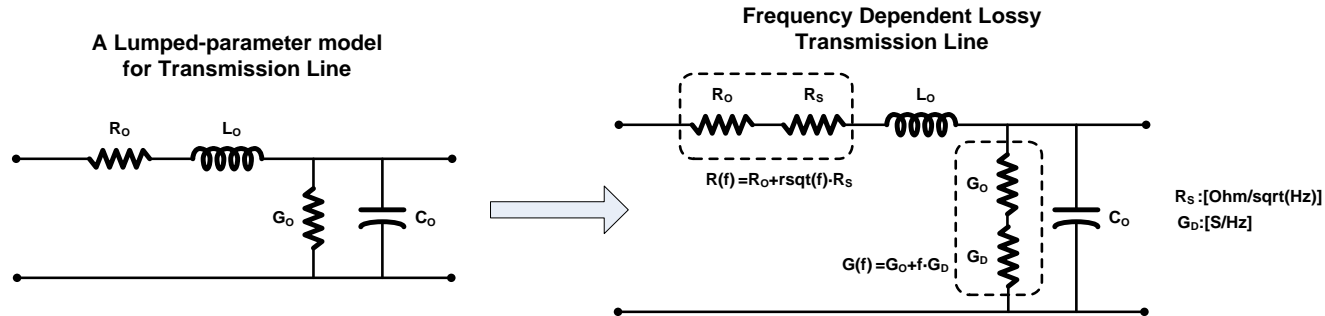

RG58 Coaxial Cable Frequency Response

 


Channel Group Delay

- **Group Delay:** A measure of the transit time of a signal through a device under test, versus frequency.


$$\text{Group Delay } \tau_g(\omega) = -\frac{d\phi}{d\omega} = -\frac{1}{360} \cdot \frac{(\text{phase}_2 - \text{phase}_1)}{(f_1 - f_2)}$$

RG58 Coaxial Cable Frequency Response

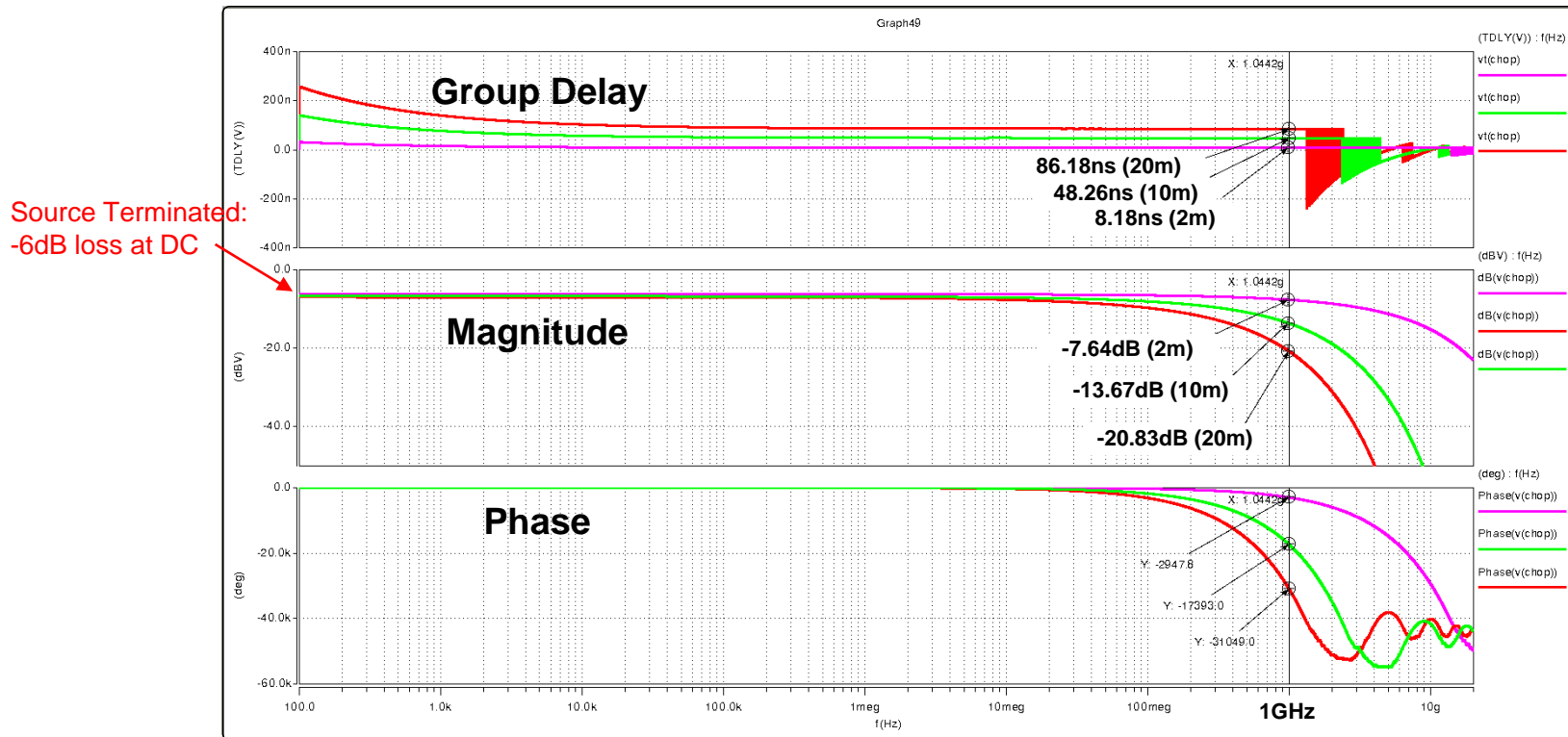


Channel Loss vs Frequency


12 inch PCB trace @ 2Gbps

 


12 inch PCB trace @ 4Gbps

 

12 inch PCB trace @ 5Gbps

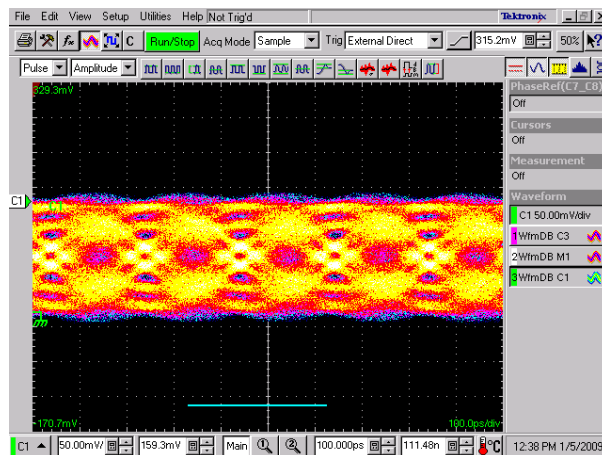


12 inch PCB trace @ 6Gbps

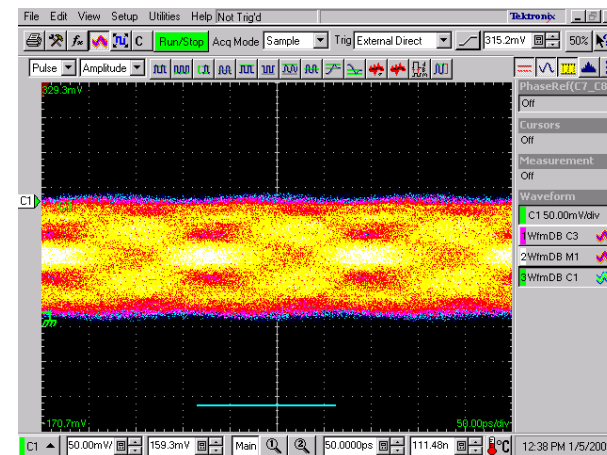


Data-Dependent Jitter: ISI

 
- Previous symbol does not settle completely



Almost no ISI,

 


ISI spanning over 1 bit,

 

ISI spanning over 2 bits

Pattern Dependent Histogram



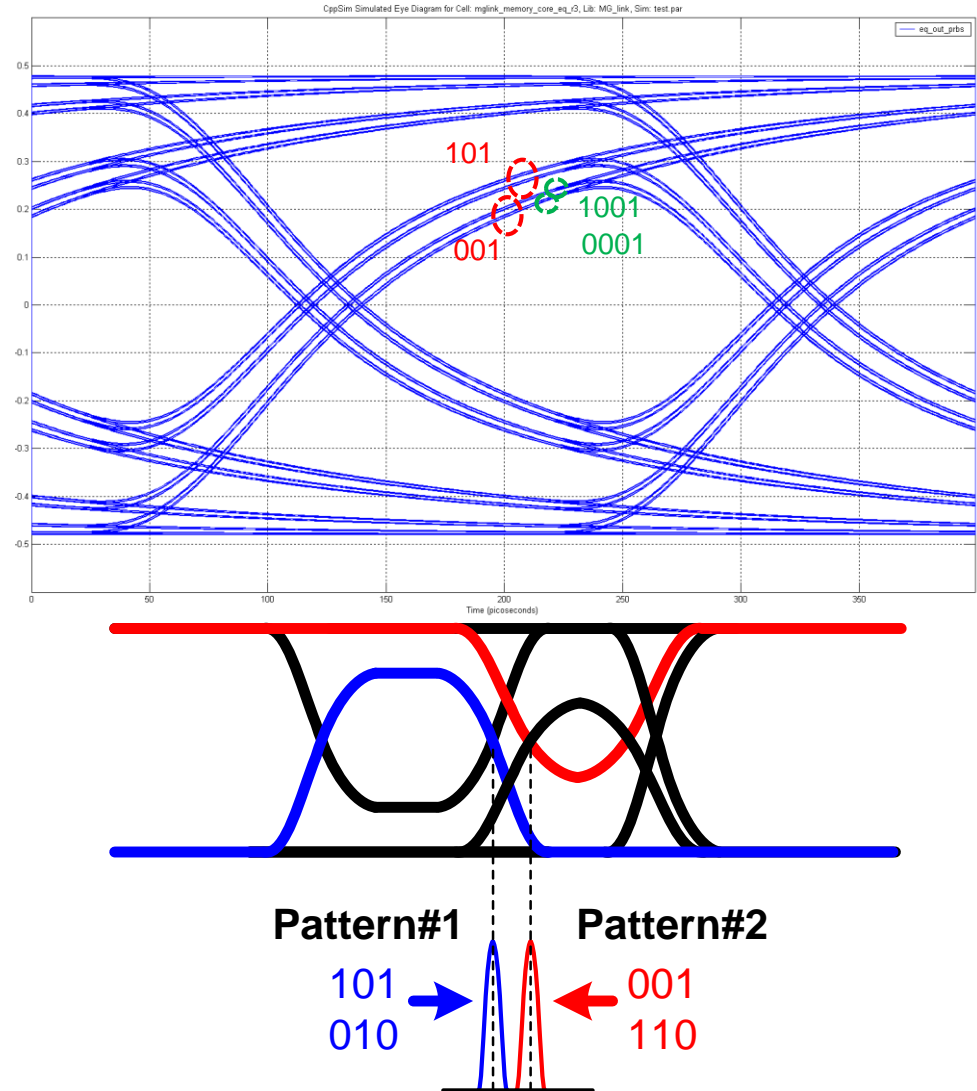
- **Data dependent jitter**
 - When a transition follows consecutive bits (e.g. 110)
→ edge-shift backward
 - When a transition follows alternating bits (e.g. 010)
→ edge-shift forward
- **Random Jitter**
 - Convolution with data dependent jitter
- **As the channel loss increases, the eye histogram splits**



References

- Bidyut K. Sen and Richard L. Wheeler. “Skin Effects Models for Transmission Line Structures using Generic SPICE Circuit Simulators”, IEEE 7th Topical Meeting on Electrical Performance of Electronic Packaging, 1998
- S Kim and D.P. Neikirk, “Compact Equivalent Circuit Model for the Skin Effect”, IEEE MTT-S International Microwave Symposium Digest, 1996
- M. Tsuk, “The Internal Impedance of Conductors with Arbitrary Cross Sections”, Progress in Electromagnetics Research Symposium, July 2000
- David M. Pozar, “Microwave Engineering” John Wiley & Sons, Inc. 2005

Backplane Example

   

Topics in IC Design

7.2 Equalizers

Deog-Kyoon Jeong

dkjeong@snu.ac.kr

School of Electrical and Computer Engineering


Seoul National University

2015 Spring

Outline

- **Equalizer Overview**
- **TX Equalizer**
 - FIR (Finite Impulse Response) Filter
 - Pre-de-emphasis
- **Continuous-Time RX Equalizer**
 - CT Linear Equalizer (CTLE)
 - Bandwidth extension techniques
- **Discrete-Time Equalizer**
 - Feed-Forward Equalizer (FFE)
 - Decision Feedback Equalizer (DFE)
- **Equalizer Adaptation**


Channel Bandwidth and ISI

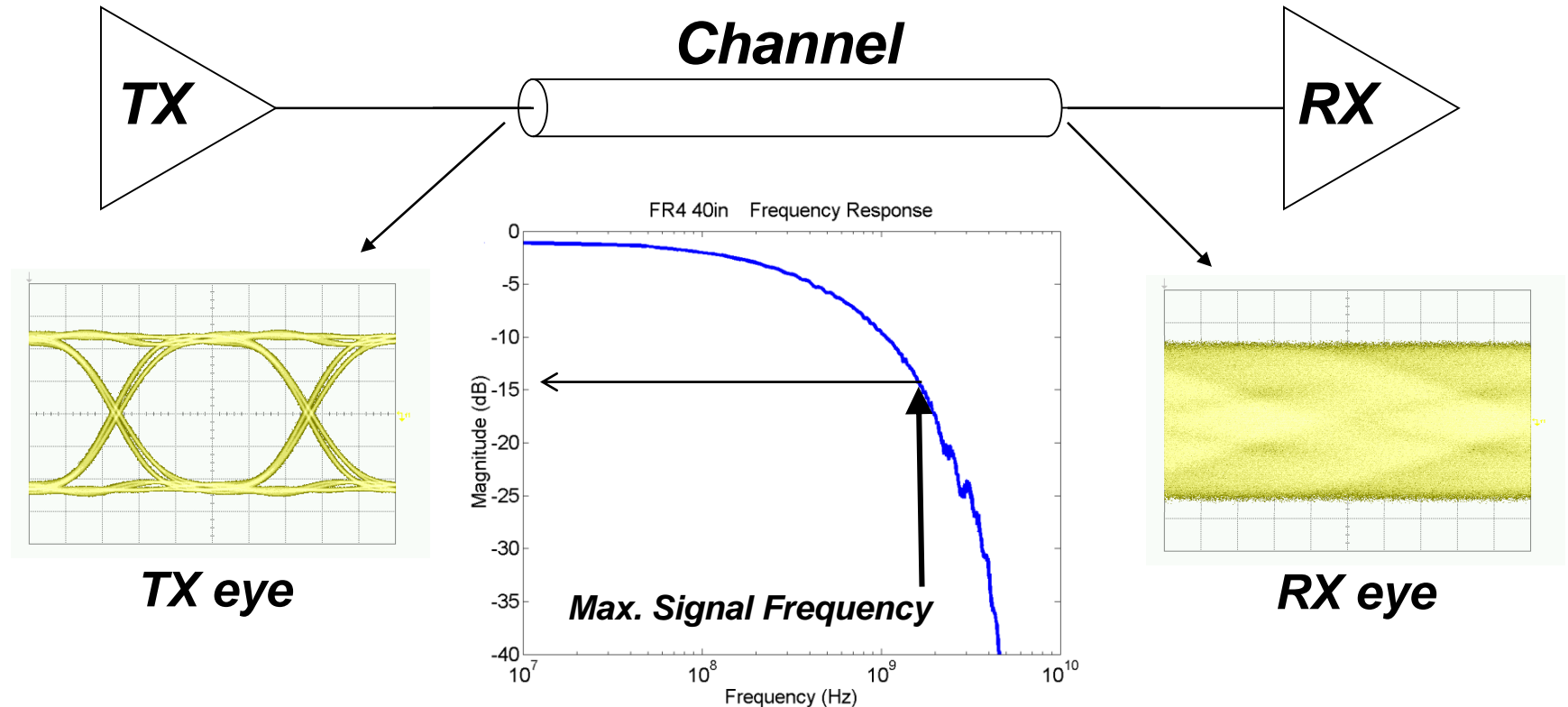

- An I/O link = transmitter (TX) + channel + receiver (RX)
- TX,RX contributes voltage noise and timing jitter
- Limited channel bandwidth introduces inter-symbol interference (ISI)
- Bit error rate (BER) depends on voltage noise, timing jitter and ISI

[Broadcom Corp., Wong]

Channel Equalization

 

- ITRS roadmap predicts that I/O clock rate increases 20% per year
- Channel bandwidth is not scaling at the same rate
- **One of the bottlenecks of increasing I/O speed is limited channel bandwidth.**
- **Channel equalization compensates ISI**


[Broadcom Corp., Wong]

Definitions of Equalization


- Equalization is the process of using passive or active electronic elements or digital algorithms for the purpose of flattening the frequency response characteristics of a system.

Channel Loss and Equalization


6Gbps @
RG58 - 2m

 


6Gbps @
RG58 - 10m

 

6Gbps @
RG58 - 20m

 


Equalization in frequency domain

 


Equalizer Classification

 - **On-chip vs Off-chip**
 - On-chip: Pre-emphasis, CT-Linear, FFE, DFE
 - Off-chip: Cable equalization
- **TX vs RX**
 - TX: Pre-de-emphasis
 - Rx: CT-Linear equalizer, DFE, FIR filter
- **Continuous Time vs Digitally Sampled**
 - Analog: Linear equalizer, Continuous-time equalizer
 - Digital: DFE, FIR filter
- **Decision Feedback vs Feed-forward**




Power Spectral Density of NRZ


- $\text{sinc}^2(f)$

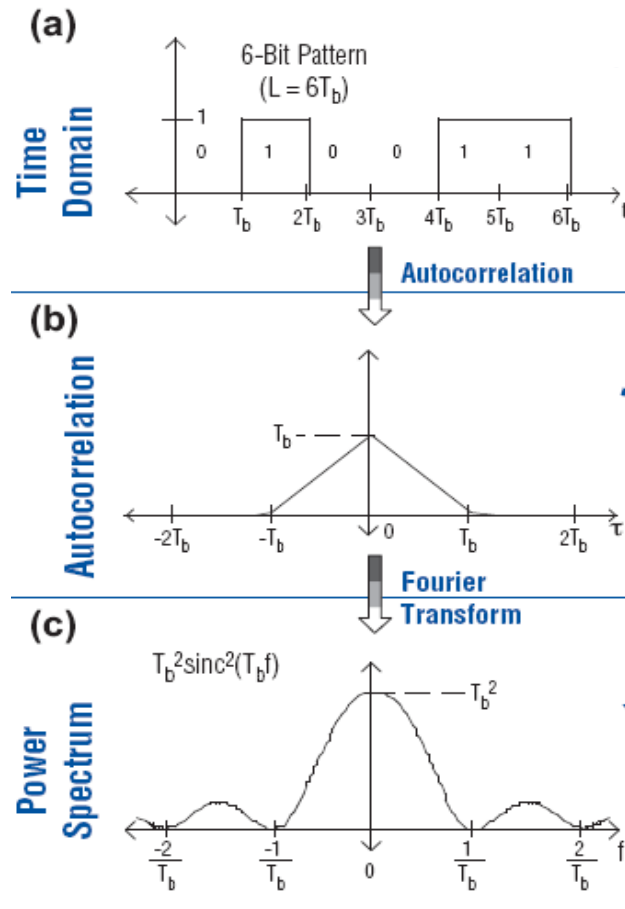


PSD after FIR filter

 


PSD of NRZ

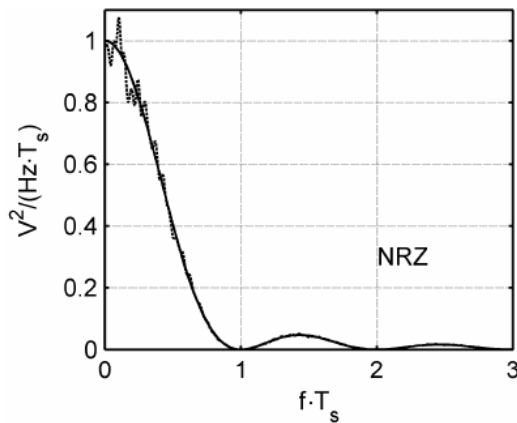

PSD of FIR filter

 


Eye after FIR filter

 


Pre-emphasis

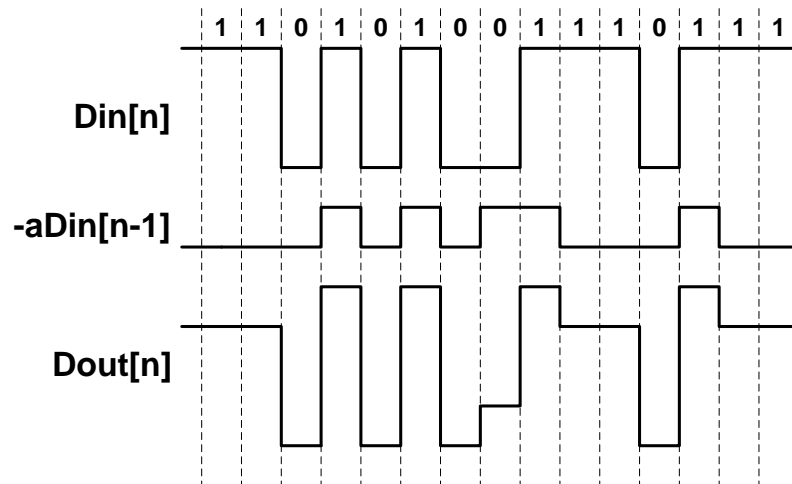- Attenuates the low-frequency contents.
- The output swing of the Tx driver is limited.
 - Be careful about the amplitude of output signal.
 - Sum of all abs values of coeffs must be smaller than the allowed peak.




Symbol Rate pre-emphasis

 


$$Dout[n] = a_{-1}Din[n+1] + Din[n] - a_1Din[n-1] - a_2Din[n-2]$$

Pre-emphasis

 - Half-symbol rate by using latch with a half-cycle delay




Half-symbol Rate pre-emphasis

 


$$Dout[n] = a_1 Din[n+1/2] + Din[n] - a_1 Din[n-1/2] - a_2 Din[n-1]$$

TX Equalization Example(1)

Pulse Response of FIR

 


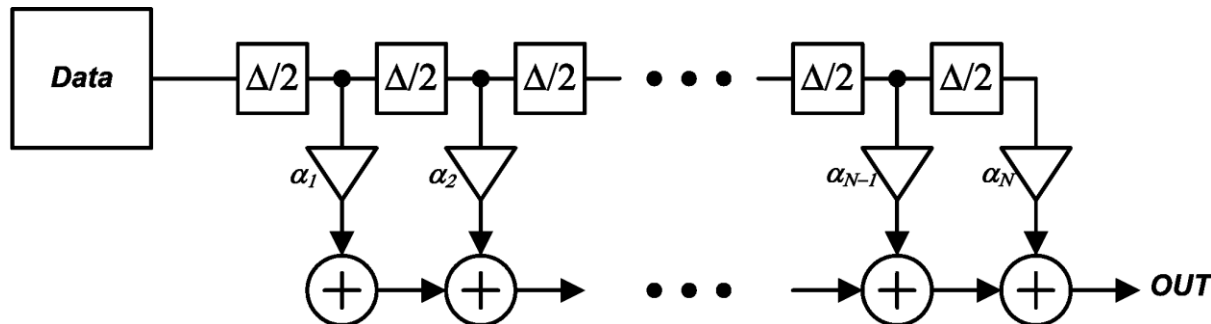- Delay signal by multiple of $\frac{1}{2}$ cycle time
- FIR with edge equalization (XFIR)
- Trade-off between voltage and timing margin



[JSSC'08, Wong]


Tx Equalization Example(1)

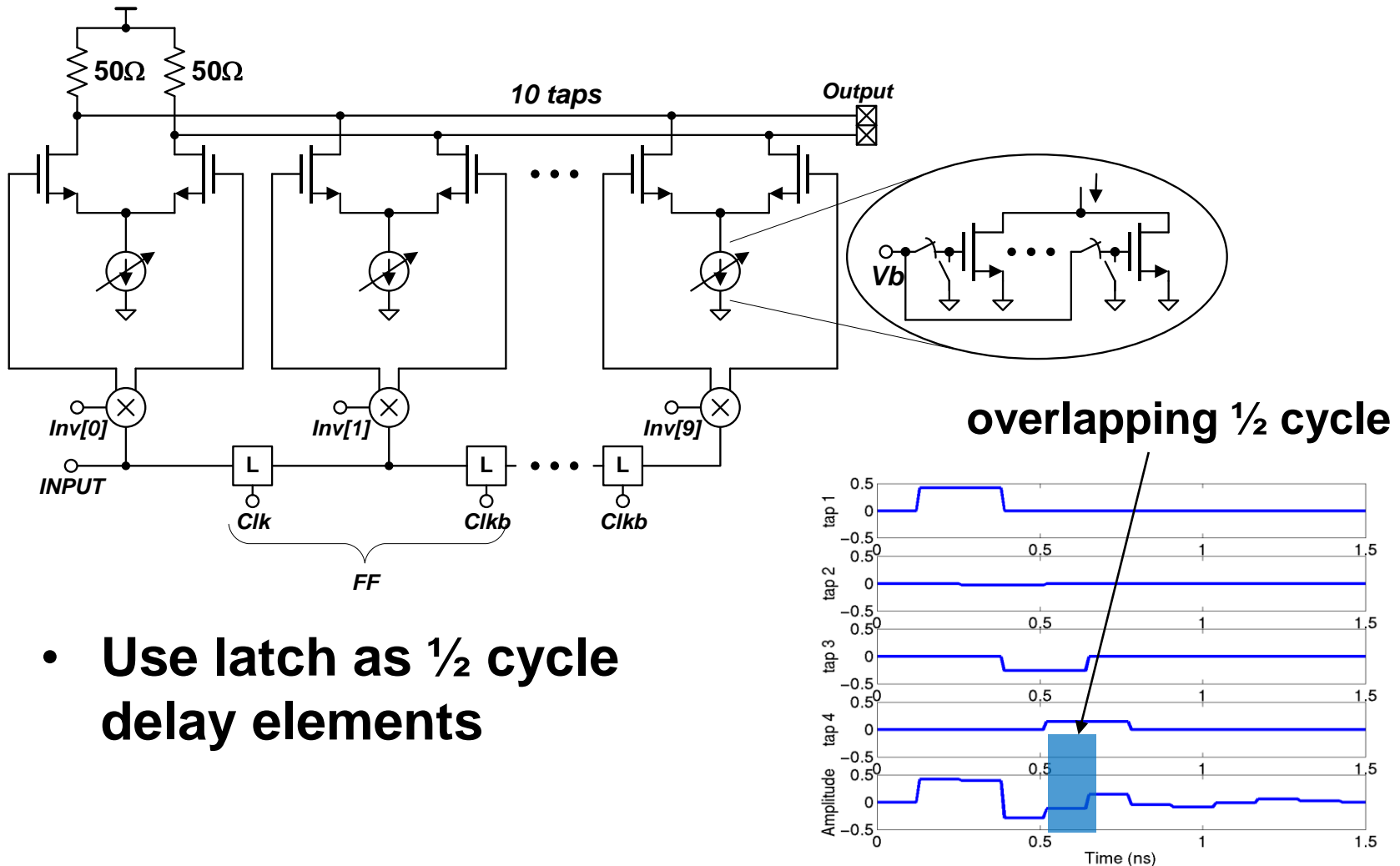

- Use latch as $\frac{1}{2}$ cycle delay elements

[JSSC'08, Wong]

Linear Equalizer

 

$$A_V = \frac{-g_m R_L}{1 + g_m Z_S}$$

$$A_V = \frac{-\frac{g_m R_L}{1 + 0.5 R_D g_m} (1 + s R_D C_D)}{1 + \frac{s R_D C_D}{1 + 0.5 g_m R_D}}$$


$$\omega_Z \approx \frac{1}{R_D C_D}$$

$$\omega_P \approx \frac{1 + 0.5 g_m R_D}{R_D C_D}$$


$$A_{V,Low} \approx \frac{g_m R_L}{1 + 0.5 R_D g_m}$$

- Addition of zero to boost high frequency
- Capacitive and resistive degeneration

Resistance Tuning


 


Capacitance Tuning

 

High Performance Techniques

- Inductive Peaking

  

$$f_{-3\text{dB}} = \frac{1}{2\pi R_D C_L}$$



$$\frac{V_{\text{out}}}{V_{\text{in}}} = -g_m R_D \frac{s + 2\zeta\omega_n}{s^2 + 2\zeta\omega_n s + \omega_n^2} \frac{\omega_n}{2\zeta}$$

$$f_{-3\text{dB}} = \frac{1.79}{2\pi R_D C_L} \quad \text{for } \zeta = 1/\sqrt{2}$$

- Bandwidth extension by 79%
- No extra power consumption
- Area penalty

High Performance Techniques

- f_T Doubler

 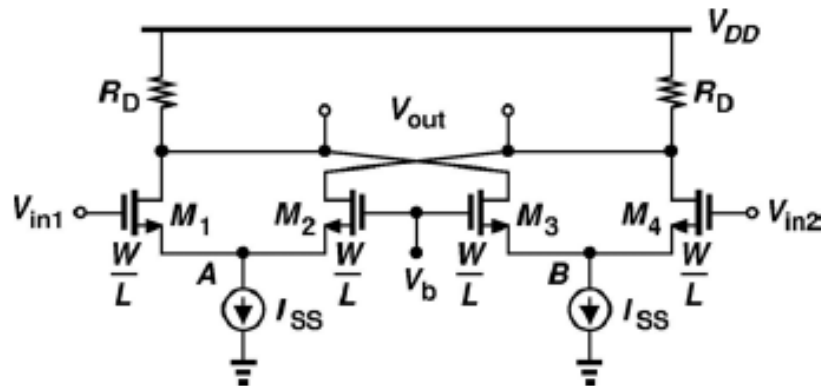


$$V_{out} = g_m (V_{in1} - V_{in2}) R_D$$

- Bandwidth Extension

- Decrease the effective input capacitance
- Parasitics on tail current sources degrade the performance

High Performance Techniques






- Cherry Hooper Amplifier

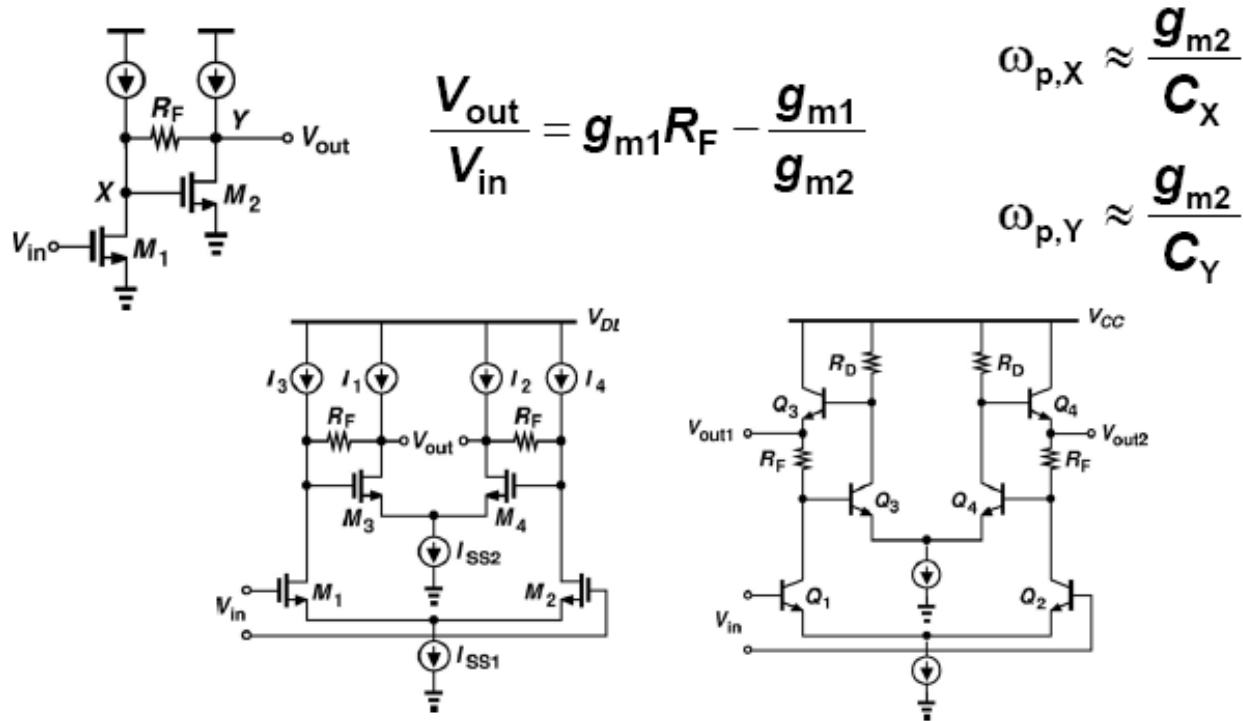


- Bandwidth Extended
- Reduced voltage headroom

High Performance Techniques


3dB Bandwidth

     

Peaking

 


Linear Equalizer Examples(1)


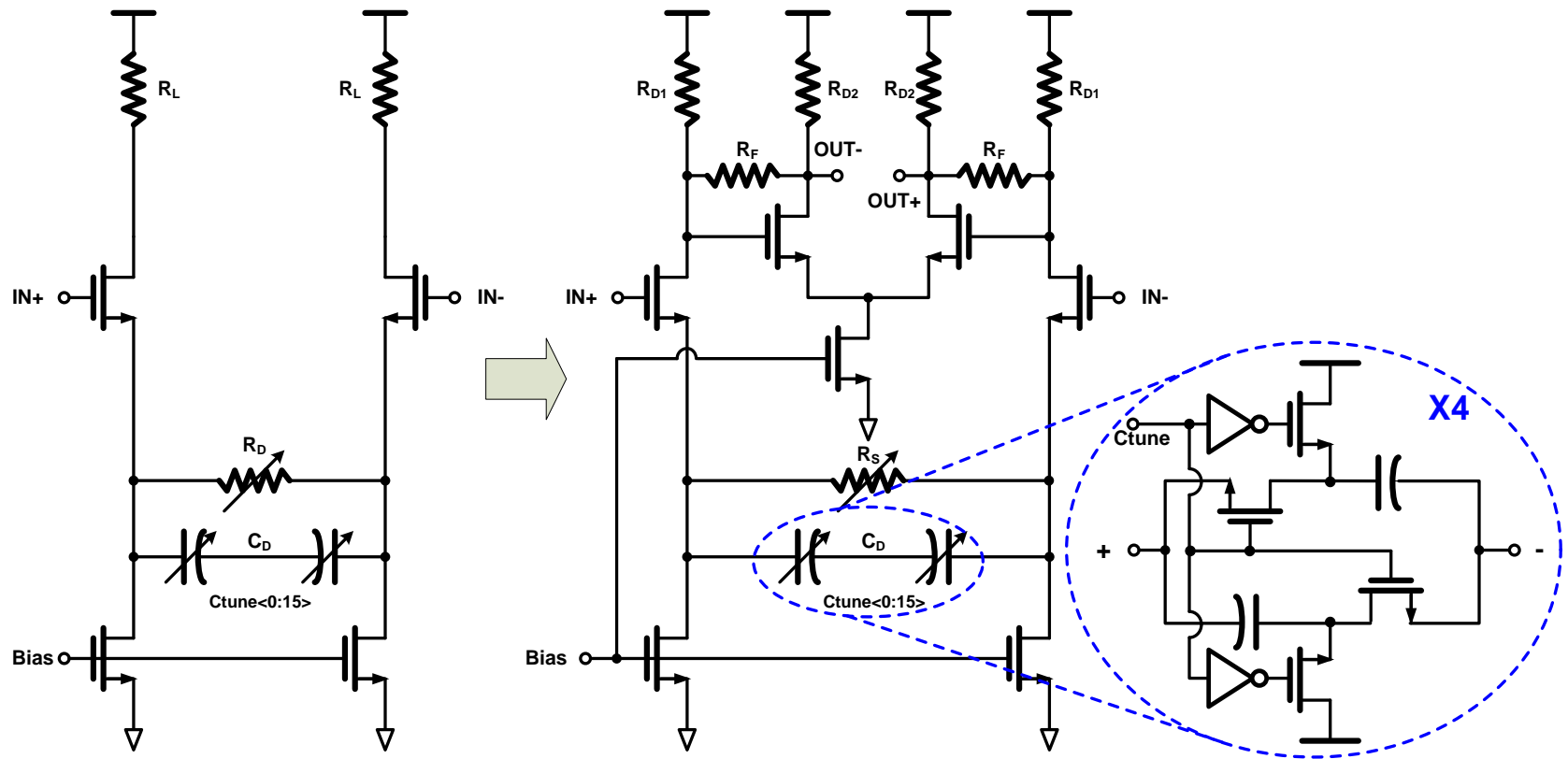


- **30% Bandwidth increase**



Linear Equalizer Examples(1)

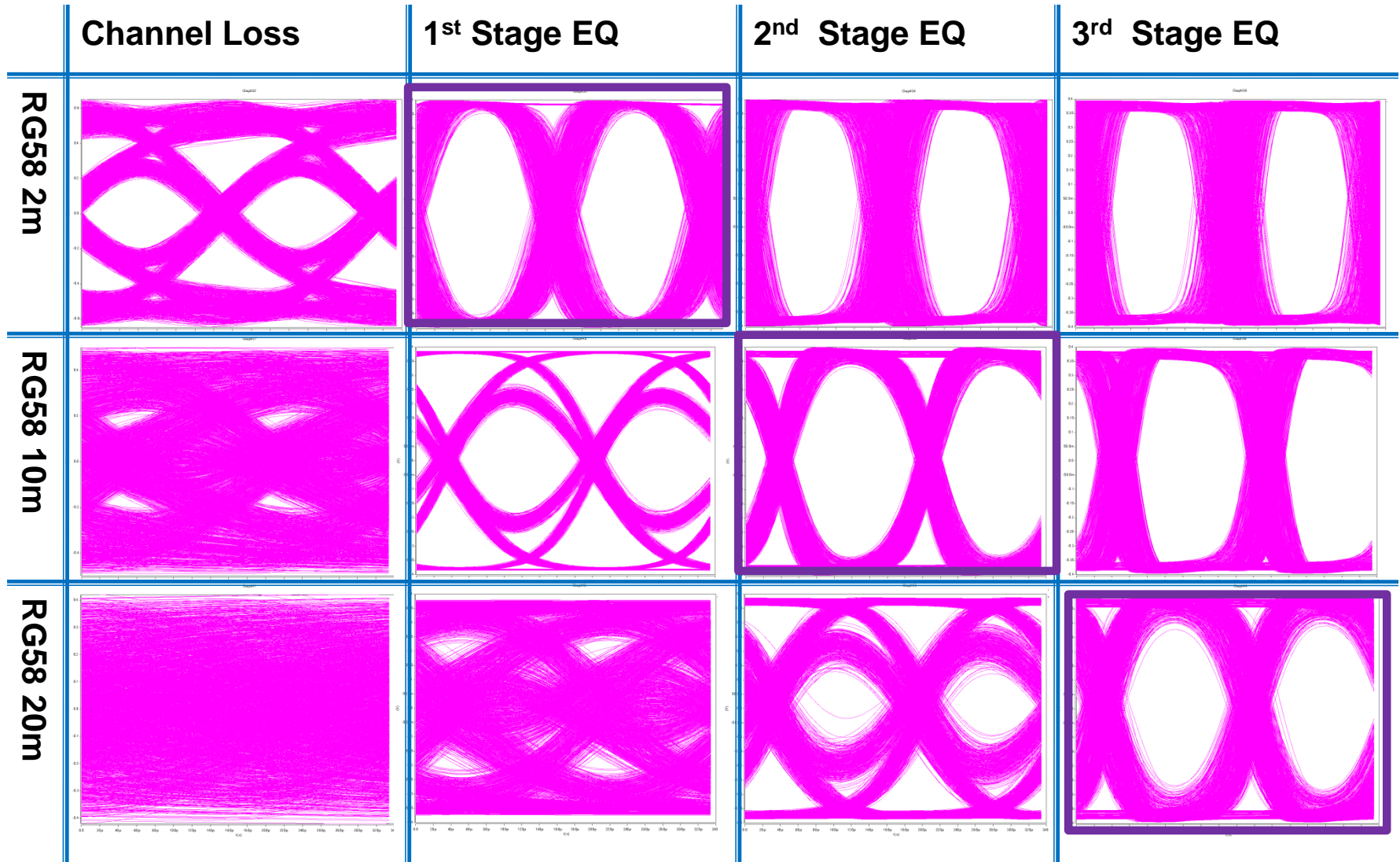

Linear Equalizer Examples(2)

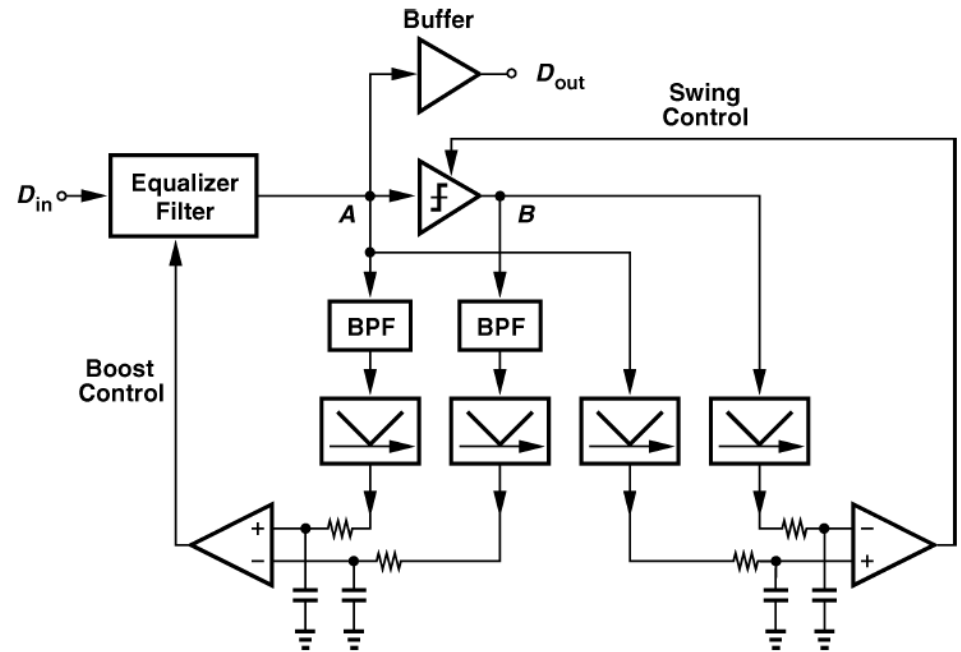
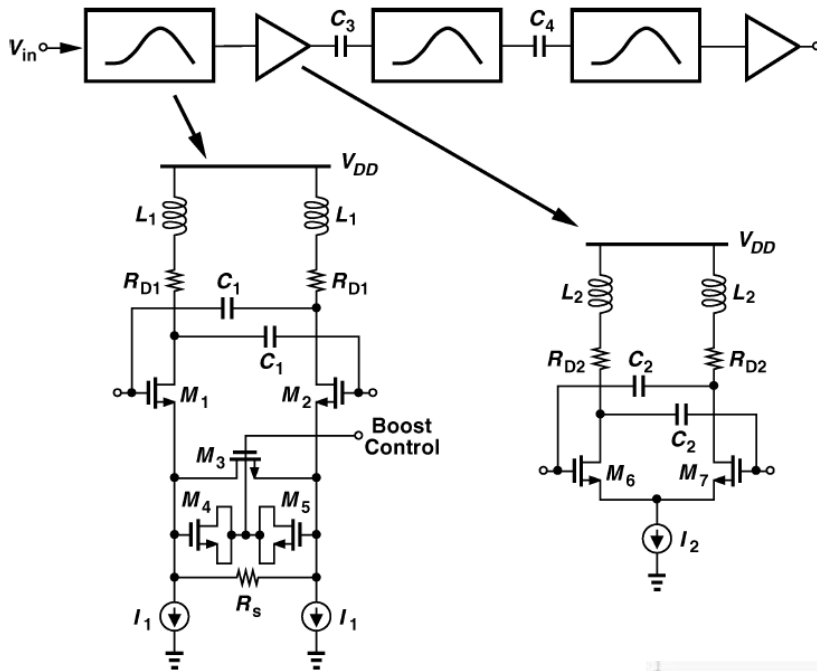


10Gbps Eye diagram →

 
 


[JSSC'07, Razavi]

Linear Equalizer Examples(3)

  



40Gbps Eye(before LE)

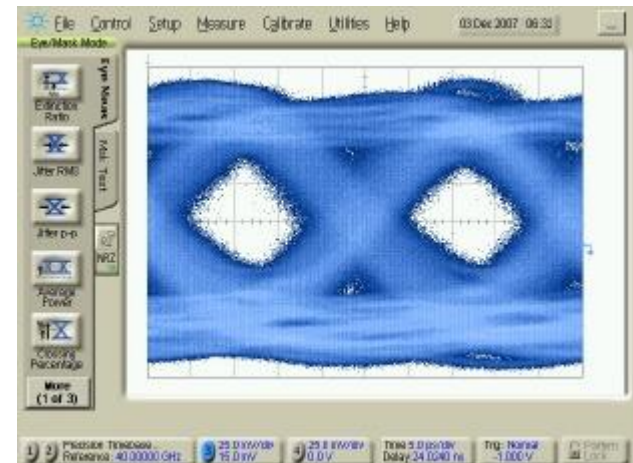 


40Gbps Eye(after LE)

[SOVC'08, Jian-Hao Lu]

Linear Equalizer Examples(4)

  


AC response in nominal corner

 

$$A_V(s) = \frac{g_m}{g_{m,L}} \cdot \frac{sR_G C_G + 1}{s^2 \frac{R_G C_G C_L}{g_{m,L}} + s \frac{(C_L + C_G)}{g_{m,L}} + 1}$$

[JSSC'09, Haechang Lee]


Continuous-Time Equalizer

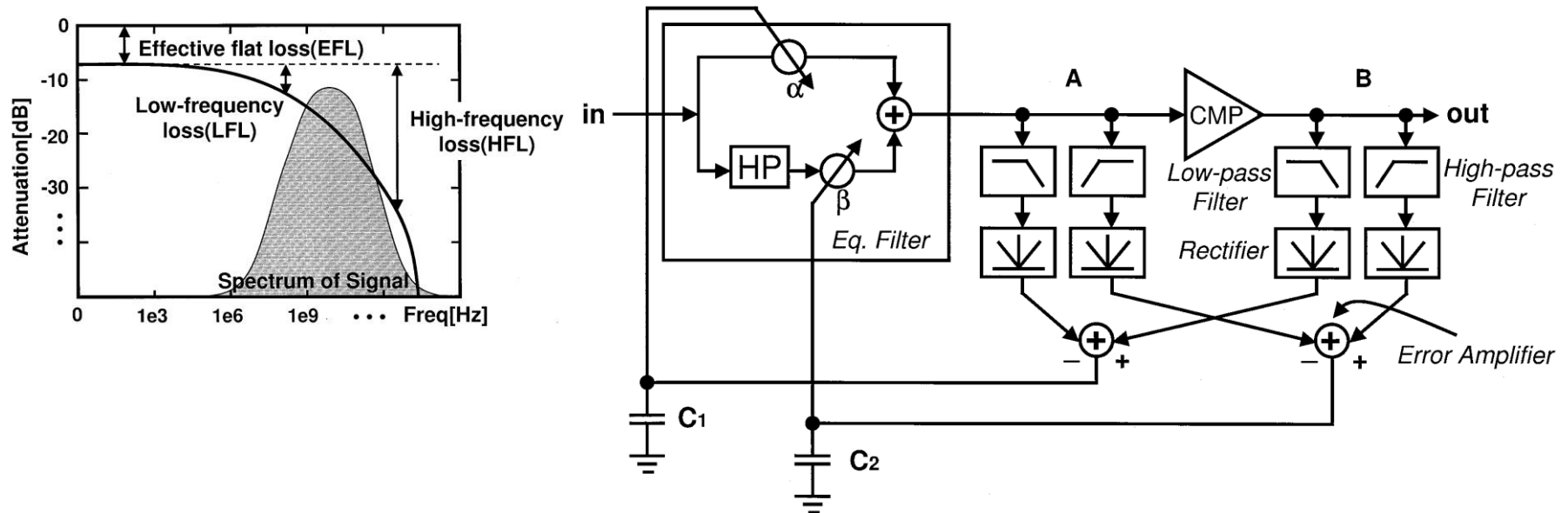

- **Advantages and Disadvantages**
 - No dependency with the timing recovery
 - Speed is limited by the equalizing filter
 - Tradeoff between adaptation accuracy and operating frequency


[JSSC'04, Choi]

Discrete-time Channel Modeling

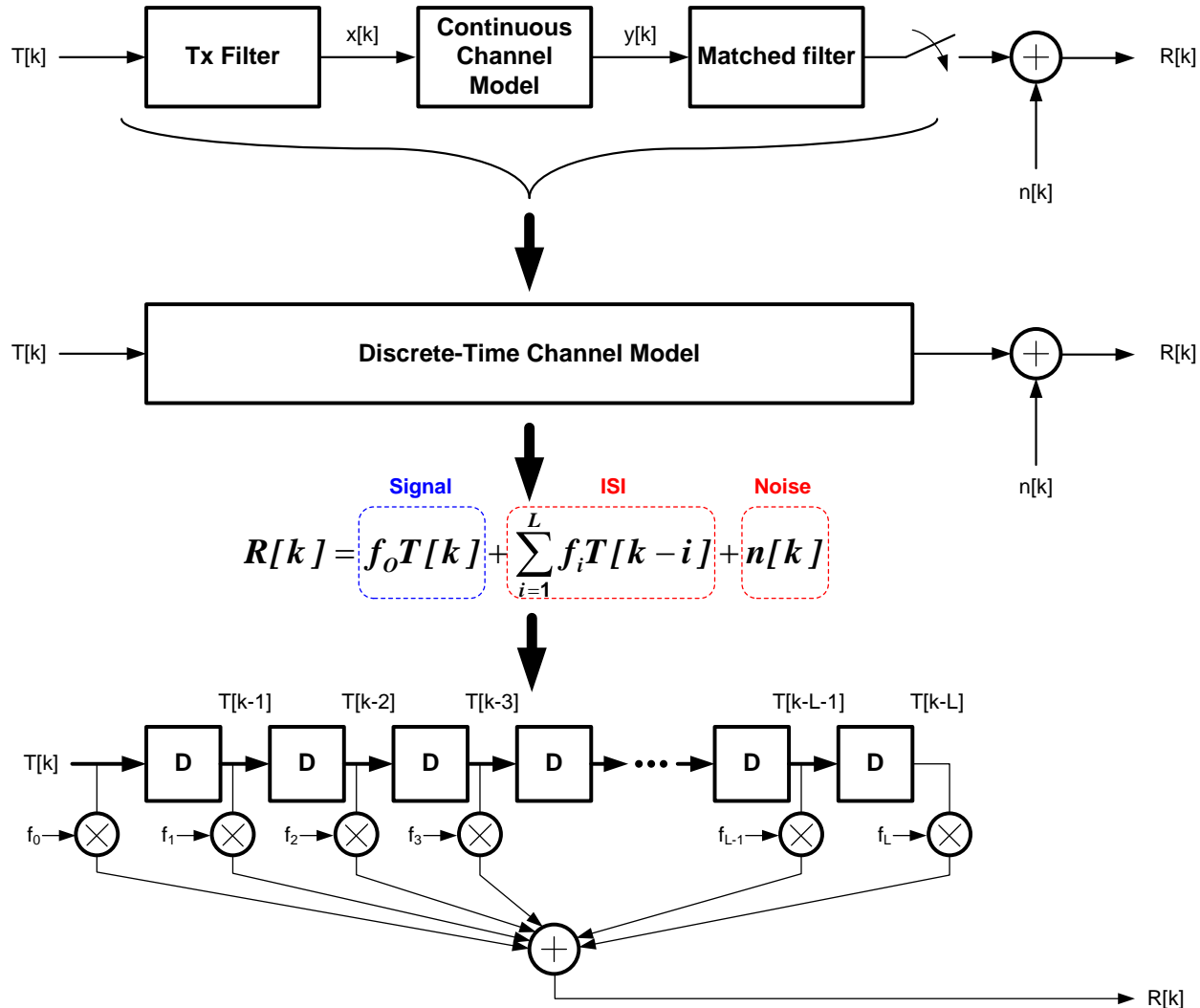


Feed-Forward Equalizer

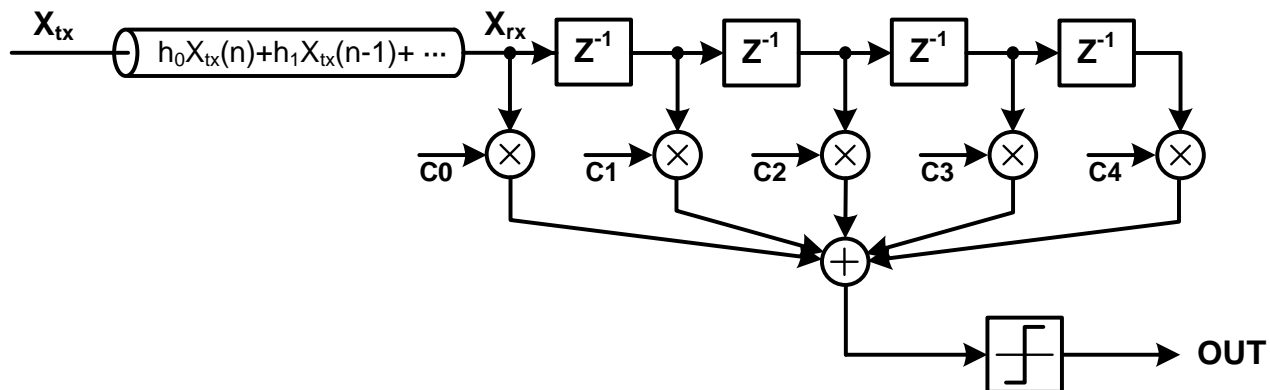
- **AD conversion required**
- **Relaxed timing constraints**
 - Timing constraint easy to meet
 - No time-critical feedback path
- **Boosts high-freq. noise as well**
- **High power consumption**
 - ADC and digital blocks




FFE Examples(1)

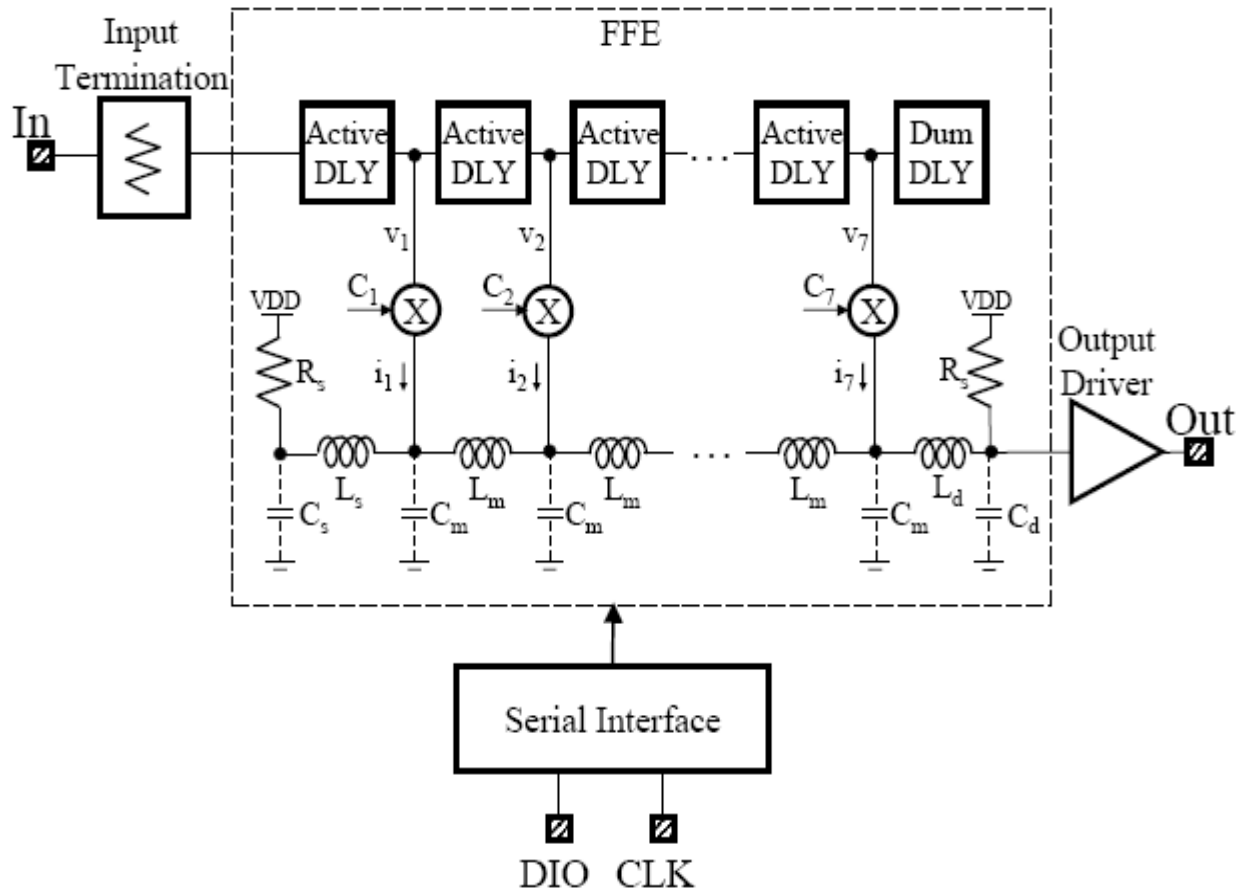

40Gb/s 7-Tap FFE

 

FFE ↓

 

[ISSCC'09, A. Momtaz]


Decision Feedback Equalizer

- Superior performance but timing constraints
 - Hard to design DFE
- Only post-cursor cancelled
 - Linear equalizer can equalize both pre- and post-cursors

$$X_{rx}(n) = h_0 X_{tx}(n) + h_1 X_{tx}(n-1) + \dots$$


$$X_{fb}(n) = C_0 X_{tx}(n) + C_1 X_{tx}(n-2) + \dots$$
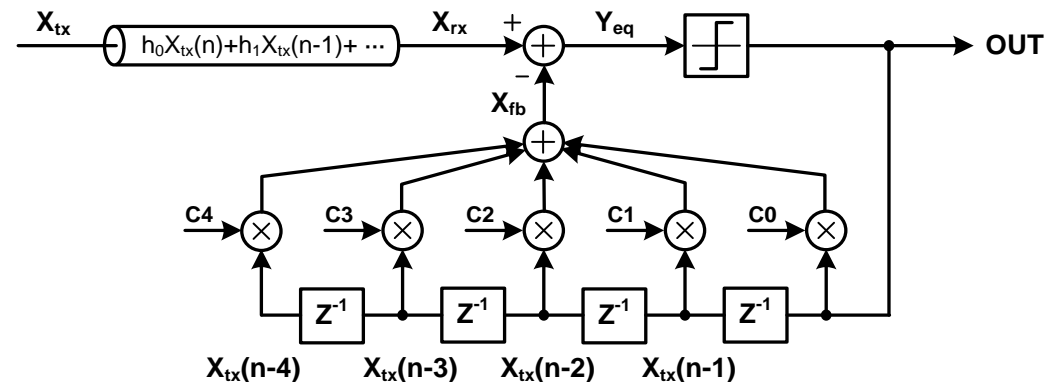
$$Y_{eq}(n) = h_0 X_{tx}(n) + h_1 X_{tx}(n-1) + \dots - C_0 X_{tx}(n) - C_1 X_{tx}(n-2) - \dots$$





**If $C_0=0$ & $C_1= h_1$ & $C_2= h_2$ & ..., then $Y_{eq}(n)=h_0 X_{tx}(n)$
 - All ISI due to post-cursors cancelled.**

Summer Implementation

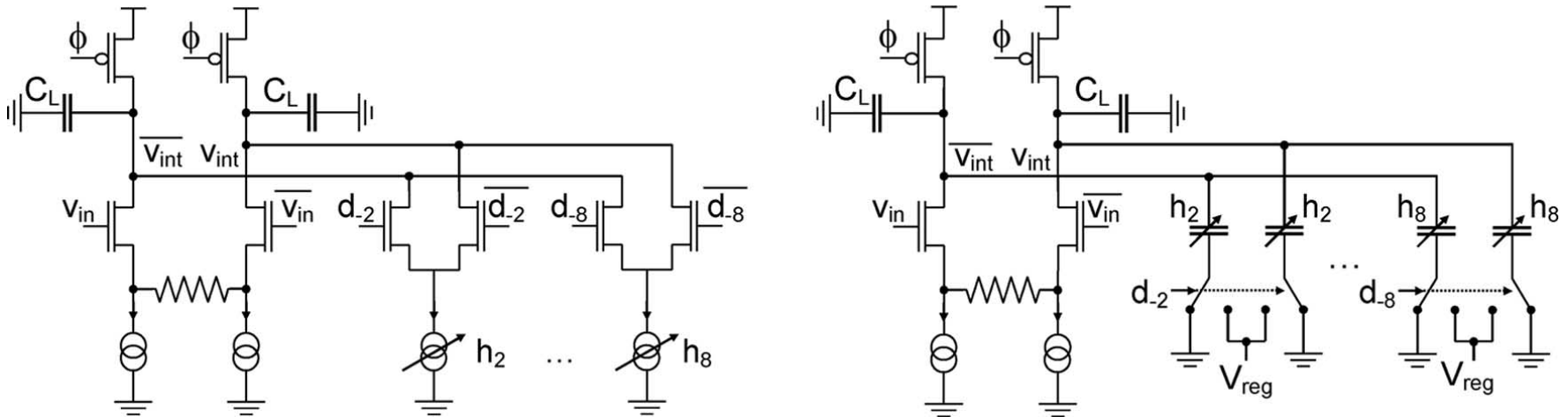

- **Current summer or Capacitor switching**
 - In front of a sampler
 - Resettable PMOS load can replace load resistor
 - Summer must settle within a certain level of accuracy for ISI cancellation
 - Trade-off between summer output swing and settling time
 - Can result in large bias current for input and taps
- [JSSC'12, Thomas Toifl]


Summing Sampler Implementation

  


- **Summer merged at sampler**
 - Both current and capacitance switching can be used
 - Latency reduced
 - Speed limited by increased summation node capacitance

DFE Implementation

Direct Feedback

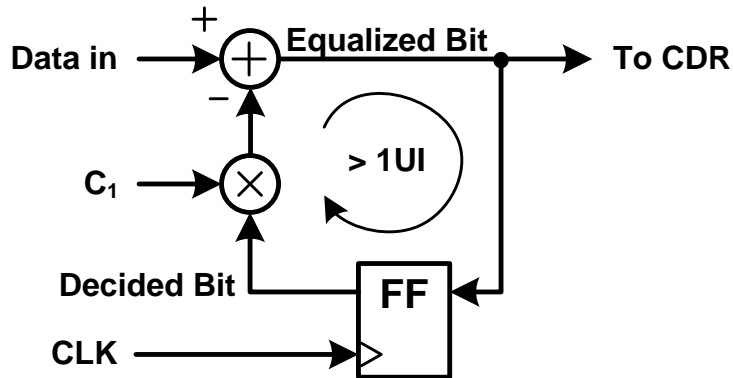


Loop Unrolling

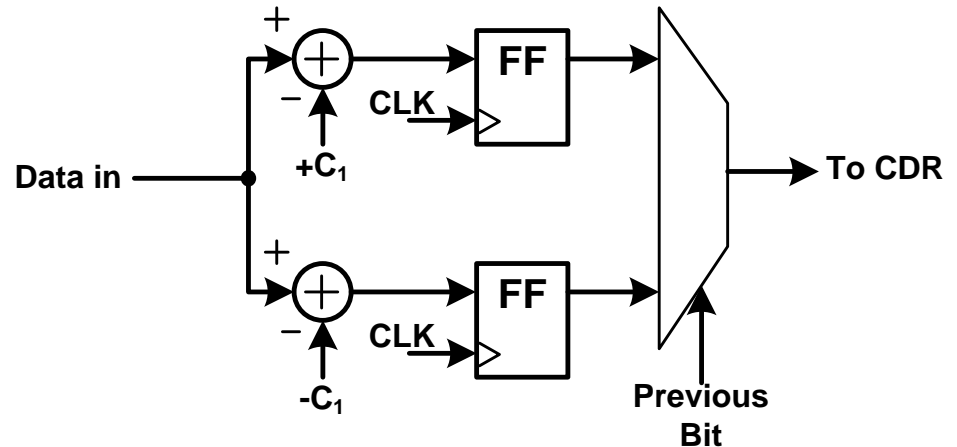

- **Direct feedback**
 - Simple architecture
 - Critical path delay should be less than $1UI$
- **Loop unrolling**
 - Relaxes time constraints
 - Reduces the loading at the summing node
 - Increase complexity


Loop Unrolling (Speculation)

- Half-rate 2-tap DFE Architecture

 


Reduction of Critical Path Delay

Flip-Flop Topology

 

Latch Topology('09 JSSC Pozzoni)

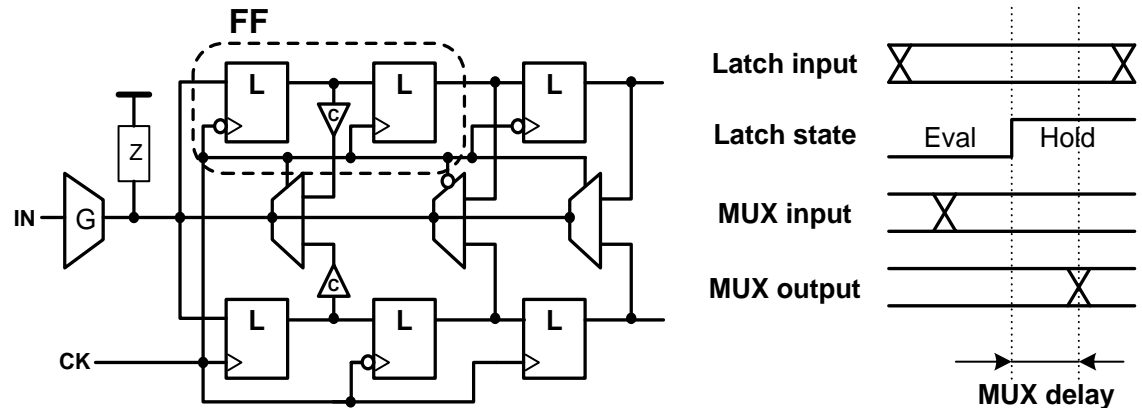

- **Flip-Flop Topology**

- The 1st tap feedback delay consists of FF and MUX delay.

- **Latch-Based Topology**

- MUX incorporates the function of the 2nd latch in a FF.
- The propagation delay to be limited to the MUX delay.

[JSSC'09, Pozzoni]

References

- Sameh Abraham and Behzad Razavi, “A 20-Gbps Serial Link for High-Loss Channels” UCLA
- MAXIM, “Spectral Content of NRZ Test Patterns”
- Koon-Lun Jackie Wong, E-Hung Chen, and Chih-Kong Ken Yang, “Edge and Data Adaptive Equalization of Serial-Link Transceivers” IEEE, JSSC Sep. 2008
- Haechang Lee, “A 16 Gb/s/Link, 64 GB/s Bidirectional Asymmetric Memory Interface” IEEE, JSSC April 2009
- Massimo Pozzoni, “A Multi-Standard 1.5 to 10 Gb/s Latch-Based 3-Tap DFE Receiver With a SSC Tolerant CDR for Serial Backplane Communication” IEEE, JSSC Apr. 2009
- Srikanth Gondi and Behzad Razavi, “Equalization and Clock and Data Recovery Techniques for 10-Gb/s CMOS Serial-Link Receivers”, IEEE JSSC Sept. 2007
- Jian-Hao Lu “A 40Gb/s Low-Power Analog Equalizer in 0.13um CMOS Technology”, IEEE SOVC 2008
- A. Momtaz “An 80mW 40Gb/s 7-Tap T/2-Spaced FFE in 65nm CMOS”, IEEE ISSCC 2009

Topics in IC Design

7.3 DFE (by example)

Deog-Kyoon Jeong

dkjeong@snu.ac.kr


School of Electrical and Computer Engineering

Seoul National University

2020 Fall

 
Example Channel

- Channel characteristics
 - 1st-order RC channel ($R=50\ \Omega$, $C = 20\text{pF}$)
 - At the transmission rate of 1 Gbps
 - Attenuation at Nyquist Frequency = $1/\sqrt{1+\pi^2} = -10.352\ \text{dB}$
 - Phase delay at Nyquist Frequency = -72.3°




TX and RX Eye Diagrams

- PRBS-7 NRZ

 


Height: 1 V
Time width: 1 ns

 

Height: 0.143 V
Time width: 546 ps

Eye Diagram and Channel Loss

 - **Loss at the Nyquist frequency.**
 - The 1010 pattern contains the Nyquist frequency
 - Swing of this pattern indicates the attenuation
 - See the dotted line and arrow in the picture above.
- $20\log(0.17/0.5) = -9.4\text{dB}$ (-10.35dB)




Single Bit Response

A. h_0 at maximum height

B. h_0 at maximum width

 C. h_0 at mid-point between two points of $h_{1/2} = h_{-1/2}$



Single Bit Response

A. h_0 at maximum height

B. h_0 at maximum width

C. h_0 at mid-point between two points of $h_{1/2} = h_{-1/2}$


CASE	h_0	h_1	h_2	h_3	h_4
A. Maximum height	0.5718	0.2446	0.0889	0.0323	0.0114
B. Maximum time width	0.5716	0.2411	0.0875	0.0318	0.0113
C. $h_{1/2}=h_{-1/2}$	0.5692	0.2346	0.0852	0.0309	0.0110

- **Precursor $h_{-1} \approx 0.05$**
- **Sum of all coefficients = 0.949, 0.9433, 0.9309 + precursor ≈ 1**

DFE Architecture

- 1-tap DFE

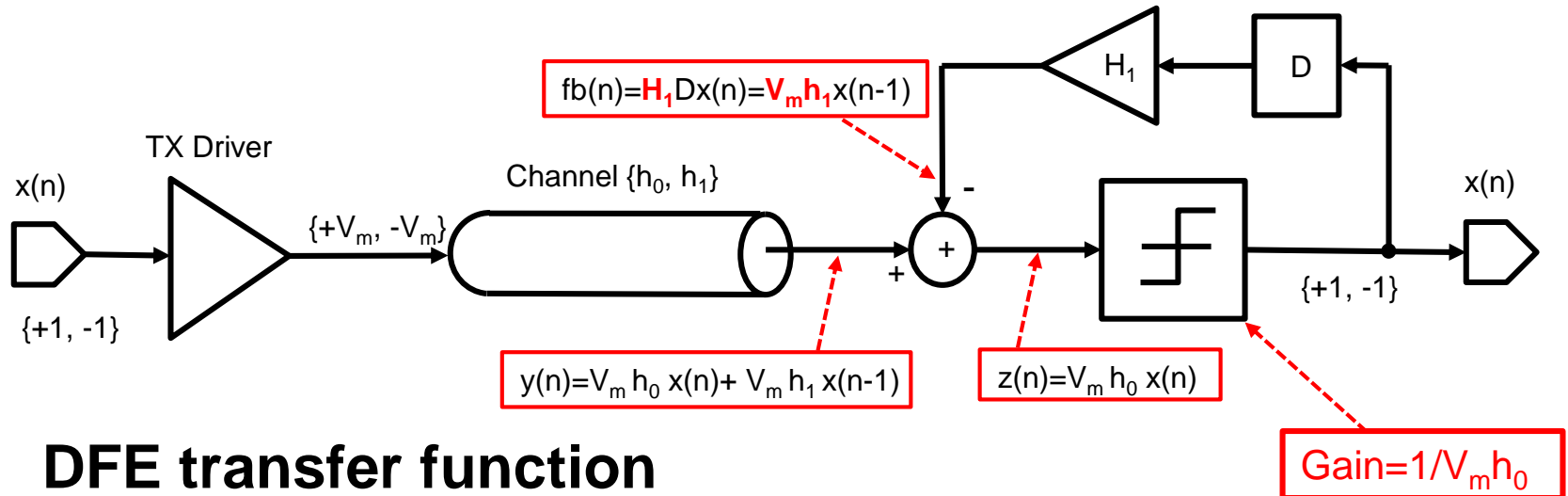- $H_1 = V_m^* (h_1 \text{ of SBR}) = V_m^* 0.2446 (= 0.1223 \text{ if } V_m = 0.5V)$
- Other post-cursors not cancelled



- DFE transfer function

$$DFE \text{ Gain}(z) = \frac{\frac{1}{V_m h_0}}{1 + H_1 \frac{1}{V_m h_0} z^{-1}} = \frac{1}{V_m h_0} \frac{1}{1 + h_1 z^{-1}}$$



Maximum Boost of 1-tap DFE

$$\begin{aligned}\text{DFE Gain}(\omega) &= \frac{1}{V_m} \frac{1}{|h_0 + h_1 e^{-j\omega T}|} \\ &= \frac{1}{V_m} \frac{1}{\sqrt{h_0^2 + 2h_0 h_1 \cos(\omega T) + h_1^2}}\end{aligned}$$

- DFE Gain at DC = $1/(h_0+h_1)/V_m = 2.450 = 7.78\text{dB}$ (with $V_m=0.5\text{V}$)
- DFE Gain at Nyquist = $1/(h_0-h_1)/V_m = 6.112 = 15.72\text{dB}$ (with $V_m=0.5\text{V}$)
- DFE Max Boost
= $(h_0+h_1)/(h_0-h_1) = (0.5718+0.2446)/(0.5718-0.2446)$
= $2.496 = 7.94\text{dB}$
- Channel DC Gain with all postcursors = $V_m = 0.5\text{V}$
- Overall DC gain = $0.5 \times 2.450 = 1.225 = 1.76\text{dB}$ ($\neq 1$, due to no 2nd or higher-order postcursor cancellation)
- Overall gain at Nyquist = $-10.53\text{dB} + 7.94\text{dB} = -2.59\text{dB}$



Eye Diagram with 1-tap DFE

- With feedback delay of 0.25ns

  

What if input amplitude changed?

  - Input amplitude (V_m) is increased from 1.0V to 0.5V, while DFE tap coefficient ($V_m * h_1$) is fixed.
- Tap coeff is reduced by half in effect.
- Need to change tap coeffs depending on the input amplitude!





4-Tap DFE

$$\text{DFE Gain}(\omega) = \frac{1}{V_m} \frac{1}{|h_0 + h_1 e^{-j\omega T} + h_2 e^{-j2\omega T} + h_3 e^{-j3\omega T} + h_4 e^{-j4\omega T}|}$$

- DFE Gain at DC = $1/(h_0+h_1+h_2+h_3+h_4)/V_m = 2.107 = 6.47\text{dB}$ (with $V_m=0.5\text{V}$)
- DFE Gain at Nyquist = $5.061 = 14.08\text{dB}$ (with $V_m=0.5\text{V}$)
- DFE Max Boost
= $14.08\text{dB} - 6.47\text{dB} = 7.61\text{dB}$
- Channel DC Gain with all postcursors = $V_m = 0.5\text{V}$
- Overall DC gain = $0.5 \times 2.107 = 1.054 = 0.45\text{dB}$ ($\neq 1$, due to no 2nd or higher-order postcursor cancellation)
- Overall gain at Nyquist = $-10.53\text{dB} + 7.61\text{dB} = -2.92\text{dB}$

Eye Diagram with 4-tap DFE

  - With feedback delay of 0.25ns
- Almost all the post-cursors removed
- Remaining ISI due to precursors



References

- Sameh Abraham and Behzad Razavi, “A 20-Gbps Serial Link for High-Loss Channels” UCLA
- MAXIM, “Spectral Content of NRZ Test Patterns”
- Koon-Lun Jackie Wong, E-Hung Chen, and Chih-Kong Ken Yang, “Edge and Data Adaptive Equalization of Serial-Link Transceivers” IEEE, JSSC Sep. 2008
- Haechang Lee, “A 16 Gb/s/Link, 64 GB/s Bidirectional Asymmetric Memory Interface” IEEE, JSSC April 2009
- Massimo Pozzoni, “A Multi-Standard 1.5 to 10 Gb/s Latch-Based 3-Tap DFE Receiver With a SSC Tolerant CDR for Serial Backplane Communication” IEEE, JSSC Apr. 2009
- Srikanth Gondi and Behzad Razavi, “Equalization and Clock and Data Recovery Techniques for 10-Gb/s CMOS Serial-Link Receivers”, IEEE JSSC Sept. 2007
- Jian-Hao Lu “A 40Gb/s Low-Power Analog Equalizer in 0.13um CMOS Technology”, IEEE SOVC 2008
- A. Momtaz “An 80mW 40Gb/s 7-Tap T/2-Spaced FFE in 65nm CMOS”, IEEE ISSCC 2009

Topics in IC Design


7.4 Adaptive DFE and Timing Recovery

Deog-Kyoon Jeong
dkjeong@snu.ac.kr

School of Electrical and Computer Engineering
Seoul National University
2020 Fall

Equalizer Adaptation

 - **Adaptive Equalization**
 - Compensate changes in the transmission channel characteristics
 - Compensate manufacturing variation
 - Suitable for multi-standard
- **Can be applied to any equalizers; FFE, CTLE, and DFE**



DFE Adaptation

- LMS algorithm**

$$fb = \sum_{k=1}^2 C_k y(n-k)$$

$$e(n) = y(n) - a(n)$$

$$a(n) = x(n) - \sum_{k=1}^2 C_k y(n-k)$$



With LMS updating equation

$$C_k(n+1) = C_k(n) + \mu e(n) y(n-k)$$



Or use sign-sign adaptation

- How to set $A_m h_0$?**

  - Must know a priori or
- Adapt so that $E[e(n)] = 0$.



Single Bit Response & Eye Diagram

  

- **Data Samples:**

$$y(n) = h_3x(n-3) + h_2x(n-2) + h_1x(n-1) + h_0x(n) + h_{-1}x(n+1)$$

ISI due to Post-Cursor

Main Cursor


ISI due to Pre-Cursor

- **Edge Samples:**

$$y\left(n - \frac{1}{2}\right) = h_{2\frac{1}{2}}x(n-3) + h_{1\frac{1}{2}}x(n-2) + h_{\frac{1}{2}}x(n-1) + h_{-\frac{1}{2}}x(n) + h_{-1\frac{1}{2}}x(n+1)$$

$$y\left(n + \frac{1}{2}\right) = h_{2\frac{1}{2}}x(n-2) + h_{1\frac{1}{2}}x(n-1) + h_{\frac{1}{2}}x(n) + h_{-\frac{1}{2}}x(n+1) + h_{-1\frac{1}{2}}x(n+2)$$

Eye Diagram and Timing Recovery

 

For the -1 \rightarrow +1 transition at $(n-1/2)$ (A),
if $h_{\frac{1}{2}} > h_{-\frac{1}{2}}$, then $y(n-1/2) > 0$.

Alexander PD asserts DOWN (VCO too fast),
and the next sampling time pushed down,
then $h_{-\frac{1}{2}}$ goes down and $h_{\frac{1}{2}}$ goes up,
eventually making $h_{\frac{1}{2}} = h_{-\frac{1}{2}}$.

Same result for +1 \rightarrow -1 transition (B)

- **Zero Crossing levels at $y(n-1/2)$**


A. -1 \rightarrow +1 transition at $y(n-1) = -1$, $y(n) = +1$

$$y\left(n - \frac{1}{2}\right) = h_{\frac{1}{2}}x(n-3) + h_{-\frac{1}{2}}x(n-2) - h_{\frac{1}{2}} + h_{-\frac{1}{2}} + h_{-\frac{1}{2}}x(n+1)$$

B. +1 \rightarrow -1 transition at $y(n-1) = +1$, $y(n) = -1$

$$y\left(n - \frac{1}{2}\right) = h_{\frac{1}{2}}x(n-3) + h_{-\frac{1}{2}}x(n-2) + h_{\frac{1}{2}} - h_{-\frac{1}{2}} + h_{-\frac{1}{2}}x(n+1)$$

Eye Diagram and Timing Recovery

 

For the $-1 \rightarrow +1$ transition at $(n+1/2)$ (B), if $h_{\frac{1}{2}} < h_{-\frac{1}{2}}$, then $y(n+1/2) > 0$.

Alexander PD asserts UP (VCO too slow), and the next sampling time pulled up, then $h_{-\frac{1}{2}}$ goes up and $h_{\frac{1}{2}}$ goes down, eventually making $h_{\frac{1}{2}} = h_{-\frac{1}{2}}$.

Same result for $+1 \rightarrow -1$ transition (B)

- **Zero Crossing levels at $y(n+1/2)$**

A. $-1 \rightarrow +1$ transition at $y(n) = -1$, $y(n+1) = +1$



$$y\left(n + \frac{1}{2}\right) = h_{\frac{1}{2}}x(n-2) + h_{-\frac{1}{2}}x(n-1) - h_{\frac{1}{2}} + h_{-\frac{1}{2}} + h_{-\frac{1}{2}}x(n+2)$$

B. $+1 \rightarrow -1$ transition at $y(n) = +1$, $y(n+1) = -1$

$$y\left(n + \frac{1}{2}\right) = h_{\frac{1}{2}}x(n-2) + h_{-\frac{1}{2}}x(n-1) + h_{\frac{1}{2}} - h_{-\frac{1}{2}} + h_{-\frac{1}{2}}x(n+2)$$

Eye Diagram and Timing Recovery

  - 2x oversampling with Alexander PD,
 - $h_{\frac{1}{2}} = h_{-\frac{1}{2}}$ holds.
 - may not offer max SNR when SBR is not symmetric.



Edge Equalization

- Reduce DDJ at edge for low-jitter clock recovery
- Edge DFE
 - Reduce the ISI due to edge post-cursors $h_{1\frac{1}{2}}$, $h_{2\frac{1}{2}}$, etc.
 - Not possible to cancel ISI due to edge pre-cursors $h_{-1\frac{1}{2}}$, etc.

- **Edge Samples:**


$$y\left(n - \frac{1}{2}\right) = h_{2\frac{1}{2}}x(n-3) + h_{1\frac{1}{2}}x(n-2) + \color{red}{h_{\frac{1}{2}}x(n-1)} + \color{red}{h_{-\frac{1}{2}}x(n)} + h_{-1\frac{1}{2}}x(n+1)$$

$$y\left(n + \frac{1}{2}\right) = h_{2\frac{1}{2}}x(n-2) + h_{1\frac{1}{2}}x(n-1) + \color{red}{h_{\frac{1}{2}}x(n)} + \color{red}{h_{-\frac{1}{2}}x(n+1)} + h_{-1\frac{1}{2}}x(n+2)$$

Edge DFE Architecture

- Edge Adaptation
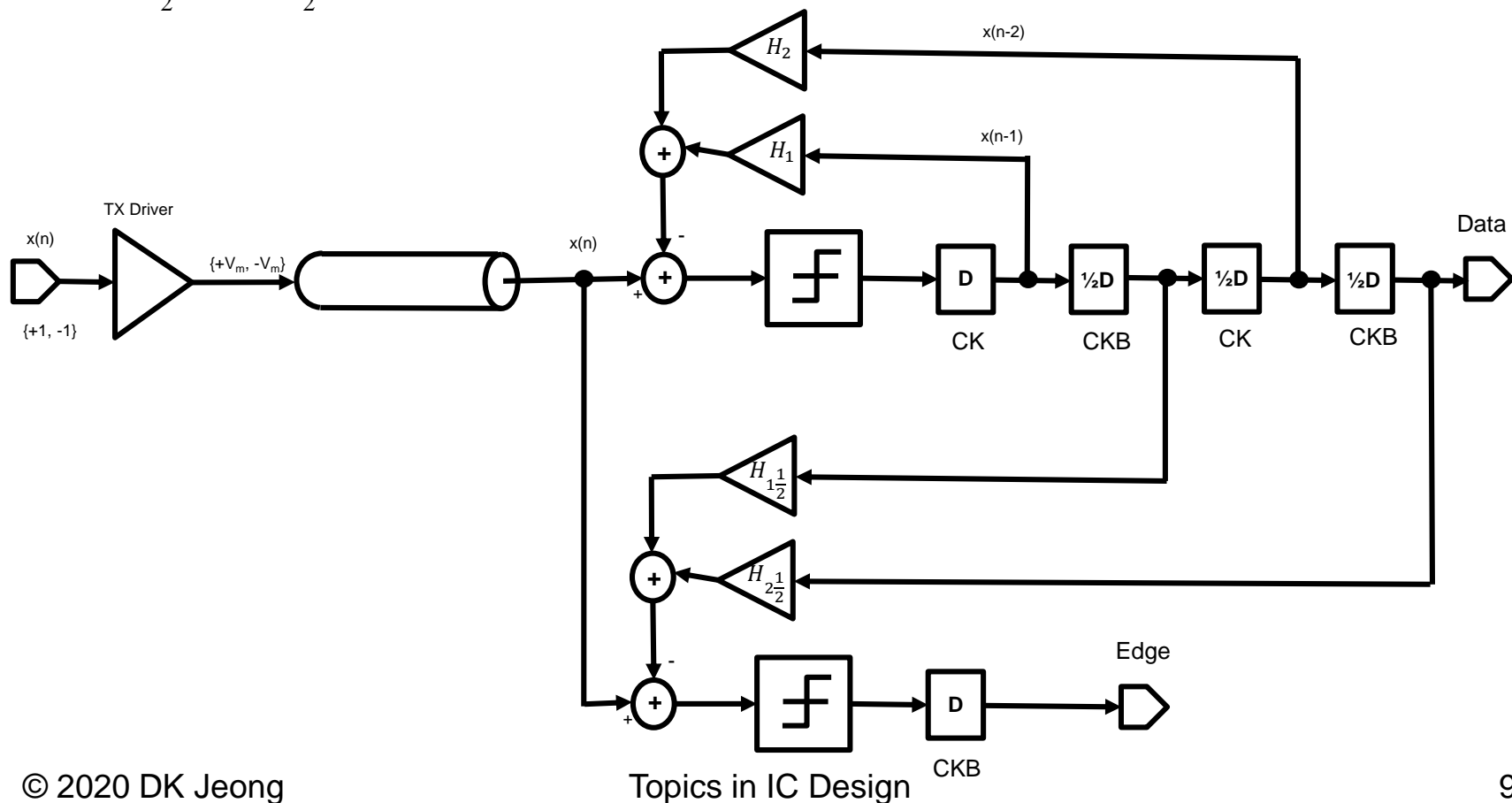
$$H_{k+\frac{1}{2}}' = H_{k+\frac{1}{2}} - \mu \cdot x(n-k) \cdot [x(n) - x(n-1)] \cdot \text{sign}[x(n + \frac{1}{2})]$$



References

- Sameh Abraham and Behzad Razavi, “A 20-Gbps Serial Link for High-Loss Channels” UCLA
- MAXIM, “Spectral Content of NRZ Test Patterns”
- Koon-Lun Jackie Wong, E-Hung Chen, and Chih-Kong Ken Yang, “Edge and Data Adaptive Equalization of Serial-Link Transceivers” IEEE, JSSC Sep. 2008
- Haechang Lee, “A 16 Gb/s/Link, 64 GB/s Bidirectional Asymmetric Memory Interface” IEEE, JSSC April 2009
- Massimo Pozzoni, “A Multi-Standard 1.5 to 10 Gb/s Latch-Based 3-Tap DFE Receiver With a SSC Tolerant CDR for Serial Backplane Communication” IEEE, JSSC Apr. 2009
- Srikanth Gondi and Behzad Razavi, “Equalization and Clock and Data Recovery Techniques for 10-Gb/s CMOS Serial-Link Receivers”, IEEE JSSC Sept. 2007
- Jian-Hao Lu “A 40Gb/s Low-Power Analog Equalizer in 0.13um CMOS Technology”, IEEE SOVC 2008
- A. Momtaz “An 80mW 40Gb/s 7-Tap T/2-Spaced FFE in 65nm CMOS”, IEEE ISSCC 2009