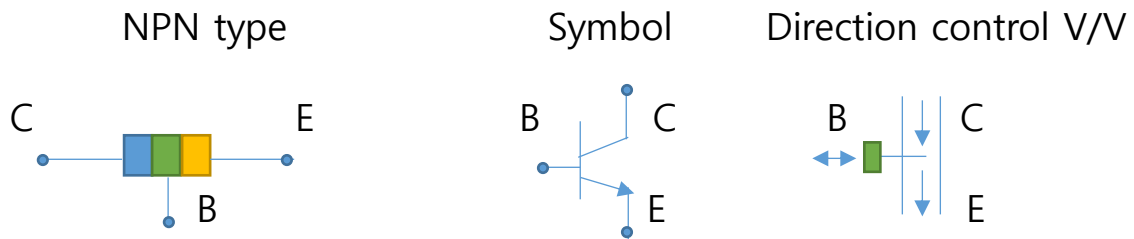


Lecture 10 - Transistor : 3 Legged device of semiconductor

: To give current amplification with voltage following

C(Collector), E(Emitter), B(Base)



Rules: (for NPN type)


1. $V_C > V_E$ (or $V_C - V_E \geq 0.2V$) for flowing
2. $V_B - V_E \approx 0.6V$ when flowing
3. $I_C = \beta I_B$ where $\beta \approx 100$, and $I_E = I_C + I_B = (\beta + 1)I_B \approx \beta I_B = I_C$

Application:


1. Current source or current supply

: To provide *constant current* into circuit, regardless of R_{LOAD}

(1) Big R

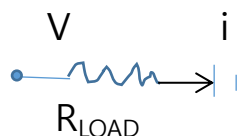


$$i = V/R_{LOAD}$$

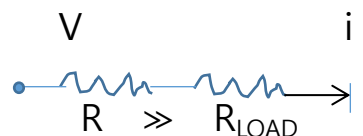

$$i = V/(R + R_{LOAD}) = V/R(1 + R_{LOAD}/R)$$

$$\approx V/R = \text{const} \therefore \text{Big } R (\gg R_{LOAD}) \text{ needed}$$

(2) Transistor Current Source

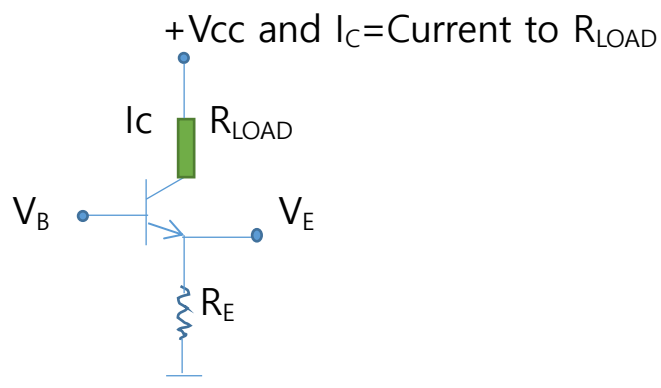

When $V_B \geq 0.6V$, $V_E = V_B - 0.6$ and


$$I_C = I_E = V_E / R_E = (V_B - 0.6) / R_E$$

Thus I_C is supplied to R_{LOAD} that is regardless of R_{LOAD}

\therefore Current Source or Current Supply

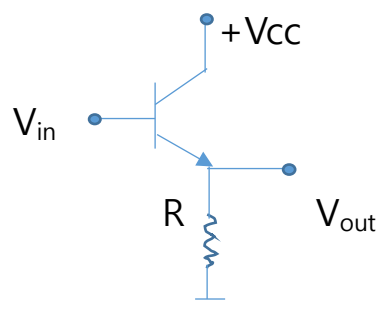2. Emitter Follower

: Current is amplified by β times while voltage is following



$V_{out} = V_E = V_{in} - 0.6 \quad \therefore \Delta V_{out} = \Delta V_{in}$; Replica of Input voltage,

where Gain = $\Delta V_{out} / \Delta V_{in} = 1$

And $I_E \approx I_C = \beta I_B$; Thus current is amplified while voltage is following.

\therefore Emitter Follower

Emitter follower is to be driven or to drive a device.

Thus input impedance, Z_{in} , is of interest at the V_{in} point.

Impedance is defined as the ratio of ΔV to ΔI at any point within circuit.

$$Z_{out} = Z_E = \Delta V_E / \Delta I_E = R$$

$$Z_{in} = Z_B \equiv \Delta V_B / \Delta I_B = \Delta V_E / (\Delta I_E / \beta) = \beta \Delta V_E / \Delta I_E = \beta R = \beta Z_{out}$$


As $Z_{out} \ll Z_{in}$, Emitter follower is a very nice device to drive or to be driven.

Note that very big or infinite Z_{in} is an ideal to be driven by any circuit.

Also very small or zero Z_{out} is an ideal to drive any circuit.

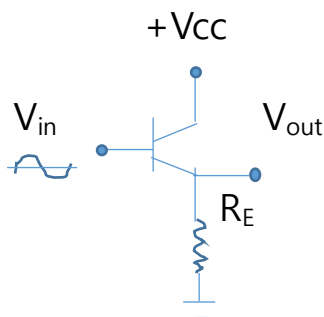3. AC coupled Emitter Follower

In the above Emitter Follower, TR is not active when $V_{in} < 0.6V$



How to cope with the AC voltage signal for V_{in} ? Answer is to use

1) Biasing :


To pull TR's quiescent voltage to midpoint between V_{cc} and GND

where the quiescent voltage is when no AC signal is applied.

Then the TR becomes active, and Emitter following is possible.

⇒ AC signal is to ride over the pulled TR's quiescent voltage(DC)

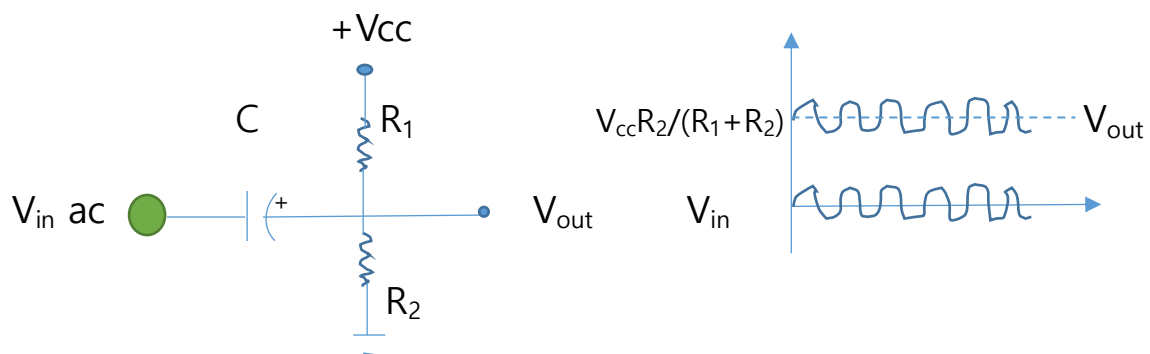A good method of biasing or DC offsetting is to add capacitor together with the voltage divider as follows;



Electrons from $V_{in\ ac}$ is getting into the charged capacitor, then overflown (or discharged) electrons are flowing to the voltage divider, riding over the DC offset voltage given by R_1, R_2 voltage divider.

Thus $V_{in\ ac}$ signal is adding to the DC voltage of $V_{CC}R_2/(R_1+R_2)$, then leads to V_{out}

Note the symbol + where + sign is higher voltage (or biased) direction.


Q: $V_{in\ ac}$ can have Impedance?

Yes. It can be a signal from a sensor that can have impedance Z_{in} , that is viewed from the sensor output.

Thus $Z_{in} \ll Z_{TOTAL}$ also should be checked.

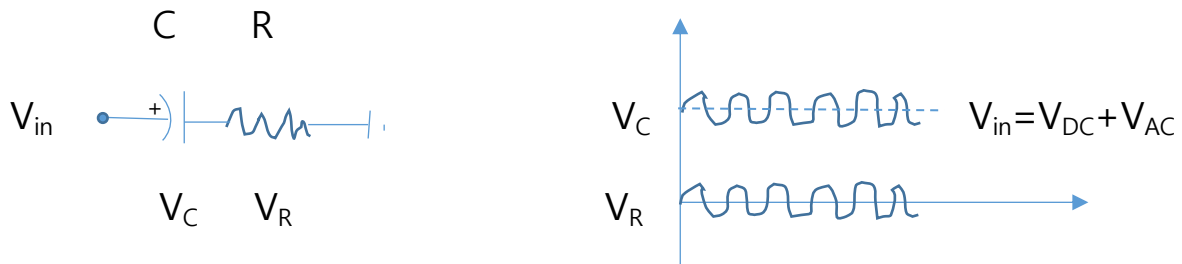2) DC Blocking

To remove the biased DC component from the signal by adding the blocking capacitor.



$$V_{in} = V_C + V_R \quad \text{and} \quad Z_C = 1/j\omega C, \quad Z_R = R$$

$$V_C = V_{in} Z_C / (Z_C + Z_R) = V_{in} / (1 + j\omega RC)$$

⇒ Low freq. part ($V_C = V_{DC}$ if $\omega = 0$)

$$V_R = V_{in} Z_R / (Z_C + Z_R) = V_{in} \{j\omega RC / (1 + j\omega RC)\}$$

⇒ High freq. part ($V_R = V_{in} - V_C = V_{AC}$, when $\omega = 0$)

∴ V_R is the AC voltage signal after the V_{DC} is removed.

(Q: What happens if the sequence of C, R is changed?)

This is a DC blocking capacitor or a kind of HPF with $\omega_{3dB} = 1/R_{eq}C$

where R_{eq} is the total equivalent resistor including *back and forth* resistors relevant to C.

Also note the symbol + for biased direction.


Ex) Design a AC coupled Emitter Follower that drives AC coupled load.

Design Spec:

$V_{CC}=+15V$, TR's $I_{quiescent}=0.5mA$, $R_{LOAD}=4.7K\Omega$, V_{in} is ac voltage signal from a sensor of $10K\Omega$ input impedance. Choose $f_{3dB}=100Hz$

(Source: Student Manual for The Art of Electronics, Thomas C. Hayes, Paul Horowitz, Cambridge University Press, 1989)

AC coupled Emitter Follower

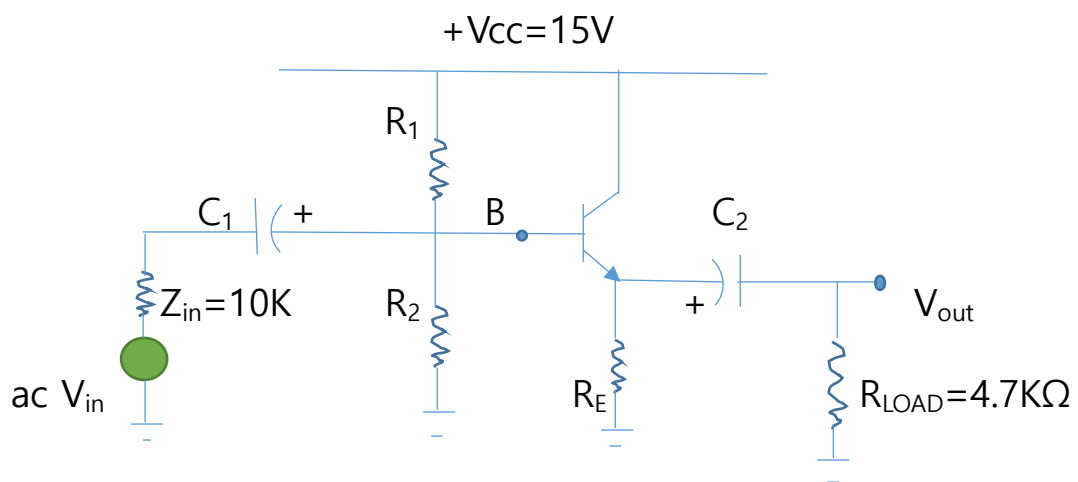

1) V_E centering in quiescence of TR

In quiescence, $V_E=15V/2=7.5V$ (chosen)

Thus $R_E=V_E/I_{quiescence}=7.5/0.5E-3=15K\Omega$

$V_B=7.5+0.6$ (Diode drop)= $8.1(V)$

(1) DC component

When quiescence, Voltage divider gives

$V_B=V_{CC}R_2/(R_1+R_2)$, thus $8.1/15=R_2/(R_1+R_2)$ eq(1)

When quiescence, the voltage divider should drive the circuit below B,

Thus $R_1 \parallel R_2 \ll Z_B$ and $Z_B=\beta(R_E \parallel \infty)=\beta R_E$

$$\therefore R_1 R_2 / (R_1 + R_2) = Z_B / 10 = 10(15) = 150 \text{K}\Omega \quad \text{eq(2)}$$

From eq(1),(2); $R_1 = 277 \text{K}\Omega$ and $R_2 = 325 \text{K}\Omega$

(2) AC component

For the ac signal, the DC component is added by the biasing circuit; and removed by the blocking capacitor, respectively. Thus we need a DC blocking capacitor (or a kind of HPF passing over 100Hz), to block the DC component, and the relevant $R_{eq} = R_E \parallel 0 + R_{LOAD} = 4.7 \text{K}$

This is a kind of Cascaded HPF, and ω_{3dB} adjustment is needed to prevent excessive attenuation near the ω_{3dB} frequency range. Thus ω_{3dB} can be adjusted such as $\omega_{13dB} = \omega_{3dB} = 100 \text{Hz}$ and $\omega_{23dB} = \omega_{3dB} / 3 = 33 \text{Hz}$

For the DC blocking capacitor, $\omega_{23dB} = (2\pi)(100/3) = 1/R_{eq}C_2$

$$\therefore C_2 = 1 / \{2\pi(33)(4700)\} \approx 1 \mu\text{F} \text{ from the commercial choice}$$

For the biasing circuit, $\omega_{13dB} = (2\pi)(100 \text{Hz}) = 1/R_{TOT}C_1$

where R_{TOT} is the total resistance relevant for C_1 .

$$R_{TOT} = 10 \text{K} + R_1 \parallel R_2 \parallel \beta(R_E \parallel R_{LOAD}) \text{ and } R_E \parallel R_{LOAD} = (15)(4.7) / (15 + 4.7) = 3.58 \text{K}\Omega$$

$$\text{As } R_1 \parallel R_2 = 150 \text{K}\Omega, \text{ thus } R_{TOT} = 10 \text{K} + (150)(3.58) / (150 + 3.58) = 115.7 \text{K}\Omega$$

$$\text{Thus } C_1 = 1 / \{(115.7)(2\pi)(100)\} \approx 0.02 \mu\text{F}$$

Quick check for $Z_{in} (=10 \text{K}\Omega) \ll Z_{emitter \text{ follower}} (=105.7 \text{K}\Omega)$ and it is OK!!

Thus design is completed for the AC coupled Emitter follower.

HW7) Design a AC coupled Emitter follower such that

$V_{CC}=+12V$, TR's $I_{quiescent}=0.5mA$, $R_{LOAD}=10K\Omega$, V_{in} is ac voltage signal from a sensor of $10K\Omega$ input impedance. Choose $f_{3dB}=100Hz$ and use alternative method for preventing excessive attenuation at ω_{3dB}