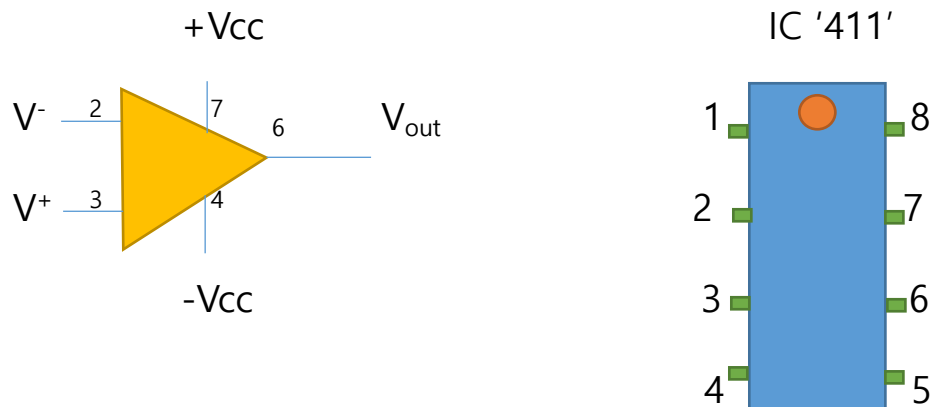


Lecture 12 : Operational Amplifier (OP Amp)

: Integrated Circuit that consists of TRs with feedback circuits

Symbol:




Rules for OP Amp

1. $Z_{in} = \infty$ (or $i^- \cong i^+ \cong 0$) and Z_{out} is very small ($\cong 0$)
2. In open loop (or no feedback)
 - If $V^+ > V^-$ then $V_{out} = +V_{CC}$
 - If $V^+ < V^-$ then $V_{out} = -V_{CC}$
3. In closed loop (or negative feedback or feedback to V^-)
 - Then $V^- \cong V^+$ is always attempted
4. $|V_{out}| \leq +V_{CC}$. Equality indicates OP Amp saturation (to be avoided)

Application

1. Analog Comparator

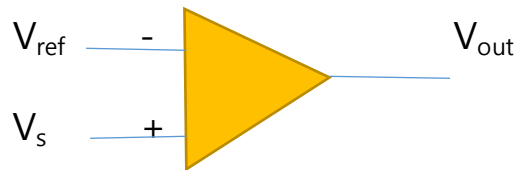

IF $V_s > V_{ref}$ THEN $V_{out} = V_{cc}$

IF $V_s < V_{ref}$ THEN $V_{out} = -V_{cc}$

This OP Amp can be used as an Analog Comparator

that can make comparison between the two analogue voltages


(Q: What happen if $V_s = V_{ref}$ in open loop? A: Never Happen!!)

EX) Logic Circuit, A/D Converter, etc

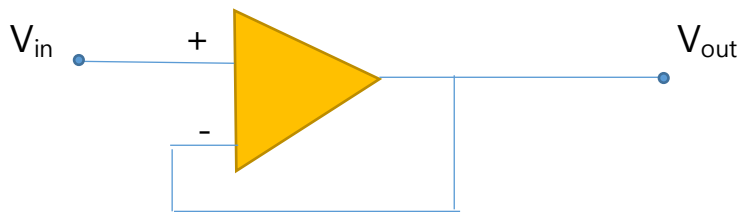2. Voltage Follower

:To follow the input voltage with Impedance "Refined"

For better performance in driving or being driven to/from the neighbouring circuit



$V_{in} = V^+ = V^- = V_{out}$ (\because closed loop with negative feedback)

$\therefore V_{out} = V_{in}$ $\therefore V_{out}$ follows V_{in} and $\text{Gain} = V_{out}/V_{in} = 1$

(Q: Why do we need this circuit ?)

Let's consider the input impedance, Z_{in} , and output impedance, Z_{out}

$Z_{in} = \infty$ = Impedance when viewing from Input (V_{in})

$Z_{out} \cong 0$ = Impedance when viewing from output (V_{out})

As $Z_{in} = \infty$, this circuit can be driven from any upstream circuit.

As $Z_{out} \cong 0$, this circuit can drive any following circuit.

($Z_{out} \ll Z_{in}$ for ideal condition for driving or being driven!!)

Therefore the voltage follower can be a good device to drive or to be driven in practical circuit design application, as Slave and Master!

Ex) For a circuit design to drive A




If there exists $Z_{UPSTREAM}$ of zero(0) Ω , A can be driven nicely.

But when there exists unknown $Z_{UPSTREAM}$ as in the fig, the condition of driving may not be satisfied if the $Z_{UPSTREAM}$ is big.

$Z_{UPSTREAM} \ll R_A$ should be satisfied for 10X rule. Thus the voltage follower is better to be located just before the A device, to refine the impedance.

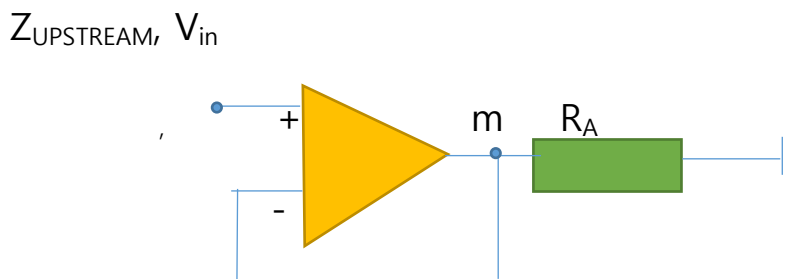Therefore the design can be modified as follows;



At V_{in} : $Z_{UPSTREAM} \ll Z_{in} (= \infty)$


At m; Z_{out} from Op amp $\cong 0 \ll R_A$

\therefore A can be driven nicely with the OP Amp voltage follower,

even under the uncertain $Z_{UPSTREAM}$

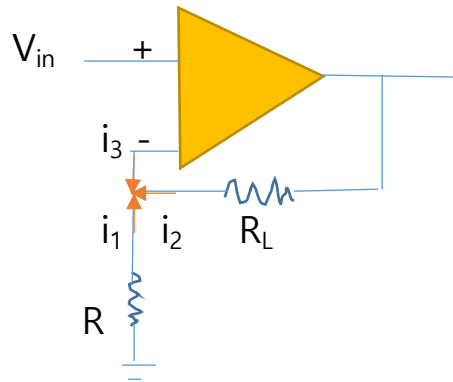3. Current Source or Current Supply

: To provide constant current supply or current source



At the Junction, $i_1 + i_2 + i_3 = 0$ from the Kirchhoff's law.

$$i_1 = (0 - V^-) / R = -V^- / R \quad (\because V^- = V^+ = V_{in} \text{ from closed loop})$$

$$i_2 = i_L = \text{current flow from } R_L$$

$$i_3 = -i^- \cong 0$$

$$\text{Thus } i_1 + i_2 + i_3 = (-V_{in} / R) + i_L + 0 = 0$$


$\therefore i_L = V_{in} / R$ indicates Constant Current to/from R_L , regardless of R_L

\therefore Current Source or Current Supply

This current supply can give wider range of voltage when compared to the TR's version, where $I_E = (V_{in} - 0.6) / R_E$ and $V_{in} \geq 0.6$ are assumed.

4. Inverting Amplifier

: To amplify the inverted voltage

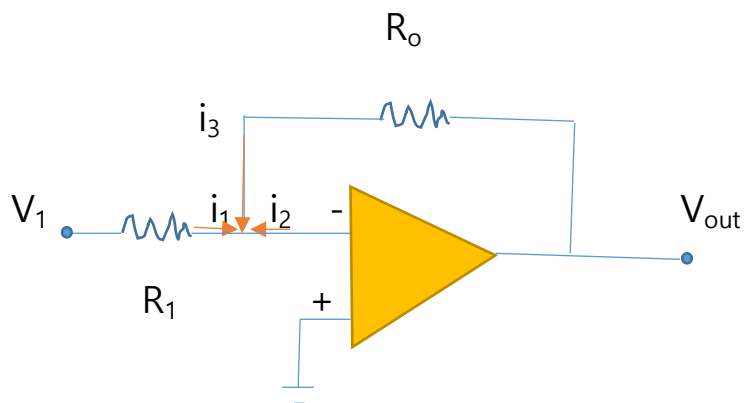

At the junction, $i_1 + i_2 + i_3 = 0$

$$i_1 = (V_1 - V^-) / R_1 = (V_1 - V^+) / R_1 = V_1 / R$$

$$i_2 = 0$$

$$i_3 = (V_{out} - V^-) / R_o = V_{out} / R_o$$

$$\text{Thus } V_1 / R_1 + V_{out} / R_o = 0$$

$$\therefore V_{out} = (-R_o / R_1) V_1$$

\therefore This is inverting amplifier, and Gain = $-R_o / R_1$


If $R_o > R_1$ then $|\text{Gain}| > 1$ (Amplification)

If $R_o < R_1$ then $|\text{Gain}| < 1$ (Attenuation)

If $R_o = R_1$ then Gain = -1 (Inverter or only Sign-change)

5. Summing amplifier

: To sum of voltages amplified

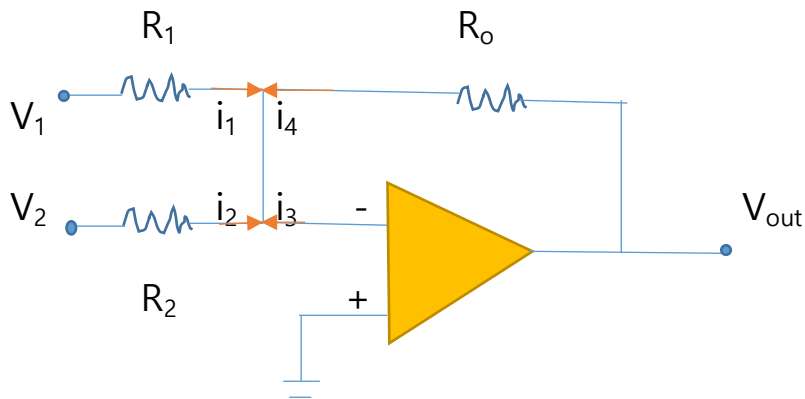

At the junction, $i_1 + i_2 + i_3 + i_4 = 0$

$$i_1 = (V_1 - V^-) / R_1 = V_1 / R_1; \quad i_2 = (V_2 - V^-) / R_2 = V_2 / R_2$$

$$i_3 = 0; \quad i_4 = (V_{out} - V^-) / R_0 = V_{out} / R_0$$

$$\therefore i_1 + i_2 + i_3 + i_4 = V_1 / R_1 + V_2 / R_2 + V_{out} / R_0 = 0$$

$$\text{Thus } V_{out} = -(R_0 / R_1) V_1 - (R_0 / R_2) V_2 = -\{(R_0 / R_1) V_1 + (R_0 / R_2) V_2\}$$

\therefore Sum of Voltages amplified

If $R_1 = R_2 = R_0 = R$ then $V_{out} = -V_1 - V_2 = -(V_1 + V_2)$: Adder

and $V_1 = V_s$, $V_2 = \text{DC_offset}$, then $V_{out} = -(V_s + \text{DC_offset})$: DC biasing

If $R_1 = R_2 = 2R$, $R_0 = R$ then $V_{out} = -(V_1 + V_2) / 2$: Average

If $R_1 = 3R$, $R_2 = 3R/2$, $R_0 = R$ then $V_{out} = -(V_1 + 2V_2) / 3$: Weighing Average


If $R_1 = R/a$, $R_2 = R/b$, $R_0 = R$ then $V_{out} = -(aV_1 + bV_2)$: Linear combination

If this circuit is extended to n inputs such as V_n voltage with R_n resistor

$$\text{Then } V_{out} = -\sum (R_0 / R_n) V_n$$

6. Non-inverting Amplifier

: To amplify non-inverted voltage

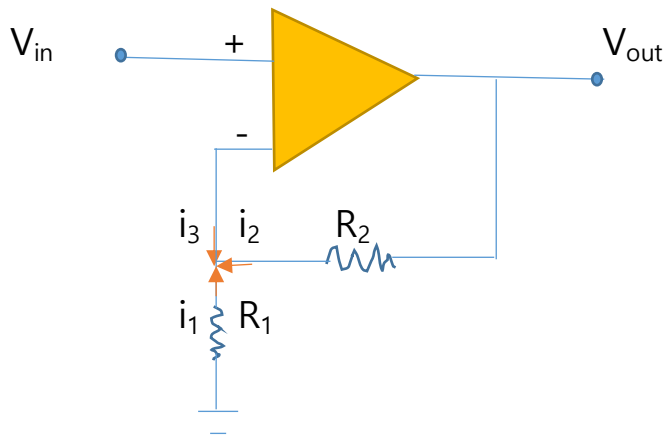

At the Junction, $i_1 + i_2 + i_3 = 0$

$$i_1 = (0 - V^-) / R_1 = -V_{in} / R_1$$

$$i_2 = (V_{out} - V^-) / R_2 = (V_{out} - V_{in}) / R_2$$

$$i_3 = 0$$

$$i_1 + i_2 + i_3 = 0 = -V_{in} / R_1 + (V_{out} - V_{in}) / R_2$$


$$\therefore V_{out} = (1 + R_2 / R_1) V_{in}$$

This is Non-inverting amplifier, Gain = $1 + R_2 / R_1 > 1$

Thus the sign is not changed and amplification only

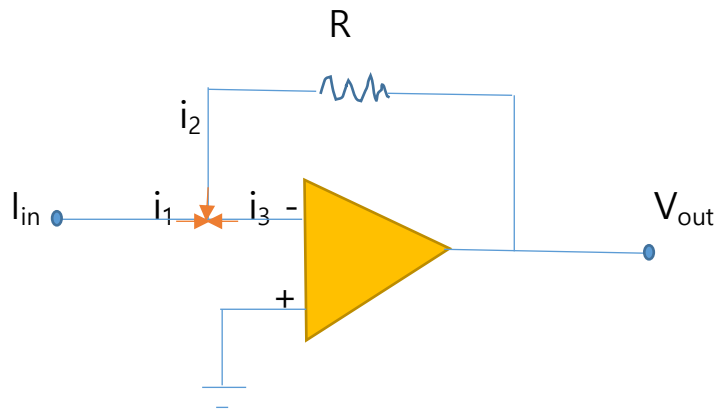7. Current to Voltage Converter (C/V converter)

: To convert current to voltage with the refined Z_{in} and Z_{out}



At the junction, $i_1 + i_2 + i_3 = 0$

$$i_1 = I_{in}, \quad i_2 = (V_{out} - 0)/R = V_{out}/R, \quad i_3 = 0$$

$$\text{Thus } I_{in} + V_{out}/R = 0$$

$\therefore V_{out} = -I_{in}R$ and this is the current to voltage converter


It is of interest to know the input impedance (Z_{in}), and output impedance (Z_{out}).

Input Impedance, $Z_{in} \approx \infty$ ($\because Z_{in} \approx Z^- \approx \infty$)

Output Impedance, $Z_{out} \approx 0$

$\therefore Z_{out} \ll Z_{in}$ can be achieved and thus it is a good device!

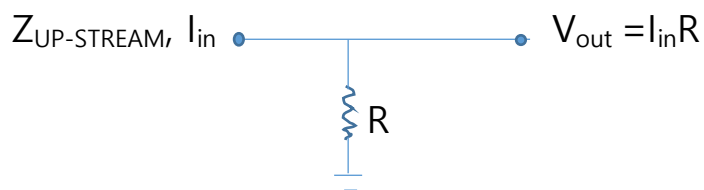For comparison, a simple C/V (current to voltage) converter is



$$Z_{in} = R, Z_{out} = Z_{up-stream} \parallel R$$

Q) $Z_{out} \ll Z_{in}$ can be achieved? Yes or No

Comparison is as follows;

\Rightarrow Simple C/V can be nicely driven only when $Z_{UP-STREAM} \ll Z_{in} (=R)$


while OP Amp C/V can be driven by any up-stream circuit ($\because Z_{in} \doteq \infty$)

\Rightarrow Simple C/V can nicely drive only when $Z_{out} \ll Z_{LOAD}$

while OP Amp C/V can drive any down-stream circuit ($\because Z_{out} \doteq 0$)

\therefore OP Amp C/V shows better performance with the "refined" impedance

8. Differential Amplifier

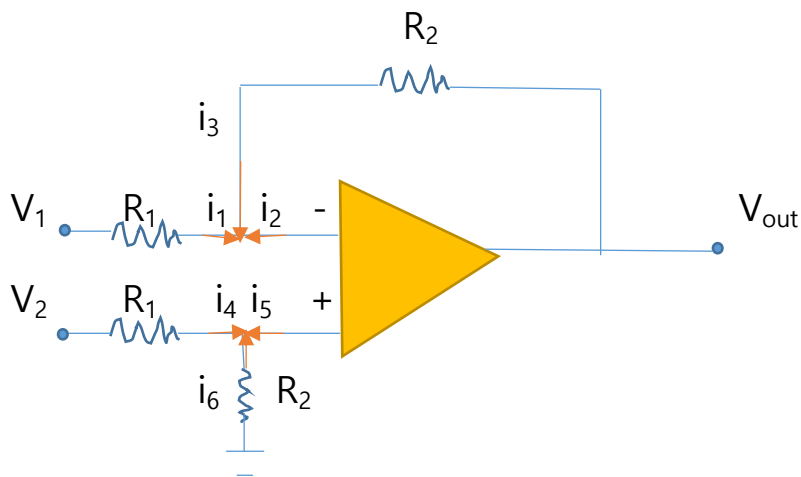

At Lower Junction: $i_4 + i_5 + i_6 = 0$

$$i_4 = (V_2 - V^+)/R_1 ; i_5 = 0 ; i_6 = (0 - V^+)/R_2 = -V^+/R_2$$

$$i_4 + i_5 + i_6 = (V_2 - V^+)/R_1 - V^+/R_2 = 0 \therefore V^+ = R_2 V_2 / (R_1 + R_2)$$

At Upper Junction: $i_1 + i_2 + i_3 = 0$

$$i_1 = (V_1 - V^-)/R_1 ; i_2 = 0 ; i_3 = (V_{out} - V^-)/R_2$$

$$i_1 + i_2 + i_3 = (V_1 - V^-)/R_1 + (V_{out} - V^-)/R_2 = 0 \text{ and } V^- = V^+$$

$$\therefore V_{out} = -R_2 V_1 / R_1 + (1 + R_2 / R_1) V^- = (V_2 - V_1) R_2 / R_1$$

\therefore Differential Amplifier with Gain = R_2 / R_1

This is to amplify the voltage difference $V_2 - V_1$

Ex) $V_2 = \text{Signal} + \text{DC_offset}$, $V_1 = \text{DC_offset}$

Then $V_2 - V_1 = \text{Signal}$, and it can be amplified with R_2 / R_1 gain.