

## Lecture Note2: Electrical Components-Resistor

### 1. Resistor

:About 70% of widely used components

:To restrict/regulate/control the current


:To drop the voltage

:To divide voltage

:To dissipate energy

:To work

Symbol

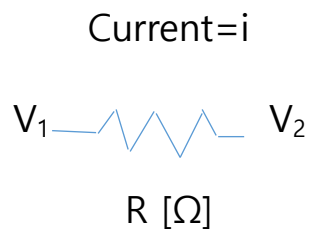

<Ohm's Law>

$i=(V_1-V_2)/R$ =current through resistor

$R$ =Resistance[ $\Omega$ ]=1/conductance


where conductance=current when 1V is applied across two points

The Ohm's law is only applicable to elements behaving like resistors,

NA to Diode, Transistor, etc.

<Resistivity>

Voltage  $V$ , Current  $I$

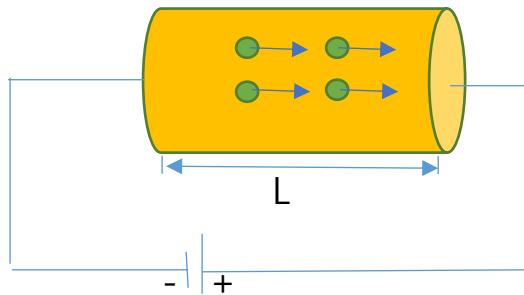

Resistance,  $R \equiv V/I = \rho L/A$ ,

where  $\rho$  = Resistivity [ $\Omega\text{m}$ ] and  $\sigma = 1/\rho$  = conductivity [ $1/\Omega\text{m}$ ]

Resistivity,  $\rho$ , for various material

<Conductor>

$10\text{E-}8$  for Fe

$2.82\text{E-}8$  for Al

$1.72\text{E-}8$  for Cu

$1.59\text{E-}8$  for Ag

<Semiconductor>

0.46 for Ge

64 for Si

<Insulator>

$1.0\text{E}10 \sim 1.0\text{E}14$  for Glass


$5.0\text{E}5$  for Human skin

2.5E5 for water

0.2E5 for salt water

## Serial and Parallel Connections for Resistors

### 1) Serial connection

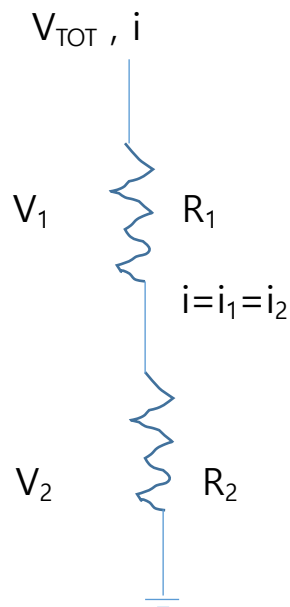

Conductance=Current when 1V applied

$$= 1/(R_1 + R_2) = 1/R_{TOT}$$

$$\text{Thus } R_{TOT} = R_1 + R_2$$

From Kirchhoff's law,

$$i_1 = i_2 = i$$

$$V_{TOT} = V_1 + V_2 = iR_1 + iR_2 = i(R_1 + R_2) = iR_{TOT}$$

$$\text{Thus } R_{TOT} = R_1 + R_2 = R_1(1 + R_2/R_1)$$

$$\text{If } R_1 = R_2 = R, \text{ then } R_{TOT} = 2R$$


$$\text{If } R_1 = 10R, R_2 = R, \text{ then } R_{TOT} = 1.1R_1 = 11R$$

$$\text{If } R_1 \gg R_2, \text{ then } R_{TOT} \approx R_1 (\because R_2/R_1 \ll 1)$$

Thus R<sub>1</sub> (Larger resistor) dominates circuit in serial connection !

It indicates that R<sub>1</sub>=Master, R<sub>2</sub>=Slave

## 2) Parallel connection

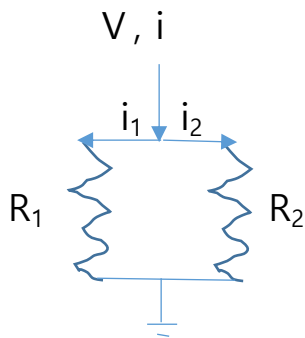

Kirchhoff's law,

$$i = i_1 + i_2 = V/R_1 + V/R_2 = V/R_{TOT}$$

$$1/R_{TOT} = 1/R_1 + 1/R_2, \text{ thus } R_{TOT} = R_1 R_2 / (R_1 + R_2) = R_2 / (1 + R_2/R_1)$$

Also from Total Conductance

$$= \text{Conductance}_1 + \text{Conductance}_2$$

$$= 1/R_1 + 1/R_2 = 1/R_{TOT}$$

$$\text{Thus } 1/R_{TOT} = 1/R_1 + 1/R_2 \text{ and } R_{TOT} = R_1 R_2 / (R_1 + R_2)$$

$$\text{If } R_1 = R_2 = R, \text{ then } R_{TOT} = R/2$$

$$\text{If } R_1 = 10R, R_2 = R, \text{ then } R_{TOT} = 10R^2 / 11R = R/1.1 \approx 0.909R$$

$$\text{If } R_1 \gg R_2, \text{ then } R_{TOT} = R_1 R_2 / (R_1 + R_2) = R_2 / (1 + R_2/R_1) \approx R_2 \text{ (} \because R_2/R_1 \ll 1 \text{)}$$

Thus  $R_2$  (Smaller resistor) dominates circuit in parallel connection!

$R_1$  = Slave,  $R_2$  = Master

It gives us very good understanding and insight for the circuits.


"Master and Slave" for Circuit Design

Also it leads to the "10X Rule for Circuit Design"
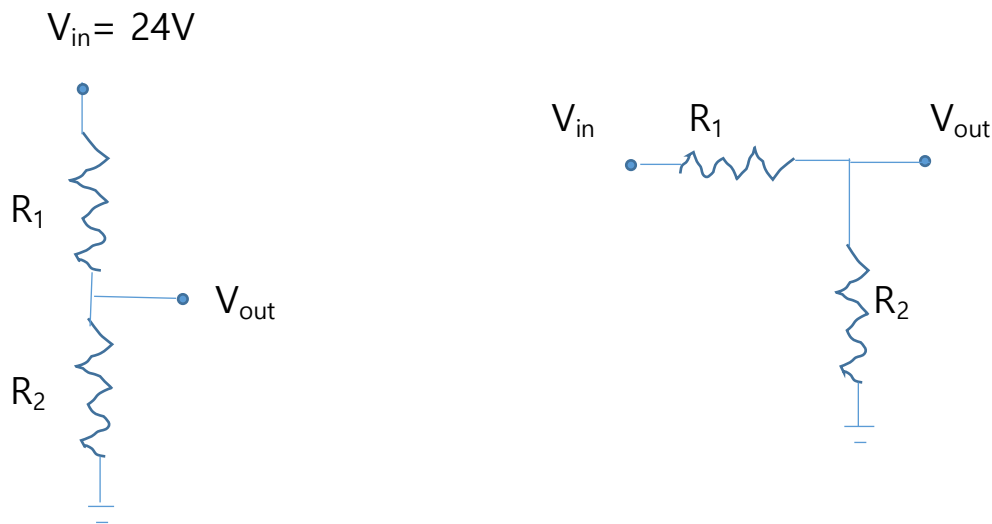
## Voltage Divider

:To divide/drop the voltage into appropriate range

Ex) How can we get 12V from 24V voltage supply of car-battery?



From Ohm's law, the current  $i$  flowing from top to bottom,

$$i = V_{in} / (R_1 + R_2)$$

$$\therefore V_{out} = iR_2 = R_2 V_{in} / (R_1 + R_2) \text{ or } V_{out} / V_{in} = R_2 / (R_1 + R_2) = 1 / (1 + R_1 / R_2)$$


$$\therefore V_{out} = 12V \text{ when } R_1 = R_2 = R \text{ (=10K, for example)}$$

Thus,  $V_{out} / V_{in}$  can be adjusted by changing  $R_1$ ,  $R_2$  resistors.

There are lots of application for this.

(Q: There can be many potential  $R_1$ ,  $R_2$  combinations. Is there existing optimum one? How can we get them then? Any assumption is needed for this? Etc.)

## Generalized Voltage Divider

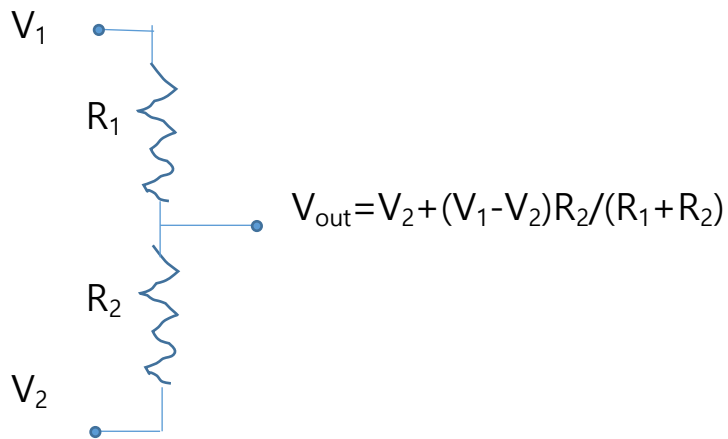

This general voltage divider becomes simple version of previous page if  $V_2=0$ , and it gives better understanding and meaningful insight.

Also, it is possible to set  $V_2$  as the negative voltage, such as  $-5V$ .

Q) How can we get  $-5V$ ?

HW1) Derive  $V_{out}$  in the above generalized voltage divider

(due in next week)