


Lecture 3 - Thevenin equivalent circuit

: To simplify complex circuit of Resistors and Voltage sources into simple serial circuit of V_{th} (Thevenin voltage) and R_{th} (Thevenin resistance).

: Any two terminal network of resistors and voltage sources is equivalent to a single voltage source V_{th} in series with a single resistor R_{th}

This method is called as Thevenin's method for "Circuit Fragmentation"

<Thevenin's Equivalent Circuit>

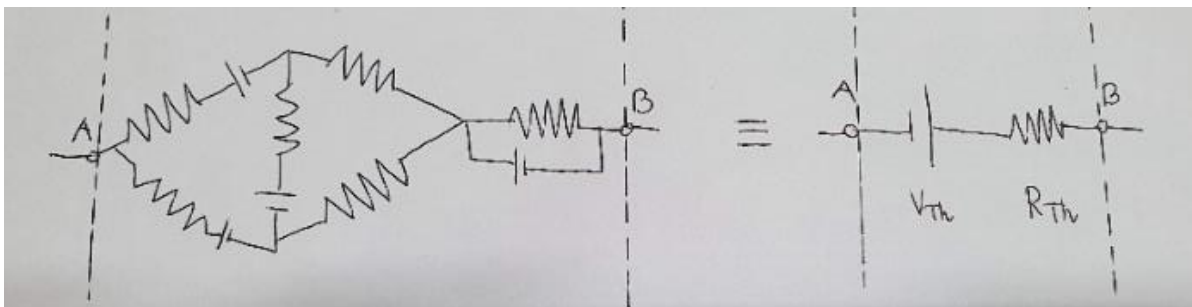

Networks of Resistors and Voltages \equiv $V_{th} + R_{th}$ (in series)


Circuit Simplification/Fragmentation by Thevenin's equivalent circuit,
 V_{th} =Thevenin voltage, or

Open circuit voltage at B when nothing is attached to B, or

Voltage measured/calculated at B when $R_{in B} = \infty$

$R_{th} \equiv V_{th} / I_{sc}$ and $I_{sc} = I_{short-circuit}$ = Current flowing from the circuit to ground when B is shorted, or connected to ground, or saturation current.

For the voltage divider,

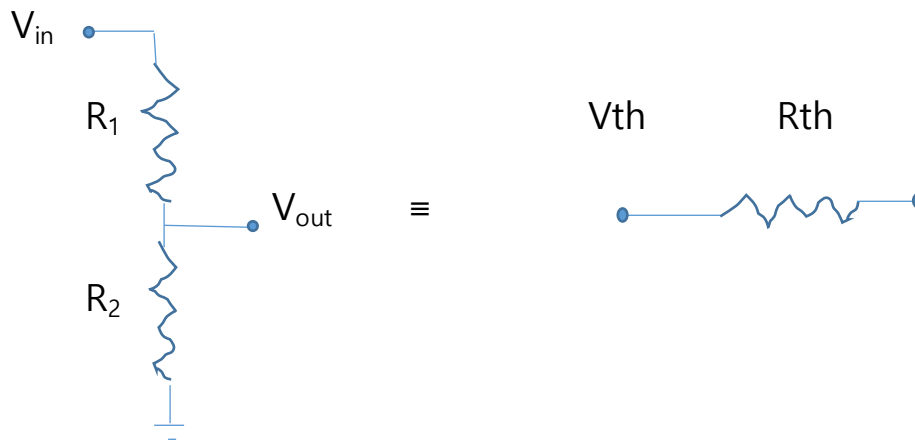

V_{th} = Open voltage at $V_{out} = V_{in} R_2 / (R_1 + R_2)$

I_{sc} = Current flowing when V_{out} is shorted = V_{in} / R_1 (why?)


Thus $R_{th} \equiv V_{th} / I_{sc} = R_1 R_2 / (R_1 + R_2) = 1 / (1/R_1 + 1/R_2) = R_1 \parallel R_2$

= Parallel resistance of resistors viewed from V_{out}

This is a great knowledge, and there are so many applications!

Ex) Multiple voltage divider

V_{out} ?

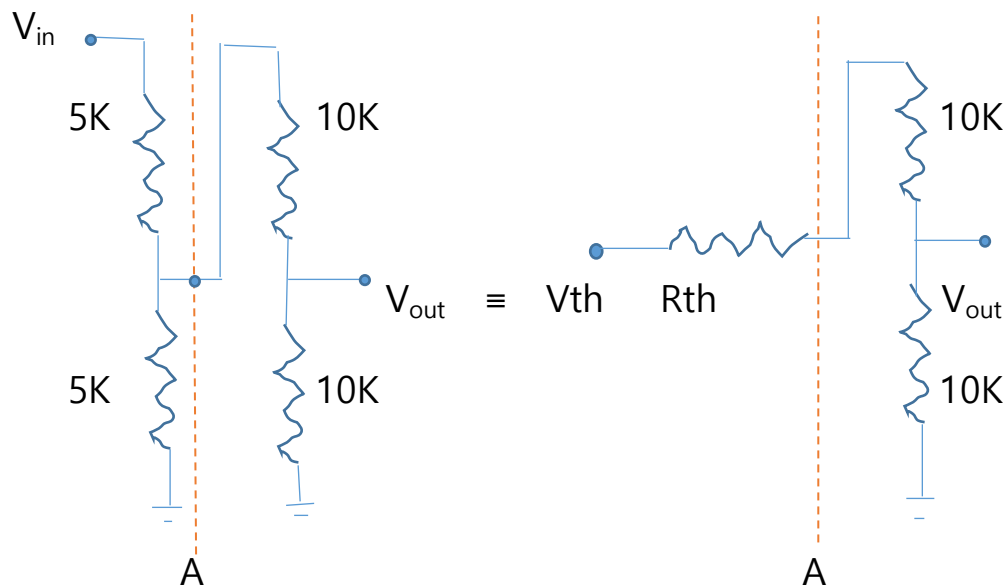

$$V_{th} = V_{in}(5K)/(5K+5K) = V_{in}/2, \quad R_{th} = 5K \parallel 5K = 2.5K$$


$$\therefore V_{out} = V_{th}(10K)/(2.5K+10K+10K) = 10V_{th}/22.5 = 5V_{in}/22.5 = 0.222V_{in}$$

This example demonstrates the strength of fragmented circuit using the Thevenin method!


It might be very difficult to solve without the Thevenin method.

HW2)

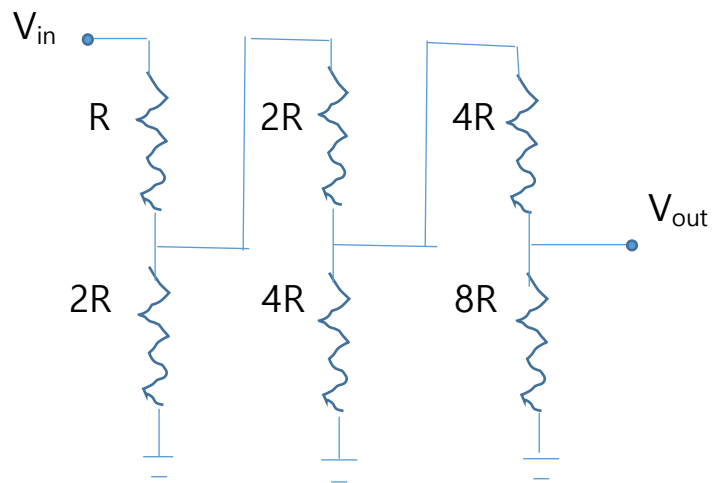Given the multiple voltage divider, derive V_{out} as the function of V_{in} and R . Also calculate V_{out} when $V_{in}=10V$, and $R=5K\Omega$



Revisit to Generalized Voltage Divider

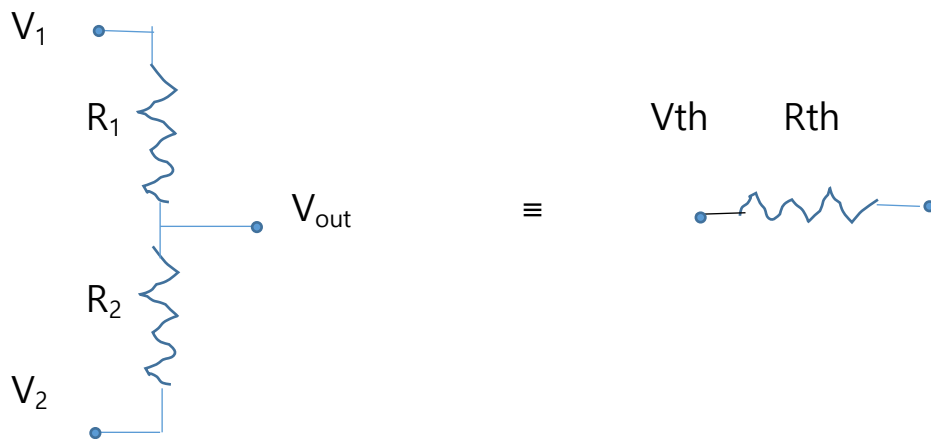

V_{th} is the open circuit voltage, and it is the same as V_{out}

I_{SC} = Saturation Current = Current when V_{out} is ground.

Thus $I_{SC} = V_1/R_1 + V_2/R_2$

R_{th}

$= R_1 \parallel R_2 = R_1 R_2 / (R_1 + R_2)$

And,

$V_{out} = V_{th} = R_{th} * I_{SC} = (R_2 V_1 + R_1 V_2) / (R_1 + R_2)$

$= V_2 + (V_1 - V_2) R_2 / (R_1 + R_2)$

\therefore Thevenin method gives simplification and insight.