

## Lecture 4 – Design Rule or 10X rule


### Design Rule or 10X Rule

When Device A is to drive Device B, this case can be that A is the 'Slave', B is the 'Master', because the ultimate target is to drive B, Master.

Thus Device B must have MAJOR allocation of voltage, while device A has MINOR allocation of voltage for the given voltage signal,  $V_s$ .

It can be generally accepted that 90% of  $V_s$  is allocated to  $V_B$ , while 10% of  $V_s$  is allocated to  $V_A$ .

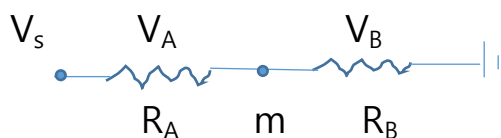This situation can be implemented as  $R_A:R_B=1:10$ , where  $R_A$  and  $R_B$  are resistors of device A and device B, respectively.



When  $R_A/R_B=1/10$ , from Ohm's law

$$V_B = V_s R_B / (R_A + R_B) = V_s / (1 + R_A/R_B) = 0.909V_s, \quad V_A = V_s - V_B = 0.091V_s$$

$\therefore$  90.9% of  $V_s$  is allocated to  $V_B$ , while 9.1% of  $V_s$  is allocated to  $V_A$

Thus  $R_A:R_B=1:10$  or  $R_A=R_B/10$  is a practical guideline for the situation "A drives B"

This is called as '10X rule', and very useful for practical circuit design

Sometimes  $R_A$  and  $R_B$  are expressed as  $R_{out,A}$  and  $R_{in,B}$

where  $R_{out,A}$  is the resistor out of A that viewed at midpoint, m

$R_{in,B}$  is the resistor into B that viewed at the mid-point, m

Thus  $R_{out,A} \leq R_{in,B} / 10$  is the '10X rule' in more general form.

In more general expression

$$Z_{out,A} \leq Z_{in,B} / 10 \quad \text{for more general AC environment}$$


where impedance Z is used instead of R

Two Exceptions for the 10X rule

1.  $Z_{out} = Z_{in}$  for "Impedance matching" in radio frequency application
2.  $Z_{out} / 10 \geq Z_{in}$  for current signal rather than voltage signal ("reverse situation"), and  $Z_{out} = \infty$  for current source
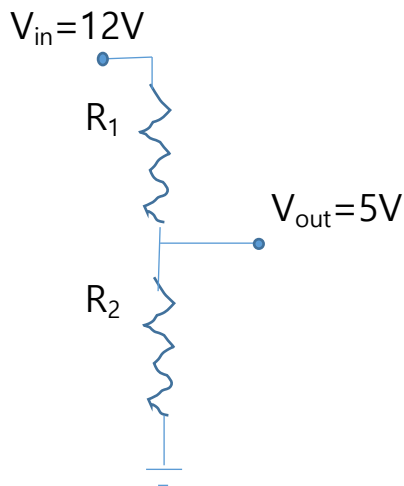
## Voltage Divider Design

Design a voltage divider:  $V_{in}=12V$ ,  $V_{out}=5V$



$$V_{out}/V_{in}=R_2/(R_1+R_2)=5/12 \quad \text{eq(1)}$$

-Two unknowns  $R_1, R_2$  with eq(1)

-Too many  $R_1, R_2$  solutions

$\therefore$  One more eq is needed to solve

Thus, from design point of view, we need 'For what application?'

Answer can be 'To drive a A/D converter from the  $V_{out}$  signal'

Now we need to know the load resistor,  $R_L$ , of the A/D converter,


and we can obtain the  $R_L$  data from;

-Input impedance of A/D (Analog to Digital) converter

from specification sheet, or

-Direct measurement of resistor the A/D converter with multi-meter

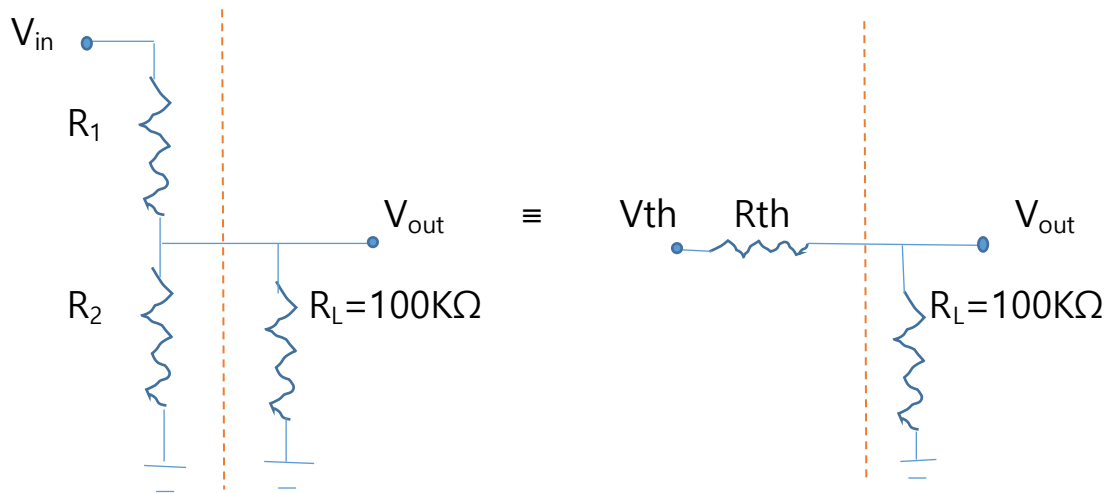Typical A/D's loading resistor,  $R_L$ , is  $100K\Omega$ , and it can be connected to the  $V_{out}$  signal as follows.



Thevenin's equivalent circuit gives

$$R_{th} = R_1 \parallel R_2 = R_1 R_2 / (R_1 + R_2), \text{ and}$$

$$V_{th} = \text{open voltage} = V_{in} R_2 / (R_1 + R_2)$$

$R_{th}$  is to drive  $R_L$ , thus from 10X rule

$$R_{th} = R_1 R_2 / (R_1 + R_2) = R_L / 10 = 10K\Omega \quad \text{eq(2)}$$

Thus two unknowns,  $R_1$ ,  $R_2$  can be solved from two eqs(1) and (2)

$$5R_1 / 12 = 10K\Omega \text{ Thus } R_1 = 24K\Omega, \text{ and } R_2 = 5R_1 / 7 = 17.1K\Omega$$

Therefore  $R_1 = \underline{24K\Omega}$ ,  $R_2 = \underline{17.1K\Omega}$  are uniquely determined.

Now  $V_{out} = V_{th} R_L / (R_{th} + R_L) = V_{th}(100) / (10 + 100) \approx 4.5V$ , while the design target is 5V.

Is it acceptable? Ans) Yes or No.

It can be generally accepted as an approximate solution, when  $R_L$  is sufficiently large.

What happen?

This time  $V_{out}$  is connected to  $R_L (=100K\Omega)$  instead of open voltage (no-connection, and  $R_L = \infty$ ). The current flow,  $i_L$  into  $R_L$ , gives voltage drop at  $V_{out}$  by the amount of  $i_L R_{th}$  from  $V_{th}$ .

The smaller  $R_L$  gives the bigger voltage drop at  $V_{out}$ .

Here is an exact solution that keeps  $V_{out}$  as the design target, 5V.

Eq(1) should be modified as

$$V_{out} = V_{th} R_L / (R_{th} + R_L) = 5V \quad \text{eq(1')}, \text{ where}$$

$$V_{th} = V_{in} R_2 / (R_1 + R_2) \quad \text{eq(3)}$$

Three unknowns,  $R_1, R_2, V_{th}$ ; with eq(2), eq(1'), eq(3)

$$\text{From eq(1'), eq(2); } V_{out} = V_{th} R_L / 1.1 R_L = V_{th} / 1.1 = 5V, \therefore V_{th} = 5.5V$$

$$\text{From eq(3), } R_2 / (R_1 + R_2) = V_{th} / V_{in} = 5.5 / 12$$

$$\text{Applying to eq(2); } R_{th} = 5.5 R_1 / 12 = 10K\Omega \therefore R_1 = \underline{21.8K\Omega}$$

$$\text{From eq(3), } 5.5(R_1 + R_2) = 12 R_2 \therefore R_2 = 5.5 R_1 / 6.5 = \underline{18.4K\Omega}$$

Thus we observe  $R_1, R_2$  are adjusted to accommodate  $R_L$



Q) What happen if AC voltage is used instead of DC voltage?

Ans) Same? or Different? It is same.

Note: Ohm's law is not influenced by whether it is DC or AC.
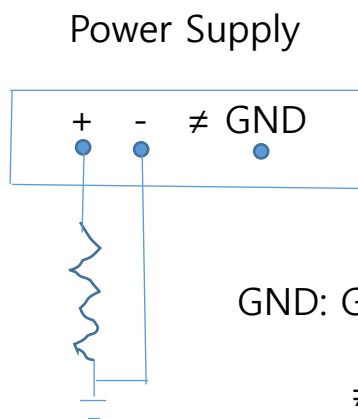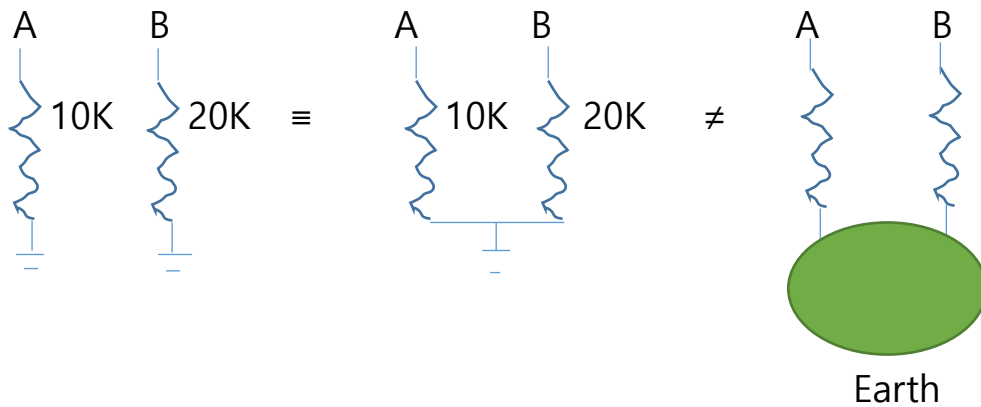
## Local ground vs Global ground (or Earth)

Local ground or signal ground: common points in the circuit arbitrary chosen as zero volts



GND: Global ground or Chasis ground

≠ Local ground(-)

-Due to static electricity

or Chasis' voltage

-Better to be connected to the Earth line