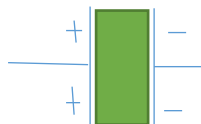


Lecture 5-Capacitors

:Conductor plates with insulator (vacuum, dielectric material such as ceramic, plastic, metal oxide) to give greater capacitance (or storage capacity) per unit area. (Mechanical analogy =Tank, Accumulator)



d, A

Capacitance $C = \epsilon A/d$ [Farad] or [F]


where $\epsilon =$ permittivity [F/m]

Application: Filtering or Conditioning, Smoothing, DC blocking, etc

Laws for Capacitor

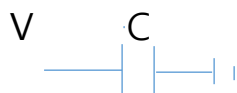
1. Static description

Charge $Q = CV$ [Coloumb], or $V = Q/C = \int i dt / C$ and $i =$ current



Serial connection:

$V_T \quad V_1 \quad V_2$

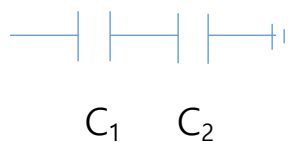


$V_T = V_1 + V_2 = Q_1/C_1 + Q_2/C_2 = Q/C_T$ ($Q_1 = Q_2 = Q$ why?)

Thus $1/C_T = 1/C_1 + 1/C_2$, and $C_T = C_1 C_2 / (C_1 + C_2) = C_2 / (1 + C_2/C_1)$

$= C/2$ (if $C_1 = C_2 = C$)

$\approx C_2$ (if $C_1 \gg C_2$) \therefore Smaller capacitor dominates

Parallel connection

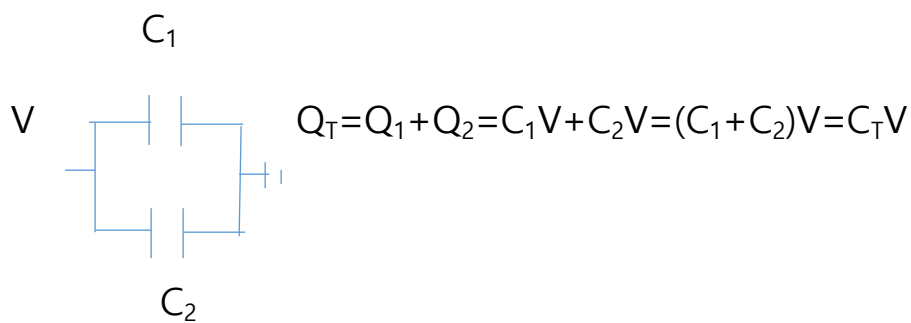

Thus $C_T = C_1 + C_2 = C_1(1 + C_2/C_1) = 2C$ (if $C_1 = C_2 = C$)

$\approx C_1$ (if $C_1 \gg C_2$)



\therefore Larger capacitor dominates

2. Dynamic description

:Differentiation of static description w.r.t. time. That is,


$$dQ/dt = i = CdV/dt$$

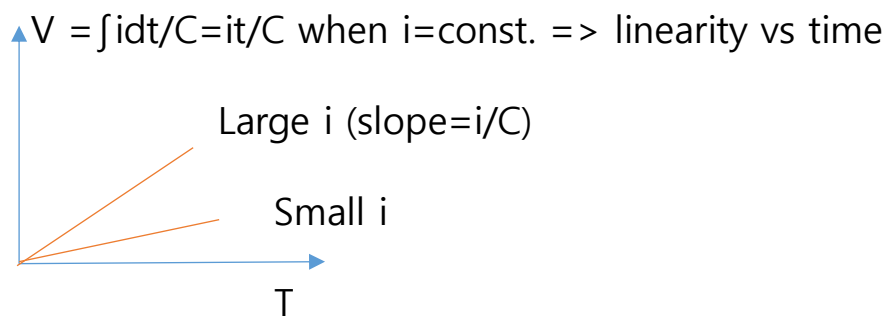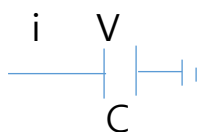\therefore Current $\propto dV/dt$ where $V =$ voltage across capacitor




Thus bigger current gives faster voltage change.

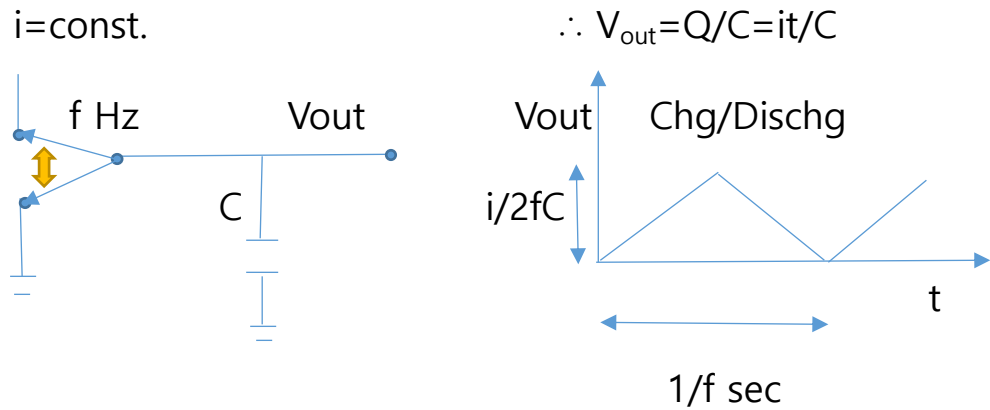Application 1 (Constant current input): Ramp generator




Application 2 (Constant voltage input)

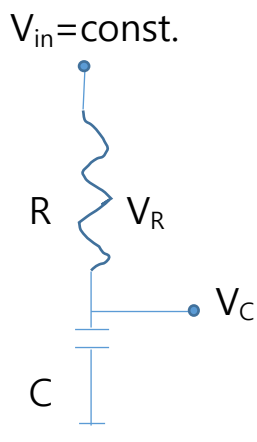

$V_{in} = V_R + V_C = iR + \int i dt / C$, assuming very little current flows into V_C

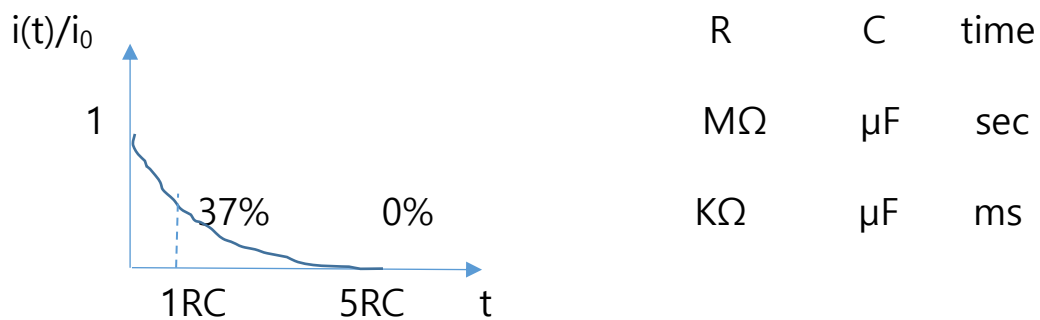
$RC di/dt + i = 0 \therefore i(t) = i_0 \exp(-t/RC)$ and $i_0 = V_{in}/R$



\therefore After $5RC$ time, no current flows $\rightarrow Z_C \equiv \text{Impedance of capacitor} = \infty$

$$V_C = \int i dt / C = V_{in}(1 - \exp(-t/RC)) \approx V_{in} \text{ (after } 5RC), \text{ or}$$
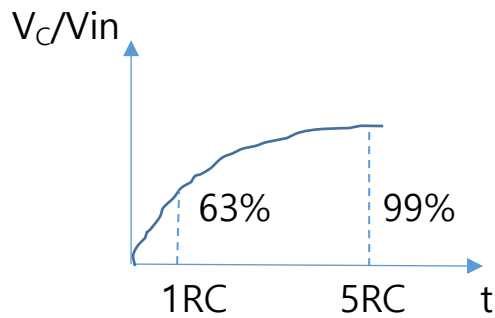
$$V_C = V_{in} Z_C / (R + Z_C) = V_{in}(1 + R/Z_C) \approx V_{in} \text{ (} \because Z_C = \infty)$$



R	C	time
MΩ	μF	sec
KΩ	μF	ms

Application3 (Varying voltage input or AC input)


When $V=AC$ (Alternating Current) voltage, it can be expressed as

$$V = \sum V_i \exp(j\omega_i t) = \sum V_i (\cos\omega_i t + j\sin\omega_i t), \text{ and } i=1 \text{ to } \infty$$

For a specific i th component,

$V = V \exp(j\omega t) = V(\cos\omega t + j\sin\omega t)$ is applied to the following elements

(1) Resistor

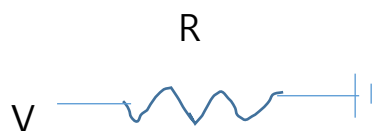

$$i = V/R = V \exp(j\omega t) / R$$


$\therefore Z \equiv$ Impedance or Generalized resistance

$=$ Resistance (by resistor) + Reactance (by capacitor or inductor)

$$\equiv \Delta V / \Delta i = V / i = R \text{ (} \omega \text{ independent)}$$

∴ Resistor gives constant impedance for AC or DC

(2) Capacitor

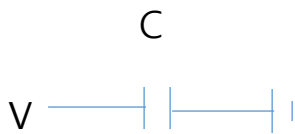

$$i = C \frac{dV}{dt} = C j\omega V \exp(j\omega t) = j\omega C V \quad \therefore Z = \text{Impedance} = \frac{V}{i} = \frac{1}{j\omega C} = f(\omega)$$

If $\omega \rightarrow 0$ then $Z \approx \infty$ (Disconnect or DC blocking)

if $\omega \rightarrow \infty$ then $Z \approx 0$ (Connect or Current free-flowing)


∴ Capacitor can give DC blocking or Filtering (ω dependant)

Application 4 (RC filters or RC voltage dividers)

LPF (Low Pass Filter)

:To pass low frequency component, or

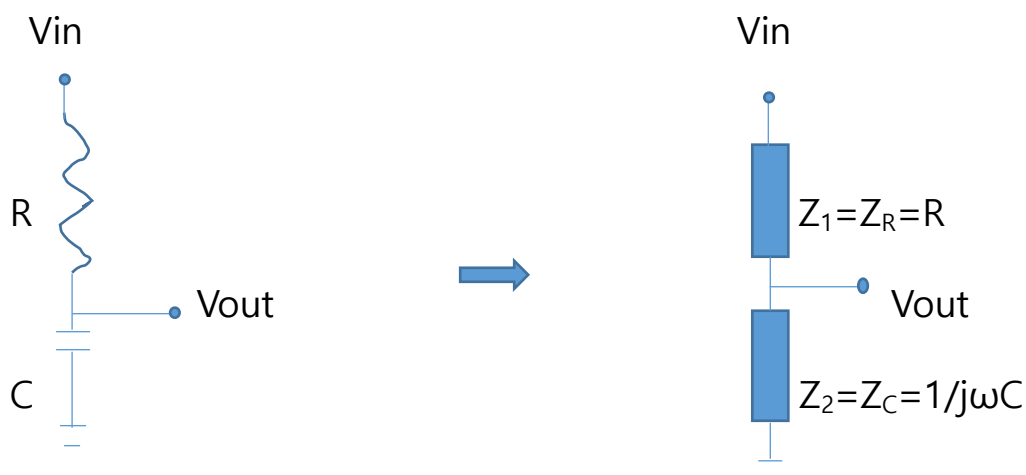To filter out the high frequency noise from the signal



The left RC circuit can be changed as the right circuit of voltage divider, considering that $Z_R = R$ and $Z_C = 1/j\omega C$

Transfer function= $V_{out}/V_{in}=Z_2/(Z_1+Z_2)=(1/j\omega C)/(R+1/j\omega C)$

= $1/(1+j\omega RC)$, assuming very little current flows into V_{out} .

This is the complex number, thus magnitude, phase are of interest.

Magnitude= $|H|=|V_{out}/V_{in}|=1/\sqrt{1+(\omega RC)^2}$

Phase= $\angle H=\angle V_{out}/V_{in}=0 - \angle(1+j\omega RC)=-\tan^{-1}(\omega RC)$

where ω =angular velocity of signal [rad/sec]= $2\pi f$


and f =frequency of signal [Hz]

Let's plot the magnitude and phase in the ω domain;

If $\omega < 1/RC$; then $|H| \approx 1$ and $\angle H \approx 0^\circ$ (or $[-45^\circ, 0^\circ]$)

If $\omega = 1/RC$ then $|H| = 1/\sqrt{2} = 0.707$ and $\angle H = -45^\circ$

If $\omega > 1/RC$ then $|H| \approx 0$ and $\angle H \approx -90^\circ$

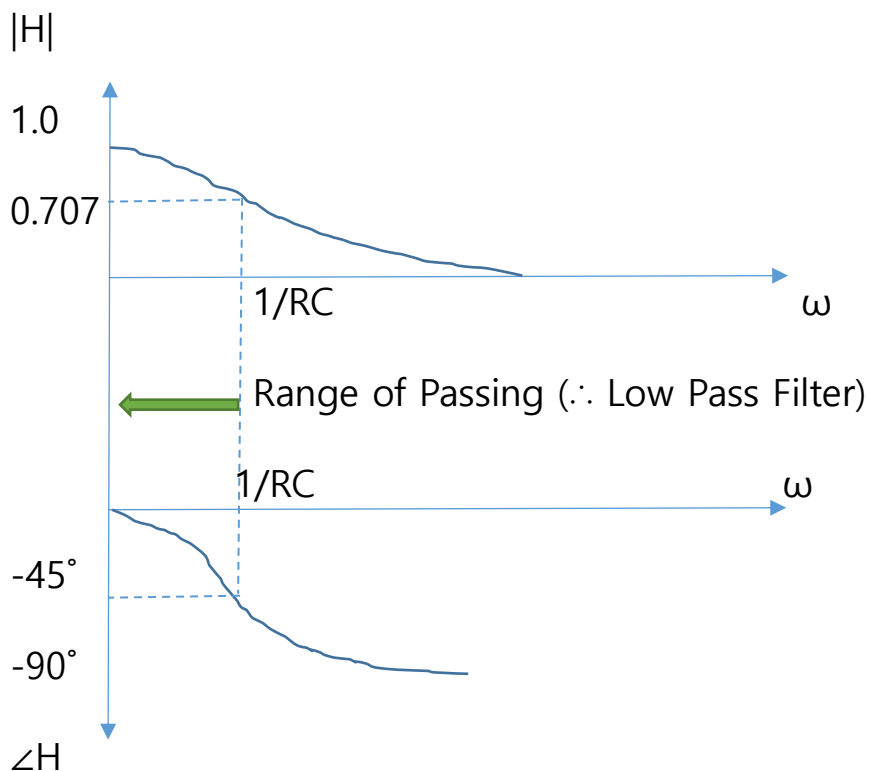

If $\omega \leq 1/RC$ then $|H| \geq 0.707$ and $|\angle H| \leq 45^\circ$, and they are acceptable for many engineering application. This circuit effectively can pass the signal of frequency range under $1/RC$. Thus it is LPF, Low Pass Filter.

At $\omega = 1/RC$, $\text{dB} = -20\text{Log}|H| = -20\text{Log}(1/\sqrt{2}) = 3$, thus $1/RC$ is called as $\omega_{3\text{dB}}$ which is very important for application. At $\omega = \omega_{3\text{dB}}$, 70% amplitude of signal is delivered, while 30% of signal is attenuated, which is quite acceptable for many engineering application. Ex) $\omega_{3\text{dB}}$ for sensor?

This LPF is very useful tool for signal conditioning, or removing the high frequency noise from the signal.

5 Design Procedures or 5 Steps for LPF

1) Frequency identification of signal

Measured signal can be analyzed by oscilloscope or frequency spectrum analysis. Then identify f_{signal} and f_{noise}

2) Choose $f_{3\text{dB}}$

You can assign $f_{3\text{dB}}$ at your design target, and f_{signal} can be conveniently chosen as the $f_{3\text{dB}}$

3) Choose R, C such that $1/RC = \omega_{3\text{dB}} = 2\pi f_{3\text{dB}}$ among commercially available components


4) Use 10X rule for components choosing if necessary

5) Performance Verification by using Signal to Noise ratio, or S/N ratio, etc

Ex) LPF design

Design a LPF to remove the noise from the signal. This LPF will be connected to A/D converter of $100\text{K}\Omega$ input impedance.

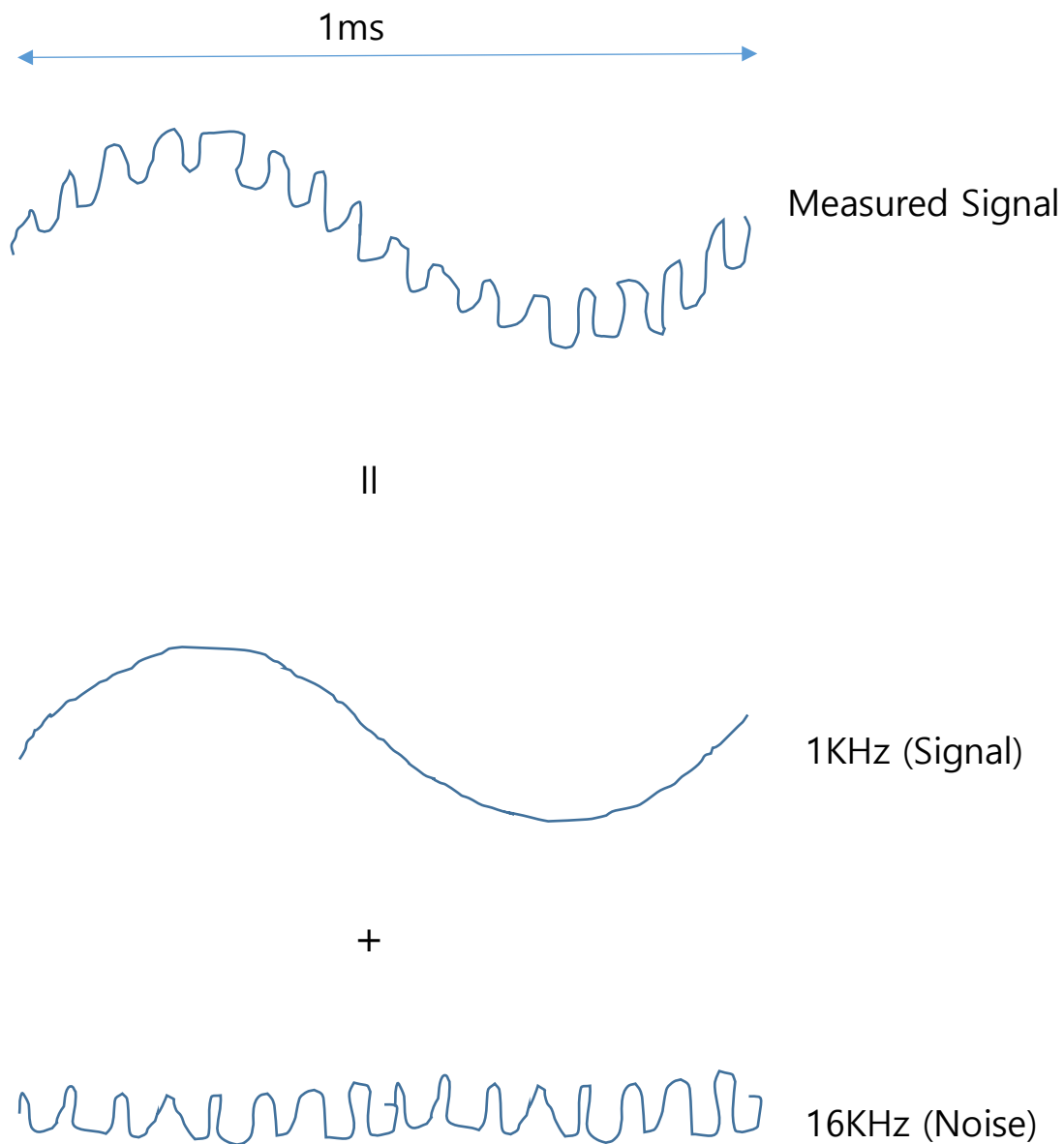Oscilloscope shows the measured signal as follows;



1) Frequency identification

$f_{\text{signal}}=1\text{KHz}$, $f_{\text{noise}}=16\text{KHz}$ by oscilloscope or spectrum analysis

2) Choose $f_{3\text{dB}}$

$$f_{3\text{dB}}=f=1\text{KHz}$$

(Q: What happen if we chose $f_{3\text{dB}}$ as 16KHz?)

3) Choose R,C from $\omega_{3\text{dB}} = 1/RC$


$$\text{Thus } 1/RC = \omega_{3\text{dB}} = 2\pi f_{3\text{dB}} = 6280[\text{rad/sec}]$$

There are so many combinations to satisfy, thus we need more information from the 10X rule

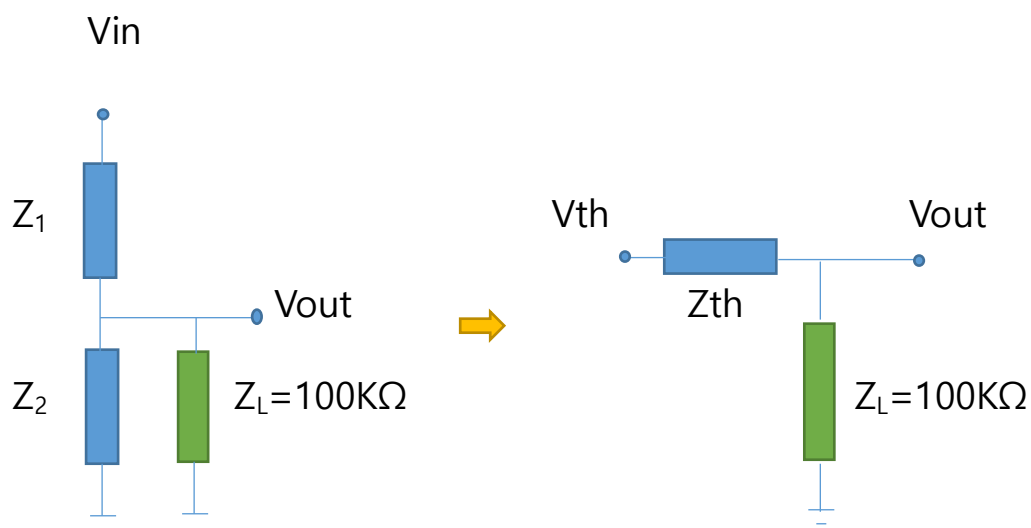4) 10X rule

This LPF is to drive the ADC of $100\text{K}\Omega$ input impedance as follows;

And it can be transformed to Thevenin's equivalent circuit



$$Z_{th} = Z_1 \parallel Z_2 = \frac{Z_1 Z_2}{Z_1 + Z_2} = \frac{(R/j\omega C)}{(R + 1/j\omega C)} = \frac{R}{1 + j\omega RC}$$

Magnitude of Z_{th} , $|Z_{th}| = R/\sqrt{1+(\omega RC)^2} \leq R$

Thus maximum of Z_{th} is R , and Z_{th} is to drive the Z_L ; therefore it is quite reasonable to choose R as one tenth of $Z_L (=100K\Omega)$ by the 10X rule, satisfying $Z_{out} \leq Z_{in}/10$ in general application of voltage circuit.

Thus $R = 10K\Omega$, and $C = 1.59E-8F \approx 0.02\mu F$ from commercial availability.

5) Verification

For 1KHz signal, or $\omega = 2\pi(1000)$ rad/sec

$$|H| = |V_{out}/V_{in}| = 1/\sqrt{1+(\omega RC)^2} \approx 0.623 \text{ (why not 0.707 ?)}$$

$$\angle H = -\angle(1+j\omega RC) = -\tan^{-1}(\omega RC) \approx -51.5^\circ \text{ (why not } -45^\circ \text{ ?)}$$

For 16KHz noise, or $\omega = 2\pi(16000)$ rad/sec

$$|H| = |V_{out}/V_{in}| = 1/\sqrt{1+(\omega RC)^2} \approx 0.06 \text{ (6%)}$$

$$\angle H = -\angle(1+j\omega RC) = -\tan^{-1}(\omega RC) \approx -87.2^\circ$$

Before LPF application, Given $S=1$, $N=1$, then $S/N=1$

After LPF application, $S = 0.623$, $N=0.06$, then $S/N=0.623/0.06 \approx 10.4$

Thus S/N ratio changes from 1 to 10.4, which is more than 10 times improvement!

It is wonderful result for S/N ratio improvement by the LPF application.

Q: What happen if only Z_L is changed to $10K\Omega$, while others are unchanged?

→ Hint : $H = V_{out}/V_{in} = 1/\{1 + R/R_L + j\omega RC\}$