

## Lecture 8: Inductor and RLC filter

### Inductor

Coil wound on various core materials such as iron, iron alloys, ferrite to multiply the inductance of a given coil by permeability of core material. It is to store the electric energy into the inductor's magnetic field



Symbol

L[H]



Law

$$V = L \frac{di}{dt} \text{ or } i = \int V dt / L \text{ or } L = V / (di/dt)$$

Where  $V$  = Across voltage,  $i$  = current flow,  $L$  = Inductance [H]

Let alternating voltage signal,  $V = V_0 \exp(j\omega t)$ ,




$$\text{then } i = \int V dt / L = V_0 \exp(j\omega t) / j\omega L = V / j\omega L$$

Thus Impedance,  $Z = V/i = j\omega L$  [ $\Omega$ ] for alternating voltage or current

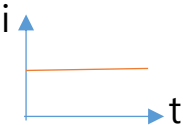

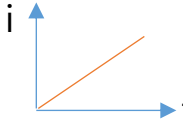
Application: Transformer (primary coil -> magnetic field -> secondary coil)

Filters, RF circuit, etc

## Comparison between Resistor/Capacitor/Inductor

Resistor(R)	Capacitor(C)	Inductor(L)
		
Energy into	Energy into	Energy into
Heat dissi.	Electric field	Magnetic field
$i=V/R$	$i=CdV/dt$	$i=\int Vdt/L$

(When  $V=const.$ )


		
(Proportional)	(Derivative)	(Integral)

Impedance	Impedance	Impedance
$Z=R$	$Z=1/j\omega C$	$Z=j\omega L$

The above three elements are complimentary each other, thus can be used for variety of application.

## RL filter


### High Pass Filter

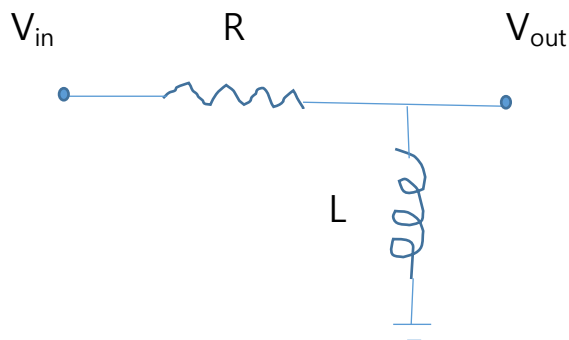

$$H = V_{out}/V_{in} = Z_L / (Z_R + Z_L) = j\omega L / (R + j\omega L)$$

$$\text{Magnitude} = |H| = \omega L / \sqrt{R^2 + (\omega L)^2}$$
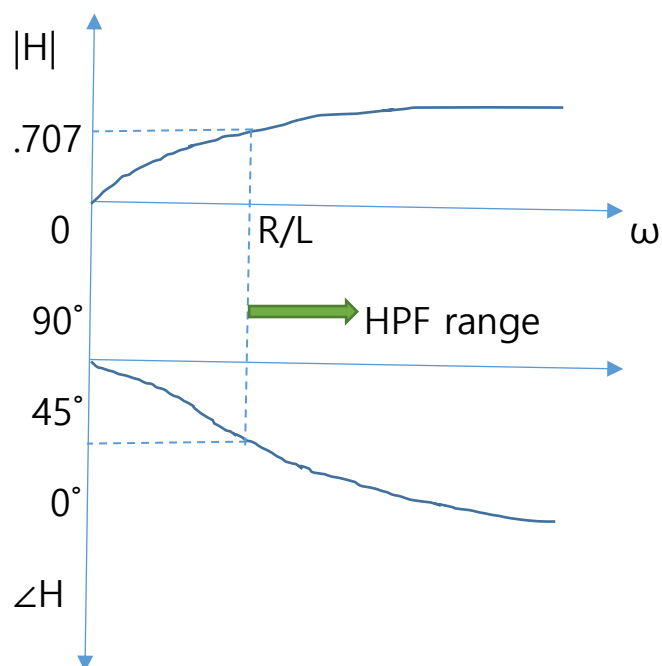
$$\text{Phase} = \angle H = 90^\circ - \tan^{-1}(\omega L / R)$$




∴ This is a HPF with  $\omega_{3dB} = R/L$

Thevenin's equivalent impedance,  $Z_{th} = Z_R \parallel Z_L = j\omega L R / (j\omega L + R)$ ,

and  $|Z_{th}| = \omega L R / \sqrt{(\omega L)^2 + R^2} \leq R$  (at  $\omega = \infty$ )


## Low Pass Filter

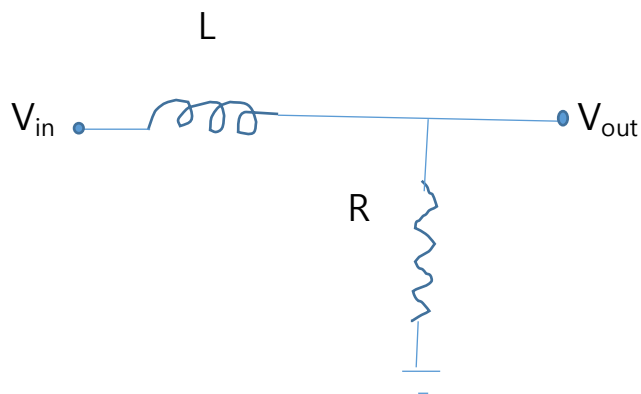

$$H = V_{out}/V_{in} = Z_R/(Z_R + Z_L) = R/(R + j\omega L)$$

$$\text{Magnitude} = |H| = R/\sqrt{R^2 + (\omega L)^2}$$
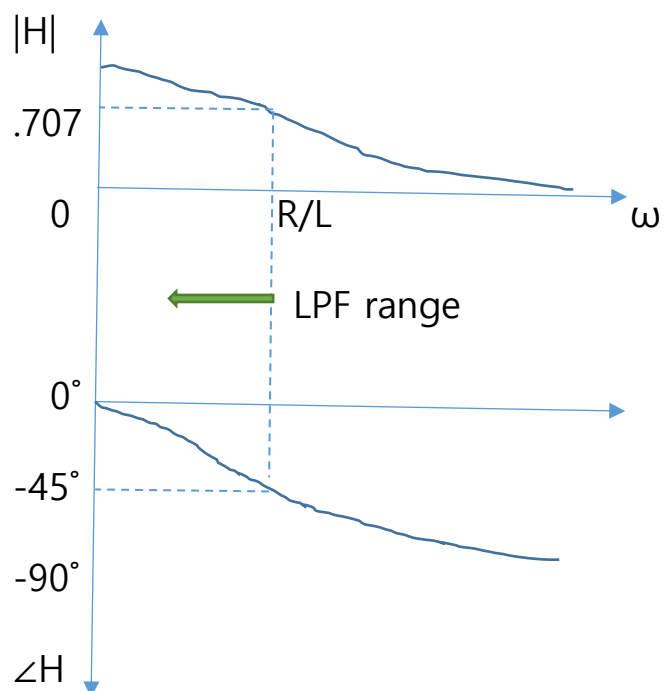
$$\text{Phase} = \angle H = -\tan^{-1}(\omega L/R)$$




$\therefore$  This is a LPF with  $\omega_{3dB} = R/L$

Thevenin's equivalent impedance,  $Z_{th} = Z_L \parallel Z_R = j\omega L R / (j\omega L + R)$ ,

and  $|Z_{th}| = \omega L R / \sqrt{(\omega L)^2 + R^2} \leq R$  (at  $\omega = \infty$ )

## RLC filter

:Narrow Bandpass Filter

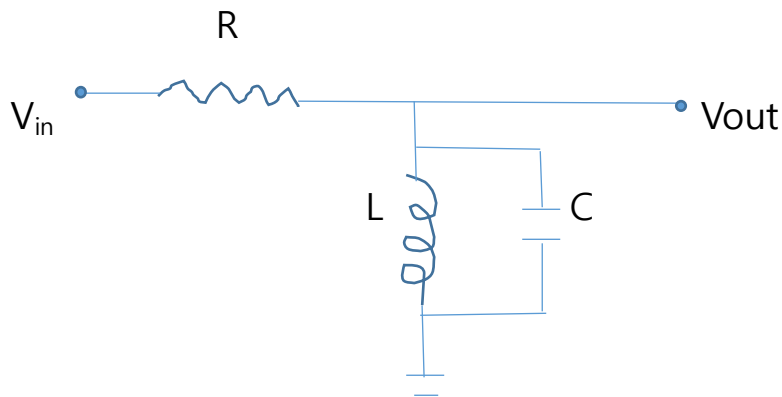

The impedance of LC parallel connection becomes  $Z_L \parallel Z_C$  and

$$Z_L \parallel Z_C = Z_L Z_C / (Z_L + Z_C) = j\omega L / j\omega C / (j\omega L + 1/j\omega C)$$

$$= j\omega L / (1 - \omega^2 LC)$$

$$H = V_{out} / V_{in} = Z_L \parallel Z_C / (Z_R + Z_L \parallel Z_C)$$

$$= j\omega L / (1 - \omega^2 LC) / \{R + j\omega L / (1 - \omega^2 LC)\}$$

$$= j\omega L / \{R(1 - \omega^2 LC) + j\omega L\}$$

$$\text{Magnitude, } |H| = \omega L / \sqrt{\{R^2(1 - \omega^2 LC)^2 + (\omega L)^2\}}$$


$$\text{Phase, } \angle H = \angle(j\omega L) - \angle\{R(1 - \omega^2 LC) + j\omega L\}$$

Plot for performance

$$\text{If } \omega \ll 1/\sqrt{LC} \text{ then } |H| \approx 0 \text{ and } \angle H \approx 90^\circ - 0^\circ = 90^\circ$$

$$\text{If } \omega = 1/\sqrt{LC} \text{ then } |H| = 1 \text{ and } \angle H = 90^\circ - 90^\circ = 0^\circ$$

$$\text{If } \omega \gg 1/\sqrt{LC} \text{ then } |H| \approx 0 \text{ and } \angle H \approx 90^\circ - 180^\circ = -90^\circ$$

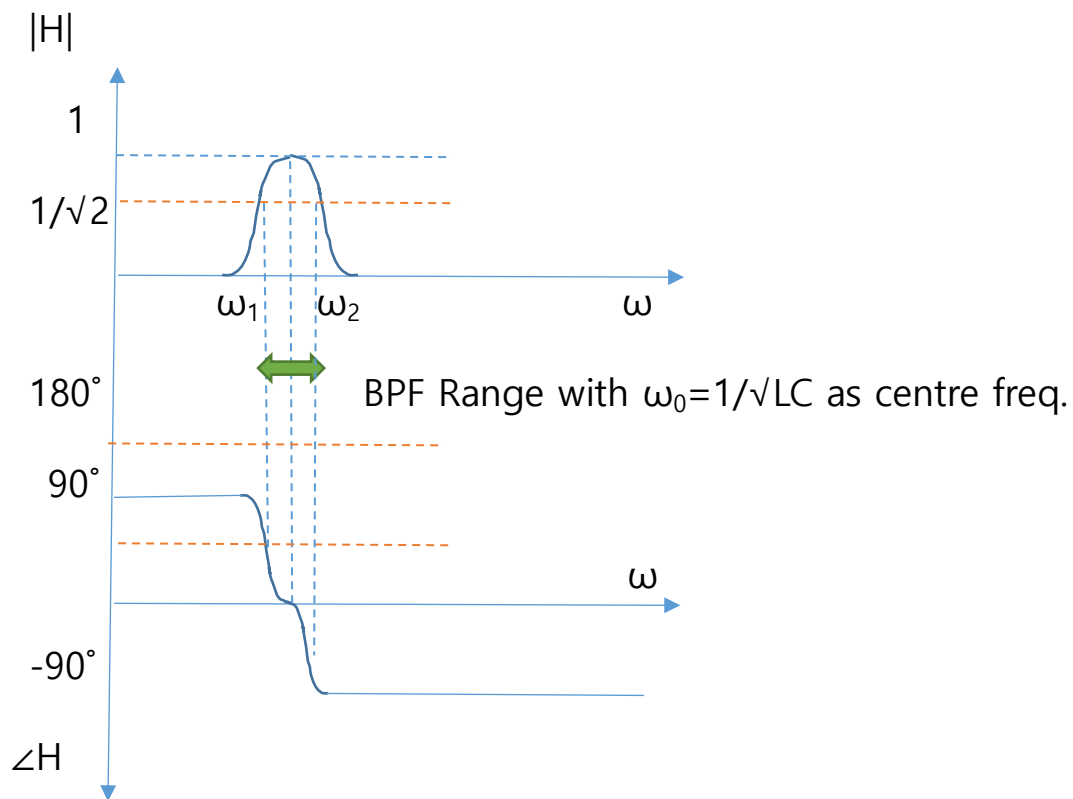

This is the Narrow Band Pass Filter that gives much narrower BPF with centre frequency  $\omega_0 = 1/\sqrt{LC}$

The *3dB frequency*  $\omega_1$  and  $\omega_2$  can be evaluated as the freqs that gives the height of  $1/\sqrt{2}$ , by solving the equation

$$|H| = \omega L / \sqrt{\{R^2(1 - \omega^2 LC)^2 + (\omega L)^2\}} = 1/\sqrt{2}, \text{ and if } 0 < \omega_1 < \omega_2 \text{ then}$$

$$\omega_1 = \{-L + \sqrt{L^2 + 4R^2 LC}\} / 2RLC \text{ and } \omega_2 = \{L + \sqrt{L^2 + 4R^2 LC}\} / 2RLC$$

$$\text{Thus } \Delta\omega = \omega_2 - \omega_1 = 2L / 2RLC = 1/RC \equiv \Delta\omega_{3dB}$$

And Quality Factor, Q is defined as follows;

$$Q \equiv \omega_0 / \Delta\omega_{3dB} = \omega_0 RC = \text{Measure of Profile Sharpness} = 10 \sim 50, \text{ typically,}$$

and it is one of meaningful design parameters

Thevenin's equivalent impedance,  $Z_{th}$ , for the narrow BPF is,

$$Z_{th} = Z_R \parallel Z_L \parallel Z_C = Z_R \parallel (Z_L \parallel Z_C) = Z_R (Z_L \parallel Z_C) / (Z_R + Z_L \parallel Z_C)$$


and  $Z_L \parallel Z_C = Z_L Z_C / (Z_L + Z_C) = j\omega L / (1 - \omega^2 LC)$ , thus

$$Z_{th} = \{j\omega R L / (1 - \omega^2 LC)\} / \{R + j\omega L / (1 - \omega^2 LC)\}$$

$$= j\omega R L / \{R(1 - \omega^2 LC) + j\omega L\}$$

$\therefore$  Magnitude  $|Z_{th}| = \omega R L / \sqrt{\{R^2(1 - \omega^2 LC)^2 + (\omega L)^2\}} \leq R$  (at  $\omega = 1/\sqrt{LC}$ )

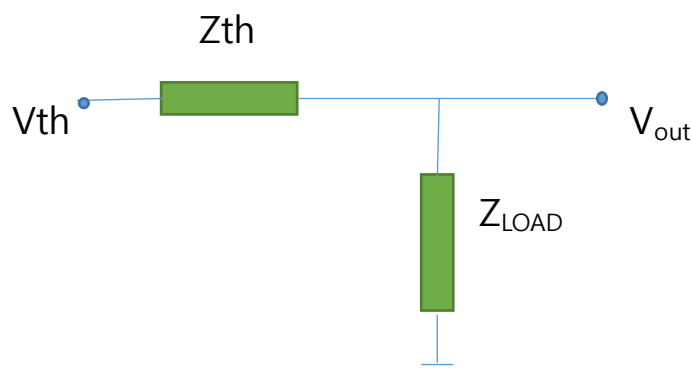Thevenin's equivalent circuit is as follows when  $Z_{LOAD}$  is applied,



$Z_{th}$  should drive  $Z_{LOAD}$ , and  $Z_{th} \ll Z_{LOAD}$  is to be satisfied. Therefore,

$$R = R_{LOAD} / 10 \text{ from the 10X rule} \quad \text{eq(1)}$$

$$\omega_0 = \text{centre frequency} = 1/\sqrt{LC} \quad \text{eq(2)}$$


$$Q = \omega_0 / \Delta\omega_{3dB} = \omega_0 RC = \text{Profile Sharpness} \quad \text{eq(3)}$$

= 10 to 50 in practice (Design parameter)

With the above 3 equations, the R,L,C components can be determined.

Note that bigger R gives sharper profile, when L,C are fixed.

## RLC notch filter

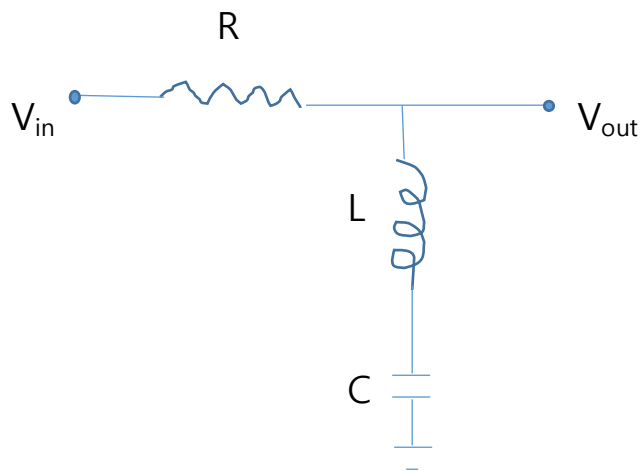

Serial connection of L and C gives the impedance of  $Z_L + Z_C$

$$= j\omega L + 1/j\omega C$$

$$H = V_{out}/V_{in} = (Z_L + Z_C)/(Z_R + Z_L + Z_C)$$

$$= (j\omega L + 1/j\omega C)/(R + j\omega L + 1/j\omega C)$$

$$= (1 - \omega^2 LC)/\{(1 - \omega^2 LC) + j\omega RC\}$$

$$\text{Magnitude} = |H| = (1 - \omega^2 LC)/\sqrt{\{(1 - \omega^2 LC)^2 + (\omega RC)^2\}}$$

$$\text{Phase} = \angle H = \angle(1 - \omega^2 LC) - \angle\{(1 - \omega^2 LC) + j\omega RC\}$$

For plot of performance,

$$\text{If } \omega \ll 1/\sqrt{LC} \text{ then } |H| \approx 1 \text{ and } \angle H \approx 0^\circ - 0^\circ = 0^\circ$$

$$\text{If } \omega =^- 1/\sqrt{LC} \text{ then } |H| = 0 \text{ and } \angle H = 0^\circ - 90^\circ = -90^\circ$$


$$\text{If } \omega =^+ 1/\sqrt{LC} \text{ then } |H| = 0 \text{ and } \angle H = 180^\circ - 90^\circ = 90^\circ$$

$$\text{If } \omega \gg 1/\sqrt{LC} \text{ then } |H| \approx 1 \text{ and } \angle H \approx 180^\circ - 180^\circ = 0^\circ$$

( $^-$  indicates the slightly less,  $^+$  indicates the slightly bigger)



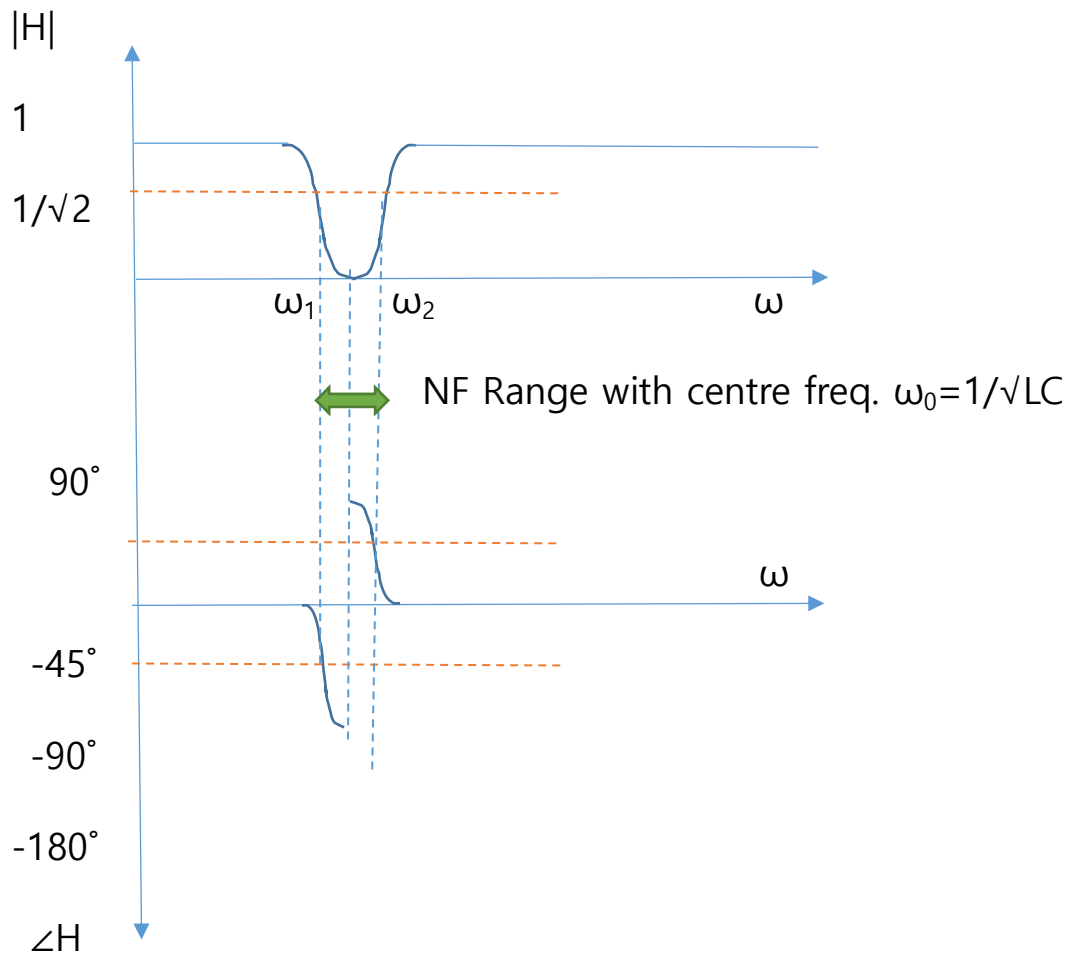∴ This is the notch filter or to trap with the centre frequency  $\omega_0$



The 3dB frequency  $\omega_1$  and  $\omega_2$  can be evaluated as the freqs that gives the height of  $1/\sqrt{2}$ , by solving the equation

$$|H| = \frac{1 - \omega^2 LC}{\sqrt{\{(1 - \omega^2 LC)^2 + (\omega RC)^2\}}} = 1/\sqrt{2}, \text{ and if } 0 < \omega_1 < \omega_2 \text{ then}$$

$$\omega_1 = \{-RC + \sqrt{(R^2 C^2 + 4LC)}\} / 2LC \text{ and } \omega_2 = \{+RC + \sqrt{(R^2 C^2 + 4LC)}\} / 2LC$$

$$\text{Thus } \Delta\omega = \omega_2 - \omega_1 = 2RC / 2LC = R/L \equiv \Delta\omega_{3dB}$$

And Quality Factor, Q is defined as follows;

$Q \equiv \omega_0 / \Delta\omega_{3dB} = \omega_0 L / R =$  Measure of Profile Sharpness, 10~50, typically and it is one of meaningful design parameters.

Thevenin's equivalent impedance  $Z_{th}$  for the Notch filter is,


$$Z_{th} = Z_R \parallel (Z_L + Z_C) = Z_R (Z_L + Z_C) / (Z_R + Z_L + Z_C)$$

$$= R(j\omega L + 1/j\omega C) / \{R + j\omega L + 1/j\omega C\}$$

$$= R(1 - \omega^2 LC) / \{(1 - \omega^2 LC) + j\omega RC\}$$

$$\therefore \text{Magnitude, } |Z_{th}| = R(1 - \omega^2 LC) / \sqrt{\{(1 - \omega^2 LC)^2 + (\omega RC)^2\}} \leq R \text{ (at } \omega = 0 \text{ or } \infty)$$

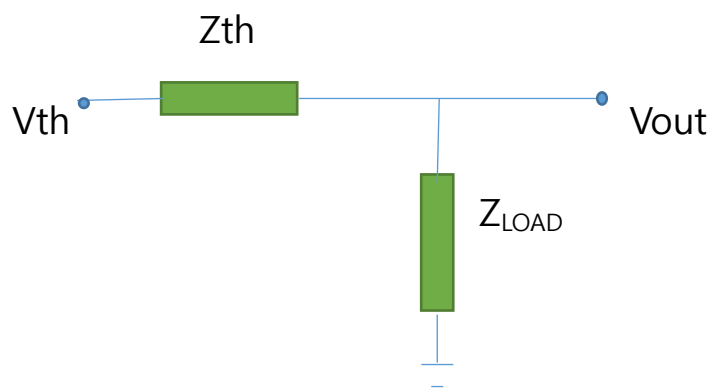Thevenin's equivalent circuit is as follows when  $Z_{LOAD}$  is applied,



$Z_{th}$  should drive  $Z_{LOAD}$ , and  $Z_{th} \ll Z_{LOAD}$  is to be satisfied. Therefore,

$$R = R_{LOAD} / 10 \text{ from the 10X rule} \quad \text{eq(4)}$$

$$\omega_0 = \text{centre frequency} = 1/\sqrt{LC} \quad \text{eq(5)}$$

$$Q = \omega_0 / \Delta\omega_{3dB} = \omega_0 L / R = \text{Profile Sharpness} \quad \text{eq(6)}$$

= 10 to 50 in practice (Design parameter)

With the above 3 equations, the R,L,C components can be determined.


Note that smaller R gives sharper profile, when L,C are fixed.

HW5) Design a Narrow Band Pass Filter as follows;

Centre freq=5KHz, Quality factor=20,  $R_{LOAD}=200K\Omega$

### RC Circuits revisited

#### 1) HPF as Differentiator

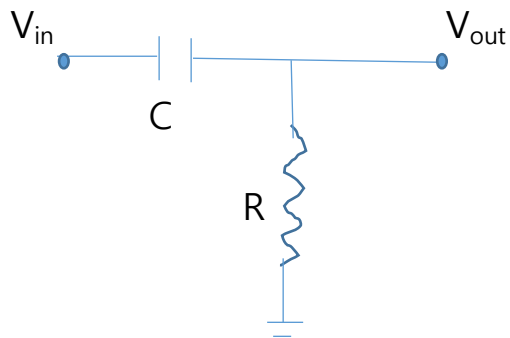

$$V_{out}/V_{in} = R/(1/j\omega C + R) = j\omega RC/(1 + j\omega RC)$$

If  $RC \ll 1$  then  $j\omega RC$  is very small

From Taylor's expansion formula,

$$1/(1 + j\omega RC) \approx 1 - j\omega RC + (j\omega RC)^2 - (j\omega RC)^3 \dots$$

$$\text{Thus } V_{out}/V_{in} = j\omega RC(1 - j\omega RC + (j\omega RC)^2 \dots)$$

$$= j\omega RC - (j\omega RC)^2 + (j\omega RC)^3 - \dots$$

$$\approx j\omega RC \quad (\because \text{Higher order term can be very small})$$

$$\text{Thus } V_{out} \approx j\omega RC V_{in}$$

As  $V_{in}$  can be generally expressed as  $V \exp(j\omega t)$ ,



$$dV_{in}/dt = j\omega V \exp(j\omega t) = j\omega V_{in}, \text{ therefore,}$$

$$V_{out} \approx j\omega RC V_{in} = RC dV_{in}/dt \quad \text{if } RC \ll 1 \text{ or } 1/RC \text{ is very big.}$$

∴ HPF can be a differentiator if  $\omega_{3dB}=1/RC$  is very high


For a practical example,  $R=10K\Omega$  and  $C=0.01\mu F$  in the above HPF design gives  $RC=1.0E-4$  (i.e.  $f_{3dB}\approx 1600Hz$ ) as quite small and can be used as a differentiator. This observation is really wonderful as the differentiator can be easily implemented with the HPF.

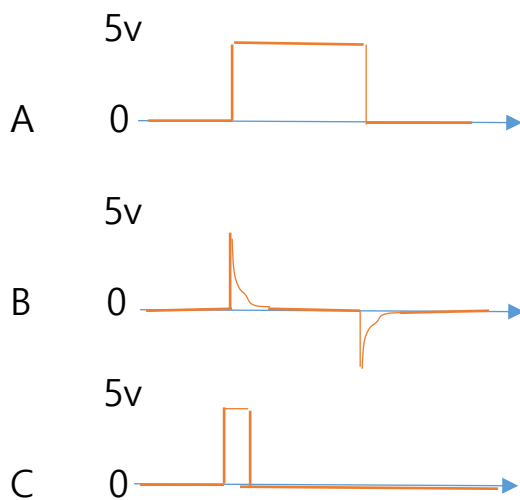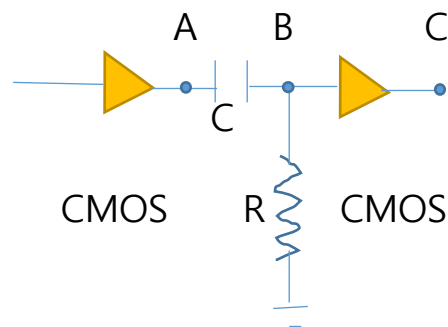The following demonstrates a good example for the leading edge detector in CMOS circuit with  $C=100pF$  and  $R=10K\Omega$  (or  $RC=1.0E-6$ )



(Q: What about trailing edge detector?)

## 2) LPF as Integrator

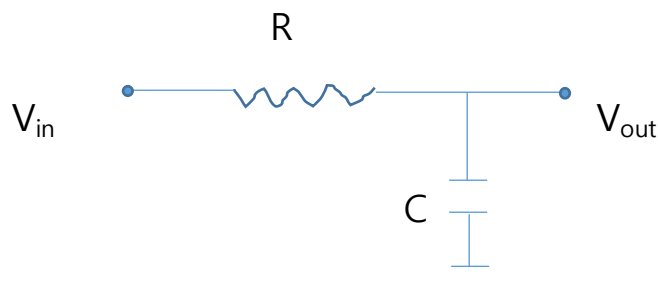

$$V_{out}/V_{in} = 1/j\omega C / (R + 1/j\omega C) = 1/(1 + j\omega RC)$$

If RC is quite big such as  $RC \gg 1$ , then  $1/(1 + j\omega RC) \cong 1/j\omega RC$

Thus  $V_{out}/V_{in} \cong 1/j\omega RC$ , and  $V_{out} \cong V_{in}/j\omega RC$

Remembering  $V_{in} = V \exp(j\omega t)$ , then  $\int V_{in} dt = V \exp(j\omega t) / j\omega = V_{in} / j\omega$

Thus  $V_{out} \cong V_{in} / j\omega RC = \int V_{in} dt / RC$  if  $RC \gg 1$  or  $\omega_{3dB} = 1/RC \ll 1$

$\therefore$  LPF can be an Integrator if  $\omega_{3dB} = 1/RC$  is quite low

For a LPF with  $R = 100K$ ,  $C = 100\mu F$ , then  $RC = 10$ , and  $f_{3dB} \cong 0.016Hz$ .

Thus it can be used as Integrator.

HPF/LPF based Integrator/Differentiator is quite simple to implement, but it needs some care for the assumption.

-> OP amp based Differentiator/Integrator will give wider application.