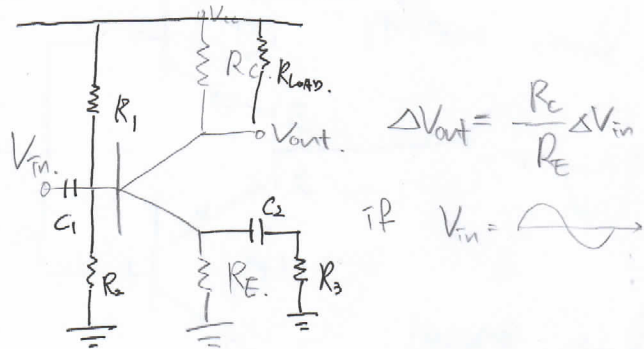


11/6. ①
AC-Coupled
Common emitter Follower.



2. AC component (signal) $R_{LOAD} \gg R_C$

$$Gain = -100 = - \frac{R_C // R_{LOAD}}{R_E // R_3 + r_e}$$

$$r_e = \frac{25 \text{ mV}}{I_E} = 50 \Omega \text{ (very small)}$$


$$= - \frac{20 \text{ k}}{R_E // R_3 + r_e} = -100$$

$$\therefore R_E // R_3 = 150 \Omega$$

$$\therefore \frac{R_E \cdot R_3}{R_E + R_3} = 150$$

$$R_3 \approx 150 \Omega$$

C_1 ① $\omega_{3dB} = 100 \text{ Hz}$

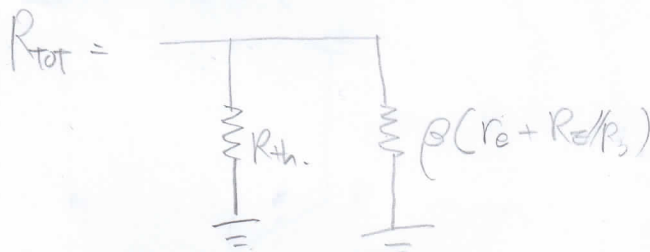

$$R_{th} = 20 \text{ k}$$

$$\beta(re + R_E // R_3) = 100 \left(50 + 2 // 150 \right) = 20 \text{ k}$$

$$R_{tot} = 10 \text{ k}$$

$$f'_{3dB} = 50 \text{ Hz} \leftarrow 100 \text{ Hz} \cdot \frac{C_1 = 0.3 \mu\text{F}}{10 \text{ k}}$$

(∴ Cascaded HPF)

to avoid excessive attenuation

ex) $V_{CC} = 20 \text{ V}$, $Gain = -100$, $I_C = 0.5 \text{ mA}$ (given)

$f_{3dB} = 100 \text{ Hz}$ for biasing

1. DC component (Quiescent Case)

$V_E = 1 \text{ V}$ (given for temp stability)


$$R_E = \frac{1 \text{ V}}{0.5 \text{ mA}} = 2 \text{ k}\Omega$$

$$\frac{R_2}{R_1 + R_2} = \frac{1.6}{20} \dots \text{①}$$

$$R_{th} = \frac{R_1 R_2}{R_1 + R_2} = 20 \text{ k} \dots \text{②}$$

$$R_1 = 220 \text{ k}, R_2 = 20 \text{ k}$$

From R_C Centering at V_{out} .

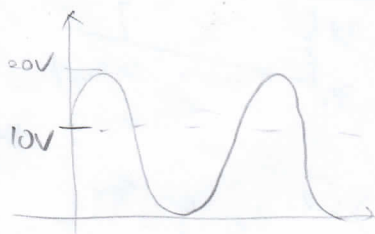

$$V_{out} = 10 \text{ V} = V_{CC} - I_C R_C = 20 - (0.5) R_C = 10 \text{ V}$$

$$\therefore R_C = 20 \text{ k}$$


C_2

$R = R_3 + r_e = 200 \Omega$


$\frac{C_2}{R}$

$f_{2dB} = 50 \text{ Hz}, C_2 \approx 16 \mu\text{F}$


Unit Gain

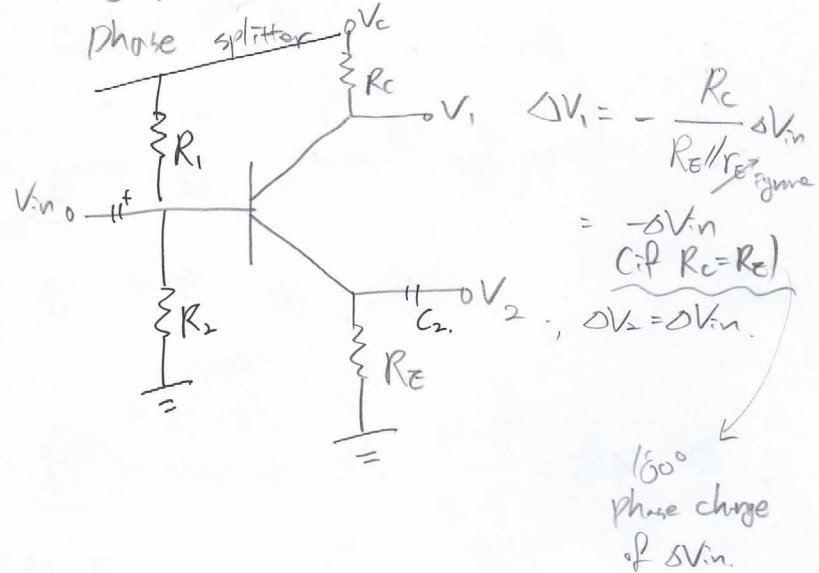


TR switch.

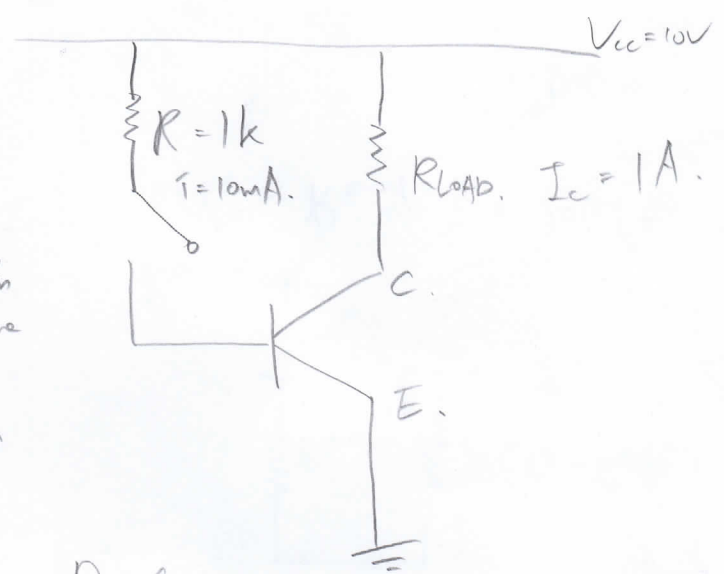


Darlington circuit

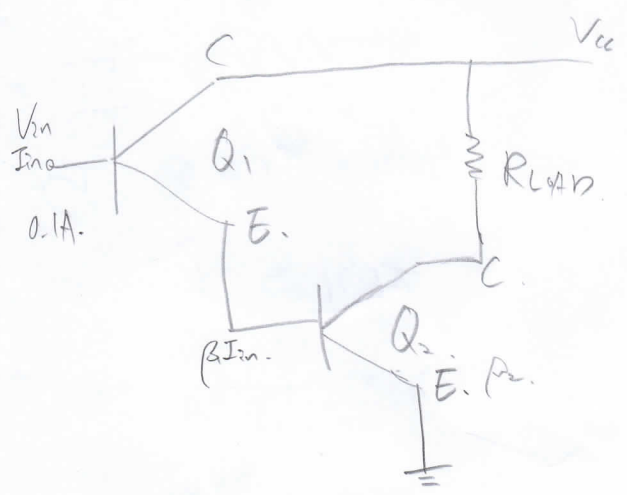

application example.

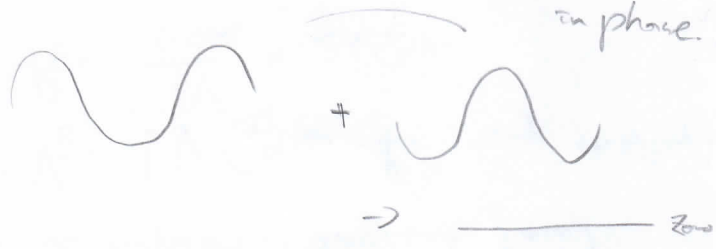

Push Pull Amplifier.

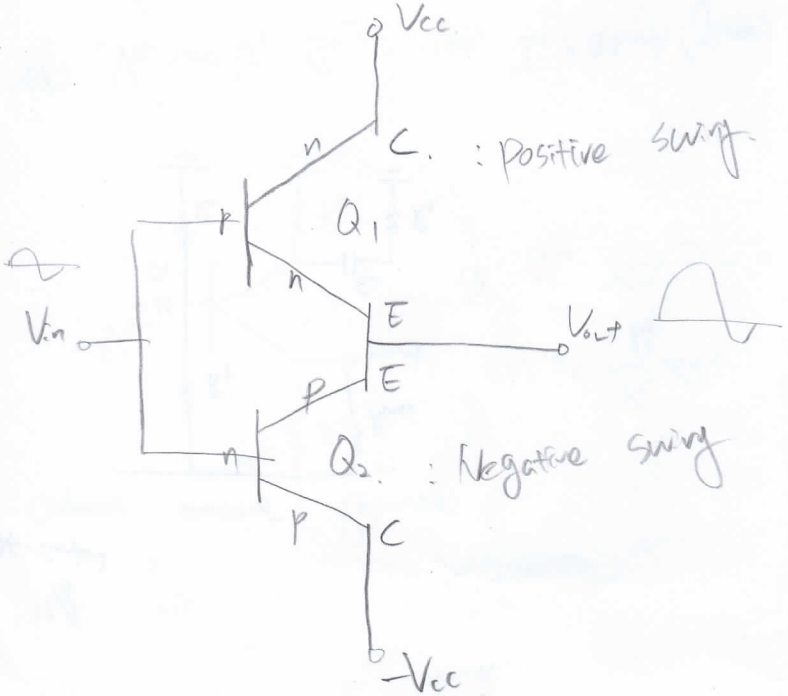

$\beta_2 \beta_1 I_{in} = I_c = 1kA$

$d_1 = \sqrt{x^2 + (y-h)^2}$

$d_2 = \sqrt{x^2 + y^2}$

$d_3 = \sqrt{\dots}$

