
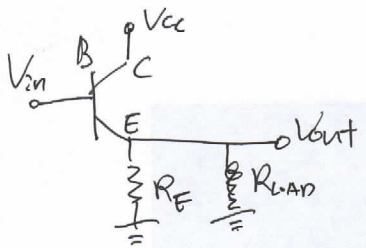


Emitter follower

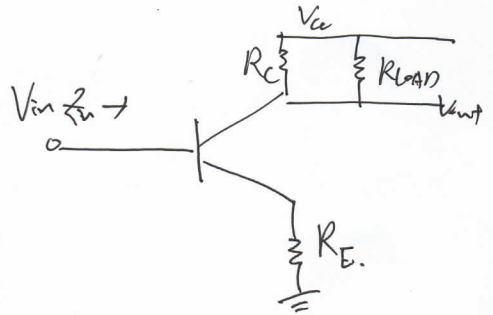

$\Delta V_{out} = \Delta V_{in}$
 $I_{out} = \beta I_{in}$
 $Z_{in} = \beta \cdot R_E$
 $Z_{out} = R_E \parallel R_{LOAD}$


Common Emitter follower



$\Delta V_{out} = -\frac{R_c}{R_E} \Delta V_{in}$, $Z_{out} = R_c \parallel R_{LOAD}$
 $I_{out} = \beta I_{in}$
 $Z_{in} = \beta \cdot R_E$

If $V_{in} = \sin(\omega t)$ (f.c)

Voltage Bypassing circuit is needed.

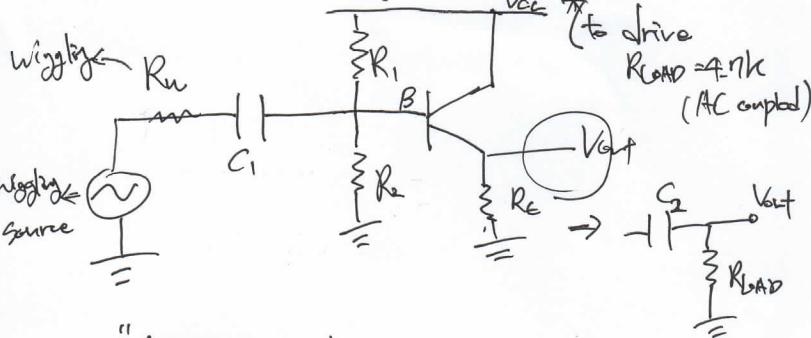

→ "AC-coupled Emitter Follower"

1. Choose V_E to centering to $V_{cc}/2$
 $V_E = 7.5V$ to V_{out} maximum range.

$R_E = \frac{V_E}{I_{quie}} = \frac{7.5V}{0.5mA} = 15k\Omega$

2. Choose R_1, R_2

$\frac{8.1}{15} = \frac{R_2}{R_1 + R_2} \dots \textcircled{1}$


$R_{TH} = R_1 \parallel R_2$

$R_{TH} = \frac{1}{10} Z_B$ (10X rule)

$\frac{R_1 R_2}{R_1 + R_2} = \frac{1}{10} \beta \cdot R_E = 150k \dots \textcircled{2}$

$\therefore R_1 = 277k, R_2 = 325k$

3. Choose C_1

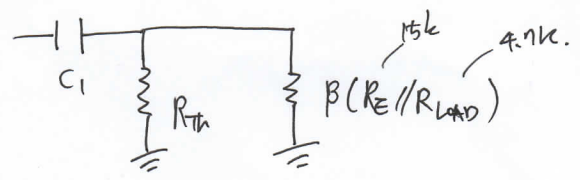


$\therefore R_{TOT} = R_{TH} \parallel \beta (R_E \parallel R_{LOAD})$
 $= 105.7k\Omega \approx 100k\Omega$

$\therefore \omega_{3dB} = 100Hz (2\pi) = \frac{1}{R_{TOT} \cdot C_1}$

$C_1 = 1.5 \times 10^{-8} F \approx 0.02\mu F$ (commercially)

4. Choose C_2

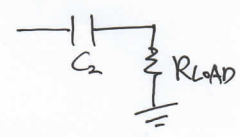


$\omega_{3dB} = 100Hz (2\pi) = \frac{1}{R_{LOAD} \cdot C_2} \therefore C_2 = 0.3\mu F$

For two cascaded HPF.

$C_2 = 3 \cdot C_1$ practice to prevent excessive attenuation @ 3dB

10/23 ②

Two cascaded HPF (LRF)

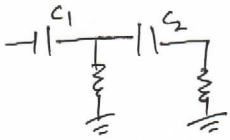

1) $C_1'_{new} = C_1 / 10$ $C_2' = 3 \cdot C_2$


2) $C_1' = 2 C_1$, $C_2' = 2 C_2$

if LRF? $3 \rightarrow \frac{1}{3}$, $2 \rightarrow \frac{1}{2}$


1) $C_2' = \frac{1}{3} C_2$, "

2) $C_1' = \frac{1}{2} C_1$, $C_2' = \frac{1}{2} C_2$

HPF.

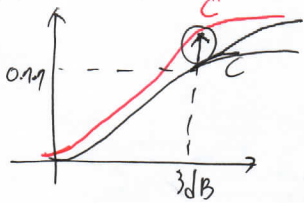

LRF

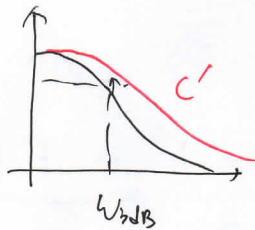


5.

$R_w \leq \frac{1}{10} R_w = 10k\Omega$



$R_{tot} = 105k\Omega$

Ebers-Moll Model for TR.

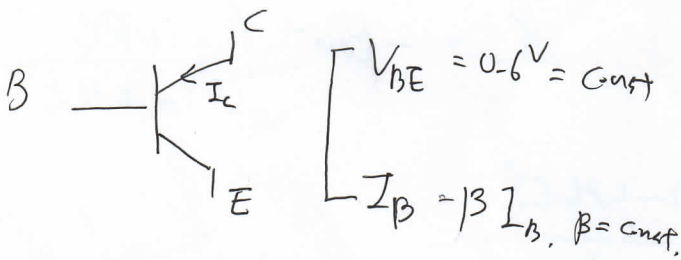

$$I_C = I_S \left[\exp\left(\frac{V_{BE}}{V_T}\right) - 1 \right] - I_S \cdot \exp\left(\frac{V_{BE}}{V_T}\right)$$

- E-M eqn

$I_S = \text{saturation current} = \text{const}$

$V_{BE} = V_B - V_E$

$V_T = \frac{kT}{q}$

$k = \text{Boltzmann's constant}$, $q = \text{charge}$

$T = \text{Temp. (Kelvin)}$

$V_{BE} = V_T \cdot \ln\left(\frac{I_C}{I_S}\right) = V_T (\ln I_C - \ln I_S)$

$\frac{\partial V_{BE}}{\partial I_C} = V_T \frac{1}{I_C}$

③ $Z_{BE} \approx \frac{\partial V_{BE}}{\partial I_C} \left(= \frac{\Delta V_{BE}}{\Delta I_C} \right) = \frac{V_T}{I_C}$

def

$\equiv r_e = \text{Intrinsic resistance}$

at an E

$\neq \text{const } r_e \left(\frac{V_T}{I_C} \right)$


③ $\frac{\Delta V_{BE}}{\Delta T} \approx \frac{-2.1 \text{ mV}}{K}$

④

$\Delta V_{BE} = -0.0001 \Delta V_{CE}$

$= -0.01\% \text{ of } \Delta V_{CE}$


Revisit to previous model

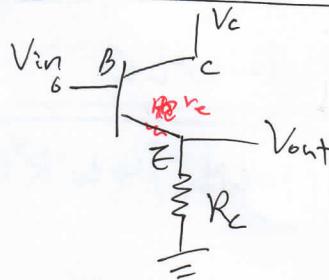

Emitter Follower

$\Delta V_{out} = \frac{R_E}{R_E + r_e} \Delta V_{in}$

Common Emitter follower

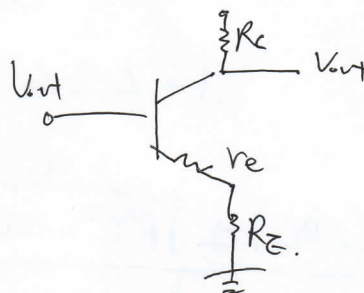

$\Delta V_{out} = - \frac{R_C}{R_C + r_e} \Delta V_{in}$

$r_e = \frac{25.3}{I_C}$