 

CMOS Logic Circuits – Switch model


Switch Logic

Digital systems use binary variables to represent information and switches to be controlled by the variables to process information.

Variable **a** controls a switch that connects a voltage source to a light bulb.




(a)

 



(b)

AND, OR, OR-AND Switch Networks

 


$$f = a \wedge b$$

(a)

  


$$f = a \vee b$$

(b)

 


$$f = (a \vee b) \wedge c$$

 Two switch networks of 3-input majority function




(a)

 


(b)

$$f = (a \wedge b) \vee (a \wedge c) \vee (b \wedge c)$$

Switch networks of XOR

 


(a)

 


(b)

 Example: Series-parallel networks


Draw and simplify a series-parallel circuit that realizes the function $f(d,c,b,a) = 1$ if $dcba$ is a legal thermometer encoding (0000, 0001, 0011, 0111, or 1111).




(a)

 


(b)

 


(c)

 

(d)

 


(e)



 


(f)

MOS Transistor 구조

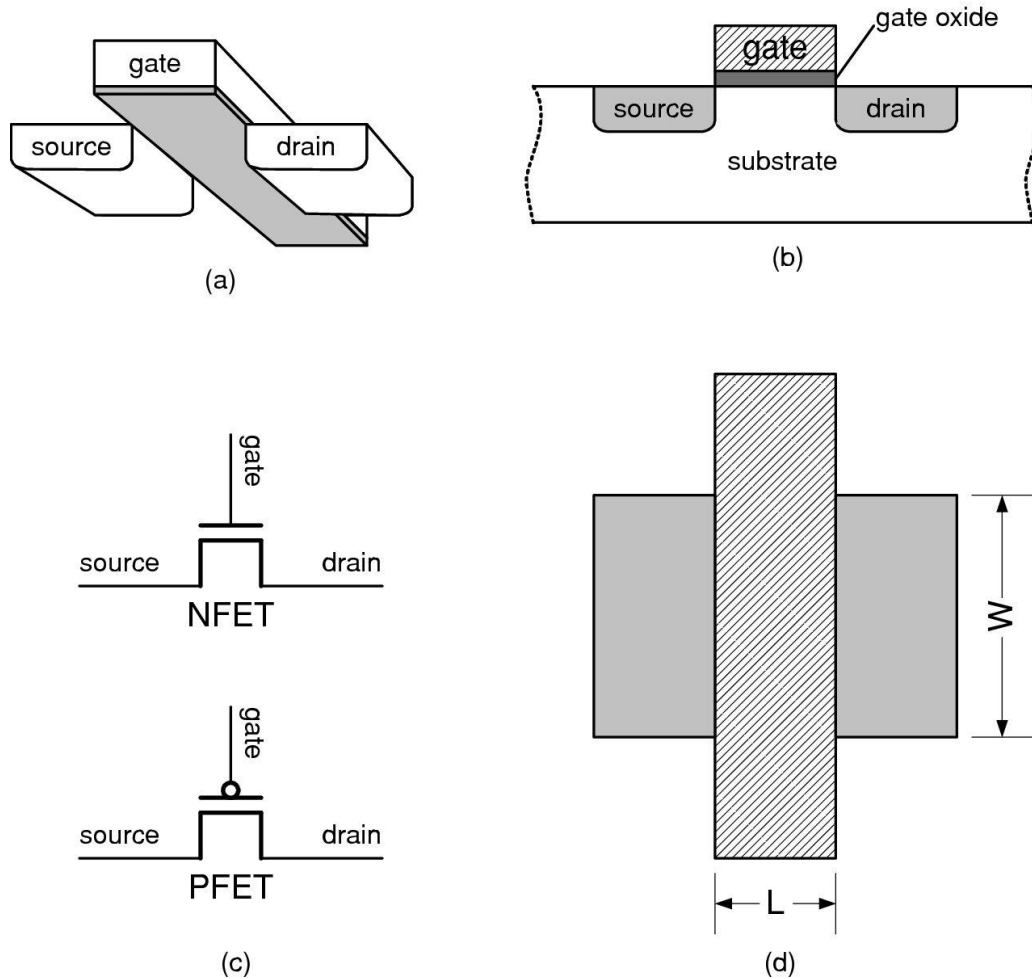


Operation of n-channel MOSFET

   

$$|g = 0$$



(a)

 


$$|g = 1$$





(b)


Operation of p-channel MOSFET

 


$|g = 1$

  


$|g = 0$

 

Electrical Model of PFET and NFET

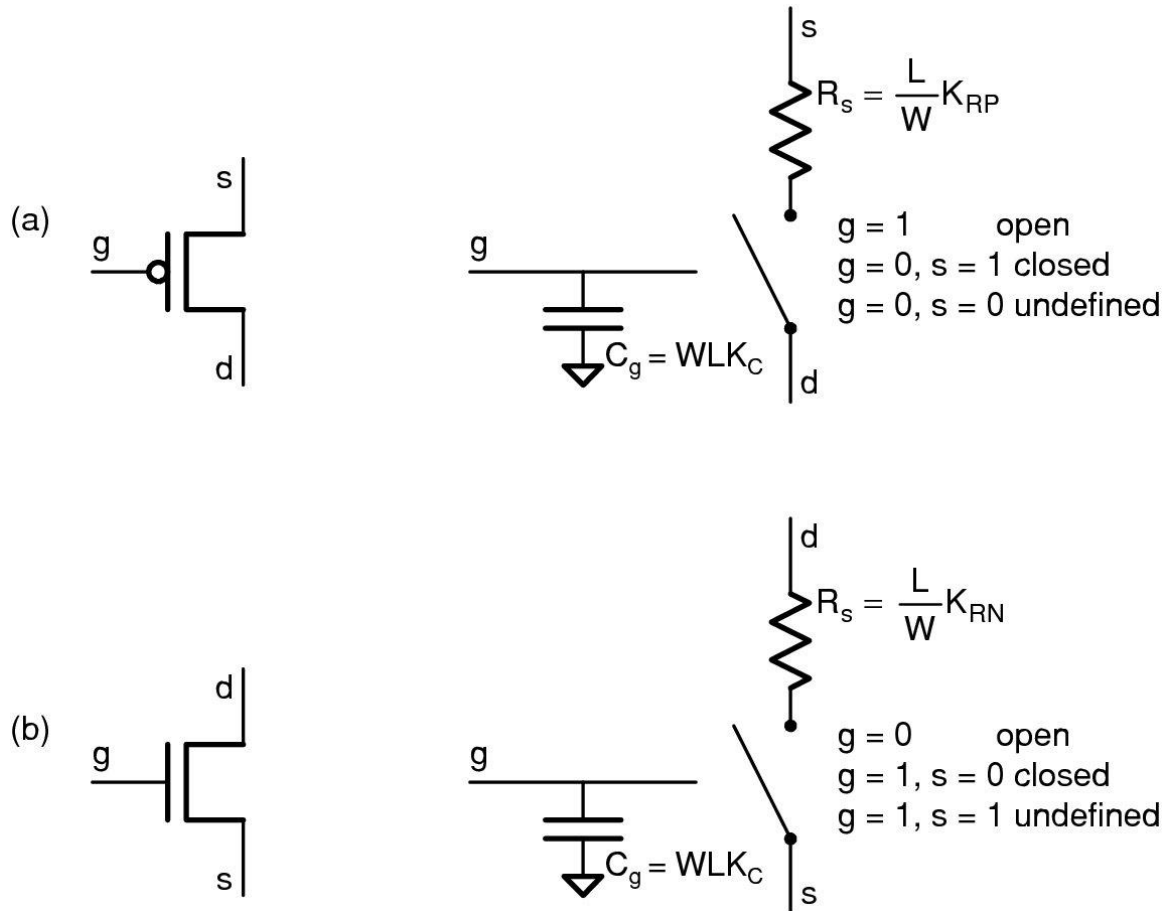

 Output voltage of an inverter as a function of input voltage



Logic circuit → Switches

Switches → MOS transistors

Logic circuit → MOS transistors


Gate with restoring output → static CMOS gate

Summary

- **Switch logic** to drive gate circuits
- **NMOS ad PMOS transistors** act as switches with restrictions
- **NMOS ad PMOS transistors have the parasitic resistance and capacitance, which affect the switching delay.**

CMOS Logic Circuits - Gates

Static CMOS Gate Circuits

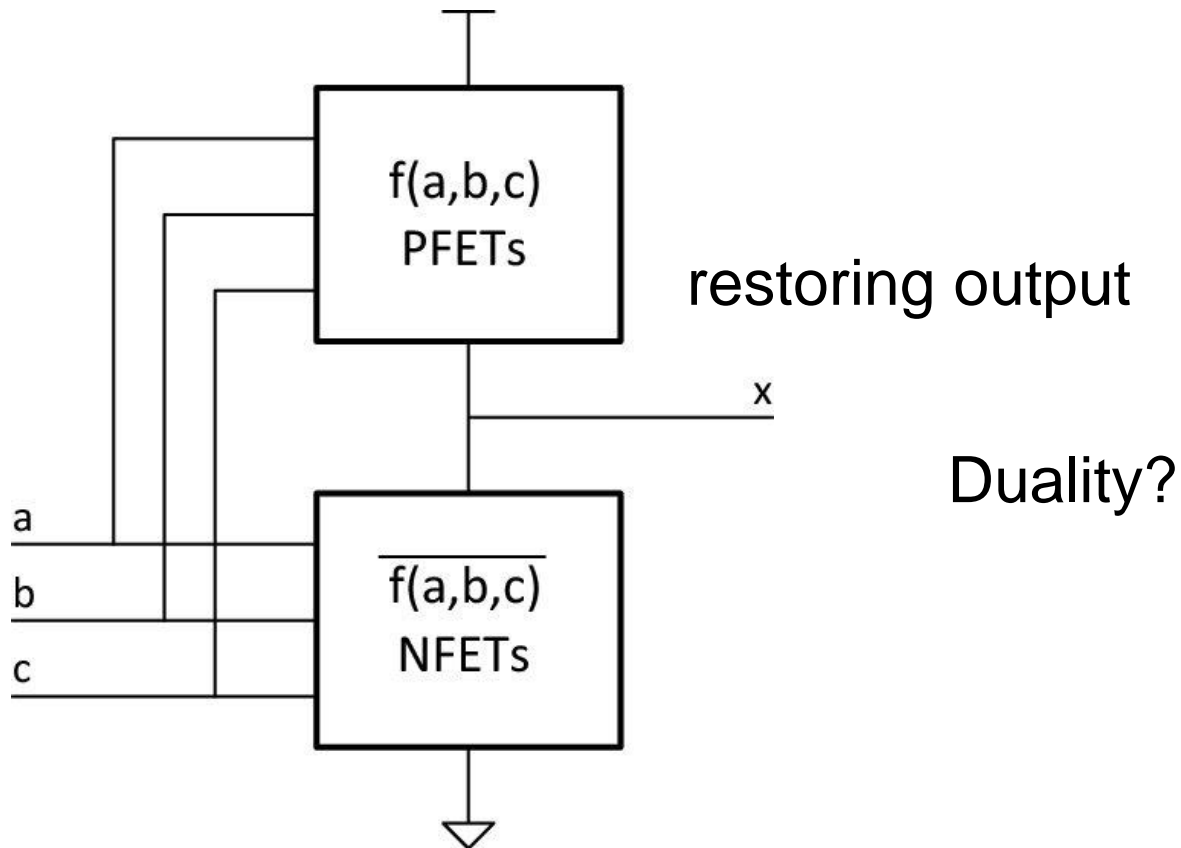


CMOS gate: Monotonic decreasing function

If the transitions on the outputs are in the opposite direction to the transitions on the inputs, it is a ***monotonic decreasing*** or inverting logic function.


If the transitions are in the same direction, it is called a *monotonic increasing* function.

To realize a non-inverting or monotonic increasing logic function requires multiple stages of CMOS gates.

A CMOS Inverter

 


(a)

 


(b)

Bubble rule Where possible, signals that are output from a gate with an inversion bubble on its output shall be input to a gate with an inversion bubble on its input.

 
Switch networks used to realize NAND and NOR gates




(a)

 

(b)


 


(c)


 


(d)

A CMOS NAND

 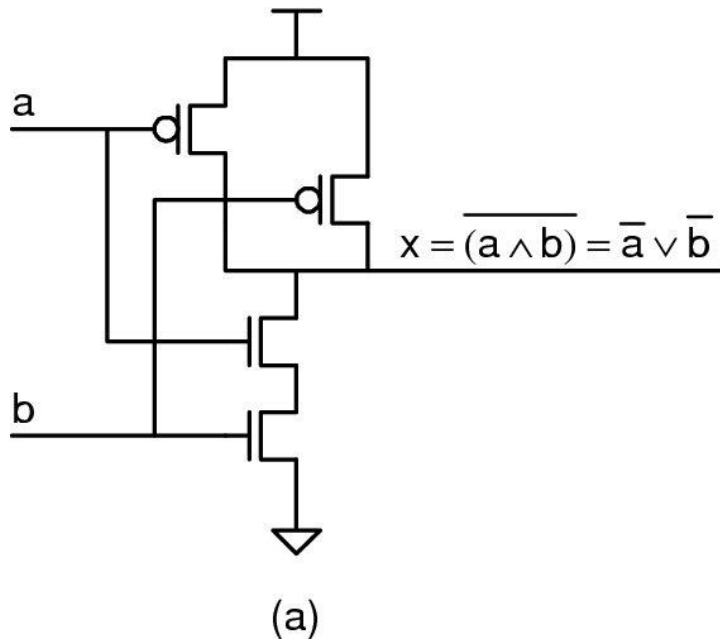


A CMOS NOR

 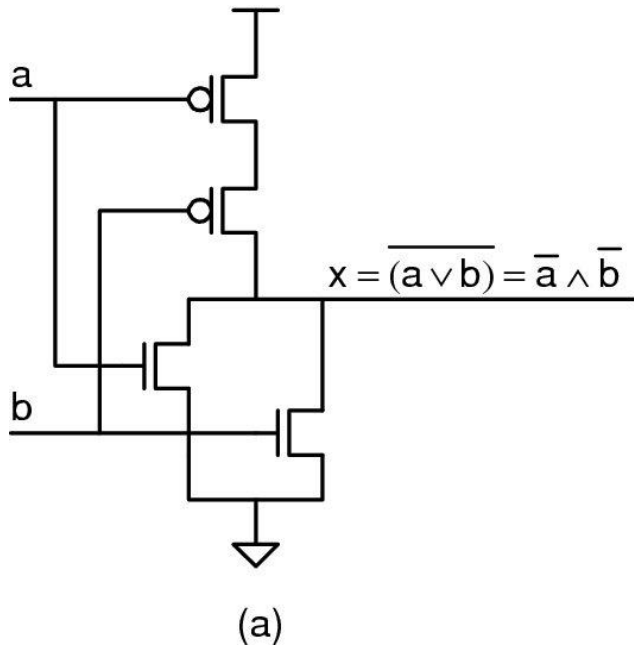


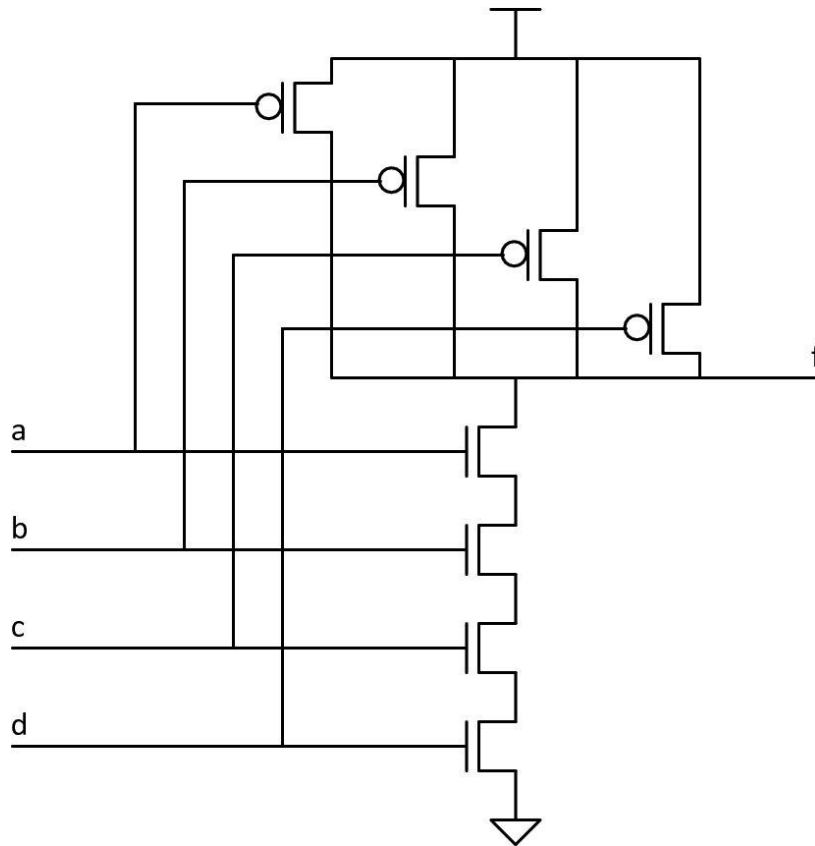
Example: Four-input static CMOS NAND

Draw the transistor-level implementation of a four-input NAND gate

$$f = \overline{a \wedge b \wedge c \wedge d}$$



Complex Gates

 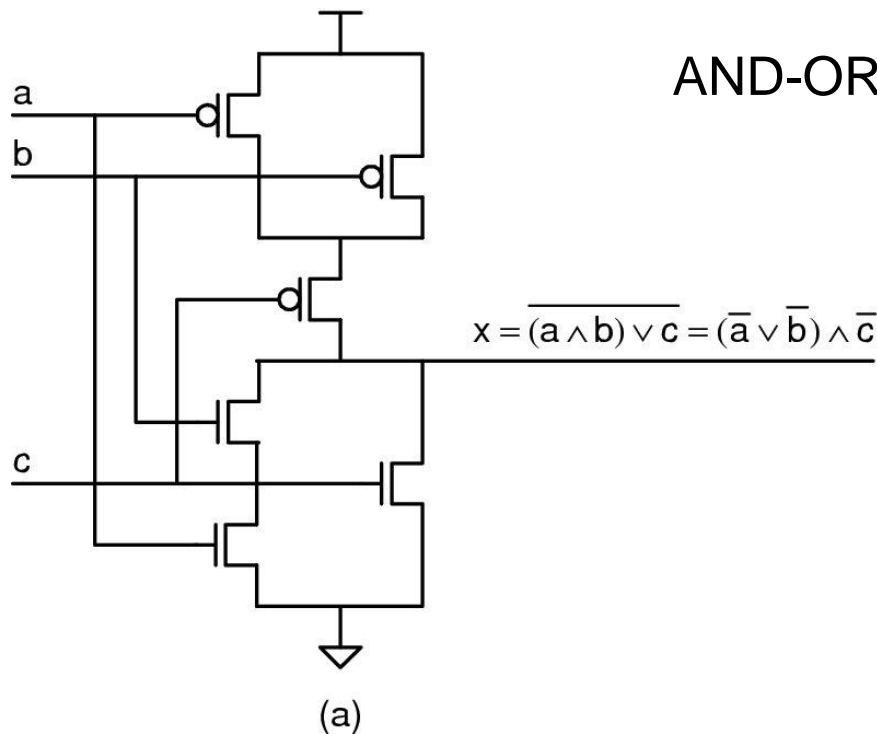

Gates built from arbitrary series-parallel (i.e., not a simple series and parallel) networks or networks that are not series-parallel.

XOR gates

Boolean equation for 2-input XOR gate?


Can we build a single-stage 2-input XOR gate ?

Boolean equation for 3-input XOR gate?

Can we build a single-stage 3-input XOR gate ?

 Example: CMOS gate synthesis

Draw a complex gate for $f = \overline{(\bar{c} \wedge \bar{b}) \vee (b \wedge a)}$






Summary

- CMOS gate circuit to implement a logic function f .
 - Pull-down NFET network to implement for $f = 0$.
 - Pull-up PNET network to implement for $f = 1$.
 - Dual network of NFET network
- Inverters, NANDs, NORs, and Complex gates
- All CMOS gates are *monotonically decreasing*.
- Multiple stages of CMOS gates are required to build increasing or non-inverting functions.

CMOS Logic Circuits – Tri-state


Tri-state circuit

   


Tri-state-inverter Multiplexer using tri-state-inverters

Circuits to avoid

 
These are NOT static gates: do not use these circuits




(a)

 

(b)

 


(c)

 


(d)

(a) Would-be-buffer

 


It attempts to pass 1 through NFET and a 0 through PFET.

(b) No-restoring circuit

 


It does not restore its output. If $b = 0$, a noise in input a is passed directly to the output.

(c) Tri-state circuit

 

When $a = 1$ and $b = 0$, its output is disconnected. Due to parasitic capacitance, the previous output value will be stored for a short period of time on the output node. However, after a period, the stored charge will _____ and the output node becomes _____ value.

(d) Short circuit

 

Both of the pull-up and pull-down network conduct when a and b are not equal. This static current from power to ground outputs _____ value, wasting _____, and potentially _____ the chip.

Summary

- **Tri-state circuits:** Not a CMOS gate, can be in unconnected state